

Chapter 12. Operational Amplifier Circuits


8.6.1 A Two Stage CMOS Op Amp

9.7.2 Analysis of the Current-Mirror-Loaded MOS Amplifier

12.1 The Two Stage CMOS Op Amp

12.2 The Folded Cascode CMOS Op Amp

12.1 The Two Stage CMOS Op Amp

 


12.1.1 The Circuit

- Voltage gain
 - Voltage gain of 1st stage: $A_1 = -g_{m1}(r_{o2} \parallel r_{o4})$
 - Voltage gain of 2nd stage: $A_2 = -g_{m6}(r_{o6} \parallel r_{o7})$
 - DC open-loop gain: $A_v = A_1 \times A_2$
- Input offset voltage
 - *Random offset*: device mismatches as random in nature
 - *Systematic offset*: due to design technique $\Rightarrow$ predictable

$$\Rightarrow \frac{(W/L)_6}{(W/L)_4} = 2 \frac{(W/L)_7}{(W/L)_5} \quad \text{If this condition is not met, a systematic offset will result.}$$

- C_C is Miller-multiplied by the gain of the second stage to provide the required dominant pole.

Bias generation

 

1st stage

2nd stage

12.1.2 Input Common-Mode Range

- To keep Q_1 and Q_2 in saturation.

$$V_{ICM} \geq -V_{SS} + V_{tn} + V_{OV3} - |V_{tp}|$$


- The highest value of V_{ICM} ensures Q_5 in saturation.

$$V_{ICM} \leq V_{DD} - |V_{OV5}| - V_{SG1}$$

$$\Rightarrow V_{ICM} \leq V_{DD} - |V_{OV5}| - |V_{tp}| - |V_{OV1}|$$

$$\Rightarrow -V_{SS} + V_{OV3} + V_{tn} - |V_{tp}| \leq V_{ICM} \leq V_{DD} - |V_{tp}| - |V_{OV1}| - |V_{OV5}|$$

 From the point view of V_{ICM} , select the values of V_{OV} as low as possible!!



Output swing

to keep Q_6 and Q_7 saturated

$$\Rightarrow -V_{SS} + V_{OV6} \leq v_O \leq V_{DD} - |V_{OV7}|$$


Select the values of V_{OV} (of Q_6 and Q_7) as low as possible!!

But $f_T \propto V_{OV}$; the high-frequency performance improved with the higher overdrive voltage.

- A substantial allowable range of V_{ICM} and v_O needed for an unity-gain application.

 12.1.3 Voltage Gain

Simplified small-signal equivalent circuit



- $R_{in} = \infty$
- $G_{m1} = g_{m1} = g_{m2} \Rightarrow G_{m1} = \frac{2(I/2)}{V_{OV1}} = \frac{I}{V_{OV1}}$
- $R_1 = r_{o2} \parallel r_{o4} \quad r_{o2} = \frac{|V_{A2}|}{I/2} \quad r_{o4} = \frac{V_{A4}}{I/2}$
- Dc gain of 1st stage

$$A_1 = -G_{m1}R_1 = -g_{m1}(r_{o2} \parallel r_{o4}) = -\frac{2}{V_{OV1} \left(\frac{1}{|V_{A2}|} + \frac{1}{V_{A4}} \right)}$$

A_1 is increased by

- ❶ Q_1 and Q_2 with a low overdrive
- ❷ Choosing a longer channel length to obtain larger Early voltage, $|V_A|$.

Both, however, degrade the frequency response of the amplifier.

- $G_{m2} = g_{m6} = \frac{2I_{D6}}{V_{OV6}}$
- $R_2 = r_{o6} \parallel r_{o7} \quad r_{o6} = \frac{V_{A6}}{I_{D6}} \quad r_{o7} = \frac{|V_{A7}|}{I_{D7}} = \frac{|V_{A7}|}{I_{D6}}$
- Dc gain of 2nd stage
$$A_2 = -G_{m2}R_2 = -g_{m6}(r_{o6} \parallel r_{o7}) = -\frac{2}{V_{OV6} \left(\frac{1}{V_{A6}} + \frac{1}{|V_{A7}|} \right)}$$
- Overall dc gain
$$A_v = A_1 A_2 = G_{m1} R_1 G_{m2} R_2 = g_{m1}(r_{o2} \parallel r_{o4}) g_{m6}(r_{o6} \parallel r_{o7})$$


Generally, 500 ~5000 V/V of $A_{v,\max}$.
- Output resistance $R_o = r_{o6} \parallel r_{o7}$

12.1.4 Common-Mode Rejection Ratio (CMRR)

Section 8.5.5; eq. (8.158)

$$CMRR = \frac{|A_d|}{|A_{cm}|} = [g_m(r_{o2} // r_{o4})][2g_{m3}R_{SS}]$$

Q_5 's output resistance R_{SS}

 


$$CMRR \propto (g_m r_o)^2$$

$$g_m r_o \propto \frac{V_A}{V_{OV}} = \frac{V'_A \cdot L}{V_{OV}}$$

$$\therefore L \uparrow \Rightarrow CMRR \uparrow$$

12.1.5 Frequency Response

 


$$C_1 = C_{gd2} + C_{db2} + C_{gd4} + C_{db4} + C_{gs6}$$

$$C_2 = C_{db6} + C_{db7} + C_{gd7} + C_L$$

$$C_C \gg C_{gd6} \rightarrow C_{gd6} \text{ is neglected}$$

$$R_1 = r_{o2} \parallel r_{o4}$$

$$R_2 = r_{o6} \parallel r_{o7}$$

 

$$G_{m1} V_{id} + \frac{V_{i2}}{R_1} + sC_1 V_{i2} + sC_C (V_{i2} - V_o) = 0$$

$$G_{m2} V_{i2} + \frac{V_o}{R_2} + sC_2 V_o + sC_C (V_o - V_{i2}) = 0$$

$$\frac{V_o}{V_{id}} = \frac{G_{m1} (G_{m2} - sC_C) R_1 R_2}{1 + s[C_1 R_1 + C_2 R_2 + C_C (G_{m2} R_1 R_2 + R_1 + R_2)] + s^2 [C_1 C_2 + C_C (C_1 + C_2)] R_1 R_2}$$

$$S_Z = \frac{G_{m2}}{C_C} \Rightarrow \omega_Z = \frac{G_{m2}}{C_C}$$

$$D(s) = (1 + \frac{s}{\omega_{P1}})(1 + \frac{s}{\omega_{P2}}) = 1 + s(\frac{1}{\omega_{P1}} + \frac{1}{\omega_{P2}}) + \frac{s^2}{\omega_{P1}\omega_{P2}}$$

$$\omega_{P1} \ll \omega_{P2} \Rightarrow D(s) \approx 1 + \frac{s}{\omega_{P1}} + \frac{s^2}{\omega_{P1}\omega_{P2}}$$

$$\omega_{P1} = \frac{1}{C_1 R_1 + C_2 R_2 + C_C (G_{m2} R_1 R_2 + R_1 + R_2)} \quad \omega_{P2} = \frac{C_C G_{m2}}{C_1 C_2 + C_C (C_1 + C_2)}$$



$$\because C_C \gg C_1, C_2 \gg C_1, G_{m2} R_2 \gg 1 \Rightarrow \omega_{P1} \approx \frac{1}{C_C G_{m2} R_1 R_2}, \quad \omega_{P2} \approx \frac{G_{m2}}{C_2}$$

$$\omega_t = A_M \omega_{P1} = G_{m1} G_{m2} R_1 R_2 \frac{1}{C_C G_{m2} R_1 R_2} = \frac{G_{m1}}{C_C}$$

$$\omega_t \ll \omega_{P2}, \omega_Z \Rightarrow \frac{G_{m1}}{C_C} < \frac{G_{m2}}{C_2} \text{ and } G_{m1} < G_{m2}$$

When $f \gg f_{p1}$, a uniform -20dB/decade gain rolloff down to 0dB

→ Simplified Equivalent Circuit

  

Phase margin

$$A(s) = \frac{A_o(1 - s / \omega_Z)}{(1 + s / \omega_{P1})(1 + s / \omega_{P2})}$$

$$\omega = \omega_t$$

$$\phi_{P1} = -\tan^{-1}\left(\frac{f_t}{f_{P1}}\right) \approx -90^\circ$$

$$\phi_{P2} = -\tan^{-1}\left(\frac{f_t}{f_{P2}}\right)$$

$$\phi_Z = -\tan^{-1}\left(\frac{f_t}{f_Z}\right)$$


$$\phi_{\text{total}} = 90^\circ + \tan^{-1}(f_t / f_{P2}) + \tan^{-1}(f_t / f_Z)$$

$$\text{Phase Margin(PM)} = 180^\circ - \phi_{\text{total}}$$


$$= 90^\circ - \tan^{-1}(f_t / f_{P2}) - \tan^{-1}(f_t / f_Z)$$

$$\text{If } f_Z \geq 10 f_t, \text{PM} = 60^\circ \Rightarrow 60^\circ = 90^\circ - \tan^{-1}(f_t / f_{P2}) - 5.71^\circ$$

$$\Rightarrow f_{P2} / f_t \approx 2.2$$

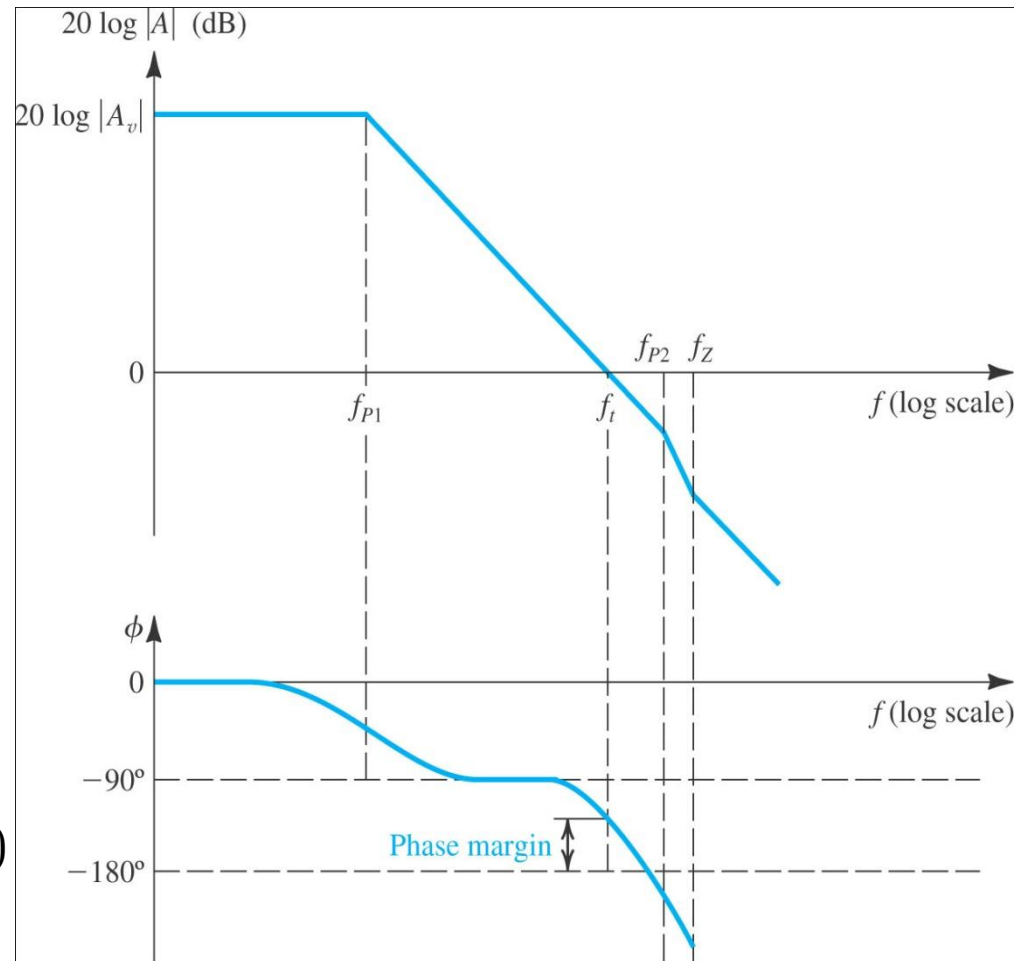

 The right-half-plane zero reduces the phase margin.
How to improve it?



- Find zero: $V_o=0$

$$\frac{V_{i2}}{R + 1/sC_C} = G_{m2}V_{i2} \Rightarrow s_z = \frac{1}{C_C(1/G_{m2} - R)}$$


- $R = 1/G_{m2}$, the zero can be placed at infinite frequency.
 - $R > 1/G_{m2}$, a left-half plane zero improves the phase margin.
- Discussion: The second pole is not very far from ω_t . Thus the second pole introduces appreciable phase shift at ω_t , which reduces the phase margin.

12.1.6 Slew Rate

- When a large output signal is present, slew-rate limiting can cause nonlinear distortion.
- Slew rate: the maximum rate of change possible at the output of a real op amp.

$$SR = \left. \frac{dv_o}{dt} \right|_{\max}$$

 - A unity-gain follower with a large step input.
(the output voltage cannot change immediately.)



Relationship Between SR and f_t

Slew rate

$$SR = \frac{I}{C_C}$$

$$G_{m1} = g_{m1} = \frac{I}{V_{OV1}}$$

$$\omega_t = \frac{G_{m1}}{C_C}$$

$$\Rightarrow SR = V_{OV1} \omega_t$$



- For a given ω_t , the slew rate is determined by the overdrive voltage at which the input transistor are operated.
- $V_{OV} \uparrow \Rightarrow SR \uparrow$.
 - ❶ For a given bias current I , a large V_{OV} is obtained if Q_1 and Q_2 are p -channel devices. (1st stage)
 - ❷ It allows the 2nd stage to employ an n -channel device that has a greater transconductance, G_{m2} , resulting in a higher second-pole frequency and a corresponding higher ω_t .

12.1.7 Power-Supply Rejection Ratio (PSRR)


PSRR is defined as the ratio of the amplifier differential gain to the gain experienced by a change in the power-supply voltage (v_{dd} and v_{ss})

$$PSRR^+ = \frac{A_d}{A^+} \text{ and } PSRR^- = \frac{A_d}{A^-}$$
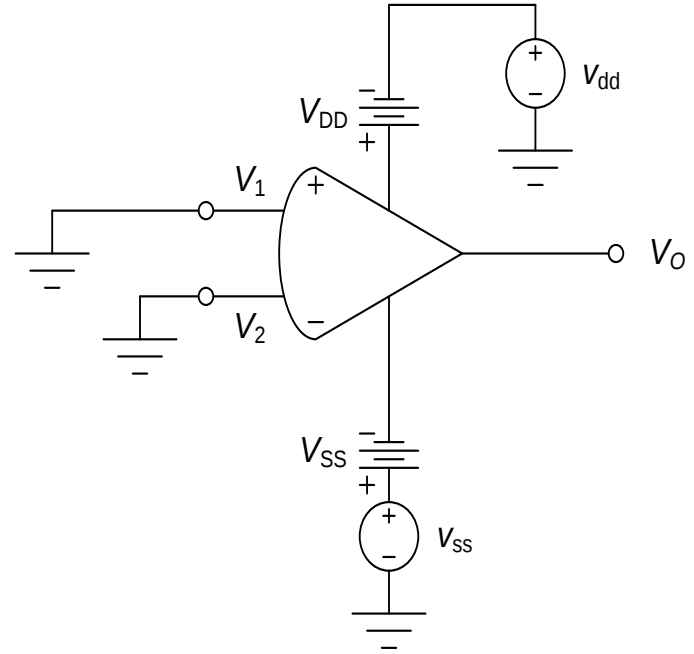 
$$A^+ = \frac{V_o}{V_{dd}} \quad \text{and} \quad A^- = \frac{V_o}{V_{ss}}$$



 $PSRR^+$ is high
since Q_5 and Q_7 are current sources



$$PSRR^-$$

$$v_o = v_{ss} \frac{r_{o7}}{r_{o6} + r_{o7}}$$

$$A^- = \frac{v_o}{v_{ss}} = \frac{r_{o7}}{r_{o6} + r_{o7}}$$

$$PSRR^- = \frac{A_d}{A^-} = g_{m1}(r_{o2} // r_{o4})g_{m6}r_{o6}$$

$$PSRR^- \propto (g_m r_o)^2$$

$$g_m r_o \propto \frac{V_A}{V_{OV}} = \frac{V_A' \cdot L}{V_{OV}}$$

$$\therefore L \uparrow \Rightarrow PSRR^- \uparrow$$

12.1.8 Design Tradeoffs

1. The length L used for each MOSFET
2. Overdrive voltage $|V_{OV}|$ for each MOSFET

$$CMRR \propto (g_m r_o)^2$$

$$g_m r_o \propto \frac{V_A}{V_{OV}} = \frac{V_A' \cdot L}{V_{OV}}$$

$$\therefore L \uparrow \Rightarrow CMRR \uparrow$$

$$PSRR^- \propto (g_m r_o)^2$$

$$g_m r_o \propto \frac{V_A}{V_{OV}} = \frac{V_A' \cdot L}{V_{OV}}$$

$$\therefore L \uparrow \Rightarrow PSRR^- \uparrow$$


$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV}$$

$$C_{gs} \approx \frac{2}{3} W L C_{ox}$$

transition frequency

$$f_T = \frac{\omega_T}{2\pi} = \frac{g_m}{2\pi(C_{gs} + C_{gd})} \approx \frac{1.5\mu_n V_{OV}}{2\pi L^2}$$

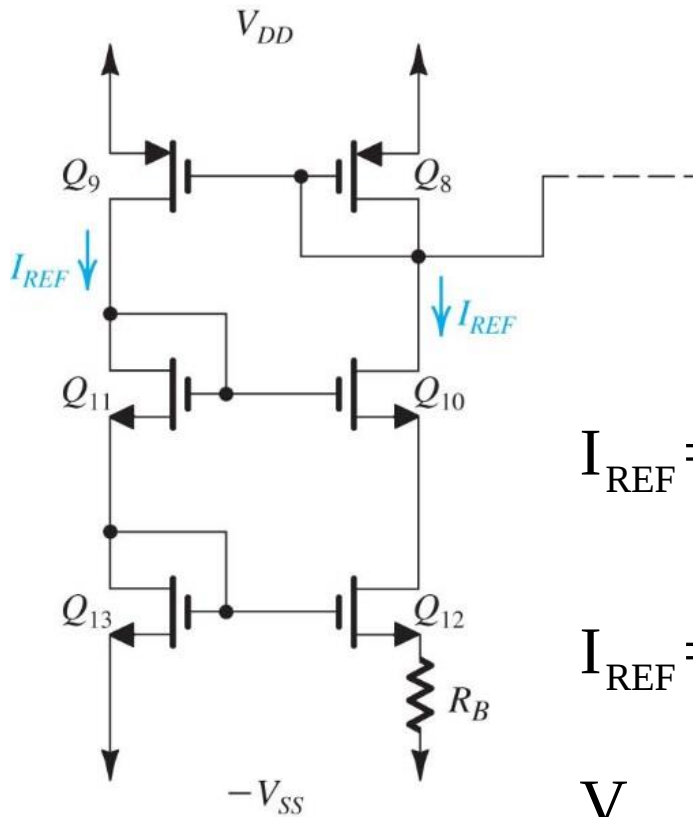12.1.9 A Bias Circuit for the Two-Stage CMOS Op Amp



1. All devices are in the saturation region
2. Q8 and Q9, Q10 and Q11 matched
3. Q12 and Q13 not matched
4. Positive feedback; $R_B \downarrow \Rightarrow I_{D13} \uparrow \Rightarrow V_{G13} \uparrow$
5. Need a kick-off circuit

$$I_{REF} = \frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_{12} (V_{GS12} - V_t)^2$$

$$I_{REF} = \frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_{13} (V_{GS13} - V_t)^2$$

$$V_{GS13} = V_{GS12} + I_{REF} R_B \Rightarrow$$

$$\sqrt{\frac{2I_{REF}}{\mu_n C_{OX} (W/L)_{13}}} = \sqrt{\frac{2I_{REF}}{\mu_n C_{OX} (W/L)_{12}}} + I_{REF} R_B$$

$$I_{\text{REF}} = \frac{2}{\mu_n C_{\text{OX}} (W/L)_{12} R_B^2} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)^2$$

$$R_B = \frac{2}{\sqrt{2\mu_n C_{\text{OX}} (W/L)_{12} I_{\text{REF}}}} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$= \frac{2}{g_{m12}} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$\Rightarrow g_{m12} = \frac{2}{R_B} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$\therefore g_{m12} = \sqrt{2\mu_n C_{\text{OX}} (W/L)_{12} I_{\text{REF}}}$$

for each n-channel transistor in this bias circuit

$$\frac{g_{mi}}{g_{m12}} = \sqrt{\frac{(W/L)_i I_{Di}}{(W/L)_{12} I_{\text{REF}}}}$$


for each p-channel transistor in this bias circuit

$$\frac{g_{mi}}{g_{m12}} = \sqrt{\frac{\mu_p (W/L)_i I_{Di}}{\mu_n (W/L)_{12} I_{\text{REF}}}}$$

Ex.12.1 Two-Stage CMOS Op Amp Design

Design a dc gain of 4000 V/V in a 0.5- μm CMOS technology. $V_{tn} = |V_{tp}| = 0.5\text{V}$, $k'_n = 200 \mu\text{A}/\text{V}^2$, $k'_p = 80 \mu\text{A}/\text{V}^2$, $V'_{An} = |V'_{Ap}| = 20\text{V}/\mu\text{m}$, $V_{DD} = V_{SS} = 1.65\text{V}$, $L = 1\mu\text{m}$ for all devices. Let $I = 200\mu\text{A}$, $I_{D6} = 0.5\text{mA}$. If $C_1 = 0.2\text{pF}$ and $C_2 = 0.8\text{pF}$, find the required C_C and R to place the transmission zero at $s = \infty$ for phase margin of 85° .

Solution

 

- Voltage gain $A_v = g_{m1}(r_{o2} \parallel r_{o4})g_{m6}(r_{o6} \parallel r_{o7}) = \frac{2(I/2)}{V_{OV}} \cdot \frac{1}{2} \cdot \frac{V_A}{(I/2)} \cdot \frac{2I_{D6}}{V_{OV}} \cdot \frac{1}{2} \cdot \frac{V_A}{I_{D6}} = \left(\frac{V_A}{V_{OV}} \right)^2$

$$A_v = 4000 \text{ and } V_A = 20\text{V} \Rightarrow 4000 = \frac{400}{V_{OV}^2} \Rightarrow V_{OV} = 0.316\text{V}$$

- $(W/L)_1$ and $(W/L)_2$:

$$I_{D1} = \frac{1}{2} k'_p \left(\frac{W}{L} \right)_1 v_{OV}^2 \Rightarrow 100 = \frac{1}{2} \cdot 80 \left(\frac{W}{L} \right)_1 \cdot 0.316^2 \Rightarrow \left(\frac{W}{L} \right)_1 = \frac{25\mu\text{m}}{1\mu\text{m}} = \left(\frac{W}{L} \right)_2$$

- $(W/L)_3$ and $(W/L)_4$:

$$I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L} \right)_3 v_{OV}^2 \Rightarrow 100 = \frac{1}{2} \cdot 200 \left(\frac{W}{L} \right)_3 \cdot 0.316^2 \Rightarrow \left(\frac{W}{L} \right)_3 = \frac{10 \mu m}{1 \mu m} = \left(\frac{W}{L} \right)_4$$

- $(W/L)_5$:

$$I_{D5} = \frac{1}{2} k_p' \left(\frac{W}{L} \right)_5 v_{OV}^2 \Rightarrow 200 = \frac{1}{2} \cdot 80 \left(\frac{W}{L} \right)_5 \cdot 0.316^2 \Rightarrow \left(\frac{W}{L} \right)_5 = \frac{50 \mu m}{1 \mu m}$$

- $(W/L)_6$ and $(W/L)_7$:

$$\left(\frac{W}{L} \right)_7 = 2.5 \left(\frac{W}{L} \right)_5 = \frac{125 \mu m}{1 \mu m} \quad 500 = \frac{1}{2} \cdot 200 \left(\frac{W}{L} \right)_6 \cdot 0.316^2 \Rightarrow \left(\frac{W}{L} \right)_6 = \frac{50 \mu m}{1 \mu m}$$

- Select $I_{REF} = 20 \mu A$, thus $\left(\frac{W}{L} \right)_8 = 0.1 \left(\frac{W}{L} \right)_5 = \frac{5 \mu m}{1 \mu m}$

- Input CM range: $-1.33 \text{ V} \leq V_{ICM} \leq 0.52 \text{ V}$

$$(-V_{SS} + V_{OV3} + V_{tn} - |V_{tp}| \leq V_{ICM} \leq V_{DD} - |V_{tp}| - |V_{OV1}| - |V_{OV5}|)$$

- Max. signal swing: $-1.33 \text{ V} \leq v_o \leq 1.33 \text{ V}$
- Input resistance: $R_i = \infty$
- Output resistance: $R_o = r_{o6} \parallel r_{o7} = 20 \text{ k}\Omega$

$$CMRR = [g_m(r_{o2} // r_{o4})][2g_{m3}R_{SS}]$$

- $R_{SS} = r_{o5} = V_A / I$

$$\begin{aligned} CMRR &= \frac{2(I/2)}{V_{OV}} \cdot \frac{1}{2} \cdot \frac{V_A}{(I/2)} \cdot 2 \cdot \frac{2(I/2)}{V_{OV}} \cdot \frac{V_A}{I} \\ &= 2\left(\frac{V_A}{V_{OV}}\right)^2 = 2\left(\frac{20}{0.316}\right)^2 = 8000 \end{aligned}$$

$$CMRR = 20 \log(8000) = 78 \text{dB}$$

- $PSRR^- = g_{m1}(r_{o2} // r_{o4})g_{m6}r_{o6}$

$$= \frac{2(I/2)}{V_{OV}} \cdot \left(\frac{1}{2} \cdot \frac{V_A}{(I/2)}\right) \cdot \frac{2I_{D6}}{V_{OV}} \cdot \frac{V_A}{I_{D6}}$$

$$= 2\left(\frac{V_A}{V_{OV}}\right)^2 = 2\left(\frac{20}{0.316}\right)^2 = 8000$$

$$PSRR^- = 20 \log(8000) = 78 \text{dB}$$

• Determine f_{p2} :

$$G_{m2} = g_{m6} = \frac{2I_{D6}}{V_{OV}} = \frac{2 \times 0.5}{0.316} = 3.2 \text{mA/V} \quad f_{p2} \approx \frac{G_{m2}}{2\pi C_2} = \frac{3.2 \times 10^{-3}}{2\pi \cdot 0.8 \times 10^{-12}} = 637 \text{MHz}$$

- To move the transmission zero to $s = \infty$, we select the value of R as

$$R = \frac{1}{G_{m2}} = \frac{1}{3.2 \times 10^{-3}} = 316\Omega$$

- For a phase margin of 85° , the phase shift due to f_{p2} at $f = f_t$ must be 5° , that is

$$\tan^{-1} \frac{f_t}{f_{p2}} = 5^\circ$$

$$\Rightarrow f_t = 637 \times \tan 5^\circ = 55.7 \text{ MHz}$$

- Determine C_C :


$$C_C = \frac{G_{m1}}{2\pi f_t} \quad \text{where} \quad G_{m1} = g_{m1} = \frac{2 \cdot 100 \mu A}{0.316 V} = 0.63 \text{ mA} / V$$


$$\therefore C_C = \frac{0.6 \times 10^{-3}}{2\pi \cdot 55.7 \times 10^6} = 1.8 \text{ pF}$$

- Slew rate: [Eq. (12.46)]

$$SR = 2\pi f_t V_{OV} = 2\pi \cdot 55.7 \times 10^6 \times 0.316 = 111 \text{ V} / \mu s$$

12.2 The Folded Cascode CMOS Op Amp

 

 

- Input common-mode range:

$$V_{ICM \max} = V_{DD} - |V_{OV9}| + V_{tn}$$

$$V_{ICM \min} = -V_{SS} + V_{OV11} + V_{OV1} + V_{tn}$$

$$-V_{SS} + V_{OV11} + V_{OV1} + V_{tn} \leq V_{ICM} \leq V_{DD} - |V_{OV9}| + V_{tn}$$

Output voltage swing:

Select V_{BIAS1} so that Q_{10} operates at the edge of saturation:

$$V_{BIAS1} = V_{DD} - |V_{OV10}| - V_{SG4}$$


$$\Rightarrow v_{o \max} = V_{DD} - |V_{OV10}| - |V_{OV4}|$$

$v_{o, \min}$ is obtained when Q_6 reaches the edge of saturation.

$$v_{o \min} = -V_{SS} + V_{OV7} + V_{OV5} + V_{tn}$$

- Voltage gain

Small-signal equivalent circuit:

 

- Transconductance

$$G_m = g_{m1} = g_{m2} \quad G_m = \frac{2(I/2)}{V_{OV1}} = \frac{I}{V_{OV1}}$$

- Output resistance


$$R_o = R_{o4} \parallel R_{o6} \quad R_{o4} \approx (g_{m4} r_{o4})(r_{o2} \parallel r_{o10}) \quad R_{o6} \approx g_{m6} r_{o6} r_{o8}$$

$$\Rightarrow R_o = [g_{m4} r_{o4} (r_{o2} \parallel r_{o10})] \parallel (g_{m6} r_{o6} r_{o8})$$

- Open-loop gain

$$A_v = G_m R_o = g_{m1} \{ [g_{m4} r_{o4} (r_{o2} \parallel r_{o10})] \parallel (g_{m6} r_{o6} r_{o8}) \}$$

- Unity-gain buffer (voltage follower):

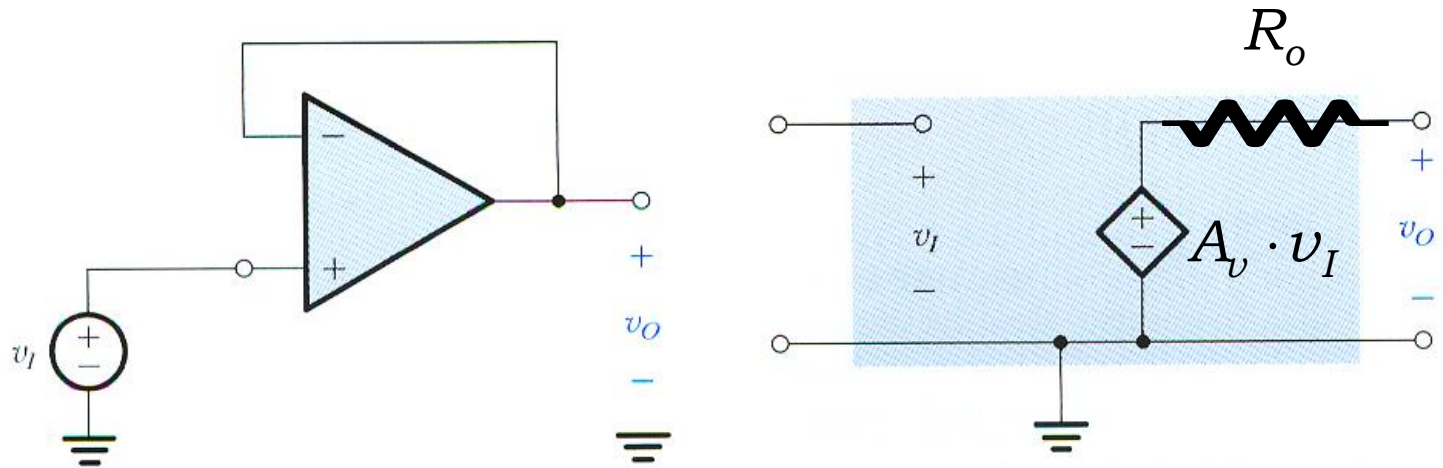

- Output resistance

$$R_{of} = \frac{R_o}{1 + A_v} \approx \frac{R_o}{A_v} = \frac{R_o}{G_m R_o} = \frac{1}{G_m} = \frac{1}{g_{m1}}$$

- It is not very small for a single-stage op amp (OTA, operational transconductance amplifier).
- An ideal op amp has an zero output resistance!

- Frequency response:

Since the primary purpose of CMOS op amps is to feed capacitive loads, C_L is usually large, and the pole at the output becomes dominant.

- Transfer function
$$\frac{V_o}{V_{id}} = \frac{G_m R_o}{1 + sC_L R_o}$$

- Dominant pole
$$f_p = \frac{1}{2\pi C_L R_o}$$


- Unity-gain frequency

$$f_t = A_v f_p = G_m R_o f_p = \frac{G_m}{2\pi C_L}$$


- Discussion

Folded-cascode op amp: $C_L \uparrow \Rightarrow f_{p1}, f_t \downarrow \Rightarrow$ phase margin $\uparrow$

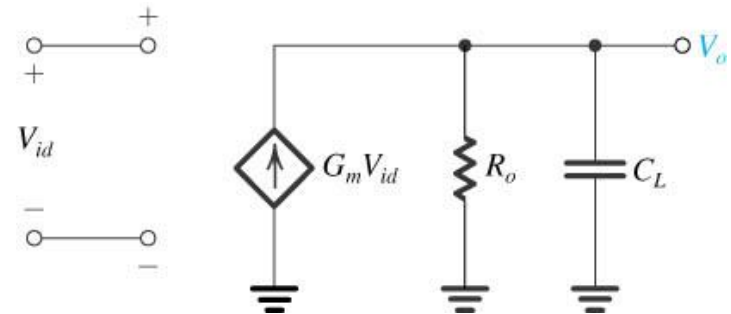
Two-stage op amp: $C_L \uparrow \Rightarrow f_{p2} \downarrow \Rightarrow$ phase margin $\downarrow$



 - Slew Rate: a large differential input signal is applied. ($I_B > I$)



- Slew Rate: a large differential input signal is applied. ($0.5I < I_B < I$)

 

Ex 12.2: Design of a folded-cascode op amp.

$I = 240\mu\text{A}$, $I_B = 150\mu\text{A}$, and $|V_{OV}| = 0.25\text{V}$ for all transistors. $V_{DD} = V_{SS} = 2.5\text{V}$
 $K_n' = 100\mu\text{A}/\text{V}^2$, $K_p' = 40\mu\text{A}/\text{V}^2$, $|V_A'| = 20\text{V}/\mu\text{m}$ and $|V_t| = 0.75\text{V}$. $L = 1\mu\text{m}$,
 $C_L = 5\text{pF}$.

- Find I_D , g_m , r_o and W/L for all transistors.

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2I_D}{0.25}$$


$$r_o = \frac{|V_A|}{I_D} = \frac{20}{I_D}$$

$$\left(\frac{W}{L}\right)_i = \frac{2I_{Di}}{k'V_{OV}^2}$$

Note: for all transistors

$$g_m r_o = 160 \text{ V/V}$$

$$V_{GS} = 1.0 \text{ V}$$

 

	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9	Q_{10}	Q_{11}
I_D (μA)	120	120	30	30	30	30	30	30	150	150	240
g_m (mA/V)	0.96	0.96	0.24	0.24	0.24	0.24	0.24	0.24	1.2	1.2	1.92
r_o (k Ω)	167	167	667	667	667	667	667	667	133	133	83
W/L	38.4	38.4	24	24	9.6	9.6	9.6	9.6	120	120	76.8

- Find the allowable range of V_{ICM} and of the output voltage swing.

$$-1.25V \leq v_o \leq 2V$$

$$-1.25V \leq V_{ICM} \leq 3V$$

$$-V_{SS} + V_{OV11} + V_{OV1} + V_{tn} \leq V_{ICM} \leq V_{DD} - |V_{OV9}| + V_{tn}$$

$$\begin{aligned} v_{o\max} &= V_{DD} - |V_{OV10}| - |V_{OV4}| \\ v_{o\min} &= -V_{SS} + V_{OV7} + V_{OV5} + V_{tn} \end{aligned}$$

- Determine the values of A_v , f_t , f_p , and SR .

$$R_{o4} = (g_{m4}r_{o4})(r_{o2} \parallel r_{o10}) = 160(167 \parallel 133) = 11.85M\Omega \quad R_{o6} = g_{m6}r_{o6}r_{o8} = 106.7M\Omega$$

$$R_o = R_{o4} \parallel R_{o6} = 10.7M\Omega$$

$$A_v = G_m R_o = 0.96 \times 10^{-3} \cdot 10.7 \times 10^6 = 10240V/V$$

$$f_t = \frac{G_m}{2\pi C_L} = \frac{0.96 \times 10^{-3}}{2\pi \cdot 5 \times 10^{-12}} = 30.6MHz$$


$$f_p = \frac{f_t}{A_v} \left(\text{or } = \frac{1}{2\pi C_L R_o} \right) = \frac{30.6MHz}{10240} = 3kHz$$

$$SR = \frac{I_B}{C_L} = \frac{150 \times 10^{-6}}{5 \times 10^{-12}} = 30V/\mu s$$

- What is the power dissipation of the op amp?


$$P_D = 5V \times 0.3mA = 1.5mW$$

 12.2.6 Increasing the Input Common-Mode Range: Rail-to-Rail Input Operation




Over the remainder of the input CM range, only one of two differential pairs will be operational, and the gain drops to half.

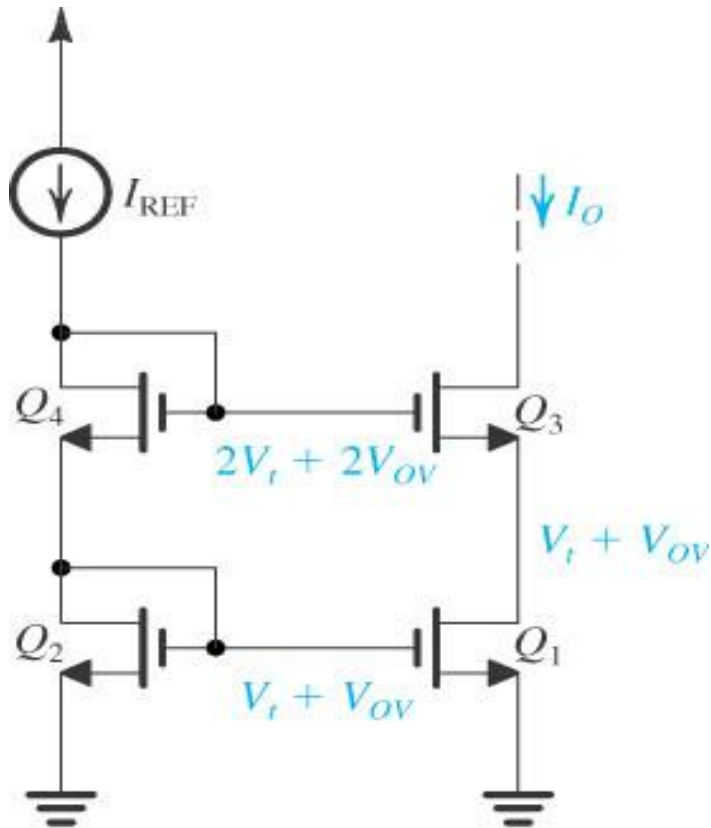12.2.7 Wide-Swing Current Mirror (Increasing the Output Voltage Range)



(a)

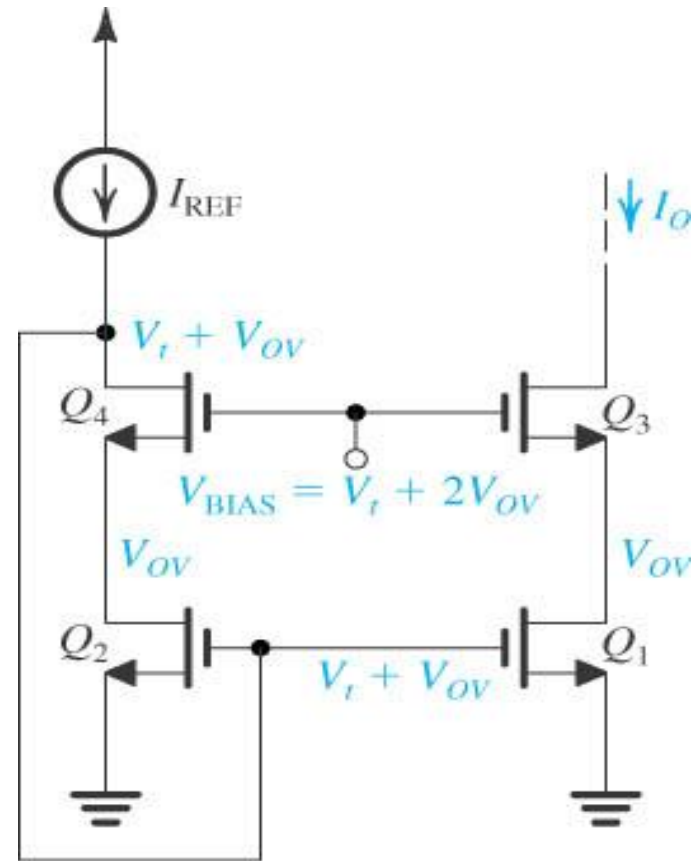

(b)

For Q_4 in saturation, $V_{ds} > V_{gs} - V_t$
 $V_{ds} = V_t$, $V_{gs} - V_t = V_{ov}$
 $\rightarrow V_t > V_{ov}$