 


CHAPTER 15 CMOS Digital Logic Circuits

15.1 CMOS Logic-Gate Circuits

15.1.1 Switch-Level Transistor Model



$$V_G = V_{DD} \\ (G = 1)$$

(a)


$$V_G = 0 \\ (G = 0)$$

Gate voltage = $V_{DD} \rightarrow$ Logic "1"
Gate voltage = 0 \rightarrow Logic "0"

Logic "1" at G



NMOS on and PMOS off

 

$$V_G = V_{DD} \\ (G = 1)$$

(b)


$$V_G = 0 \\ (G = 0)$$

Logic "0" at G



NMOS off and PMOS on

15.1.2 The CMOS Inverter

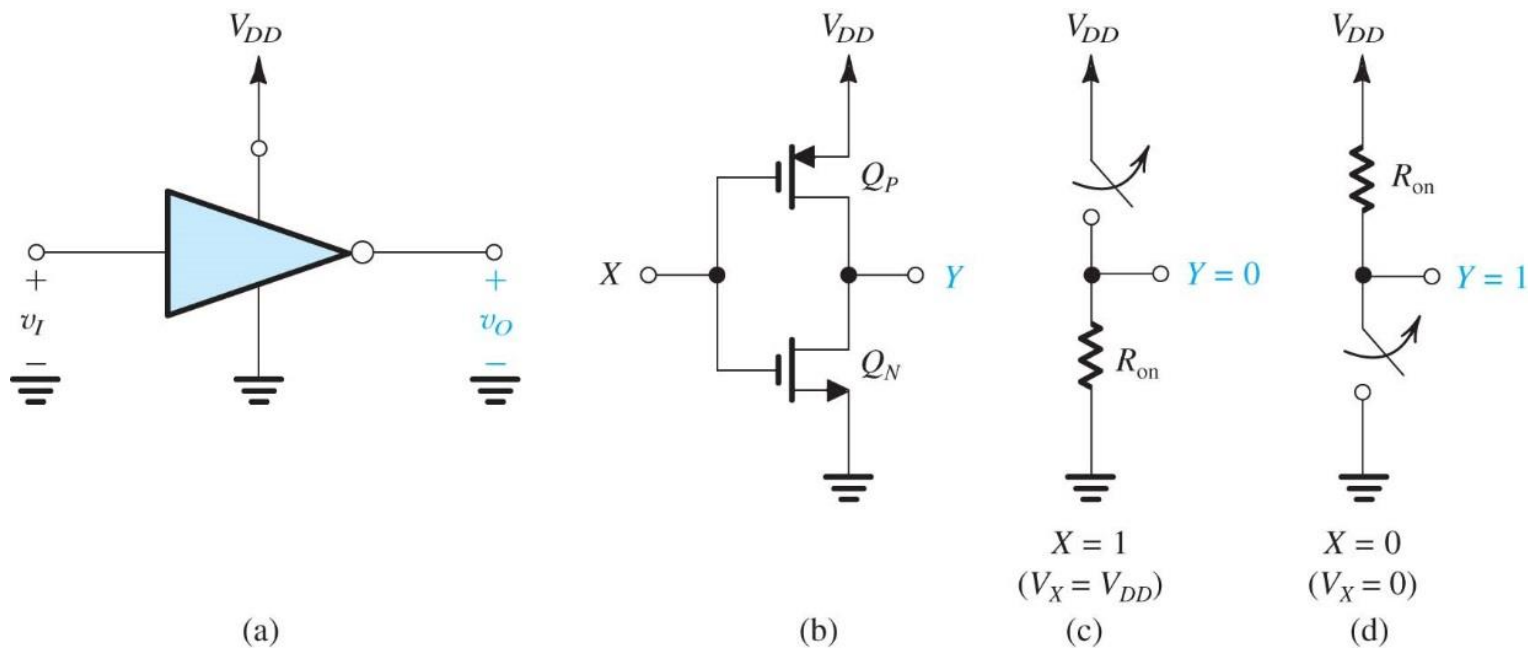


$$\text{Logic: } Y = \overline{X}$$




NMOS : Pull Down transistor
PMOS : Pull Up transistor

 15.1.3 General Structure of CMOS Logic

CMOS Logic Gate: Pull Down Network and Pull Up Network



Pull Down Network (PDN)

   

Logic: $\bar{Y} = A + B$

or $Y = \overline{A + B}$



$\bar{Y} = AB$

or $Y = \overline{AB}$


$\bar{Y} = A + BC$

or $Y = \overline{A + BC}$


Pull UP Network (PUN)

  

$$Y = \overline{A} + \overline{B}$$

 


$$Y = \overline{A} \cdot \overline{B}$$

 

$$Y = \overline{A} + \overline{B} \cdot \overline{C}$$

Logic: $Y = \overline{A} + \overline{B}$ $Y = \overline{A} \cdot \overline{B}$ $Y = \overline{A} + \overline{B} \cdot \overline{C}$


15.1.4 Two-Input NOR Gate

 

From PDN: $\bar{Y} = A + B$


or $Y = \overline{A + B}$

From PUN: $Y = \bar{A} \cdot \bar{B}$

 

Logic: $Y = \overline{A + B} = \bar{A} \cdot \bar{B}$


15.1.5 The Two-Input NAND Gate

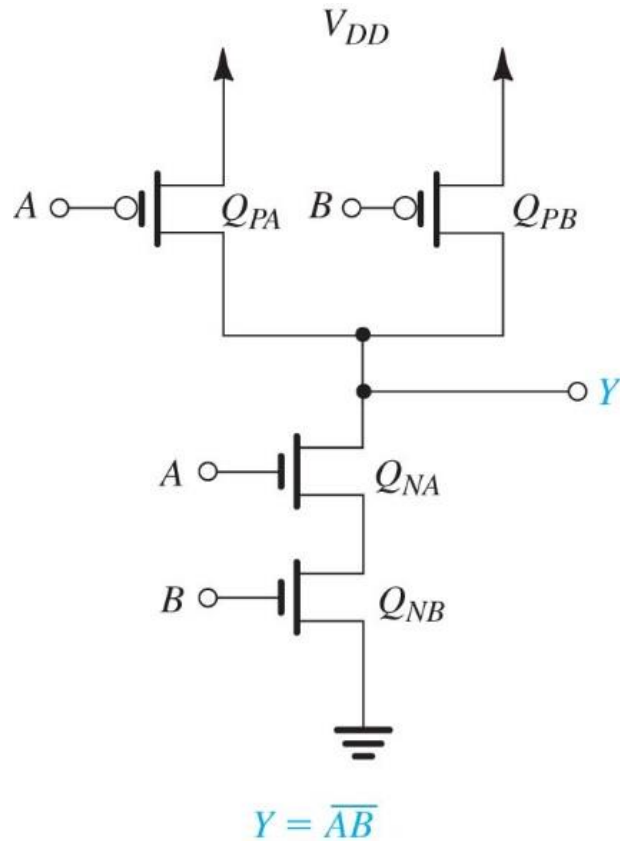

Logic: $Y = \overline{AB} = \overline{A} + \overline{B}$

15.1.6 A Complex Gate

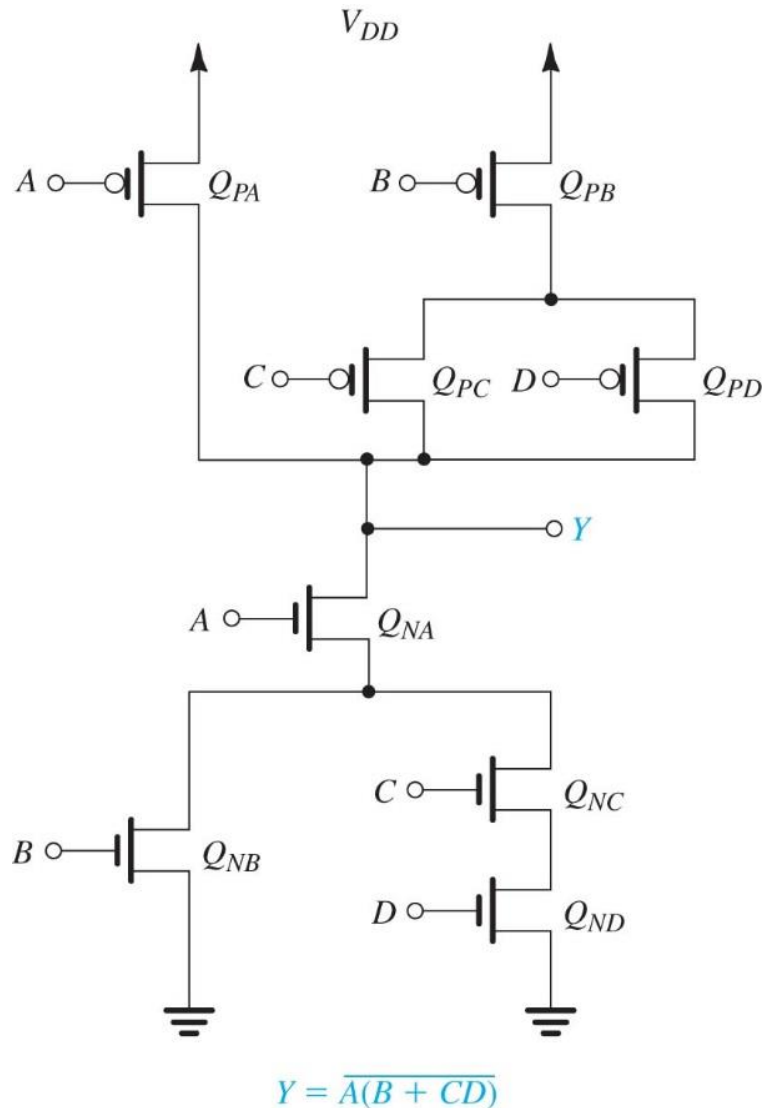15.1.7 Obtaining the PUN from the PDN and Vice Versa



From PDN (**relatively easy**)

$$\text{Logic: } \bar{Y} = A(B + CD)$$

We can use the duality property to obtain PUN from PDN


From PUN (De-Morgan's law)

$$\bar{Y} = A(B + CD)$$


\Rightarrow

$$\begin{aligned} Y &= \overline{A(B + CD)} = \bar{A} + \overline{B + CD} \\ &= \bar{A} + \bar{B} \cdot \overline{CD} = \bar{A} + \bar{B}(\bar{C} + \bar{D}) \end{aligned}$$

15.1.8 The Exclusive-OR Function

 

(a)

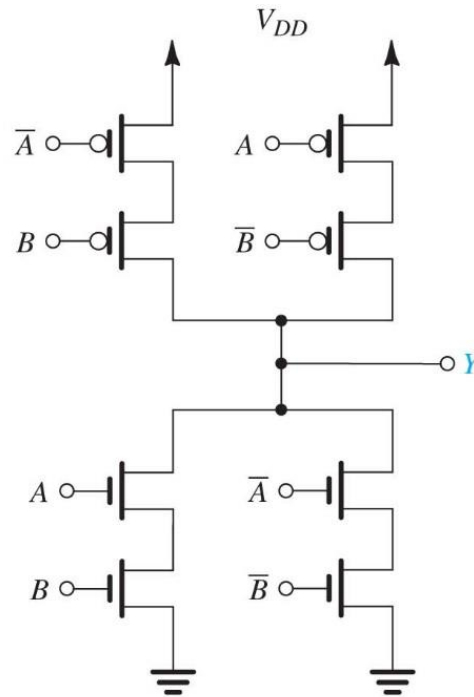

(b)

From PUN (relatively easy)

$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

From PDN

$$\bar{Y} = AB + \bar{A} \cdot \bar{B}$$

From PUN (De-Morgan's law)

$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

$$\Rightarrow \bar{Y} = \overline{A \cdot \bar{B} + \bar{A} \cdot B} = \overline{A \cdot \bar{B}} \cdot \overline{\bar{A} \cdot B}$$


$$= (\bar{A} + B) \cdot (A + \bar{B}) = AB + \bar{A} \cdot \bar{B}$$

1. Two inverters are required. So, totally 12 transistors are needed.
2. PUN and PDN are not dual networks.
Two networks are not necessarily duals.

15.1.9 Summary of the Synthesis Method

1. The PDN can be synthesized by expressing $/Y$ as a function of the **un-complemented variables**. If the complemented variables appear, additional inverters are needed.
2. The PUN can be synthesized by expressing Y as a function of the **complemented variables**. Then, applying the **un-complemented variables** to the gates of the PMOS transistors. If the un-complemented variables appear, additional inverters are needed.
3. The PDN can be obtained from the UN (vice versa) using the duality property.

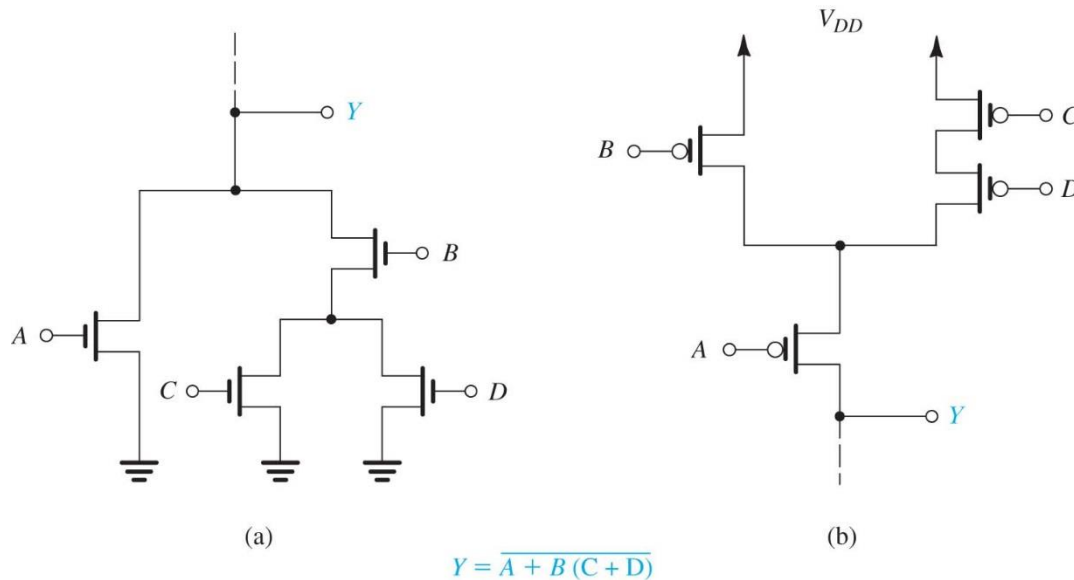Example 15.1 Synthesize $Y = \overline{A + B(C + D)}$








From PDN: $\overline{Y} = A + B(C + D)$

From PUN: $Y = \overline{A + B(C + D)} = \overline{A} \cdot \overline{B(C + D)}$
 $= \overline{A} \cdot (\overline{B} + \overline{C + D}) = \overline{A} \cdot (\overline{B} + \overline{C} \cdot \overline{D})$

15.2 Digital Logic Inverters

  15.2.1 The Voltage Transfer Characteristic (VTC)



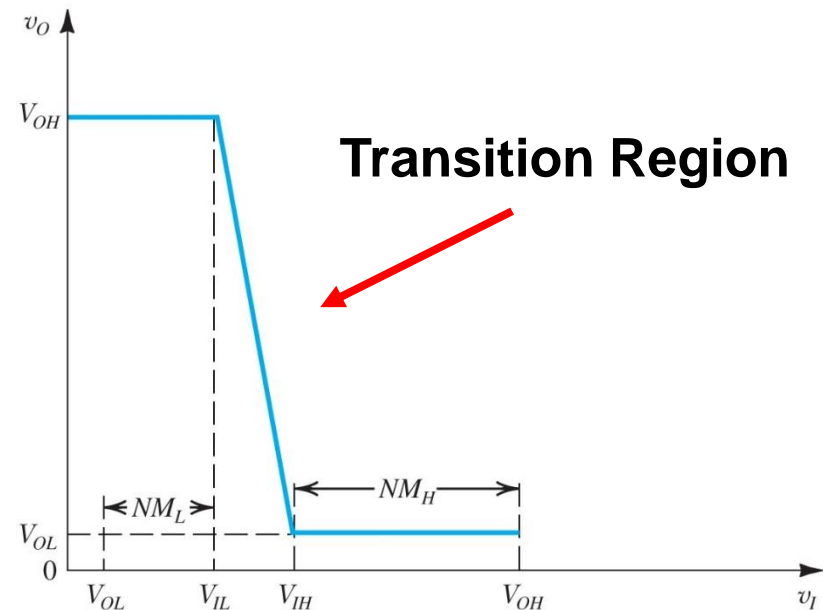 
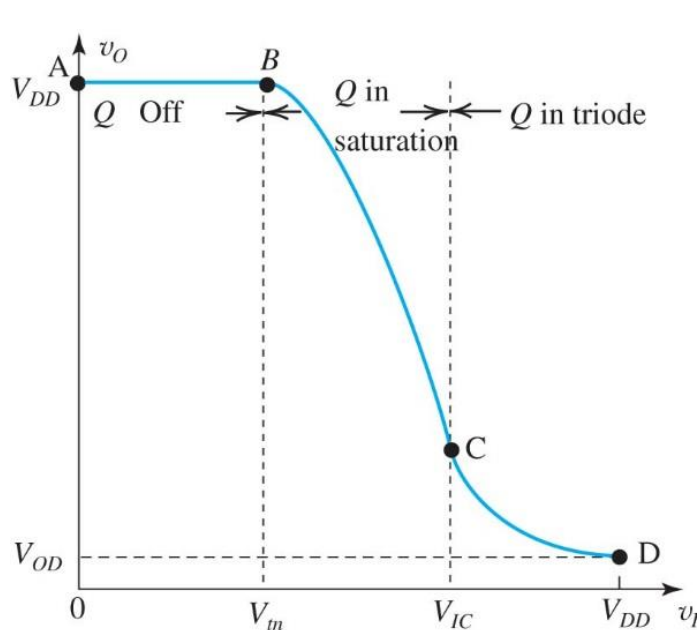


Four parameters (V_{OH} , V_{OL} , V_{IL} , and V_{IH}) to determine the noise margins (N_{MH} and N_{ML})

Table 15.1 Important Parameters of the VTC of the Logic Inverter (Refer to Fig. 15.13)

V_{OL} :	Output low level
V_{OH} :	Output high level
V_{IL} :	Maximum value of input interpreted by the inverter as a logic 0
V_{IH} :	Minimum value of input interpreted by the inverter as a logic 1
NM_L :	Noise margin for low input = $V_{IL} - V_{OL}$
NM_H :	Noise margin for high input = $V_{OH} - V_{IH}$

15.2.2 Noise Margin

  

Noise voltage v_N is coupled to the interconnection between G_1 and G_2 . The input of G_2 becomes

$$v_{I2} = v_{O1} + v_N$$


G_2 has a noise margin for input low @ $v_{O1} = v_{OL}$ & $v_N > 0$

$$v_{I2} = v_{O1} + v_N < v_{IL} \Rightarrow v_N < (v_{IL} - v_{OL}) \equiv NM_L$$

G_2 has a noise margin for input high @ $v_{O1} = v_{OH}$ & $v_N < 0$


$$v_{I2} = v_{O1} + v_N > v_{IH} \Rightarrow |v_N| < (v_{OH} - v_{IH}) \equiv NM_H$$

 V_{IL} and V_{IH} : The VTC points at which the slope is -1



V_M : The M point at which $V_O = V_I$

15.2.3 The Ideal VTC

 


$$V_{OH} = V_{DD}$$
$$V_{IH} = V_{IL} = V_M = V_{DD}/2$$

$$NM_L = v_{IL} - v_{OL} = V_{DD} / 2$$

$$NM_H = v_{OH} - v_{IH} = V_{DD} / 2$$

15.2.4 Inverter Implementation

 


Voltage-controlled Switch:
on-resistance R_{on} is small and off-resistance R_{off} is large

$$\text{When } V_I \text{ is high, } V_{OL} = V_{DD} \frac{R_{on}}{R + R_{on}}$$

$$R_{on} \approx \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)}$$

The logic inverter utilizing two complementary switches.

 
Pull UP (PU) Switch
Pull Down (PD) Switch




Double-Throw Switch

**Current-Steering Logic or
Current-Mode Logic (CML)**

**BJT version:
Emitter-Coupled Logic (ECL)**

 

 
Example 15.2 Resistively Loaded MOS Inverter



(a) When $V_I < V_t$
 $i_D = 0$ and $V_{OH} = V_{DD}$

 (a) When $V_I > V_t$
 Q in Saturation

$$i_D = \frac{\mu_n C_{OX} W}{2L} (V_{GS} - V_t)^2 \Rightarrow i_D = \frac{k_n}{2} (v_I - V_t)^2, \lambda = 0$$



$$i_D = \frac{k_n}{2} (v_I - V_t)^2, \lambda = 0$$

$$v_o = V_{DD} - i_D R = V_{DD} - \frac{k_n R_D}{2} (v_I - V_t)^2$$

$$k_n R_D = \frac{1}{V_x}$$

$$\Rightarrow v_o = V_{DD} - \frac{1}{2V_x} (v_I - V_t)^2$$

To determine V_{IL} @ $dv_o/dv_I = -1$

$$\Rightarrow -1 = -\frac{1}{V_x} (V_{IL} - V_t) \Rightarrow V_{IL} = V_x + V_t \quad (15.12)$$


To determine V_M @ $v_o = v_I = V_M$

$$\Rightarrow V_M = V_{DD} - \frac{1}{2V_x} (V_M - V_t)^2 \Rightarrow V_M = V_t + \sqrt{2(V_{DD} - V_t)V_x + V_x^2} - V_x \quad (15.14)$$

The boundary of the saturation-segment BC : Point C

Substituting $v_o = V_{GS} - V_t = v_I - V_t$ **into** $v_o = V_{DD} - \frac{1}{2V_x} (v_I - V_t)^2$

 The boundary of the saturation-segment BC : Point C



(b)

$$\Rightarrow V_{OC} = \sqrt{2V_{DD}V_x + V_x^2} - V_x$$

$$V_{IC} = V_t + \sqrt{2V_{DD}V_x + V_x^2} - V_x$$

Beyond Point C, i.e., segment CD, the transistor in the triode region

$$i_D = k_n \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right]$$

$$\Rightarrow i_D = k_n \left[(v_I - V_t)v_O - \frac{1}{2}v_O^2 \right]$$

$$v_O = V_{DD} - i_D R \Rightarrow v_O = V_{DD} - \frac{(v_I - V_t)v_O - \frac{1}{2}v_O^2}{V_x} \quad (15.17)$$

To determine V_{IH} @ $dv_O/dv_I = -1$

$$\Rightarrow V_{IH} = 2v_O - V_x + V_t \quad (15.18)$$

Substituting (15.18) into (15.17) and $v_I = V_{IH}$

Substituting (15.18) into (15.17) and $v_I = V_{IH}$

$$\Rightarrow v_O |_{v_I = V_{IH}} = 0.816 \sqrt{V_{DD} V_x}$$

Substituting into (15.18)

$$\Rightarrow V_{IH} = V_t + 1.63 \sqrt{V_{DD} V_x} - V_x \quad (15.20)$$

To determine V_{OL} @ $v_I = V_{DD}$


$$v_O = V_{DD} - \frac{1}{V_x} \left[(v_I - V_t) v_O - \frac{1}{2} v_O^2 \right]$$


$$\Rightarrow V_{OL} = V_{DD} - \frac{1}{V_x} \left[(V_{DD} - V_t) V_{OL} - \frac{1}{2} V_{OL}^2 \right]$$

To determine $V_{OL} \ll V_{DD} - V_t$

$$\Rightarrow V_{OL} \cong V_{DD} - \frac{1}{V_x} \left[(V_{DD} - V_t) V_{OL} \right]$$
 
$$\Rightarrow V_{OL} \cong \frac{V_{DD}}{1 + (V_{DD} - V_t) / V_x} \quad (15.22)$$



 

It is interesting that V_{OL} can be found by

$$V_{OL} \cong V_{DD} \frac{r_{DS}}{R_D + r_{DS}} \quad @ \quad r_{DS} = R_{on} \cong \frac{1}{k_n (V_{DD} - V_t)}$$

$$\Rightarrow V_{OL} = \frac{V_{DD}}{1 + (V_{DD} - V_t) / V_x} \quad \text{Same as (15.22)}$$


(b) If $V_M = V_{DD}/2$, what is V_x


$$V_M = V_t + \sqrt{2(V_{DD} - V_t)V_x + V_x^2} - V_x \quad (15.14)$$

$$\Rightarrow V_x |_{V_M = V_{DD}/2} = \frac{(V_{DD}/2 - V_t)^2}{V_{DD}} \quad (15.25)$$

(c) If $V_{DD} = 1.8V$, $V_t = 0.5V$, $V_M = V_{DD}/2$

$$V_x |_{V_M = 0.9V} = 0.089V$$

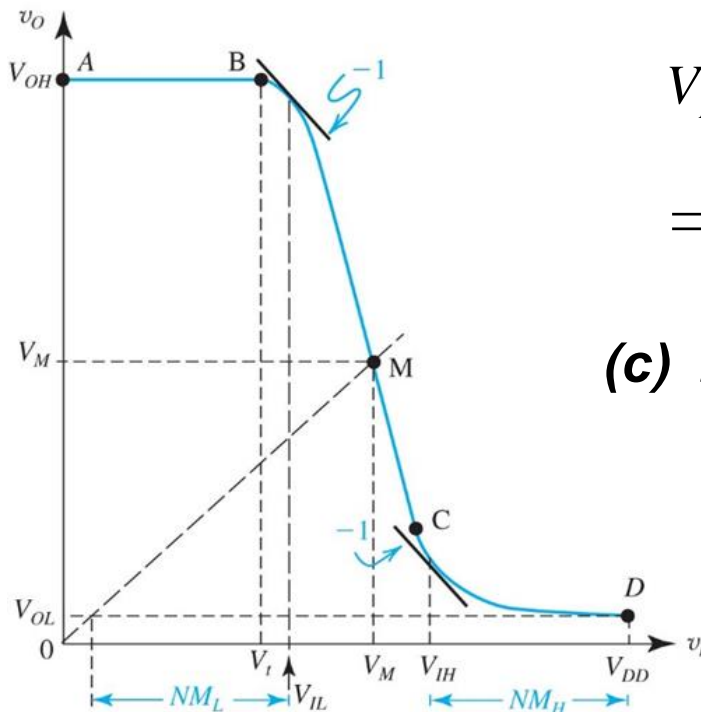

 

(b)

$$V_{OH} = V_{DD} = 1.8V$$

$$(15.22) : V_{OL} = 0.12V \quad NM_L = V_{IL} - V_{OL} = 0.47V$$

$$(15.12) : V_{IL} = 0.59V \quad NM_H = V_{OH} - V_{IH} = 0.74V$$

$$(15.20) : V_{IH} = 1.06V$$

(d) If $k'_n = 300 \mu A/V^2$ and $W/L = 1.5$, determine R_D

$$\begin{aligned} k_n R_D &= \frac{1}{V_x} \Rightarrow R_D = \frac{1}{k_n V_x} = \frac{1}{k'_n (W/L) V_x} \\ &= \frac{1}{300 \cdot 10^{-6} \cdot 1.5 \cdot 0.089} = 25k\Omega \end{aligned}$$

When $v_O = V_{OL}$, the current from the supply is


$$I_{DD} = \frac{V_{DD} - V_{OL}}{R_D} = \frac{1.8 - 0.12}{25k} = 67 \mu A$$

$$P_D = V_{DD} I_{DD} = 1.8 \times 67 = 121 \mu W$$

The inverter spends half of the time in this state:

$$P_{D,average} = P_D / 2 = 60.5 \mu W$$

 Example 15.3 To eliminate R_D , the **pseudo-NMOS Inverter** is used.



(a) If $V_{DD}=1.8V$, $V_{tn}=-V_{tp}=V_t=0.4V$,
 $k_n=300\mu A/V^2$, $k_n=5k_p$

When $V_I < V_t$

$$i_{DN}=i_{DP}=0 \text{ and } V_{OH}=V_{DD}$$

When $V_I = V_{DD}$

Q_P in Saturation; Q_N in Triode

$$i_{DP} = k_p (V_{DD} - V_t)^2 / 2$$


$$i_{DN} = k_n \left[(V_{DD} - V_t)V_{OL} - \frac{1}{2}V_{OL}^2 \right] = i_{DP}$$

$$\Rightarrow V_{OL} = (V_{DD} - V_t) [1 - \sqrt{1 - k_p / k_n}]$$

(b) $V_{OH}=V_{DD}=1.8V$; $V_{OL}=0.15V$



$$i_{DP}=58.8\mu A; P_D=i_{DP}V_{DD}=105.8\mu W$$

$$P_{D, \text{average}}=52.9\mu W$$

 

$$i_{DP} = k_p (V_{DD} - V_t)^2 / 2 = 300 / 5 (1.8 - 0.4)^2 / 2 = 58.8\mu A$$



15.3 The CMOS Inverter

  

When $v_I = 0V$ (Logic 0), $V_{OH} = V_{DD}$




When $v_I = V_{DD}$ (Logic 1), $V_{OL} = 0V$

When $v_I = V_{DD}$, $V_{OL} = 0V$

  

$$r_{DSN} \cong \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{tn})} = \frac{1}{k'_n \left(\frac{W}{L}\right)_n (V_{DD} - V_{tn})}$$


When $v_I = 0V$, $V_{OH} = V_{DD}$

   

$$r_{DSP} \cong \frac{1}{k'_p \left(\frac{W}{L}\right)_p (V_{DD} - |V_{tp}|)}$$

1. The output levels are 0 and V_{DD}
2. Static power=0 in the two states; neglecting the leakage currents
3. The low output resistance makes the inverter less sensitive to the effects of noises and other disturbances
4. The pull-up and pull-down devices provide the high output driving capability in both directions
5. The input resistance of the inverter is high

15.3.2 The VTC

 

Q_N in Triode, $v_O \leq v_I - V_{tn}$

$$i_{DN} = k'_n \left(\frac{W}{L} \right)_n \left[(v_I - V_{tn}) v_O - \frac{1}{2} v_O^2 \right]$$

Q_N in Sat., $v_O \geq v_I - V_{tn}$

$$i_{DN} = k'_n \left(\frac{W}{L} \right)_n (v_I - V_{tn})^2 / 2$$

Q_P in Triode, $v_O \geq v_I + |V_{tp}|$

$$i_{DP} = k'_p \left(\frac{W}{L} \right)_p \left[(V_{DD} - v_I - |V_{tp}|)(V_{DD} - v_O) - \frac{1}{2} (V_{DD} - v_O)^2 \right]$$

Q_P in Sat., $v_O \leq v_I + |V_{tp}|$

$$i_{DP} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - v_I - |V_{tp}|)^2 / 2$$

Let Q_p and Q_n have the same channel lengths,

$$k'_n \left(\frac{W}{L} \right)_n = k'_p \left(\frac{W}{L} \right)_p \Rightarrow \frac{\mu_n}{\mu_p} = \frac{W_p}{W_n}$$

**If $V_{tn} = -V_{tp} = V_t$ to determine V_{IH} @ slope=-1
 Q_p in Sat. and Q_n in Triode**

$$i_{DN} = k'_n \left(\frac{W}{L} \right)_n \left[(v_I - V_{tn}) v_O - \frac{1}{2} v_O^2 \right]$$

$$i_{DP} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - v_I - |V_{tp}|)^2 / 2$$


$$\Rightarrow (v_I - V_t) v_O - \frac{1}{2} v_O^2 = (V_{DD} - v_I - V_t)^2 / 2 \quad (15.33)$$

Differentiate (15.33); let $v_I = V_{IH}$ @ slope=-1;


$$\Rightarrow v_O = V_{IH} - \frac{V_{DD}}{2} \quad (15.34)$$

Substituting (15.34) into (15.33); let $v_I = V_{IH}$
 
$$\Rightarrow V_{IH} = \frac{5V_{DD} - 2V_t}{8}$$



 V_{IL} can be determined similarly. Alternatively, we can use the symmetrical property



$$V_{IH} - \frac{V_{DD}}{2} = \frac{V_{DD}}{2} - V_{IL} \Rightarrow V_{IL} = \frac{3V_{DD} + 2V_t}{8}$$

$$NM_L = V_{IL} - V_{OL} = \frac{3V_{DD} + 2V_t}{8}$$

$$NM_H = V_{OH} - V_{IH} = \frac{3V_{DD} + 2V_t}{8}$$

$$(\because V_{IH} = \frac{5V_{DD} - 2V_t}{8})$$

15.3.2 When Q_N and Q_P are not matched

Assume Q_N and Q_P are in Sat., $v_I = V_M$


$$i_{DN} = k'_n \left(\frac{W}{L} \right)_n (v_I - V_{tn})^2 / 2$$

$$i_{DP} = k'_p \left(\frac{W}{L} \right)_p (V_{DD} - v_I - |V_{tp}|)^2 / 2$$

Q_p and Q_n have the same channel lengths,

$$i_{DN} = i_{DP} \Rightarrow V_M = \frac{r(V_{DD} - |V_{tp}|) + V_{tn}}{1 + r}$$

 
$$r = \sqrt{\frac{k_p}{k_n}} = \sqrt{\frac{\mu_p W_p}{\mu_n W_n}}$$



For a 0.18 μ m process,

- V_M increases with r , i.e., if $k_p > k_n$, V_M moves to V_{DD}**
- V_M is not a strong function of r . Change r from 1 to 0.5, reduces V_M by 0.13V.**
- For matched case, PMOS's W/L increases \rightarrow Increase Area
But, maximize NM_L and NM_H**

Example 15.4 CMOS Inverter Design

 

$V_{DD}=1.8V$, $V_{tn}=|V_{tp}|=0.5V$, $\mu_n C_{ox}=300\mu A/V^2$,
 $\mu_n=4\mu_p$, $L=0.18\mu m$, $(W/L)_n=1.5$,

$$V_M = \frac{r(V_{DD} - |V_{tp}|) + V_{tn}}{1 + r} \quad r = \sqrt{\frac{k_p}{k_n}} = \sqrt{\frac{\mu_p W_p}{\mu_n W_n}}$$

Ex. $r=1$, $V_M = \frac{(1.8 - 0.5) + 0.5}{2} = 0.9V$


(a) If $V_M=0.9V$, find $W_p=?$

$r=1 \rightarrow W_p=4W_n \rightarrow W_n=0.27\mu m$ and $W_p=1.08\mu m$

 (b) $V_{IH} = \frac{5V_{DD} - 2V_t}{8} = \frac{5 \cdot 1.8 - 2 \cdot 0.5}{8} = 1V$

$$V_{IL} = \frac{3V_{DD} + 2V_t}{8} = 0.8V$$

$$NM_L = V_{IL} - V_{OL} \text{ \& } NM_H = V_{OH} - V_{IH}$$



Ideally, $NM_H = V_{OH} - V_{IH} = 1.8 - 1 = 0.8V$

$NM_L = V_{IL} - V_{OL} = 0.8 - 0 = 0.8V$

at slope=-1, $v_{OL} = V_{IH} - \frac{V_{DD}}{2} \quad (15.34)$


$\Rightarrow V_{OL,max} = 1 - 0.9 = 0.1V$

From symmetry, $V_{OH,min} = V_{DD} - 0.1 = 1.7V$

Worst Case

$NM_H = V_{OH,min} - V_{IH} = 1.7 - 1 = 0.7V$

 $NM_L = V_{IL} - V_{OL,max} = 0.8 - 0.1 = 0.7V$




(c) Inverter's output resistance at low-state

$$r_{DSN} \cong \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{DD} - V_{tn})} = \frac{1}{300\mu \cdot 1.5 \cdot (1.8 - 0.5)} = 1.71k\Omega$$

Since symmetry, Inverter's output resistance at high-state

$r_{DSP} = r_{DSN} = 1.71k\Omega$

 

(d) $V_I = V_O = V_M = 0.9V$, $V_{OV} = V_M - V_{tn} = 0.4V$, Q_P and Q_N are in sat. $\lambda_n = \lambda_p = 0.2 \text{ V}^{-1}$

$$i_{DN} = \mu_n C_{ox} \left(\frac{W}{L} \right)_n (v_I - V_{tn})^2 / 2 = 36 \mu A$$


$$g_{mn} = g_{mp} = \frac{I_D}{V_{OV}} = 0.18 \text{ mA} / \text{V}^2$$

$$r_{on} = r_{op} = \frac{1}{\lambda_n I_D} = 139 \text{ k}\Omega$$

$$A_v = -(g_{mn} + g_{mp})(r_{on} // r_{op}) = -25 \text{ V} / \text{V}$$

15.4 Dynamic Operation of the CMOS Inverter

15.4.1 Propagation Delay

 

1. The output signal is not longer an ideal pulse.
2. There is a time delay between the edges of the input and the corresponding inverter output. For example, t_{PHL} and t_{PLH} .

The inverter's Propagation Delay is defined as $t_P = \frac{t_{PHL} + t_{PLH}}{2}$

To consider the inverter's **maximum switching frequency**;

i.e., the **minimum period** for each cycle is

$$T_{\min} = t_{PHL} + t_{PLH} = 2t_P \qquad f_{\max} = \frac{1}{T_{\min}} = \frac{1}{2t_P}$$

The propagation delay is owing to the time to charge and discharge the various capacitances in the circuit.

- 1. A fundamental rule to analyze the dynamic operation of a circuit***


$$I\Delta t = \Delta Q = C\Delta V$$

- 2. To consider a step input for a single-time-constant (STC) circuit,***

$$y(t) = Y_{\infty} - (Y_{\infty} - Y_{0+})e^{-t/\tau}$$

where Y_{∞} is the final value, Y_{0+} is the initial value, and τ is the time constant of an STC circuit.

 Example 15.5 Calculating the propagation delay of a simple Inverter




(a)

$$v_o(t) = V_{OH} - (V_{OH} - V_{OL})e^{-t/\tau}, \tau = RC$$


$$v_o(t_{PLH}) = V_{OH} - (V_{OH} - V_{OL})e^{-t_{PLH}/\tau} = \frac{V_{OH} + V_{OL}}{2}$$
 
$$\Rightarrow t_{PLH} = \tau \ln 2 = 0.69\tau = 0.69RC$$




(b)

 The **propagation delay** and the **transition time** of the logic Inverter




1. t_r rise time: The time from 10% to 90% of the input swing
($V_{OH}-V_{OL}$)
2. t_f : fall time: The time from 90% to 10% of the input swing
($V_{OH}-V_{OL}$)
3. t_{PHL} , t_{PLH} : The time from $V_I = (V_{OL}+V_{OH})/2$ to $V_O = (V_{OL}+V_{OH})/2$
4. t_{THL} and t_{TLH} : The time from 10% to 90% of the output swing
($V_{OH}-V_{OL}$)

 15.4.2 Determining the Propagation Delay of the CMOS Inverter




(a)

 

(b)

 1. **Cap. C :** consider all the parasitic cap. of Q_N and Q_P , the interconnection cap. and the input cap. of the next logics.
2. To calculate t_{PHL} , t_{PLH} , and t_p





1. Let the initial voltage $v_O = V_{DD}$
2. At $t=0$, $v_I = V_{DD} \rightarrow Q_N$ on and Q_P off.
3. i_{DN} will discharge C . It operates from $E \rightarrow F \rightarrow M \rightarrow D$.
4. E - F : Q_N is in saturation.
5. F - M - D : Q_N is in triode.
6. E - M : Assume an average current I_{ave}

$$I_{ave} = [i_{DN}(E) + i_{DN}(M)] / 2, \quad i_{DN}(E) = k'_n \left(\frac{W}{L} \right)_n (V_{DD} - V_{tn})^2 / 2$$

$$i_{DN}(M) = k'_n \left(\frac{W}{L} \right)_n \left[(V_{DD} - V_{tn}) V_{DD} / 2 - \frac{1}{2} (V_{DD} / 2)^2 \right]$$

$$I_{ave} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_n [(V_{DD} - V_m)^2 / 2 + (V_{DD} - V_m) V_{DD} / 2 - \frac{1}{2} (V_{DD} / 2)^2]$$
  
$$= \frac{k'_n \left(\frac{W}{L} \right)_n V_{DD}^2}{4} \left[\left(1 - \frac{V_m}{V_{DD}}\right)^2 + \left(1 - \frac{V_m}{V_{DD}}\right) - \frac{1}{4} \right] = \frac{k'_n \left(\frac{W}{L} \right)_n V_{DD}^2}{4} \left[\frac{7}{4} - \frac{3V_m}{V_{DD}} + \left(\frac{V_m}{V_{DD}}\right)^2 \right] = \frac{k'_n \left(\frac{W}{L} \right)_n V_{DD}^2}{2\alpha_n}$$




$$\alpha_n = 2 / \left[\frac{7}{4} - \frac{3V_m}{V_{DD}} + \left(\frac{V_m}{V_{DD}}\right)^2 \right]$$

$$I_{ave} t_{PHL} = C [V_{DD} - V_{DD} / 2]$$

$$t_{PHL} = \frac{C V_{DD}}{2 I_{ave}}$$

\Rightarrow
 
$$t_{PHL} = \frac{\alpha_n C}{k'_n (W / L)_n V_{DD}}$$




$$t_{PLH} = \frac{\alpha_p C}{k'_p (W / L)_p V_{DD}}$$

$$\alpha_p = 2 / \left[\frac{7}{4} - \frac{3|V_{tp}|}{V_{DD}} + \left(\frac{|V_{tp}|}{V_{DD}}\right)^2 \right]$$

$$\Rightarrow t_P = \frac{t_{PHL} + t_{PLH}}{2}$$

1. When $V_{tn}=|V_{tp}|$, $\alpha_n=\alpha_p$. By selecting W/L and $k'_n(W/L)_n=k'_p(W/L)_p$, one can **equalize t_{PHL} and t_{PLH}** .
2. Since t_p is proportional to C , one shall minimize all the parasitic capacitances; such as devices (minimizing the length), wiring, and coupling cap.
3. For 0.25 μ m, 0.18 μ m, and 0.13 μ m processes, $\mu_n C_{ox}$ is 110, 300, 430 μ A/V². So, one can select high $\mu_n C_{ox}$ to reduce t_p . But, for such process, C_{ox} is increased.
4. One can increase W/L to reduce t_p . Sometimes, it works, but it may also increase C .
5. One can increase V_{DD} to reduce t_p . But, it depends upon the supply voltage which determined by the process.
6. The conclusion is “there is a trade-off in designing CMOS digital circuits”.

An Alternative Approach

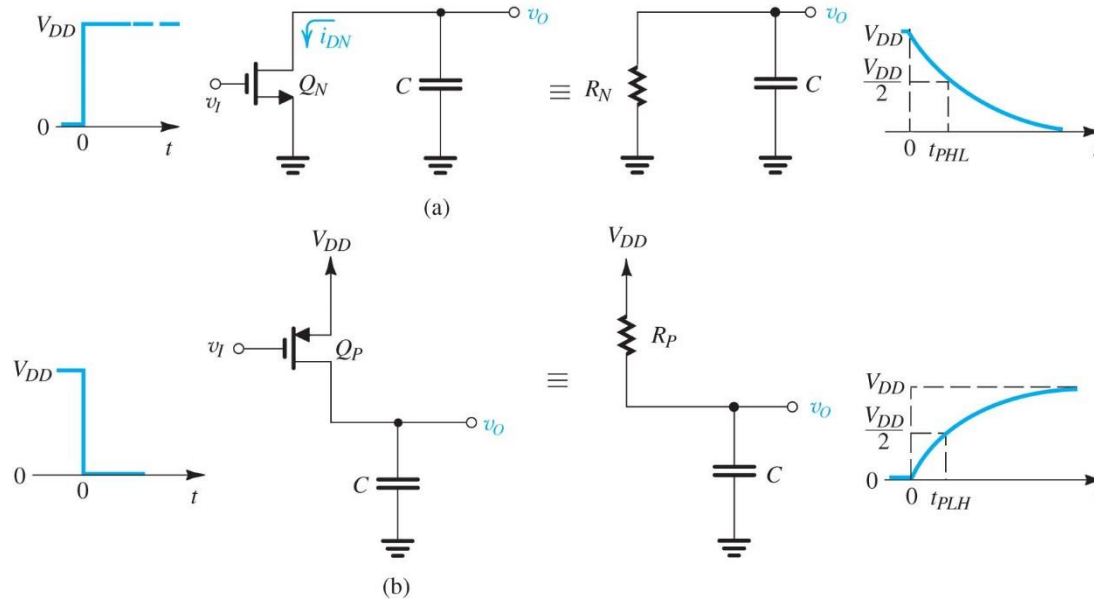


For a step input, $t_{PHL} = \tau \ln 2 = 0.69\tau = 0.69R_N C$ & $t_{PLH} = 0.69R_P C$

Empirical values $R_N = \frac{12.5}{(W/L)_n} k\Omega$ & $R_P = \frac{30}{(W/L)_p} k\Omega$



For a ramp input, $t_{PHL} \approx R_N C$ & $t_{PLH} \approx R_P C$


15.4.3 Determining the Equivalent Load Capacitance

 1. Wiring Cap. C_w is the cap. of the wire or interconnection.
2. Interconnection cap. becomes dominant as technology scaled down



3. Miller Effect for Cap. C_{gd1}

 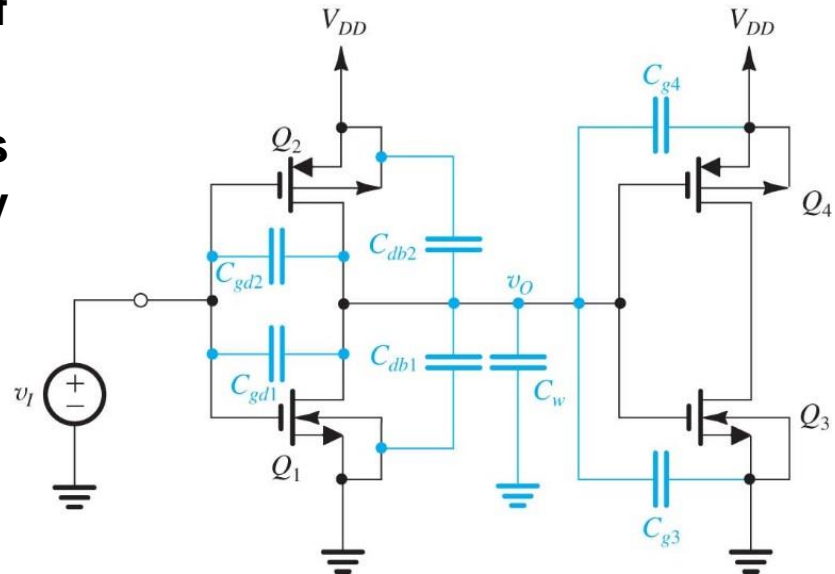

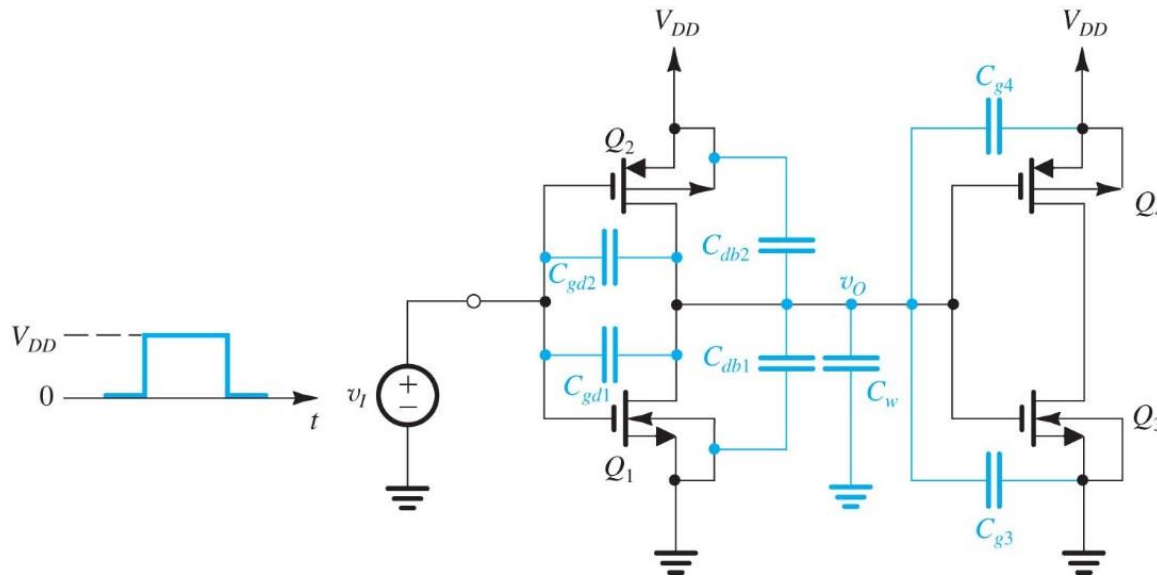

Junction cap.

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_o}}} \quad C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$

V_o junction built-in voltage (0.6~0.8V)

V_{DB} , V_{SB} reverse-bias voltage

Cap. C_{db1} and $C_{db2} \rightarrow (9.25)$

Cap. C_{g3} and C_{g4}


$$C_{g3} + C_{g4} = (WL)_3 C_{ox} + (WL)_4 C_{ox} + C_{gsov3} + C_{gdov3} + C_{gsov4} + C_{gdov4}$$

Equivalent Load Capacitance

$$C = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_W$$

 Example 15.7 Determining the Equivalent Load Capacitance and Propagation Delay

To consider a $0.25\mu\text{m}$ process, $V_{DD}=2.5\text{V}$, $V_{tn}=-V_{tp}=0.5\text{V}$, $\mu_n C_{ox}=110\mu\text{A}/\text{V}^2$, $\mu_p C_{ox}=30\mu\text{A}/\text{V}^2$, $C_{ox}=6\text{fF}/\mu\text{m}^2$, Qn's $W_n/L_n=0.375\mu\text{m}/0.25\mu\text{m}$, Qp's $W_p/L_p=1.125\mu\text{m}/0.25\mu\text{m}$, overlap capacitance $C_{gdn}=0.3\text{fF}/\mu\text{m} \times W_n$, $C_{gdp}=0.3\text{fF}/\mu\text{m} \times W_p$, $C_{dbn}=0.1\text{fF}$, $C_{dbp}=0.1\text{fF}$, wire capacitance $C_W=0.2\text{fF}$



$$C = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_W$$

$$C_{gd1} = 0.3 \times W_n = 0.3 \times 0.375 = 0.1125\text{fF}$$

$$C_{gd2} = 0.3 \times W_p = 0.3 \times 1.125 = 0.3375\text{fF}$$

$$C_{g3} = W_n L_n C_{ox} + 2C_{gdn} = 0.375 \times 0.25 \times 6 + 2 \times 0.3 \times 0.375 = 0.7875\text{fF}$$

$$C_{g4} = W_p L_p C_{ox} + 2C_{gdp} = 1.125 \times 0.25 \times 6 + 2 \times 0.3 \times 1.125 = 2.3625\text{fF}$$

$$\Rightarrow C = 6.25\text{fF}$$

$$I_{ave} t_{PHL} = C[V_{DD} - V_{DD} / 2]$$


$$t_{PHL} = \frac{CV_{DD}}{2I_{ave}} \Rightarrow \alpha_n = 2 / \left[\frac{7}{4} - \frac{3V_{tn}}{V_{DD}} + \left(\frac{V_{tn}}{V_{DD}} \right)^2 \right] = 1.7 \quad \& \quad t_{PHL} = \frac{\alpha_n C}{k'_n (W / L)_n V_{DD}} = 25.8 ps$$

$$\alpha_p = 2 / \left[\frac{7}{4} - \frac{3|V_{tp}|}{V_{DD}} + \left(\frac{|V_{tp}|}{V_{DD}} \right)^2 \right] = 1.7 \quad \& \quad t_{PLH} = \frac{\alpha_p C}{k'_p (W / L)_p V_{DD}} = 31.5 ps$$

$$\Rightarrow t_P = \frac{t_{PHL} + t_{PLH}}{2} = 28.7 ps$$

15.5 Transistor Sizing

15.5.1 Inverter Sizing

 

1. To minimize area, the minimum length given by the technology is selected.
2. To minimize area, $(W/L)_n$ is selected in the range of 1 to 1.5. The selection of $(W/L)_p$ relative to $(W/L)_n$ has an impact on **Noise Margin** and **t_{PLH}** . Both are optimized by matching Q_N and Q_P . It wastes area and increases C .
Thus, selecting $(W/L)_p = (W/L)_n$ or $(W/L)_p = 2(W/L)_n$ for compromise.
3. Having settled on the ratio of $(W/L)_p$ to $(W/L)_n$. Let us consider **t_p**

$C = C_{\text{int}} + C_{\text{ext}}$; intrinsic cap. C_{int} and

extrinsic cap. C_{ext} : wire cap. and the input cap. from the driven stage

Increase $(W/L)_p$ and $(W/L)_n$ by a factor of S relative to the minimum-size inverter by which $C_{int}=C_{int0}$.

$$C = C_{int} + C_{ext} = S \cdot C_{int0} + C_{ext}$$

For a given equivalent resistance,

$$R_{eq} = \frac{1}{2}(R_N + R_P) \Rightarrow t_P = 0.69 R_{eq} C$$

If the minimum-size inverter has R_{eq0} , increasing $(W/L)_p$ and $(W/L)_n$ by a factor of S reduces $R_{eq}=R_{eq0}/S$.


$$\Rightarrow t_P = 0.69 \frac{R_{eq0}}{S} (S \cdot C_{int0} + C_{ext}) = 0.69 R_{eq0} \cdot C_{int0} + 0.69 \frac{R_{eq0}}{S} \cdot C_{ext}$$

Thus, this scaling does not change the part of t_P caused by Q_N and Q_P

It reduces the part of t_P caused by C_{ext} . Of course, the area will be increased.


15.5.2 Transistor Sizing in CMOS Logic Gates

 1. For a basic inverter, $(W/L)_n = n$ and $(W/L)_p = p$ where n is usually 1 to 1.5. For match design $p = (\mu_n/\mu_p) * n$; **often $p=2n$** , and for minimum design, $p=n$.



PDN has a discharging current equal to that of $(W/L)_n = n$

 and PUN has a charging current equal to that of $(W/L)_p = p$



2. If a number of MOSFETs with $(W/L)_1, (W/L)_2, \dots$ are in series,

$$R_{Series} = R_{N1} + R_{N2} + \dots = \frac{\text{constant}}{(W/L)_1} + \frac{\text{constant}}{(W/L)_2} + \dots = \frac{\text{constant}}{(W/L)_{eq}}$$

$$\Rightarrow (W/L)_{eq} = \frac{1}{\frac{1}{(W/L)_1} + \frac{1}{(W/L)_2} + \dots}$$

E.g., Two transistors in series, $(W/L)_{eq} = (W/L)_{1,2}/2$



If a number of MOSFETs with $(W/L)_1$, $(W/L)_2$,
... are in parallel,

$$(W/L)_{eq} = (W/L)_1 + (W/L)_2 + \dots$$

E.g., Two transistors in parallel, $(W/L)_{eq} = 2(W/L)_{1,2}$


For example, for a 4-input OR gate in the worst case (the lower current), only a NMOS with $(W/L)_n = n$ is on. To have the same charging current compared to a basic inverter, PMOS has $(W/L)_p = 4p$.

Similarly, for a 4-input NAND gate, NMOS has $(W/L)_n = 4n$.

 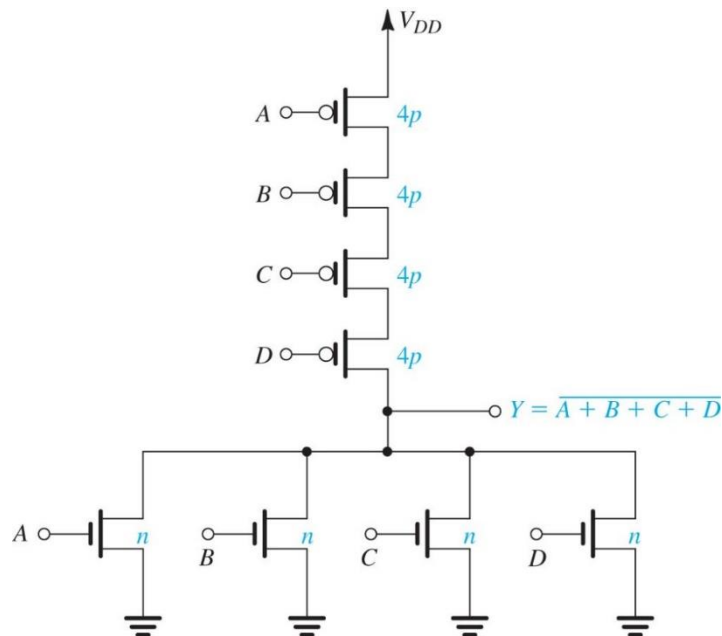

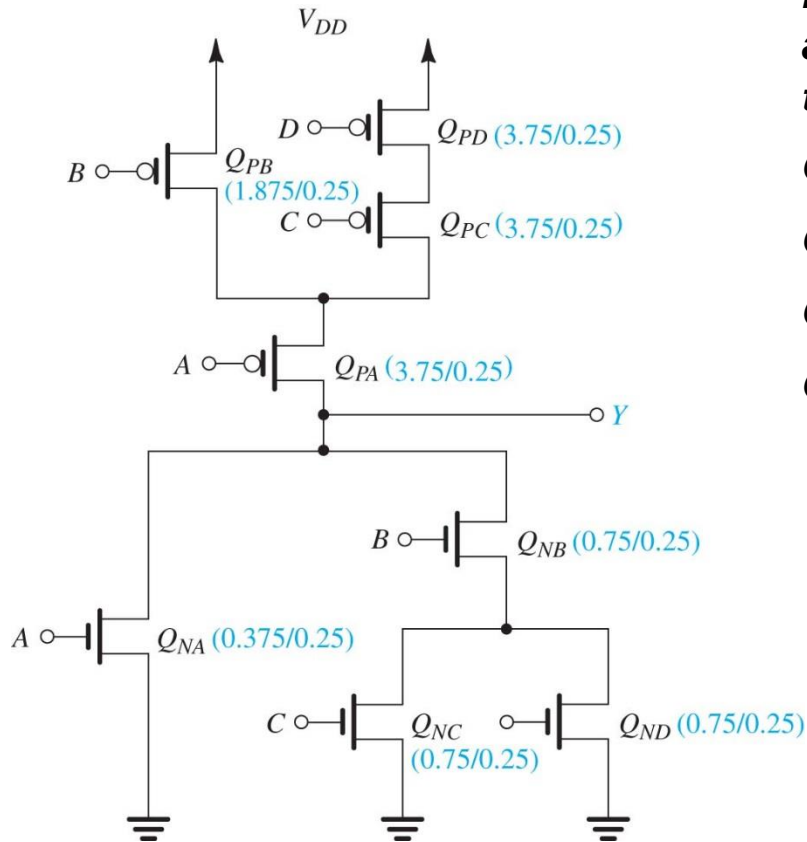Example 15.8 Transistor Sizing of a CMOS Gate

For a basic inverter, $n=1.5$ and $p=5$ and $L=0.25\mu\text{m}$.



PDN: to consider a worst case, Q_{NB} is active and either Q_{NC} or Q_{ND} is active. Thus, we have two transistors in series.

$$Q_{NB}: W/L=2n=3=0.75/0.25$$

$$Q_{NC}: W/L=2n=3=0.75/0.25$$

$$Q_{ND}: W/L=2n=3=0.75/0.25$$

$$Q_{NA}: W/L=n=1.5=0.375/0.25$$

PUN: to consider a worst case, three transistors are in series.

$$Q_{PD}: W/L=3p=15=3.75/0.25$$


$$Q_{PC}: W/L=3p=15=3.75/0.25$$

$$Q_{PA}: W/L=3p=15=3.75/0.25$$

The equivalent W/L of the series connection of Q_{PB} and Q_{PA} should be equal to p .

$$Q_{PB}: W/L=1.5p=7.5=1.875/0.25$$

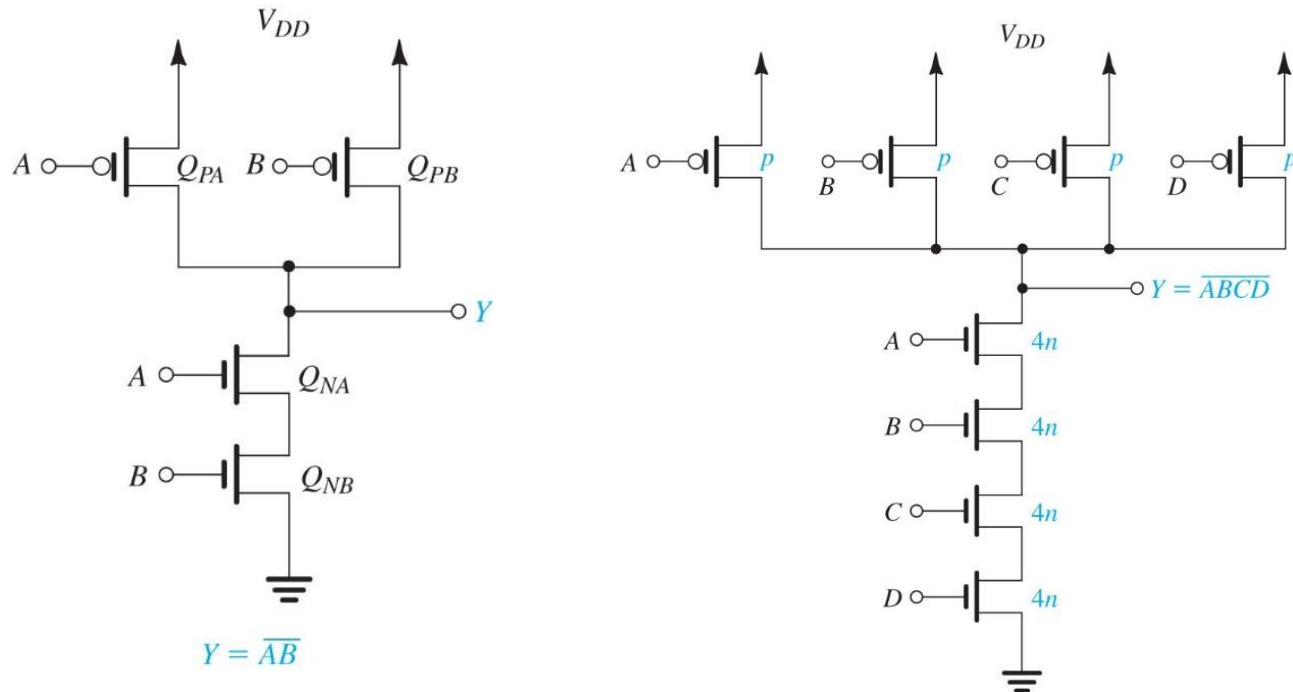
15.5.3 Effects of Fan-in and Fan-out on Propagation Delay



1. **Each additional input to a CMOS gate, two transistors are required (ex. 2-NAND and 4-NAND). To increase with fan-in, it increases the chip area, capacitance, and propagation delay. Thus, the fan-in of a NAND gate is limited to 4.**
2. **When a CMOS gate increases its fan-out, the capacitance will be increase which increases the propagation delay. If a higher number of inputs is required, one can realize the Boolean function with the gates of no more than 4-inputs.**

15.5.4 Driving a Large Capacitance

Assume a ramp input,

 


(a)

$$t_P = \tau = C_L R$$

$$C_{in} = C$$

 To drive a large capacitance load, one can increase the size to reduce the equivalent resistance. But, the input capacitance increases.




(b)

$$t_P = \tau = C_L (R / m)$$

$$C_{in} = mC$$

A chain of inverters in cascade is used.

 

Each inverter in the chain is scaled by a factor of x .

For example, the input capacitance of the n -th inverter is

$$C_{in,n-th} = x^{n-1}C$$

For the 1st~($n-1$)th inverters, the time constant is $\tau = xCR$

For the n -th inverter, the time constant is $\tau_n = C_L R / x^{n-1}$

To have the minimum delay (will be verified later),

$$\tau_n = \tau \Rightarrow x^n = \frac{C_L}{C}$$

The total propagation delay is $t_p = n \cdot x \cdot CR$

$$t_P = (n-1)xRC + \frac{1}{x^{n-1}}RC_L \quad \text{Q.E.D.} \quad (1)$$

(b) Differentiating t_P in Eq. (1) relative to x gives

$$\frac{\partial t_P}{\partial x} = (n-1)RC - \frac{(n-1)}{x^n}RC_L$$

Equating $\frac{\partial t_P}{\partial x}$ to zero gives

$$x^n = \frac{C_L}{C} \quad \text{Q.E.D.} \quad (2)$$

(c) Differentiating t_P in Eq. (1) relative to n gives

$$\frac{\partial t_P}{\partial n} = xRC - \frac{1}{x^{n-1}}(\ln x)RC_L$$

Equating $\frac{\partial t_P}{\partial n}$ to zero gives

$$x^n \left(\frac{C}{C_L} \right) = \ln x \quad \text{Q.E.D.} \quad (3)$$

To obtain the value of x for optimum performance, we combine the two optimality conditions in (2) and (3). Thus

$$\ln x = 1$$

$$\Rightarrow x = e \quad \text{Q.E.D.}$$

$$\mathbf{x=e=2.718}$$

In practice, $x=2.5\sim 4$

Example 15.8 Design an inverter chain to drive a large load capacitance

An inverter has an input capacitance $C=10\text{fF}$ and an equivalent output resistance $R=1\text{k}\Omega$ to drive a load capacitance $C_L=1\text{pF}$.

1. An inverter directly drives a C_L . The propagation delay is around

$$t_p = C_L R = 1\text{ns}$$

2. An inverter chain is selected to drive C_L .

$$x^n = \frac{C_L}{C} = 100 \Rightarrow \text{if } x = e = 2.718, \text{ then } n = 4.6$$

Assume $n=5$,

$$x^5 = \frac{C_L}{C} = 100 \Rightarrow \text{if } x = 2.51$$


The total propagation delay is

$$t_p = n \cdot x \cdot CR = 5 \cdot 2.51 \cdot (10 \cdot 10^{-15}) \cdot 1\text{k} = 125.5\text{ps}$$


It reduces the total propagation delay by a factor of about 8.

15.6 Power Dissipation

15.6.1 Sources of Power Dissipation

 


 1. When v_I is low, Q is off. → No power dissipation
2. When v_I is high, Q is on. The power is around V_{DD}^2 / R
3. If the inverter is not switching, the power dissipates. → **Static Power Dissipation**



1. If the inverter is not switching → no **Static Power Dissipation**
2. If the inverter switching, the current will charge or discharge the load capacitance.
→ **Dynamic Power Dissipation**

 1. When v_I is low, Q_P (or R_{PU}) is active.



$$P_{DD}(t) = V_{DD} \cdot i_D(t)$$

Within a charging time T_C , the power supply delivered the energy to the load is

$$E_{DD} = \int_0^{T_C} V_{DD} \cdot i_D(t) dt = V_{DD} \int_0^{T_C} i_D(t) dt = V_{DD} \cdot Q$$

Assume the initial voltage on C is zero, the charge Q is


$$Q = V_{DD} \cdot C \Rightarrow E_{DD} = C \cdot V_{DD}^2$$

At the end of the charging process, the energy stored on C is


$$E_{stored} = \frac{C \cdot V_{DD}^2}{2}$$

The energy dissipated in the pull-up switch is
 
$$E_{dissipated} = E_{DD} - E_{stored} = \frac{C \cdot V_{DD}^2}{2}$$



(a)

 

2. When v_I is high, Q_N (or R_{PD}) is active. The energy dissipated in the pull-down switch is

$$C \cdot V_{DD}^2 / 2$$

Thus, the total energy dissipated per cycle is

$$E_{dissipated} / cycle = C \cdot V_{DD}^2$$

If the inverter is switching at the frequency of f Hz, the dynamic power dissipation of the inverter


$$P_{dyn} = f \cdot C \cdot V_{DD}^2$$

To reduce the dynamic power, C or/and V_{DD} must be reduced.

 3. Another power dissipation results from the current flows through Q_N and Q_P during the switching. The current versus v_I is given for a matched inverter. The peak current occurs at $v_I = V_{DD} / 2$.

$$I_{peak} = \frac{\mu_n C_{OX}}{2} \left(\frac{W}{L} \right)_n \left(\frac{V_{DD}}{2} - V_{tn} \right)^2$$

The width of the current pulse depends upon the rate of change of v_I with time. In general, this power is less than P_{dyn} .



15.6.2 Power–Delay and Energy-Delay Products

The power dissipation of an inverter is P_D . Power–Delay Product (PDP) of the inverter is

$$PDP = P_D \cdot t_P$$

Assume the static power dissipation of an inverter is zero. Then, P_D will be equal to the dynamic power dissipation P_{dyn} .

$$P_{dyn} = f \cdot C \cdot V_{DD}^2 = P_D \Rightarrow PDP = f \cdot C \cdot V_{DD}^2 \cdot t_P$$

When the inverter is operated at the maximum switching speed; i.e., $f=1/(2t_P)$.

$$PDP = \frac{1}{2} \cdot C \cdot V_{DD}^2$$

PDP → It is the energy consumed by the inverter for each output transition.

One can reduce V_{DD} to minimize PDP. But, it may not be true since t_P is increased while V_{DD} is reduced. So, Energy-Delay Product (EDP) is better and given as

$$EDP = \text{Energy per transition} \times t_P = \frac{1}{2} \cdot C \cdot V_{DD}^2 \cdot t_P$$