

Advanced Phase-Locked Loops




National Taiwan University
Department of Electrical Engineering
& Graduate Institute of Electronics Engineering

Issues in PLLs

Crystal Oscillator

1. Low power
2. Fast start-up, Low start-up energy

MEMS Oscillator

 

Low Noise PLLs


How to reduce the phase noise or jitters of PLLs in SOC's

Several solutions

- **Multiplying Delay-Locked Loop**
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture

Multiplying Delay-Locked Loop (I)



Ring Oscillator

 

Noise is accumulated

This is at least 2.5 higher than PLLs' highest bandwidth ($f_{REF}/10$).

MDLL

  


Accumulated Noise reduced

IEEE JSSC, pp. 1416-, June 2013

ISSCC, Feb. 2012

Multiplying Delay-Locked Loop (II)

 

Recirculating DLL


IEEE JSSC, pp. 1759-, Dec. 2002
IEEE JSSC, pp. 1804-, Dec. 2002
IEEE JSSC, pp. 1222-, Aug. 2004

Low Noise PLLs


Several solutions

- Multiplying Delay-Locked Loop
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture

Noises in Fractional-N PLLs

 

Noises Vs. PLL's Bandwidth

 


- $OSR_{eff} \sim f_{ref} / (2f_{BW})$

$\Delta\Sigma$ quantization noise will degrade the PN.




IEEE JSSC, pp. 2426-, Sep. 2009

FIR-Embedded Noise Filtering Method

 

IEEE JSSC, pp. 2426-, Sep. 2009


Noise Filtering in Wideband PLL

   

$$H(Z) = (1 + Z^{-n} + \dots + Z^{-(k-1)n})/k$$

$\Delta\Sigma$ quantization noise multiplied by $H(z)$

PLL with FIR-Embedded Phase Interpolator

 


ISSCC, Feb. 2011

IEEE JSSC, pp.
2795-, Sep. 2013

$\Delta\Sigma$ quantization noise multiplied by an FIR filter

 All-Digital FIR-Embedded Noise Filtering (I)




$$D_0[k] \frac{(-7 + z^{-1} + z^{-2} + z^{-3} + z^{-4} + z^{-5} + z^{-6} + z^{-7})}{8} + D_0[k]$$

$$= D_0[k] \cdot \frac{(1 + z^{-1} + z^{-2} + z^{-3} + z^{-4} + z^{-5} + z^{-6} + z^{-7})}{8}$$


IEEE T-CAS-II, pp. 267-, May 2012

 All-Digital FIR-Embedded Noise Filtering (II)



$$\Phi_{out} = \frac{H(z)}{1+H(z)} \cdot D_0[k] \cdot \frac{2\pi z^{-1}}{1-z^{-1}} \cdot \frac{1}{8} (1 + z^{-1} + z^{-2} + z^{-3} + z^{-4} + z^{-5} + z^{-6} + z^{-7})$$


Fractional-N PLL with a Noise Filter

 

$\Delta\Sigma$ quantization noise multiplied by $H_{NF}(s)$

IEEE T-CAS-II, pp. 139-, March 2011

Fractional-N PLL with a Nested PLL

 

- Feedback divider is split to increase the operating frequency of the DSM
- Suppress quantization noise





IEEE JSSC, pp. 2433-, Oct. 2012

Low Noise PLLs

Several solutions

- Multiplying Delay-Locked Loop
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture

    
Sub-harmonically Injection-Locked Technique




Realigned PLL

IEEE JSSC, pp. 1759-, Dec. 2002
IEEE JSSC, pp. 1539-, May 2009
IEEE TCAS-I, pp. 355-, Jan. 2019

Sub-harmonically Injection-Locked PLLs


 


Can it be automatically controlled?

 


IEEE JSSC, pp. 1539-, May 2009

Injection Timing Issue

  


 A PLL with Self-Calibrated Injection Timing




- Calibrate the CP current mismatch to reduce the static phase error
- Calibrate the injection timing to tolerate the process variations



IEEE JSSC, pp. 417-, Feb. 2013

 

Dual-Pulse Ring Oscillator (DPRO) (I)

 



(a)

  

Even inverters --> the loop will not oscillate

DPRO is considered as perfect replica VCOs

Dual-Pulse Ring Oscillator (DPRO) (II)

  


IEEE JSSC, pp. 2989-, Dec. 2012

Low Noise PLLs


Several solutions

- Multiplying Delay-Locked Loop
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture

Conceptual Sub-Sampling PD

 


(a)

 

(b)



IEEE JSSC, pp. 3253-, Dec. 2009

High-Gain Sub-Sampling PD

 

IEEE JSSC, pp. 3253-, Dec. 2009

A PLL Using A Sub-Sampling PD

  


Why low noise?

 1. Dividerless in Locking
2. High-Gain PD


IEEE JSSC, pp. 3253-, Dec. 2009

An Injection-Locked PLL with Self-Aligned Injection (I)



ISSCC, pp.90-91, Feb. 2011


 
An Injection-Locked PLL with Self-Aligned Injection (II)




ISSCC, pp.90-91, Feb. 2011

An Injection-Locked PLL with Self-Aligned Injection (III)

  - Selected VCO architecture for injection
- Defining β as the injection strength
 - $0.83 < \beta < 0.91$ in this work



 


Low Noise PLLs

Several solutions


- Multiplying Delay-Locked Loop
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture

PLL Noise Analysis (I)

 

IEEE JSSC, pp. 2566-, Dec. 2010

PLL Noise Analysis (II)

 


Increasing I_{pump} reduces Input-Referred Loop Filter Noise, but Open Loop Gain increases.

Area gets larger since C_2 is typically increased to maintain desired open loop gain

IEEE JSSC, pp. 2566-, Dec. 2010


PLL Noise Analysis (III)

 

But how do we increase the PD gain?





IEEE JSSC, pp. 2566-, Dec. 2010

Phase Gain of a Classical Tristate PFD

 

IEEE JSSC, pp. 2566-, Dec. 2010

High Gain Phase Detector

   
 


- Reduce phase detection range to 1/4 of the Ref period
 - Achieves 8X increase in phase detector gain


IEEE JSSC, pp. 2566-, Dec. 2010

A High-Gain PFD

  Delay Buffer For Non-Overlapping Up/Down Pulses




Phase Detector Characteristic

 


IEEE JSSC, pp. 2566-, Dec. 2010

Phase-to-Voltage Converter

 


 Phase-error pre-amplification to enable reduction of PLL in-band phase noise floor





IEEE JSSC, pp. 2079-, Sept. 2008

Aperture Phase Detector

 


Aperture Phase Detector

  


IEEE TCAS-I, pp. 37-, Jan. 2013

Phase-to-Analog Converter


 


(a)

 

(b)

Phase-to-Analog Converter

  


Low Noise PLLs

Several solutions

- Multiplying Delay-Locked Loop
- Noise filter: embedded FIR filter
- Sub-harmonically Injection-locked Technique
- Sub-sampling PD
- High-gain PFD
- Dual-Loop Hybrid Architecture


Dual-Loop Hybrid Architecture

 

- High BW analog PLL suppresses VCO noise
- Digital PLL achieves low BW with area efficient digital LF

ISSCC, Feb. 2006

Detail Circuit Block Diagram

 


Limited digital code $\Rightarrow$ Low frequency resolution

$\Delta-\Sigma$ modulator + fractional divider $\Rightarrow$ fine resolution


ISSCC, Feb. 2006

Hybrid PLL Architecture

 



ISSCC, pp. 98-. Feb. 2011

Thee-input PFD

 

ISSCC, pp. 98-. Feb. 2011

Dual-Tuning Architecture (I)

 
 


Pros: CP/LPF noise can be suppressed by integrator and lowering fine-path gain K_F . Coarse path achieves wide tracking range.

Cons: Limitation of lowering K_F because of stability.



ISSCC, pp. 248-, Feb. 2012

Dual-Tuning Architecture (II)

  

ISSCC, pp. 248-, Feb. 2012


Dual-Tuning Architecture (III)

  

$$\begin{aligned}
 H(s) &= H_F(s) + H'_{CA}(s) \\
 &= H_F(s) + \frac{H_F(s)}{K_F} H_{CA}(s) \\
 \left(H_{CA}(s) &= \frac{\omega_{IA} \cdot K_C}{s} \right)
 \end{aligned}$$


ISSCC, pp. 248-, Feb. 2012

Dual-Tuning Architecture (IV)

 

$$H(s) = H_F(s) \cdot \left(\frac{s + \omega_{IA} (K_C / K_F)}{s} \right)$$

 $H(s)$ has three poles at origin. $\rightarrow$ **Type-III**



ISSCC, pp. 248-, Feb. 2012

Design Constraint for Sufficient Stability

Our design has

$$K_C = 10\text{GHz/V} \quad f_{\text{REF}} = 10\text{MHz}$$

$$f_c = 1\text{MHz}$$

$$f_z = 100\text{kHz}$$

$$f_{zc} = f_{IA}(K_C/K_F) = 10\text{kHz}$$


(for sufficient phase margin)

If $K_F = 10\text{MHz/V}$,


f_{IA} must be set to 10Hz!!!

Quite tough for CMOS design

 (e.g. **>1nF capacitor** for
1uS conventional Gm-C filter.)



Digitally Stabilized DT-PLL

 

- Digital coarse path greatly improves PLL stability.
- Coarse path always keeps V_{ctl} between V_L and V_H .