

Chapter 10 Integer-N Frequency Synthesizers

- **10.1 General Considerations**
- **10.2 Basic Integer-N Synthesizers**
- **10.3 Settling Behavior**
- **10.4 Spur Reduction Techniques**
- **10.5 PLL-Based Modulation**
- **10.6 Divider Design**
- **13.4 Synthesizer Design**
- **Simulations of PLL Transfer Function**

Chapter Outline

Basic Synthesizer

- ✓ Settling Behavior
- ✓ Spur Reduction Techniques

PLL-Based Modulation

- ✓ In-Loop Modulation
- ✓ Offset-PLL TX


Divider Design

- ✓ Pulse-Swallow Divider
- ✓ Dual-Modulus Dividers
- ✓ CML and TSPC Techniques
- ✓ Miller and Injection-Locked Dividers




- Synthesizer Design
- Simulations of PLL Transfer Function

 General Considerations: Why We Need Synthesizers?




 - The synthesizer performs the precise setting of LO frequency






- A slight shift leads to significant spillage of a high-power interferer into a desired channel

Reciprocal Mixing

 

   
- The output frequency is generated as a multiple of a precise reference.
- Sidebands: upon downconversion mixing, the desired channel is convolved with the carrier and the interferer with the sideband



$$\omega_o - \omega_{LO} = \omega_{int} - \omega_s \equiv \omega_{IF}$$


Lock Time

Synthesizer
Output Frequency

 


- Lock time directly subtracts from the time available for communication

Synthesizer
Output Frequency

 


- The lock time is typically specified as the time required for the output frequency to reach within a certain margin around its final value

Basic Integer-N Synthesizer

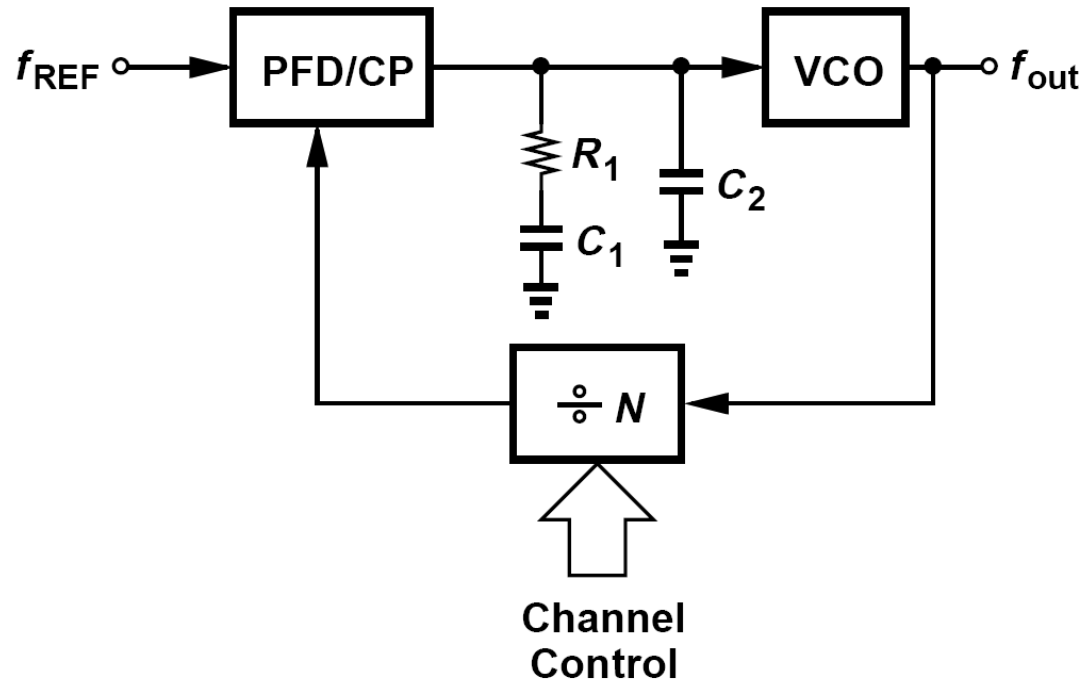

- Integer- N synthesizer produce an output frequency that is an integer multiple of the reference frequency.
- The choice of f_{REF} : it must be equal to the desired channel spacing and it must be the greatest common divisor of f_1 and f_2 .

Settling Behavior: Channel Switching

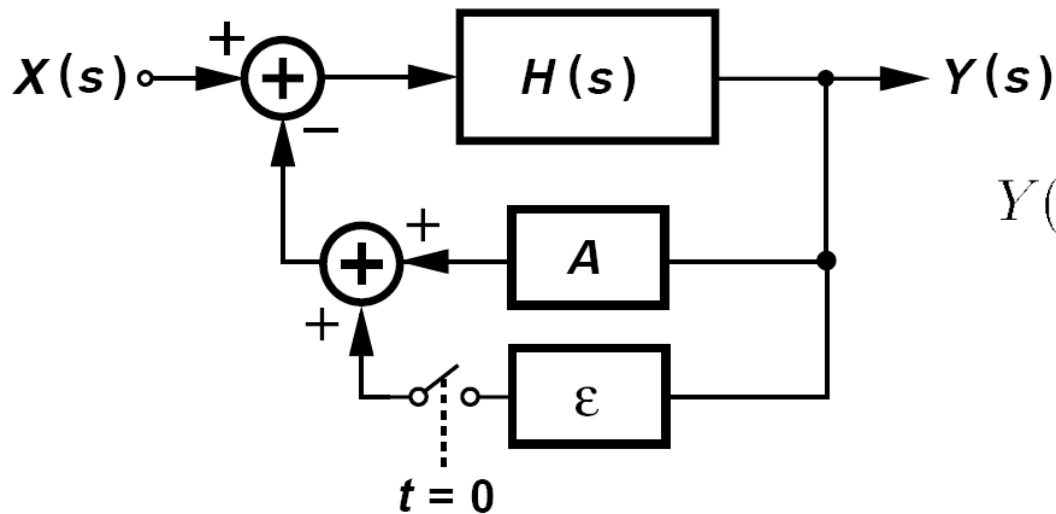


$$\begin{aligned}
 Y(s) &= \frac{H(s)}{1 + (A + \epsilon)H(s)} X(s) \\
 &\approx \frac{H(s)}{1 + AH(s)} \cdot \frac{1}{1 + \epsilon/A} X(s) \\
 &\approx \frac{H(s)}{1 + AH(s)} \left(1 - \frac{\epsilon}{A}\right) X(s)
 \end{aligned}$$

Retaining the transfer function, an equivalent multiplication by $(1 - \epsilon/A)$ as a step function from f_0 to $f_0(1 - \epsilon/A)$, i.e., a frequency jump of $-(\epsilon/A)f_0$.

- When the divide ratio changes, the loop responds as if an input frequency step was applied

Worst Case Settling and Example of Error

 

- The worse case occurs when the synthesizer output frequency must go from the first channel, $N_1 f_{REF}$, to the last, $N_2 f_{REF}$, or vice versa

In synthesizer settling, the quantity of interest is the frequency error, $\Delta\omega_{out}$, with respect to the final value. Determine the transfer function from the input frequency to this error.

The error is equal to $\omega_{in}[N - H(s)]$, where $H(s)$ is the transfer function of a type-II PLL (Chapter 9). Thus,

$$\frac{\phi_{out}}{\phi_{in}}(s) = \frac{\omega_{out}}{\omega_{in}}(s) = H(s) = N \frac{2s\zeta\omega_n + \omega_n^2}{s^2 + 2s\zeta\omega_n + \omega_n^2}$$

$$\frac{\Delta\omega_{out}}{\omega_{in}} = N \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Calculation of Settling Time

Assuming $N_2 - N_1 \ll N_1$. If the divide ratio jumps from N_1 to N_2 , this change is equivalent to an input frequency step of $\Delta\omega_{in} = (N_2 - N_1)\omega_{REF}/N_1$. The settling time should be normalized by the output frequency $N_2\omega_{REF}$. The normalized error to fall below a certain amount, α , will be

$$\left| \frac{\omega_{ref}(N_2 - N_1) - \Delta\omega_{out}}{\omega_{out,final}} \right| \equiv \left| \frac{\omega_{ref}(N_2 - N_1) - \frac{(N_2 - N_1)\omega_{ref}}{N_1} H(s)}{N_2\omega_{ref}} \right| \leq \alpha, \quad H(s) = N_1 \frac{2s\zeta\omega_n + \omega_n^2}{s^2 + 2s\zeta\omega_n + \omega_n^2}$$

$$\Rightarrow \left| 1 - \frac{N_1}{N_2} \right| \cdot \left| 1 - \frac{H(s)}{N_1} \right| \leq \alpha$$

$$\left| 1 - \frac{N_1}{N_2} \right| g(t) u(t) \leq \alpha, \quad g(t) = e^{-\zeta\omega_n t} \left[\cos(\omega_n \sqrt{1-\zeta^2} \cdot t) - \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_n \sqrt{1-\zeta^2} \cdot t) \right], \quad \zeta < 1 \quad (10.8)$$

For example, if $\zeta = \sqrt{2}/2$, $\left| 1 - \frac{N_1}{N_2} \right| \left(\cos \frac{\omega_n t_s}{\sqrt{2}} - \sin \frac{\omega_n t_s}{\sqrt{2}} \right) e^{-\omega_n t_s / \sqrt{2}} = \alpha$.

$$\left| 1 - \frac{N_1}{N_2} \right| \sqrt{2} e^{-\omega_n t_s / \sqrt{2}} = \alpha \quad \Rightarrow \quad t_s = \frac{\sqrt{2}}{\omega_n} \ln \left| \sqrt{2} \left(1 - \frac{N_1}{N_2} \right) \frac{1}{\alpha} \right|$$

Example : Settling Time Calculation

A 900-MHz GSM synthesizer operates with $f_{REF} = 200$ kHz and provides 128 channels. If $\zeta = \sqrt{2}/2$, determine the settling time required for a frequency error of 10 ppm.

The divide ratio is approximately equal to 4500 and varies by 128, i.e., $N_1 \approx 4500$ and $N_2 - N_1 = 128$. Thus,


$$t_s \approx \sqrt{2} \frac{8.3}{\omega_n} \quad \text{or} \quad t_s = \frac{8.3}{\zeta \omega_n}$$

From Chapter 9, we note that the loop time constant is roughly equal to one-tenth of the input period. It follows that $(\zeta \omega_n)^{-1} \approx 10 T_{REF}$ and hence

$$t_s \approx 83 T_{REF}$$


In practice, the settling time is longer and a rule of thumb for the settling of PLLs is 100 times the reference period.

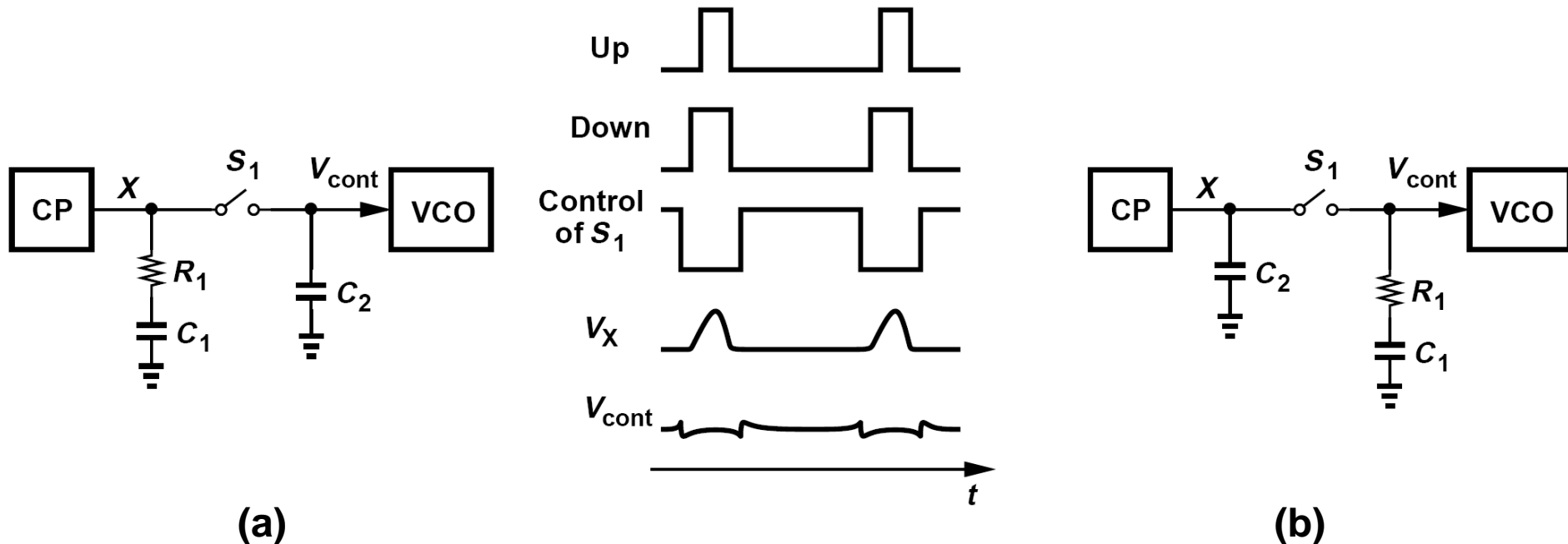Spur Reduction Techniques: Masking the Ripple by Insertion of a Switch



- V_{cont} is disturbed for a short duration (at the phase comparison instant) and remains relatively constant for the rest of the input period.
- The arrangement of (a) leads to an unstable PLL. (\because As V_X was settled, V_{cont} senses the voltage is independent of R_1 . R_1 has no function to serve as a zero)
- Topology of (b) can yield a stable PLL.

 Spur Reduction Techniques: Stabilization of PLL by Adding K_1 to the Transfer Function of VCO (I)



Open-loop transfer function of a type-II second-order PLL

$$H_{open}(s) = \frac{I_P}{2\pi} \left(R_1 + \frac{1}{C_1 s} \right) \frac{K_{VCO}}{s}$$

Can we realize:


$$H_{open}(s) = \frac{I_P}{2\pi} \frac{1}{C_1 s} \left(\frac{K_{VCO}}{s} + K_1 \right) \quad \text{to obtain a zero?}$$

$$\frac{\phi_1}{V_{cont}}(s) = \frac{K_{VCO}}{s} + K_1$$

Indeed, K_1 represents a variable-delay stage having a “gain” of K_1 :

$$K_1 = \frac{\Delta T_d}{\Delta V_{cont}}$$

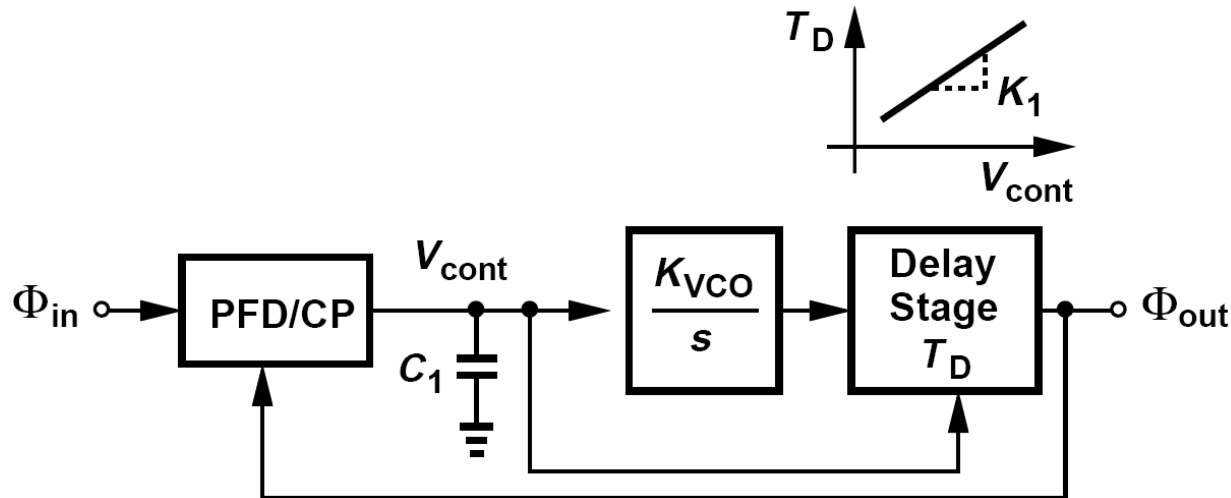
Stabilization of PLL by Adding K_1 to the Transfer Function of VCO (II)



$$\begin{aligned}
 H_{closed}(s) &= \frac{\frac{I_P}{2\pi C_1 s} \left(\frac{K_{VCO}}{s} + K_1 \right)}{1 + \frac{I_P}{2\pi C_1 s} \left(\frac{K_{VCO}}{s} + K_1 \right)} \\
 &= \frac{\frac{I_P K_1}{2\pi C_1} s + \frac{I_P K_{VCO}}{2\pi C_1}}{s^2 + \frac{I_P K_1}{2\pi C_1} s + \frac{I_P K_{VCO}}{2\pi C_1}}.
 \end{aligned}$$

$$\begin{aligned}
 \zeta &= \frac{K_1}{2} \sqrt{\frac{I_P}{2\pi C_1 K_{VCO}}} \\
 \omega_n &= \sqrt{\frac{I_P K_{VCO}}{2\pi C_1}}.
 \end{aligned}$$

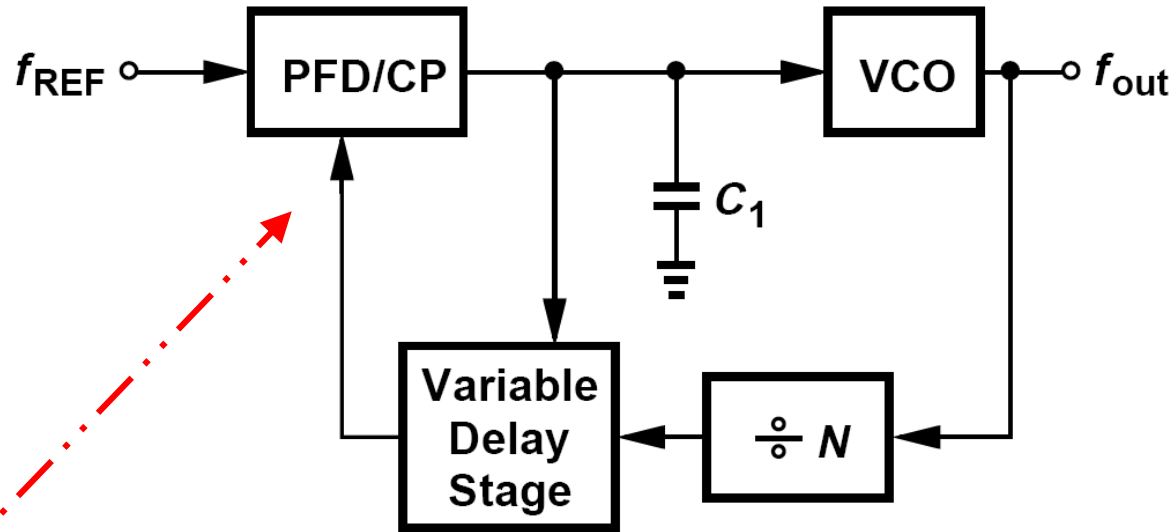
Stabilization of PLL by Adding K_1 to the Transfer Function of VCO: Modified Architecture




$$\zeta = \frac{K_1}{2} \sqrt{\frac{I_P N}{2\pi C_1 K_{VCO}}} \quad \omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_1 N}}.$$

- A retiming flip-flop can be inserted between the delay line and the PFD to remove the phase noise of the former

Noise Filtration by Means of a PLL

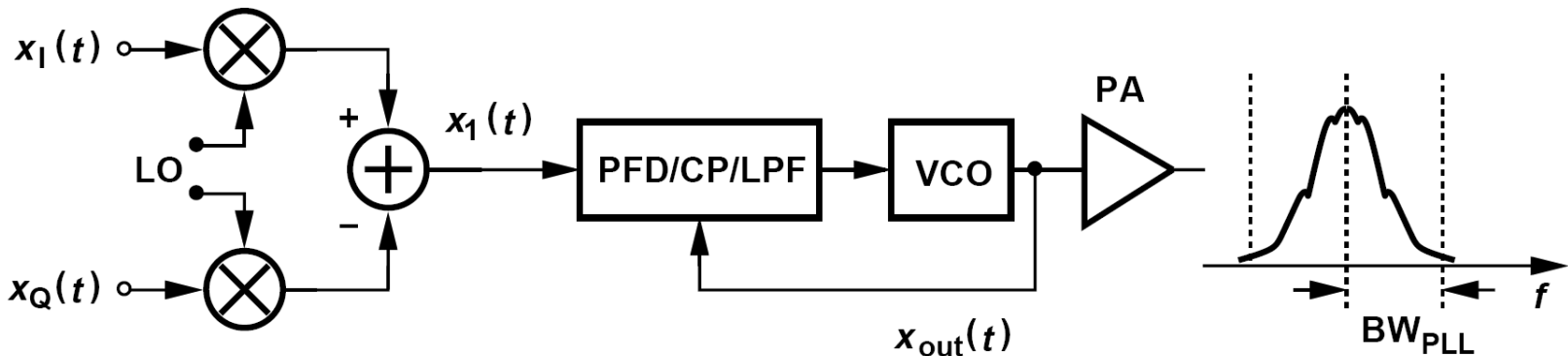

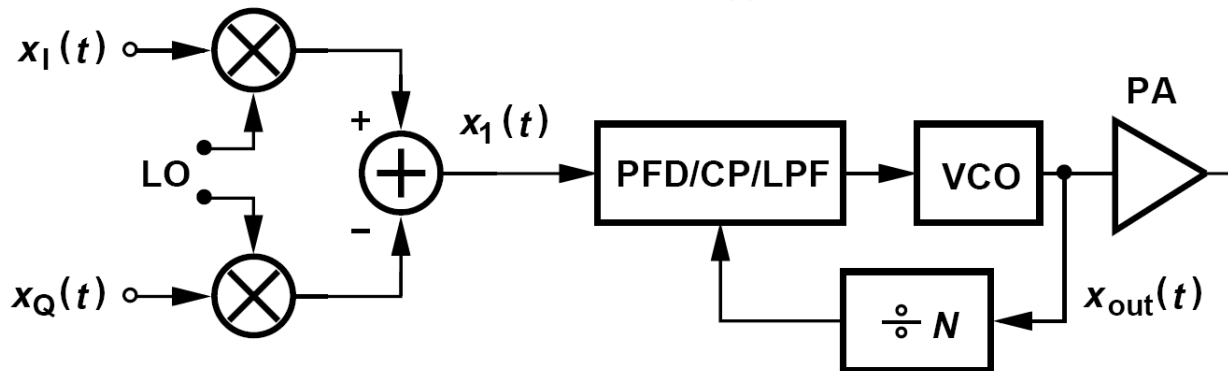
- $x_I(t)$ and $x_Q(t)$: quadrature baseband signals; LO: $A\cos(\omega_1 t)$ and $A\sin(\omega_1 t)$; $x_1(t) = A\cos(\omega_1 t + \phi(t))$; $x_{out}(t) = B\cos(N\omega_1 t + N\phi(t))$



$$x_1(t) = A_1 \cos[\omega_1 t + \phi(t)] \rightarrow x_{out}(t) = A_2 \cos[N\omega_1 t + N\phi(t)]$$

- The PLL multiplies the phase by a factor of N , altering the signal bandwidth and modulation

Offset-PLL Architecture

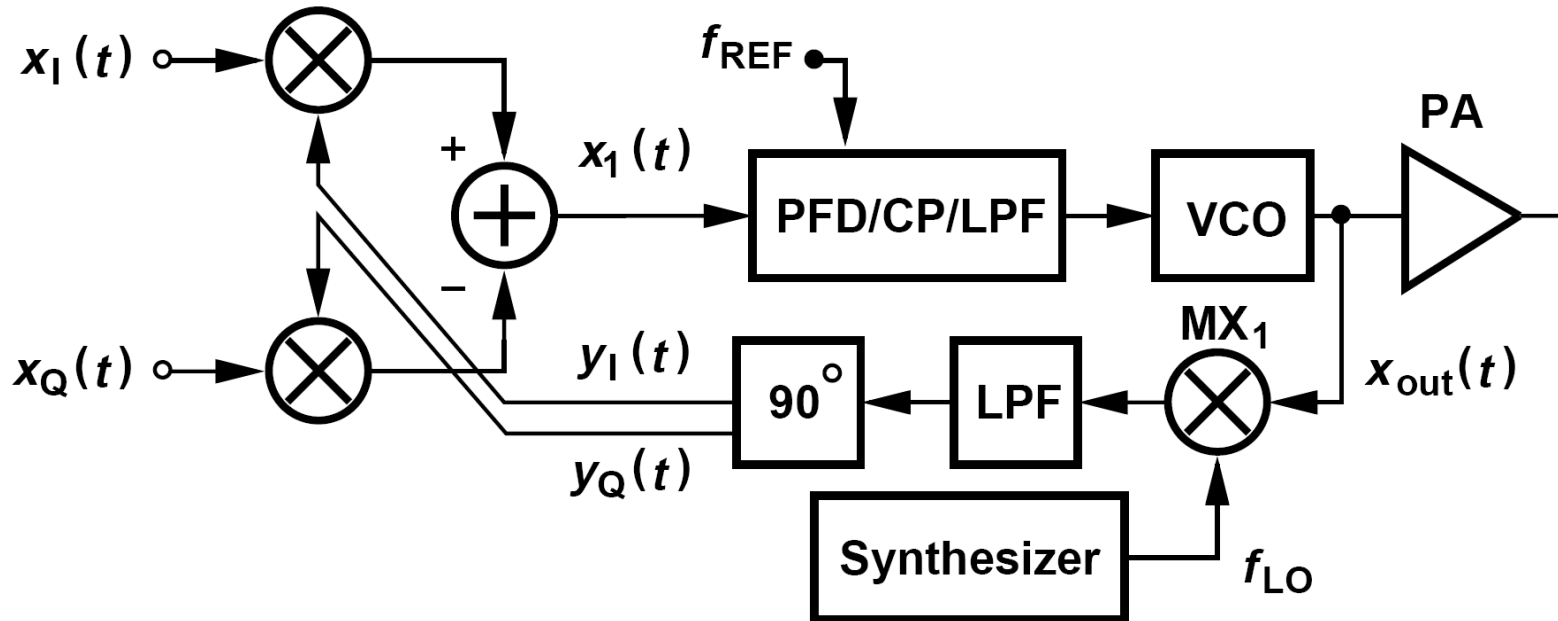

- With the loop locked, $x_1(t)$ must become a faithful replica of the reference input, thus containing no modulation. Consequently, $y_I(t)$ and $y_Q(t)$ “absorb” the modulation information of the baseband signal.

Example : Offset-PLL Architecture

If $x_I(t) = A \cos[\Phi(t)]$ and $x_Q(t) = A \sin[\Phi(t)]$,

Centered around f_{REF} , y_I and y_Q can be respectively expressed as

$$y_I(t) = a \cos[\omega_{REF}t + \phi_y(t)]$$

$$y_Q(t) = a \sin[\omega_{REF}t + \phi_y(t)],$$

where $\omega_{REF} = 2\pi f_{REF}$ and $\Phi_y(t)$ denotes the phase modulation information. Carrying the quadrature upconversion operation and equating the result to an unmodulated tone, $x_1(t) = A \cos \omega_{REF} t$, we have

$$A_1 a \cos[\phi(t)] \cos[\omega_{REF}t + \phi_y(t)] - A_1 a \sin[\phi(t)] \sin[\omega_{REF}t + \phi_y(t)] = A \cos \omega_{REF} t.$$

It follows that $A_1 a \cos[\omega_{REF}t + \phi(t) + \phi_y(t)] = A \cos \omega_{REF} t$


And hence

$$\phi_y(t) = -\phi(t)$$


Note that $x_{out}(t)$ also contains the same phase information $\Phi_y(t)$.

Divider Design: Requirements

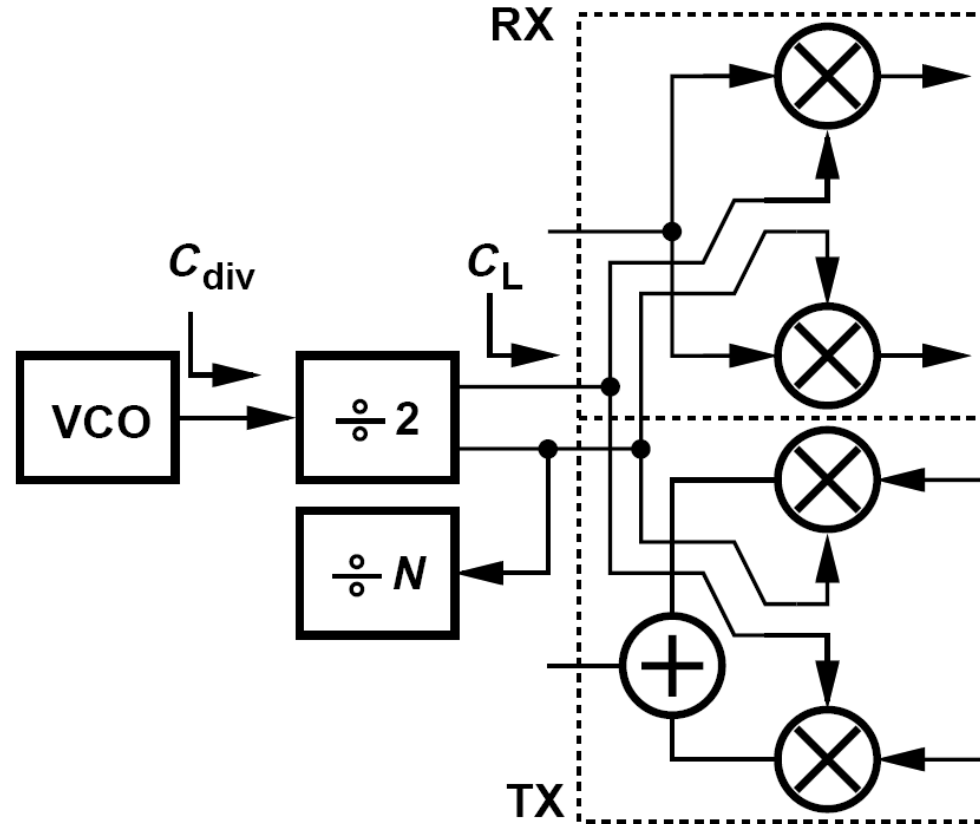- The divider modulus, N , must change in unity steps
- The first stage of the divider must operate as fast as the VCO
- The divider input capacitance and required input swing must be commensurate with the VCO drive capability
- The divider must consume low power, preferably less than the VCO




Pulse Swallow Divider

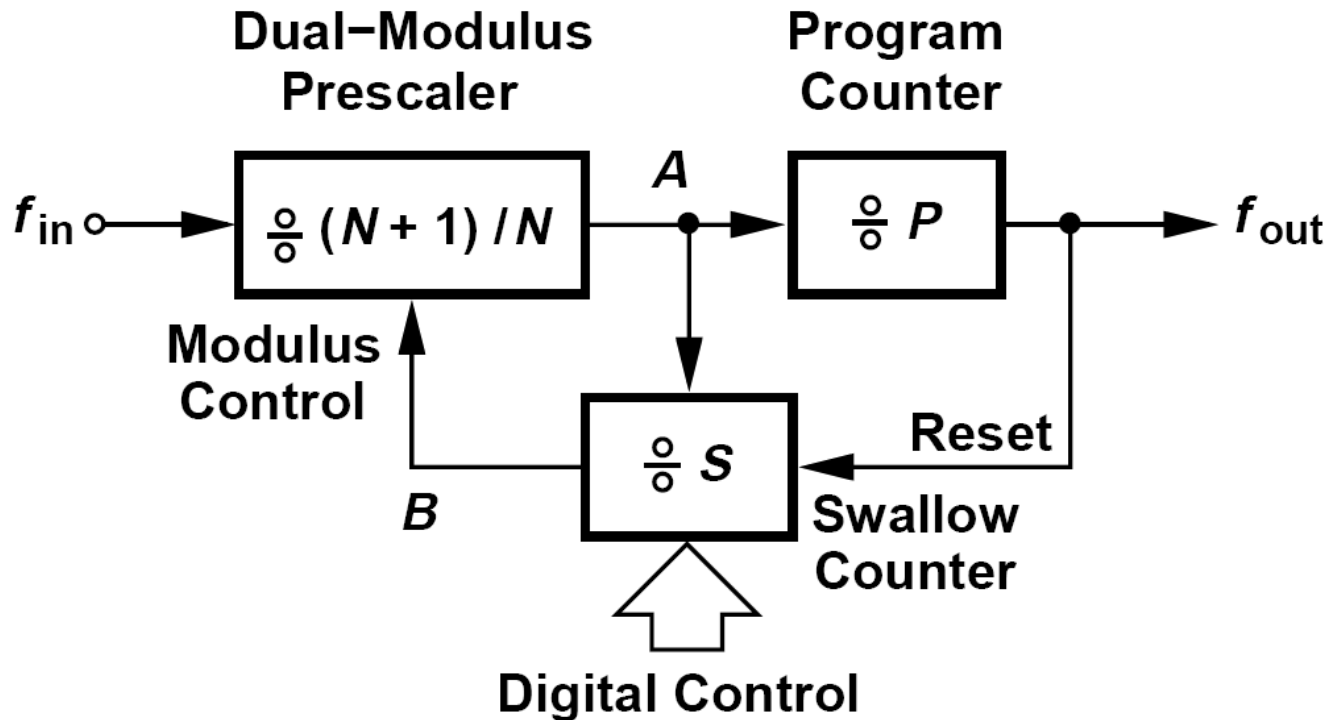


- Sensing the high-frequency input, the prescaler proves the most challenging of the three building blocks.
- **$S(N+1)+(P-S)N=NP+S$, $P>S$**
- As a rule of thumb, dual-modulus prescalers are about a factor of two slower than $\div 2$ circuits

Swallow Counter Realization

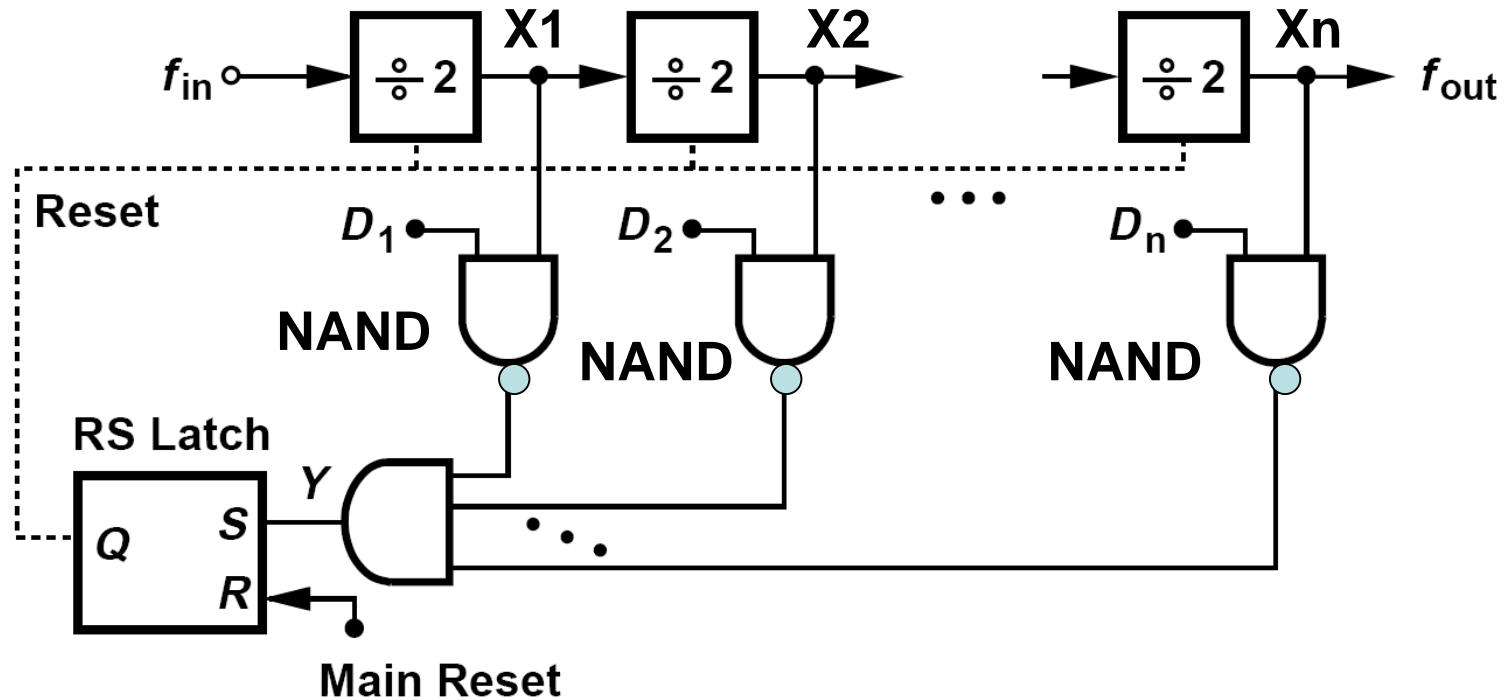


- The swallow counter is typically designed as an asynchronous circuit for the sake of simplicity and power saving
- initial $[X_4, \dots, X_1] = [1111]$, $[D_4, \dots, D_1] = [1000]$
 $[X_4, \dots, X_1] = 1111, 1110, 1101, 1100, 1011, 1010, 1001, 1000, 0111 \rightarrow Y = \text{High}$

 Modular Divider Realizing Multiple Divider Ratios




➤ This method incorporates $\div 2/3$ stages in a modular form so as to reduce the design complexity. Each $\div 2/3$ block receives a modulus control from the next stage. The digital inputs set the overall divide ratio according to:

2/3 CELL

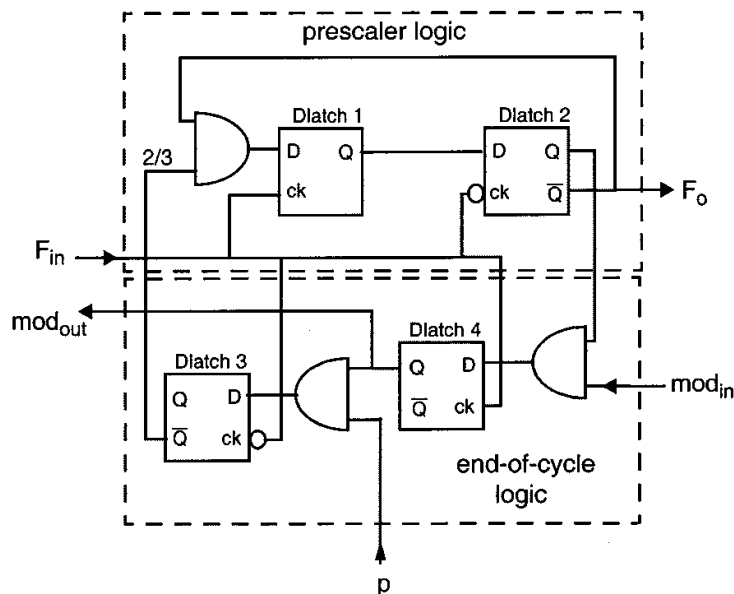

$$N = 2^n + D_n 2^{n-1} + D_{n-1} 2^{n-2} + \dots + 2D_2 + D_1$$

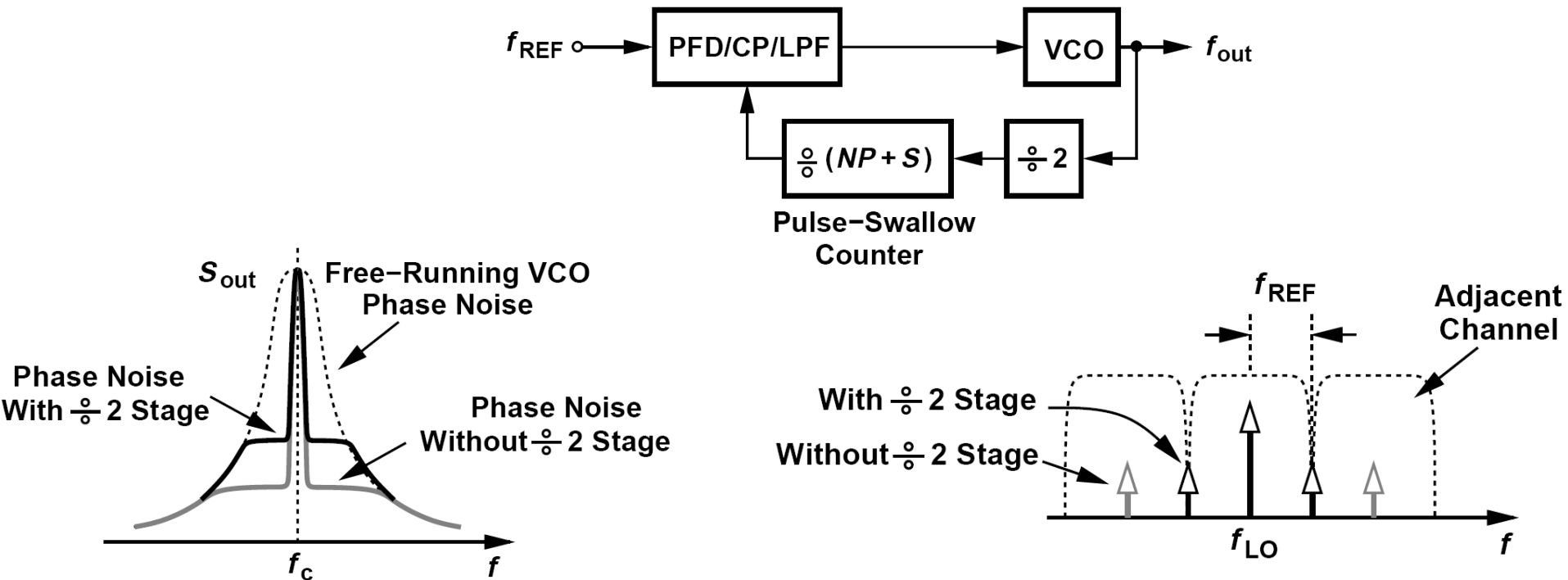
Example : Preceding the Pulse Swallow Divider by a $\div 2$



Here, $f_{out} = 2(NP + S)f_{REF}$. Thus, a channel spacing of f_{ch} dictates $f_{REF} = f_{ch}/2$. The lock speed and the loop bandwidth are therefore scaled down by a factor of two, making the VCO phase noise more pronounced. One advantage of this approach is that the reference sideband lies at the edge of the adjacent channel rather than in the middle of it.

Divide-by-3 Divider



Divide-by-3 Circuit:

 


Suppose the circuit begins with $Q_1\bar{Q}_2 = 00$. next three cycles, $Q_1\bar{Q}_2$ goes to 10, 11, and 01. Note that the state $Q_1\bar{Q}_2 = 00$ does not occur again because it would require the previous values of \bar{Q}_2 and X to be ZERO and ONE, respectively.

$$Q_1 \overline{Q_2} = 00 \rightarrow X = 0 \rightarrow Q_2 = 0, \overline{Q_2} = 1 \rightarrow \textcolor{red}{Q_1 \overline{Q_2} = 01}$$
$$\rightarrow Q_1 \overline{Q_2} = 11 \rightarrow X = 1 \rightarrow Q_2 = 1, \overline{Q_2} = 0 \rightarrow Q_1 \overline{Q_2} = 10 \rightarrow \mathbf{Q_1 \overline{Q_2} = 01}$$

  
Example : $A \div 3$ Circuit Using a NOR Gate rather than an AND Gate



(a)

 


(b)

 


The reader can prove that this circuit cycles through the following three states: $Q_1Q_2 = 00; 01; 10$.

Speed Limitation of the $\div 3$ Stage

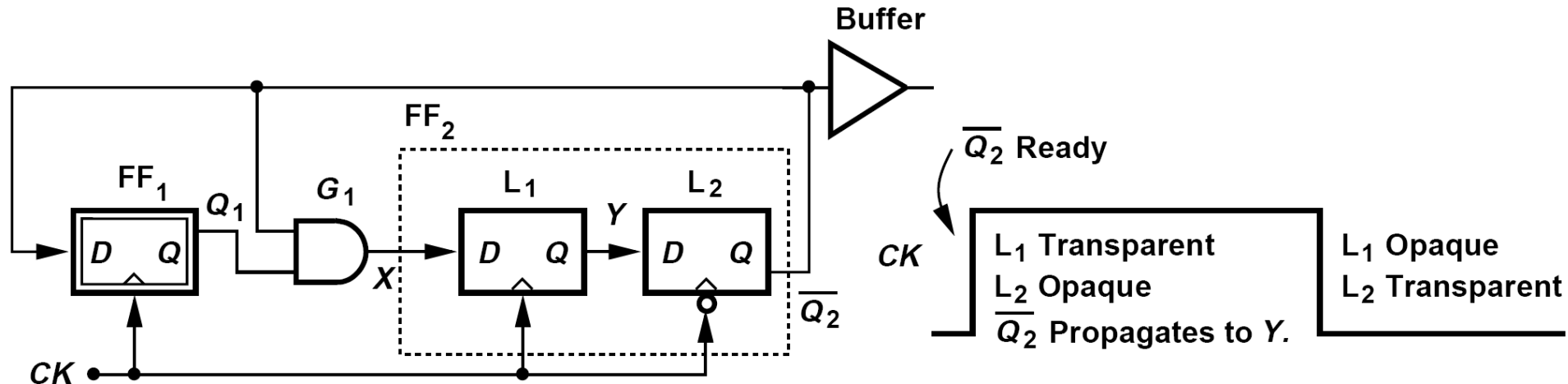


Suppose CK is initially low, L_1 is opaque (in the latch mode), and L_2 is transparent (in the sense mode). When CK goes high and L_1 begins to sense, the value of Q_2 must propagate through G_1 and L_1 before CK can fall again. Thus, the delay of G_1 enters the critical path. Moreover, L_2 must drive the input capacitance of FF_1 , G_1 , and an output buffer. These effects degrade the speed considerably, requiring that **CK remain high long enough for Q_2 to propagate to Y .**


Divide-by-2/3 Circuits

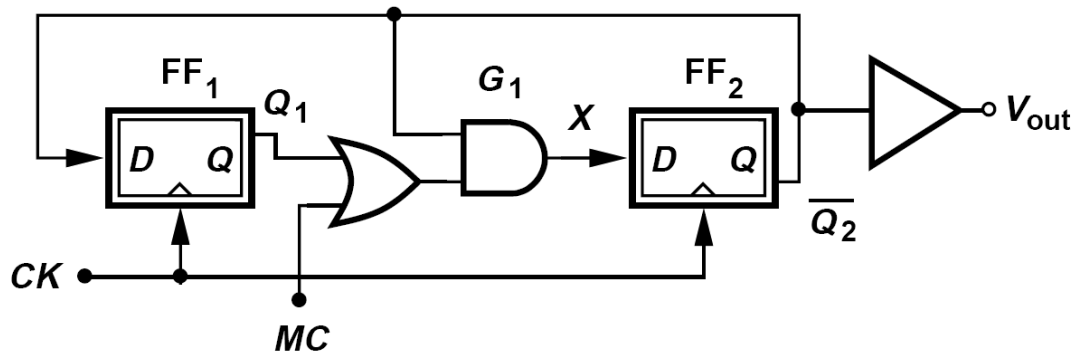

 ➤ The $\div 2/3$ circuit employs an OR gate to permit $\div 3$ operation if the modulus control, MC, is low or $\div 2$ operation if it is high.



 
➤ The output can be provided by only FF_1 . This circuit has a 40% speed advantage over previous $\div 2/3$ circuit by reducing the loadings of FF2




MC=0

➤ MC=1, Q2=0, \rightarrow DFF1 : Divide-by-two

 Divide-by-3/4 Circuit and Divide-by-8/9 Circuit




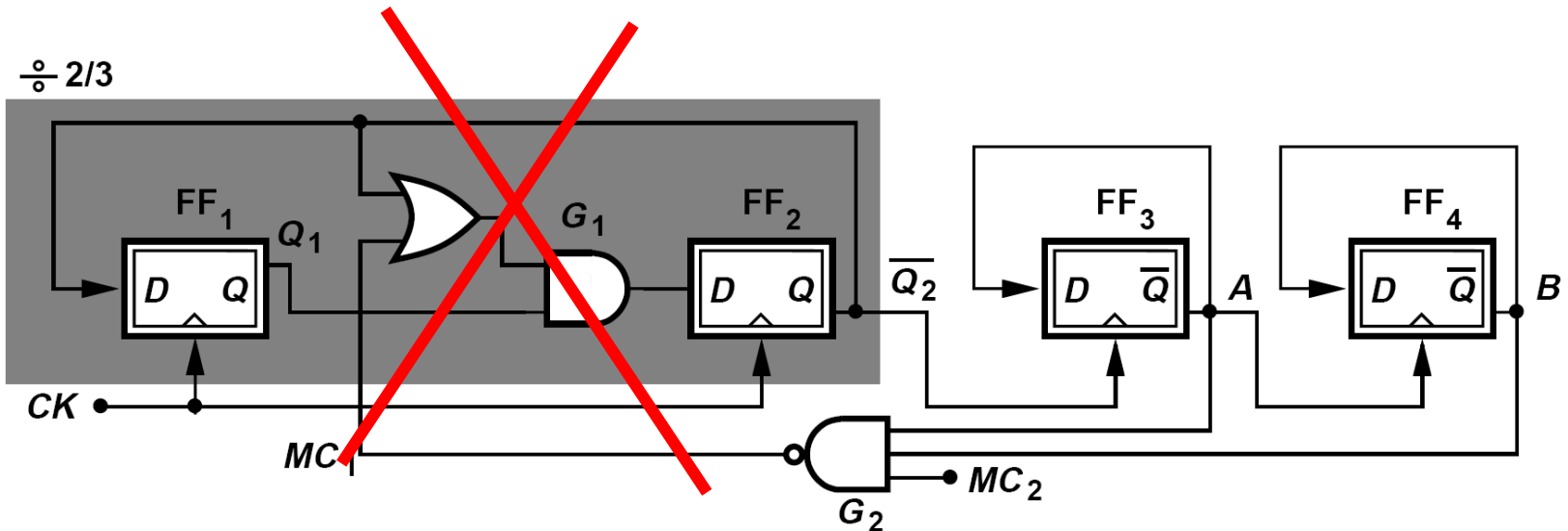- When $MC=1$, the circuit divides by 4;
- If $MC=0$, it divides by 3



- If MC_2 is low, MC_1 is high, the overall circuit operates as a $\div 8$ circuit; if MC_2 is high, the circuit divides by 9.

Example: a Divide-by-15/16 Circuit

 

Since the $\div 3/4$ stage (D34) divides by 4 when MC is high, we surmise that only two more $\div 2$ circuits must follow to provide $\div 16$. To create $\div 15$, we must force D34 to divide by 3 for one clock cycle. Shown in the figure above, the circuit senses **the outputs of the asynchronous $\div 2$ stages by an OR gate and lowers MF when $AB = 00$** . Thus, if MC is high, the circuit divides by 16. If MC is low and the $\div 2$ stages begin from 11, MF remains high and D34 divides by 4 until $AB = 00$. At this point, MF falls and D34 divides by 3 for one clock cycle before A goes high.

$\div 4$ three times & $\div 3$ once

$$4 \times 3 + 3 \times 1 = 15$$


Potential Race Conditions @ Divide-by-15

	Q_1	$\overline{Q_2}$	$\overline{Q_3}$	$\overline{Q_4}$			Q_1	$\overline{Q_2}$	$\overline{Q_3}$	$\overline{Q_4}$		
	0	0	1	0	←	Change in	0	0	1	1		
	0	1	0	0		$\overline{Q_3}$	0	1	1	1		
	1	1	0	0			1	1	1	1		
Skip State →	1	0	0	0			1	0	0	0	←	Change in
	0	1	1	1			0	1	0	0		$\overline{Q_3}$ and $\overline{Q_4}$

(a) (b)


- First suppose FF_3 and FF_4 change their output state on the rising edge of their clock inputs. If MC is low, the circuit continues to divide by 16. As in (a), state 00 ($Q_1\overline{Q_2}$) is skipped. The propagation delay through FF_3 and G_3 need not be less than a cycle of CK_{in}
- In the case (b), FF_3 and FF_4 change their output state on the falling edge of their clock inputs, the $\div 3/4$ circuit must skip the state 00. **The delay through FF_3 , FF_4 , and G_3 should be less than half of a CK_{in} cycle.** This is in general difficult to achieve and demands higher power dissipation. Thus the first choice is preferable.

Example : Choice of Prescaler Modulus

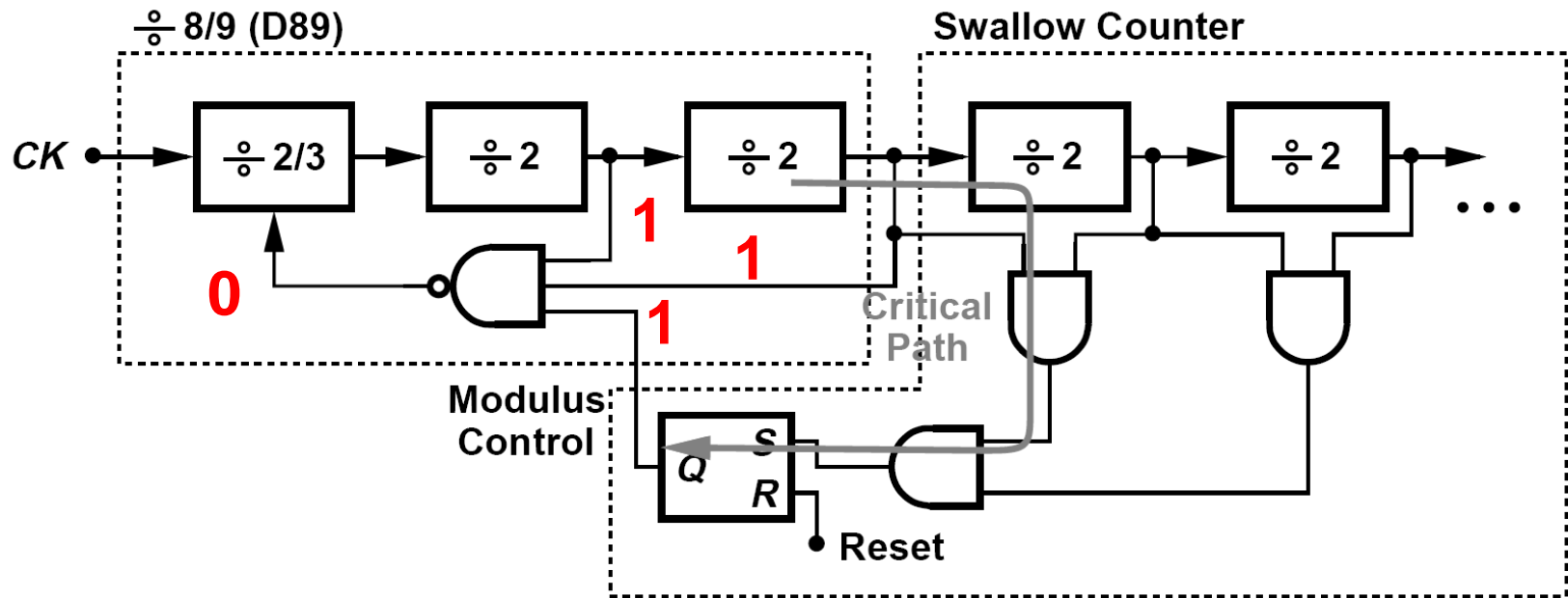


- The last pulse generated by the prescaler in the previous $\div 8$ mode (just before the $\div 9$ mode begins) must propagate through the first $\div 2$ stage in the swallow counter, the subsequent logic, and the RS latch in **fewer than seven input cycles**.
- **A large N** for the prescaler permits a long delay for an asynchronous stages and feedback loop, but it leads a higher power.

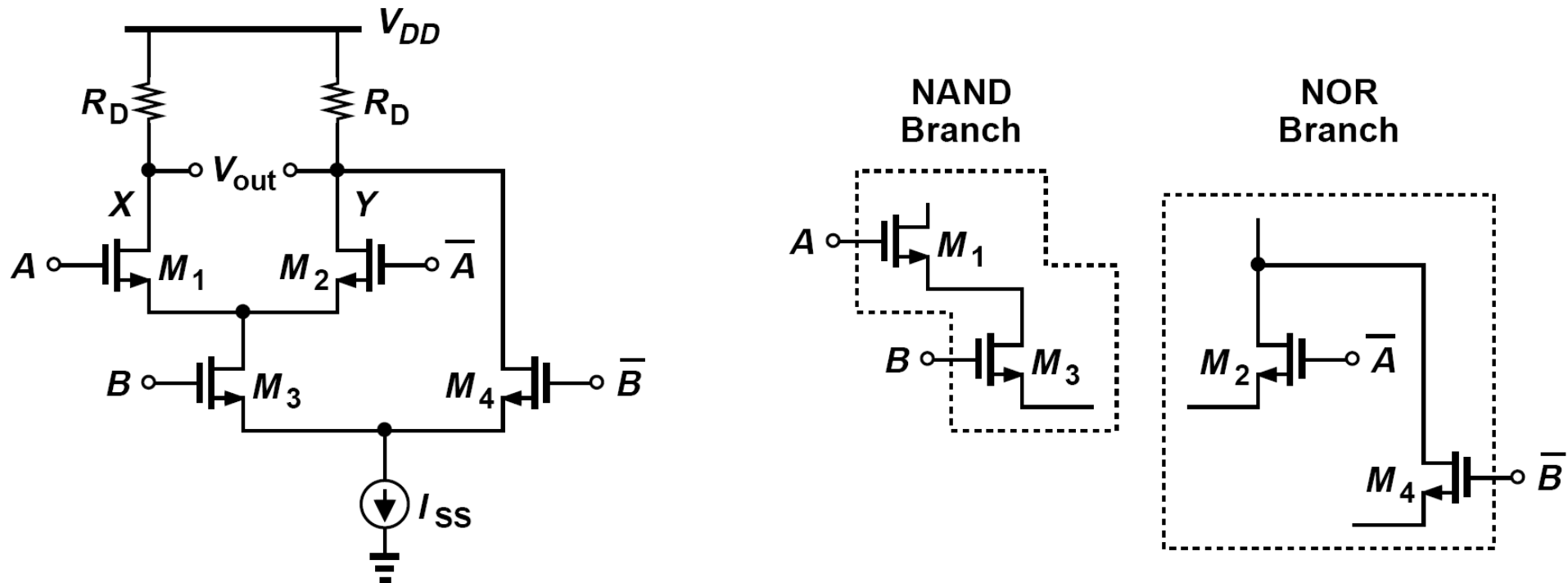Divider Logic Styles-Current Steering Circuit




- CML operates with moderate input and output swings, and provides differential outputs and hence a natural inversion.
- The circuit above is typically designed for a single-ended output swing of $R_D I_{SS} = 300\text{mV}$, and the transistors are sized such that they experience complete switching with such input swings

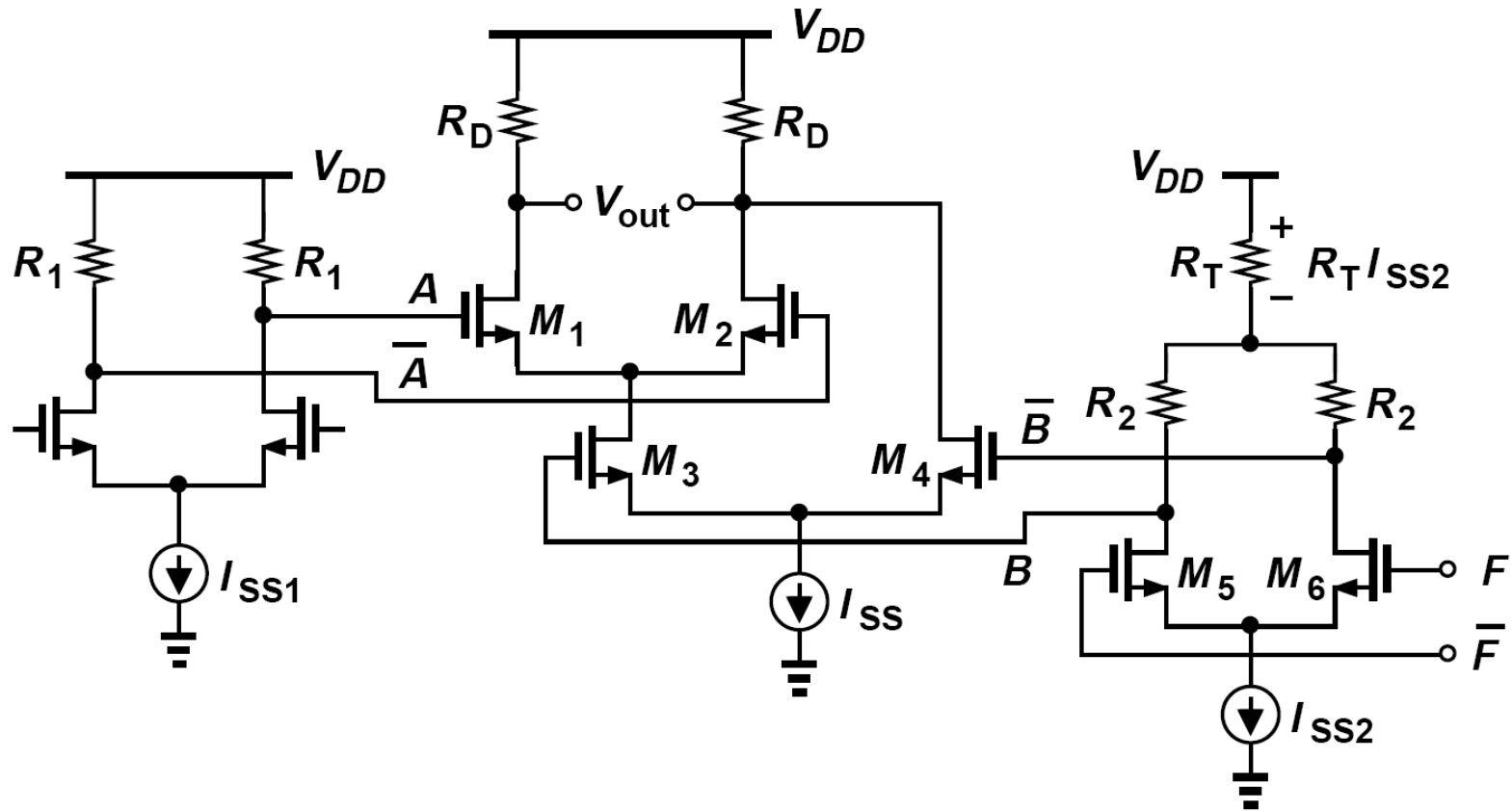Problem of Common-Mode Compatibility at NAND Inputs




- A and /A swing : V_{DD} and $V_{DD} - I_{SS1}R_1$
- B and /B swing: $V_{DD} - R_T I_{SS2} - R_2 I_{SS2}$ and $V_{DD} - R_T I_{SS2}$
- The high level of F and \bar{F} does not exceed $V_{DD} - R_T I_{SS2} - R_2 I_{SS2} + V_{TH}$ if M_5 and M_6 must not enter the triode region

Choice at Low Supply Voltages

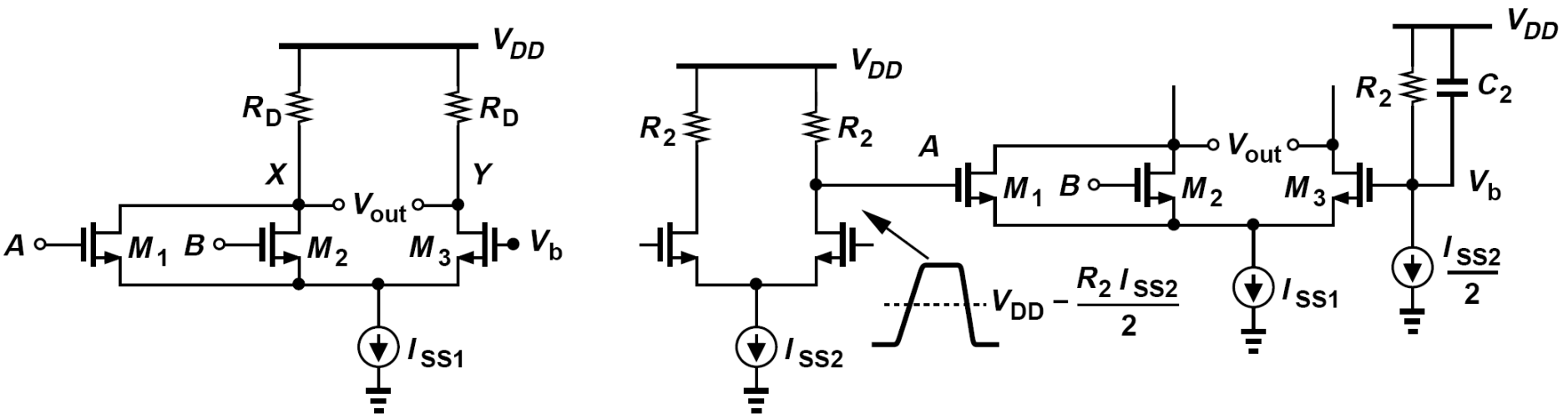


- The CML NOR/OR gate, avoid stacking. This stage operates only with single-ended inputs.
- the worst case occurs if only M_1 or M_2 is on. Thus, for either transistor to “overcome” M_3 , we require that the widths $W_1 = W_2 \geq W_3$.

CML XOR Implementation

 

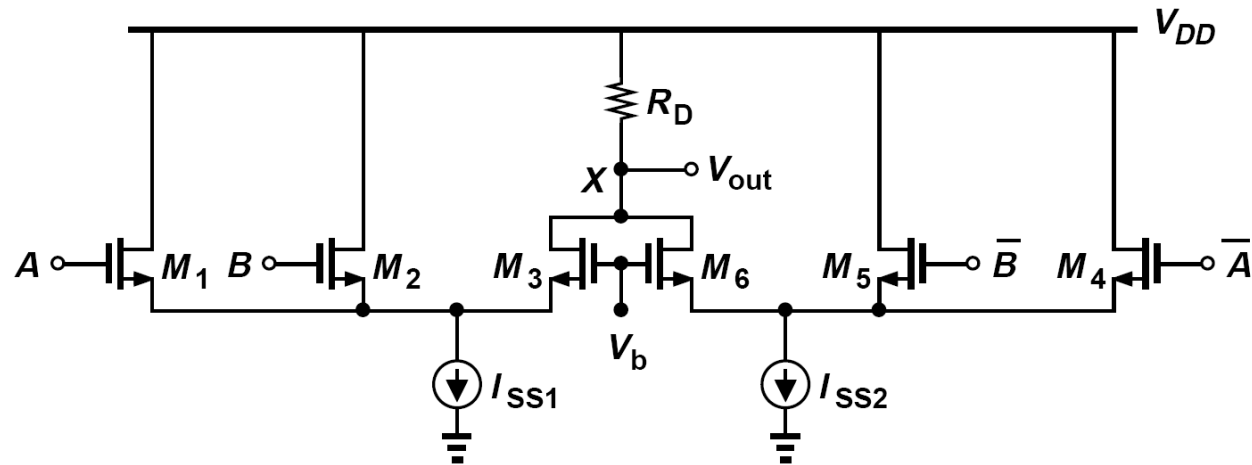➤ The topology is identical to the Gilbert cell mixer. As with the CML NAND gate, this circuit requires proper CM level shift and does not easily operate with low supply voltages.





➤ Symmetric low-voltage XOR gate.

$$V_{out} = \overline{(\overline{A + B + \overline{A} + \overline{B}})}$$

$$= \overline{A}B + A\overline{B}.$$


Speed Attributes of CML Latch

 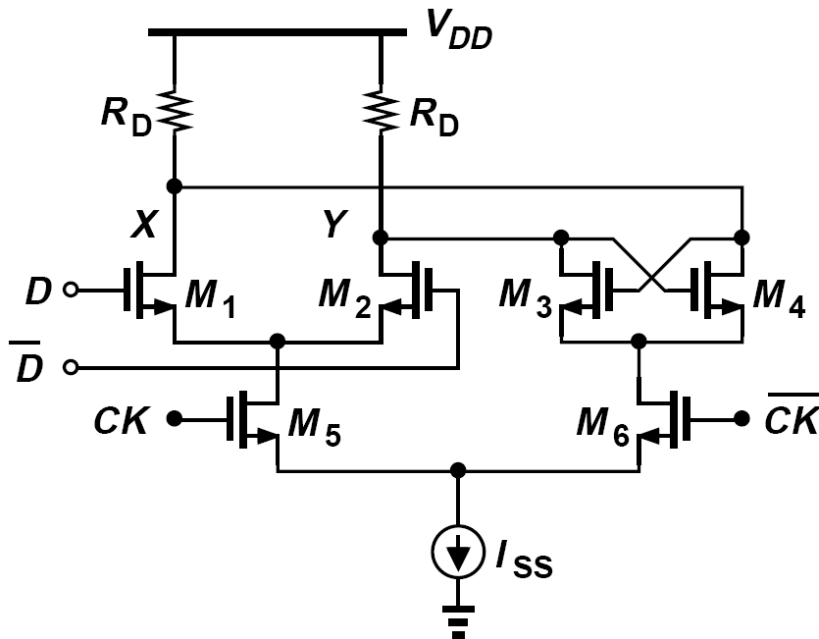



- Speed advantage of CML circuits is especially pronounced in latches.
- The latch operates properly even with a limited bandwidth at X and Y if
 - (a) in the sense mode V_X and V_Y begin from their full levels and cross,
 - and (b) in the latch mode, the initial difference between V_X and V_Y can be amplified to a final value of $I_{SS}R_D$

Example : Regenerative Amplification (I)

Regeneration mode

 

Small-signal Model

  

If V_{XY0} is small, M_3 and M_4 are near equilibrium and the small-signal equivalent circuit can be constructed as shown above. Here, C_D represents the total capacitance seen at X and Y to ground, including $C_{GD1} + C_{DB1} + C_{GS3} + C_{DB3} + 4C_{GD3}$ and the input capacitance of the next stage. The gate-drain capacitance is multiplied by a factor of 4 because it arises from both M_3 and M_4 and it is driven by differential voltages. Writing a KCL at node X gives

$$\frac{V_X}{R_D} + C_D \frac{dV_X}{dt} + g_{m3,4} V_Y = 0$$

Example to Formulate Regenerative Amplification (II)

Similarly, $\frac{V_Y}{R_D} + C_D \frac{dV_Y}{dt} + g_{m3,4}V_X = 0$

Subtracting and grouping the terms, we have

$$-R_D C_D \frac{d(V_X - V_Y)}{dt} = (1 - g_{m3,4}R_D)(V_X - V_Y)$$


We denote $V_X - V_Y$ by V_{XY} , divide both sides by $-R_D C_D V_{XY}$, multiply both sides by dt , and integrate with the initial condition $V_{XY}(t=0) = V_{XY0}$. Thus,

$$V_{XY} = V_{XY0} \exp \frac{(g_{m3,4}R_D - 1)t}{R_D C_D}$$

Interestingly, V_{XY} grows exponentially with time, exhibiting a “regeneration time constant” of

$$\tau_{reg} = \frac{R_D C_D}{g_{m3,4}R_D - 1}$$

 Of course, as V_{XY} increases, one transistor begins to turn off and its g_m falls toward zero. Note that, if $g_{m3,4}R_D \gg 1$, then $\tau_{reg} \approx C_D/g_{m3,4}$.




Example to Derive Relation Between Circuit Parameters and Clock Period

Initial voltage difference $V_{XY0} = 0.9I_{SS}R_D \exp \frac{-0.5T_{ck}}{\tau_{reg}}$ (10.45)

The minimum initial voltage must be established by the input differential pair in the sense mode [just before $t = t_3$]. In the worst case, when the sense mode begins, V_X and V_Y are at the opposite extremes and must cross and reach V_{XY0} in $0.5T_{ck}$ seconds. For example, V_Y begins at V_{DD} and falls according to

$$V_Y(t) = V_{DD} - I_{SS}R_D \left(1 - \exp \frac{-t}{R_DC_D}\right)$$
 
$$V_X(t) = V_{DD} - I_{SS}R_D \exp \frac{-t}{R_DC_D}$$




Since $V_X - V_Y$ must reach V_{XY0} in $0.5T_{ck}$ seconds, we have

$$-2I_{SS}R_D \exp \frac{-0.5T_{ck}}{R_DC_D} + I_{SS}R_D = 0.9I_{SS}R_D \exp \frac{-0.5T_{ck}}{\tau_{reg}}$$

$$\Rightarrow 0.9 \exp \frac{-0.5T_{ck}}{\tau_{reg}} + 2 \exp \frac{-0.5T_{ck}}{R_DC_D} = 1 \Rightarrow$$


It limits the upper value of R_DC_D and the lower one of $g_{m3,4}$.

Merging Logic with Latch

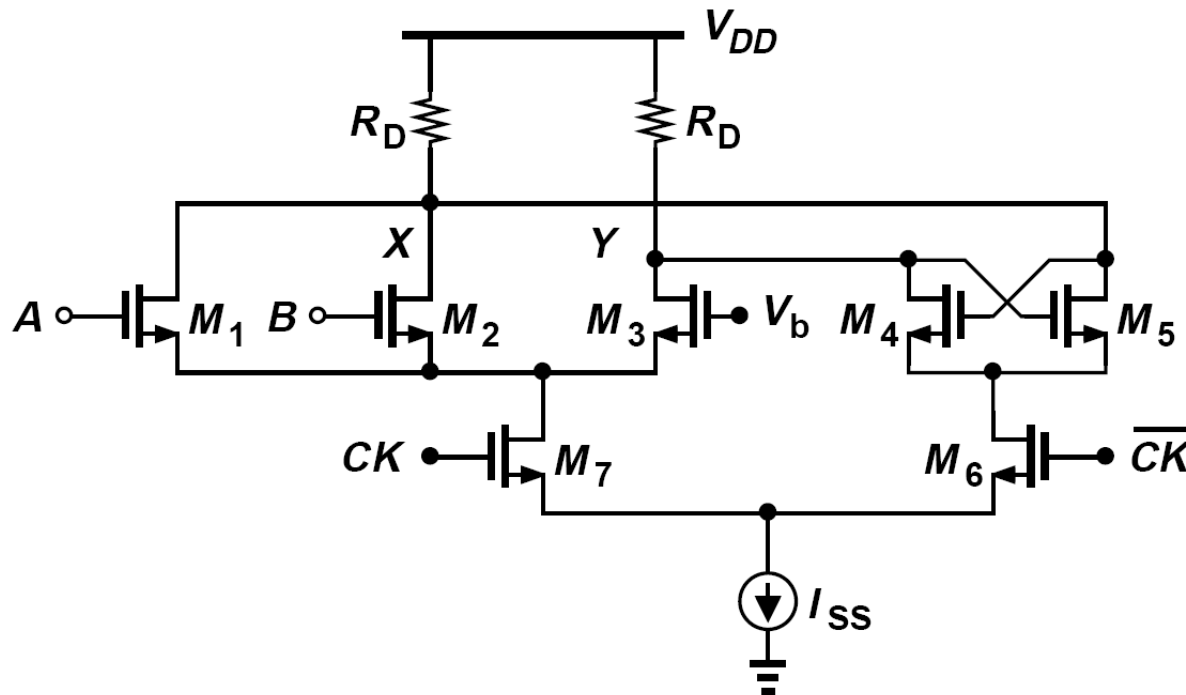

- It is possible to merge logic with a latch, thus reducing both the delay and the power dissipation. For example, the NOR and the master latch of FF_1 depicted in previous high-speed divide-by-2/3 circuit can be realized as shown above. The circuit performs a NOR/OR operation on A and B in the sense mode, and stores the result in the latch mode.

Design Procedure


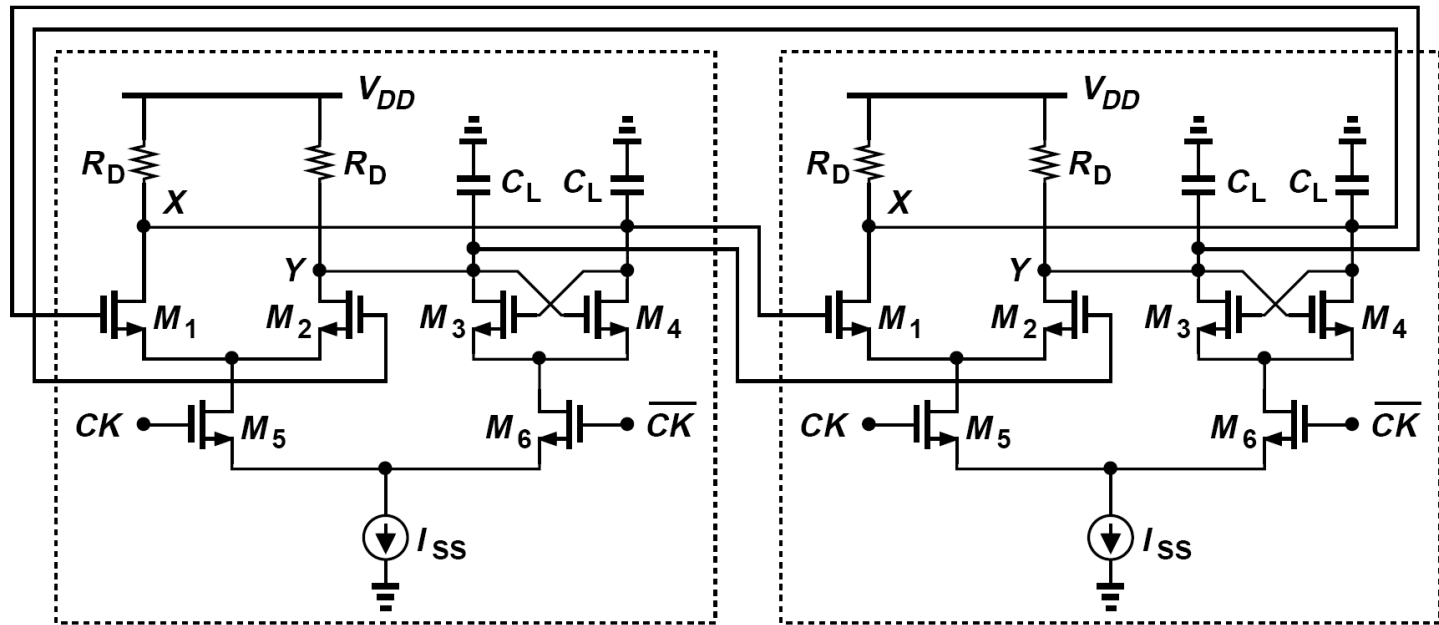


- (1) Select I_{SS} based on the power budget ; (2) Select $R_D I_{SS} \approx 300\text{mV}$
- (3) Select $(W/L)_{1,2}$ such that the diff. pair experiences nearly complete switching for a diff. input of 300mV
- (4) Select $(W/L)_{3,4}$ so that small-signal gain around regenerative loop exceeds unity
- (5) Select $(W/L)_{5,6}$ such that the clocked pair steers most of the tail current with the specified clock swing

  Example : Sensitivity of the $\div 2$ Circuit

The performance of high-speed dividers is typically characterized by plotting the minimum required clock voltage swing (“sensitivity”) as a function of the clock frequency.


Minimum Required
Clock Swing
(Sensitivity)



For square clock waveforms, a small swing fails to steer all of the tail current, thereby keeping M_1 - M_2 and M_3 - M_4 simultaneously on. The circuit may therefore oscillate at $f_1/2$ (or injection-pulled by the clock).


The “self-oscillation” of the divider also proves helpful in the design process: We thus first test the circuit with a zero clock swing to ensure that it oscillates.

Class-AB Latch

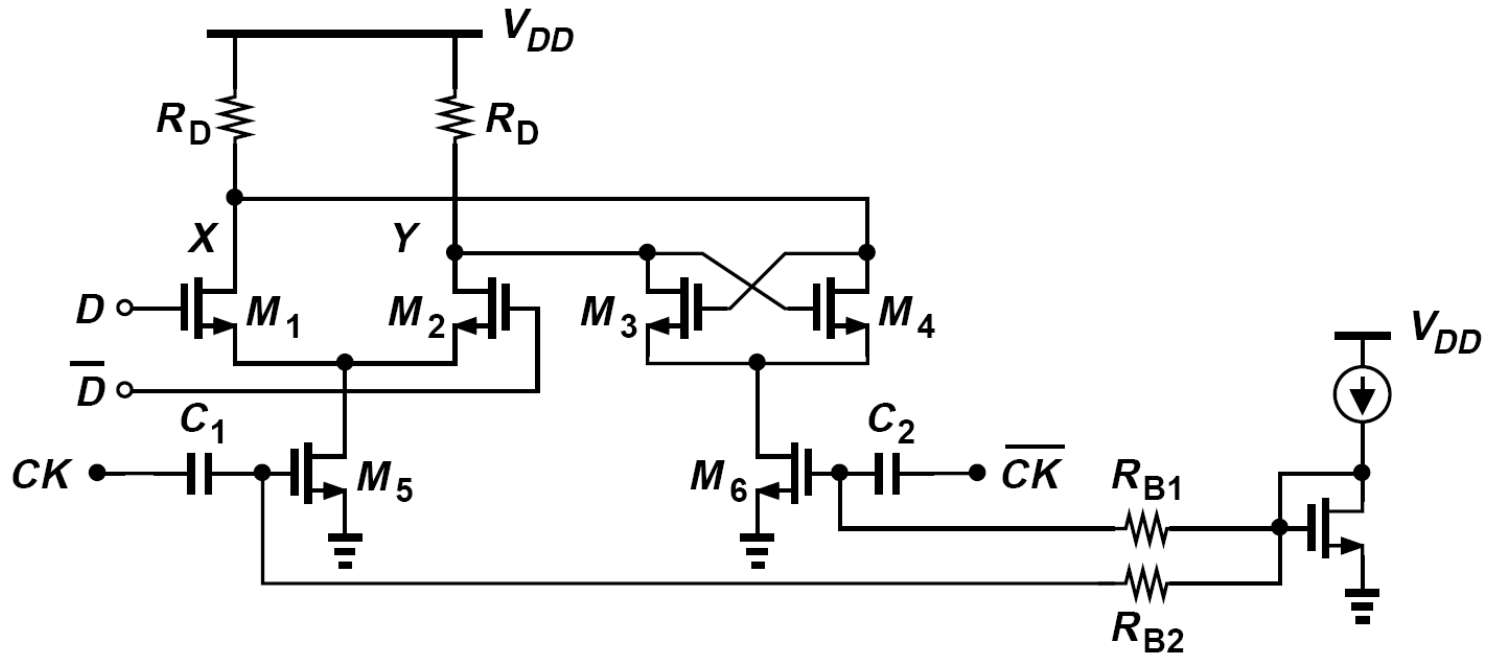



- The bias of the clocked pair is defined by a current mirror and the clock is coupled capacitively.
- Large clock swings allow transistors M_5 and M_6 to operate in the class AB mode, i.e., their peak current well exceed their bias current. This attribute improves the speed of the divider.

Example : Choosing Coupling Capacitance

 

Suppose the VCO output swing is twice that required by the divider. We simply choose each coupling capacitor to be equal to the input capacitance of the divider. This minimizes the size of the coupling capacitors, the load capacitance seen by the VCO (half of the divider input capacitance), and the effect of divider input capacitance variation on the VCO.

 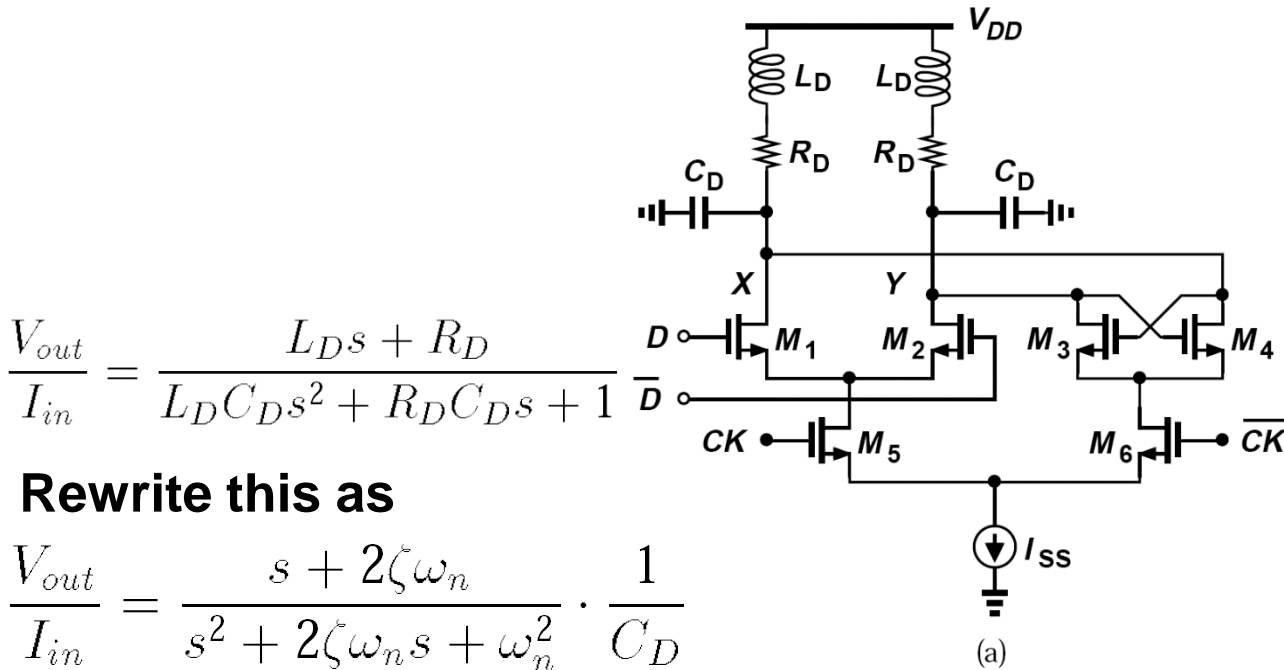CML Using Inductive Peaking (Shunt Peaking)



where $\zeta = \frac{R_D}{2} \sqrt{\frac{C_D}{L_D}}$ $\omega_n = \frac{1}{\sqrt{L_D C_D}}$


To determine the -3 dB bandwidth:

$$\frac{\omega_{-3dB}^2 + 4\zeta^2\omega_n^2}{(\omega_{-3dB}^2 - \omega_n^2)^2 + 4\zeta^2\omega_n^2\omega_{-3dB}^2} = \frac{2\zeta^2}{\omega_n^2}$$

It follows that

$$\omega_{-3dB}^2 = \left[-2\zeta^2 + 1 + \frac{1}{4\zeta^2} + \sqrt{\left(-2\zeta^2 + 1 + \frac{1}{4\zeta^2} \right)^2 + 1} \right] \omega_n^2$$

Series Peaking

 

$$\frac{V_{out}}{I_{in}}(s) = \frac{R_D}{L_D C_D s^2 + R_D C_D s + 1}$$

$$\zeta = \frac{R_D}{2} \sqrt{\frac{C_D}{L_D}}$$

$$\omega_n = \frac{1}{\sqrt{L_D C_D}}$$



The -3 dB bandwidth is computed as

$$\omega_{-3dB}^2 = [-(2\zeta^2 - 1) + \sqrt{(2\zeta^2 - 1)^2 + 1}] \omega_n^2,$$

If $\zeta = 1/\sqrt{2}$, $\omega_{-3dB} = \omega_n = \sqrt{2}/(R_D C_D)$



➤ Series peaking increases the bandwidth by about 40%

Inductively-peaked Latch

  


- As the value of L_D becomes large enough, the circuit begins to fail at low frequencies. This is because the circuit approaches a quadrature LC oscillator that is injection-locked to the input clock
- $Q = L_D \omega / R_D$
 $L_D \uparrow \quad Q \uparrow \rightarrow$ locking range decreases

True Single-Phase Clocking

  

- When CK is high, the first stage operates as an inverter, impressing \bar{D} at A and E . When CK goes low, the first stage is disabled and the second stage becomes transparent, writing \bar{A} at B and C and hence making Q equal to A . The logical high at E and the logical low at B are degraded but the levels at A and C ensure proper operation of the circuit.

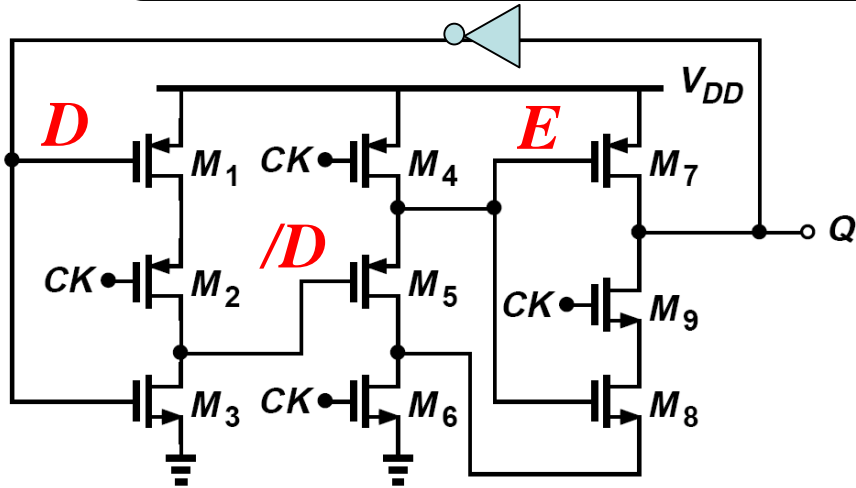TSPC Divide-by-2 Circuit and DFF with a NAND gate




Break the feedback, input=D

CK=low, E=high, M7&M9 off, Q holds


CK=high, D=low, /D=high, M6&M8&M9 on, Q=D=low

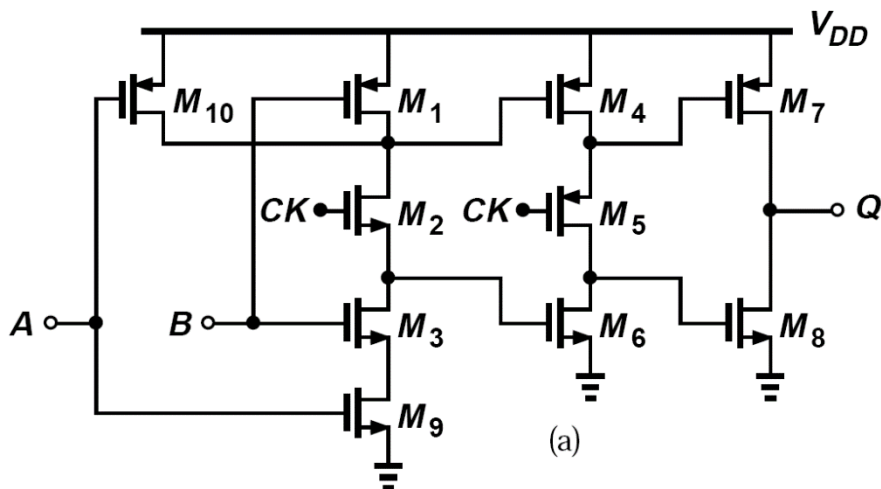CK=high, D=high, /D=low, M5&M6 on, E=low,
M7 on, M8 off, Q=D=high




- This topology achieves relatively high speeds with low power dissipation, but, unlike CML dividers, it requires rail-to-rail clock swings for proper operation.
- The circuit consumes no static power and as a dynamic logic topology, the divider fails at very low clock frequencies due to the leakage of the transistors.
- A NAND gate can be merged with the master latch.
- In the design of TSPC circuit, one observes that wider clocked devices raises the maximum speed, but at the cost of loading the preceding stage.

TSPC Using Ratioed Logic

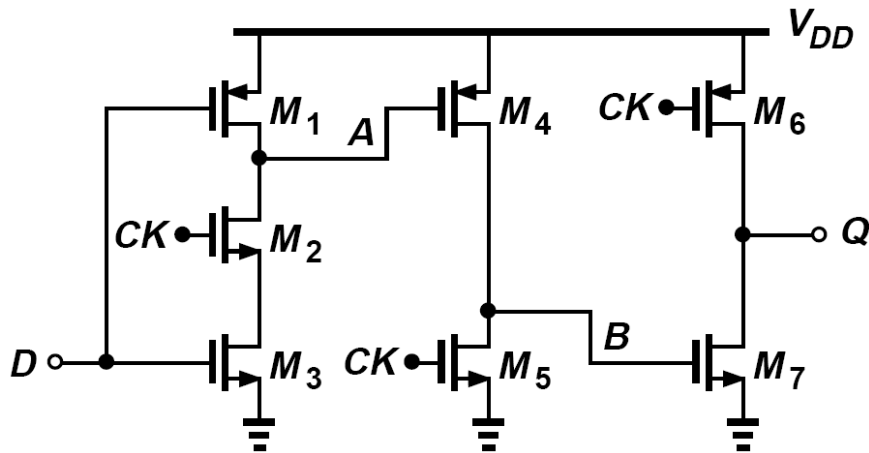



- The slave latch is designed as “ratioed” logic, achieving higher speeds.

IEEE JSSC, SC-31, pp. 749-, May 1996.

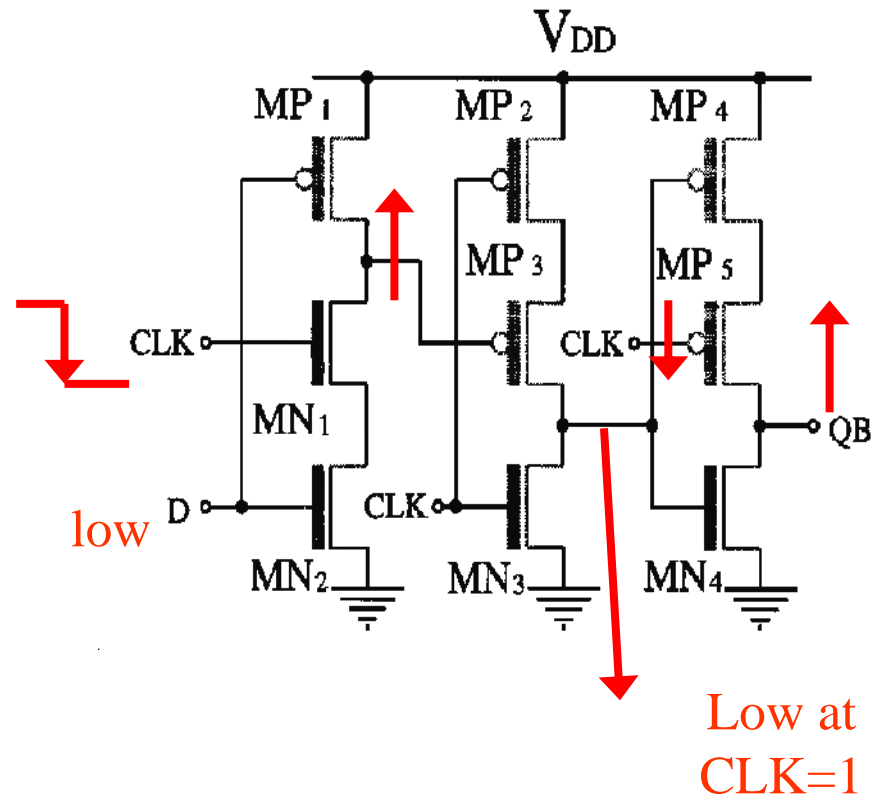

IEEE JSSC, SC-24, pp. 62-, Feb. 1989.


Miller Divider

  

$$\cos(\alpha)\cos(\beta) = \cos(\alpha + \beta) + \cos(\alpha - \beta)$$

- If the required speed exceeds that provided by CML circuits, one can consider the “Miller divider”, also known as the “dynamic divider”
- The Miller divider can achieve high speeds for two reasons: (1) the low-pass behavior can simply be due to the intrinsic time constant at the output node of the mixer and (2) the circuit does not rely on latching and hence fails more gradually than flipflops as the input frequency increases

 Why the Component at $3f_{in}/2$ Must be Sufficiently Small?




$$\begin{aligned} V_X(t) &= \alpha(V_0 \cos \omega_{in} t) \left(V_m \cos \frac{\omega_{in} t}{2} \right) \\ &= \frac{\alpha V_0 V_m}{2} \left(\cos \frac{\omega_{in} t}{2} + \cos \frac{3\omega_{in} t}{2} \right) \end{aligned}$$

- This sum exhibits additional zero crossings, prohibiting frequency division if traveling through the LPF unchanged.


$$\cos(\alpha)\cos(\beta) = \cos(\alpha + \beta) + \cos(\alpha - \beta)$$

 Introducing Phase Shift in Miller Divider




- The Miller divider operates properly if the third harmonic is attenuated and shifted so as to avoid the additional zero crossings.

Miller Divider with Inductive Load

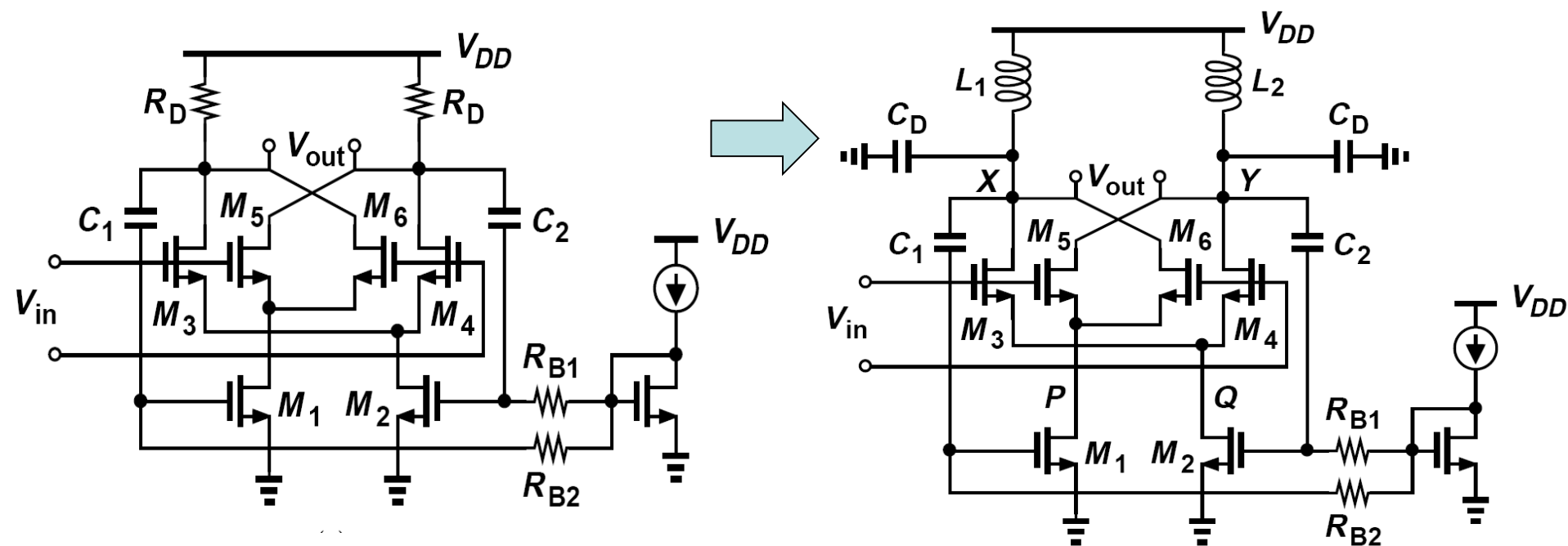


➤ The tanks suppress the third-order harmonics

Miller Divider with Passive Mixers

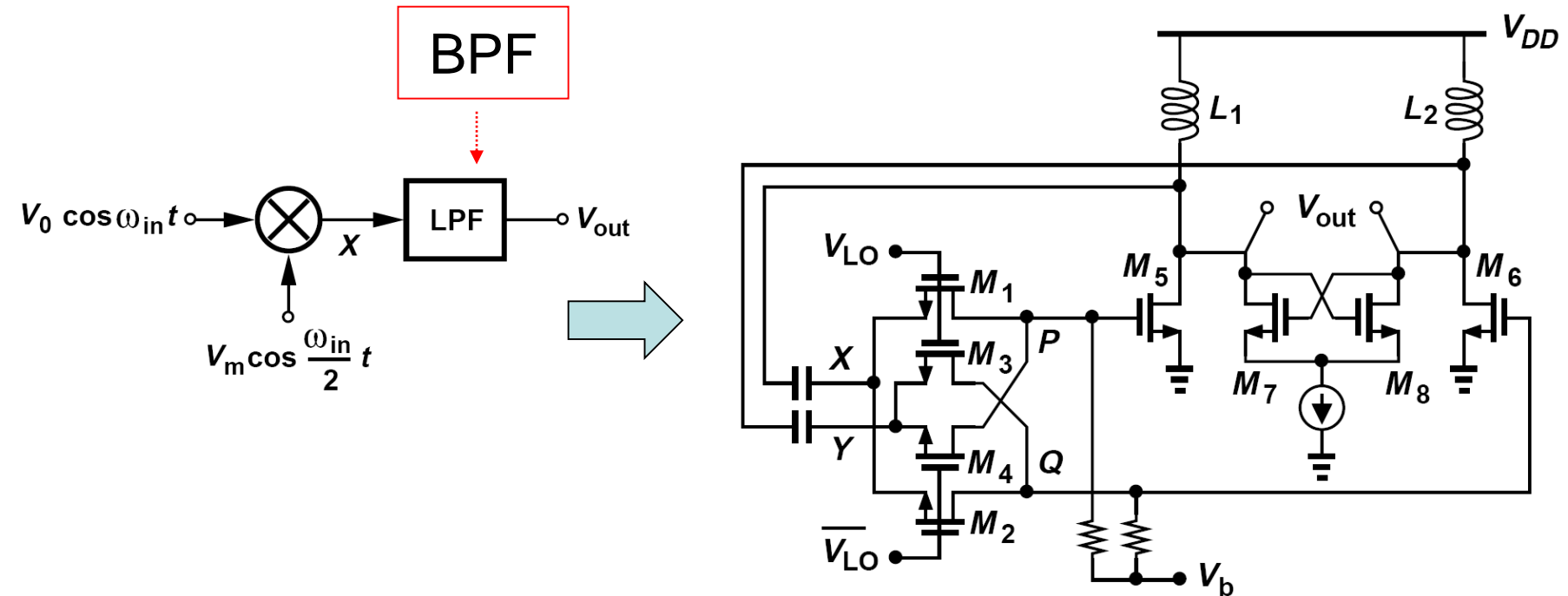

- Since the output CM level is near V_{DD} , the feedback path incorporates capacitive coupling, allowing the sources and drains of M_1 - M_4 to remain about 0.4V above the ground. The cross-coupled pair M_7 - M_8 can be added to increase the gain by virtue of its negative resistance.

Miller Divider with Other Moduli

 


A $\div N$ circuit in the feedback path creates $f_b = f_{out}/N$, yielding $f_{in} \pm f_{out}/N$ at X . If the sum is suppressed by the LPF, then $f_{out} = f_{in} - f_{out}/N$ and hence

$$f_{out} = \frac{N}{N+1} f_{in} \quad f_b = \frac{1}{N+1} f_{in}$$

- The sum component at X comes closer to the difference component as N increases, dictating a sharper LPF roll-off.
- Another critical issue relates to the port-to-port feedthroughs of the mixer

Example : Effect of Feedthrough


 


Assume $N = 2$. The feedthrough from the main input to node X produces a spur at f_{in} . Similarly, the feedthrough from Y to X creates a component at $f_{in}/3$. The output therefore contains two spurs around the desired frequency. The additional zero crossing will result in a malfunction.

$$f_{in} - \frac{f_{out}}{2} = f_{out} \Rightarrow f_{out} = \frac{2f_{in}}{3}$$

The spectrum at Y : Example 9.12


Miller Divider Using SSB Mixer

  


$$\cos(\alpha)\cos(\beta) \mp \sin(\alpha)\sin(\beta) = \cos(\alpha \pm \beta)$$

- The Miller divider frequency range can be extended through the use of a single-sideband (SSB) mixer. It suppresses the sum component by SSB mixing rather than filtering to avoid the additional zero crossing.
- The use of SSB mixing prove useful if the loop contains a divider that generates quadrature outputs. Topology in (b) achieves a wide frequency range and generates quadrature outputs. But it requires quadrature LO phases.

Injection-Locked Dividers (ILDs)

 

 - Based on oscillators that are injection-locked to a harmonic of their oscillation frequency
- If f_{in} varies across a certain “lock range”, the oscillator remains injection-locked to **the $f_{in} - f_{out}$** component at node X



The mixer yields two components at node X , namely, $f_{in} - f_{out}/N$ and $f_{in} + f_{out}/N$. If the oscillator locks to the former, then $f_{in} - f_{out}/N = f_{out}$ and hence

$$f_{out} = \frac{N}{N+1} f_{in}$$

The oscillator lock range must therefore be **narrow enough** to lock to only one of the two components.


Similarly, if the oscillator locks to the latter then

$$f_{out} = \frac{N}{N-1} f_{in}$$

Miller Divider and Injection-Locked Divider

What is the difference between Miller divider and ILD?


 
The ILD oscillates even input amplitude is zero, but Miller divider does not. Generally, ILD has a narrower operation range than Miller divider.



IEEE JSSC, pp. 2109-, Aug. 2019

IEEE JSSC, pp. 2122-, Aug. 2019

Implementation of ILD

  


$$[18] \quad \Delta\omega_{\text{out,two-side}} = \frac{\omega_0}{Q} \times \frac{I_{\text{inj}}}{I_{\text{SS}}} = \frac{\omega_0}{Q} \times \frac{I_{\text{inj}}}{I_{\text{osc}}} \quad I_{\text{inj}} = \frac{2}{\pi} \times I_{\text{in}} \quad \text{Page 371}$$

The output frequency range across which the circuit remains locked is given by

$$\Delta\omega_{\text{out}} = \frac{\omega_0}{Q} \left(\frac{2}{\pi} \frac{I_{\text{in}}}{I_{\text{osc}}} \right)$$

The input lock range is twice this value: $\Delta\omega_{\text{in}} = \frac{\omega_0}{Q} \left(\frac{4}{\pi} \frac{I_{\text{in}}}{I_{\text{osc}}} \right)$

 Divider Delay and Phase Noise: Effect of Divider Delay



A stage with a constant delay of ΔT

$$H_{open}(s) = \frac{I_P}{2\pi} \left(R_P + \frac{1}{C_1 s} \right) \frac{K_{VCO}}{NS} e^{-\Delta T \cdot s}$$

$$e^{-s \cdot \Delta T} \approx 1 - s \cdot \Delta T \quad \text{if } |s \cdot \Delta T| \ll 1$$


- The **zero** has two undesirable effects: it flattens the gain, pushing the gain crossover frequency to higher values (in principle, infinity), and it bends the phase profile downward.

This zero must remain well above the original unity-gain bandwidth of the loop:



$$\omega_u^2 = \left(2\zeta^2 + \sqrt{4\zeta^4 + 1} \right) \omega_n^2 \quad (9.67)$$

Effect of Divider Phase Noise

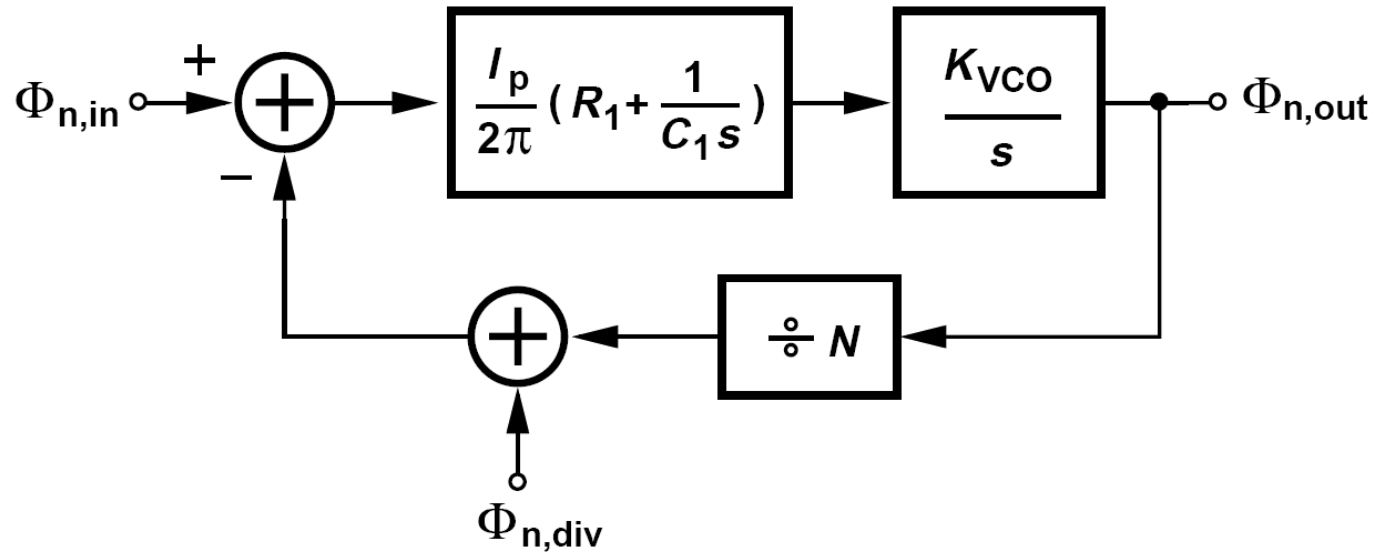


- The output phase noise of the divider directly adds to the input phase noise, experiencing the same low-pass response as it propagates to ϕ_{out} . In other words, $\phi_{n,div}$ is also multiplied by a factor of N within the loop bandwidth.

For the divider to contribute negligible phase noise, we must have

$$\phi_{n,div} \ll \phi_{n,in}$$

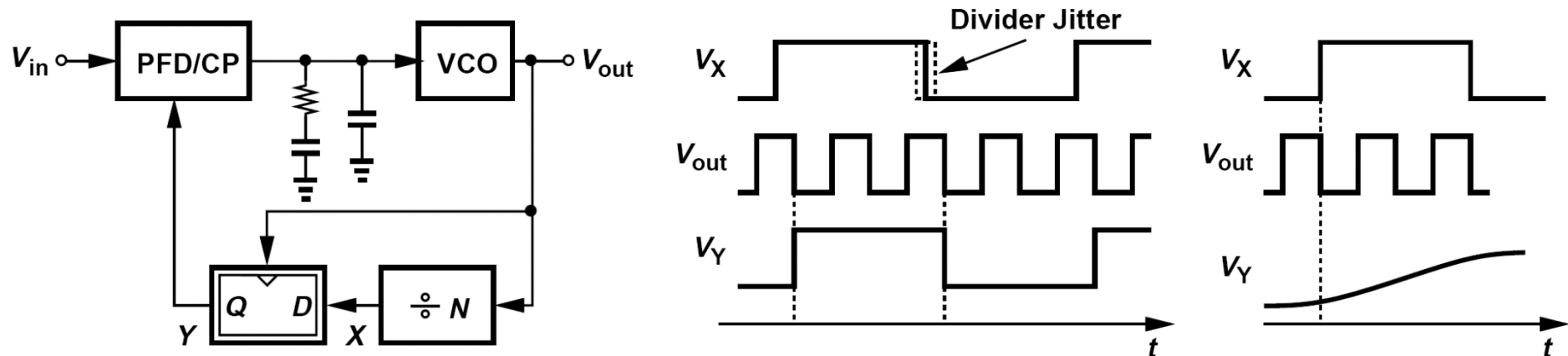Use of Retiming FF to Remove Divider Phase Noise




- If the divider phase noise is significant, a retiming flipflop can be used to suppress its effect.
- In essence, the retiming operation bypasses the phase noise accumulated in the divider chain.
- “Metastable” problem occurs, if a VCO edge is close to the transition at node V_X .

Synthesizer Design: Section 13.4

We want to design an integer-N synthesizer with a reference of 20MHz for 11a (5.1~5.9GHz) and 11g (2.4~2.48GHz) bands.

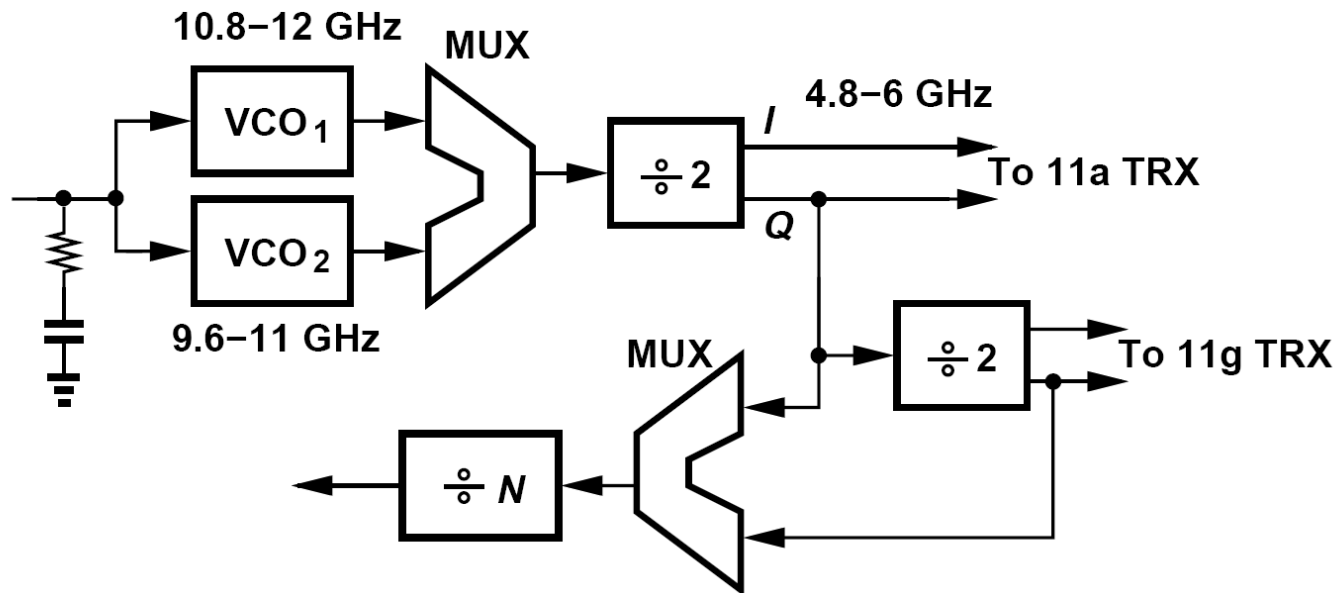A VCO of 2.4GHz and A VCO of 5-6GHz with the phase noise of -101dBc/Hz at an offset frequency of 1MHz. The VCO₂ from 10.8 GHz to 12 GHz has the phase noise of -101+6=-95dBc/Hz.




VCO Design (I)---Preliminary 12 GHz VCO

We choose the tuning range of the VCOs as follows. One VCO, VCO_1 , operates from 9.6 GHz to 11 GHz, and the other, VCO_2 , from 10.8 GHz to 12 GHz. We begin with VCO_2

$$f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.75\text{nF} \cdot (180 + 15)\text{fF}}} = 13\text{GHz}$$

$$R_p = Q\omega_o L = 10 \cdot 2\pi \cdot 13\text{GHz} \cdot 0.75\text{nF} = 613\Omega$$


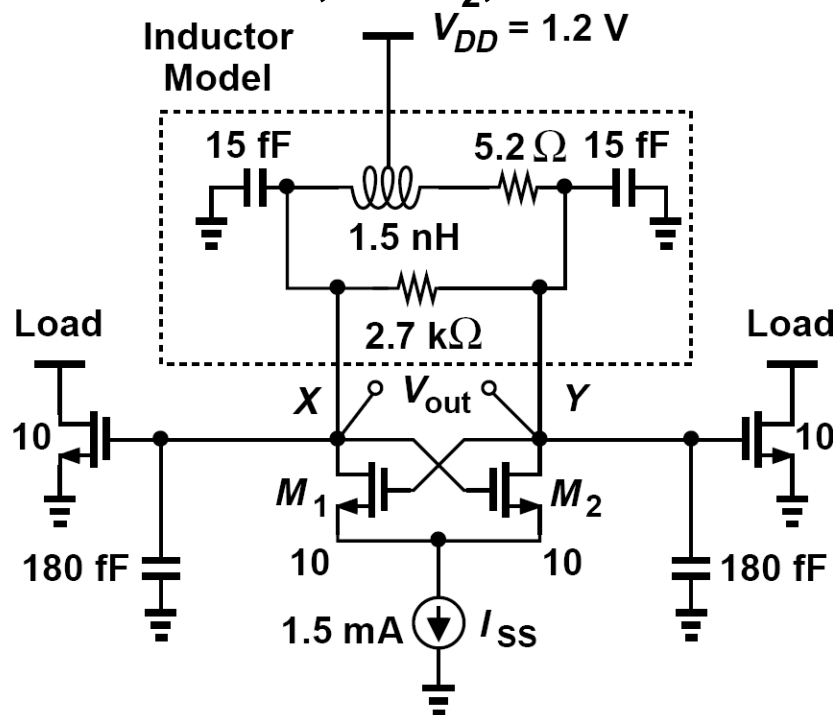
$$V_{pp} = \frac{4}{\pi} R_p I_{SS} = 1.17\text{V}$$



➤ Assume a single-ended load inductance of 0.75 nH, $Q = 10$. Yielding a single-ended peak-to-peak output swing of 1.2 V. We choose a width of 10 μm for cross-coupled transistors. Finally we add enough constant capacitance to obtain an oscillation frequency of about 12 GHz.

VCO Design (II)---Simulation Result of Preliminary Design

  We wish to briefly simulate the performance of the circuit before adding the tuning devices.




- Simulations suggest a single-ended peak-to-peak swing of about 1.2 V. Also, the phase noise at 1-MHz offset is around -109 dBc/Hz, well below the required value. The design is thus far promising.
- However, the phase noise is sensitive to the tail capacitance. (CH8, p. 556)

VCO Design (III)---Add Capacitance for Tuning


Now, we add a switched capacitance of 90 fF to each side so as to discretely tune the frequency from 12 GHz to 10.8 GHz.

- The size of the switches in series with the 90-fF capacitors must be chosen according to the trade-off between their parasitic capacitance in the off state and their channel resistance in the on state.
- The voltage swing decreases considerably if the on-resistance is not sufficiently small.
- Simulations indicate that the frequency can be tuned from 12.4 GHz to 10.8 GHz but the single-ended swings fall to about 0.8 V at the lower end. To remedy the situation, we raise the tail current to 2mA.

 


VCO Design (IV)---Add Varactors

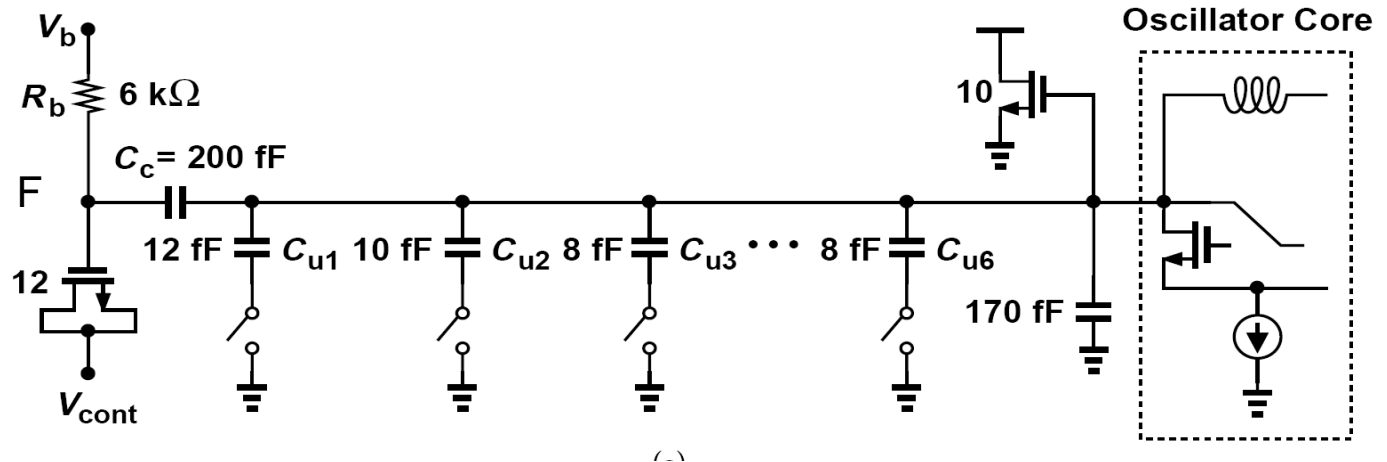In the next step, we add varactors to the VCO and decompose the switched capacitors into smaller units, thus creating a set of discretely-spaced continuous tuning curves with some overlap.




 - It demands some iteration in the choice of the varactors' size and the number and values of the unit capacitors.
- We still have floating switches even though they are not shown.
- To obtain a wide continuous tuning range, the gate of the varactor is capacitively coupled to the core and biased at $V_b \approx 0.6\text{ V}$.



VCO Design (V)---Tuning Characteristics and Phase Noise


Figure below shows VCO's tuning characteristics obtained from simulations and phase noise with all of the capacitors switched into the tank.

 

➤ The control can operate properly across this range. We note that K_{VCO} varies from about 200 MHz/V to 300 MHz/V.

VCO Design (VI)---Replace Ideal Tail Current with Current Mirror


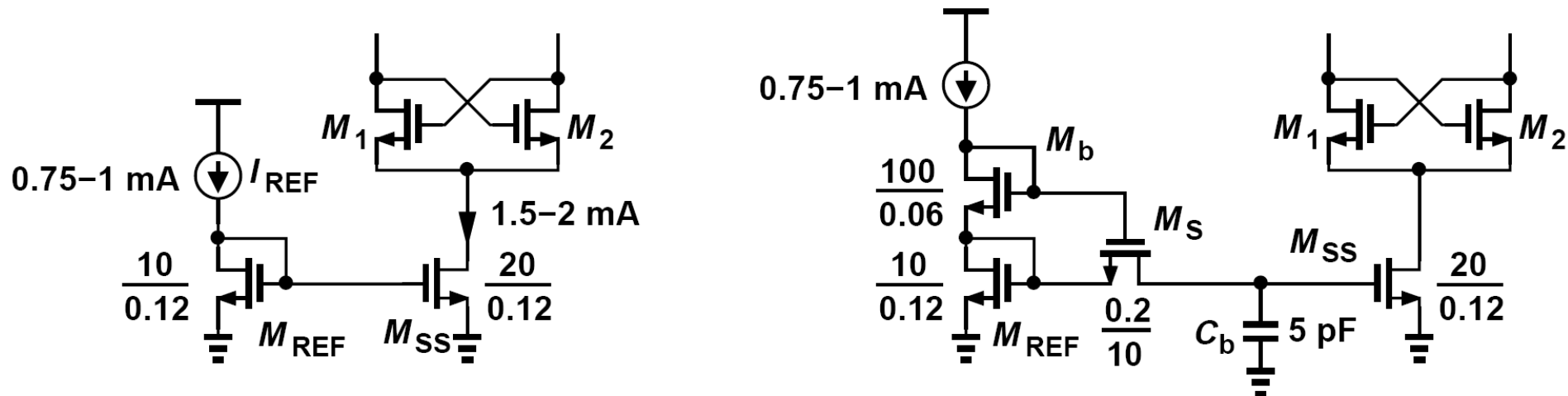
In the last step of our VCO design, we replace the ideal tail current source with a current mirror.



- This arrangement incorporates a channel length of $0.12\ \mu\text{m}$ to improve the matching between the two transistors in the presence of a V_{DS} difference. The width of M_{SS} is chosen so as to create a small overdrive voltage, allowing the V_{GS} to be approximately equal to V_{DS} ($\approx 500\ \text{mV}$).

VCO Design (VII)---Raised Phase Noise

 
 
The current mirror drastically raises the phase noise of the VCO, from -111 dBc/Hz to -100 dBc/Hz at 10.8 GHz and from -109 dBc/Hz to -98 dBc/Hz at 12.4 GHz (both at 1-MHz offset)



➤ Most of the phase noise now arises from the thermal and flicker noise of M_{REF} and M_{SS} .

VCO Design (VIII)---Modification to Suppress the Noise

  
A simple modification can suppress the contribution of M_{REF} . As shown above, we insert a low-pass filter between the two transistors, suppressing the noise of M_{REF} (and I_{REF}).



- To obtain a corner frequency well below 1 MHz:
- (1) bias MS with a small overdrive voltage, which is provided by the wide diode-connected transistor M_b ;
 - (2) select a width of $0.2 \mu\text{m}$ and a length of $10 \mu\text{m}$ for M_S ;
 - (3) choose a value of 5 pF for C_b .

Multiplexing Two VCOs

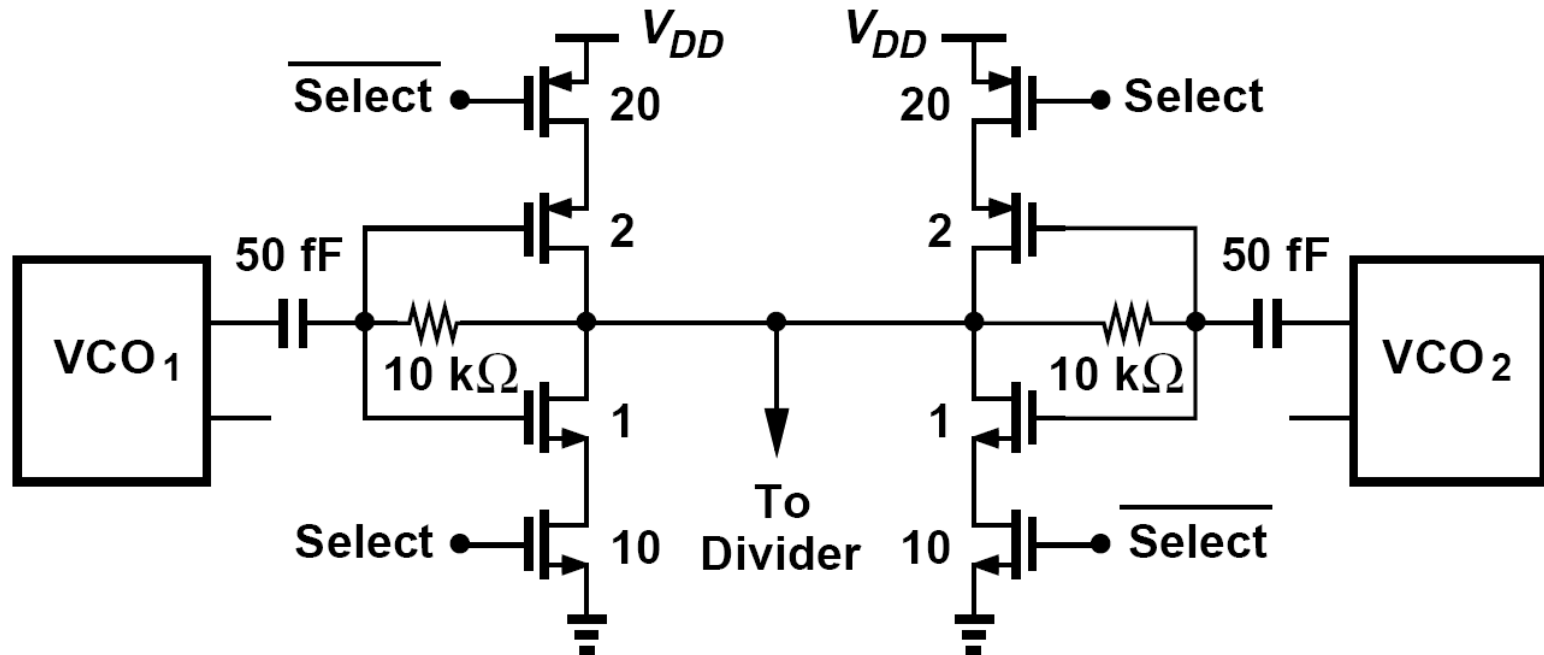
The outputs of the two VCOs must be multiplexed. With rail-to-rail swings available, simple inverters can serve this purpose.



- Each inverter is sized according to an estimated fanout necessary to drive the subsequent divide-by-2 circuit.
- The VCO outputs have a CM level equal to V_{DD} and are therefore capacitively coupled to the MUX.

Divider Design: Latch in a Divide-by-2 Circuit

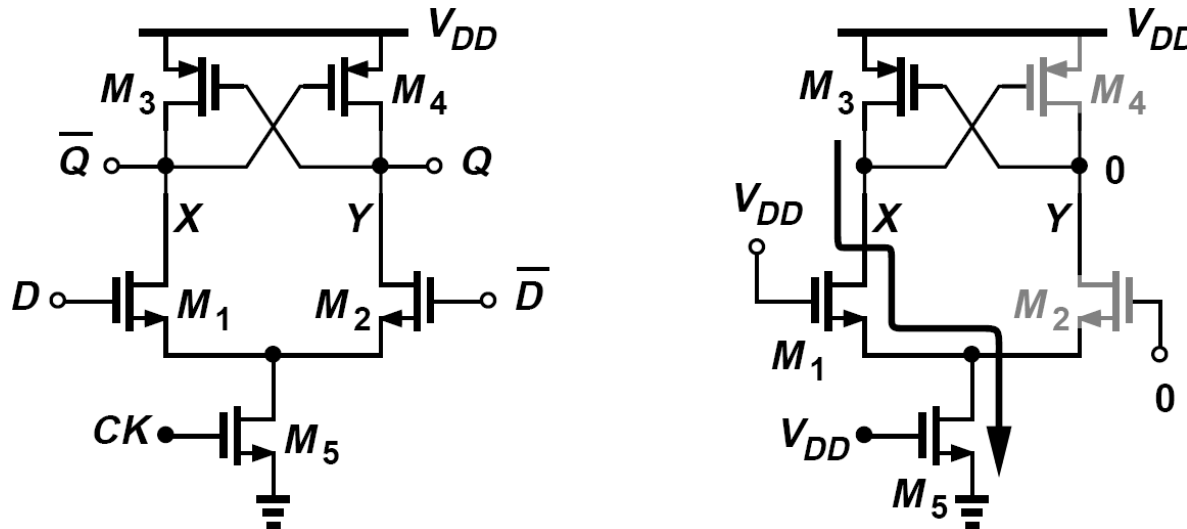
The multiplexed VCO outputs must be divided by two so as to generate quadrature outputs. With rail-to-rail swings available at the MUX output, we seek a simple and efficient topology.



- This topology employs dynamic logic; leakage currents eventually destroy the stored state if CK is low for a long time.
- The latch is based on ratioed logic, requiring careful sizing.

Divide-by-2 Circuit: Driving a Large Load Capacitance


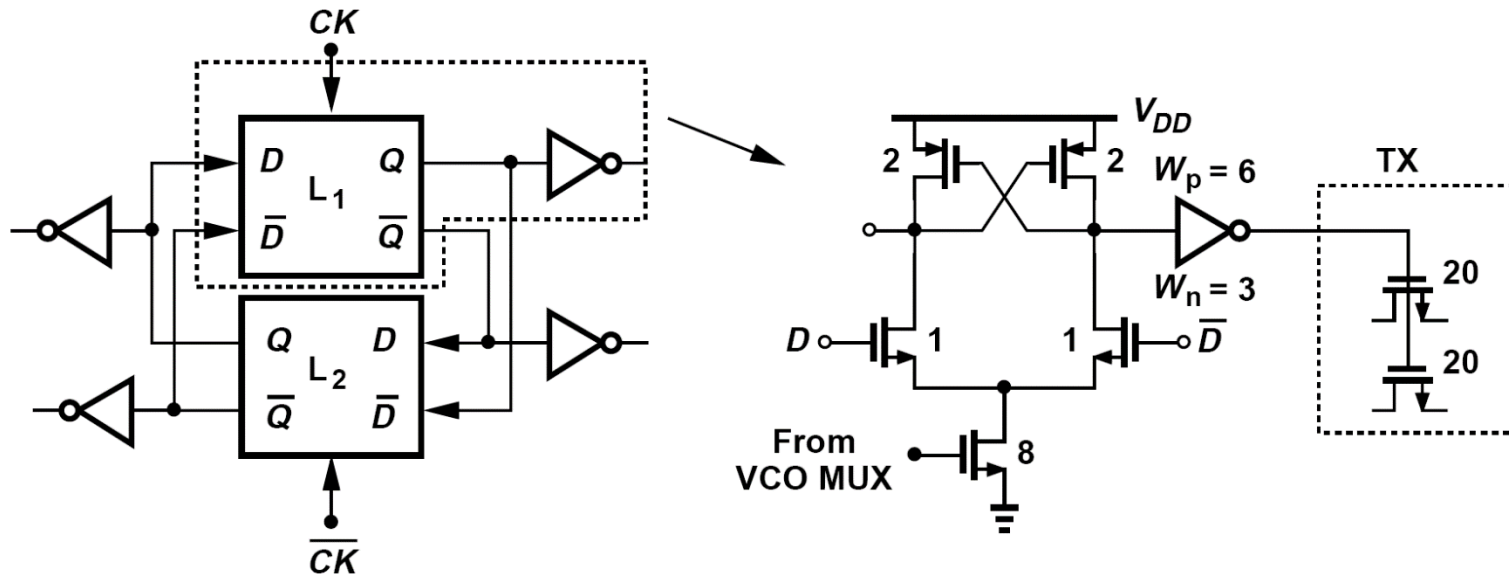
As with other latches, the above circuit may fail if loaded by a large load capacitance. For this reason, we immediately follow each latch in the divide-by-2 circuit by inverters.



- The inverters present a small load to the latch but must drive a large capacitance themselves, thereby producing slow edges.
- Frequency dividers typically demand a conservative design because:
 - (1) the layout parasitics tend to lower the speed considerably
 - (2) in the presence of process and temperature variations, the divider must handle the maximum frequency arriving from the VCO.


Dual-Modulus Divider

  The pulse-swallow counter necessary for the synthesizer requires a prescaler, which itself employs a dual-modulus divider. Such a divider must operate up to about 6.5 GHz.




➤ The Chang-Park-Kim flipflop – shown in (a) provides only a Q output. We modify it to that shown in (b), where FF_1 is preceded by an inverter.

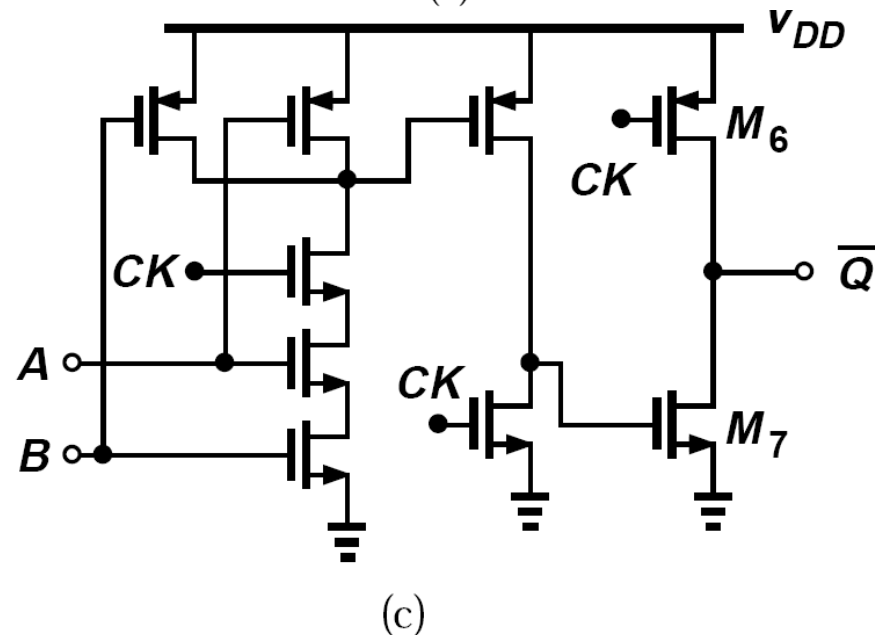➤ We also wish to merge the AND gate with the second flipflop so as to improve the speed (c)



$\div 3/4$ Circuit


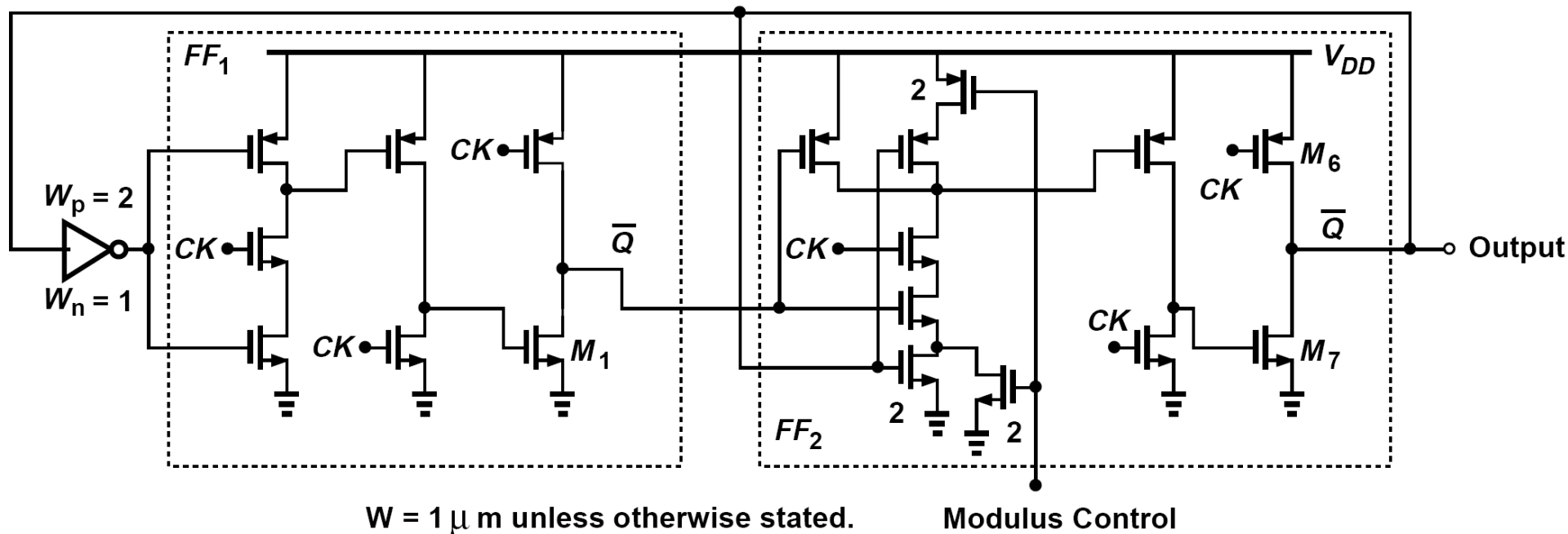
We must now add an OR gate to the above topology to obtain a $\div 3/4$ circuit. Again, we prefer to merge this gate with either of the flipflops.



➤ The modulus control OR gate is embedded within the AND structure.

÷ 3/4 Circuit: Simulation Result

  For a 6.5GHz clock, this ÷ 3/4 divider draws 0.5mA from a 1.2V supply.



For a frequency range of 5180 to 5320 in 20MHz steps, the division ratio of a prescaler is $NP+S=259$ to 266. if S varies from 9 to 16, $N=10$ and $P=25$ and a ÷ 11/10 divider are needed. Or, $N=5$, $P=50$, a ÷ 5/6 divider are needed.

For high 11a carrier frequencies; **5745~5808MHz**, a 5MHz reference is used. $NP+S=1149-1161$. So, $S=9\sim 21$, $N=10$ and $P=114$.

Loop Design

The CP and LPF are designed based on the lowest value of $KVCO$ ($2\pi \cdot 200$ MHz) and the highest value of the divide ratio, M (2×1161 for a 5MHz reference). We begin with a loop bandwidth of 500 kHz and a charge pump current of 1 mA. Thus, $2.5\omega_n = 2\pi(500 \text{ kHz})$ and hence $\omega_n = 2\pi(200 \text{ kHz})$. We have

$$2\pi(200 \text{ kHz}) = \sqrt{\frac{I_p KVCO}{2\pi C_1 M}},$$

If $I_p = 1 \text{ mA}$ and $C_1 = 54.5 \text{ pF}$, occupied a large area.

We instead choose $I_p = 2 \text{ mA}$ and $C_1 = 27 \text{ pF}$, trading area for power consumption. Setting the damping factor to unity,


$$\zeta = \frac{R_1}{2} \sqrt{\frac{I_p KVCO C_1}{2\pi M}} = 1$$

$R_1 = 29.3 \text{ k ohm}$ and $C_2 = C_1/5 = 5.4 \text{ pF}$ (section 9.7)


Charge Pump

For the charge pump, we return to the gate-switched topology as it affords the maximum voltage headroom.

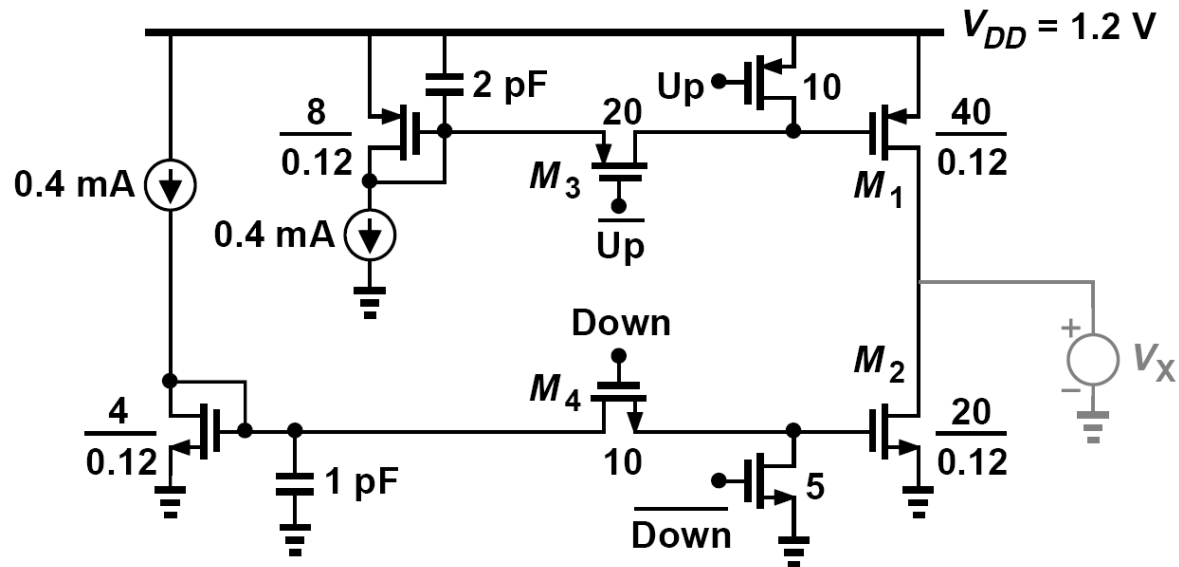
➤ The gate-switched topology still proves rather slow, primarily because of the small overdrive of M_3 and M_4



 ➤ In this design, the maximum mismatch occurs at $V_{out} = 1.1 \text{ V}$ and is equal to $60 \mu\text{A}$, about 3%.





Loop Simulation: Time Contraction

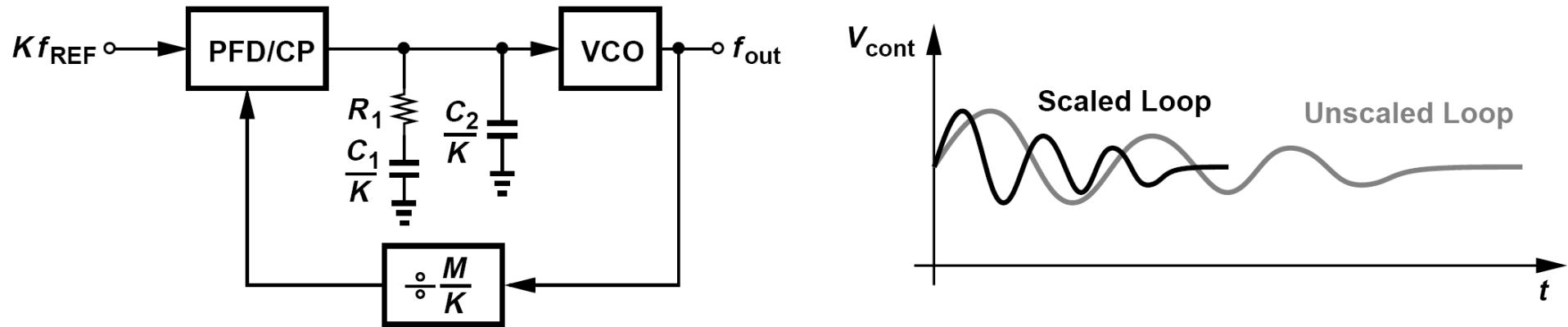

- We wish to scale down the lock time of the loop by a large factor, e.g., **$K = 100$** . To this end, we raise f_{REF} by a factor of K and reduce C_1 , C_2 , and M by a factor of K .
- Note that time contraction does not scale R_1 , I_p , or K_{VCO} , and it retains the value of ζ while scaling down the loop “time constant,” $(\zeta\omega_n)^{-1} = 4\pi M/(R_1 I_p K_{VCO})$, by a factor of K .

Loop Simulation: Behavioral Model

  In addition to time contraction, we also employ a behavioral model for the VCO with the same value of K_{VCO} and f_{out}





- The PFD, the CP, and the loop filter incorporate actual devices, thus producing a realistic ripple. The loop locks in about 150 ns, incurring a peak-to-peak ripple of nearly 30 mV.
- We observe that our choice of the loop parameters has yielded a well-behaved lock response. This simulation takes about 40 seconds.

Simulations of Transfer Function

➤ One-pole approximation

 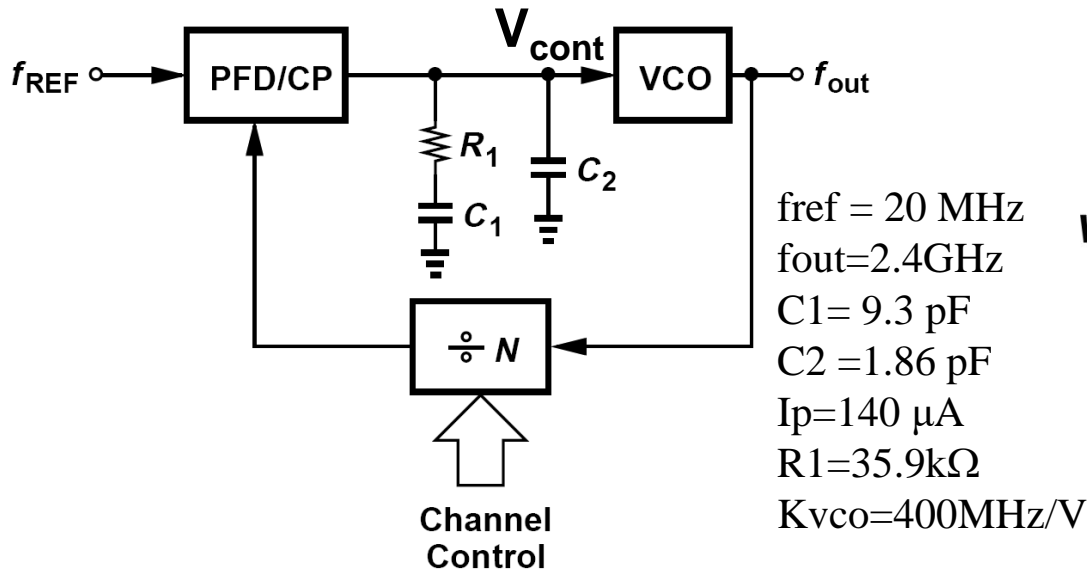B. Razavi, Design of CMOS Phase-locked Loops, Ch 9.5, pp. 289



- Approximate the transfer function of a PLL as a one-pole system. The PLL locked at V_0 & V_1 .
- $t_2 - t_1 = \tau \times \ln(2) = 0.69 \times \tau$, where τ is the time constant.
- The closed-loop bandwidth is $1/(2\pi\tau)$
- Note as $\zeta=1$, it leads to two coincident poles and the one pole approximation does not hold.


Simulations of Transfer Function

➤ By input FM source

$$V_{FM}(t) = V_a + V_a \cos[\omega_{REF}t + K \int \cos \omega_m t dt]$$

$$V_{FM}(t) = V_a + V_a \cos \left(\omega_{REF}t + \frac{K}{\omega_m} \sin \omega_m t \right)$$

- A clock with an input frequency is modulated by a cosine. Its input peak-to-peak phase variation is $2K/\omega_m$ and the output phase variation should be reduced by a factor of $\sqrt{2}$ at the -3dB frequency.
- While $\omega_m = 2\pi(1\text{MHz})$ with a peak-to-peak jitter of 31ps, the transient simulation is done (simulation time is over 1us after the PLL locked). The simulated PLL at the divider output with a peak-to-peak jitter of 25ps.
- It translate to an attenuation of 1.9dB.

 

Simulations of Transfer Function

➤ Do the transient simulations for various ω_m .

➤ Estimated ω_{3dB} is around 1.2MHz.

fref = 20 MHz

fout=2.4GHz

C1= 9.3 pF

C2 =1.86 pF

I_p=140 μ A


R1=35.9k Ω

K_{vco}=400MHz/V


➤ Calculated $\omega_z = 1/(2\pi C_1 R_1) \sim 477$ kHz,

$\omega_{3dB} = 2\pi (2.4\text{MHz})$

 ➤ It is not consistent between the calculations and simulations. It is partially occurs because the pole caused by C2R1 is not far from the unity gain frequency.



 
Simulation/Measurement of Transfer Function



- By observing both input and output spectra, the sidebands are induced by phase modulations.
- The ratio of input to output jitter is given by $\Delta_2 + 20\log(N) - \Delta_1$ in dB (N is the divide ratio of 120).
- Note that the measurement can be done by this way.

IEEE TCAS-II, vol. 68, pp. 873-, March 2021.

 Simulations of Phase Noise & Transfer Function





- A White-Noise-Spectrum voltage source is applied in series to the supply of the input inverter of the PLL.
- This noise modulates the delay of inverter thereby inducing an output phase that has a K_{DD} different from K_{VCO} .

$$V_{inv}(t) = V_a + V_a \cos(\omega_{REF}t + K_{DD}V_n)$$


- PSS (periodic steady state) and Pnoise (periodic noise) analysis are done in Cadence to simulate the transfer function for the phase modulated input.

  Simulations of Phase Noise & Transfer Function



- To avoid the convergence issue, we put resistors of 1MΩ tied to ground for the NOR gates in pss simulation. The simulation time should be long enough such that the PLL settles.
- RC network is used to generate a band-limited noise which is amplified 1000 times so that this phase modulation far exceeds the intrinsic PLL phase noise.

Simulations of Transfer Function

 

- Since the PLL's internal noise sources contribute much less phase noise, the phase noise plots reflect the PLL transfer function.
- For $C_2=1.86$ pF, the noise peak is 2.7dB and $\omega_{3dB}=2\pi$ (2.5MHz) which close to the calculated 2.4MHz.
- For $C_2=0.93$ pF, the noise peak is 1.7dB and $\omega_{3dB}=2\pi$ (2.8MHz)
- A lower C yields lower area under phase noise plot (random jitter reduces) but the ripple in Vcont increase (deterministic jitter increases)