



# Study of 10GBase-T Transmitter


指導教授：汪重光  
學生：葉治億



- Survey on IEEE 802.3an task force material
- The impairment of the DAC
- Random walk method
- Dynamic random walk
- Working Items



# PSD Specification

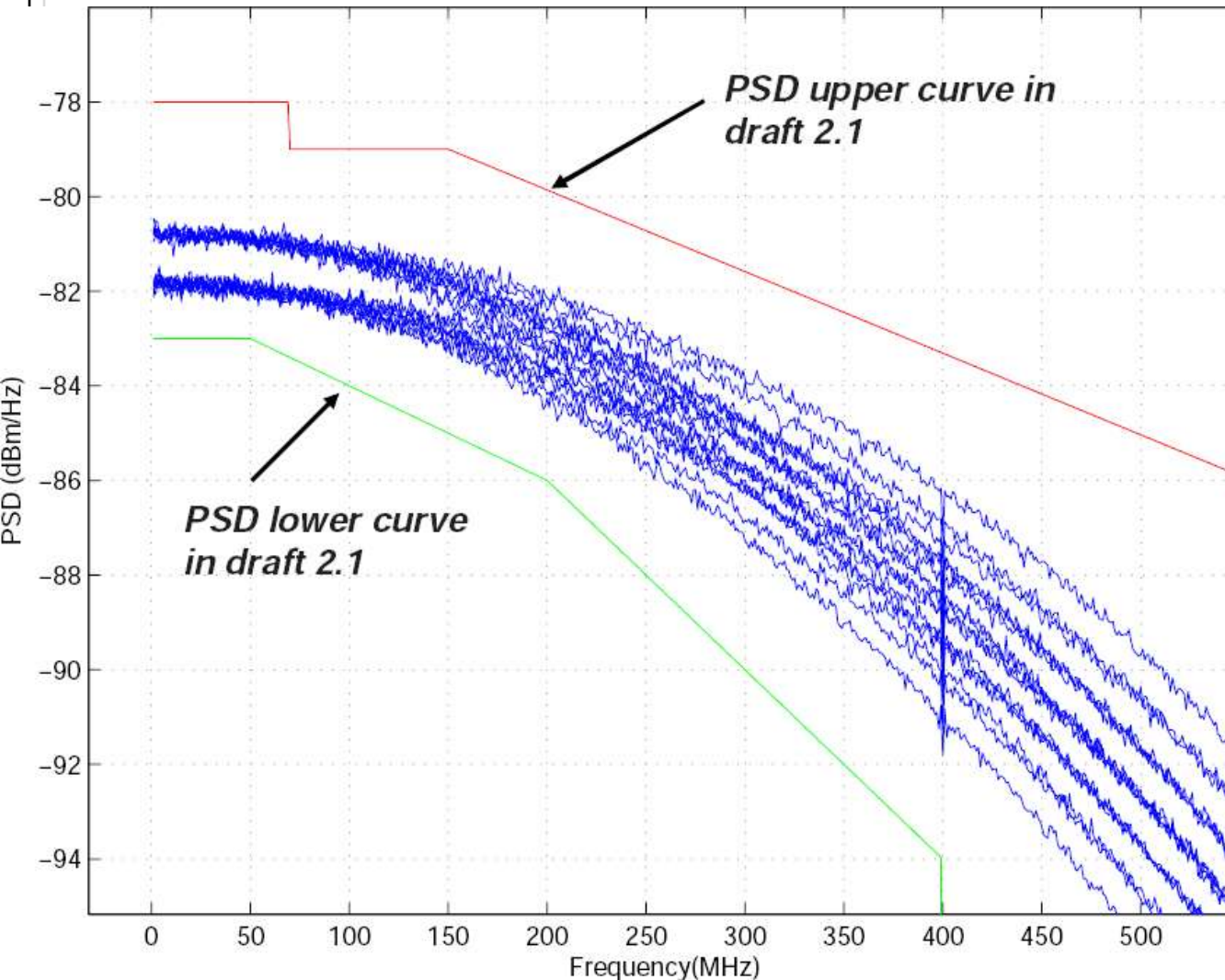


**Note:**

- With 2V +/- 6% at the transformer output, the lower PSD curve has smaller margin at lower end.
- 2V +/- 6% with the filter tolerances as specified meets the power spec
- Upper PSD has a larger margin, especially the lower 0-70MHz range.


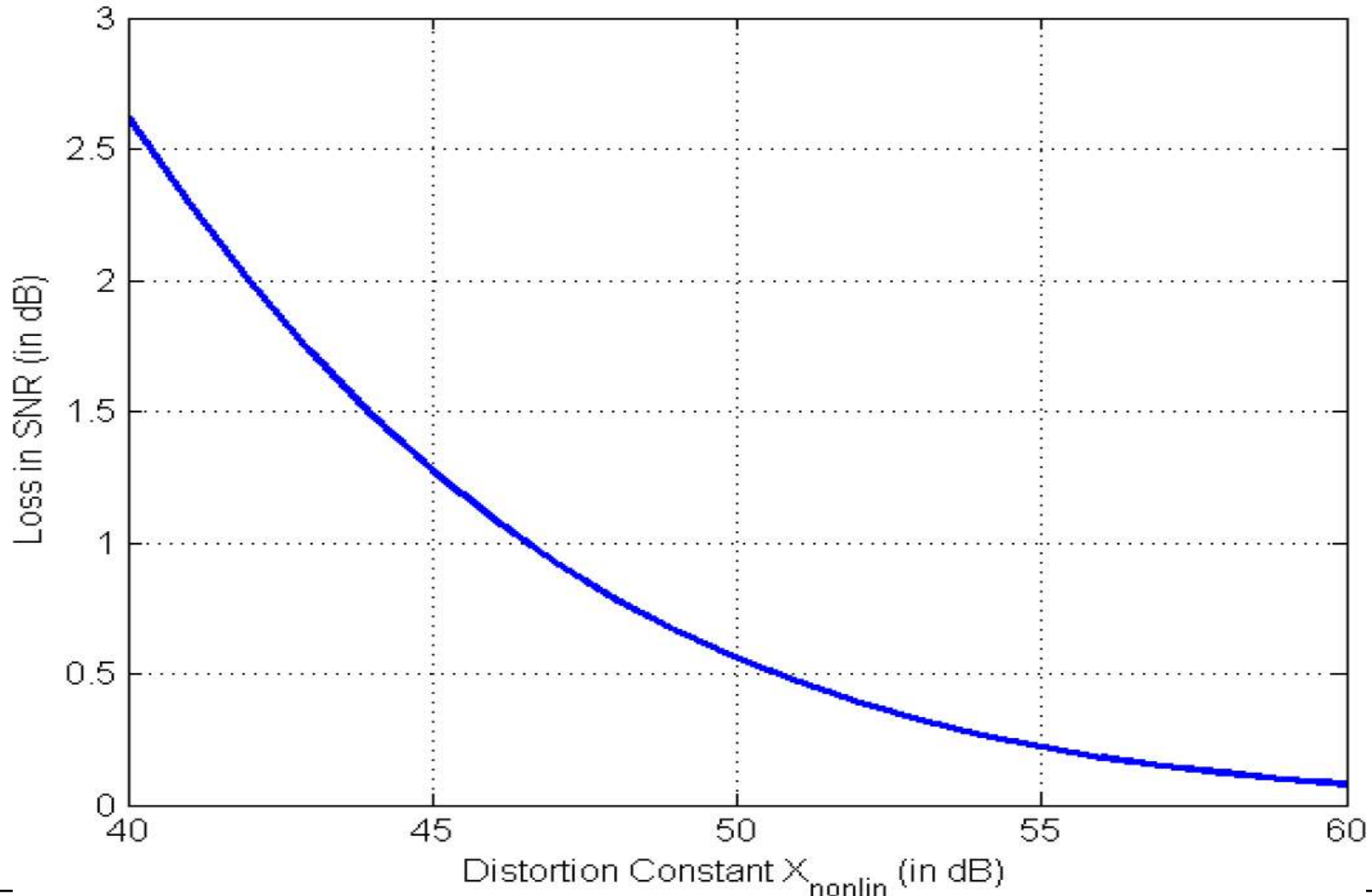
# Nonlinear Distortion


SNR Loss vs. Distortion Constant for 100m Class E Cable




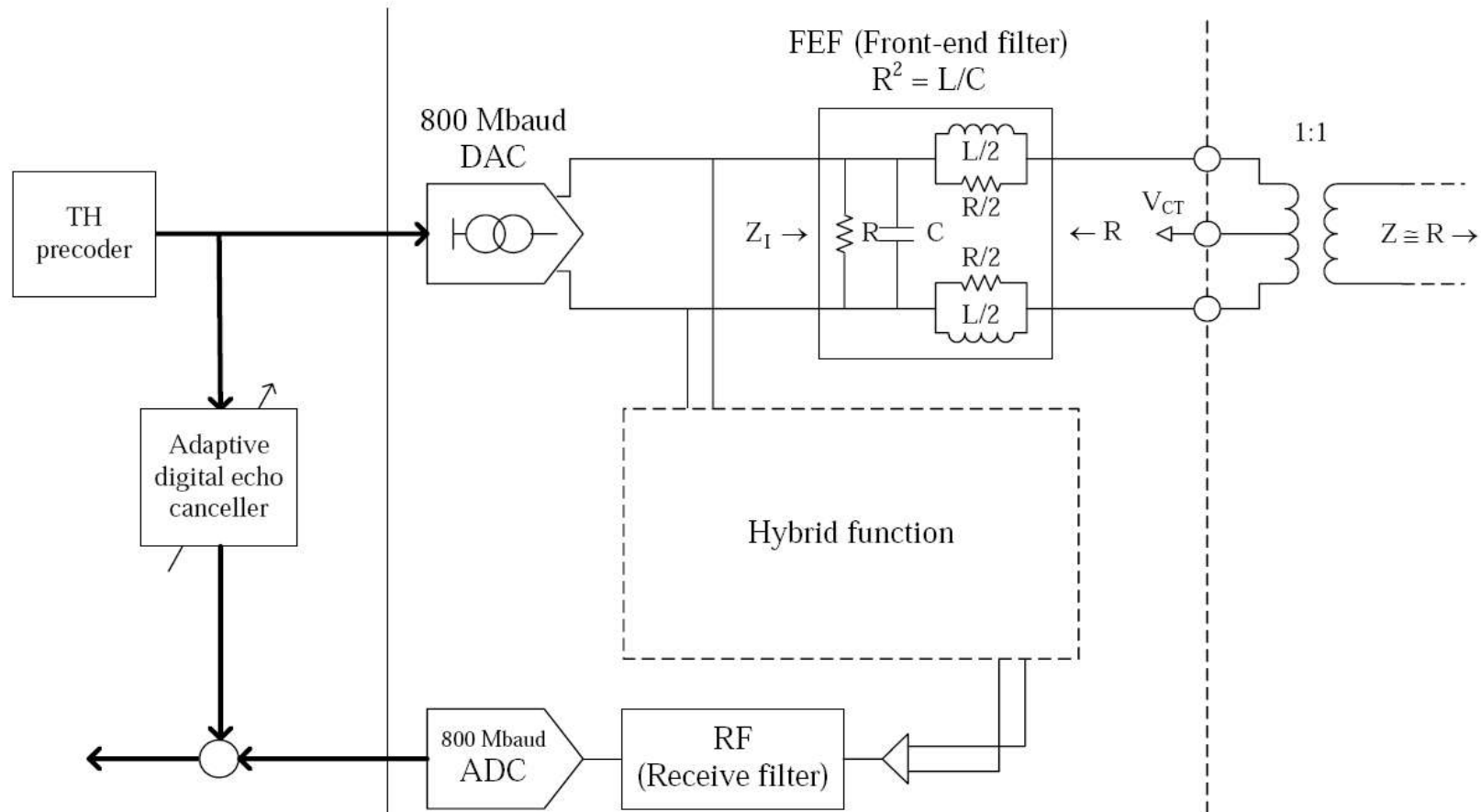
# Transmitter from Broadcom (I)


No digital filtering, T-spaced DAC, front-end filter with frequency-dependent input impedance  $Z_I$  and constant output impedance  $R$





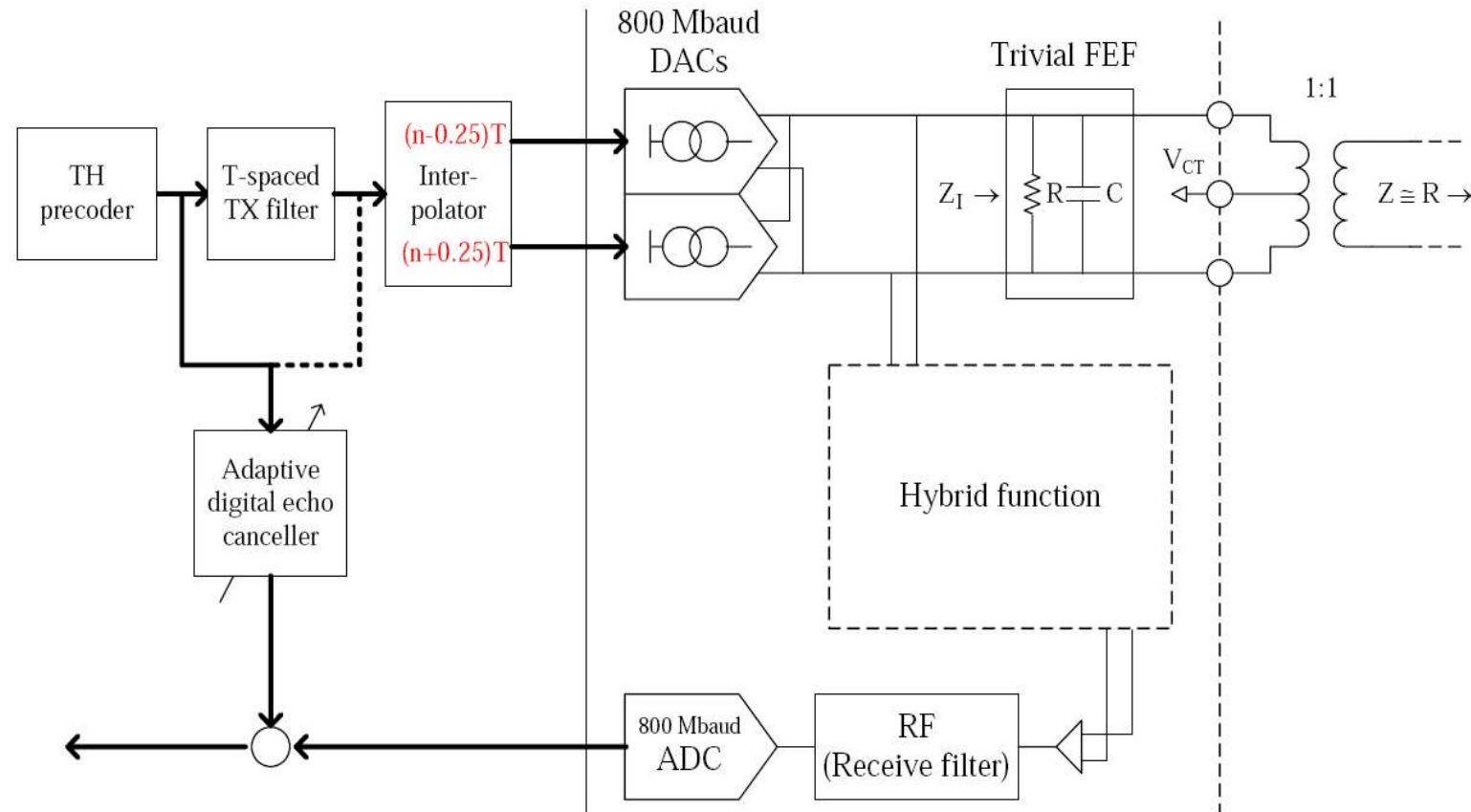
# Transmitter from Broadcom (II)

Digital TX-filtering & T/2-interpolation, T/2-overlapping DACs,  
trivial front-end filter






# Transmitter from Broadcom (III)

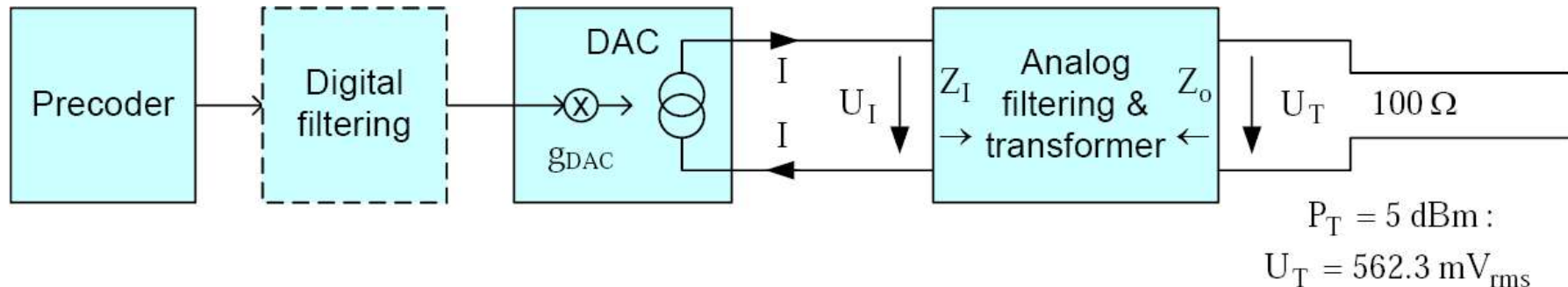

Baseline approach:  $I = 15.9 \text{ mA}_{\text{rms}}$ ,  $U_I = 891.1 \text{ mV}_{\text{rms,diff}} \triangleq V_{\text{CT}} \pm 445 \text{ mV}_{\text{rms}}$

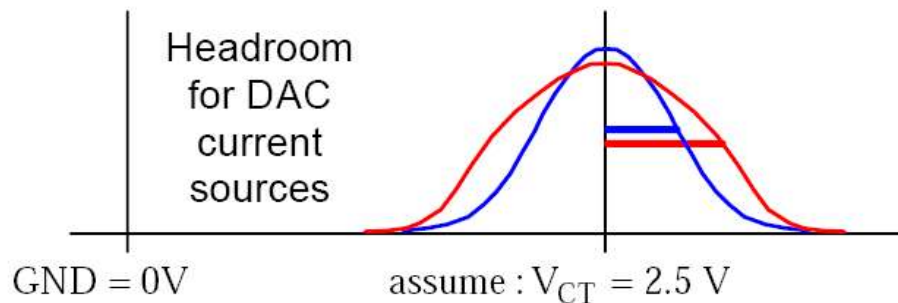Preferred approach:  $I = 12.7 \text{ mA}_{\text{rms}}$ ,  $U_I = 630.7 \text{ mV}_{\text{rms,diff}} \triangleq V_{\text{CT}} \pm 315.3 \text{ mV}_{\text{rms}}$



Preferred approach has lower (-3 dB) rms-voltage at DAC outputs than baseline approach, but (presumably) higher peak-to-average ratio.





# The Impairment of the DAC


- DC accuracy
  - Random errors: device mismatches
  - Systemic errors:
    - Linear gradient: common centroid
    - Higher order effects
- AC accuracy
  - Voltage Fluctuation
  - Control signals feedthrough
  - Clock synchronization




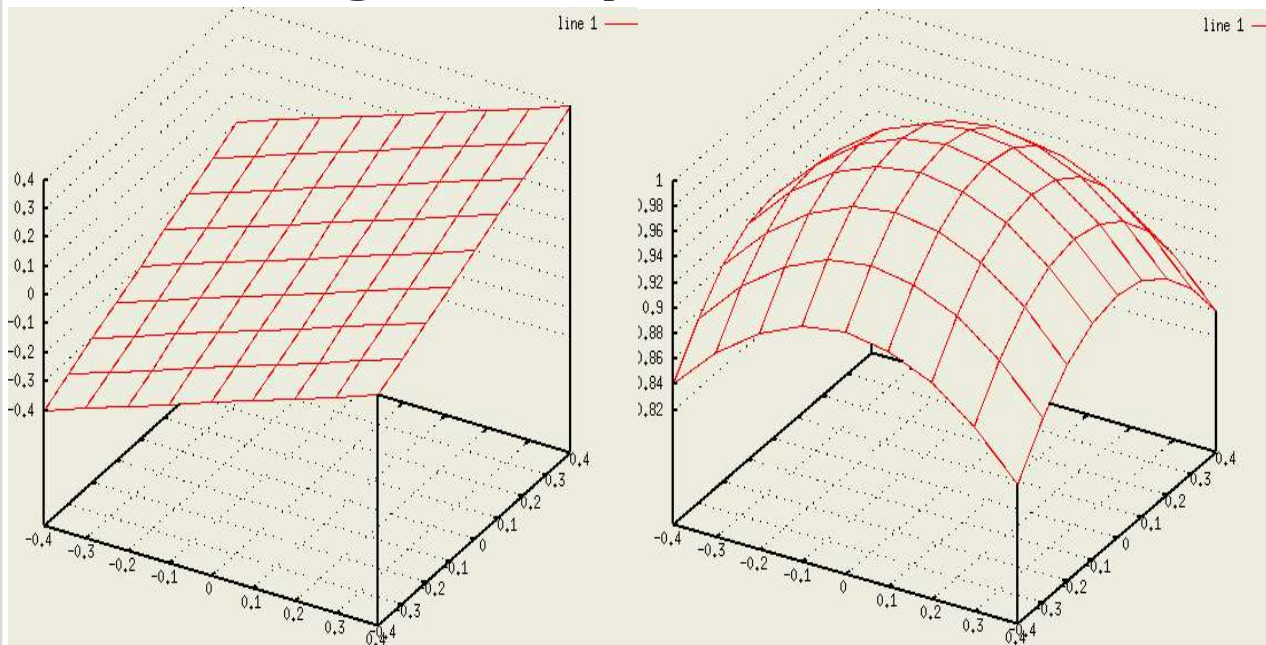
# Random Walk Method

- Use random walk method to mitigate systemic mismatch




1	2	3						
							3	
			1					

[Geert A. M. et al, "A 14-bit Intrinsic Accuracy Q<sup>2</sup> Random Walk CMOS DAC", IEEE JSSC Vol. 34, No. 12, Dec. 1999]






# Dynamic Random Work

- Use switch as round robin

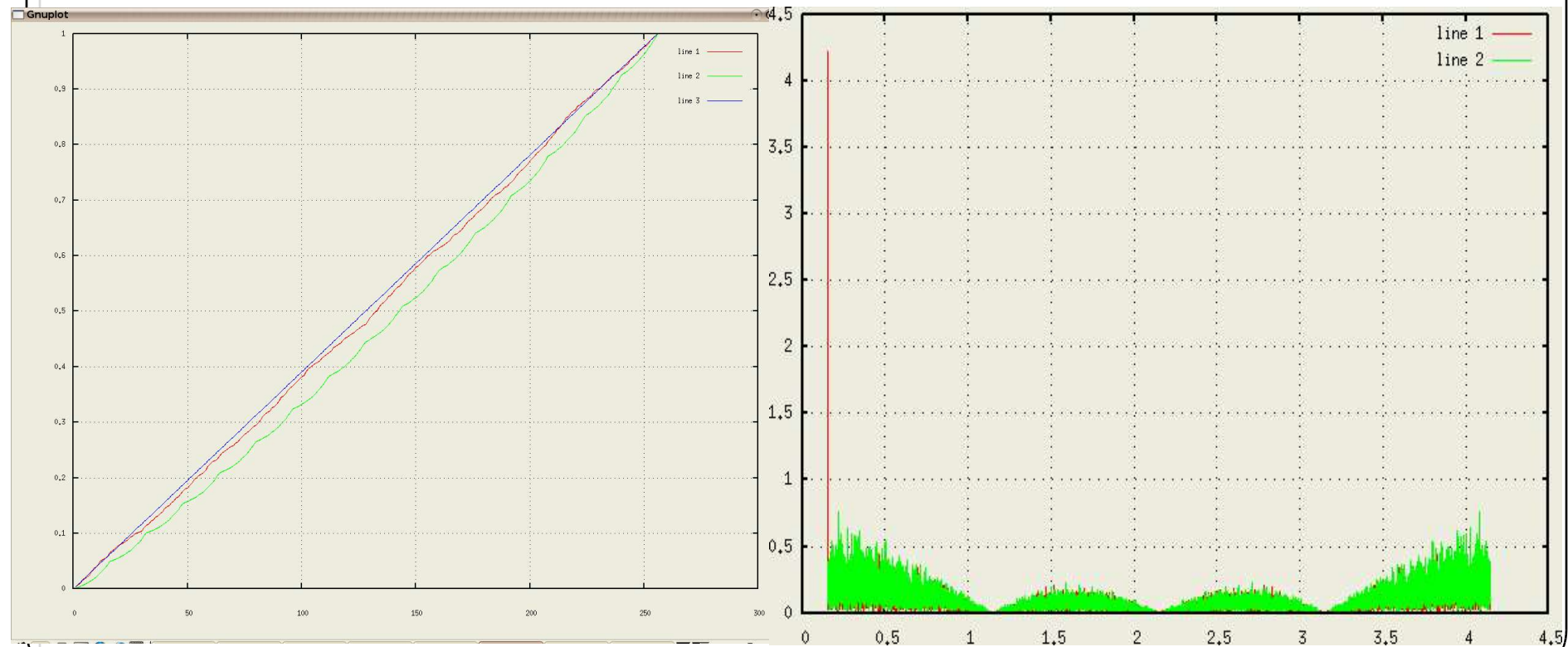



# Spur in the Sine Wave Simulation

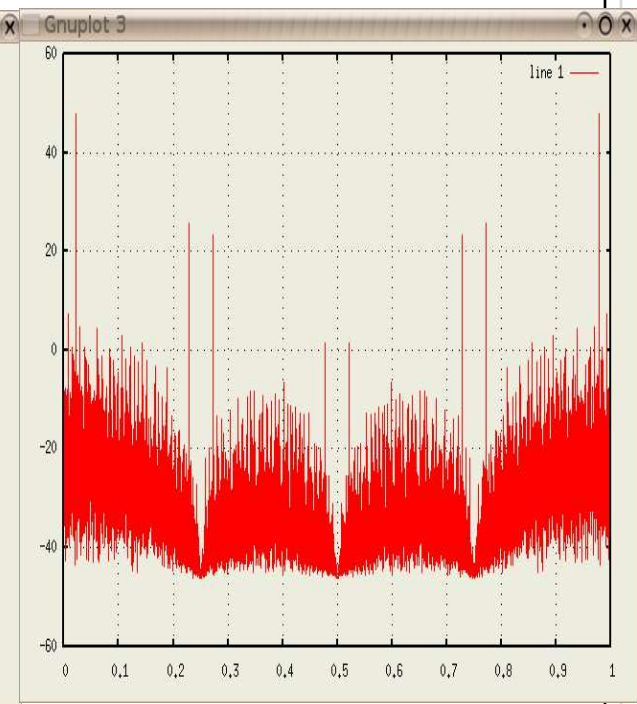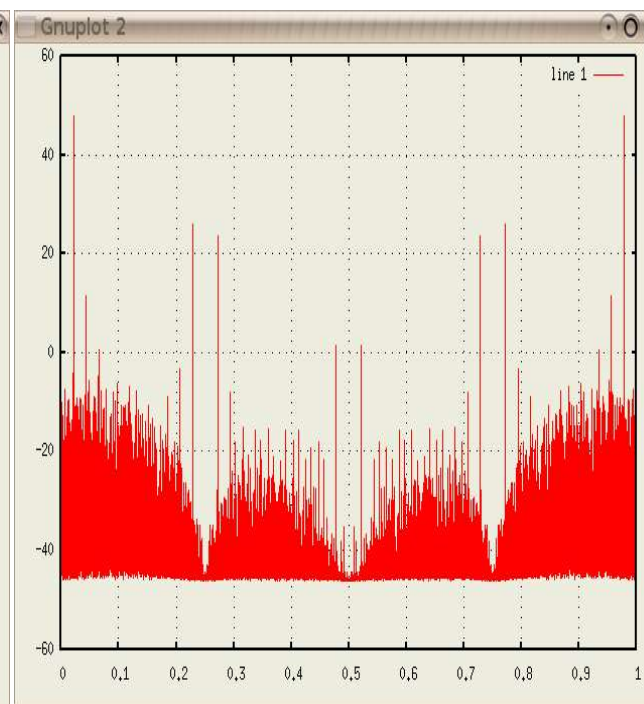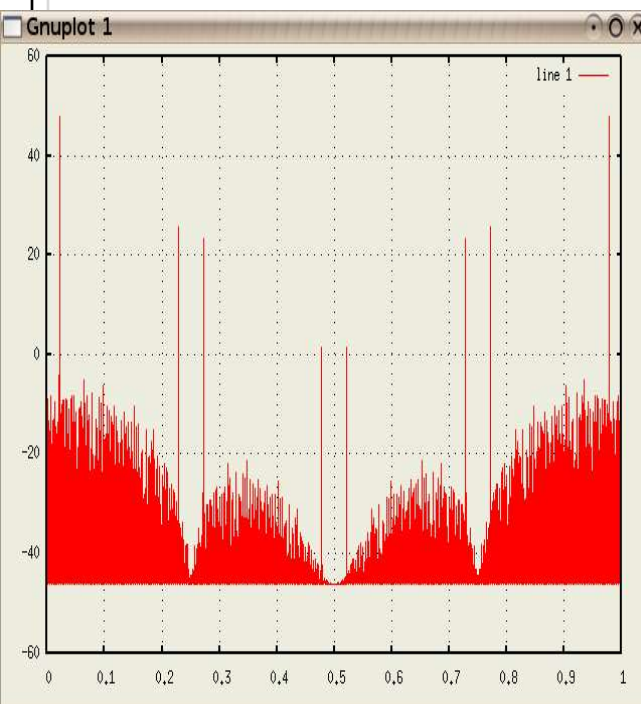



# Working Items

## **10Gbase-T Transmitter**

☒ Transmitter architecture design

☒ DAC design

☒ System design

☐ Circuits design

☐ Layout and verification

☐ Line driver design

☐ System design

☐ Circuits design

☐ Layout and verification

☐ Hybrid design

☐ System design

☐ Circuits design

☐ Layout and verification

■ Finished    ☒ On-going    ☐ Future work