

電工學 HW 5 Solution

$$\begin{aligned}
 \text{P5.16} \quad V_{rms} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\int_0^1 [3 \exp(-t)]^2 dt} = \sqrt{\int_0^1 [9 \exp(-2t)] dt} \\
 &= \sqrt{[-4.5 \exp(-2t)]_{t=0}^{t=1}} = \sqrt{4.5[1 - \exp(-2)]} = 1.973 \text{ V}
 \end{aligned}$$

$$\text{P5.22*} \quad \omega = 2\pi f = 400\pi$$

$$v_1(t) = 10 \cos(400\pi t + 30^\circ)$$

$$v_2(t) = 5 \cos(400\pi t + 150^\circ)$$

$$v_3(t) = 10 \cos(400\pi t + 90^\circ)$$

$$v_1(t) \text{ lags } v_2(t) \text{ by } 120^\circ$$

$$v_1(t) \text{ lags } v_3(t) \text{ by } 60^\circ$$

$$v_2(t) \text{ leads } v_3(t) \text{ by } 60^\circ$$

P5.25

$$v_1(t) = 100 \cos(\omega t + 45^\circ)$$


$$v_2(t) = 150 \sin(\omega t + 60^\circ) = 150 \cos(\omega t - 30^\circ)$$

$$\mathbf{V}_1 = 100 \angle 45^\circ = 70.71 + j70.71$$

$$\mathbf{V}_2 = 150 \angle -30^\circ = 129.9 - j75$$

$$\mathbf{V}_s = \mathbf{V}_1 + \mathbf{V}_2 = 200.6 - j4.29 = 200.6 \angle -1.23^\circ$$
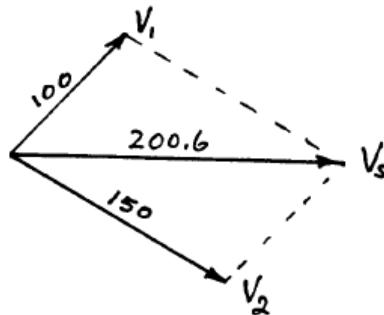
$$v_s(t) = 200.6 \cos(\omega t - 1.23^\circ)$$




V_2 lags V_1 by 75°

V_s lags V_1 by 46.23°

V_s leads V_2 by 28.77°

P5.26 $V_m = 3 \text{ V}$ $T = 0.5 \text{ s}$
 $f = \frac{1}{T} = 2 \text{ Hz}$ $\omega = 2\pi f = 4\pi \text{ rad/s}$
 $\theta = -360^\circ \frac{t_{\max}}{T} = -45^\circ$
 $v(t) = 3 \cos(4\pi t - 45^\circ) \text{ V}$
 $\mathbf{V} = 3 \angle -45^\circ \text{ V}$
 $V_{rms} = \frac{3}{\sqrt{2}} = 2.121 \text{ V}$

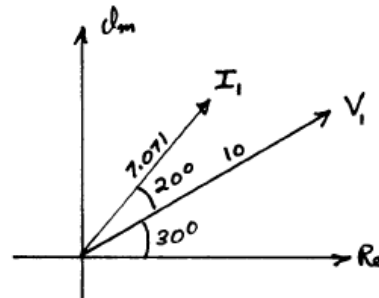P5.27 $v_1(t) = 10 \cos(\omega t + 30^\circ)$
 $I_{1m} = \sqrt{2} \times I_{1rms} = 7.071$
 $\mathbf{V}_1 = 10 \angle 30^\circ$
 $\mathbf{I}_1 = 7.071 \angle 50^\circ$
 $i_1(t) = 7.071 \cos(\omega t + 50^\circ)$



P5.35 (a) Notice that the voltage is a sine rather than a cosine.
 $\mathbf{V} = 100 \angle -60^\circ$ $\mathbf{I} = 1 \angle 30^\circ$ $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 100 \angle -90^\circ = -j100$
 Because \mathbf{Z} is pure imaginary and negative, the element is a capacitance.
 $\omega = 200$ $C = \frac{1}{|\mathbf{Z}| \omega} = 50 \mu\text{F}$

(b) $\mathbf{V} = 500 \angle 50^\circ$ $\mathbf{I} = 2 \angle 50^\circ$ $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 250 \angle 0^\circ = 250 + j0$
 Because \mathbf{Z} is pure real, the element is a resistance of 250Ω .


(c) Notice that the current is a sine rather than a cosine.
 $\mathbf{V} = 100 \angle 30^\circ$ $\mathbf{I} = 1 \angle -60^\circ$ $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = 100 \angle 90^\circ = j100$
 Because \mathbf{Z} is pure imaginary and positive, the element is an inductance.
 $\omega = 400$ $L = \frac{|\mathbf{Z}|}{\omega} = 0.25 \text{ H}$

5.38 (a) From the plot, we see that $T = 4 \text{ ms}$, so we have $f = 1/T = 250 \text{ Hz}$ and $\omega = 500\pi$. Also, we see that the current lags the voltage by 1 ms or 90° , so we have an inductance. Finally, $\omega L = V_m / I_m = 5 \Omega$, from which we find that $L = 3.18 \text{ mH}$.
 (b) From the plot, we see that $T = 8 \text{ ms}$, so we have $f = 1/T = 125 \text{ Hz}$ and $\omega = 250\pi$. Also, we see that the current leads the voltage by 2 ms or

90° , so we have a capacitance. Finally, $1/\omega C = V_m / I_m = 2500 \Omega$, from which we find that $C = 0.5093 \mu\text{F}$.


P5.42
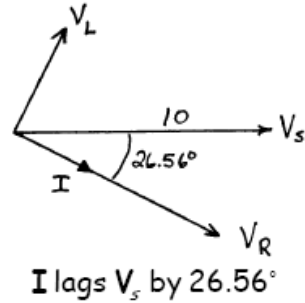
$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{R + j\omega L} \\ &= \frac{10 \angle 0^\circ}{100 + j50} \\ &= 89.44 \angle -26.56^\circ \text{ mA} \\ \mathbf{V}_R &= R\mathbf{I} = 8.944 \angle -26.56^\circ \text{ V} \\ \mathbf{V}_L &= j\omega L\mathbf{I} = 4.472 \angle 63.44^\circ \text{ V} \end{aligned}$$




P5.47
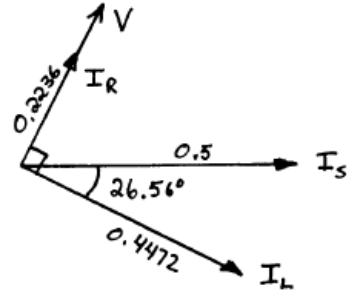
$$\begin{aligned} \mathbf{I}_s &= 0.5 \angle 0^\circ \\ \mathbf{V} &= \mathbf{I}_s \frac{1}{1/200 + 1/j100} \\ &= 44.72 \angle 63.44^\circ \\ \mathbf{I}_R &= \mathbf{V}/R = 0.2236 \angle 63.44^\circ \\ \mathbf{I}_L &= \mathbf{V}/j\omega L = 0.4472 \angle -26.56^\circ \\ \mathbf{V} &\text{ leads } \mathbf{I}_s \text{ by } 63.44^\circ \end{aligned}$$



P5.50

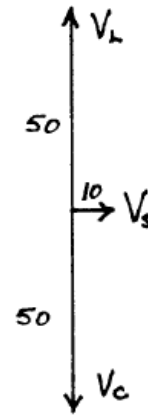
$$\begin{aligned} \mathbf{V}_s &= 10 \angle 0^\circ \\ \mathbf{I} &= \frac{\mathbf{V}_s}{j\omega L + R - j/\omega C} \\ &= \frac{10}{j500 + 100 - j500} \\ &= 0.1 \angle 0^\circ \text{ A} \\ \mathbf{V}_L &= j500 \times \mathbf{I} = 50 \angle 90^\circ \\ \mathbf{V}_R &= 100\mathbf{I} = 10 \angle 0^\circ \\ \mathbf{V}_C &= -j500\mathbf{I} = 50 \angle -90^\circ \end{aligned}$$



The peak value of $v_L(t)$ is five times larger than the source voltage! This is possible because the impedance of the capacitor cancels the impedance of the inductance.

P5.52
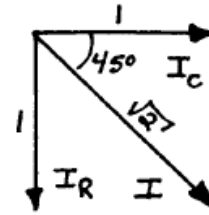
$$\begin{aligned} Z_{total} &= j\omega L + \frac{1}{1/R + j\omega C} \\ &= j100 + \frac{1}{0.01 + j0.01} \\ &= j100 + 50 - j50 \\ &= 50 + j50 \\ &= 70.71 \angle 45^\circ \end{aligned}$$



$$\mathbf{I} = \frac{100 \angle 0^\circ}{Z_{total}} = 1.414 \angle -45^\circ$$

$$\begin{aligned} \mathbf{I}_R &= \mathbf{I} \frac{Z_C}{R + Z_C} = (1.414 \angle -45^\circ) \times \frac{-j100}{100 - j100} \\ &= 1 \angle -90^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \mathbf{I} \frac{R}{R + Z_C} = (1.414 \angle -45^\circ) \times \frac{100}{100 - j100} \\ &= 1 \angle 0^\circ \end{aligned}$$

P5.56 Writing KCL equations at nodes 1 and 2 we obtain

$$\frac{V_1}{10} + \frac{V_1 - V_2}{5 + j15} = 1 \angle 0^\circ$$

$$\frac{V_2}{-j10} + \frac{V_2 - V_1}{5 + j15} = 1 \angle 30^\circ$$

Solving these equations, we obtain

$$V_1 = 6.735 \angle -38.54^\circ$$

$$V_2 = 16.25 \angle -55.52^\circ$$

P5.71 $\theta = \theta_v - \theta_i = 30^\circ - 60^\circ = -30^\circ$

power factor = $\cos(\theta) = 86.60\%$ leading

$$P = V_{rms} I_{rms} \cos(\theta) = 12.99 \text{ kW}$$

$$Q = V_{rms} I_{rms} \sin(\theta) = -7.5 \text{ kVAR}$$

apparent power = $V_{rms} I_{rms} = 1000 \times 15 = 15 \text{ KVA}$

$$Z = \frac{V}{I} = \frac{1000 \sqrt{2} \angle 30^\circ}{15 \sqrt{2} \angle 60^\circ} = 66.67 \angle -30^\circ$$

$$\text{P5.76} \quad \mathbf{I} = \frac{240\sqrt{2}\angle 50^\circ - 220\sqrt{2}\angle 30^\circ}{1 + j2} = 52.03\angle 52.71^\circ$$

$$I_{rms} = 36.79 \text{ A}$$

Delivered by Source A:

$$P_A = 240I_{rms} \cos(50 - 52.71) = 8.820 \text{ kW}$$

$$Q_A = 240I_{rms} \sin(50 - 52.71) = -0.418 \text{ kVAR}$$

Absorbed by Source B:

$$P_B = 220I_{rms} \cos(30 - 52.71) = 7.467 \text{ kW}$$

$$Q_B = 220I_{rms} \sin(30 - 52.71) = -3.125 \text{ kVAR}$$

Absorbed by resistor:

$$P_R = I_{rms}^2 R = 1.353 \text{ kW}$$

Absorbed by inductor:

$$Q_L = I_{rms}^2 X = 2.707 \text{ kVAR}$$

$$\text{P5.82} \quad \text{Load A:} \quad P_A = 5 \text{ kW}$$

$$\theta_A = \cos^{-1}(0.9) = 25.84^\circ$$

$$Q_A = P_A \tan \theta_A = 2.421 \text{ kVAR}$$

$$\text{Load B:} \quad P_B = 10 \text{ kW}$$

$$\theta_B = \cos^{-1}(0.8) = -36.86^\circ$$

(θ is negative for a leading power factor.)

$$Q_B = P_B \tan \theta_B = -7.5 \text{ kVAR}$$


$$\text{Source:} \quad P_s = P_A + P_B = 15 \text{ kW}$$

$$Q_s = Q_A + Q_B = -5.079 \text{ kVAR}$$

$$\text{Apparent power} = \sqrt{(P_s)^2 + (Q_s)^2} = 15.84 \text{ kVA}$$

$$\text{Power factor} = \frac{P_s}{\text{Apparent power}} = 0.9472 = 94.72\% \text{ leading}$$

P5.90 Zeroing sources, we have:

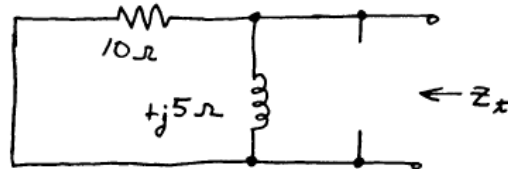

Thus, the Thévenin impedance is

$$Z_T = \frac{1}{1/10 + 1/j5} = 4.472\angle 63.43^\circ = 2 + j4$$


Writing a current equation for the node at the upper end of the current source under open circuit conditions, we have

$$\frac{V_{oc} - 100\angle 45^\circ}{10} + \frac{V_{oc}}{j5} = 5$$

$$V_t = V_{oc} = 62.56\angle 93.80^\circ$$

$$I_n = V_t / Z_t = 13.99\angle 30.36^\circ$$

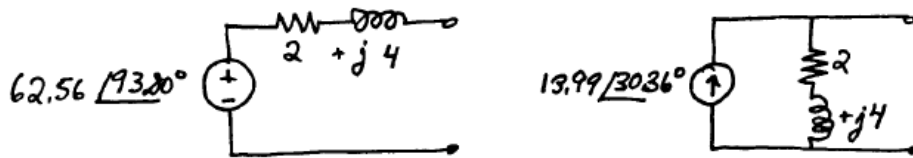Thus, the Thévenin and Norton equivalent circuits are:



For the maximum power transfer, the load impedance is

$$Z_{load} = 2 - j4$$

$$I_{load} = \frac{V_t}{Z_t + Z_{load}} = \frac{62.56\angle 93.80^\circ}{2 + j4 + 2 - j4} = 15.64\angle 93.80^\circ$$

$$P_{load} = R_{load} (I_{rms-load})^2 = 244.6 \text{ W}$$

In the case for which the load must be pure resistance, the load for maximum power transfer is

$$Z_{load} = |Z_t| = 4.472$$

$$I_{load} = \frac{V_t}{Z_t + Z_{load}} = \frac{62.56\angle 93.80^\circ}{2 + j4 + 4.472} = 8.223\angle -62.08^\circ$$

$$P_{load} = R_{load} (I_{rms-load})^2 = 151.2 \text{ W}$$

- P5.91** At the lower left-hand node under open-circuit conditions, KCL yields $I_x = 0.5I_x$ from which we have $I_x = 0$. Then, the voltages across the $5\text{-}\Omega$ resistance and the $j5\text{-}\Omega$ inductance are zero, and KVL yields

$$V_t = V_{ba-oc} = 3\angle 30^\circ$$

With short circuit conditions, we have



$$I_x = -\frac{3\angle 30^\circ}{5 + j5} = 0.4243\angle 165^\circ$$

$$I_n = I_{ba-sc} = 0.5I_x - I_x = 0.2121\angle -15^\circ$$

The Thévenin impedance is given by

$$Z_t = \frac{V_t}{I_t} = \frac{3 \angle 30^\circ}{0.2121 \angle -15^\circ} = 14.14 \angle 45^\circ$$

Finally, the equivalent circuits are:

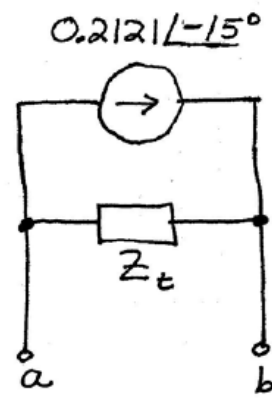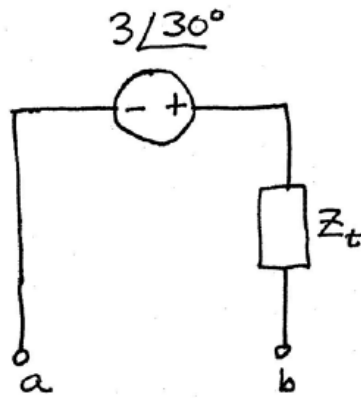

P5.92 Under open-circuit conditions, we have

$$V_t = V_{ab-oc} = (4 + j3)2 \angle 0^\circ = 10 \angle 36.87^\circ \text{ V}$$

With the source zeroed, we look back into the terminals and see

$$Z_t = -j3 + j3 + 4 = 4 \Omega$$

Next, the Norton current is

$$I_n = \frac{V_t}{Z_t} = 2.5 \angle 36.87^\circ$$

