

$V_1$  is the initial voltage

Fig.1 shows the coupled transmission line pair

The capacitive coupling induces a differential crosstalk current  $\Delta I_{c2}$ , flowing into the ungrounded conductor of line 2, given by

$$\Delta I_{c2}(\xi, t) = C_m \Delta \xi \frac{\partial V_1(\xi, t)}{\partial t} \quad (1)$$

where  $V_1(\xi, t)$  is the line-1 voltage

The inductive coupling induces a differential crosstalk voltage  $\Delta V_{c2}$ , which is given by

$$\Delta V_{c2}(\xi, t) = L_m \Delta \xi \frac{\partial I_1(\xi, t)}{\partial t} \quad (2)$$

where  $I_1 = \frac{V_1}{Z_0}$

Combining the contributions due to capacitive coupling and inductive coupling, we obtain the total differential voltages induced to the right and left of  $z = \xi$  to be

$$\begin{aligned} \Delta V_2^+ &= \frac{1}{2} Z_0 \Delta I_{c2} - \frac{1}{2} \Delta V_{c2} \\ \Delta V_2^- &= \frac{1}{2} Z_0 \Delta I_{c2} + \frac{1}{2} \Delta V_{c2} \end{aligned} \quad (3)$$

Substituting (1) and (2) into (3), we have

$$\begin{aligned} \Delta V_2^+(\xi, t) &= \left[ \frac{1}{2} C_m Z_0 \frac{\partial V_1(\xi, t)}{\partial t} - \frac{1}{2} L_m \frac{\partial I_1(\xi, t)}{\partial t} \right] \Delta \xi \\ &= \frac{1}{2} \left( C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{\partial V_1(\xi, t)}{\partial t} \Delta \xi \end{aligned} \quad (4)$$

$$\Delta V_2^-(\xi, t) = \frac{1}{2} \left( C_m Z_0 + \frac{L_m}{Z_0} \right) \frac{\partial V_1(\xi, t)}{\partial t} \Delta \xi \quad (5)$$

Integrate (4) to obtain the induced voltage on line 2

$$\begin{aligned}
V_2^+(z,t) &= \int_0^z \frac{1}{2} \left( C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{\partial}{\partial t} \left[ V_1 \left( t - \frac{\xi}{v_p} - \frac{z-\xi}{v_p} \right) \right] d\xi \\
&= \frac{1}{2} \left( C_m Z_0 - \frac{L_m}{Z_0} \right) \int_0^z \frac{\partial V_1(t - z/v_p)}{\partial t} d\xi
\end{aligned}$$

or  $V_2^+(z,t) = zK_f V_1'(t - z/v_p)$

where  $K_f$  is the forward-crosstalk coefficient

$$K_f = \frac{1}{2} \left( C_m Z_0 - \frac{L_m}{Z_0} \right)$$

Since the effect of  $V_1$  at  $z = \xi$  at time  $t$  propagate to a location  $z < \xi$  on line 2 at time  $t + (\xi - z)/v_p$ . Hence, by integrating (5) over proper integral, we have

$$\begin{aligned}
V_2^-(z,t) &= \int_z^l \frac{1}{2} \left( C_m Z_0 + \frac{L_m}{Z_0} \right) \frac{\partial}{\partial t} \left[ V_1 \left( t - \frac{\xi}{v_p} - \frac{\xi-z}{v_p} \right) \right] d\xi \\
&= \frac{1}{2} \left( C_m Z_0 + \frac{L_m}{Z_0} \right) \int_z^l \frac{\partial}{\partial t} \left[ V_1 \left( t + \frac{z}{v_p} - \frac{2\xi}{v_p} \right) \right] d\xi \\
&= -\frac{1}{4} v_p \left( C_m Z_0 + \frac{L_m}{Z_0} \right) \int_z^l \frac{\partial}{\partial t} \left[ V_1 \left( t + \frac{z}{v_p} - \frac{2\xi}{v_p} \right) \right] d\xi
\end{aligned}$$

or  $V_2^-(z,t) = K_b \left[ V_1 \left( t - \frac{z}{v_p} \right) - V_1 \left( t - \frac{2l}{v_p} + \frac{z}{v_p} \right) \right]$

where  $K_b$  is the backward-crosstalk coefficient

$$K_b = \frac{1}{4} v_p \left( C_m Z_0 + \frac{L_m}{Z_0} \right)$$

In summary, the (+) wave on line 2 is

$$\begin{aligned}
V_2^+(z, t) &= zK_f V_1'(t - z/v_p) \\
&= \begin{cases} zK_f V_0 / T_0, & \text{for } 0 < (t - z/v_p) < T_0 \\ V_0, & \text{otherwise} \end{cases} \\
&= \begin{cases} zK_f V_0 / T_0, & \text{for } (z/l)T < t < [(z/l)t + T_0] \\ V_0, & \text{otherwise} \end{cases}
\end{aligned}$$

The (-) wave on line 2 is

$$V_2^-(z, t) = K_b [V_1(t - z/v_p) - V_1(t - 2l/v_p + z/v_p)]$$

where

$$V_1\left(t - \frac{z}{v_p}\right) = \begin{cases} \frac{V_0}{T_0} \left(t - \frac{z}{l}T\right), & \text{for } \frac{z}{l}T < t < \left(\frac{z}{l}T + T_0\right) \\ V_0, & \text{for } t > \left(\frac{z}{l}T + T_0\right) \end{cases}$$

$$V_1\left(t - \frac{2l}{v_p} + \frac{z}{v_p}\right) = \begin{cases} \frac{V_0}{T_0} \left(t - 2T + \frac{z}{l}T\right), & \text{for } \left(2T - \frac{z}{l}T\right) < t < \left(2T - \frac{z}{l}T + T_0\right) \\ V_0, & \text{for } t > \left(2T - \frac{z}{l}T + T_0\right) \end{cases}$$

The induced voltage on line 2 is

$$V = V_2^+ + V_2^-$$