

Logic Synthesis and Verification

Jie-Hong Roland Jiang
江介宏

Department of Electrical Engineering
National Taiwan University



Fall 2010

1

Timing Analysis & Optimization

Reading:

Logic Synthesis in a Nutshell


Sections 5 & 6

part of the following slides are by
courtesy of Andreas Kuehlmann

2


Delay Models

Model 1

 

$A_k = \text{arrival time} = \max\{A_1, A_2, A_3\} + D_k$, where D_k is the delay at node k , parameterized according to function f_k and fanout node k

Model 2

 

Can also have different times for rise time and fall time

3

Gate Delay


The delay of a gate depends on its circuit context, and in particular:

1. Output Load

- Capacitive loading \propto the charges that a gate must move to swing the output voltage
- Due to interconnect and logic fanout

 
2. Input Slew

- Slew = transition time
- Slower transistor switching \rightarrow longer delay, longer output slew



An inverter


e.g. output $1 \rightarrow 0$

 

4

Rising and Falling Edges

 - Driving strengths of pull-up and pull-down networks may not be equivalent
 - Rising and falling outputs may have different delays




- *Idea:* maintain the latest/earliest arrival time of rising and falling transitions independently
 - Unateness of each input/output pair is encoded in the library
 - Positively unate inputs: only trigger output transitions in the same direction (e.g. an AND gate)
 - Negatively unate inputs: only trigger output transitions in the opposite direction (e.g. a NOR gate)
 - A transition on a binate input could trigger either direction on an output (e.g. an XOR gate)
 - Only considers local functionality, but allows a less conservative analysis

5

Timing Library

 - Timing library contains all relevant information about each standard cell
 - E.g., pin direction, clock, pin capacitance, etc.
- Delay (fastest, slowest, and often typical) and output slew are encoded for each input-to-output path and each pair of transition directions
- Values typically represented as 2 dimensional look-up tables (of output load and input slew)
 - Interpolation is used



```
Path(
    inputPorts(A),
    outputPorts(Z),
    inputTransition(01),
    outputTransition(10),
    "delay_table_1",
    "output_slew_table_1"
);
```


"delay_table_1"
Output Load (nF)

Input slew (ns)	1.0	2.0	4.0	10.0
0.1	2.1	2.6	3.4	6.1
0.5	2.4	2.9	3.9	7.2
1.0	2.6	3.4	4.0	8.1
2.0	2.8	3.7	4.9	10.3

6

Sequential Circuit

 - Arrival times known at I_1 , I_2 , and I_5
- Required times known at I_3 , I_4 , and I_5
- Delay analysis gives arrival and required times (hence **slacks**) for C_1 , C_2 , C_3 , C_4



7

Arrival Time Calculation

```
// level of PI nodes initialized to 0,  
// the others are set to -1.  
// Invoke LEVEL from PO  
Algorithm LEVEL(k) { // levelize nodes  
  if( k.level != -1)  
    return(k.level)  
  else  
    k.level = 1+max{LEVEL( $k_i$ ) |  $k_i \in \text{fanin}(k)$ }  
  return(k.level)  
}  
  
// Compute arrival times:  
// Given arrival times on PI's  
Algorithm ARRIVAL() {  
  for L = 1 to MAXLEVEL  
    for {k | k.level = L}  
       $A_k = \text{MAX}\{A_{k_i}\} + D_k$   
}
```


8

Required Time Calculation

Required time:

- Given required times on primary outputs
- Traverse in reverse topological order (i.e. from POs to PIs)
- If (k_i, k) is an edge between k_i and k , the required time of this edge is $R_{k_i, k} = R_k - D_k$
- The required time of output of node k is $R_k = \min \{ R_{k, k_j} \mid k_j \in \text{fanout}(k) \}$

```
// Compute required times:
// Given required times on PO's
Algorithm REQUIRED() {
  for L = MAXLEVEL-1 to 0
    for {k | k.level = L}
      R_k = MIN{R_{k, k_i}} - D_k
}
```

 


9

Slack

Slack:

 - Slack at the output of node k is $S_k = R_k - A_k$
- Since $R_{k_i, k} = R_k - D_k$
- $S_{k_i, k} = R_{k_i, k} - A_{k_i}$
- $S_{k_i, k} + A_{k_i} = R_k - D_k = S_k + A_k - D_k$
- Since $A_k = \max \{ A_{k_j} \} + D_k$
- $S_{k_i, k} = S_k + \max \{ A_{k_j} \} - A_{k_i}$ $k_j, k_i \in \text{fanin}(k)$
- $S_{k_i} = \min \{ S_{k_i, j} \}$ $j \in \text{fanout}(k_i)$



Note:

- Each edge of a circuit graph has a slack and required time
- Negative slack is bad

10

Static Timing Analysis

□ A **static critical path** of a Boolean network is a path $P = \{n_1, n_2, \dots, n_p\}$, where $S_{n_k, n_{k+1}} < 0$

■ Note:


- If a node n is on a static critical path, then at least one of the fanin edges of n is critical. Hence, all critical paths reach from an input to an output.
- There may be several critical paths

□ Timing optimization is a min-max problem:
minimize $\max\{-S_i, 0\}$

11

Static Timing Analysis

□ Example

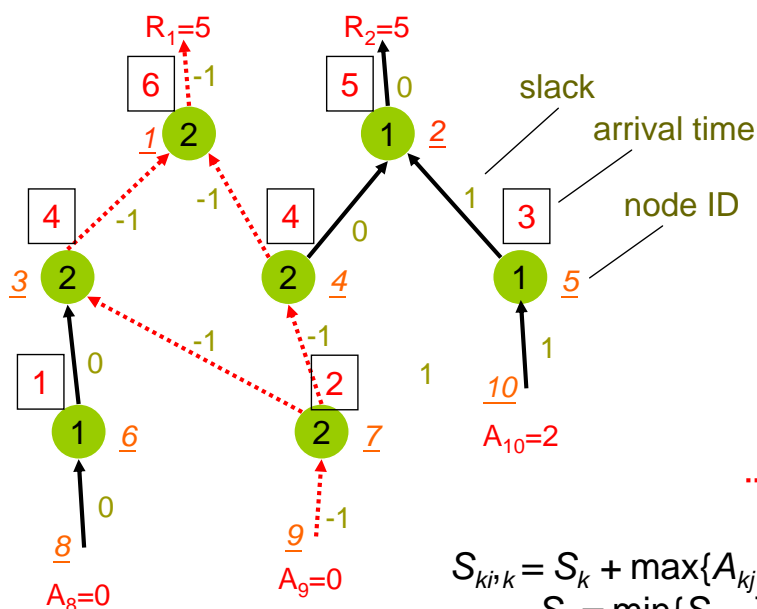

$A_1 = 6$	$R_1 = 5$
$A_2 = 5$	$R_2 = 5$
$S_1 = -1$	$R_3 = 3$
$S_2 = 0$	$R_7 = 1$
$S_{3,1} = -1$	$R_9 = -1$
$S_{4,1} = -1$	
$S_{4,2} = 0$	
$S_{5,2} = 1$	
$S_{6,3} = 0$	
$S_{7,3} = -1$	
$S_{7,4} = -1$	
$S_{7,5} = 1$	
$S_{8,6} = 0$	
$S_{9,7} = -1$	

..... critical path edges

$$S_{k_i, k} = S_k + \max\{A_{k_j}\} - A_{k_i}, k_j, k_i \in \text{fanin}(k)$$

$$S_k = \min\{S_{k, k_j}\}, k_j \in \text{fanout}(k)$$

12

Static Timing Analysis


□ Problems

- We want to determine the **true** critical paths of a circuit in order to:
 - determine the minimum cycle time that a circuit will function correctly
 - identify critical paths for performance optimization - don't want to try to optimize **wrong** (non-critical) paths
- Implications:
 - Don't want **false paths** (produced by static delay analysis)
 - Delay model is a **worst** case model
 - Need to ensure correctness for case where i^{th} gate delay $\leq D_i^{\text{Max}}$

13

Functional Timing Analysis

 - Functional timing analysis estimates when the output of a given circuit gets stable



14

Functional Timing Analysis

□ Motivation

- Timing verification
 - Verifies whether a design **meets** a given timing constraint
 - E.g., cycle-time constraint
- Timing optimization
 - Needs to identify **critical** portion of a design for further optimization
 - Critical path identification
- In both applications, **accurate** analysis is desirable

15


Gate-Level Timing Analysis

- **Naïve approach** - Simulate all input vectors with SPICE
 - Accurate, but too expensive
- **Gate-level timing analysis (our focus)**
 - Less accurate than SPICE due to the level of abstraction, but much more **efficient**
 - Scenario:
 - Gate/wire delays are **pre-characterized** (accuracy loss)
 - Perform timing analysis of a gate-level circuit assuming the **gate/wire delays**

16

Gate-Level Timing Analysis

 
- A naive approach is topological analysis
 - Easy longest-path problem
 - Linear in the size of a network
- Not all paths can propagate signal events
 - **False paths**
 - If all longest paths are false, topological analysis gives delay **over-estimation**
- **Functional timing analysis** = **false-path-aware** timing analysis
 - Compute false-path-aware arrival time



17

Gate-Level Timing Analysis

- Example
 - 2-bit carry-skip adder

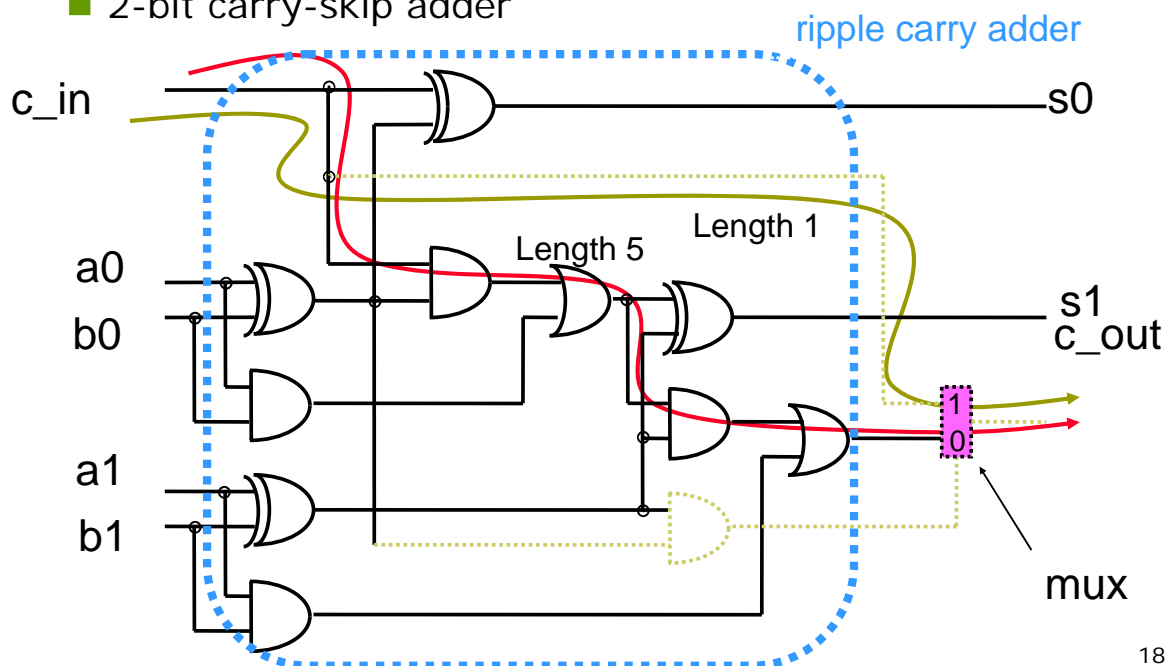

18



False Path Analysis

- Is a path **responsible** for circuit delay?
 - If the answer is no, can **ignore** the path for delay computation
- Check the falsity of long paths until we find the longest true path
 - How can we determine whether a path is a false path?
- Delay under-estimation is **unacceptable**
 - Can lead to overlooking timing **violation**
- Delay over-estimation is **acceptable**, but not desirable
 - **Topological** analysis may yield over-estimation, but never under-estimation

19

False Path Analysis

- Controlling and non-controlling values

  


20

False Path Analysis

Static Sensitization

Static sensitization

 - A path is *statically-sensitizable* if there exists an input vector such that all the side-inputs to the path are of non-controlling values
 - This is *independent* of gate delays



The longest *true* path is of length 2?


21

False Path Analysis

Static Sensitization

 Example

- The (*dashed*) path is responsible for delay!
- Delay *under-estimation* by static sensitization (*delay = 2* when *true delay = 3*)
 - incorrect* condition




22

False Path Analysis Static Sensitization

- ❑ Problem: The idea of forcing non-controlling values to side inputs is okay, **but** timing was ignored
 - The same signal can have a **controlling** value at one time and a **non-controlling** value at another time
- ❑ How about **timing simulation** as a correct method?

23


False Path Analysis Timing Simulation

 

Implies delay = 0 under input vector (0,1)
BUT!

24

False Path Analysis Timing Simulation

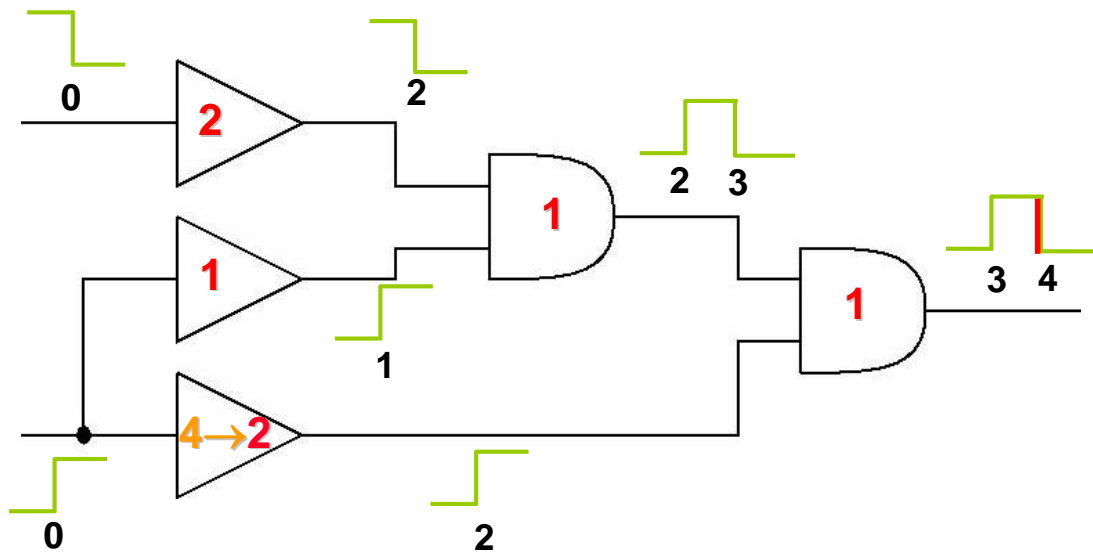

Implies delay = 4 under the same input (0,1) as before

25

False Path Analysis Timing Simulation

- ❑ Problem: If gate delays are **reduced**, delay estimates can **increase**
- ❑ **Not** acceptable since
 - Gate delays are just **upper-bounds**, actual delay is in $[0,d]$
 - ❑ Delay **uncertainty** due to manufacturing
 - We are implicitly analyzing a **family** of circuits where gate delays are **within** the upper-bounds


26


False Path Analysis Timing Simulation

- Definition: Given a circuit C and a delay estimation method `delay_estimate`, if
 - C* is obtained from C by reducing some gate delays, and
 - $\text{delay_estimate}(C^*) \leq \text{delay_estimate}(C)$,then `delay_estimate` has *monotone speedup*
- Timing simulation does **not** have such a property

27

False Path Analysis Timing Simulation

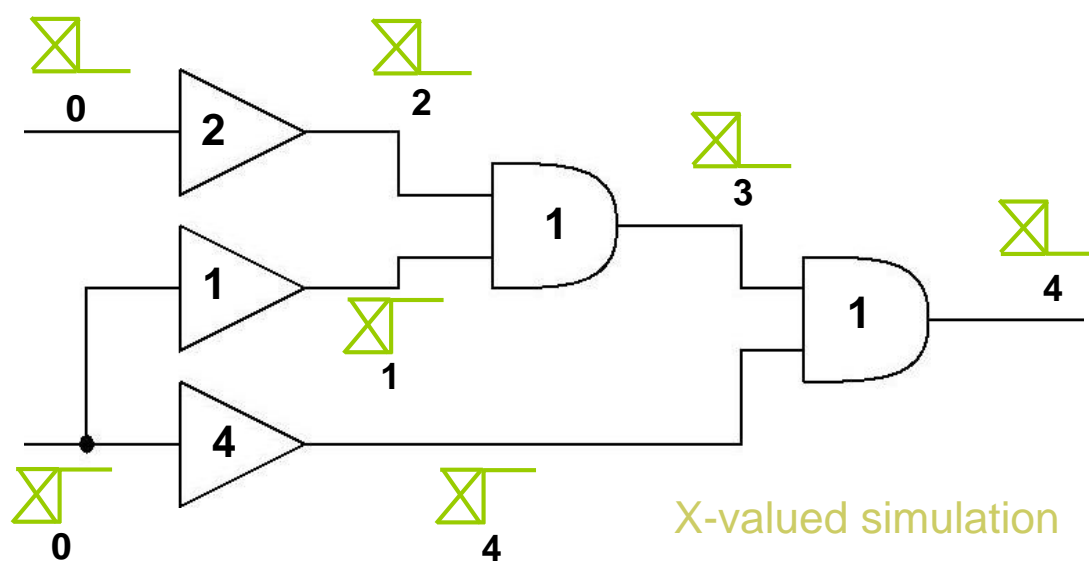

 means that the rising signal occurs anywhere between $t = -\infty$ and $t = 4$.

28

False Path Analysis Timing Simulation

- Timed 3-valued (0,1,X) simulation
 - called X-valued simulation
 - monotone speedup property is satisfied

- Underlying model of
 - floating mode condition
 - Applies to “simple gate” networks only
 - viability
 - Applies to general Boolean networks

29

False Path Analysis Timing Simulation

- Checking the falsity of every path explicitly is too expensive due to the exponential number of paths
 - Modern approach:
 1. Start:
 $L = L_{top}$ = topological longest path delay
 $L_{old} = 0$
 2. Binary search:
if (Delay(L)) (*) $L_d = |L - L_{old}|/2, L_{old} = L, L = L + L_d$
else $L_d = |L - L_{old}|/2, L_{old} = L, L = L - L_d$
if ($L > L_{top}$ or $L_d < \text{threshold}$) $L = L_{old}$, **done**
- (*) Delay(L) = 1 if there is an input vector under which an output gets stable only at time t where $L \leq t$?
Can be reduced to
- a SAT or timed-ATPG problem

30

SAT-Based False Path Analysis

Decision problem:

Is there an input vector under which the output gets stable only after $t = T$?

Idea:

1. Characterize the set of all input vectors $S(T)$ that make the output stable no later than $t = T$
2. Check if $S(T)$ contains S (all possible input vectors)

Can be solved as a SAT problem:


Is $S \setminus S(T)$ empty? - set difference + emptiness checking

- Let F and $F(T)$ be the characteristic functions of S and $S(T)$
- Is $F \wedge \neg F(T)$ satisfiable?

31

SAT-Based False Path Analysis

Example

 


Assume all the PIs arrive at $t = 0$, all gate delays = 1
Is the output stable time $t > 2$?

32

SAT-Based False Path Analysis

Example

 


- $g(1, t=2)$: the set of input vectors under which g gets **stable to value = 1** no later than t = 2
- $g(1, t=2) = d(1, t=1) \cap f(1, t=1) = (a(0, t=0) \cap b(0, t=0)) \cap (c(1, t=0) \cup e(1, t=0)) = \neg a \neg b (c \cup \emptyset) = \neg a \neg b c = S1(t=2)$
- $g(1, t=\infty) = \text{onset} = \neg a \neg b c = g(1, t=2) = S1$

33

SAT-Based False Path Analysis

Example

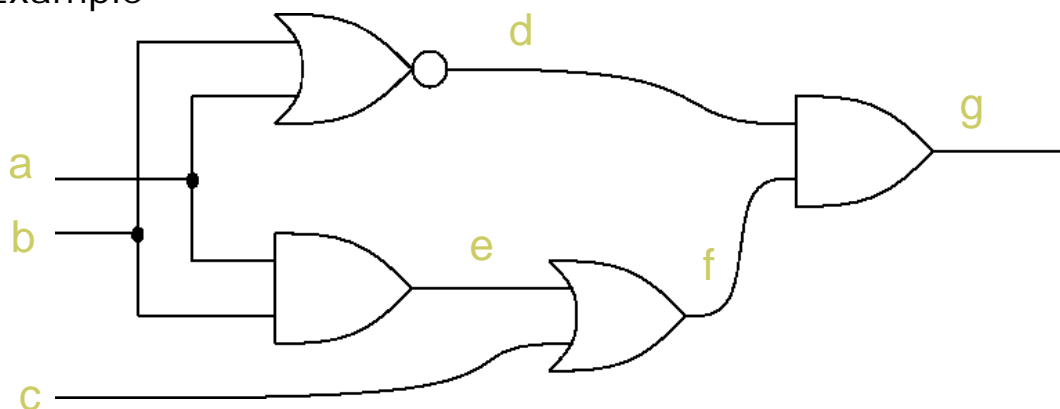


- $g(0, t=2)$: the set of input vectors under which g gets stable to value = **0** no later than t = 2
- $g(0, t=2) = d(0, t=1) \cup f(0, t=1) = (a(1, t=0) \cup b(1, t=0)) \cup (c(0, t=0) \cap e(0, t=0)) = (a+b) + (\neg c \cap \emptyset) = a+b = S0(t=2)$
- $g(0, t=\infty) = \text{offset} = a+b+\neg c = S0$

34

SAT-Based False Path Analysis

Example

 

- $g(0, t=2)$: the set of input vectors under which g gets stable to 0 no later than $t=2$
- $g(0, t=2) = a+b$
- $g(0, t=\infty) = \text{offset} = a+b+\neg c$
- $g(0, t=\infty) \setminus g(0, t=2) = (a+b+\neg c) \neg(a+b) = \neg a \neg b \neg c$ **satisfiable**

35

Timing Analysis

Summary

- False-path-aware arrival time analysis is **well-understood**
 - **Practical** algorithms exist
- Remaining problems
 - **Incremental** analysis (make it so that a small change in the circuit does not make the analysis start all over)
 - Integration with logic **optimization**
 - DSM issues such as **cross-talk-aware** false path analysis

36

Timing Optimization

Several factors affecting circuit delay:

- Technology
 - Design type (e.g. domino, static CMOS, etc.)
 - Gate type
 - Gate size
- Circuit structure
 - Length of computation paths
 - False paths
 - Buffering
- Electrical parasitics
 - Wire loads
 - Layout

37

Timing Optimization

□ Problem statement

Given:

- Initial circuit function description
- Library of primitive functions
- Performance constraints (arrival/required times)

Generate:

- An implementation of the circuit using the primitive functions, such that:
 - performance constraints are met
 - circuit area is minimized

38

Timing Optimization

□ Design flow

Behavioral description

Logic and latches

Logic equations

Gate netlist

Layout

Behavior optimization
(scheduling)

RTL synthesis

Logic synthesis
•Technology independent
•Technology mapping


•Gate library
•Timing constraints
•Delay models

Timing-driven place and route

39

Timing Optimization

□ Buffered circuit structure

 

40

Timing Optimization

- Circuit restructuring
 - Reschedule operations to reduce computation time
- Timing-driven technology mapping
 - Selection of gates from library
 - Minimum delay
 - Similar to area minimization under the **load independent model**
 - Minimize delay and area
- Implementation of **buffer trees**
- Gate/wire sizing
- Constant delay synthesis

41

Timing Optimization

- Circuit restructuring
 - **Global**: Reduce depth of entire circuit
 - Partial collapsing
 - Boolean simplification
 - **Local**: Mimic optimization techniques in **adders**
 - Carry lookahead (**THR** tree-height reduction)
 - Conditional sum (**GST** transformation)
 - Carry bypass (**GBX** transformation)

42

Timing Optimization


□ Circuit restructuring

- Performance measured by logic levels, sensitisable paths, technology-dependent delays
- Level-based optimization
 - Tree height reduction
 - Partial collapsing and simplification
 - Generalized select transform
- Sensitisable path based optimization
 - Generalized bypass transform

43

Timing Optimization


□ Tree height reduction

 

44

Timing Optimization


Tree height reduction

 

45

Timing Optimization

Generalized bypass transform

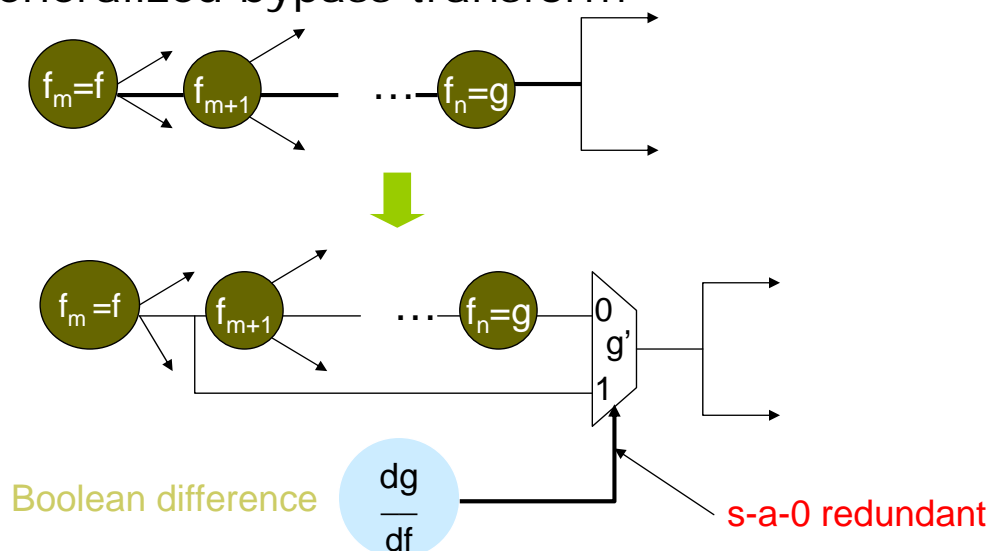


- Make critical path false to bypass critical logic and speed up circuit

46

Timing Optimization


False path removal by logic duplication

 

47

Timing Optimization

Generalized select transform

 

48

Timing Optimization

□ Summary

- There are various methods for delay optimization at different synthesis stages
 - No single technique dominates
 - Most techniques (except false path removal by logic duplication) ignore **false paths** when assessing the delay and critical regions