 


# Introduction to FPGA

---

Guan-Lin Wu






# Outline

- Introduction to PLD
- Introduction to FPGA
- FPGA Example – Altera Cyclone II
- Altera Quartus II
- Lab


# World of Integrated Circuits

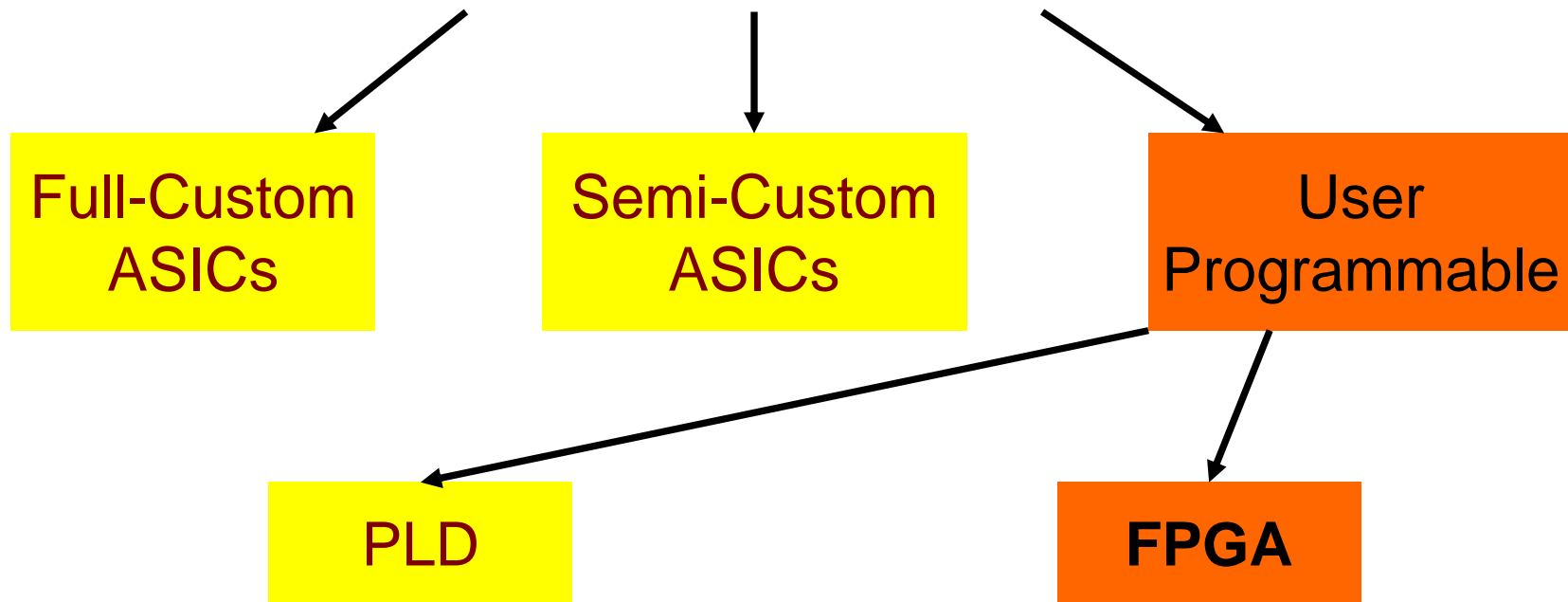

# Digital Logic



## Digital Logic Function


 


**Product AND (&)  
Sum OR (∨)**


## Boolean Logic Minimisation

**Connect Standard Logic Chips  
Very Simple Glue Logic**

**FIXED Logic**

 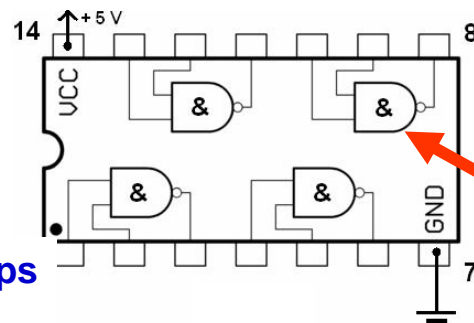

## CMOS NAND gate

 


X1	X2	T1	T2	T3	T4	f
0	0	On	On	Off	Off	1
0	1	On	Off	Off	On	1
1	0	Off	On	On	Off	1
1	1	Off	Off	On	On	0

**Transistor Switches**
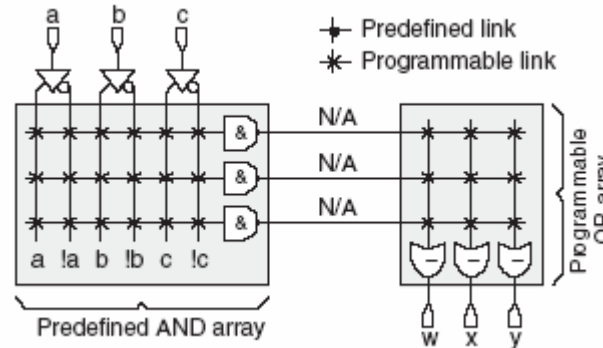
# Programmable Logic Devices PLDs



- Different Types
- SUM of PRODUCTS
- Prefabricated
- Programmable Links
- Reconfigurable




Un-programmed State


Planes of ANDs, ORs

$$\begin{aligned}
 y &= (a \& b \& c) \\
 x &= (a \& b \& c) \mid (\bar{b} \& \bar{c}) \\
 w &= (a \& c) \mid (\bar{b} \& \bar{c})
 \end{aligned}$$


Logic Function

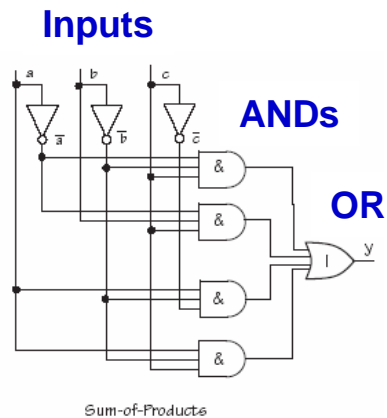

Sum of Products

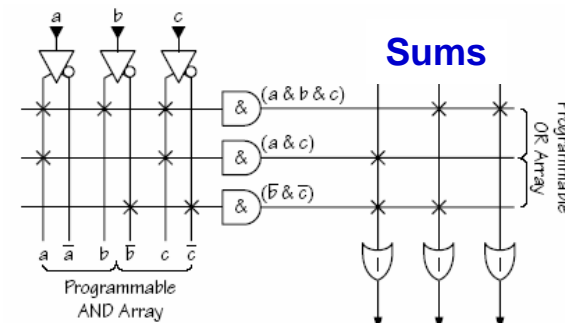

Product Terms

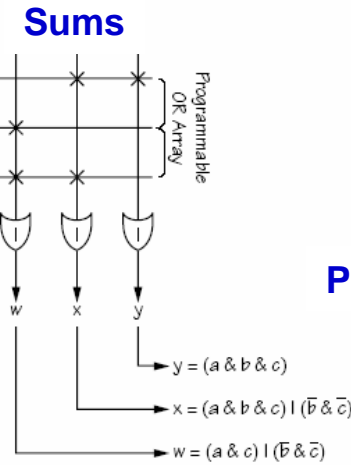


Programmed PLD



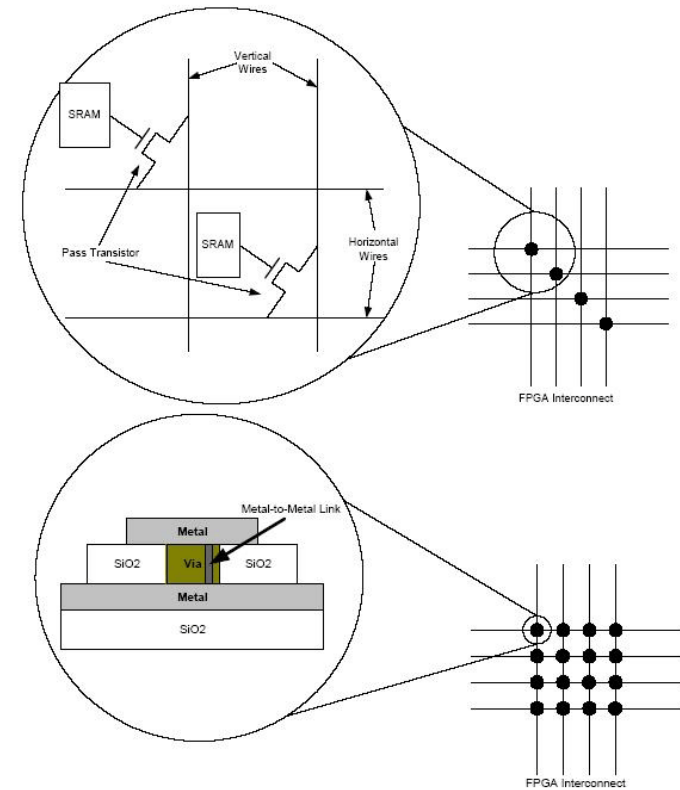
# How can we make a “programmable logic”?




- SRAM-based
  - Reconfigurable
  - Track latest SRAM technology
  - Volatile
  - Generally high power
- Anti-fuse technique
  - One-time programmable
  - Non-volatile – security app.





# Complex PLDs

 

 - CPLDs
- Programmable PLD Blocks
- Programmable Interconnects
- Electrically Erasable links



**CPLD Architecture**

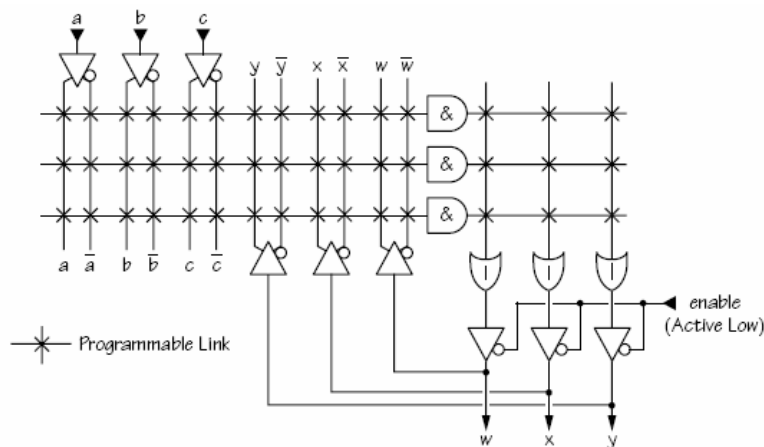 


**Feedback Outputs**
 
# Field Programmable Gate Arrays FPGA




- Field Programmable Gate Array
  - New Architecture
  - 'Simple' Programmable Logic Blocks
  - Massive Fabric of Programmable Interconnects



Large Number of Logic Block 'Islands'  
1,000 ... 100,000+  
in a 'Sea' of Interconnects

**FPGA Architecture**

 



 
# Logic Blocks



- Logic Functions implemented in Lookup Table LUTs
- Multiplexers (select 1 of N inputs)
- Flip-Flops. Registers. Clocked Storage elements.






# Lookup Tables LUTs



- LUT contains Memory Cells to implement small logic functions
- Each cell holds '0' or '1' .
- Programmed with outputs of Truth Table
- Inputs select content of one of the cells as output


3 – 6 Inputs

  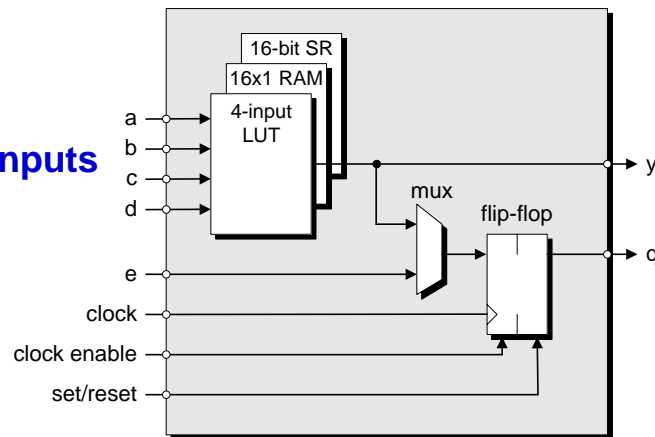




Multiplexer MUX

3 Inputs LUT -> 8 Memory Cells

Required function

 

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

  
 


Static Random Access Memory  
SRAM cells


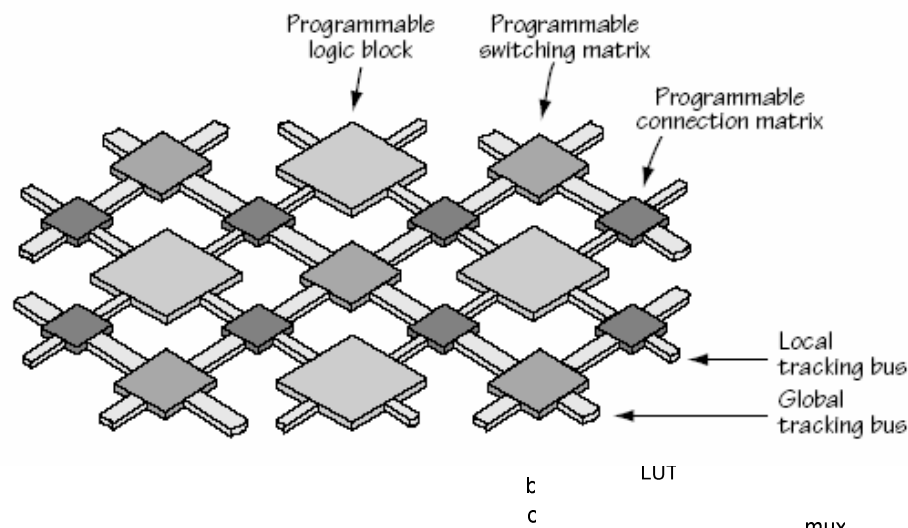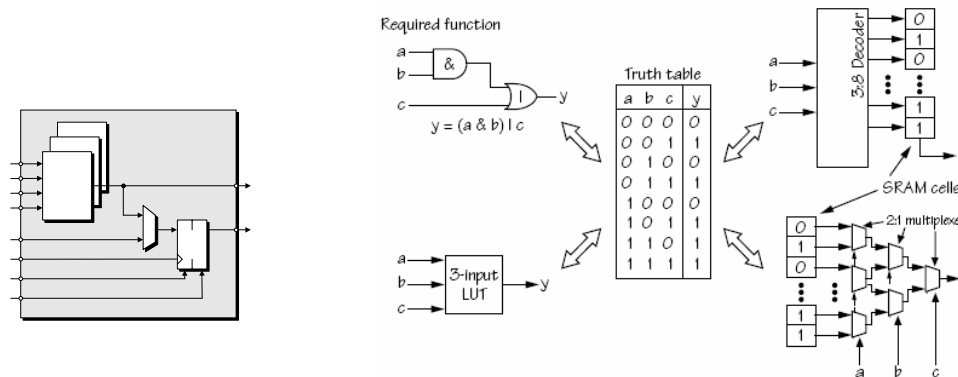
# Logic Blocks


- Larger Logic Functions built up by connecting many Logic Blocks together





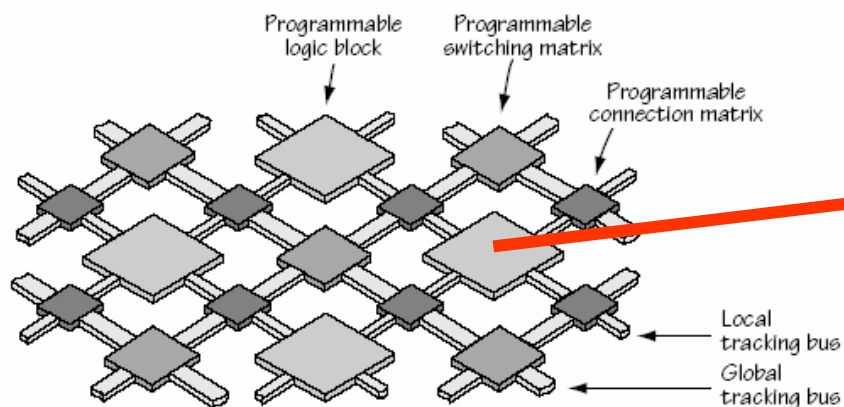
# Clocked Logic



- Flip Flops on outputs. CLOCKED storage elements.
- Sequential Logic Functions (cf Combinational Logic LUTs)
- Pipelines. Synchronous Logic Design
- FPGA Fabric driven by Global Clock (e.g. BX frequency)




FPGA Fabric

   


# Circuit Compilation



## 1. Technology Mapping

 


## 2. Placement

 

## 3. Routing



# Routing Example



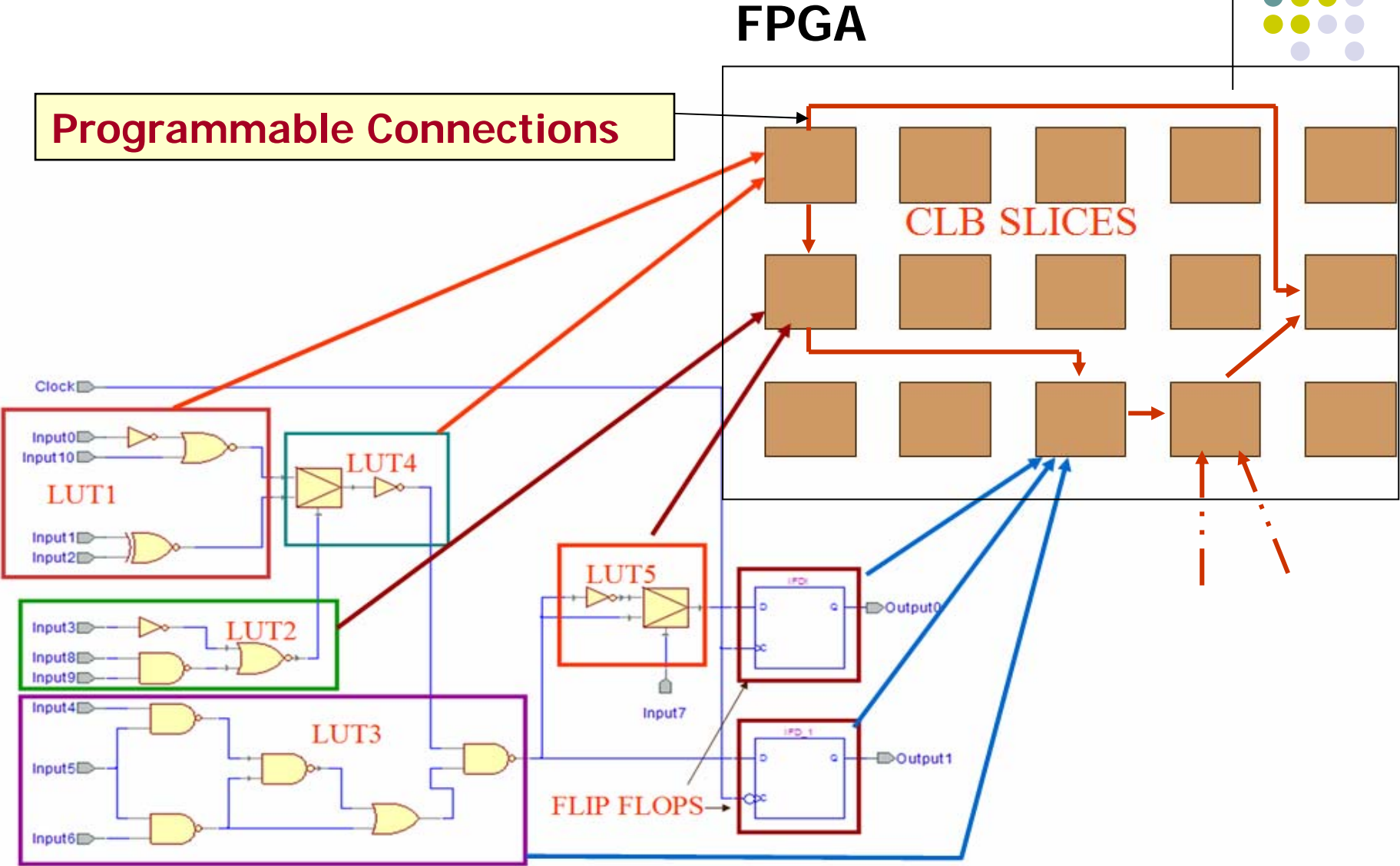


# Which Way to Go?



**ASICs**

**FPGAs**

 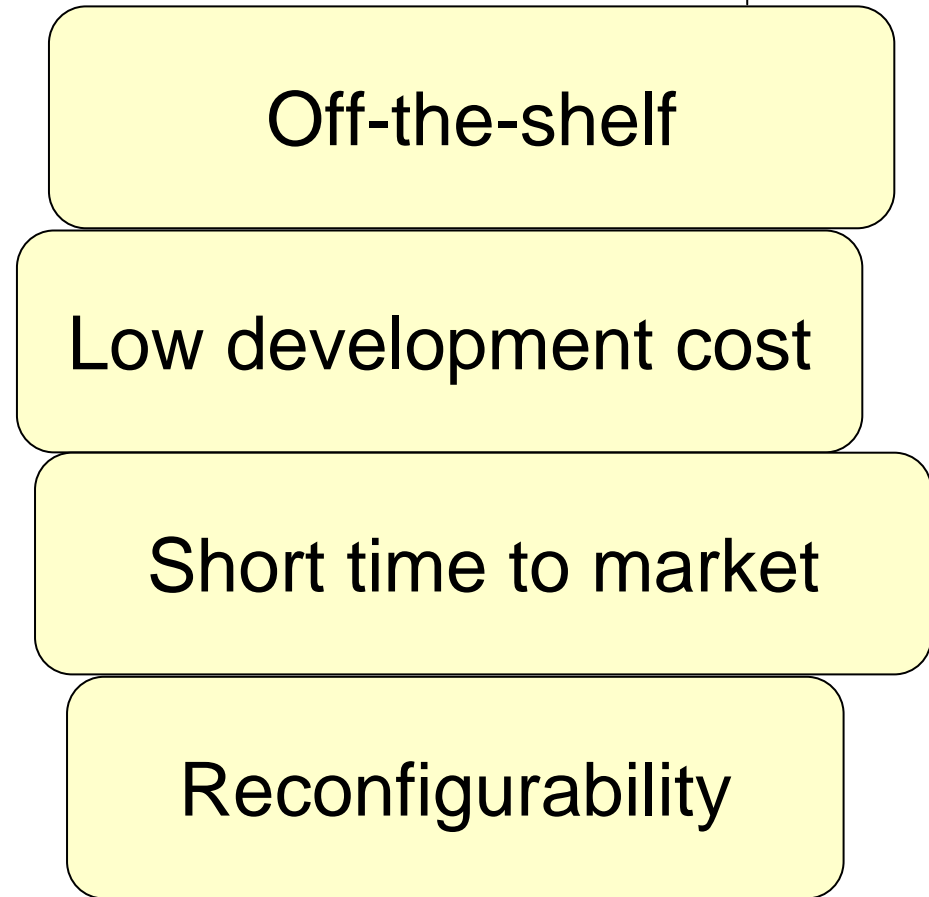 

# Other FPGA Advantages



- Manufacturing cycle for ASIC is very costly, lengthy and engages lots of manpower
  - Mistakes not detected at design time have large impact on development time and cost
  - FPGAs are perfect for rapid prototyping of digital circuits
- Easy upgrades like in case of software
- Unique applications
  - reconfigurable computing



# Major FPGA Vendors



## SRAM-based FPGAs


- Xilinx, Inc.
- Altera Corp. } Share over 60% of the market
- Atmel
- Lattice Semiconductor

## Flash & antifuse FPGAs

- Actel Corp.
- Quick Logic Corp.

---


# FPGA Example – Altera Cyclone II

 



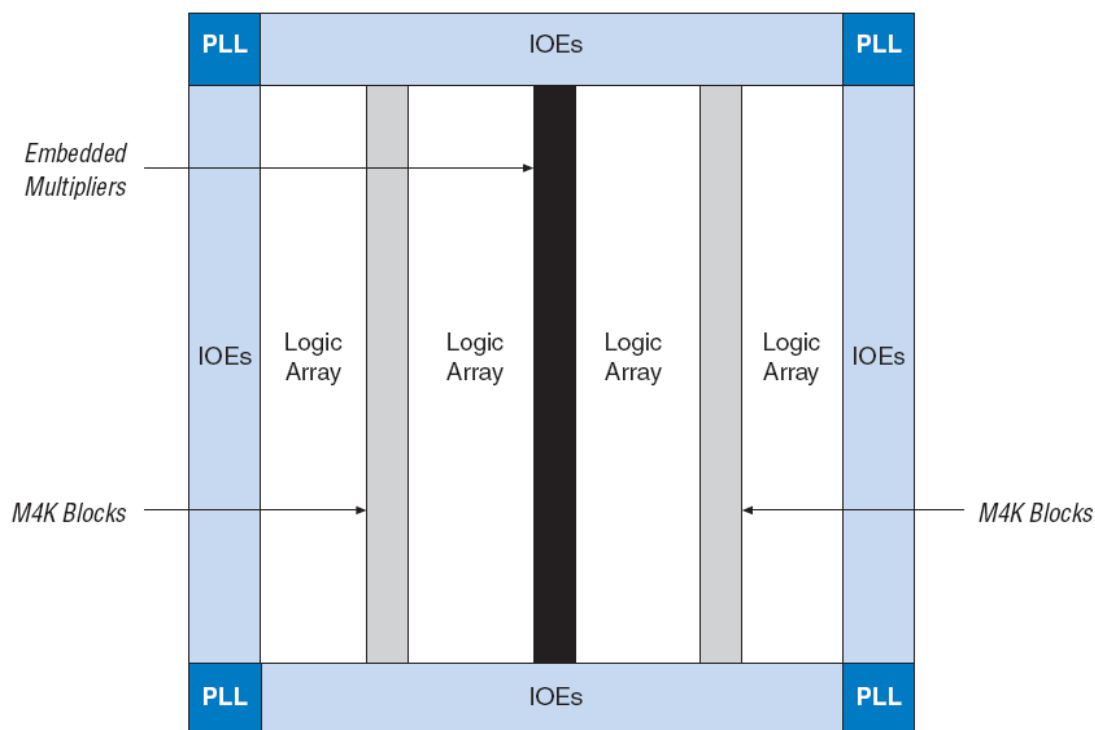
# Cyclone II EP2C20 Block

- Logic array – LUTs
- Block memory – M4K blocks
- Embedded Multipliers
- Input/output Modules (IOEs)
- PLLs



# Cyclone II EP2C20 Block

 

# Cyclone II EP2C20




- 18,752 LEs
- 52 M4K RAM blocks
- 240K total RAM bits
- 52 9x9 embedded multipliers
- 4 PLLs
- 16 Clock networks
- 315 user I/O pins
- SRAM Based volatile configuration



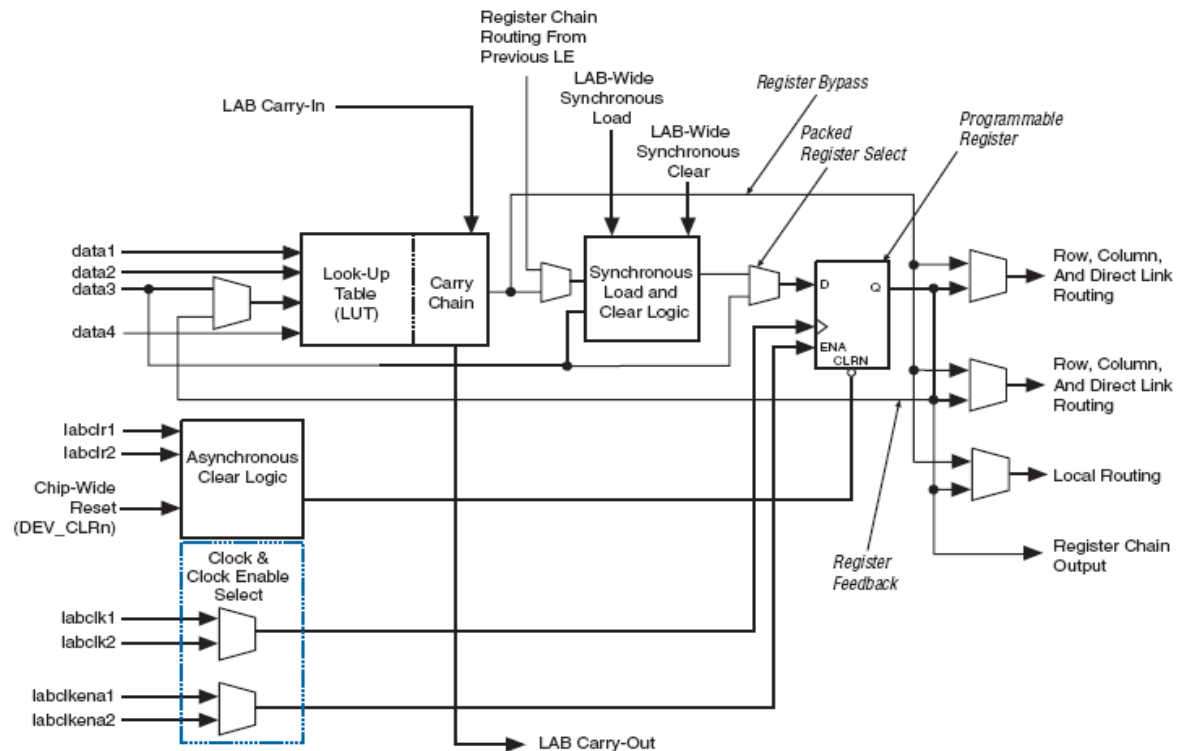
# Logic Element

- 16 LEs forms a Logic Array Block (LAB)
  - Normal mode
  - Arithmetic mode






# Logic Element

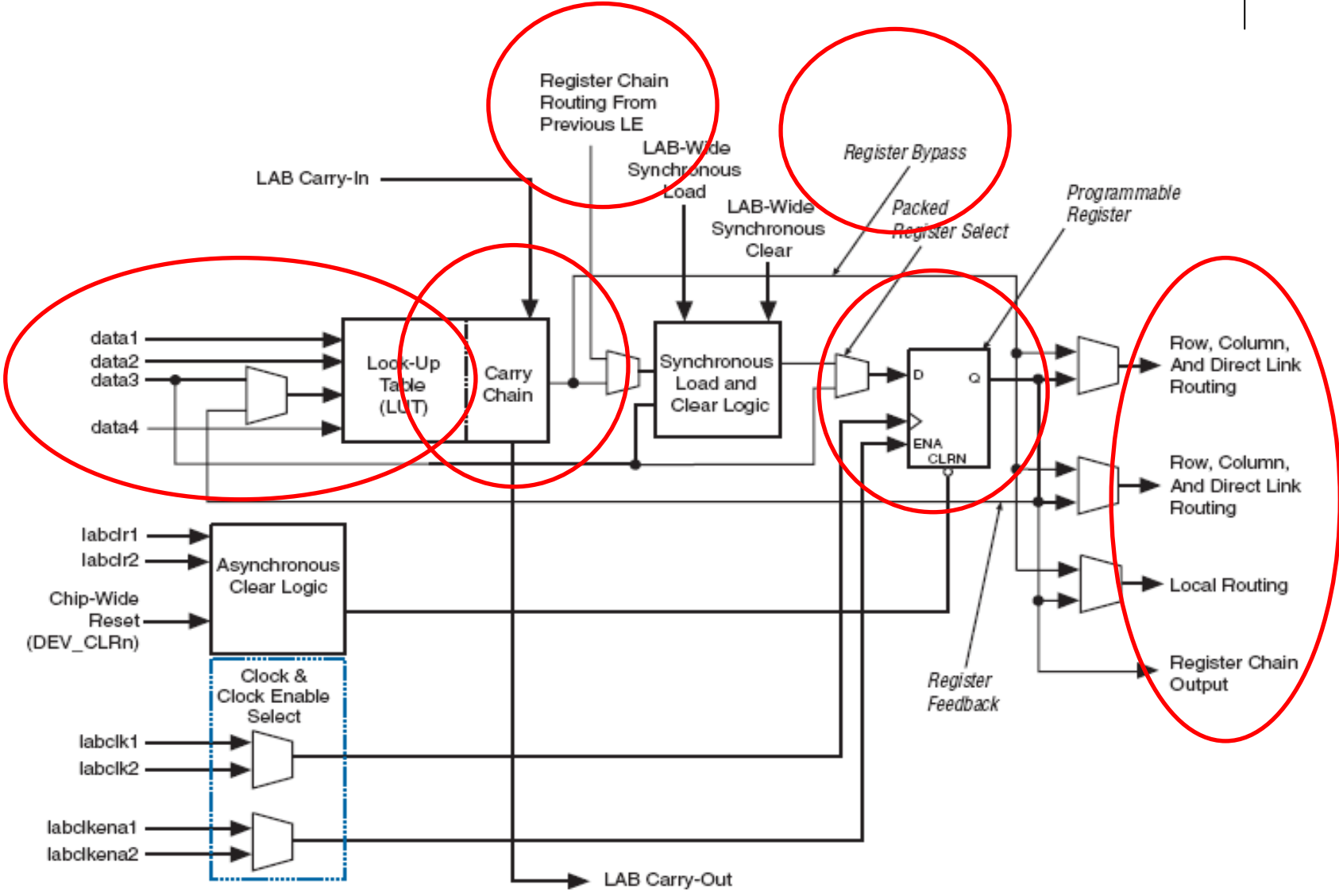



# Logic Element

- Normal Mode – general logic operations

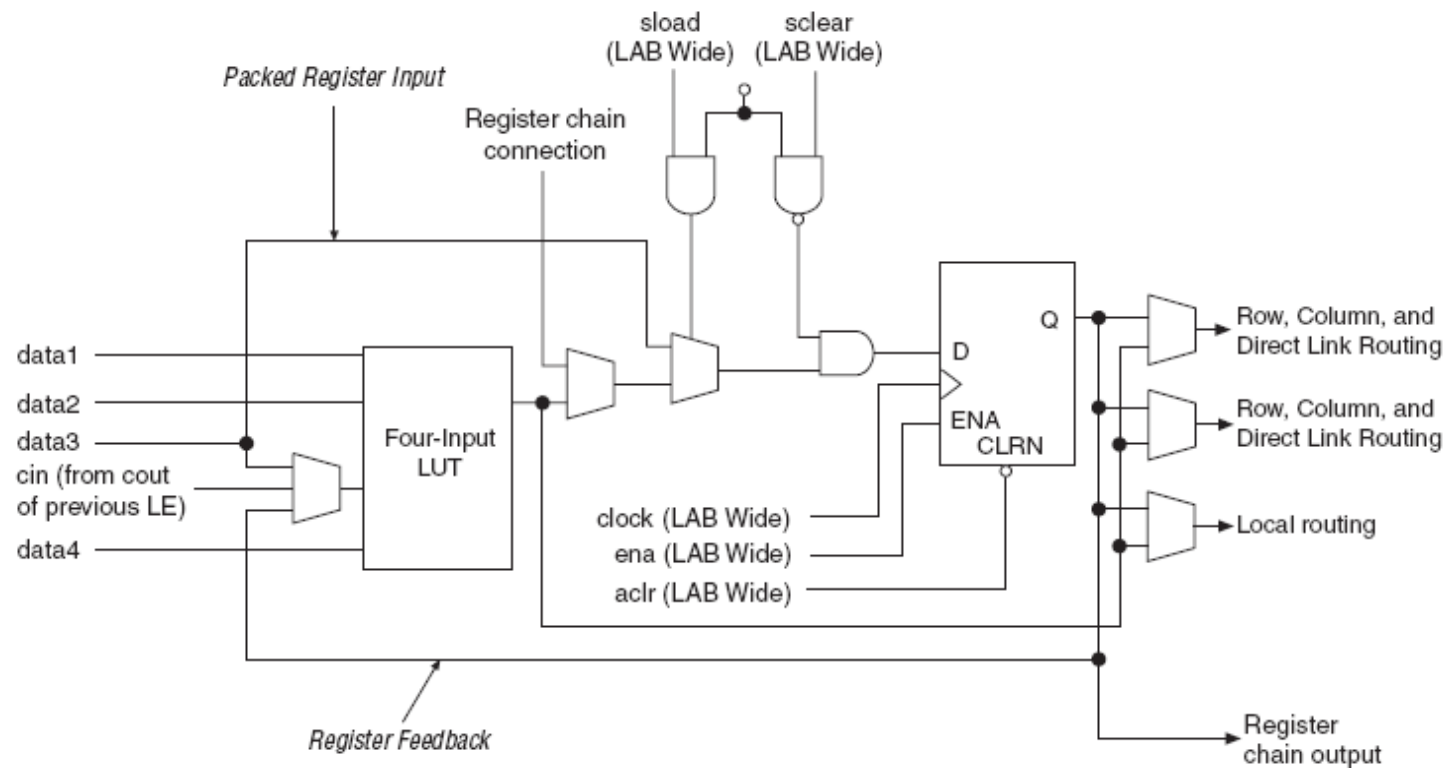






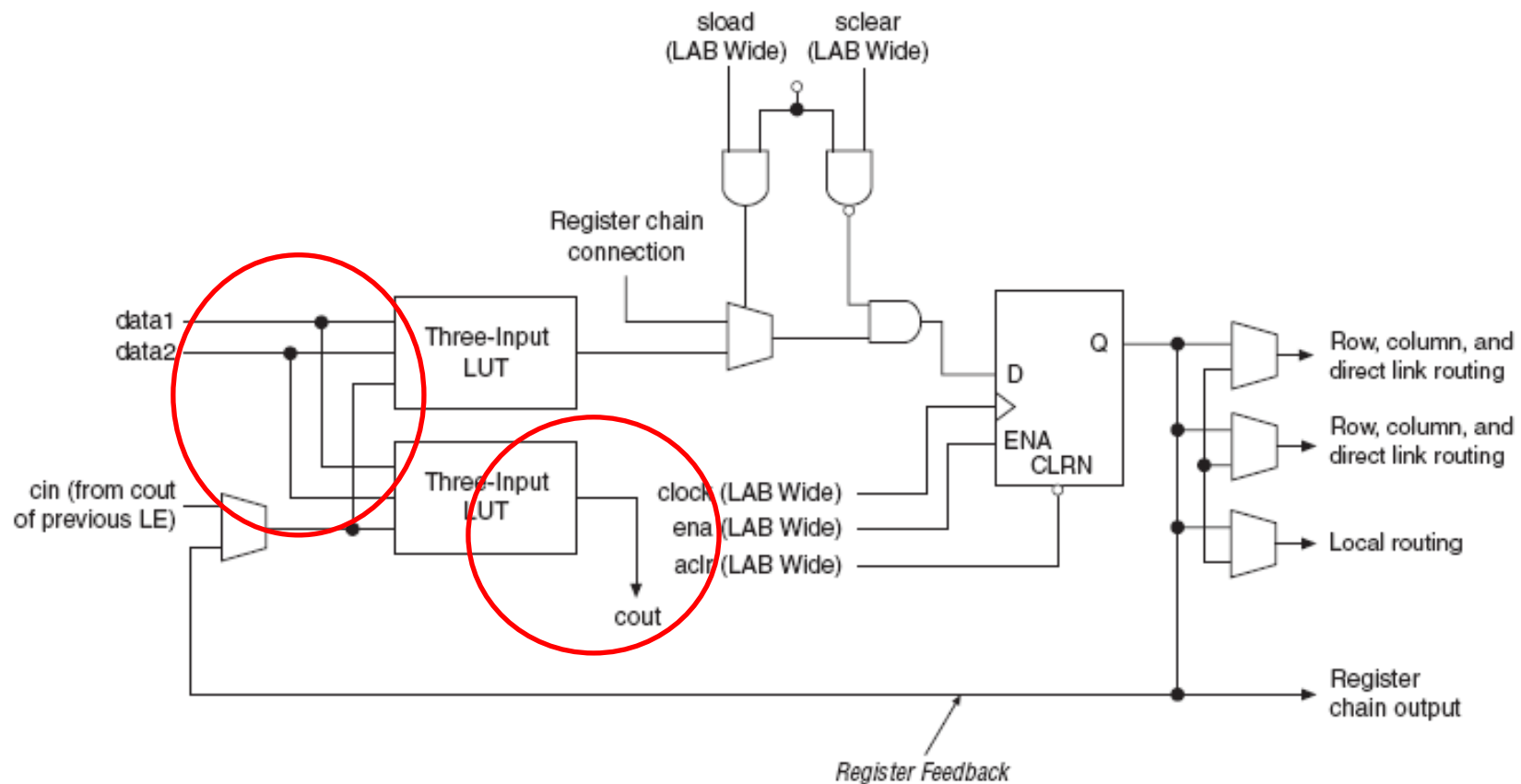
# Logic Element

- Arithmetic Mode – adder, counter, accumulators, comparator




# Logic Array Blocks Structure

 
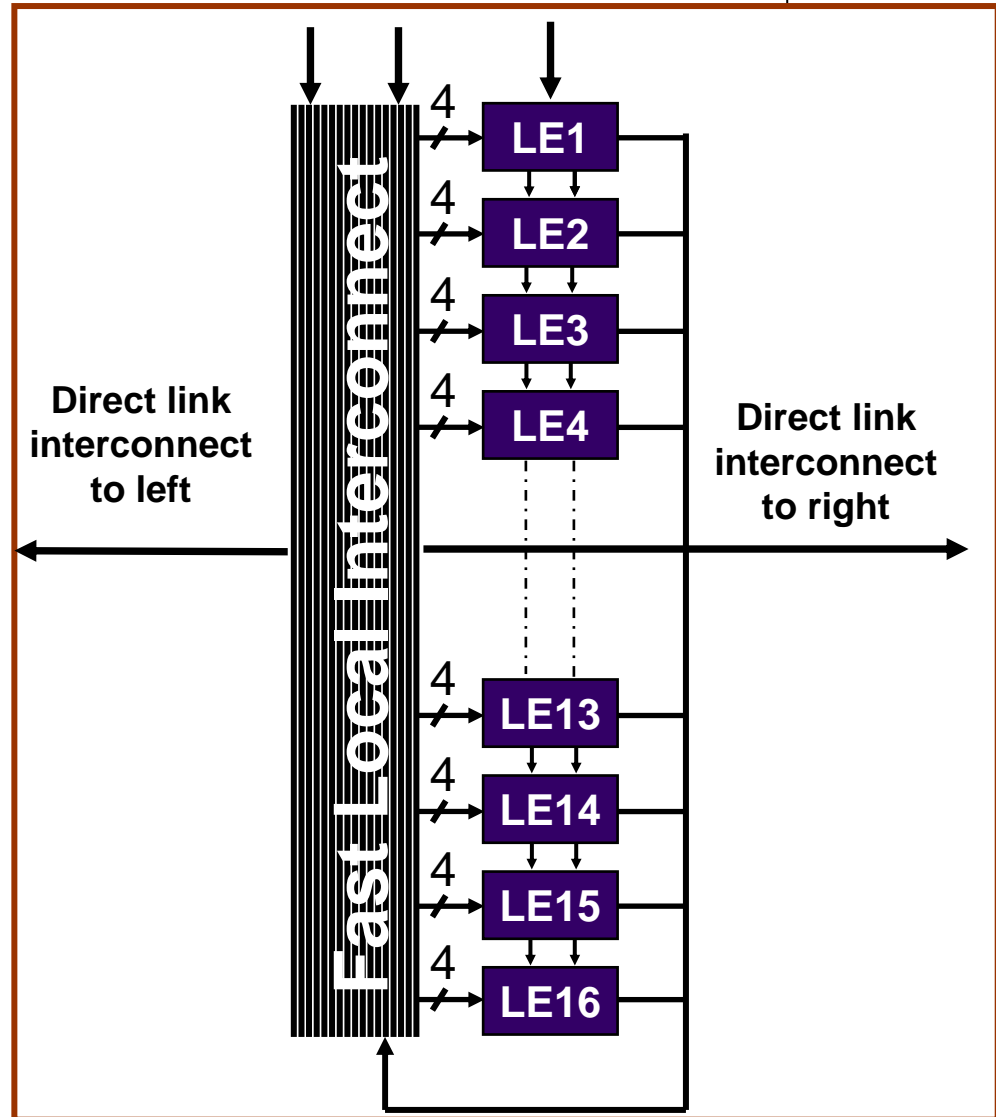
# Cyclone II Logic Array Block (LAB)




- 16 LEs
- Local Interconnect
- LE carry chains
- Register chains





# Row Interconnect Connections


- Direct link, R4, R24 interconnects

 

# Column Interconnect Connections




- Register chain, C4, C16

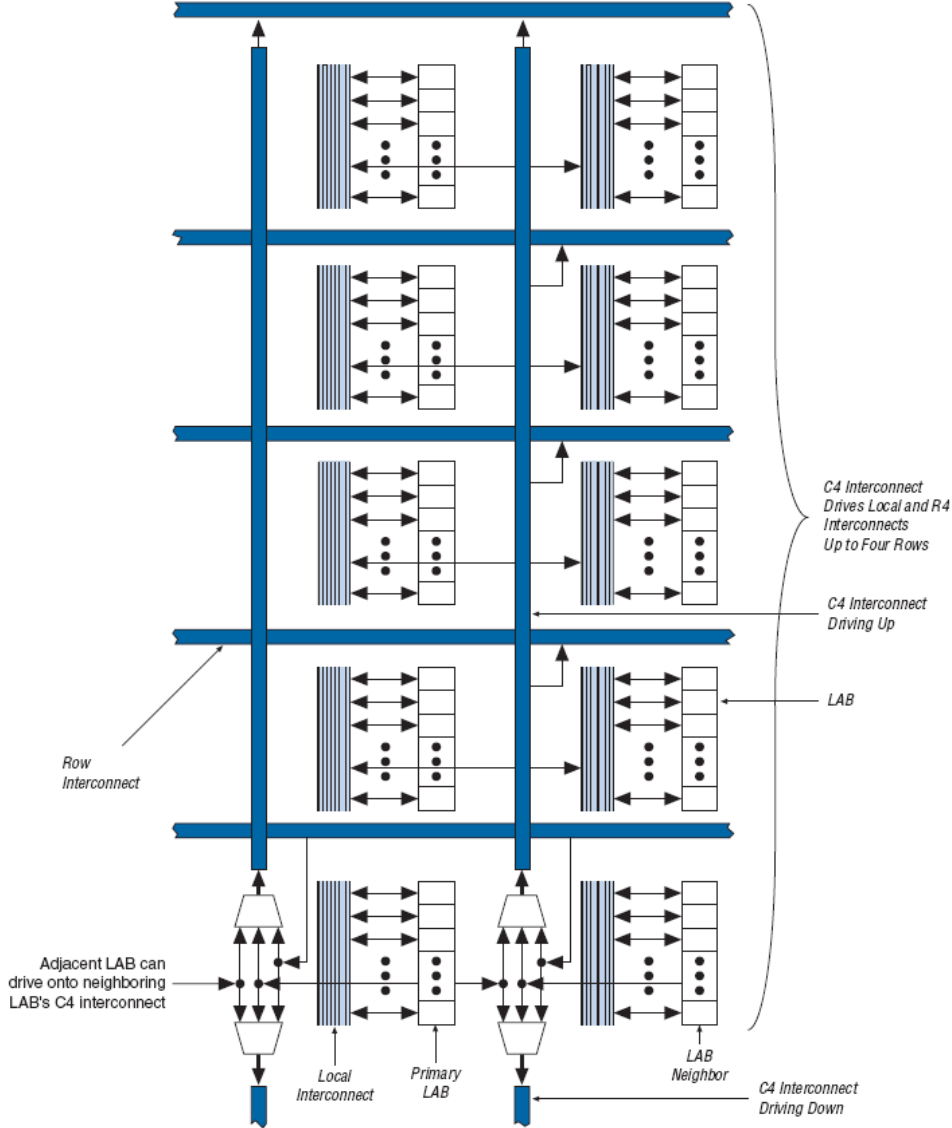


 
# Register Chain Interconnects


- LEs can be connected for implementing fast adder, counters, shift register



# M4K RAM



Memory Mode	Description
Single-port memory	M4K blocks support single-port mode, used when simultaneous reads and writes are not required. Single-port memory supports non-simultaneous reads and writes.
Simple dual-port memory	Simple dual-port memory supports a simultaneous read and write.
Simple dual-port with mixed width	Simple dual-port memory mode with different read and write port widths.
True dual-port memory	True dual-port mode supports any combination of two-port operations: two reads, two writes, or one read and one write at two different clock frequencies.
True dual-port with mixed width	True dual-port mode with different read and write port widths.
Embedded shift register	M4K memory blocks are used to implement shift registers. Data is written into each address location at the falling edge of the clock and read from the address at the rising edge of the clock.
ROM	The M4K memory blocks support ROM mode. A MIF initializes the ROM contents of these blocks.
FIFO buffers	A single clock or dual clock FIFO may be implemented in the M4K blocks. Simultaneous read and write from an empty FIFO buffer is not supported.

 




# Cyclone II I/O Features

- In/Out/Tri-state
- Different Voltages and I/O Standards
  - PCI, PCI-X, LVDS I/O standard
- Flip-flop option
- Pull-up resistors
- DDR interface
- Series resistors
- Bus keeper
- Drive strength control
- Slew rate control
- Single ended/differential



---

# Advance Architecture on Modern FPGAs

 


# More Guts


- Additional components
  - Dedicated computation units
  - Processor cores
  - DSP blocks



# Dedicate Arithmetic Blocks

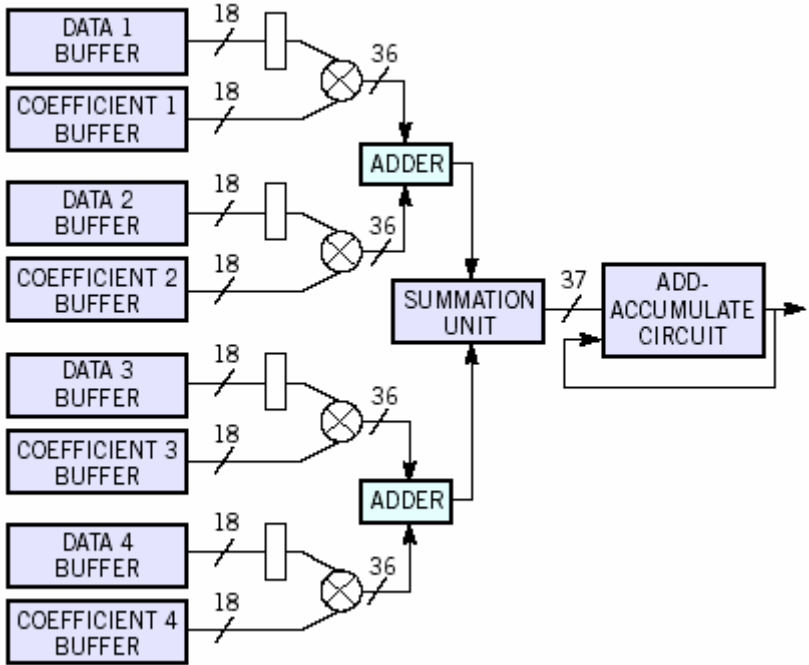

Altera

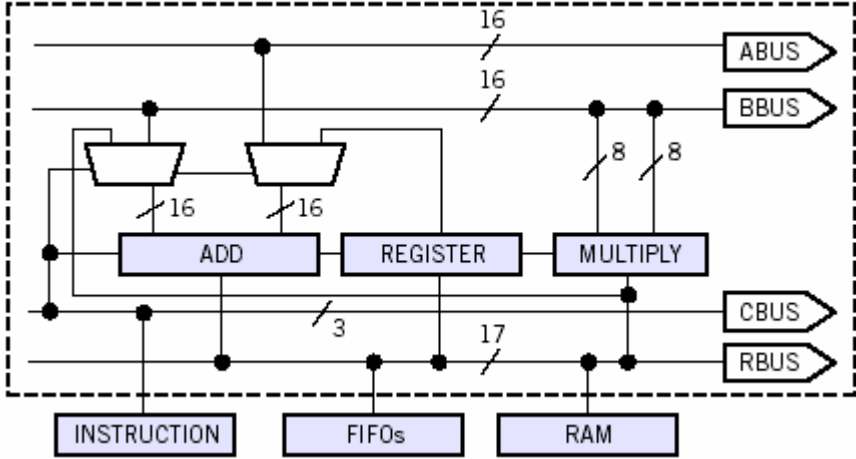

QuickLogic




Xilinx

# Processor Cores



Features	Altera	Xilinx
Hard Processor	ARM9227 RISC (200MHz) Host Device: Excalibur	IBM PowerPC405 (300MHz) Host Device: Vertex II Pro
Soft Processor	Nios (32bits, 50MHz) Host Devices: Flex, APEX, ACEX, Mercury, Stratix	MicroBlaze (32bits, 150MHz) Host Devices: Spartan II, III, all Vertex families
Tools	Excalibur Solution Pack which includes GNUPro for SW design and Quartus II for HW design	Embedded Development Kit (EDK) which include WindRiver GNU compiler for SW design and ISE5.2i for HW design
Debuggers	SW debugger only	SW and HW (Chipscope Pro) debugger

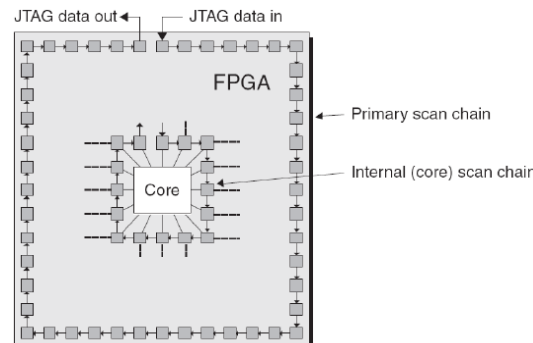

# Altera DE2-70

