

# Switching Circuits & Logic Design

Jie-Hong Roland Jiang  
江介宏

Department of Electrical Engineering  
National Taiwan University




Fall 2012

1

## §5 Karnaugh Maps

K-map Walks and Gray Codes

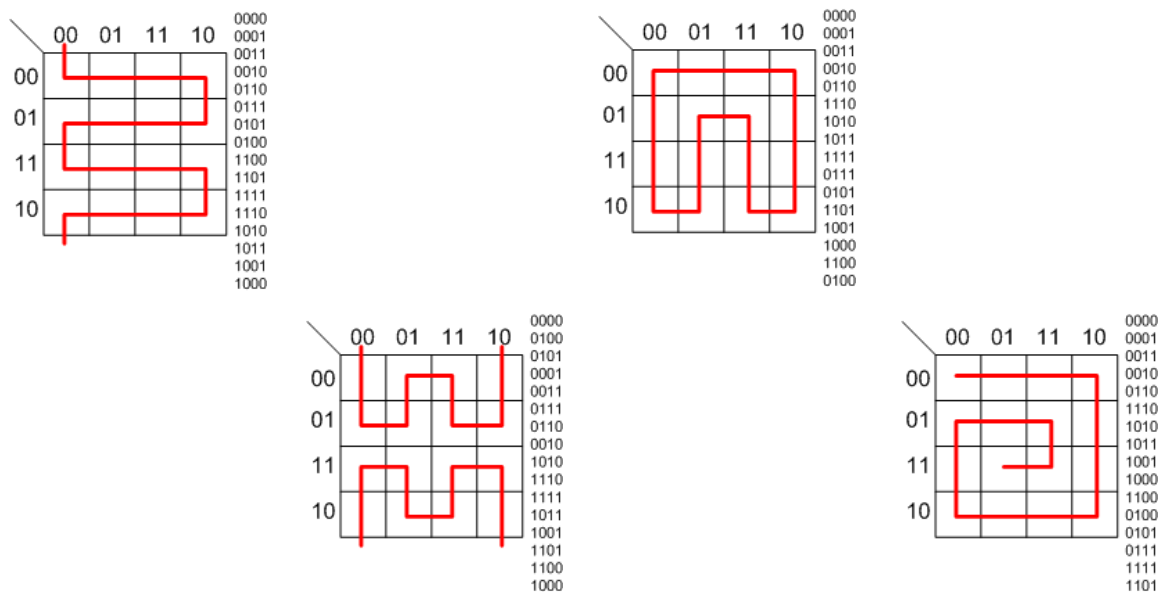

# Outline

- Minimum forms of switching functions
- Two- and three-variable Karnaugh maps
- Four-variable Karnaugh maps
- Determination of minimum expressions using essential prime implicants
- Five-variable Karnaugh maps
- Other uses of Karnaugh maps
- Other forms of Karnaugh maps

3

# Limitations of Algebraic Simplification

- Two problems of algebraic simplification
  1. Not systematic
  2. Difficult to check if a minimum solution is achieved
- The *Karnaugh map* method overcomes these limitations
  - Typically for Boolean functions with  $\leq 5$  variables
  - The Quine-McCluskey method can deal with even larger functions
    - (Subject of Unit 6, skipped)

4

# Minimum Forms of Switching Functions

- Correspondence between Boolean expressions and logic circuits
  - SOP (POS) can be implemented with two-level AND-OR (OR-AND) gate circuits
  - Reducing the number of **terms** and **literals** of an SOP expression corresponds to reducing the number of **gates** and **gate inputs**
    - Combine terms by  $XY' + XY = X$
    - Eliminate redundant terms by consensus theorem
  - Minimum SOP is not necessarily unique
  - An SOP may be minimal (locally) but not minimum (globally)
    - E.g.,
 
$$F = a'b'c' + a'b'c + a'bc' + ab'c + abc' + abc$$


$$= a'b' + b'c + bc' + ab \text{ (minimal but not minimum)}$$

$$= a'b' + bc' + ac \text{ (minimum)}$$


5

## Two-Variable Karnaugh Maps

### □ 2-variable K-map

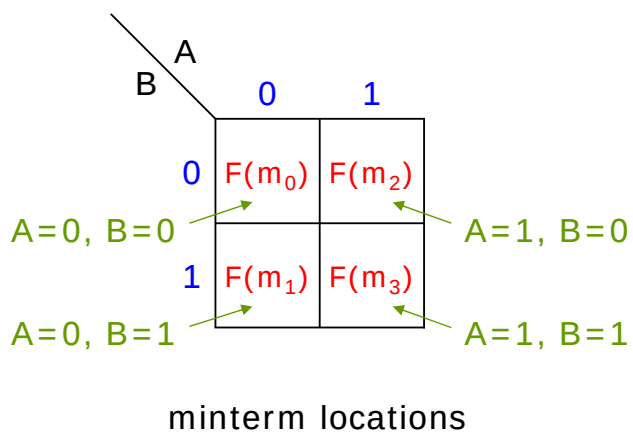

| AB | F |
|----|---|
| 00 | 1 |
| 01 | 1 |
| 10 | 0 |
| 11 | 0 |

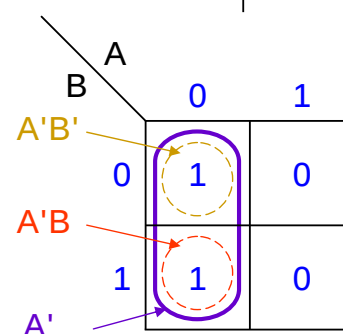

$$F = A'B' + A'B = A'(B' + B) = A'$$

6

# Three-Variable Karnaugh Maps

## 3-variable K-map

| BC \ A | 0 |   | 1 |  |
|--------|---|---|---|--|
|        |   |   |   |  |
| 00     | 0 | 4 |   |  |
| 01     | 1 | 5 |   |  |
| 11     | 3 | 7 |   |  |
| 10     | 2 | 6 |   |  |

minterm locations

| ABC | F |
|-----|---|
| 000 | 0 |
| 001 | 0 |
| 010 | 1 |
| 011 | 1 |
| 100 | 1 |
| 101 | 0 |
| 110 | 1 |
| 111 | 0 |

| BC \ A | 0 |   | 1 |  |
|--------|---|---|---|--|
|        |   |   |   |  |
| 00     | 0 | 1 |   |  |
| 01     | 0 | 0 |   |  |
| 11     | 1 | 0 |   |  |
| 10     | 1 | 1 |   |  |

$$\begin{aligned}
 F &= A'BC' + A'BC + AB'C' + ABC' \\
 &= A'B + AC' + BC' \\
 &= A'B + AC'
 \end{aligned}$$

7

# Three-Variable Karnaugh Maps

## 3-variable K-map (zeros omitted)

| BC \ A | 0 |   | 1 |  |
|--------|---|---|---|--|
|        |   |   |   |  |
| 00     |   |   |   |  |
| 01     |   |   |   |  |
| 11     | 1 | 1 |   |  |
| 10     | 1 | 1 |   |  |

B

| BC \ A | 0 |   | 1 |  |
|--------|---|---|---|--|
|        |   |   |   |  |
| 00     |   |   |   |  |
| 01     |   |   |   |  |
| 11     |   |   |   |  |
| 10     | 1 | 1 |   |  |

BC'


| BC \ A | 0 |  | 1 |  |
|--------|---|--|---|--|
|        |   |  |   |  |
| 00     |   |  | 1 |  |
| 01     |   |  |   |  |
| 11     |   |  |   |  |
| 10     |   |  | 1 |  |

AC'

8

# Three-Variable Karnaugh Maps

## 3-variable K-map

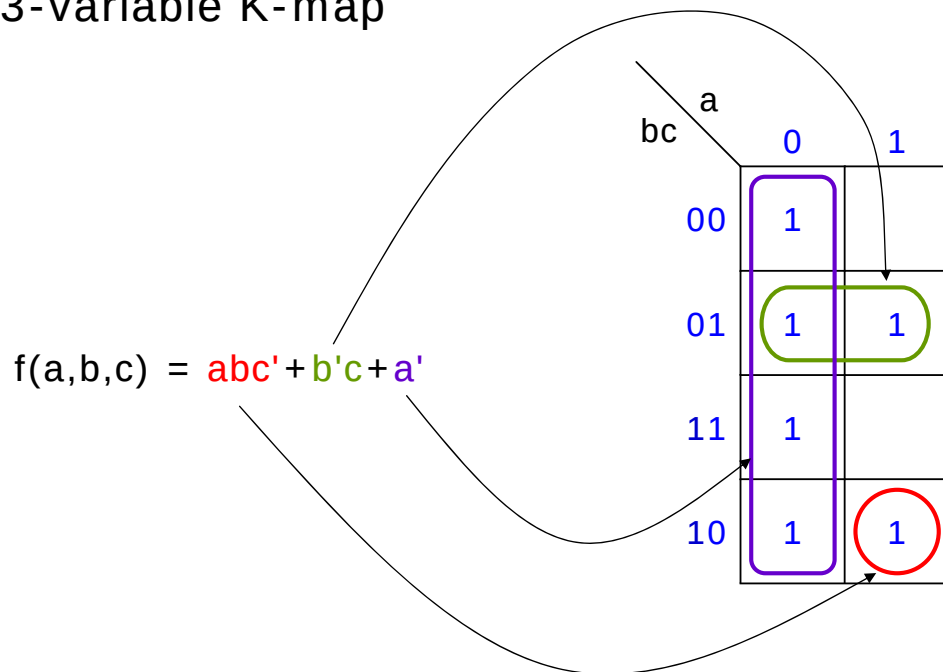

9

# Three-Variable Karnaugh Maps

## 3-variable K-map

$$F = m_1 + m_3 + m_5$$

$$= M_0 M_2 M_4 M_6 M_7$$

|    |    |   |   |
|----|----|---|---|
|    | a  | 0 | 1 |
| bc | 00 | 0 | 0 |
|    | 01 | 1 | 1 |
|    | 11 | 1 | 0 |
|    | 10 | 0 | 0 |

simplify

$$F = a'c + b'c$$

|    |    |   |   |
|----|----|---|---|
|    | a  | 0 | 1 |
| bc | 00 | 0 | 0 |
|    | 01 | 1 | 1 |
|    | 11 | 1 | 0 |
|    | 10 | 0 | 0 |

10

# Three-Variable Karnaugh Maps

## 3-variable K-map

$$G = (m_1 + m_3 + m_5)'$$

$$= (M_0 M_2 M_4 M_6 M_7)'$$

|    |    | a |   |
|----|----|---|---|
|    |    | 0 | 1 |
| bc | 00 | 1 | 1 |
|    | 01 | 0 | 0 |
|    | 11 | 0 | 1 |
|    | 10 | 1 | 1 |

simplify

|    |    | a |   |
|----|----|---|---|
|    |    | 0 | 1 |
| bc | 00 | 1 | 1 |
|    | 01 | 0 | 0 |
|    | 11 | 0 | 1 |
|    | 10 | 1 | 1 |

11

$$G = ab + c'$$

# Three-Variable Karnaugh Maps

## 3-variable K-map

|    |    | x |   |
|----|----|---|---|
|    |    | 0 | 1 |
| yz | 00 |   |   |
|    | 01 | 1 |   |
|    | 11 | 1 | 1 |
|    | 10 |   | 1 |

simplify

$$xy + x'z + yz = xy + x'z$$

(consensus theorem)

|    |    | x |   |
|----|----|---|---|
|    |    | 0 | 1 |
| yz | 00 |   |   |
|    | 01 | 1 |   |
|    | 11 | 1 | 1 |
|    | 10 |   | 1 |

# Three-Variable Karnaugh Maps

## 3-variable K-map

$$F = a'b' + bc' + ac = a'c' + b'c + ab$$

|    |    |   |   |
|----|----|---|---|
|    |    | a |   |
|    |    | 0 | 1 |
| bc | 00 | 1 |   |
|    | 01 | 1 | 1 |
|    | 11 |   | 1 |
|    | 10 | 1 | 1 |

|    |    |   |   |
|----|----|---|---|
|    |    | a |   |
|    |    | 0 | 1 |
| bc | 00 | 1 |   |
|    | 01 | 1 | 1 |
|    | 11 |   | 1 |
|    | 10 | 1 | 1 |

13

# Four-Variable Karnaugh Maps

## 4-variable K-map

$$F = acd + a'b + d'$$

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | AB |    |    |    |
|    |    | 00 | 01 | 11 | 10 |
| CD | 00 | 0  | 4  | 12 | 8  |
|    | 01 | 1  | 5  | 13 | 9  |
|    | 11 | 3  | 7  | 15 | 11 |
|    | 10 | 2  | 6  | 14 | 10 |

minterm locations

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | ab |    |    |    |
|    |    | 00 | 01 | 11 | 10 |
| cd | 00 | 1  | 1  | 1  | 1  |
|    | 01 |    | 1  |    |    |
|    | 11 |    | 1  | 1  | 1  |
|    | 10 | 1  | 1  | 1  | 1  |

14

# Four-Variable Karnaugh Maps

## 4-variable K-map

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  | 1  |    |
| 01      | 1  | 1  | 1  |    |
| 11      | 1  |    |    |    |
| 10      |    |    |    | 1  |

$$f_1 = \sum m(1,3,4,5,10,12,13)$$

simplify

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  | 1  |    |
| 01      | 1  | 1  | 1  |    |
| 11      | 1  |    |    |    |
| 10      |    |    |    | 1  |

$$f_1 = ab'cd' + a'b'd + bc'$$

15

# Four-Variable Karnaugh Maps

## 4-variable K-map

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  |    |    | 1  |
| 01      |    | 1  |    |    |
| 11      | 1  | 1  | 1  | 1  |
| 10      | 1  | 1  | 1  | 1  |

$$f_2 = \sum m(0,2,3,5,6,7,8,10,11,14,15)$$

simplify

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  |    |    | 1  |
| 01      |    | 1  |    |    |
| 11      | 1  | 1  | 1  | 1  |
| 10      | 1  | 1  | 1  | 1  |

$$f_2 = c + b'd' + a'bd$$

16



# Four-Variable Karnaugh Maps

## □ Simplify incompletely specified function

- All the 1's must be covered, but X's are optional and are set to 1's only if they will simplify the expression

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    | X  |    |
| 01      | 1  | 1  | X  | 1  |
| 11      | 1  | 1  |    |    |
| 10      |    | X  |    |    |

simplify

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    | X  |    |
| 01      | 1  | 1  | X  | 1  |
| 11      | 1  | 1  |    |    |
| 10      |    | X  |    |    |

$$f = \sum m(1,3,5,7,9) + \sum d(6,12,13)$$

$$f = a'd + c'd$$

17

# Four-Variable Karnaugh Maps

## □ Simplify product-of-sums

- Circle 0's instead of 1's
- Apply De Morgan's law converting SOP to POS

| yz \ wx | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  | 0  | 1  |
| 01      | 0  | 0  | 0  | 0  |
| 11      | 1  | 0  | 1  | 1  |
| 10      | 1  | 0  | 0  | 1  |

simplify

| yz \ wx | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  | 0  | 1  |
| 01      | 0  | 0  | 0  | 0  |
| 11      | 1  | 0  | 1  | 1  |
| 10      | 1  | 0  | 0  | 1  |

$$f = x'z' + wyz + w'y'z' + x'y$$

$$f' = y'z + wxz' + w'xy$$

$$f = (y+z')(w'+x'+z)(w+x'+y')$$

18

# Determination of Minimum Expressions Using Essential Prime Implicants

## □ Implicant

- A product term of a function
  - Any single 1 or any group of 1's on a K-map combined together forms a product term


## □ Prime implicant

- A maximal implicant
  - An implicant that cannot be combined with another term to eliminate a variable
- All of the prime implicants of a function can be obtained from a K-map by expanding the 1's as much as possible in every possible way

19

# Determination of Minimum Expressions Using Essential Prime Implicants

## Example

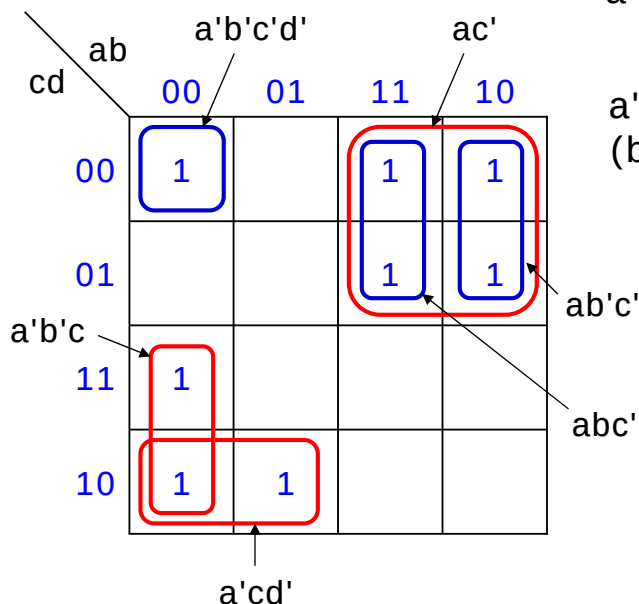

$a'b'c$ ,  $a'cd'$ ,  $ac'$  are prime implicants

$a'b'c'd'$ ,  $abc'$ ,  $ab'c'$  are implicants  
(but not prime implicants)

20


# Determination of Minimum Expressions Using Essential Prime Implicants

## □ Determine all prime implicants

- In finding prime implicants, don't cares are treated as 1's. However, a prime implicant composed entirely of don't cares can never be part of the minimum solution
- Not all prime implicants are needed in forming the minimum SOP
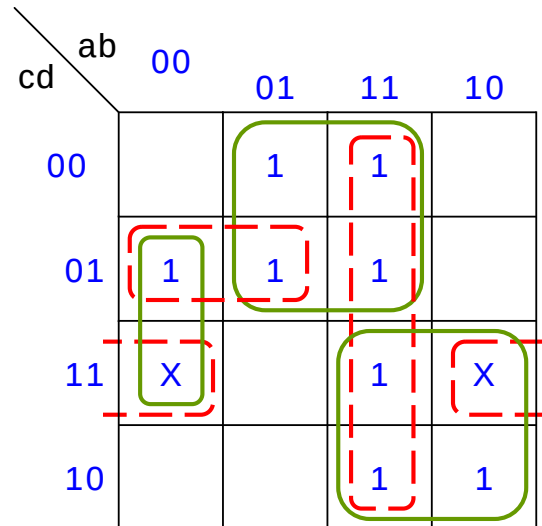
### Example

- All prime implicants:  $a'b'd$ ,  $bc'$ ,  $ac$ ,  $a'c'd$ ,  $ab$ ,  $b'cd$  (composed entirely of don't cares)
- Minimum solution:  
 $F = a'b'd + bc' + ac$




21

# Determination of Minimum Expressions Using Essential Prime Implicants
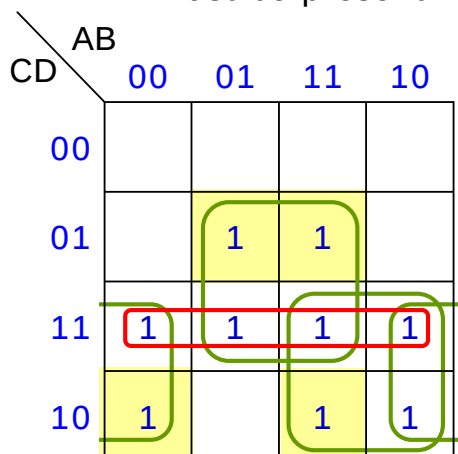
## □ Essential prime implicant (EPI)


- A prime implicant that covers some minterm not covered by any other prime implicant
  - If a single term covers some minterm and **all** of its adjacent 1's and X's, then the term is an EPI
- Must be present in the minimum SOP



$$f = CD + BD + B'C + AC$$

EPIs already cover all 1's

Minimum SOP!

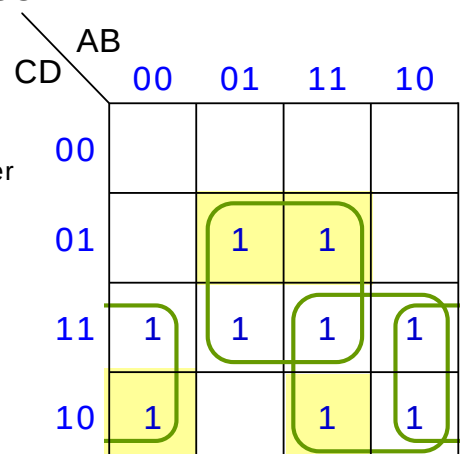

$$f = BD + B'C + AC$$


22

# Determination of Minimum Expressions Using Essential Prime Implicants

## □ SOP minimization

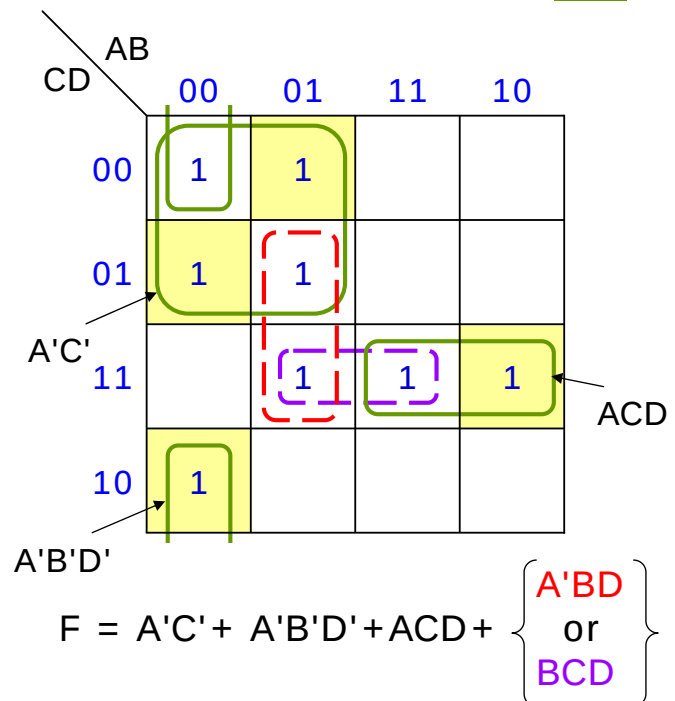1. Select all essential prime implicants
2. Find a minimum set of prime implicants which cover the minterms not covered by the essential prime implicants


- There may be freedom left after all essential prime implicants are selected (it affects optimality especially for functions with more variables)



23

# Determination of Minimum Expressions Using Essential Prime Implicants
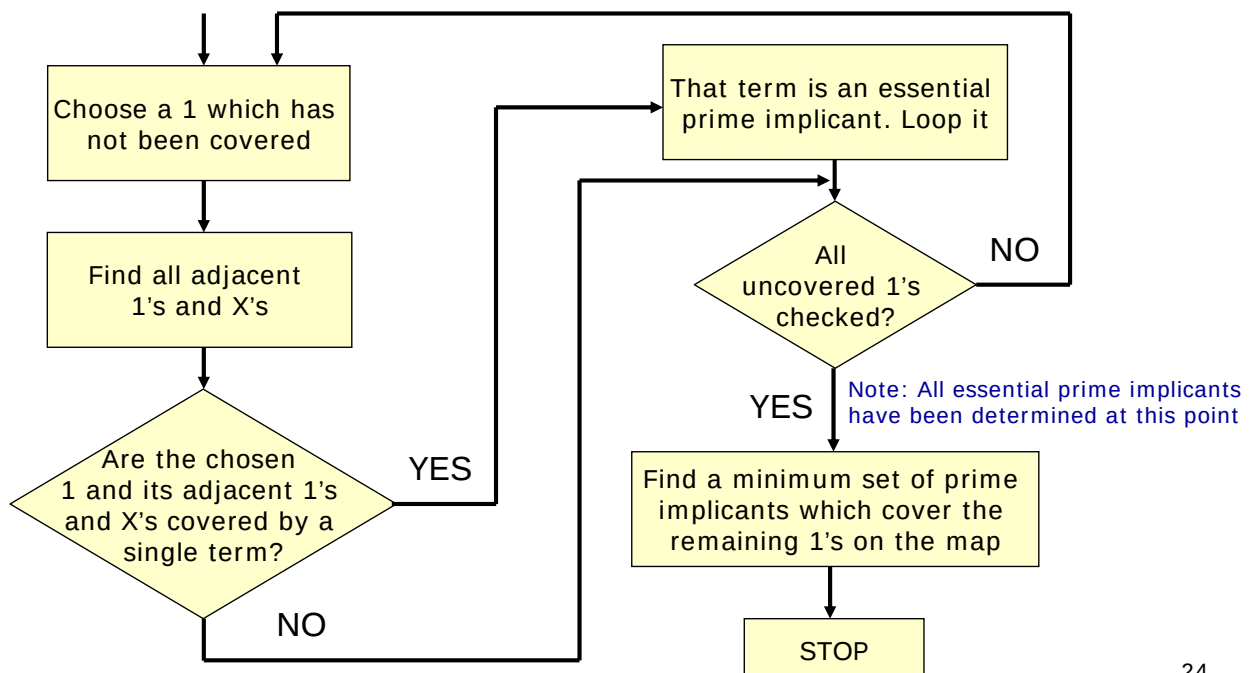
## □ Flowchart for determining a minimum SOP using K-map



24

# Determination of Minimum Expressions Using Essential Prime Implicants

## Example

|    |    | AB    |       |          |          |
|----|----|-------|-------|----------|----------|
|    |    | 00    | 01    | 11       | 10       |
| CD | 00 | $X_0$ | $1_4$ |          | $1_8$    |
|    | 01 |       | $1_5$ | $1_{13}$ | $1_9$    |
|    | 11 |       | $X_7$ | $X_{15}$ |          |
|    | 10 |       | $1_6$ |          | $1_{10}$ |

Step 1:  $1_4$  checked

Step 2:  $1_5$  checked

Step 3:  $1_6$  checked

EPI  $\rightarrow A'B$  selected

Step 4:  $1_8$  checked

Step 5:  $1_9$  checked

Step 6:  $1_{10}$  checked

EPI  $\rightarrow AB'D'$  selected

Step 7:  $1_{13}$  checked

(up to this point all EPIs determined)

Step 8:  $AC'D$  selected to cover remaining 1's

25

# Five-Variable Karnaugh Maps

## 5-var K-map

|     |    | BC |    |    |    |
|-----|----|----|----|----|----|
|     |    | 00 | 01 | 11 | 10 |
| A   | DE | 16 | 20 | 28 | 24 |
|     | 00 | 0  | 4  | 12 | 8  |
|     | 01 | 17 | 21 | 29 | 25 |
|     | 11 | 19 | 23 | 31 | 27 |
| 1/0 | 10 | 18 | 22 | 30 | 26 |
|     |    | 2  | 6  | 14 | 10 |

minterm locations

These two terms does not combine


|     |    | BC |    |    |    |
|-----|----|----|----|----|----|
|     |    | 00 | 01 | 11 | 10 |
| A   | DE | 1  | 1  | 1  | 1  |
|     | 00 | 1  | 1  | 1  | 1  |
|     | 01 | 1  | 1  | 1  | 1  |
|     | 11 | 1  | 1  | 1  | 1  |
| 1/0 | 10 | 1  | 1  | 1  | 1  |
|     |    | 1  | 1  | 1  | 1  |

$AB'DE'$     $CDE$     $BD'$

26

# Five-Variable Karnaugh Maps


## 5-var K-map

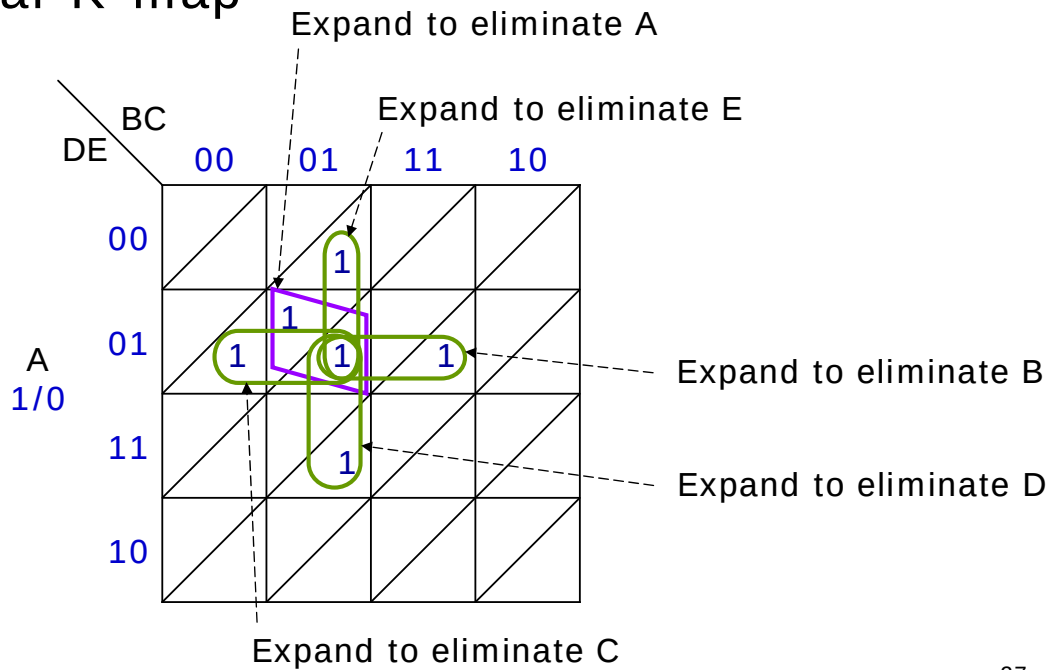

27

# Five-Variable Karnaugh Maps


## 5-var K-map

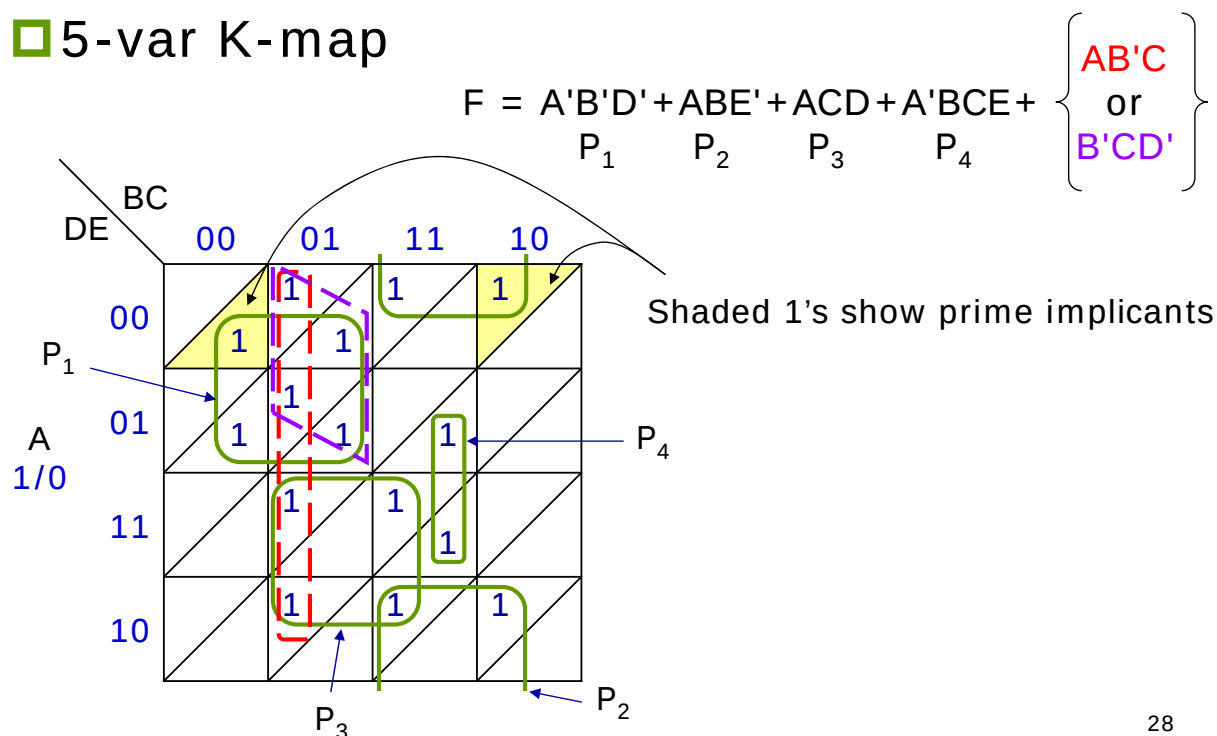

28

# Five-Variable Karnaugh Maps

## 5-var K-map

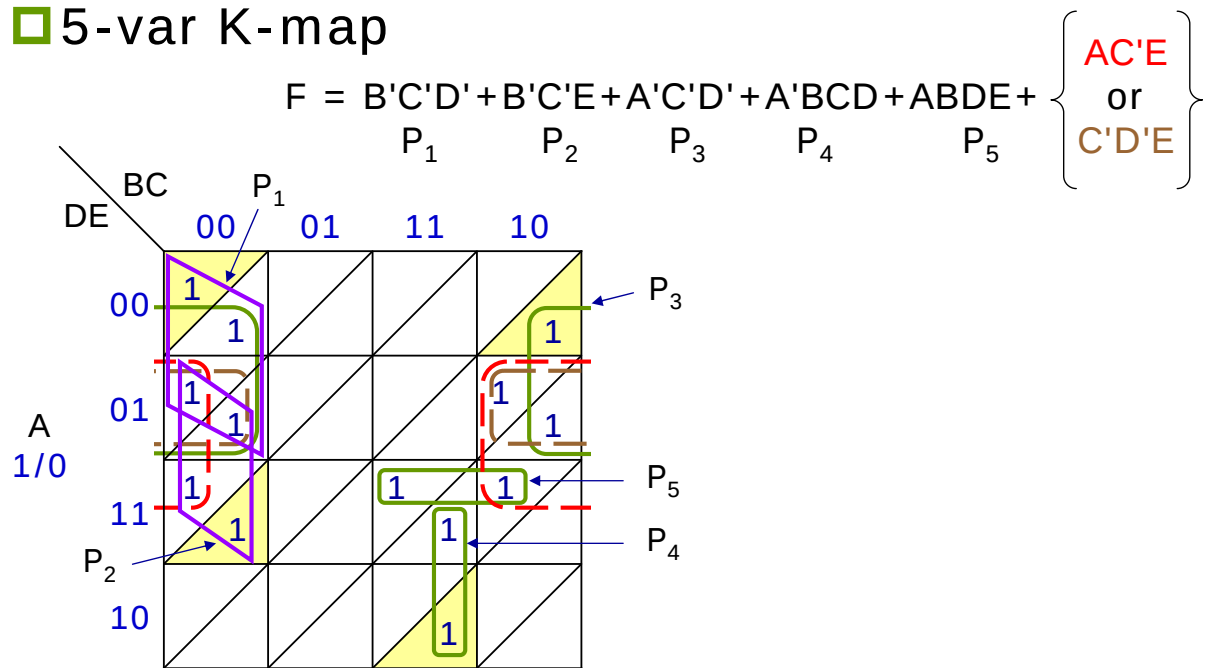

29

## Other Uses of Karnaugh Maps


- ☐ Use K-map to prove the equivalence of two Boolean expressions
  - ☐ K-maps are canonical representations of Boolean functions, similar to truth tables
- ☐ Use K-map to perform Boolean operations
  - ☐ AND, OR, NOT operations can be done over K-maps (truth tables)

30

## Other Uses of Karnaugh Maps
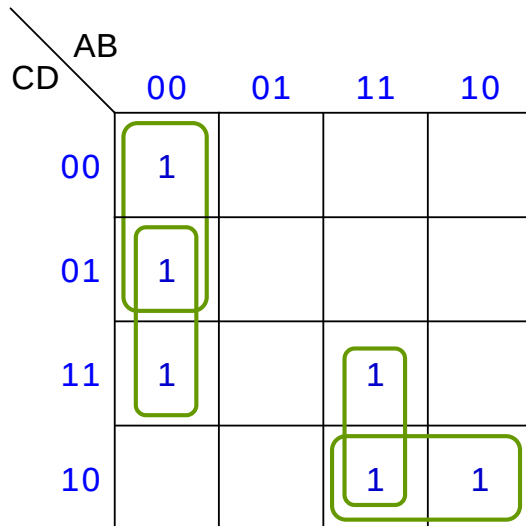
### Use K-map to facilitate factoring

- Identify common literals among product terms




$$F = A'B'C' + A'B'D + ACB + ACD'$$

$$= A'B'(C' + D) + AC(B + D')$$

31

## Other Uses of Karnaugh Maps

### Use K-map to guide simplification

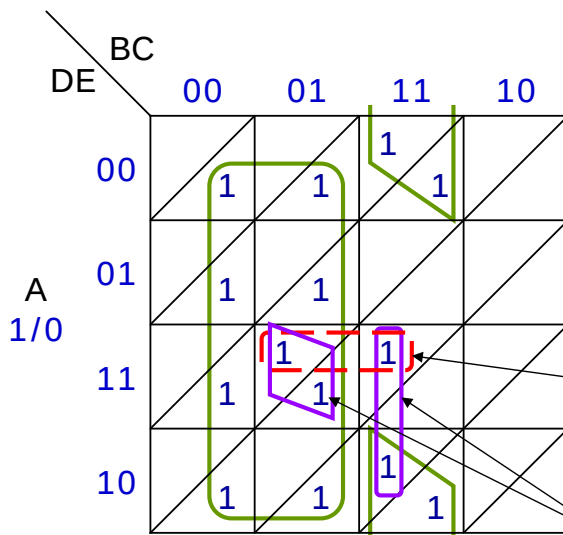

$$F = ABCD + B'CDE + A'B' + BCE'$$

$$= ABCD + B'CDE + A'B' + BCE' + ACDE$$

$$= A'B' + BCE' + ACDE$$

Add this term


Then these two terms can be removed

32



# Other Forms of Karnaugh Maps

## Other conventions (Veitch diagrams)

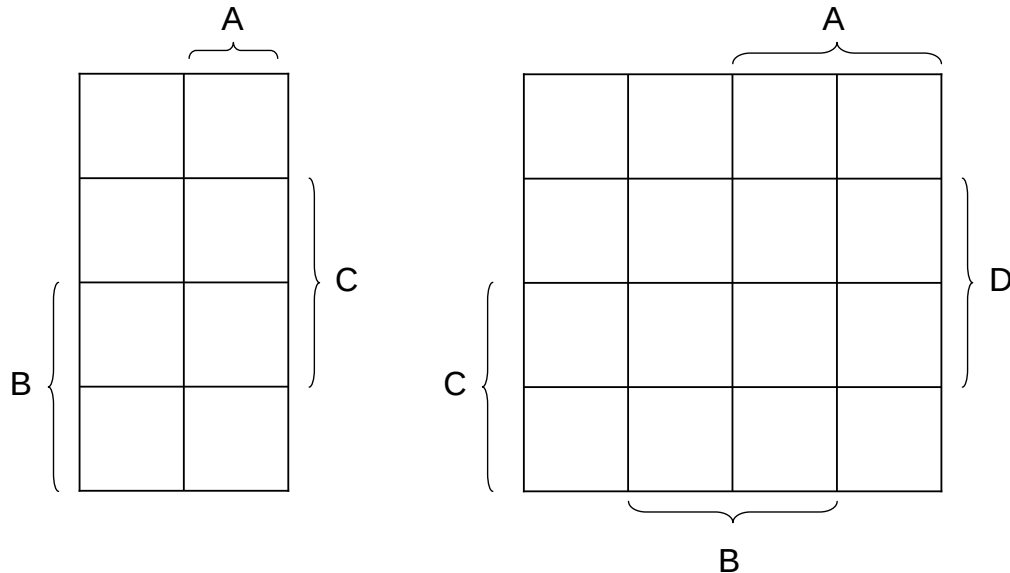


33

# Other Forms of Karnaugh Maps
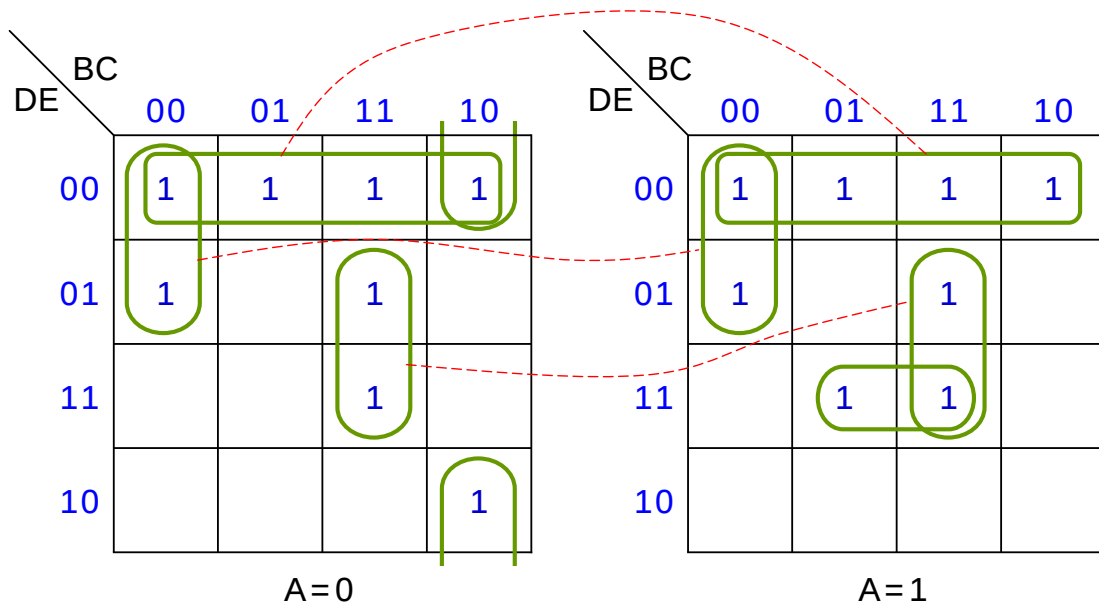
## Other conventions (5-var K-map)

$$F = D'E' + B'C'D' + BCE + A'BC'E' + ACDE$$



34

# Other Forms of Karnaugh Maps

## Other conventions (5-var Veitch diagram)

$$F = D'E' + B'C'D' + BCE + A'BC'E' + ACDE$$

