

# Logic Synthesis and Verification

Jie-Hong Roland Jiang  
江介宏

Department of Electrical Engineering  
National Taiwan University



Fall 2012

1

# Sequential Synthesis

part of the following slides are by  
courtesy of Andreas Kuehlmann

2

## Motivation

- Pure combinational optimization can be **suboptimal** since relations across register boundaries are disregarded

3

## Overview of Circuit Optimization



4

## Sequential Optimization Techniques

- Clock skew scheduling
  - balance path delays by adjusting the relative clocking schedule of individual registers
- Retiming
  - balance path delays by moving registers within circuit topology
  - can be interleaved with combinational optimization techniques
- Architectural restructuring
  - add sequential redundancy
    - fixed: does not change input/output behavior
    - flexible: change input output behavior
- System-level optimization

5

## Integration in Design Flow



- Optimization space
  - significantly more optimization freedom at a higher level for improving performance, power, area, etc.
- Distance from physical implementation
  - difficult to accurately model impacts on final implementation
  - difficult to mathematically characterize optimization space
- Verification challenge
  - departure from combinational comparison model would impede formal equivalence checking
  - different simulation behaviors cause acceptance problems
- **Necessity of tight tool integration!**

6

## Sequential Timing Constraints
  
### □ Minimum clock period

- $t_{clk}(min) = \max\{t_p, t_x\} + t_c + t_{su}$ , where  $t_x$  is the time after the active clock edge at which the X inputs are stable





7

## Sequential Timing Constraints

### □ Setup-time constraint

- $C_p \geq t_p + t_c^{max} + t_{su}$

  


$C_p$ : clock period

8

## Sequential Timing Constraints


### Hold-time constraint

- $t_p + t_c^{\min} \geq t_h$

 

9


## Clock Skew Scheduling

 

$$T_{\text{cycle}} - T_{\text{setup}} + \text{skew} \geq D_{\text{max}}$$

$$T_{\text{hold}} + \text{skew} \leq D_{\text{min}}$$

$$0 \leq |\text{skew}| < T_{\text{cycle}}$$

 

10

## Clock Skew Scheduling

### By controlling clock delays on registers, clock frequency may be increased

- Do not change transition and output functions (not the case in retiming)
  - Good for functional verification
- May require sophisticated timing verification

### Clock skew: clock signal arrives at different registers at different times

- Positive skew: the sending register gets the clock earlier than the receiving register
- Negative skew: the receiving register gets the clock earlier than the sending register

11

## Clock Skew Scheduling

### Pros


- Inexpensive “post synthesis” technique to further reduce clock period
- Combinational design model is preserved

### Cons

- Setup **and** hold time constraints must be obeyed
  - including hold time constraints from scan chain
- Interleaving with combinational optimizations impossible
- Replication of clocking tree required

12

## Retiming

 


13

## Retiming
 
### Optimize sequential circuits by repositioning registers

- Move registers so that clock cycle decreases or register count decreases
- Input-output behavior is preserved; however, transition and output functions are changed due to the register movement



14

## Retiming

### Pros


- Only setup time constraint (0 clock skew)
- Simple integration with other logical (e.g. combinational) or physical optimizations
  - E.g., iterative retiming and resynthesis
- Easy combination with clock skew scheduling to obtain global optimum

### Cons

- Change combinational model of design
  - Severe impact on verification methodology
- Inaccurate delay model
- Computation of equivalent reset state required

15

## Architectural Retiming

 

16

## Architectural Retiming

- Pros
  - Smooth extension of regular retiming
  - Potential to alleviate global performance bottlenecks by adding sequential redundancy and pipelining
- Cons
  - Significant change of design structure
    - substantial impact on verification methodology
  - Flexible architectural restructuring changes I/O behavior
    - existing RTL specification methods not always applicable

17


## Verification Issues

- Timing verification unchanged
- Functional verification affected
  - Except for clock skew scheduling, sequential optimization **does** change register (transition) functions
  - Traditional combinational equivalence checking not applicable
  - Simulation runs not recognizable by designers - acceptance problems
  - Solution:
    - preserve retime function (mapping function) from synthesis for:
      - reducing sequential EC problem back to combinational case
        - *no false positives possible!*
      - modifying simulation model to reproduce original simulation output

18
 
## Retiming Circuits

- Objectives:
  - Reduce clock cycle time
  - Reduce register count (area)
  - Reduce power, etc.
- Input: A netlist of gates and registers



19

## Retiming Circuits


- Circuit represented as retiming graph  $G(V, E)$  [Leiserson and Saxe 1983, 1991]
  - V: vertex set representing logic gates
  - E: edge set representing connections
  - $d(v)$  = delay of gate/vertex  $v$ , ( $d(v) \geq 0$ )
  - $w(e)$  = number of registers on edge  $e$ , ( $w(e) \geq 0$ )

20

# Retiming Circuits
 
## Example

- **Synchronous circuit** assumption: every cycle of a circuit has at least one register, i.e., no combinational loop



The host node represents the environment that interacts with the circuit via the primary inputs and outputs

Operation	delay
$\delta$	3
+	7


# Retiming Circuits

- For a path  $p : v_0 \xrightarrow{e_0} v_1 \xrightarrow{e_1} \dots \xrightarrow{e_{k-1}} v_k$

- Path delay  $d(p) = \sum_{i=0}^k d(v_i)$  (includes endpoints)
- Path weight  $w(p) = \sum_{i=0}^{k-1} w(e_i)$

## Minimum clock cycle


$$c = \max_{p: w(p)=0} \{d(p)\}$$

 

# Retiming Circuits
 
## Atomic operation

- Move registers across a gate in a forward or backward direction



- Does not affect gate functionality, but timing

# Retiming Circuits



- Retiming can be formalized with a **retime function**  $r: V \rightarrow \mathbb{Z}$ , where  $\mathbb{Z}$  is the set of integers

- I.e., a retime function performs integer labeling on vertices

- Weight update after retiming with  $r$

- $w_r(e) = w(e) + r(v) - r(u)$ , for edge  $e = (u, v)$
- $w_r(p) = w(p) + r(t) - r(s)$ , for path  $p$  from  $s$  to  $t$

  - A retiming with some  $r$  is **legal** if  $w_r(e) \geq 0, \forall e \in E$



# Min-Cycle Retiming

## Problem Statement: (minimum cycle retiming)

Given  $G(V, E)$  with delay function  $d$  and weight function  $w$ , find a legal retiming  $r$  so that

$$c = \max_{p: w_r(p)=0} \{d(p)\}$$

is minimized

## Retiming: two important matrices

- Register weight matrix


$$W(u, v) = \min_p \{w(p) : u \xrightarrow{p} v\}$$

- Delay matrix

$$D(u, v) = \max_p \{d(p) : u \xrightarrow{p} v, w(p) = W(u, v)\}$$

# Min-Cycle Retiming

## Example

 

For some constant  $\alpha$ , minimum clock cycle  $c \leq \alpha \Leftrightarrow \forall p, \text{ if } d(p) > \alpha \text{ then } w(p) \geq 1$

	W				D				
	V0	V1	V2	V3	V0	V1	V2	V3	
V0	0	2	2	2	0	3	6	13	V0
V1	0	0	0	0	13	3	6	13	V1
V2	0	∞	0	0	10	∞	3	10	V2
V3	0	∞	∞	0	7	∞	∞	7	V3

W = register path weight matrix (minimum # registers on all paths between u and v)  
 D = path delay matrix (maximum delay on the paths between u and v with  $w(p)=W(u,v)$ )

Don't count paths passing through the host!

# Min-Cycle Retiming

- Assume that we are asked to check if a retiming exists for a clock cycle  $\alpha$

- Legal retiming:  $w_r(e) \geq 0$  for all e. Hence

$$w_r(e) = w(e) + r(v) - r(u) \geq 0, \text{ or } r(u) - r(v) \leq w(e)$$

- For all paths  $p: u \rightarrow v$  such that  $d(p) \geq \alpha$ , we require  $w_r(p) \geq 1$ . Thus

$$1 \leq w_r(p) = \sum_{i=0}^{k-1} w_r(e_i) \\ = \sum_{i=0}^{k-1} [w(e_i) + r(v_{i+1}) - r(v_i)] \\ = w(p) + r(v_k) - r(v_0) \\ = w(p) + r(v) - r(u)$$

- Take the least  $w(p)$  (tightest constraint)  $r(u) - r(v) \leq W(u,v) - 1$

- Note: This is independent of the path from u to v, so we just need to apply it to u, v such that  $D(u,v) > \alpha$

# Min-Cycle Retiming

## Example

Assume  $\alpha = 7$

Legality:

$$r(u) - r(v) \leq w(e)$$


$$\begin{aligned} r(v_0) - r(v_1) &\leq 2 \\ r(v_1) - r(v_2) &\leq 0 \\ r(v_1) - r(v_3) &\leq 0 \\ r(v_2) - r(v_3) &\leq 0 \\ r(v_3) - r(v_0) &\leq 0 \end{aligned}$$

$D > 7$ :

$$r(u) - r(v) \leq W(u,v) - 1$$

$$\begin{aligned} r(v_0) - r(v_3) &\leq 1 \\ r(v_1) - r(v_0) &\leq -1 \\ r(v_1) - r(v_3) &\leq -1 \\ r(v_2) - r(v_0) &\leq -1 \\ r(v_2) - r(v_3) &\leq -1 \end{aligned}$$

	W				D				
	V0	V1	V2	V3	V0	V1	V2	V3	
V0	0	2	2	2	0	3	6	13	V0
V1	0	0	0	0	13	3	6	13	V1
V2	0	∞	0	0	10	∞	3	10	V2
V3	0	∞	∞	0	7	∞	∞	7	V3

 

All constraints are in the difference-of-2-variable form and closely related to shortest path problem

# Min-Cycle Retiming

## Example

Legality:  
 $r(u) - r(v) \leq w(e)$

$D > 1$ :  
 $r(u) - r(v) \leq W(u,v) - 1$

$$r(v_0) - r(v_1) \leq 2$$

$$r(v_0) - r(v_3) \leq 1$$

$$r(v_1) - r(v_2) \leq 0$$

$$r(v_1) - r(v_0) \leq -1$$

$$r(v_1) - r(v_3) \leq 0$$

$$r(v_1) - r(v_3) \leq -1$$

$$r(v_2) - r(v_3) \leq 0$$


$$r(v_2) - r(v_0) \leq -1$$

$$r(v_3) - r(v_0) \leq 0$$

$$r(v_2) - r(v_3) \leq -1$$

Search shortest path on constraint graph:  
 Bellman-Ford algorithm  $O(|V||E|)$  or  $O(|V|^3)$

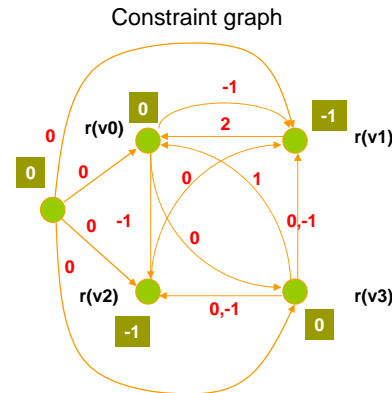
A solution exists if and only if there exists **no** negative weighted cycle



A solution is  $r(v_0) = r(v_3) = 0$ ,  
 $r(v_1) = r(v_2) = -1$

# Min-Cycle Retiming

To find the minimum cycle time, do a binary search among the entries of the D matrix  $O(|V||E| \log |V|)$

 

# Min-Cycle Retiming

**Theorem:**  $r$  is a legal retiming on  $G$  such that the clock cycle  $c \leq \alpha$  for some constant  $\alpha$  if and only if

1.  $r(v_h) = 0$
2.  $r(u) - r(v) \leq w(e)$  for every edge  $e(u,v)$
3.  $r(u) - r(v) \leq W(u,v) - 1$  (i.e. register count  $> 1$ ) for every  $(u,v)$  with  $D(u,v) > \alpha$

Solve the integer linear programming problem

- Bellman-Ford method  $O(|V|^3)$

# Min-Cycle Retiming

Algorithm of optimal retiming:

1. Compute  $W$  and  $D$
2. Binary search the minimum achievable clock period by applying Bellman-Ford algorithm to check the satisfaction of the prior Theorem
3. Derive  $r(v)$  under the minimum achievable clock period found in Step 2


Complexity  $O(|V|^3 \lg |V|)$



## Min-Cycle Retiming

### Two more algorithms:

1. Relaxation based:
  - Repeatedly find critical path
  - Retime vertex at end of path by +1 ( $O(|V||E|\log|V|)$ )

 

2. Also, Mixed Integer Linear Program formulation

33

## Min-Area Retiming

### Goal: minimize number of registers used

$$\begin{aligned}
 \min N_r &= \sum_{e \in E} w_r(e) \\
 &= \sum_{e: u \rightarrow v} (w(e) + r(v) - r(u)) \\
 &= \sum_{e \in E} w(e) + \sum_{e: u \rightarrow v} (r(v) - r(u)) \\
 &= N + \sum_{u \rightarrow v} (r(v) - r(u)) \\
 &= N + \sum_{v \in V} [r(v)(\# \text{fanin}(v) - \# \text{fanout}(v))] \\
 &= N + \sum_{v \in V} a_v r(v)
 \end{aligned}$$

where  $a_v$  is a constant

34

## Min-Area Retiming

### Minimize:

$$\sum_{v \in V} a_v r(v)$$

### Subject to:

$$w_r(e) = w(e) + r(v) - r(u) \geq 0$$

**Note:** It is reducible to a flow problem

35

## Retiming Issues

### Computation of equivalent initial states

- Equivalent initial states may not always exist



- General solution requires replication of logic for initialization

### Timing models

- Too far away from actual implementation

36

## Retiming + Clock Scheduling

### Mathematical formulation

- $s: E \rightarrow \mathbb{R}$ , a real edge labeling
- $s(e)$  denotes the clock signal delay of all registers of  $e$

- In addition to the register weight matrix and delay matrix for the maximum delay, we also need the minimum paths delays

$$W(u, v) = \min_p \{w(p) : u \xrightarrow{p} v\}$$

$$D(u, v) = \max_p \{d(p) : u \xrightarrow{p} v, w(p) = w(u, v)\}$$

$$D_{\min}(u, v) = \min_p \{d(p) : u \xrightarrow{p} v, w(p) = w(u, v)\}$$

37

## Retiming + Clock Scheduling

- A valid retiming and clock skew schedule is an assignment to  $r$  and  $s$  such that:

$$(1) \quad w_r \geq 0$$

$$(2) \quad \forall (u', u), (v, v') :$$

$$w(u', u) > 0 \wedge w(v, v') > 0 \wedge W(u, v) = 0 \Rightarrow$$

$$D_{\min}(u, v) + s(u', u) - s(v, v') \geq T_{hold} \wedge$$

$$D(u, v) + s(u', u) - s(v, v') \leq T_{clock} - T_{setup}$$

- Solution Mixed Integer Linear Program (MILP)

38

## Retiming & Resynthesis


- Combine retiming and combinational optimization

- Retime registers such that the circuit has a large combinational logic block for optimization
- Resynthesize the combinational logic block with combinational logic minimization techniques
- Retiming and resynthesis can be iterated
  - Can achieve any state re-encoding

39

## Retiming & Resynthesis

- Example

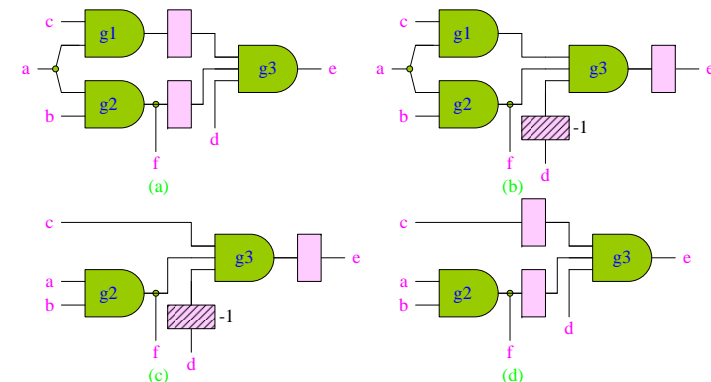

40