

# Switching Circuits & Logic Design

Jie-Hong Roland Jiang  
江介宏


Department of Electrical Engineering  
National Taiwan University



Fall 2013

1
 
## §8 Combinational Circuit Design and Simulation Using Gates



<http://arthistory.about.com/>

2

# Outline

- Gate delays and timing diagrams
- Hazards in combinational logic
- Simulation and testing of logic circuits

3

# Design of Circuits with Limited Gate Fan-in

- If a 2-level realization of a circuit requires more gate inputs than allowed, factoring the logic expression to obtain a multi-level realization may be necessary


## Example

- Realize  $f(a,b,c,d) = \sum m(0,3,4,5,8,9,10,14,15)$  using 3-input NOR gates

	ab			
cd	00	01	11	10
00			0	
01	0		0	
11		0		0
10	0	0		

$$f' = b'd(a'c' + ac) + a'c(b+d') + abc'$$
 
$$f = [b+d' + (a+c)(a'+c')][a+c'+b'd][a'+b'+c]$$




4

# Gate Delays and Timing Diagrams
 
## Gate Delays

- The output of a logic gate takes a finite time (**propagation delay**) to react to an input change
  - Propagation delays for IC gates are typically in a few nanoseconds ( $ns = 10^{-9}$  sec)
  - Propagation delays for  $0 \rightarrow 1$  and  $1 \rightarrow 0$  output changes may be different





5

# Gate Delays and Timing Diagrams
  
## Timing Diagrams

- A timing diagram shows various signals in the circuit as a function of time




6


# Gate Delays and Timing Diagrams

## Timing Diagrams

### □ Circuit with a delay element

 

 Assume AND-gate has a propagation delay  $\epsilon$   $\mu$ s



7

## Hazards in Combinational Circuits


- When the input to a combinational circuit changes, unwanted switching transients (**hazards**) may appear in the output
  - These transients occur when different paths from input to output have different propagation delays
- Hazards are undesirable
  - They consume power/energy
  - They may result in function errors in certain circuit design styles (e.g., domino logic)
  - They may slow down the performance of sequential circuits

8

# Hazards in Combinational Circuits
 
## Types of Hazards

- **Static 1-hazard:** a circuit output may momentarily go to 0 when it should remain a constant 1
- **Static 0-hazard:** a circuit output may momentarily go to 1 when it should remain a constant 0
- **Dynamic hazard:** a circuit output may change 3 or more times when it should change from 0 to 1 (or 1 to 0)



The steady-state output of the circuit is correct, but a switching transient appears at the output when the input is changed

9

# Hazards in Combinational Circuits

## Hazards in 2-level Circuits

- Hazards of 2-level AND-OR (OR-AND) circuits can be detected using K-maps and removed by adding terms (clauses)
  - Static 1-hazard can appear in 2-level AND-OR circuits
  - Static 0-hazard can appear in 2-level OR-AND circuits


10

# Hazards in Combinational Circuits

## Static 1-Hazard
 
### Example

- Letting  $A = C = 1$  and  $B$  from 1 to 0 results in a static 1-hazard ( $F = B + B'$  with delayed inversion)
  - As seen from the K-map, no loop covers both minterms  $ABC$  and  $AB'C$




11

# Hazards in Combinational Circuits

## Static 1-Hazard

### Example (cont'd)

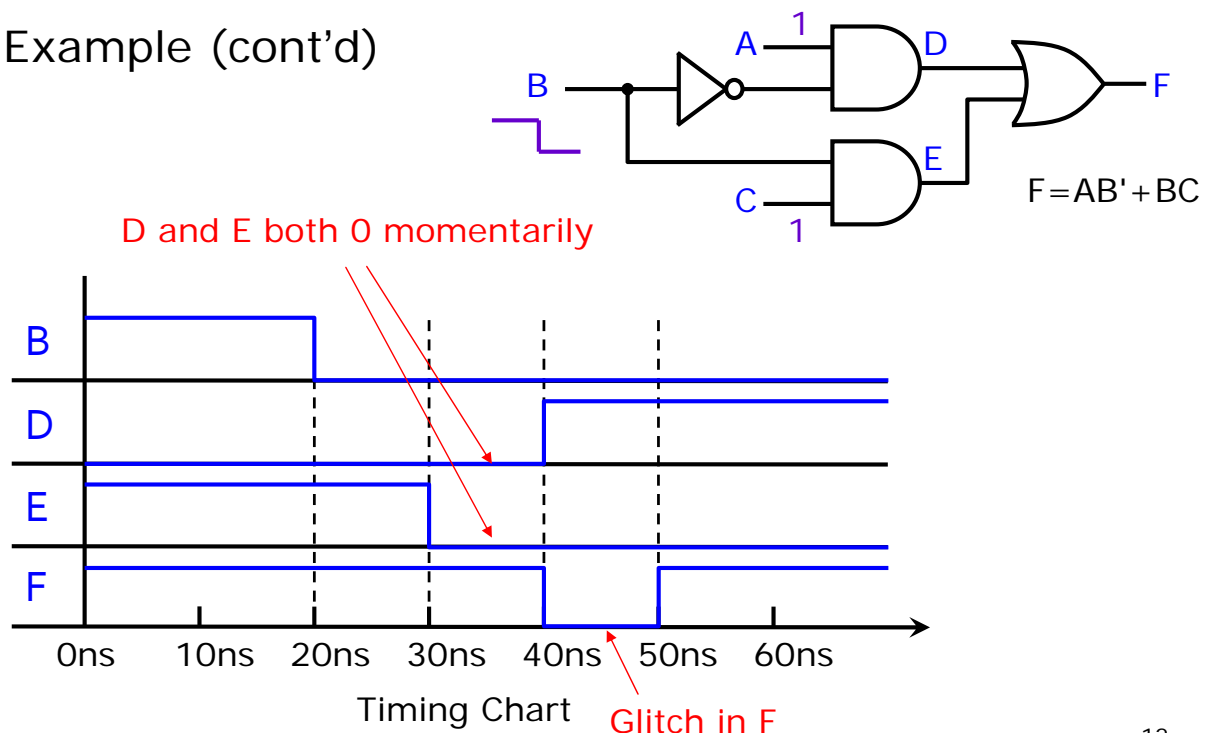

12

# Hazards in Combinational Circuits

## Hazard Detection and Removal

- **Hazard detection** procedure for 2-level AND-OR circuits
  1. Derive SOP expression of the circuit
  2. Plot each product term on K-map and loop it
  3. If any two adjacent 1's are not covered by the same loop, a 1-hazard exists for the transition between these two 1's
    - For an n-variable map, this transition occurs when one variable changes and the other n-1 variables are held constant (due to adjacent 1's )
- **Hazard removal** for 2-level AND-OR circuits
  - Add a loop to the map covering such adjacent 1's, and then add the corresponding gate to the circuit


13

# Hazards in Combinational Circuits

## Hazard Detection and Removal

 Example (cont'd)

- **Circuit with hazard removed**
  - The new added product term AC keeps on 1 (for A=C=1) when B changes from 1 to 0



BC \ A	0	1
00	0	1
01	0	1
11	1	1
10	0	0



14

# Hazards in Combinational Circuits

## Static 0-Hazard
 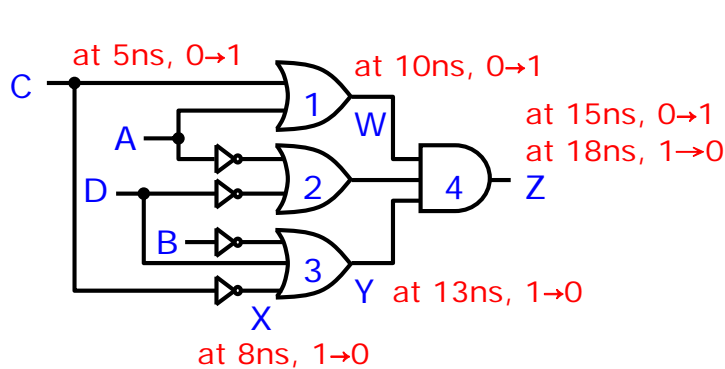
### Example

- Letting  $A=0$ ,  $B=1$ ,  $D=0$ , and  $C$  from 0 to 1 results in a static 0-hazard ( $Z = C \cdot C'$  with delayed inversion)




(assume 3ns delay for inverters and 5ns for AND/OR gates)

15


# Hazards in Combinational Circuits

## Static 0-Hazard

### Example (cont'd)

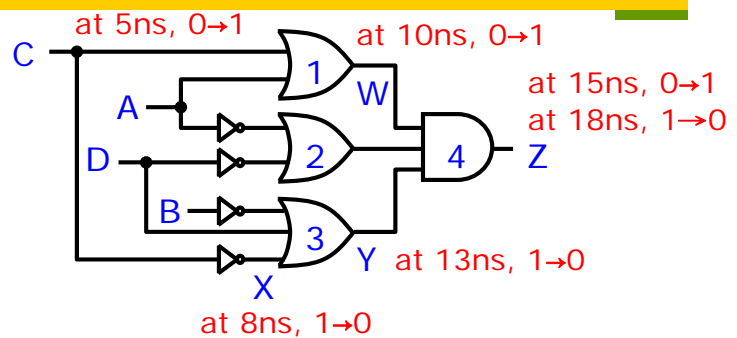

### Timing Diagram

 

16



# Hazards in Combinational Circuits

## Static 0-Hazard

Example (cont'd)

- Eliminate the 0-hazards by adding 3 additional loops

$$Z = (A+C)(A'+D')(B'+C'+D)(C+D')(A+B'+D)(A'+B'+C')$$

		AB			
		00	01	11	10
CD	00	0	0		
	01	0	0	0	0
	11			0	0
	10		0	0	

17

# Hazards in Combinational Circuits

## Hazard-Free Circuit Design

- Procedure for the design of circuits free of static and dynamic hazards
  1. Find an SOP expression  $F^t$  for the output in which every pair of adjacent 1's is covered by a 1-term. (The sum of all prime implicants will always satisfy this condition.) A two-level AND-OR circuit based on this  $F^t$  will be free of 1-, 0-, and dynamic hazards
    - Alternatively can start with a POS expression in which every pair of adjacent 0's is covered by a 0-term, and follow the dual procedure to design a hazard-free two-level OR-AND circuit
  2. If a different form of the circuit is desired, manipulate  $F^t$  to the desired form by simple factoring, DeMorgan's laws, etc. Treat each  $x_i$  and  $x_i'$  as independent variables to prevent introduction of hazards

18

# Hazards in Combinational Circuits

- Under what condition can static 0-hazard (1-hazard) appear in 2-level AND-OR (OR-AND) circuits?

19

# Verification of Logic Circuits

- Verification may take 70% of an entire circuit design time!
  - Verification methodologies:
    - Formal verification
      - Mathematical proof of design correctness
    - Informal verification
      - Error identification by **simulation** (focus of textbook)
  - Verification objectives:
    - Functional verification
      - for logical correctness
    - Timing verification
      - for timing correctness
    - **Testing**
      - for quality control of fabricated ICs (focus of textbook)
      - simulation of faulty components in the circuit as an aid to finding tests for the circuit

20

# Simulation and Testing of Logic Circuits

- Logic circuits can be verified by actually building them or by simulating them on computers
  - Simulation is easier, faster, and more economical
  - Computer simulation involves specifying a circuit, specifying its inputs, and observing its outputs

21

# Simulation and Testing of Logic Circuits


## Simulation Procedure

- Simulation procedure for combinational circuits:
  1. Valuations are performed level by level (from inputs to outputs); changes are updated from gate inputs to gate outputs
    - 0,1,X,Z four-valued simulation
      - X: unknown value (different from don't cares!)
      - Z: open circuit or high impedance (hi-Z)
  2. Step 1 is repeated until no more changes. The circuit is then in steady-state condition, and the outputs can be read
  3. Steps 1-2 are repeated every time a circuit input changes

22

# Simulation and Testing of Logic Circuits

## Four-Valued Logic Simulation

 

AND	·	0	1	X	Z
0		0	0	0	0
1		0	1	X	X
X		0	X	X	X
Z		0	X	X	X

OR	+	0	1	X	Z
0		0	1	X	X
1		1	1	1	1
X		X	1	X	X
Z		X	1	X	X

23

# Simulation and Testing of Logic Circuits

## Error Causes

- ❑ Possible causes of wrong outputs for some set of input values, e.g.,
  - In simulation
    - ❑ Incorrect design
    - ❑ Gates connected wrong
    - ❑ Wrong input signals to the circuit
  - In fabricated circuit (built in lab)
    - ❑ Defective gates
    - ❑ Defective connecting wires

24

# Simulation and Testing of Logic Circuits

## Locating Errors

### Example

- Locate the error for the circuit with function  $F = AB(C'D + CD') + A'B'(C + D)$ . Assume it, after built in lab, has an incorrect output equal to 1 when  $A=B=C=D=1$
- By locating errors from the output to inputs, the inconsistency between the inputs and output of gate 3 is identified.
  - Inputs to gate 3 can be connected wrong, gate 3 is defective, or input connections to gate 3 can be defective

