

Switching Circuits & Logic Design

Jie-Hong Roland Jiang
江介宏


Department of Electrical Engineering
National Taiwan University



Fall 2013

1

§11 Latches and Flip-Flops

 

<http://www3.niaid.nih.gov/topics/Malaria/lifecycle.htm>

2

Outline

- Introduction
- Set-reset latch
- Gated D latch
- Edge-triggered D flip-flop
- S-R flip-flop
- J-K flip-flop
- T flip-flop
- Flip-flops with additional inputs
- Summary

3

Introduction

- Combinational circuits
 - Output is a *function* depending on the present input, **but not past inputs**
 - Given an arbitrary input, a combinational circuit produces only one possible output (after certain delay)
 - Not necessarily **acyclic** (without feedback)
- Sequential circuits
 - Output is a *function* depending on the **past sequence of inputs**
 - Must be **cyclic** (with feedback)
 - **Synchronous** sequential circuits
 - With synchronization signals (clocked)
 - **Asynchronous** sequential circuits
 - Without synchronization signals (clockless)


4

Introduction

Combinational circuits (without memory)



Sequential circuits (with memory)

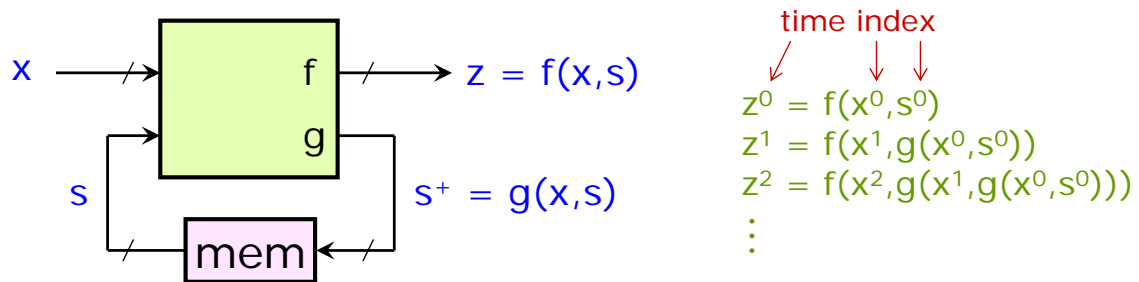

5

Introduction

To construct a **system** (e.g., circuit, neural network, etc.) that “remembers” something about the past history of the inputs

■ Need feedback!

□ Closed loops formed in a circuit connection

6

Introduction

Memory devices

□ Memory devices

- **Latches** and **flip-flops** can assume one of two stable output states, and have one or more inputs that can cause the output state to change

□ Latch

- Have no clock input

□ Flip-flop

- Change output state in response to a clock input, but not a data input

7


Introduction

Feedback


□ Unstable

Oscillator

Feedback

 



Inverter with feedback

 

Oscillation at inverter output

□ Stable


Memory (1-bit)

  


8

Set-Reset Latch


□ S-R latch

 


(a) Stable: $Q=0$

 

 (b) Set: $S: 0 \rightarrow 1 \Rightarrow Q: 0 \rightarrow 1$



(a) Stable: $Q=1$

 


(b) Reset: $R: 0 \rightarrow 1 \Rightarrow Q: 1 \rightarrow 0$

9


Set-Reset Latch

□ Cross-coupled form

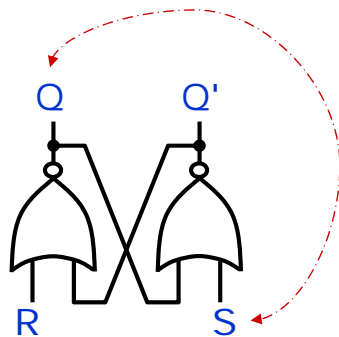

Reset Set

□ S-R latch symbol

 

Reset Set


Q directly above S (different from the cross-coupled form)

10

Set-Reset Latch

Improper S-R latch operation


 
- When $S = R = 1$, the circuit is unstable
- Disallow $S = R = 1$ for S-R latch



11

Set-Reset Latch

Timing diagram

  

ϵ : two NOR-gate delay

The duration of the S (or R) input pulse must normally be no less than ϵ in order for a change in the state of Q to occur

12

Set-Reset Latch Operation

Next-state equation (or characteristic equation):

$$Q^+ = S + R'Q \quad (SR=0, \text{ i.e., } S=R=1 \text{ disallowed})$$

Present (or current) state Q

The state of the Q output of the latch or flip-flop at the time the input signals are applied (or changed)

Next state Q⁺

The state of the Q output after the latch or flip-flop has reacted to these input signals

S(t)	R(t)	Q(t)	Q(t+ε)	
0	0	0	0	} hold
0	0	1	1	
0	1	0	0	} reset
0	1	1	0	
1	0	0	1	} set
1	0	1	1	
1	1	0	-	} prohibited
1	1	1	-	

		S(t)		
		0	1	
R(t)	Q(t)	00	0	1
	01	1	1	1
	11	0	x	x
	10	0	x	x



$$Q(t+\epsilon) = S(t) + R'(t)Q(t)$$

13

Set-Reset Latch Application

Switch debouncing

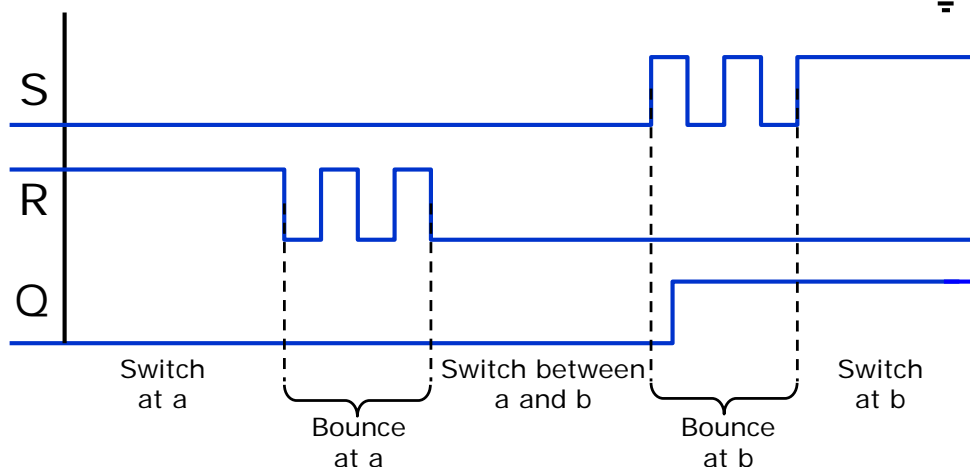 Note: only work for a double throw switch, switching between two contacts (but not for a single throw switch) why?




14

Set-Reset Latch Alternative Implementation

□ \bar{S} - \bar{R} latch

- S-R latch using NAND gates

 



\bar{S}	\bar{R}	Q	Q^+	
1	1	0	0	} hold
1	1	1	1	
1	0	0	0	} reset
1	0	1	0	
0	1	0	1	} set
0	1	1	1	
0	0	0	-	} prohibited
0	0	1	-	

Inputs S and R are **active low**


15

Gated D Latch

Gated D latch

  

Symbol

 

Truth table

G	D	Q	Q^+	
0	0	0	0	} hold ($Q^+ = Q$)
0	0	1	1	
0	1	0	0	
0	1	1	1	
1	0	0	0	} transparent ($Q^+ = D$)
1	0	1	0	
1	1	0	1	
1	1	1	1	

		GD			
Q	G	00	01	11	10
		0	0	0	1
1	1	1	1	1	0


$$Q^+ = G'Q + GD$$

16

Edge-Triggered D Flip-Flop

- Unlike D latch, D flip-flop output changes only in response to the clock, not to a change in D

 
- rising (or positive) edge triggered (0-to-1 transition on clock)
 - falling (or negative) edge triggered (1-to-0 transition on clock)



17

Edge-Triggered D Flip-Flop

 
- Timing diagram
 - (falling-edge trigger)



18


Edge-Triggered D Flip-Flop Implementation

 - D flip-flop (rising-edge trigger)
 - Composed of two gated D latches



If L_1 starts following D before L_2 takes on P , the FF will not function properly


Time analysis

 

19

Edge-Triggered D Flip-Flop Setup Time and Hold Time

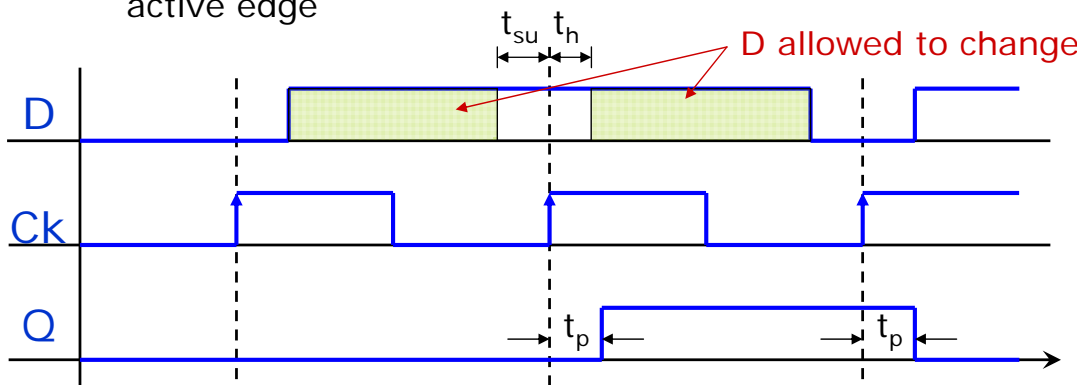- **Propagation delay:** t_p
 - The time between the active edge of the clock and the resulting change in the output
- **Setup time:** t_{su}
 - The amount of time D must be stable before the active edge
- **Hold time:** t_h
 - The amount of time D must hold the same value after the active edge







20

Edge-Triggered D Flip-Flop

Determine Minimum Clock Period

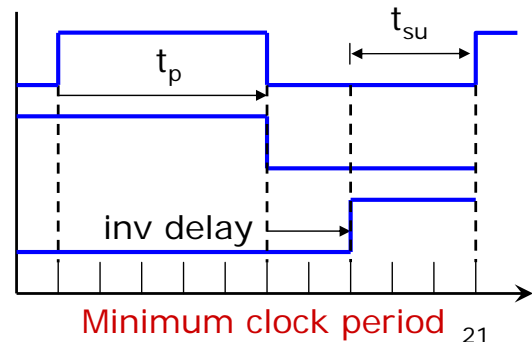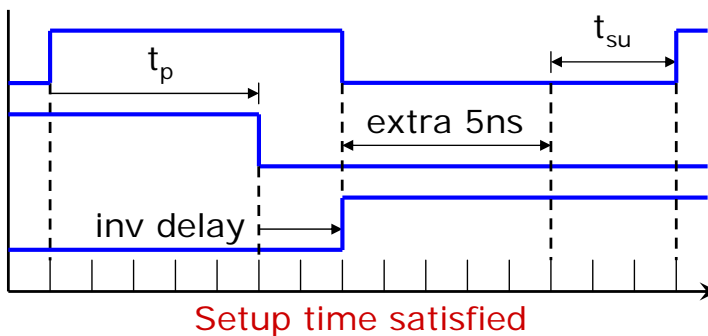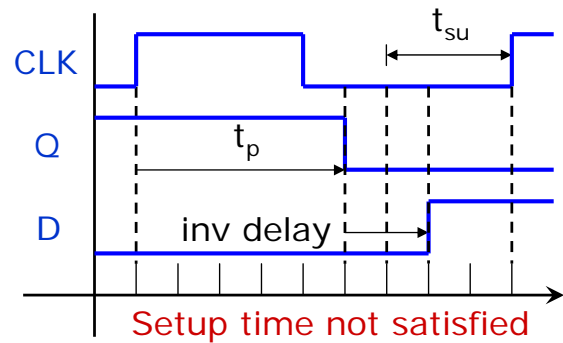 
- Simple flip-flop circuit example (t_p 5ns, t_{su} 3ns, inverter delay 2ns)



S-R Flip-Flop

- Similar to S-R latch but with clock input
 - Same truth table and characteristic equation
 - Interpretation of Q^+ is different
 - Latch: Q^+ is the value of Q after the propagation delay through the latch
 - FF: Q^+ is the value that Q assumes after the active clock edge

S-R flip-flop

 

Q changes at clock edges


Operation summary:

$S=R=0$	no state change
$S=1, R=0$	set Q to 1 (after active Ck edge)
$S=0, R=1$	reset Q to 0 (after active Ck edge)
$S=R=1$	not allowed


S-R Flip-Flop Implementation

□ S-R flip-flop (master-slave flip-flop)

 - Composed of two S-R latches
- Only allow the S and R inputs to change while CLK is high



Time analysis

 

Rising-edge-triggered FF:
Inputs can change while CLK is low

Master-slave FF:
Incorrect if inputs change while CLK is low


23

J-K Flip-Flop



□ J-K flip-flop is an extended version of S-R flip-flop

- $Q^+ = JQ' + K'Q$
- J corresponds to S (Jump to 1); K corresponds to R (Klear to 0)
- State toggled when $J=K=1$

J-K flip-flop

 


J	K	Q	Q ⁺	
0	0	0	0	Hold
0	0	1	1	
0	1	0	0	Clear to 0
0	1	1	0	
1	0	1	1	Jump to 1
1	0	0	1	
1	1	0	1	Toggle
1	1	1	0	

  

24

T Flip-Flop

 


T	Q	Q ⁺	
0	0	0	hold
0	1	1	
1	0	1	toggle
1	1	0	

$$Q^+ = T'Q + TQ' = T \oplus Q$$

$$T = 0 \Rightarrow Q^+ = Q$$

$$T = 1 \Rightarrow Q^+ = Q'$$

 

25


T Flip-Flop Implementation

Conversion of J-K to T

- Connect J and K inputs of a J-K FF together

$$Q^+ = JQ' + K'Q \Rightarrow$$

$$Q^+ = TQ' + T'Q$$

 


Conversion of D to T

- Let $D = Q \oplus T$

$$Q^+ = D \Rightarrow$$

$$Q^+ = Q \oplus T$$

 


26

Flip-Flops with Additional Inputs

Asynchronous Clear and Preset

 - Flip-flops often have additional inputs to set the flip-flops to an initial state independent of the clock



Ck	D	PreN	ClrN	Q ⁺
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)


- ClrN and PreN are **asynchronous** clear and preset inputs (they override the Ck and D inputs)
- ClrN and PreN are **active low** signals
- When ClrN=PreN=1, the FF is in normal operation
- 0 should not be applied to ClrN and PreN simultaneously

27

Flip-Flops with Additional Inputs

Asynchronous Clear and Preset

 - Timing diagram for D flip-flop with asynchronous clear and preset




28


Flip-Flops with Additional Inputs Clock Enable

□ D flip-flop with clock enable (CE)

D-CE symbol

 


Implementation 1: gating the clock

 

Loss of synchronization when
1) clock arrive at some FFs at different times
2) En changes at the wrong time

Implementation 2: no clock gating

 

$$Q^+ = D = Q \cdot (CE)' + D_{in} \cdot (CE)$$

No synchronization problem

29

Summary

- Latch (w/o clock input) vs. flip-flop (w/ clock input)
- Propagation delay, setup time, hold time
- Present (current) state, next state
- Characteristic (next-state) equations
 - $Q^+ = S + R'Q$ ($SR=0$) (S-R latch or flip-flop)
 - $Q^+ = GD + G'Q$ (gated D latch)
 - $Q^+ = D$ (D flip-flop)
 - $Q^+ = D \cdot CE + Q \cdot CE'$ (D-CE flip-flop)
 - $Q^+ = JQ' + K'Q$ (J-K flip-flop)
 - $Q^+ = T \oplus Q = TQ' + T'Q$ (T flip-flop)
- Restrictions
 - For S-R latch/flip-flop, S and R can not be 1 simultaneously
 - For master-slave S-R flip-flop, S and R should not change during the half clock cycle preceding the active edge
 - Setup and hold time constraints

30