

# Switching Circuits & Logic Design

Jie-Hong Roland Jiang  
江介宏


Department of Electrical Engineering  
National Taiwan University



Fall 2013

1

## §12 Registers and Counters

 

Drawing Hands  
M.C. Escher, 1948



<http://img106.imageshack.us/>

2

# Outline

---

- ❑ Registers and register transfers
- ❑ Shift registers
- ❑ Design of binary counters
- ❑ Counters for other sequences
- ❑ Counter design using S-R and J-K flip-flops
- ❑ Derivation of flip-flop input equations

3

# Registers and Register Transfers

---


- ❑ Several D flip-flops may be grouped together with a common clock to form a **register**

4


# Registers and Register Transfers

## 4-Bit D Flip-Flop Register


Using gated clock

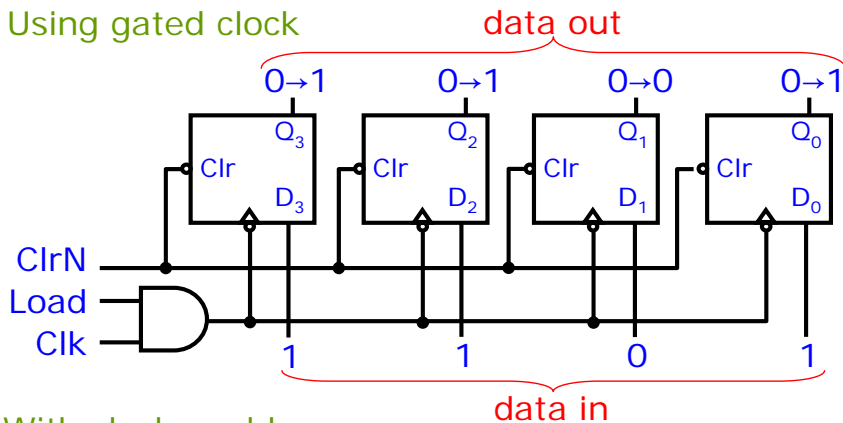

Symbol

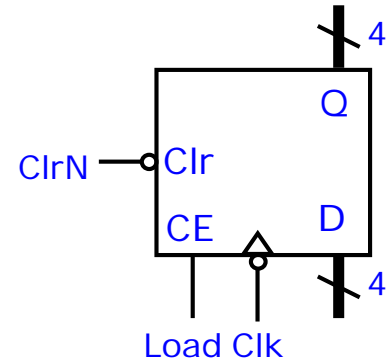


With clock enable

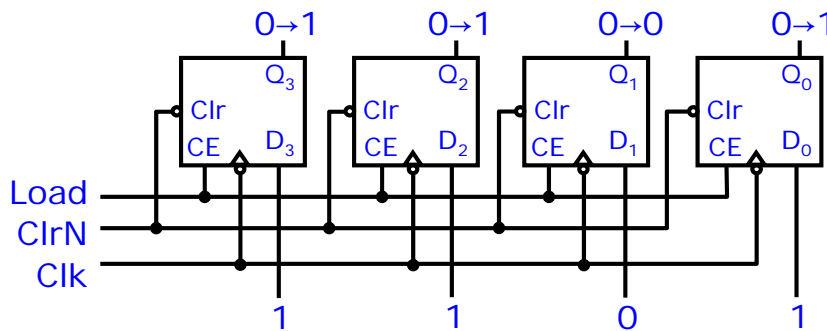

5

# Registers and Register Transfers


## Data Transfer between Registers

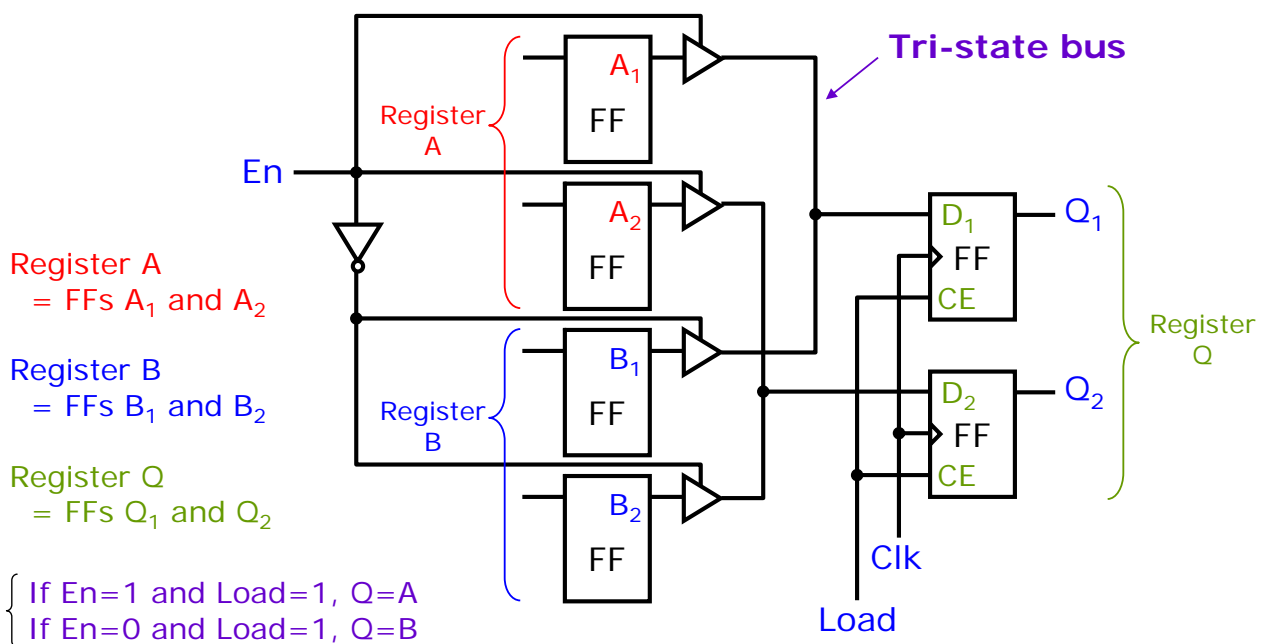

6

# Registers and Register Transfers

## 8-Bit Register with Tri-State Output

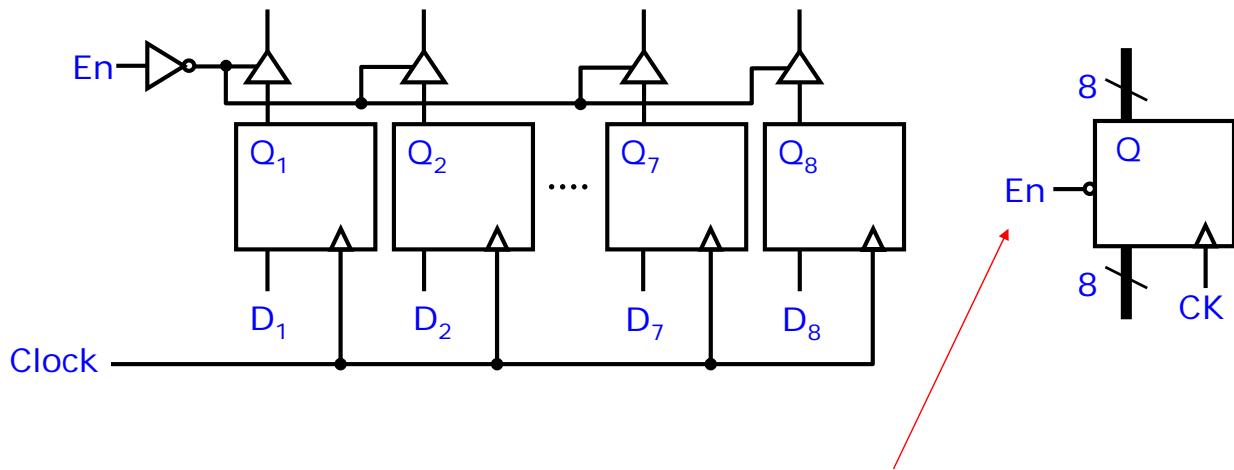


Different from clock enable

7

# Registers and Register Transfers

## Data Transfer Using a Tri-State Bus

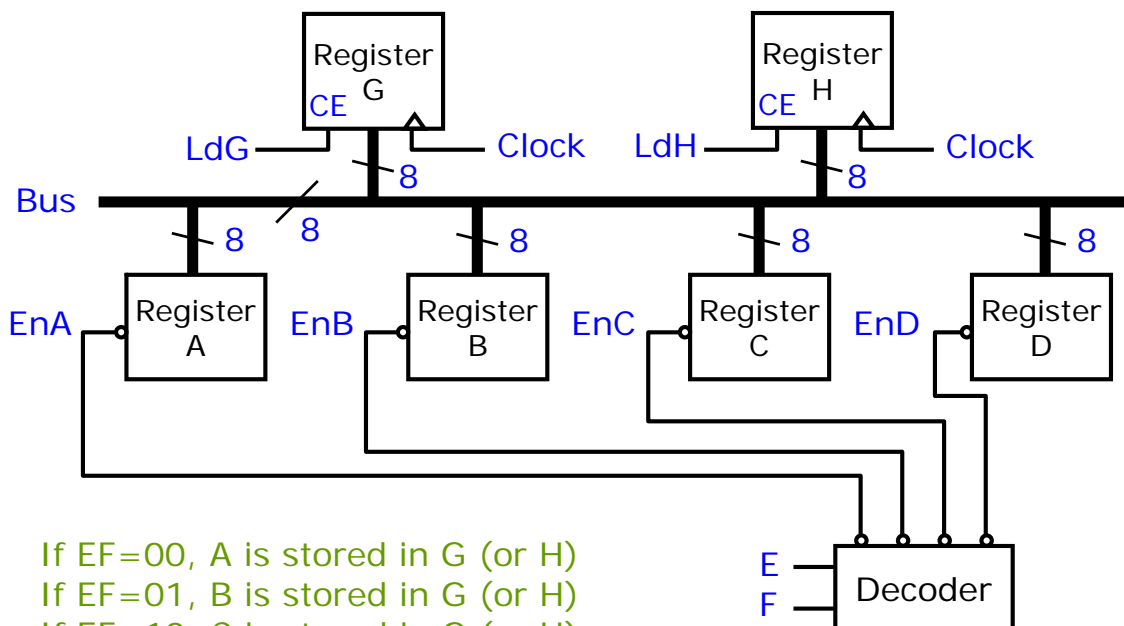

If  $EF=00$ , A is stored in G (or H)  
 If  $EF=01$ , B is stored in G (or H)  
 If  $EF=10$ , C is stored in G (or H)  
 If  $EF=11$ , D is stored in G (or H)


8

# Registers and Register Transfers

## Parallel Adder with Accumulator
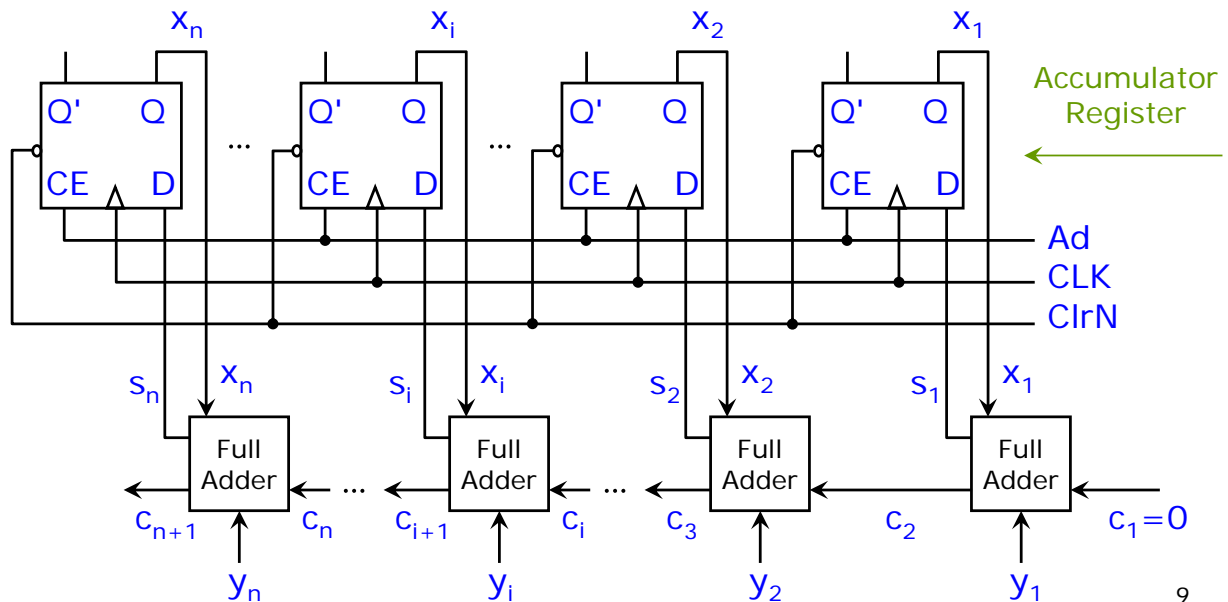
### Accumulator:

A register of FFs that can store one number and add a second number to it, leaving the result stored in it




# Registers and Register Transfers

## Parallel Adder with Accumulator (cont'd)

### Implementation of adder cells (module-based design)


E.g., using Verilog

Adder cell without MUX

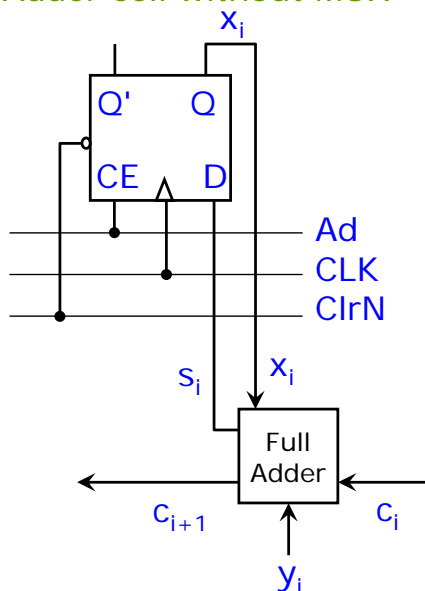

Need to clear before loading X to Y


Adder cell with MUX

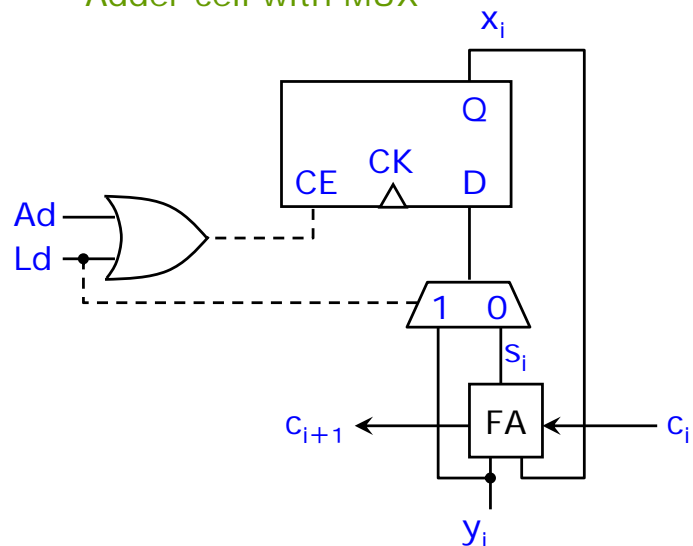

No need to clear before loading X


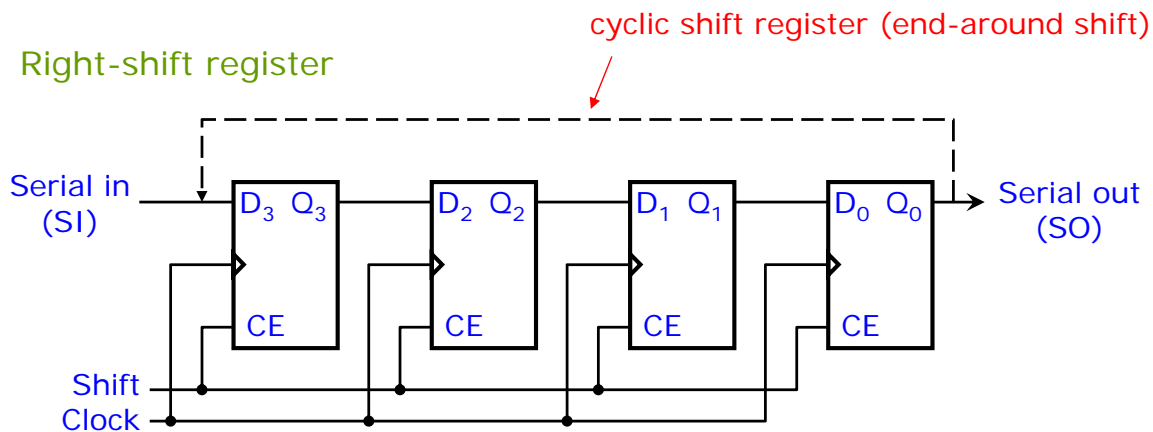
# Shift Registers

- A **shift register** is a register where binary data can be stored and shifted to the left/right when a shift signal is applied



11

# Shift Registers Right-Shift Register

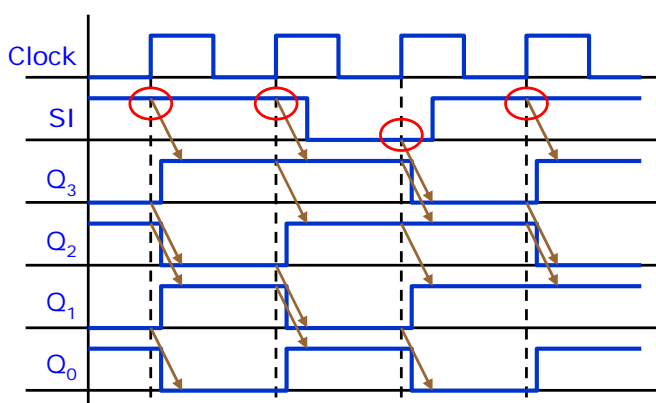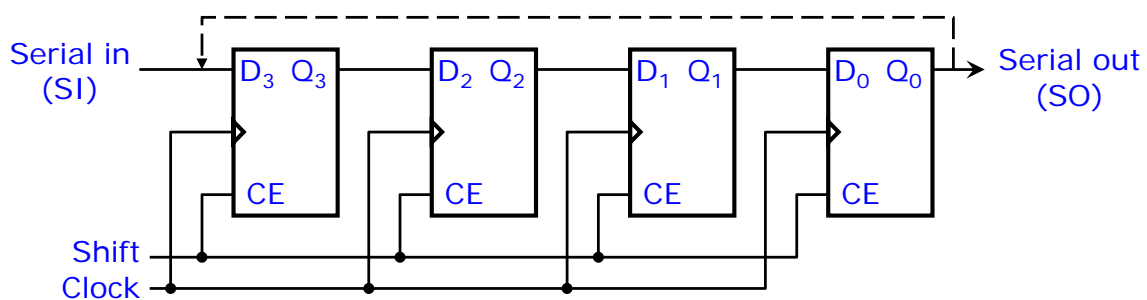

Initial state:  
 $Q_3 Q_2 Q_1 Q_0 = 0101$

SI sequence:  
 1, 1, 0, 1

Register states:  
 0101  
 1010  
 1101  
 0110  
 1011

12

# Shift Registers

## Serial-In, Serial-Out Shift Register

### Serial in

- Data is shifted into the first flip-flop one bit at a time

### Serial out

- Data can only be read out of the last flip-flop one bit at a time

13


# Shift Registers

## 8-Bit Serial-In, Serial-Out Shift Register


Block diagram



Logic diagram

 

Timing diagram

 


14

# Shift Registers

## Parallel-In, Parallel-Out Shift Register

### Block diagram

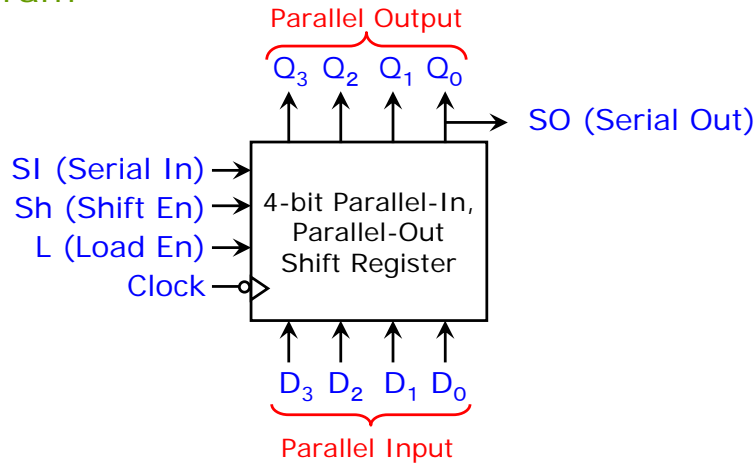


Application: conversion between parallel and serial data

15

# Shift Registers

## Parallel-In, Parallel-Out Shift Register
 
### Logic diagram (implementation using FFs and MUXes)



### Shift register operation

Inputs		Next State	Action
Sh (Shift)	L (Load)	$Q_3^+$ $Q_2^+$ $Q_1^+$ $Q_0^+$	
0	0	$Q_3$ $Q_2$ $Q_1$ $Q_0$	no change
0	1	$D_3$ $D_2$ $D_1$ $D_0$	load
1	X	SI $Q_3$ $Q_2$ $Q_1$	right shift

$$\left\{ \begin{array}{l} Q_3^+ = Sh' \cdot L' \cdot Q_3 + Sh' \cdot L \cdot D_3 + Sh \cdot SI \\ Q_2^+ = Sh' \cdot L' \cdot Q_2 + Sh' \cdot L \cdot D_2 + Sh \cdot Q_3 \\ Q_1^+ = Sh' \cdot L' \cdot Q_1 + Sh' \cdot L \cdot D_1 + Sh \cdot Q_2 \\ Q_0^+ = Sh' \cdot L' \cdot Q_0 + Sh' \cdot L \cdot D_0 + Sh \cdot Q_1 \end{array} \right.$$

16




# Shift Registers

## Parallel-In, Parallel-Out Shift Register
 
### Timing diagram

(assume  $D_3D_2D_1D_0 = 1011$  initially and 0000 afterwards)




17


# Shift Registers
 
## Shift Register with Inverted Feedback

- A circuit that cycles through a fixed sequence of states is called a **counter**
- A shift register with inverted feedback is often called a **Johnson counter**



Flip-flop connections

 

State graph

18

# Design of Binary Counters

- We focus on the synchronous counter, where flip-flops are synchronized by a common clock pulse

State table

Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

19

# Design of Binary Counters D Flip-Flop Implementation

- State table

Present State			Next State			Flip-Flop Inputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0


FF inputs are next-state functions in terms of A,B,C

20


# Design of Binary Counters

## D Flip-Flop Implementation

### Karnaugh maps for D flip-flops

 

### Binary counter with D flip-flops

 

21

# Design of Binary Counters

## T Flip-Flop Implementation

### State table

Present State			Next State			Flip-Flop Inputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

FF inputs are next-state functions in terms of A,B,C

22



# Design of Binary Counters

## Up-Down Counter

- The up-down counter can be implemented using D FFs and gates through the logic equations

$$D_A = A^+ = A \oplus (U+D)$$

$$D_B = B^+ = B \oplus (UA+DA')$$

$$D_C = C^+ = C \oplus (UBA+DB'A')$$

- When  $U=1, D=0$ , they reduce to binary up counter

- When  $U=0, D=1$ , they reduce to

$$D_A = A^+ = A \oplus 1 = A'$$

$$D_B = B^+ = B \oplus A'$$

$$D_C = C^+ = C \oplus B'A'$$

25



# Design of Binary Counters

## Up-Down Counter

$$D_A = A^+ = A \oplus (U+D)$$

$$D_B = B^+ = B \oplus (UA+DA')$$


$$D_C = C^+ = C \oplus (UBA+DB'A')$$

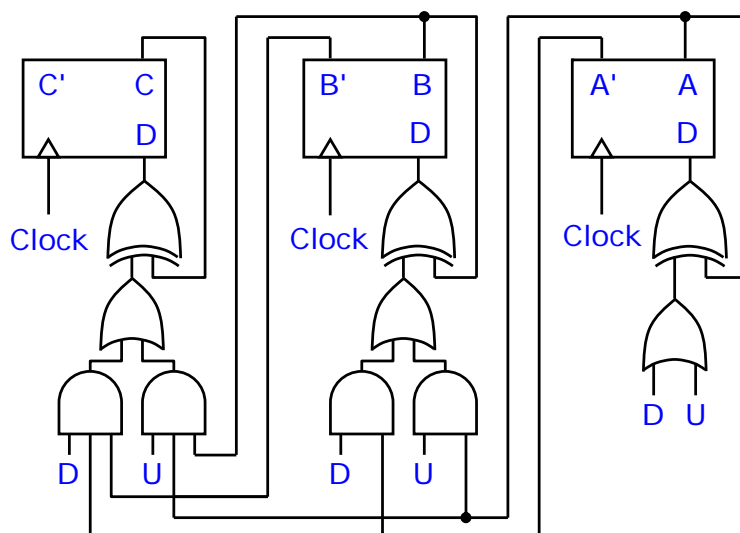 

26

# Design of Binary Counters

## Loadable Counter with Count Enable

 

ClrN	Ld	Ct	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	X	X	0	0	0
1	1	X	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub> (load)
1	0	0	C	B	A (no change)
1	0	1	Present state + 1		

$$A^+ = D_A = (Ld' \cdot A + Ld \cdot D_{Ain}) \oplus Ld' \cdot Ct$$

$$B^+ = D_B = (Ld' \cdot B + Ld \cdot D_{Bin}) \oplus Ld' \cdot Ct \cdot A$$

$$C^+ = D_C = (Ld' \cdot C + Ld \cdot D_{Cin}) \oplus Ld' \cdot Ct \cdot B \cdot A$$

Note that ClrN does not appear in these equations. Why not?

27


# Design of Binary Counters

## Loadable Counter with Count Enable

$$A^+ = D_A = (Ld' \cdot A + Ld \cdot D_{Ain}) \oplus Ld' \cdot Ct$$

$$B^+ = D_B = (Ld' \cdot B + Ld \cdot D_{Bin}) \oplus Ld' \cdot Ct \cdot A$$

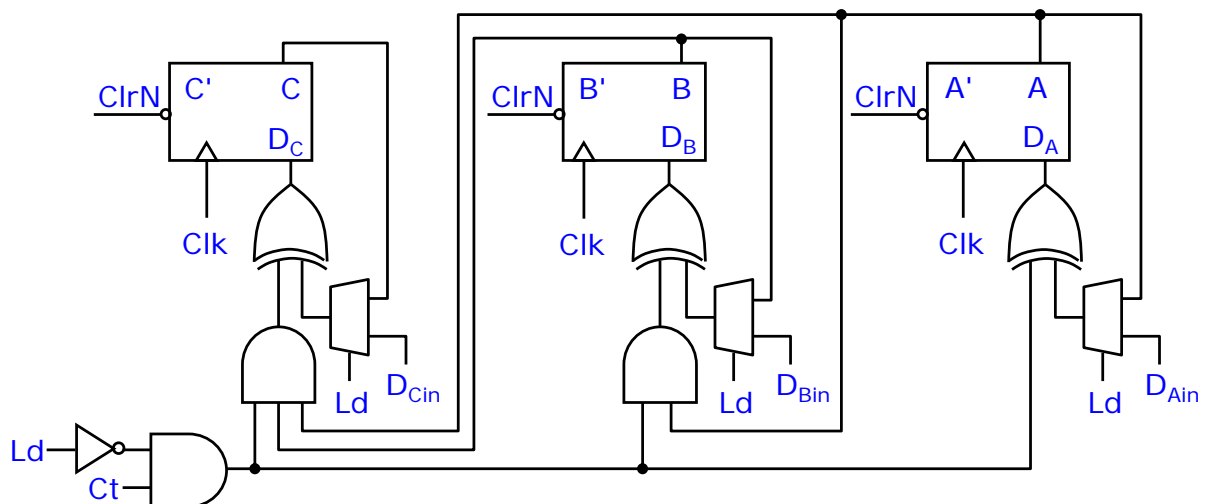
$$C^+ = D_C = (Ld' \cdot C + Ld \cdot D_{Cin}) \oplus Ld' \cdot Ct \cdot B \cdot A$$



28

# Counters for Other Sequences

State graph

 

State table

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

29

# Counters for Other Sequences Counter Design Using T Flip-Flops

State table

T FF input

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	1	0	0	1	0	0
0	0	1	-	-	-	-	-	-
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	-	-	-	-	-
1	1	0	-	-	-	-	-	-
1	1	1	0	1	0	1	0	1

QQ <sup>+</sup>	T
00	0
01	1
10	1
11	0


$$T = Q^+ \oplus Q$$

30

# Counters for Other Sequences


## Counter Design Using T Flip-Flops

### Next-state maps

 

$QQ^+$	T
00	0
01	1
10	1
11	0

### Derivation of T inputs

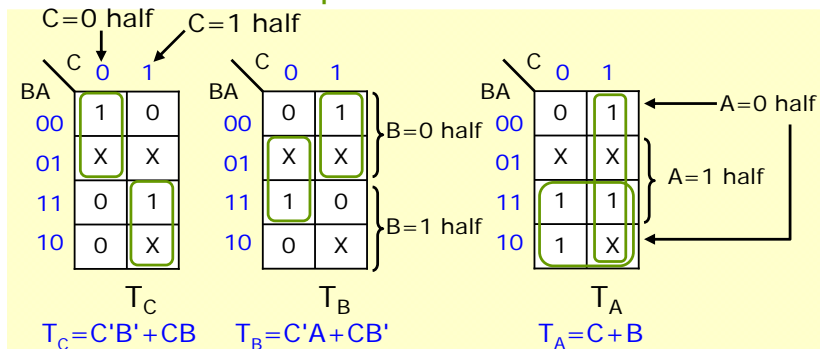

$$T = Q^+ \oplus Q$$

$$T_C = C'B' + CB$$

$$T_B = C'A + CB'$$

$$T_A = C + B$$

31

# Counters for Other Sequences

## Counter Design Using T Flip-Flops

### □ For T flip-flop implementation

- If the  $Q^+$  map has a don't care in some square, the  $T_Q$  map will have a don't care in the corresponding square
- Divide the  $Q^+$  map into two halves corresponding to  $Q=0$  and  $Q=1$ , and transform each half of the map
  - Whenever  $Q=0$ ,  $T=Q^+$ 
    - Copy the half for which  $Q=0$
  - Whenever  $Q=1$ ,  $T=(Q^+)'$ 
    - Complement the half for which  $Q=1$


32



# Counters for Other Sequences

## Counter Design Using T Flip-Flops

### □ T flip-flop realization

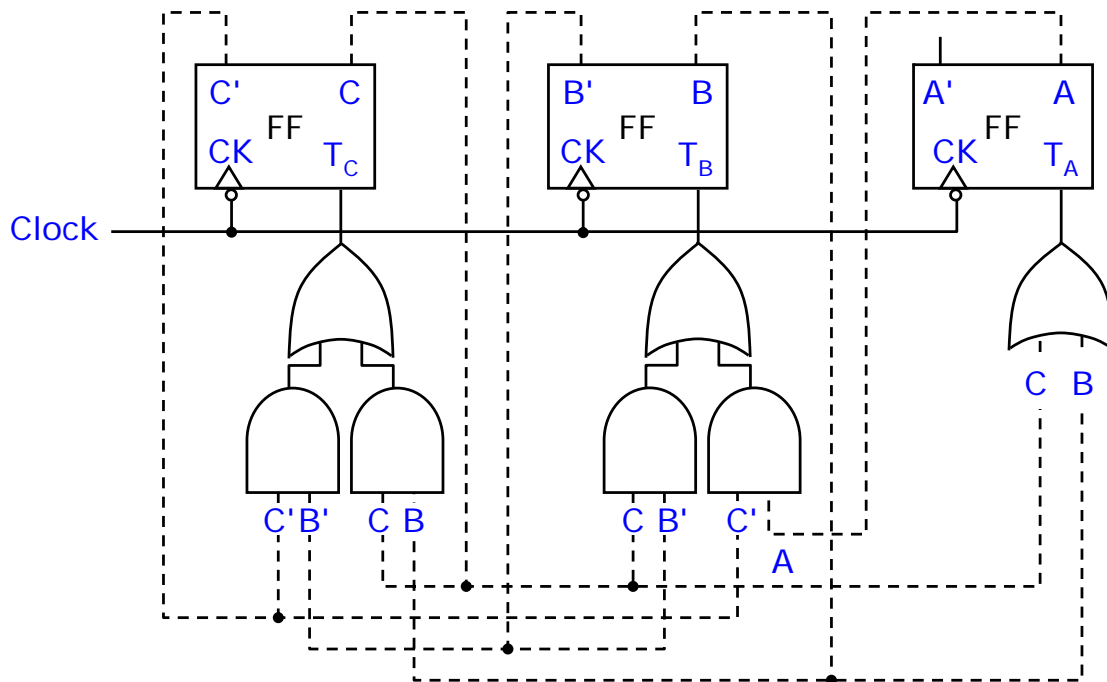


33

# Counters for Other Sequences

## Counter Design Using T Flip-Flops

### □ Timing diagram

#### ■ Negative-edge triggered

 


34

# Counters for Other Sequences
 
## Counter Design Using T Flip-Flops

- In the process of completing the circuit design, the transitions of the original don't care states will be specified
  - Don't care states need to be checked to make sure they eventually lead into the main counting sequence unless a power-up reset is provided
    - When the power in a circuit is first turned on, the initial states of the flip-flops may be unpredictable (can be in an arbitrary state)



What are the transitions for states 001, 101, 110 by the realization in Slide 33?

$$T_C = C'B' + CB$$

$$T_B = C'A + CB'$$

$$T_A = C + B$$


35

# Counters for Other Sequences

## Counter Design Using T Flip-Flops
 
### □ Example (cont'd)

If FFs are powered up at (CBA)=001, then  $T_C = T_B = 1$  and  $T_A = 0$  leads to next state 111



$$T_C = C'B' + CB$$

$$T_B = C'A + CB'$$

$$T_A = C + B$$


36

# Counters for Other Sequences


## Counter Design Using T Flip-Flops
 
### Example

- Without power-up reset, the following Johnson counter may be incorrect when powered up at states 010 and 101



Flip-flop connections

 


State graph

37

# Counters for Other Sequences

## Counter Design Using D Flip-Flops

State graph

 

State table

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	D <sub>C</sub>	D <sub>B</sub>	D <sub>A</sub>
0	0	0	1	0	0	1	0	0
0	0	1	-	-	-	-	-	-
0	1	0	0	1	1	0	1	1
0	1	1	0	0	0	0	0	0
1	0	0	1	1	1	1	1	1
1	0	1	-	-	-	-	-	-
1	1	0	-	-	-	-	-	-
1	1	1	0	1	0	0	1	0

D FF input

D	Q <sup>+</sup>
0	0
1	1

$$Q^+ = D$$

Not copy this!

$$D_C = C^+ = B'$$

$$D_B = B^+ = C + BA'$$

$$D_A = A^+ = CA' + BA' = A'(C+B)$$

38


# Counters for Other Sequences

## Counter Design Using D Flip-Flops

$$D_C = C^+ = B'$$

$$D_B = B^+ = C + BA'$$

$$D_A = A^+ = CA' + BA' = A'(C + B)$$

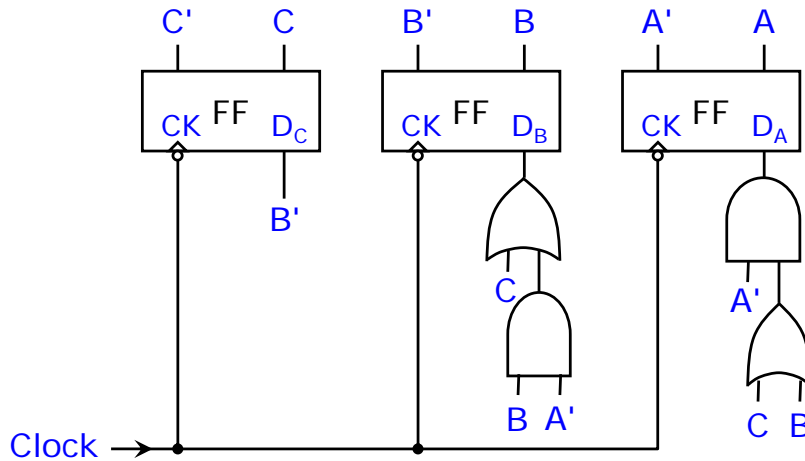

39

# Counter Design Using S-R and J-K FFs

## Counter Design Using S-R Flip-Flops

### □ S-R flip-flop inputs

S	R	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

} inputs not allowed

Q	Q <sup>+</sup>	S	R
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0
1	1	1	0


Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

40

# Counter Design Using S-R and J-K FFs

## Counter Design Using S-R Flip-Flops

State graph

 

C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	C		B		A	
						S <sub>C</sub>	R <sub>C</sub>	S <sub>B</sub>	R <sub>B</sub>	S <sub>A</sub>	R <sub>A</sub>
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	0	X	0	1	0	1
1	0	0	1	1	1	X	0	1	0	1	0
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	0	0	1


Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

41

# Counter Design Using S-R and J-K FFs

## Counter Design Using S-R Flip-Flops

Next-state maps

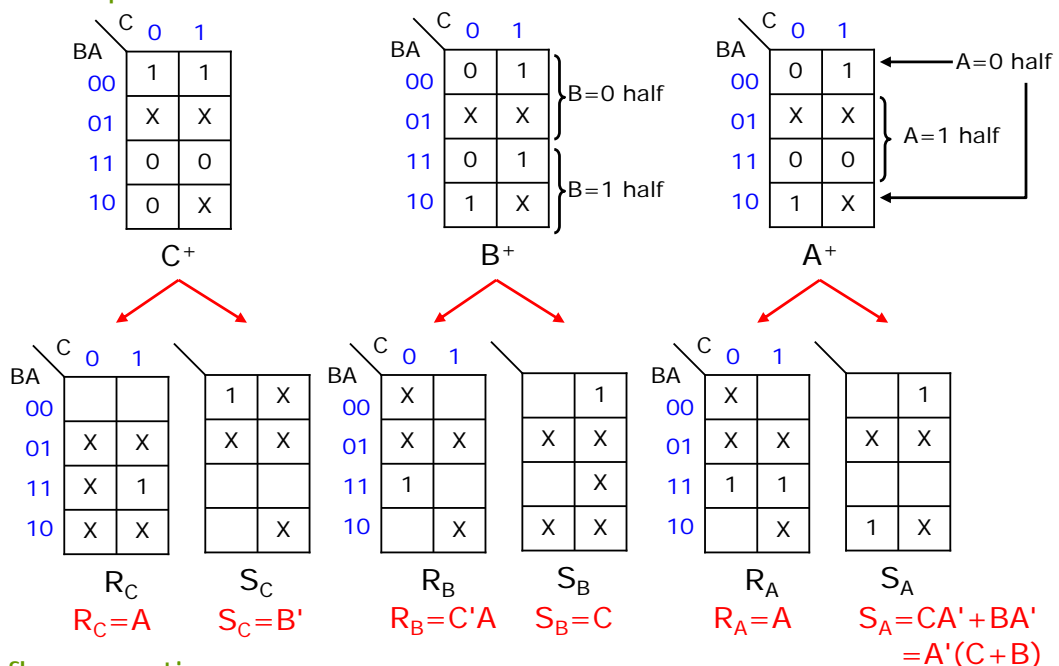


S-R flip-flop equations

42

# Counter Design Using S-R and J-K FFs

## Counter Design Using S-R Flip-Flops

### □ S-R flip-flop realization

 

(feedback lines omitted)

43

# Counter Design Using S-R and J-K FFs

## Counter Design Using J-K Flip-Flops

### □ J-K flip-flop inputs

J	K	Q	Q <sup>+</sup>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

➔

Q	Q <sup>+</sup>	J	K
0	0	{ 0 0	
0	0	{ 0 1	
-----			
0	1	{ 1 0	
0	1	{ 1 1	
-----			
1	0	{ 0 1	
1	0	{ 1 1	
-----			
1	1	{ 0 0	
1	1	{ 1 0	

➔


Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

44

# Counter Design Using S-R and J-K FFs

## Counter Design Using J-K Flip-Flops

State graph

 


			C		B		A				
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	J <sub>C</sub>	K <sub>C</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	-	-	-	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	-	-	-	X	X	X	X	X	X
1	1	0	-	-	-	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1

Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

# Counter Design Using S-R and J-K FFs

## Counter Design Using J-K Flip-Flops

Next-state maps

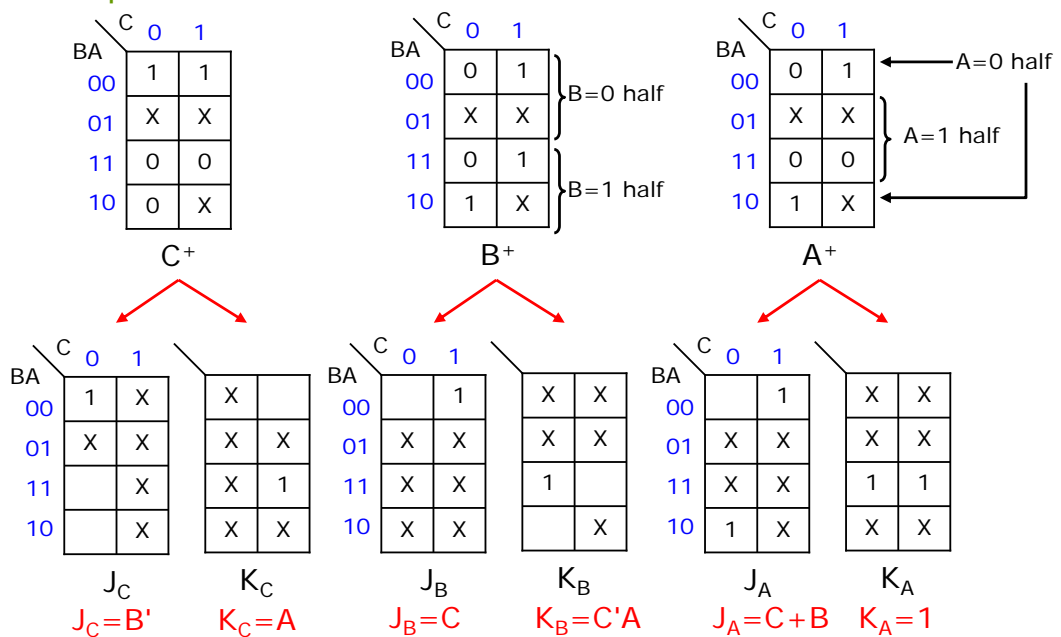


J-K flip-flop equations

# Counter Design Using S-R and J-K FFs

## Counter Design Using J-K Flip-Flops

### □ J-K flip-flop realization

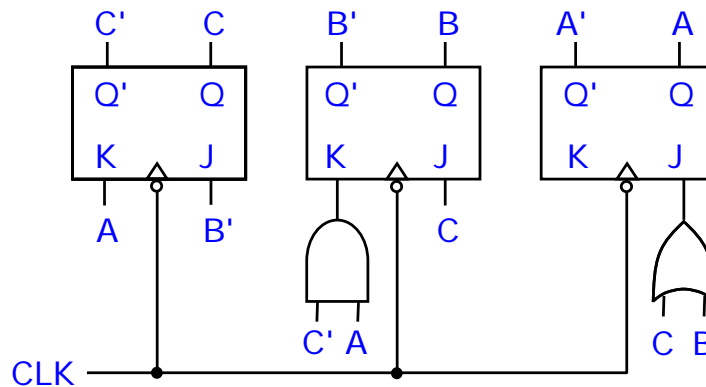

(feedback lines omitted)

47

## Derivation of Flip-Flop Input Equations

### □ Determination of flip-flop input equations from next-state equations using Karnaugh maps

Type of Flip-Flop	Input	Q = 0				Rules for Forming Input Map From Next-State Map*	
		Q <sup>+</sup> =0	Q <sup>+</sup> =1	Q <sup>+</sup> =0	Q <sup>+</sup> =1	Q=0 Half of Map	Q=1 Half of Map
Delay	D	0	1	0	1	No change	No change
Trigger	T	0	1	1	0	No change	Complement
Set-Reset	S	0	1	0	X	No change	Replace 1's with X's**
	R	X	0	1	0	Replace 0's with X's**	Complement
J-K	J	0	1	X	X	No change	Fill in with X's
	K	X	X	1	0	Fill in with X's	Complement

\*Always copy X's from the next-state map onto the input maps first

\*\*Fill in the remaining squares with 0's

48



# Derivation of Flip-Flop Input Equations

## Flip-Flop Input Tables

Q	Q <sup>+</sup>	D
0	0	0
0	1	1
1	0	0
1	1	1

Q	Q <sup>+</sup>	T
0	0	0
0	1	1
1	0	1
1	1	0

Q	Q <sup>+</sup>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Q	Q <sup>+</sup>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Realization using J-K flip flops usually yields lower cost implementation

49

# Derivation of Flip-Flop Input Equations

## Example

BA \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

Q<sup>+</sup>

Next-state map

BA \ Q	0	1
00	0	1
01	1	0
11	0	0
10	1	X

$$D = Q'A'B + QB' + AB'$$

D input map

BA \ Q	0	1
00	0	0
01	1	1
11	0	1
10	1	X

$$T = A'B + AB' + QB$$

T input map

BA \ Q	0	1
00	0	X
01	1	0
11	0	0
10	1	X

$$S = AB' + Q'A'B$$

BA \ Q	0	1
00	X	0
01	0	1
11	X	1
10	0	X

$$R = QB$$

S-R input maps

BA \ Q	0	1
00	0	X
01	1	X
11	0	X
10	1	X

$$J = A'B + AB'$$

BA \ Q	0	1
00	X	0
01	X	1
11	X	1
10	X	X

$$K = B$$

J-K input maps

50

# Derivation of Flip-Flop Input Equations Example (1/3)

- Derivation of  $Q_1$  (T flip-flop) input equation using 4-variable maps

		$Q_1A$			
		BC	00	01	11
00	00	0	1	0	1
01	01	X	1	1	0
11	11	1	X	X	1
10	10	0	0	0	X

$Q_1=0$   
half

$Q_1=1$   
half

$Q_1^+$

		$Q_1A$			
		BC	00	01	11
00	00	0	1	1	0
01	01	X	1	0	1
11	11	1	X	X	0
10	10	0	0	1	X

$T_1$

51

# Derivation of Flip-Flop Input Equations Example (2/3)

- Derivation of  $Q_2$  (S-R flip-flop) input equations using 4-variable maps

		AB			
		CQ <sub>2</sub>	00	01	11
$Q_2=0$ half	00	1	X	1	0
$Q_2=1$ half	01	0	0	X	1
	11	1	0	X	1
	10	X	0	0	1

$Q_2^+$

		AB			
		CQ <sub>2</sub>	00	01	11
00	00	0	X	0	X
01	01	1	1	X	0
11	11	0	1	X	0
10	10	X	X	X	0

$R_2$

		AB			
		CQ <sub>2</sub>	00	01	11
00	00	1	X	1	0
01	01	0	0	X	X
11	11	X	0	X	X
10	10	X	0	0	1

$S_2$

52

# Derivation of Flip-Flop Input Equations

## Example (3/3)

- Derivation of  $Q_3$  (J-K flip-flop) input equations using 4-variable maps

		AB			
	$Q_3C$	00	01	11	10
$Q_3=0$ half	00	0	0	1	X
	01	0	1	X	1
$Q_3=1$ half	11	X	X	0	0
	10	1	1	1	0

$Q_3^+$

		AB			
	$Q_3C$	00	01	11	10
00	0	0	1	X	X
01	0	1	X	1	X
11	X	X	X	X	X
10	X	X	X	X	X

$J_3 = A+BC$

		AB			
	$Q_3C$	00	01	11	10
00	X	X	X	X	X
01	X	X	X	X	X
11	X	X	1	1	X
10	0	0	0	0	1

$K_3 = C+AB'$

53

# Derivation of Flip-Flop Input Equations

## Summary

- To implement a counter of  $N$  states, we need at least  $\log_2 N$  flip-flops
- Derive input equations depending on the target implementation using D, T, SR, or JK flip-flops
- Pay attention to don't care states for power-up conditions. Sometimes reset may be needed

54