

Switching Circuits & Logic Design

Jie-Hong Roland Jiang
江介宏


Department of Electrical Engineering
National Taiwan University



Fall 2013

1

 §13 Analysis of Clocked Sequential Circuits



Magic Mirror
M.C. Escher, 1946

2

Outline

- A sequential parity checker
- Analysis by signal tracing and timing charts
- State tables and graphs
- General models for sequential circuits

3

A Sequential Parity Checker

- When binary data is transmitted or stored, an extra bit (call a **parity bit**) is frequently added for the purposes of error detection
 - Odd (even) parity: the total number of 1's in the block, including the parity bit, is odd (even)

Example (8-bit words with odd parity)

7 data bits parity bit

0000000	1
0000001	0
0110110	1
1010101	1
0111000	0

8-bit word

1010000 0

↑
error occurred



4

A Sequential Parity Checker

□ A parity checker for serial data

- $Z = 1 \Leftrightarrow$ the total number of 1 inputs received is odd (i.e., input parity is odd)
- $Z = 0$ initially


Block diagram

 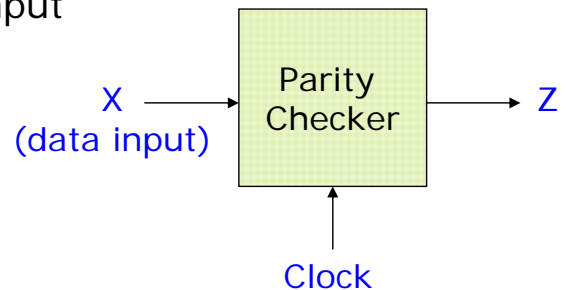

5

A Sequential Parity Checker


State graph

 

State table

Present State	Next State		Present Output	Q	Q ⁺		T		Z
	X=0	X=1			X=0	X=1	X=0	X=1	
S ₀	S ₀	S ₁	0	0	0	1	0	1	0
S ₁	S ₁	S ₀	1	1	1	0	0	1	1


Logic circuit

 

6

Signal Tracing and Timing Charts

 - Find the output sequence resulting from a given input sequence by tracing 0 and 1 signals through a circuit
 - Assume an initial state of the flip-flops
 - Given a current input at the present state, determine the circuit outputs and next state (flip-flop inputs)
 - Update the present state to the next state, and repeat 2




A sequential circuit with n FFs has 2^n states

7

Signal Tracing and Timing Charts


 
- There are two types of clocked sequential circuits
 - Moore machine**
 - Output depends only on the **present state**
 - Output function $\lambda(S)$
 - Mealy machine**
 - Output depends on both the **present state** and the **input**
 - Output function $\lambda(S,X)$



8

Signal Tracing and Timing Charts

A Moore Sequential Circuit Example

  

Assume $A=B=0$ initially

$X = 0 \ 1 \ 1 \ 0 \ 1$
 $A = 0 \ 1 \ 0 \ 1 \ 0 \ 1$
 $B = 0 \ 0 \ 1 \ 1 \ 1 \ 1$
 $Z = (0) \ 1 \ 1 \ 0 \ 1 \ 0$

Output is a function of states only
 \Rightarrow a Moore circuit

9

Signal Tracing and Timing Charts


Moore Sequential Circuit

- For a Moore circuit, the output which results from application of a given input does not appear until after the active clock edge
 - The output sequence is **displaced** in time with respect to the input sequence

10

Signal Tracing and Timing Charts

A Mealy Sequential Circuit Example

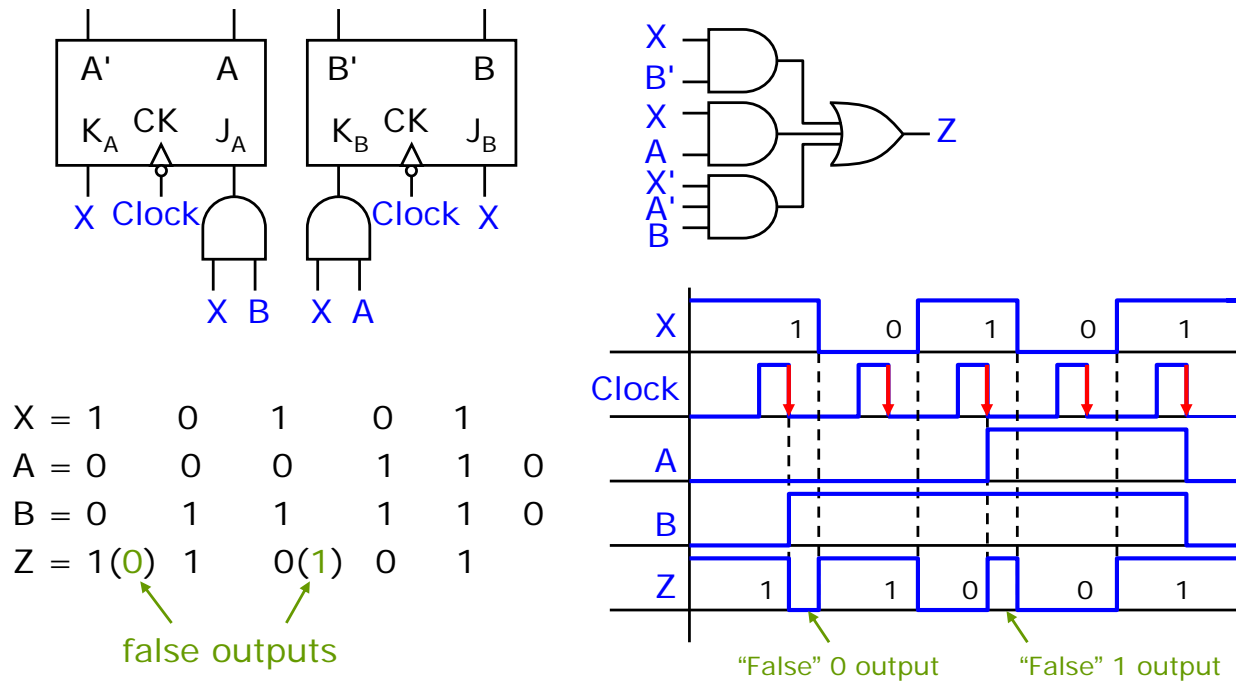


Output is a function of both states and inputs \Rightarrow a Mealy circuit 11

Signal Tracing and Timing Charts

Mealy Sequential Circuit

- For a Mealy circuit, the output may temporarily assume an incorrect value (called a **false output, glitch, spike**)
 - The false output occurs after the circuit has changed state and before the input is changed; however, the correct output must appear before the active clock edge
 - No false output can appear in a Moore circuit
 - The output sequence is **not displaced** in time with respect to the input sequence
 - If the output of the circuit is fed into a second sequential circuit which uses the same clock, the false outputs will not cause any problem because the inputs to the second circuit can cause a change of state only at the active clock edge

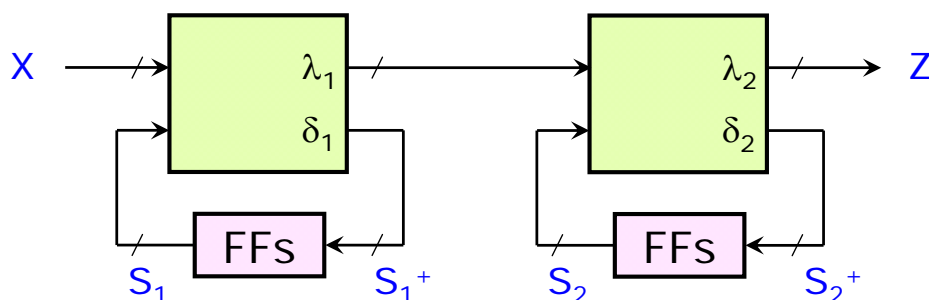

State Tables and Graphs


□ Procedure to construct the state table

1. Determine the FF input equations and output equations from the circuit
2. Derive the next-state equation for each FF from its input equations
 - D FF $Q^+ = D$
 - D-CE FF $Q^+ = D \cdot CE + Q \cdot CE'$
 - T FF $Q^+ = T \oplus Q$
 - S-R FF $Q^+ = S + R'Q$
 - J-K FF $Q^+ = JQ' + K'Q$
3. Plot a next-state map for each FF
4. Combine these maps to form the state table (or called transition table)

13

State Tables and Graphs

A Moore Sequential Circuit Example

 

Step 1

$$D_A = X \oplus B' \quad D_B = X + A \quad Z = A \oplus B$$

Step 2

$$A^+ = X \oplus B' \quad B^+ = X + A$$

Step 3

AB	A ⁺		AB	B ⁺	
	X=0	X=1		X=0	X=1
00	1	0	00	0	1
01	0	1	01	0	1
11	0	1	11	1	1
10	1	0	10	1	1

Step 4

AB	A ⁺ B ⁺		Z
	X=0	X=1	
00	10	01	0
01	00	11	1
11	01	11	0
10	11	01	1

14

State Tables and Graphs

A Moore Sequential Circuit Example


State tables

AB	A+B+		Z	Present State	Next State		Present Output (Z)
	X=0	X=1			X=0	X=1	
00	10	01	0	S ₀	S ₃	S ₁	0
01	00	11	1	S ₁	S ₀	S ₂	1
11	01	11	0	S ₂	S ₁	S ₂	0
10	11	01	1	S ₃	S ₂	S ₁	1

Symbolic representation




State graph

 

15

State Tables and Graphs

A Mealy Sequential Circuit Example

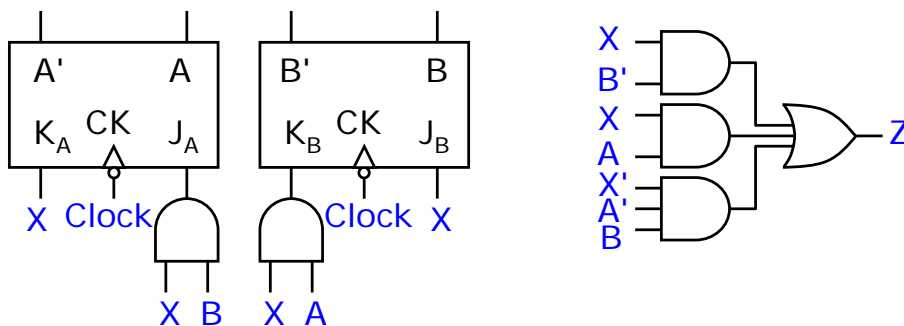

Steps 1,2

$$A^+ = J_A A' + K'_A A = XBA' + X'A$$

$$B^+ = J_B B' + K'_B B = XB' + (AX)'B = XB' + X'B + A'B$$

$$Z = X'A'B + XB' + XA$$

16

State Tables and Graphs

A Mealy Sequential Circuit Example

Step 3

		X				X				X	
	AB	0	1		AB	0	1		AB	0	1
	00	0	0		00	0	1		00	0	1
	01	0	1		01	1	1		01	1	0
	11	1	0		11	1	0		11	0	1
	10	1	0		10	0	1		10	0	1
		A ⁺			B ⁺				Z		

Step 4

		A+B ⁺		Z	
	AB	X=0	X=1	X=0	X=1
	00	00	01	0	1
	01	01	11	1	0
	11	11	00	0	1
	10	10	01	0	1

17

State Tables and Graphs

A Mealy Sequential Circuit Example


State tables

		A+B ⁺		Z		Present State	Next State		Present Output	
	AB	X=0	X=1	X=0	X=1		X=0	X=1	X=0	X=1
	00	00	01	0	1	S ₀	S ₀	S ₁	0	1
	01	01	11	1	0	S ₁	S ₁	S ₂	1	0
	11	11	00	0	1	S ₂	S ₂	S ₀	0	1
	10	10	01	0	1	S ₃	S ₃	S ₁	0	1

Symbolic representation



State graph

 


18

State Tables and Graphs


A Serial Adder Example

Serial adder with D FF

 


Truth table

x_i	y_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

State graph

 

19


State Tables and Graphs

Example w/ Multiple Inputs & Outputs

State table

Present State	Next State				Present Output ($Z_1 Z_2$)			
	$X_1 X_2 = 00$	01	10	11	$X_1 X_2 = 00$	01	10	11
S_0	S_3	S_2	S_1	S_0	00	10	11	01
S_1	S_0	S_1	S_2	S_3	10	10	11	11
S_2	S_3	S_0	S_1	S_1	00	10	11	01
S_3	S_2	S_2	S_1	S_0	00	00	01	01

State graph

 


Given an initial state and an input sequence, we know the corresponding **state trace** and **output sequence**

20

State Tables and Graphs

Timing Charts

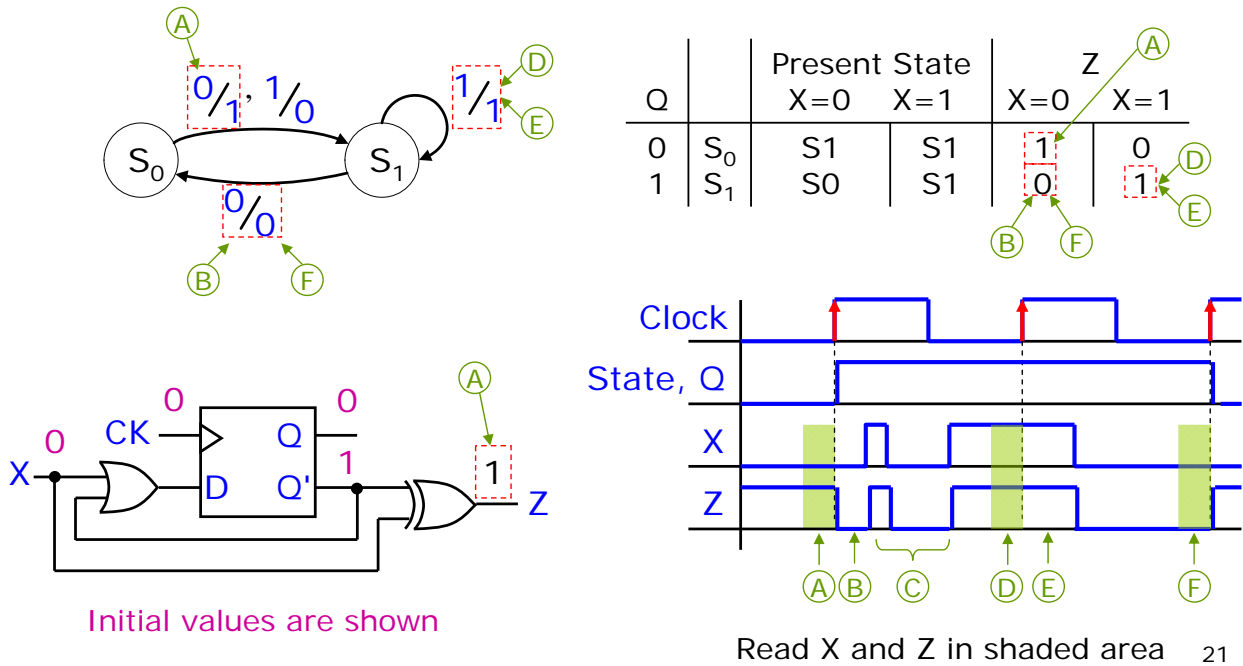Construction and interpretation of timing charts





State Tables and Graphs

Signal Tracing and Timing Charts


To plot a timing chart for a sequential circuit, the state graph (with states encoded in binary codes) can be a better reference than the circuit itself

Prior Mealy circuit example

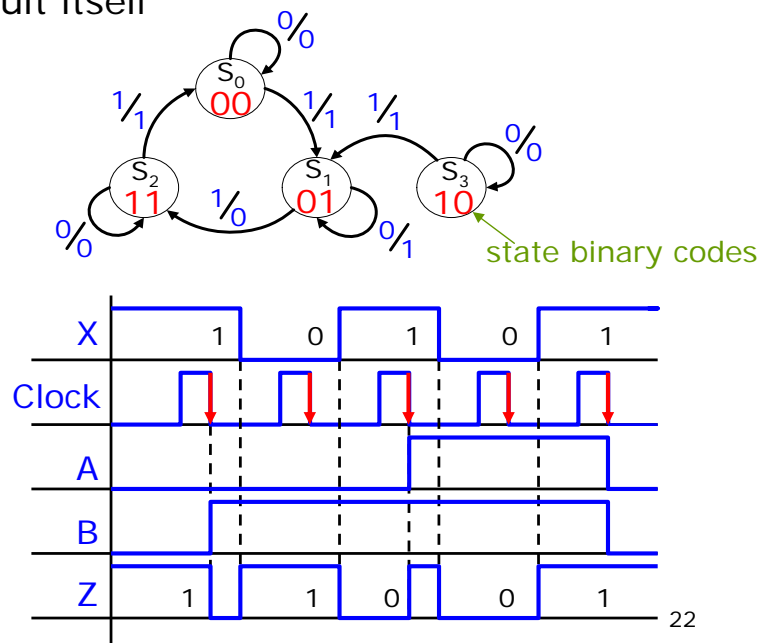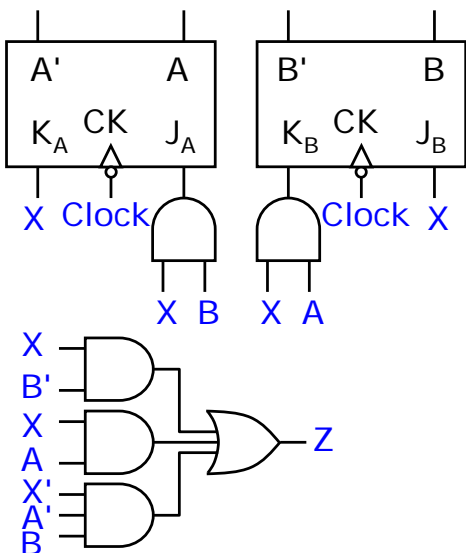

General Models for Sequential Circuits

Mealy Circuit Using D Flip-Flops

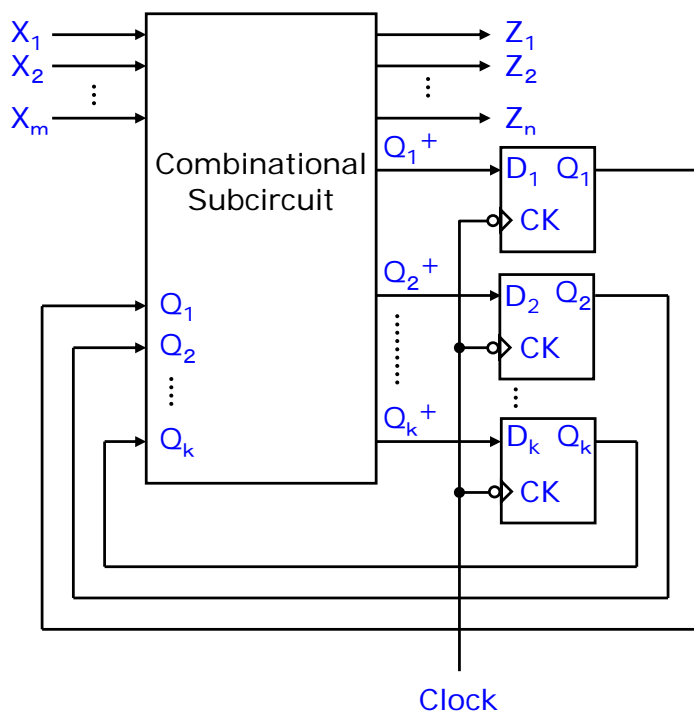

n output functions

$$\begin{aligned} Z_1 &= f_1(X_1, \dots, X_m, Q_1, \dots, Q_k) \\ &\vdots \\ Z_n &= f_n(X_1, \dots, X_m, Q_1, \dots, Q_k) \end{aligned}$$


k next-state functions

$$\begin{aligned} Q_1^+ &= D_1 = g_1(X_1, \dots, X_m, Q_1, \dots, Q_k) \\ &\vdots \\ Q_k^+ &= D_k = g_k(X_1, \dots, X_m, Q_1, \dots, Q_k) \end{aligned}$$

23

General Models for Sequential Circuits

Moore Circuit Using D Flip-Flops

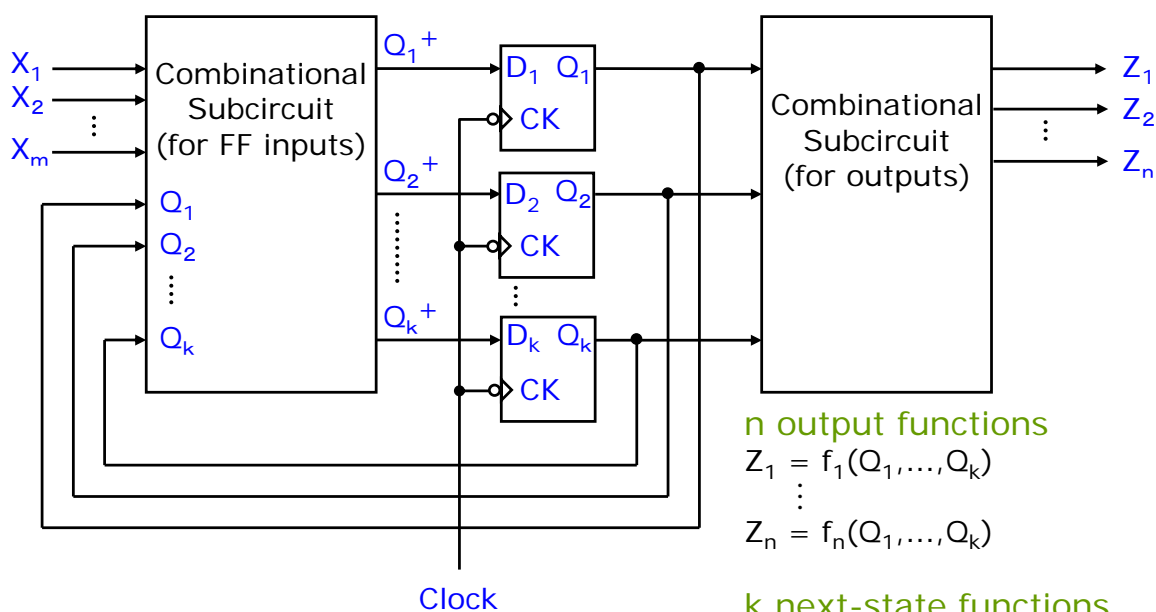

n output functions

$$\begin{aligned} Z_1 &= f_1(Q_1, \dots, Q_k) \\ &\vdots \\ Z_n &= f_n(Q_1, \dots, Q_k) \end{aligned}$$

k next-state functions

$$\begin{aligned} Q_1^+ &= D_1 = g_1(X_1, \dots, X_m, Q_1, \dots, Q_k) \\ &\vdots \\ Q_k^+ &= D_k = g_k(X_1, \dots, X_m, Q_1, \dots, Q_k) \end{aligned}$$

24

General Models for Sequential Circuits

Unary Representation

- $S^+ = \delta(S, X)$
- $Z = \begin{cases} \lambda(S, X) & \text{for Mealy machine} \\ \lambda(S) & \text{for Moore machine} \end{cases}$

Example (prior example with multiple inputs and outputs)


Present State	Next State				Present Output (Z)			
	X = 0	1	2	3	X = 0	1	2	3
S ₀	S ₃	S ₂	S ₁	S ₀	0	2	3	1
S ₁	S ₀	S ₁	S ₂	S ₃	2	2	3	3
S ₂	S ₃	S ₀	S ₁	S ₁	0	2	3	1
S ₃	S ₂	S ₂	S ₁	S ₀	0	0	1	1

25

General Models for Sequential Circuits

Minimum Clock Period

 - The minimum clock period
 - $t_{\text{clk}}(\text{min}) = t_x + t_c + t_{\text{su}}$, where t_x is the time after the active clock edge at which the X inputs are stable
 - $t_{\text{clk}}(\text{min}) = t_p + t_c + t_{\text{su}}$, if $t_x \leq t_p$





26


General Models for Sequential Circuits Timing Constraints

Setup-time constraint

$$C_p \geq t_p + t_c^{\max} + t_{su}$$

  

satisfied

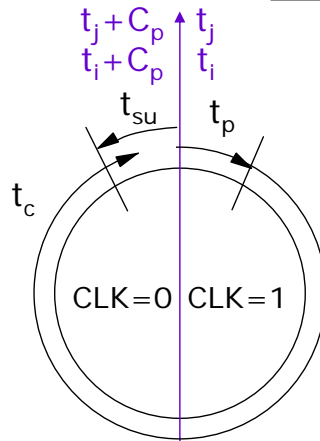

violated


C_p : clock period

27


General Models for Sequential Circuits Timing Constraints

Hold-time constraint

$$t_p + t_c^{\min} \geq t_h$$

 

satisfied

 

violated

28