

# Switching Circuits & Logic Design

Jie-Hong Roland Jiang  
江介宏

Department of Electrical Engineering  
National Taiwan University




Fall 2013

1

## §16 Sequential Circuit Design

Chomsky Hierarchy

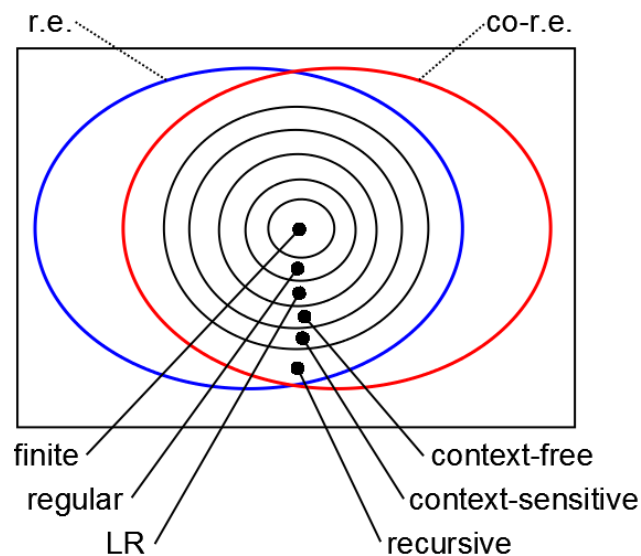

# Outline

---

- Summary of design procedure for sequential circuits
- Design example – code converter
- Design of iterative circuits
- Design of sequential circuits using ROMs and PLAs

3

# Summary of Design Procedure for Sequential Circuits


---

1. Derive state table (and/or state graph)
  - Given the problem statement, determine the required relationship between the input and output sequences and derive a state table
  - For many problems, it is easiest to first construct a state graph
2. Reduce state table
  - State minimization by row matching or using an implication table
3. Perform state assignment
  - $\lceil \log_2 m \rceil$  flip-flops are needed to encode  $m$  states
4. Form transition table
  - Substitute the assigned flip-flop states for each state in the reduced state table
5. Derive flip-flop input equations and output functions
  - Plot next-state maps and input maps for each flip-flop to derive the flip-flop input equations
6. Realize flip-flop input equations and output functions using available logic gates
7. Check design
  - Use signal tracing, computer simulation, or lab testing

4
 
# Design Example – Code Converter

- Convert BCD to excess-3 code
  - Add 3 to a binary-coded-decimal digit in the range 0 to 9
  - Assume serial input and output with the least significant bit first
  - Reset to initial state after receiving every 4 inputs



Can the converter be realized without delaying the output?


$$\begin{aligned}
 & t_0 \quad t_1 \quad t_2 \quad t_3 \quad \dots \\
 X &= X^{(0)} \quad X^{(1)} \quad X^{(2)} \quad X^{(3)} \quad \dots \\
 Z &= Z^{(0)} \quad Z^{(1)} \quad Z^{(2)} \quad Z^{(3)} \quad \dots
 \end{aligned}$$

X Input (BCD)				Z Output (excess-3)			
$t_3$	$t_2$	$t_1$	$t_0$	$t_3$	$t_2$	$t_1$	$t_0$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
other codes				-	-	-	-

# Design Example – Code Converter

- Step 1: derive state table and state graph

Time	Input Sequence Received (LSB first)	Present State	Next State		Present Output (Z)	
			X=0	1	X=0	1
$t_0$	reset	A	B	C	1	0
$t_1$	0	B	D	F	1	0
	1	C	E	G	0	1
$t_2$	00	D	H	L	0	1
	01	E	I	M	1	0
	10	F	J	N	1	0
	11	G	K	P	1	0
$t_3$	000	H	A	A	0	1
	001	I	A	A	0	1
	010	J	A	-	0	-
	011	K	A	-	0	-
	100	L	A	-	0	-
	101	M	A	-	1	-
	110	N	A	-	1	-
	111	P	A	-	1	-

 

# Design Example – Code Converter

## Step 2: Reduce state table

Time	Input Sequence Received (LSB first)	Present State	Next State		Present Output (Z)	
			X=0	1	X=0	1
t <sub>0</sub>	reset	A	B	C	1	0
t <sub>1</sub>	0	B	D	F	1	0
	1	C	E	G	0	1
t <sub>2</sub>	00	D	H	L	0	1
	01	E	I	M	1	0
	10	F	J	N	1	0
	11	G	K	P	1	0
t <sub>3</sub>	000	H	A	A	0	1
	001	I	A	A	0	1
	010	J	A	-	0	-
	011	K	A	-	0	-
	100	L	A	-	0	-
	101	M	A	-	1	-
	110	N	A	-	1	-
	111	P	A	-	1	-

Time	Present State	Next State		Present Output (Z)	
		X = 0	1	X = 0	1
t <sub>0</sub>	A	B	C	1	0
t <sub>1</sub>	B	D	E	1	0
	C	E	E	0	1
t <sub>2</sub>	D	H	H	0	1
	E	H	M	1	0
t <sub>3</sub>	H	A	A	0	1
	M	A	-	1	-

The matching assumes, under X=1, the next state is A and Z=1

The matching imposes no particular condition on these don't cares

7

# Design Example – Code Converter

- In reducing a state table by row matching, sometimes there can be multiple incompatible choices in matching a row

## Example

Present State	Next State		Present Output (Z)	
	X=0	1	X=0	1
Q	Q	S	0	1
R	-	-	-	1
S	S	Q	1	-

R can be matched with either Q or S, but not both

8

# Design Example – Code Converter

- Step 3: Perform state assignment
  - Need 3 flip-flops for 7 states

Reduced state table

Time	Present State	Next State		Present Output (Z)	
		X = 0	1	X = 0	1
t <sub>0</sub>	A	B	C	1	0
t <sub>1</sub>	B	D	E	1	0
	C	E	E	0	1
t <sub>2</sub>	D	H	H	0	1
	E	H	M	1	0
t <sub>3</sub>	H	A	A	0	1
	M	A	-	1	-

Assignment map

		Q <sub>1</sub>	
		0	1
Q <sub>2</sub> Q <sub>3</sub>	00	A	B
	01		C
	11	H	D
	10	M	E

An even better assignment?

# Design Example – Code Converter

- Step 4: Form transition table

Transition table

	Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub>	Q <sub>1</sub> <sup>+</sup> Q <sub>2</sub> <sup>+</sup> Q <sub>3</sub> <sup>+</sup>		Z	
		X=0	X=1	X=0	X=1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	xxx	1	x
-	001	xxx	xxx	x	x

Time	Present State	Next State		Present Output (Z)	
		X = 0	1	X = 0	1
t <sub>0</sub>	A	B	C	1	0
t <sub>1</sub>	B	D	E	1	0
	C	E	E	0	1
t <sub>2</sub>	D	H	H	0	1
	E	H	M	1	0
t <sub>3</sub>	H	A	A	0	1
	M	A	-	1	-

		Q <sub>1</sub>	
		0	1
Q <sub>2</sub> Q <sub>3</sub>	00	A	B
	01		C
	11	H	D
	10	M	E

# Design Example – Code Converter

- Step 5: Derive flip-flop input equations and output functions

X	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Z	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	0	0	1	1	0	0
0	0	0	1	x	x	x	x
0	0	1	0	1	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	1	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
0	1	1	1	0	0	1	1
1	0	0	0	0	1	0	1
1	0	0	1	x	x	x	x
1	0	1	0	x	x	x	x
1	0	1	1	1	0	0	0
1	1	0	0	0	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	0	0	1	0
1	1	1	1	1	0	1	1

XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub> 00	1	1	1	1
01	X	1	1	X
11	0	0	0	0
10	0	0	0	X

$D_1 = Q_1^+ = Q_2'$

XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub> 00	0	1	0	1
01	X	0	0	X
11	0	1	1	0
10	0	1	0	X

$D_2 = Q_2^+ = Q_1$

XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub> 00	1	1	0	0
01	X	0	1	X
11	0	0	1	1
10	1	1	0	X

$D_3 = Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$


XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub> 00	1	1	0	0
01	X	0	1	X
11	0	0	1	1
10	1	1	0	X

$Z = X'Q_3' + XQ_3$

11

# Design Example – Code Converter


- Step 6: Realize circuit

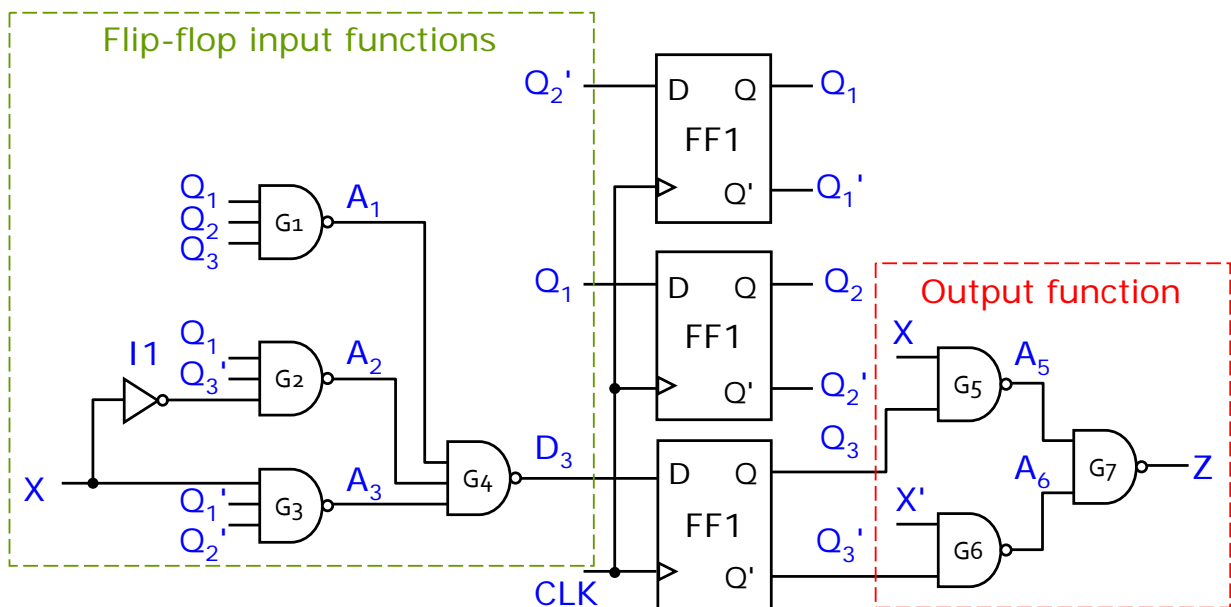

12
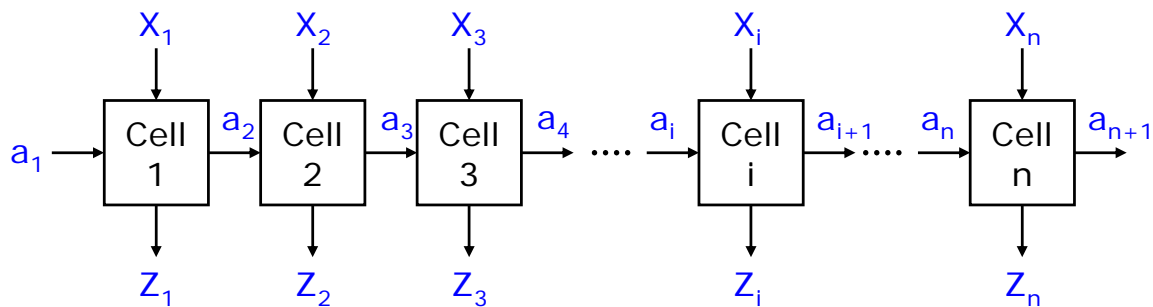
# Design of Iterative Circuits

- Many of the design procedures used for sequential circuits can be applied to the design of iterative circuits
  - E.g., the design procedure used for the (sequential) serial adder of Unit 13 can be applied to the design of the parallel adder of Unit 4
- **Unilateral iterative circuit** is the simplest form of an iterative circuit
  - A linear array of combinational cells with signals between cells traveling in only one direction




$X_i$  and  $Z_i$  are the primary input and output, respectively, of cell  $i$   
 $a_i$  and  $a_{i+1}$  resemble the present state and next state, respectively, of cell  $i$

13

# Design of Iterative Circuits
 
## Design of a Comparator

- Compare two  $n$ -bit binary numbers  
 $X = x_1x_2\dots x_n$  and  $Y = y_1y_2\dots y_n$   
 and determine if they are equal or which one is larger if they are not equal
  - Assume  $x_1$  and  $y_1$  are the most significant bits (we plan to do the comparison from left to right)



14

# Design of Iterative Circuits

## Design of a Comparator

- Steps 1,2: derive and reduce state table

		$S_{i+1}$				$Z_1$	$Z_2$	$Z_3$
		$x_i y_i = 00$	01	11	10			
$X=Y$	$S_0$	$S_0$	$S_2$	$S_0$	$S_1$	0	1	0
$X>Y$	$S_1$	$S_1$	$S_1$	$S_1$	$S_1$	0	0	1
$X<Y$	$S_2$	$S_2$	$S_2$	$S_2$	$S_2$	1	0	0

$\left\{ \begin{array}{l} Z_1: X < Y \\ Z_2: X = Y \\ Z_3: X > Y \end{array} \right.$

- Steps 3,4: Perform state assignment and form transition table

$a_i \ b_i$		$a_{i+1} b_{i+1}$				$Z_1$	$Z_2$	$Z_3$
		$x_i y_i = 00$	01	11	10			
0	0	00	10	00	01	0	1	0
0	1	01	01	01	01	0	0	1
1	0	10	10	10	10	1	0	0

state assignment

$\left\{ \begin{array}{l} S_0 = 00 \\ S_1 = 01 \\ S_2 = 10 \end{array} \right.$

15

# Design of Iterative Circuits

## Design of a Comparator

- Steps 5,6: derive and realize cell input and output functions


Typical cell for comparator

$a_i b_i$		$x_i y_i$			
		00	01	11	10
00	0	1	0	0	
01	0	0	0	0	
11	X	X	X	X	
10	1	1	1	1	


$a_{i+1} = a_i + x_i y_i b_i'$

$b_i a_i$		$x_i y_i$			
		00	01	11	10
00	0	0	0	1	
01	1	1	1	1	
11	X	X	X	X	
10	0	0	0	0	

$b_{i+1} = b_i + x_i y_i a_i'$

 

Output circuit for comparator

 


16



# Design of Iterative Circuits

## Design of a Comparator

### □ Sequential comparator

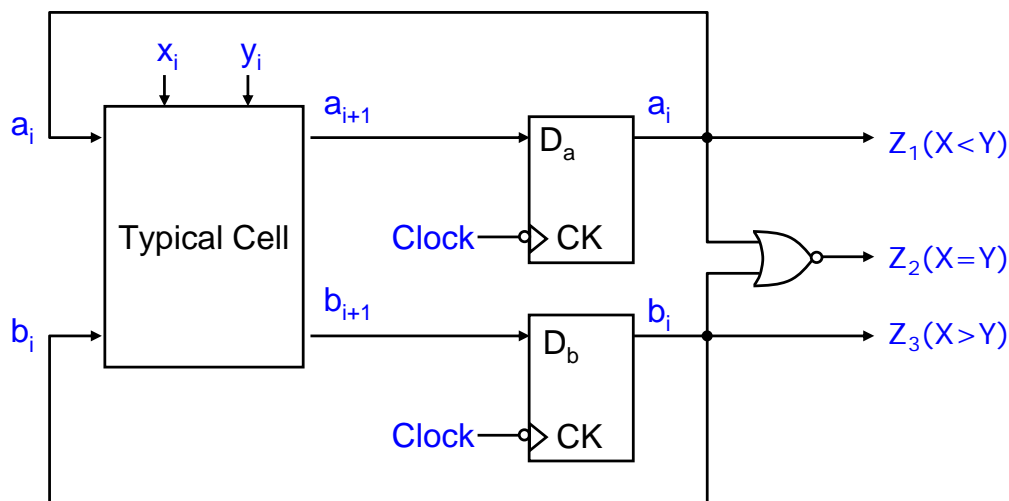

$$\begin{array}{cccc} t_1 & t_2 & t_n & \text{time} \\ X = & x_1 & x_2 \dots & x_n \dots \\ Y = & y_1 & y_2 \dots & y_n \dots \end{array}$$

17

# Design of Sequential Circuits Using ROMs and PLAs

### □ For a Mealy sequential circuit, the combinational part can be realized using a ROM (PLA)

- For the circuit with  $m$  inputs,  $n$  outputs, and  $k$  state variables, we need  $k$  D flip-flops and a ROM with  $m+k$  inputs ( $2^{m+k}$  words) and  $n+k$  outputs

### □ Similarly, for a Moore sequential circuit, the next-state and output combinational subcircuits can be realized using two ROMs (PLAs) or, alternatively, a single ROM (PLA)

18

# Design of Sequential Circuits Using ROMs

## Example

- Realize the prior BCD to excess-3 code converter using a ROM and D-FFs

State table

Present state	Next State		Present Output (Z)	
	X = 0	1	X = 0	1
A	B	C	1	0
B	D	E	1	0
C	E	E	0	1
D	H	H	0	1
E	H	M	1	0
H	A	A	0	1
M	A	-	1	-

Transition table

	$Q_1Q_2Q_3$	$Q_1+Q_2+Q_3+$		Z	
		X=0	X=1	X=0	X=1
A	0 0 0	001	010	1	0
B	0 0 1	011	100	1	0
C	0 1 0	100	100	0	1
D	0 1 1	101	101	0	1
E	1 0 0	101	110	1	0
H	1 0 1	000	000	0	1
M	1 1 0	000	-	1	-

19


# Design of Sequential Circuits Using ROMs

## Example (cont'd)

- Realize the prior BCD to excess-3 code converter using a ROM and D-FFs

Truth table

X	$Q_1$	$Q_2$	$Q_3$	Z	$D_1$	$D_2$	$D_3$
0	0	0	0	1	1	0	0
0	0	0	1	x	x	x	x
0	0	1	0	1	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	1	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
0	1	1	1	0	0	1	1
1	0	0	0	0	1	0	1
1	0	0	1	x	x	x	x
1	0	1	0	x	x	x	x
1	0	1	1	1	0	0	0
1	1	0	0	0	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	0	0	1	0
1	1	1	1	1	0	1	1

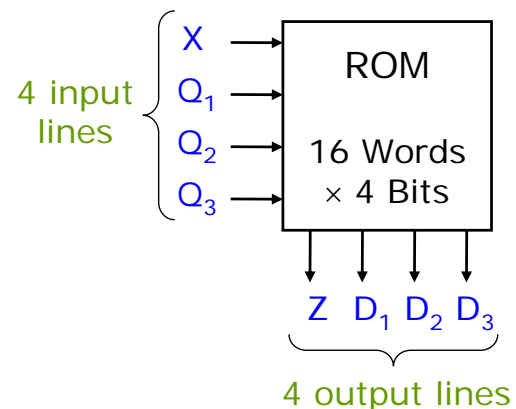


20

# Design of Sequential Circuits Using ROMs
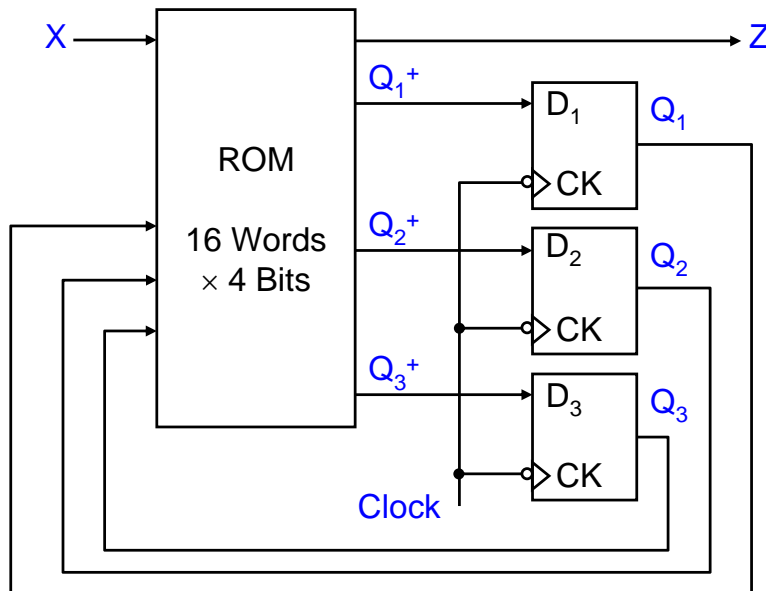
## Example (cont'd)

- Realize the prior BCD to excess-3 code converter using a ROM and D-FFs



21

# Design of Sequential Circuits Using PLAs

## Example

- Realize the prior BCD to excess-3 code converter using a PLA and D-FFs

Assignment map

	$Q_1$	
	0	1
$Q_2Q_3$		
00	A	B
01		C
11	H	D
10	M	E

Transition table

	$Q_1Q_2Q_3$	$Q_1+Q_2+Q_3+$		Z	
		X=0	X=1	X=0	X=1
A	000	100	101	1	0
B	100	111	110	1	0
C	101	110	110	0	1
D	111	011	011	0	1
E	110	011	010	1	0
H	011	000	000	0	1
M	010	000	xxx	1	x

22

# Design of Sequential Circuits Using PLAs

## Example (cont'd)

- Realize the prior BCD to excess-3 code converter using a PLA and D-FFs

	XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub>	00	1	1	1	1
	01	X	1	1	X
	11	0	0	0	0
	10	0	0	0	X

$$D_1 = Q_1^+ = Q_2'$$

	XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub>	00	0	1	1	0
	01	X	1	1	X
	11	0	1	1	0
	10	0	1	1	X

$$D_2 = Q_2^+ = Q_1$$

	XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub>	00	0	1	0	1
	01	X	0	0	X
	11	0	1	1	0
	10	0	1	0	X

$$D_3 = Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

	XQ <sub>1</sub>	00	01	11	10
Q <sub>2</sub> Q <sub>3</sub>	00	1	1	0	0
	01	X	0	1	X
	11	0	0	1	1
	10	1	1	0	X

$$Z = X'Q_3' + XQ_3$$

23

# Design of Sequential Circuits Using PLAs

## Example (cont'd)

- Realize the prior BCD to excess-3 code converter using a PLA and D-FFs

PLA table

	X	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Z	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
Q <sub>2</sub> '	-	-	0	-	0	1	0	0
Q <sub>1</sub>	-	1	-	-	0	0	1	0
Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub>	-	1	1	1	0	0	0	1
X'Q <sub>1</sub> Q <sub>3</sub> '	0	1	-	0	0	0	0	1
XQ <sub>1</sub> 'Q <sub>2</sub> '	1	0	0	-	0	0	0	1
X'Q <sub>3</sub>	0	-	-	0	1	0	0	0
XQ <sub>3</sub>	1	-	-	1	1	0	0	0

$$D_1 = Q_1^+ = Q_2'$$

$$D_2 = Q_2^+ = Q_1$$

$$D_3 = Q_3^+ = Q_1Q_2Q_3 + X'Q_1Q_3' + XQ_1'Q_2'$$

$$Z = X'Q_3' + XQ_3$$

AND plane

OR plane

24

# Design of Sequential Circuits Using PALs

## Example

- A segment of a sequential PAL realizing the next-state equation  $Q^+ = D = A'BQ' + AB'Q$

