

Fig. 2. Pattern graphs.

3 [Clock Skew Scheduling and Retiming]

Consider the circuit of Figure 4.

- (8%) What is the minimum clock period achievable by clock skew scheduling? What are the corresponding skews of r_2 , r_3 , and r_4 (with respect to the clock edge of r_1)?
- (4%) Draw the corresponding retiming graph. (You may need to create a dummy node for every fanout point.)
- (4%) What are the corresponding W and D matrices?
- (4%) Write down the inequality constraints of the integer linear program for a retime function r satisfying the condition that the clock period $c \leq 5$ ns.
- (4%) Draw the corresponding constraint graph for the set of inequality constraints in (c).
- (4%) Is there a negative-weighted cycle in the constraint graph? Derive a feasible retime function if it exists.

4 [Sequential Equivalence Checking]

Given two FSMs M_1 and M_2 , the transition and output functions of M_1 are

$$\delta_1(x, s) = s, \text{ and}$$

$$\lambda_1(x, s) = x \oplus s,$$

respectively; those of M_2 are

$$\begin{aligned}\delta_{2,0}(x, t_0, t_1) &= t_0 \oplus t_1, \\ \delta_{2,1}(x, t_0, t_1) &= x \oplus \delta_{2,0}, \text{ and} \\ \lambda_2(x, t_0, t_1) &= \delta_{2,1},\end{aligned}$$

respectively. (Note that x is the input variable, s is the state variable of M_1 , and t_0, t_1 are the state variables of M_2 .) Let $\neg s$ and $\neg t_0 \neg t_1$ be the characteristic functions of the initial states of M_1 and M_2 , respectively.

- (a) (4%) What are the transition and output functions of the product machine $M_{1 \times 2}$ of M_1 and M_2 ? What is the initial state of $M_{1 \times 2}$ in terms of a characteristic function?
- (b) (4%) Let s', t'_0, t'_1 be the corresponding next-state variables of s, t_0, t_1 , respectively. Write down the Boolean expression for the transition relation $T(s, t_0, t_1, s', t'_0, t'_1)$ of $M_{1 \times 2}$.
- (c) (7%) Perform **forward** reachability analysis using transition relation T . Show the reached state set at each iteration.
- (d) (7%) Are M_1 and M_2 equivalent? Conclude the equivalence using the computed characteristic functions. What if the initial states of M_1 and M_2 are $\neg s$ and $t_0 t_1$, respectively, instead?

 


Fig. 3. A circuit under timing analysis. Assume the arrival times for all of the primary inputs are 0, the gate delay of an inverter is 1ns, a NAND gate is 2ns, and the gate delay of a NOR gate is 3ns.)

 


Fig. 4. A circuit under timing optimization, where NOR2, NAND2, and INV are of gate delays 3ns, 2ns and 1ns, respectively. Assume the setup and hold times of the registers are 0.