

Introduction to Electronic Design Automation

Jie-Hong Roland Jiang
江介宏

Department of Electrical Engineering
National Taiwan University



Spring 2013

1

Testing

Testing

□ Recap

■ Design verification

- Is what I specified really what I wanted?
 - Property checking

■ Implementation verification


- Is what I implemented really what I specified?
 - Equivalence checking

■ Manufacture verification

- Is what I manufactured really what I implemented?
 - Testing; post manufacture verification
 - Quality control
 - Distinguish between good and bad chips

3

Design Flow

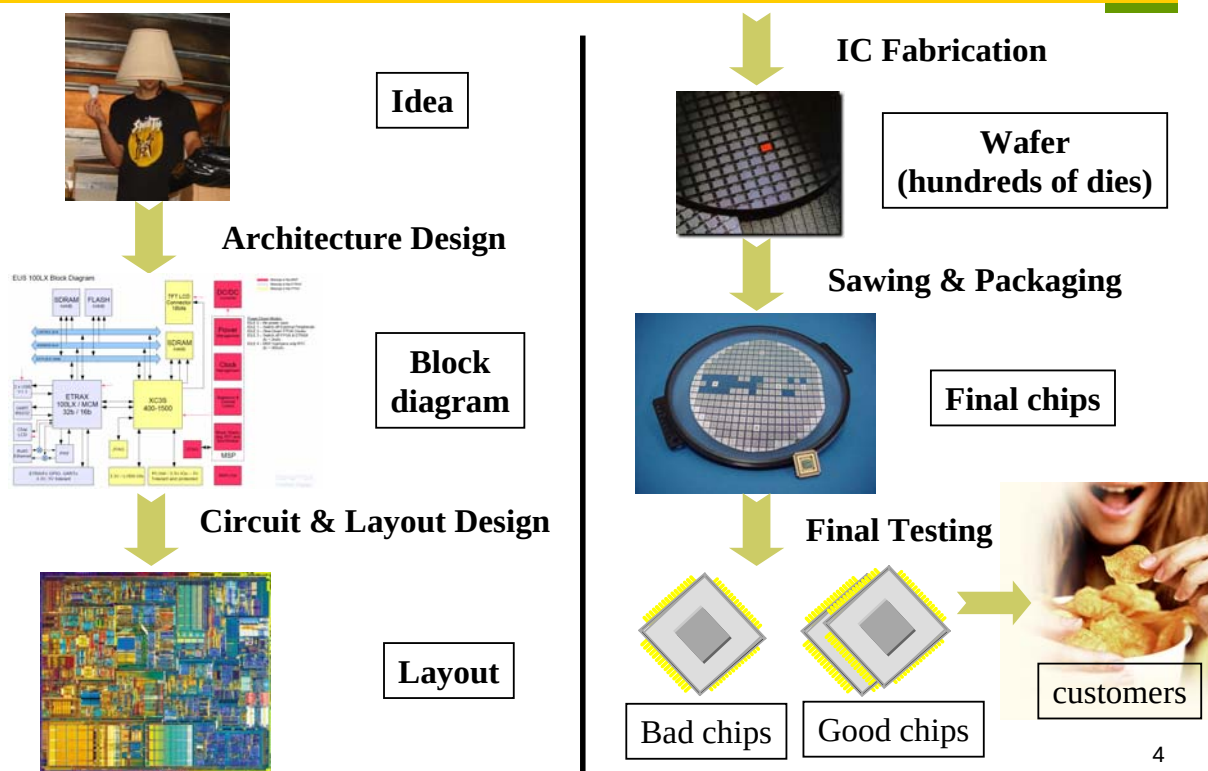

4

Manufacturing Defects

- ❑ Processing faults
 - missing contact windows
 - parasitic transistors
 - oxide breakdown
- ❑ Material defects
 - bulk defects (cracks, crystal imperfections)
 - surface impurities
- ❑ Time-dependent failures
 - dielectric breakdown
 - electro-migration
- ❑ Packaging failures
 - contact degradation
 - seal leaks

5

Faults, Errors and Failures

- ❑ Faults
 - A physical defect within a circuit or a system
 - May or may not cause a system failure
- ❑ Errors
 - Manifestation of a fault that results in incorrect circuit (system) outputs or states
 - Caused by faults
- ❑ Failures
 - Deviation of a circuit or system from its specified behavior
 - Fail to do what is supposed to do
 - Caused by errors
- ❑ Faults cause errors; errors cause failures

6

Testing and Diagnosis

□ Testing


- Exercise a system and analyze the response to ensure whether it behaves correctly **after manufacturing**

□ Diagnosis

- Locate the **causes** of misbehavior after the incorrectness is detected


7

Scenario of Manufacturing Test

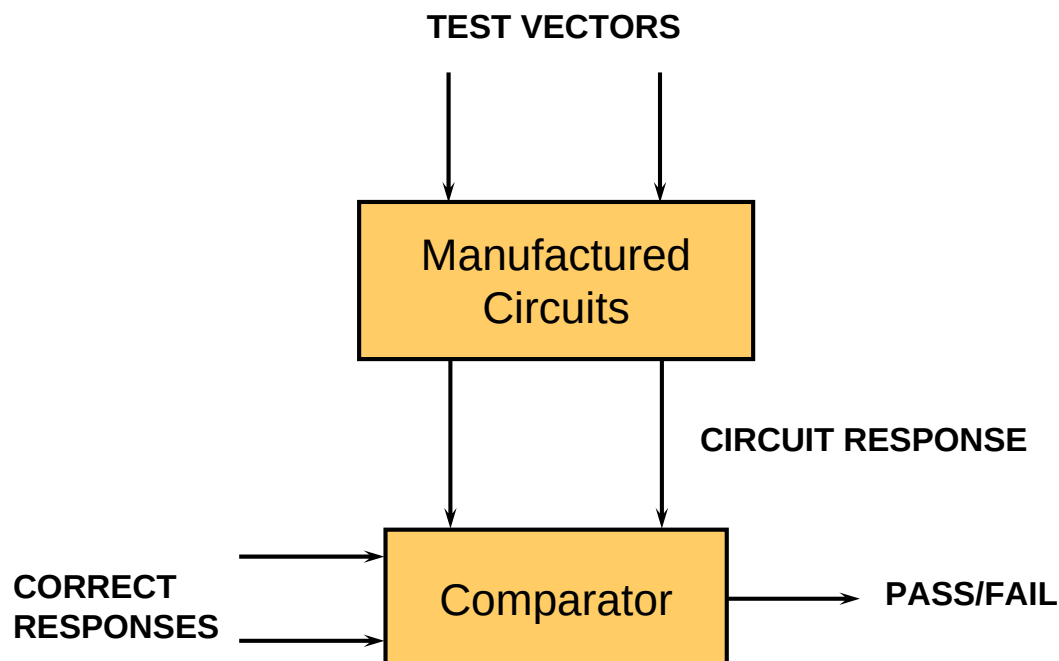

8


Test Systems

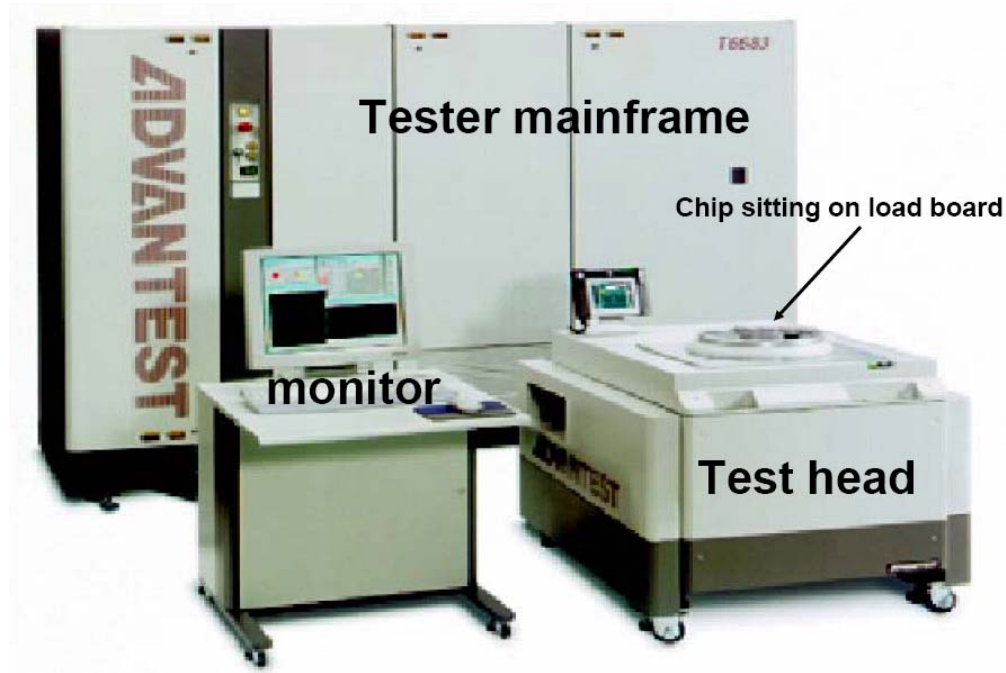

9

Purpose of Testing

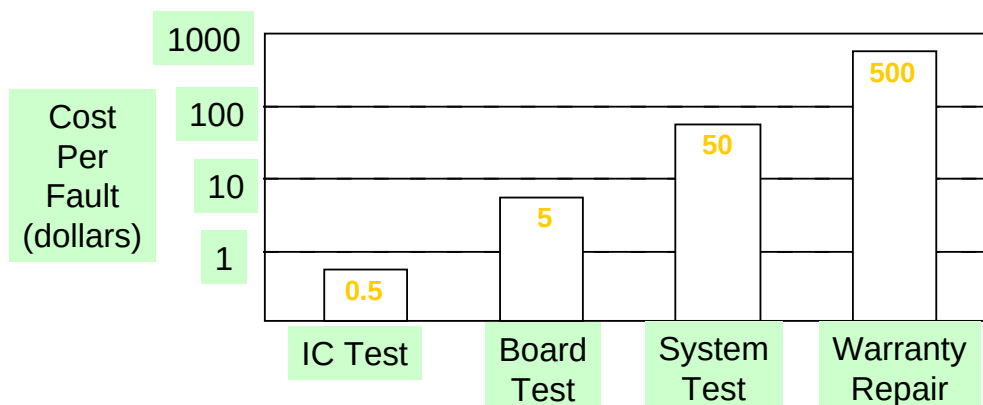- Verify manufactured circuits
 - Improve system reliability
 - Reduce repair costs
- Repair cost goes up by an order of magnitude each step away from the fab. line




B. Davis, "The Economics of Automatic Testing" McGraw-Hill 1982

10

Testing and Quality

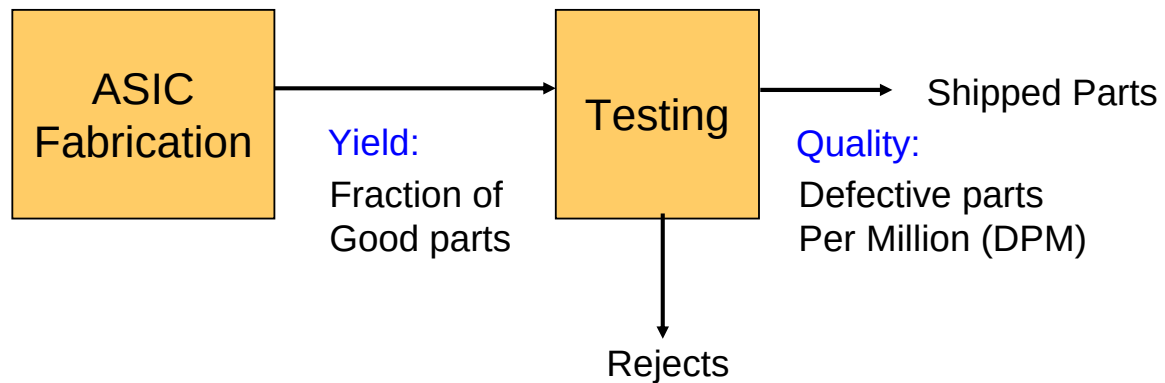- Quality of shipped part can be expressed as a function of the yield Y and test (fault) coverage T .



11

Fault Coverage

- Fault coverage T
 - Measure of the ability of a test set to detect a given set of faults that may occur on the Design Under Test (DUT)

$$T = \frac{\text{\# detected faults}}{\text{\# all possible faults}}$$

12

Defect Level

- A defect level is the fraction of the shipped parts that are defective


$$DL = 1 - Y^{(1-T)}$$

Y: yield

T: fault coverage

13

Defect Level vs. Fault Coverage

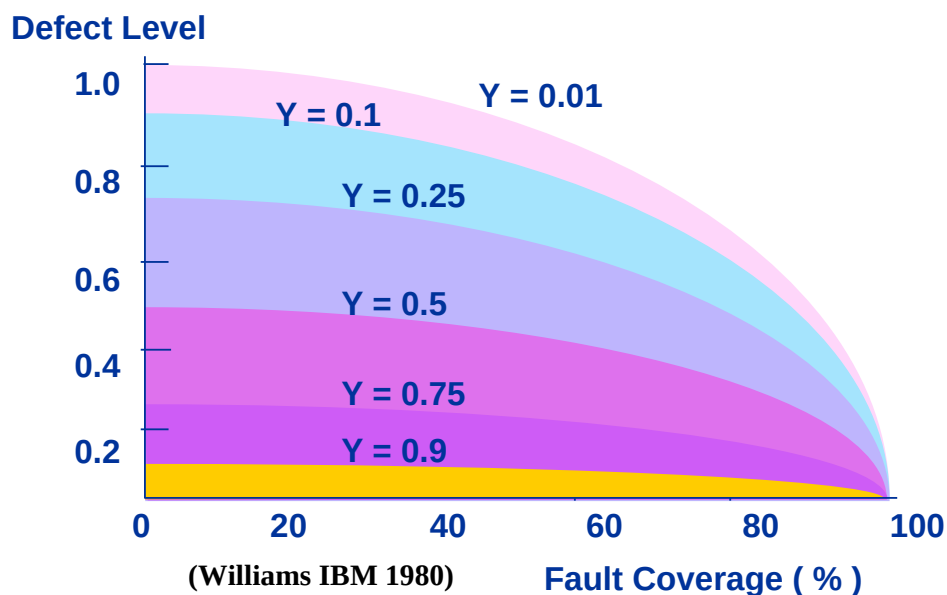

High fault coverage → Low defect level

14

DPM vs. Yield and Coverage

Yield	Fault Coverage	DPM
50%	90%	67,000
75%	90%	28,000
90%	90%	10,000
95%	90%	5,000
99%	90%	1,000
90%	90%	10,000
90%	95%	5,000
90%	99%	1,000
90%	99.9%	100

15


Why Testing Is Difficult ?

- Test time explodes exponentially in exhaustive testing of VLSI
 - For a combinational circuit with 50 inputs, need $2^{50} = 1.126 \times 10^{15}$ test patterns.
 - Assume one test per 10^{-7} sec, it takes 1.125×10^8 sec = 3.57years.
 - Test generation for **sequential circuits** are even more difficult due to the lack of **controllability** and **observability** at flip-flops (latches)
- Functional testing
 - may **NOT** be able to detect the physical faults

16

The Infamous Design/Test Wall

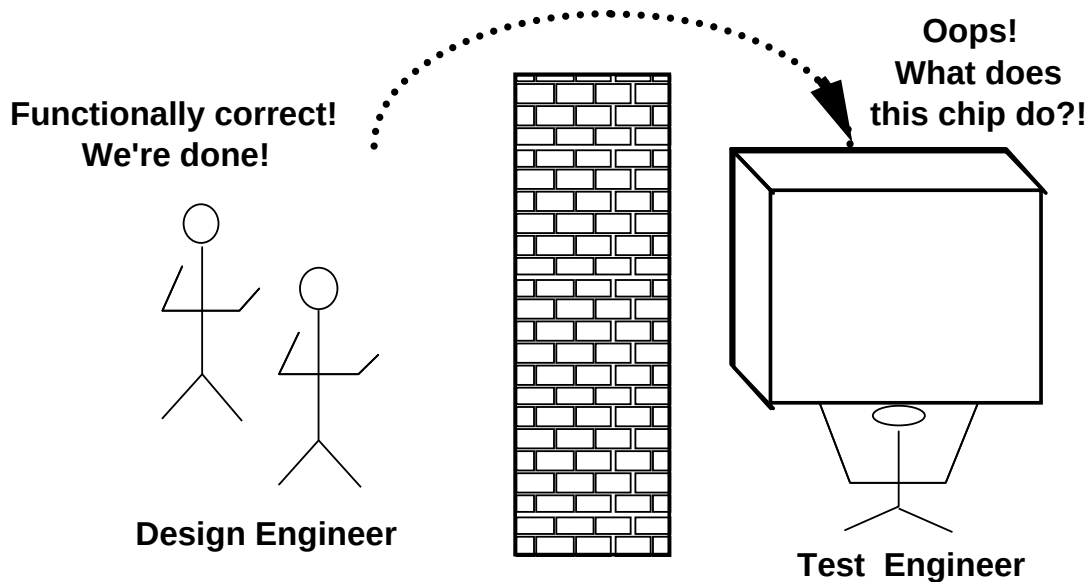30-years of experience proves that
test after design does not work!



17

Outline

- ❑ Fault Modeling
- ❑ Fault Simulation
- ❑ Automatic Test Pattern Generation
- ❑ Design for Testability

18

Functional vs. Structural Testing

- ❑ I/O functional testing is inadequate for manufacturing
 - Need fault models
- ❑ Exhaustive testing is daunting
 - Need abstraction and smart algorithms
 - Structural testing is more effective

19

Why Fault Model ?

- ❑ Fault model identifies target faults
 - Model faults that are most likely to occur
- ❑ Fault model limits the scope of test generation
 - Create tests only for the modeled faults
- ❑ Fault model makes testing effective
 - Fault coverage can be computed for specific test patterns to measure its effectiveness
- ❑ Fault model makes analysis possible
 - Associate specific defects with specific test patterns

20

Fault Modeling vs. Physical Defects

□ Fault modeling

- Model the effects of physical defects on the logic function and timing

□ Physical defects

- Silicon defects
- Photolithographic defects
- Mask contamination
- Process variation
- Defective oxides

21

Fault Modeling vs. Physical Defects (cont'd)

□ Electrical effects

- Shorts (bridging faults)
- Opens
- Transistor stuck-on/open
- Resistive shorts/opens
- Change in threshold voltages

□ Logical effects

- Logical stuck-at-0/1
- Slower transition (delay faults)
- AND-bridging, OR-bridging

22


Typical Fault Types

- ❑ **Stuck-at faults**
- ❑ Bridging faults
- ❑ Transistor stuck-on/open faults
- ❑ Delay faults
- ❑ IDDQ faults
- ❑ State transition faults (for FSM)
- ❑ Memory faults
- ❑ PLA faults

23

Single Stuck-At Fault

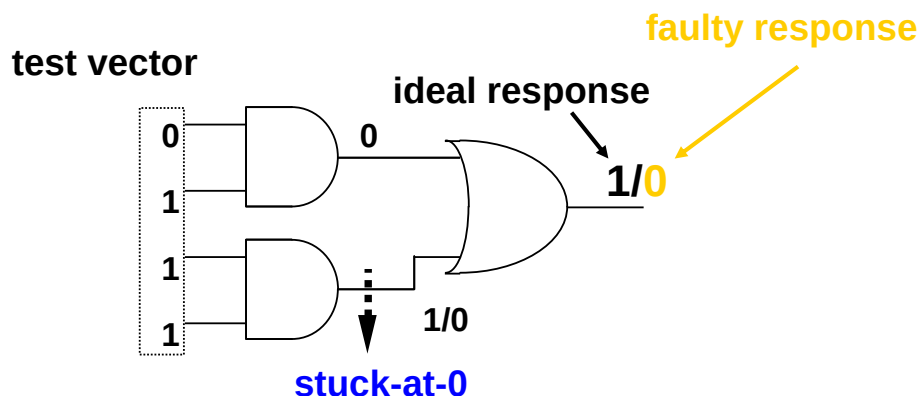- ❑ Assumptions:
 - Only one wire is faulty
 - Fault can be at an input or output of a gate
 - Faulty wire permanently sticks at 0 or 1



24

Multiple Stuck-At Faults

- ❑ Several stuck-at faults occur at the same time
 - Common in high density circuits

- ❑ For a circuit with k lines
 - There are $2k$ single stuck-at faults
 - There are $3^k - 1$ multiple stuck-at faults
 - ❑ A line could be stuck-at-0, stuck-at-1, or fault-free
 - ❑ One out of 3^k resulting circuits is fault-free

25

Why Single Stuck-At Fault Model ?

- ❑ Complexity is greatly reduced
 - Many different physical defects may be modeled by the same logical single stuck-at fault
- ❑ Stuck-at fault is technology independent
 - Can be applied to TTL, ECL, CMOS, BiCMOS etc.
- ❑ Design style independent
 - Gate array, standard cell, custom design
- ❑ Detection capability of un-modeled defects
 - Empirically, many un-modeled defects can also be detected accidentally under the single stuck-at fault model
- ❑ Cover a large percentage of multiple stuck-at faults

26

Why Logical Fault Modeling ?


- Fault analysis on logic rather than physical problem
 - Complexity is reduced
- Technology independent
 - Same fault model is applicable to many technologies
 - Testing and diagnosis methods remain valid despite changes in technology
- Wide applications
 - The derived tests may be used for physical faults whose effect on circuit behavior is not completely understood or too complex to be analyzed
- Popularity
 - Stuck-at fault is the most popular logical fault model

27

Definition of Fault Detection

- A test (vector) t detects a fault f iff t detects f (i.e. $z(t) \neq z_f(t)$)

- Example

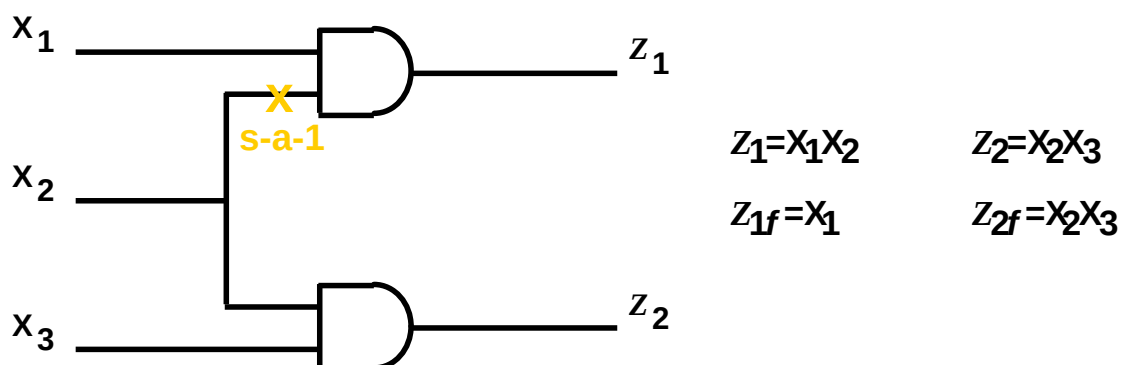

Test $(x_1, x_2, x_3) = (100)$ detects f because $z_1(100)=0$ and $z_{1f}(100)=1$


28

Fault Detection Requirement

- A test t that detects a fault f
 - **activates** f (or generate a fault effect) by creating different v and v_f values at the site of the fault
 - **propagates** the error to a primary output z by making all the wires along at least one path between the fault site and z have different v and v_f values
- Sensitized wire
 - A wire whose value in response to the test changes in the presence of the fault f is said to be **sensitized by the test** in the faulty circuit
- Sensitized path
 - A path composed of sensitized wires is called a **sensitized path**

29

Fault Sensitization

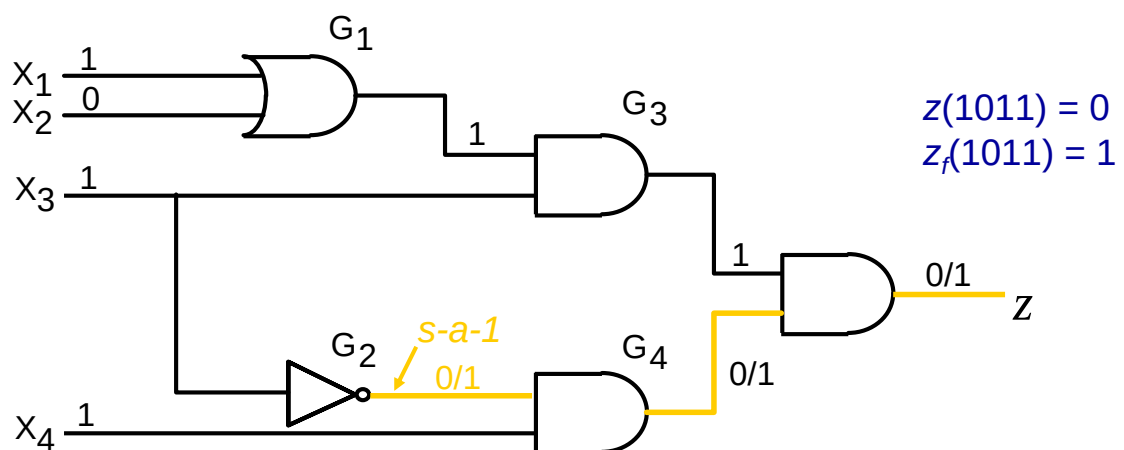

Input vector 1011 detects the fault f (G_2 stuck-at-1)

v/v_f : v = signal value in the fault free circuit

v_f = signal value in the faulty circuit

30

Detectability


- A fault f is said to be detectable
 - if there exists a test t that detects f
 - otherwise, f is an undetectable fault

- For an undetectable fault f
 - no test can **simultaneously** activate f and create a sensitized path to some primary output

31

Undetectable Fault

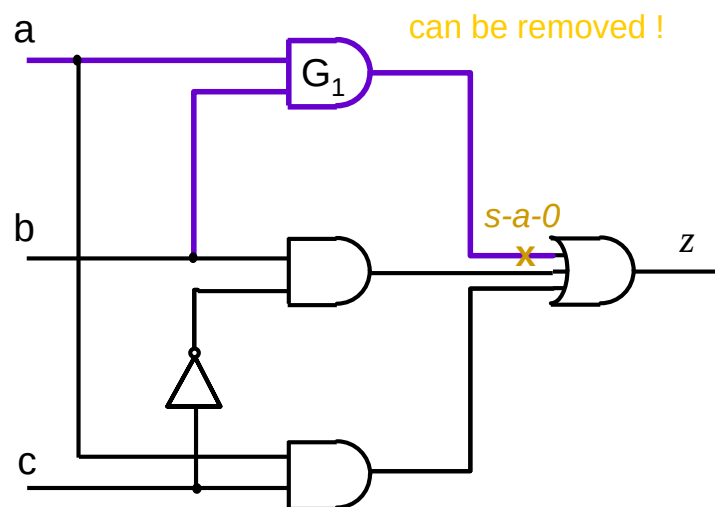- The stuck-at-0 fault at G_1 output is undetectable
 - Undetectable faults do not change the function of the circuit
 - The related circuit can be deleted to simplify the circuit



32

Test Set

□ Complete detection test set

- A set of tests that detects any detectable fault in a designated set of faults

□ Quality of a test set


- is measured by fault coverage

□ Fault coverage

- Fraction of the faults detected by a test set
- can be determined by [fault simulation](#)
- >95% is typically required under the single stuck-at fault model
- >99.9% required in the ICs manufactured by IBM

33

Typical Test Generation Flow

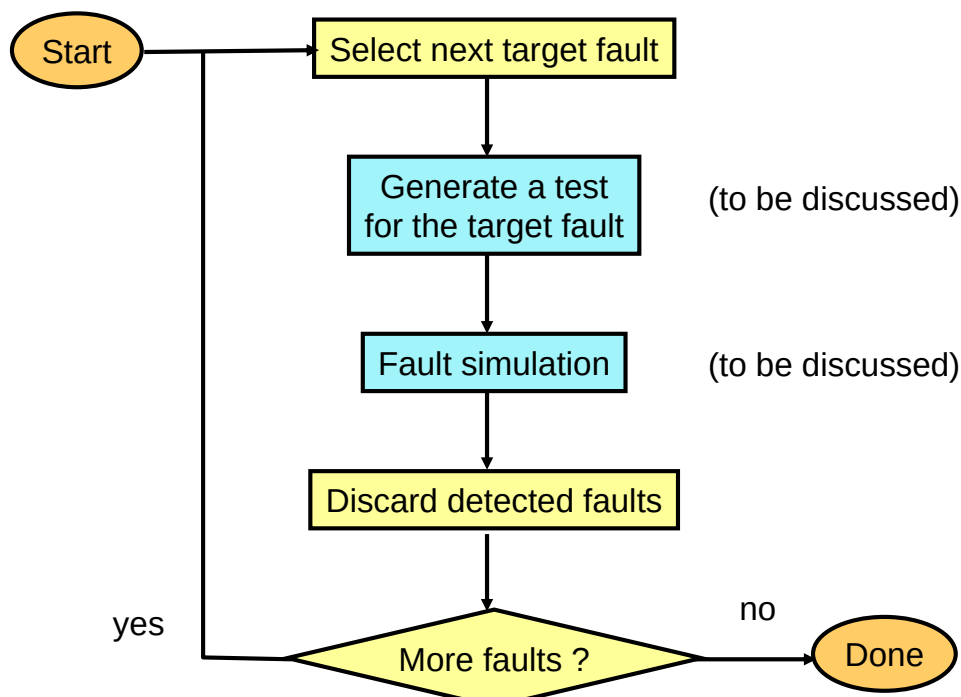

34

Fault Equivalence

□ Distinguishing test

- A test t distinguishes faults α and β if $z_\alpha(t) \neq z_\beta(t)$ for some PO function z

□ Equivalent faults

- Two faults α and β are said to be equivalent in a circuit iff the function under α is equal to the function under β for every input assignment (sequence) of the circuit.
- That is, no test can distinguish α and β , i.e., $\text{test-set}(\alpha) = \text{test-set}(\beta)$

35

Fault Equivalence

□ AND gate:

- all s-a-0 faults are equivalent

□ OR gate:

- all s-a-1 faults are equivalent

□ NAND gate:


- all the input s-a-0 faults and the output s-a-1 faults are equivalent

□ NOR gate:

- all input s-a-1 faults and the output s-a-0 faults are equivalent

□ Inverter:




 
- input s-a-1 and output s-a-0 are equivalent
- input s-a-0 and output s-a-1 are equivalent



36

Equivalence Fault Collapsing

    
- $n+2$, instead of $2(n+1)$, single stuck-at faults need to be considered for n -input AND (or OR) gates



37

Equivalent Fault Group

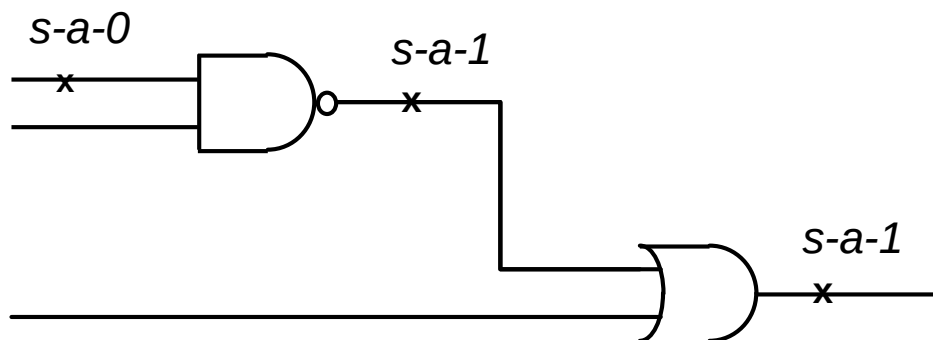- In a combinational circuit
 - Many faults may form an equivalence group
 - These equivalent faults can be found in a reversed topological order from POs to PIs




Three faults shown are equivalent !

38

Fault Dominance

□ Dominance relation

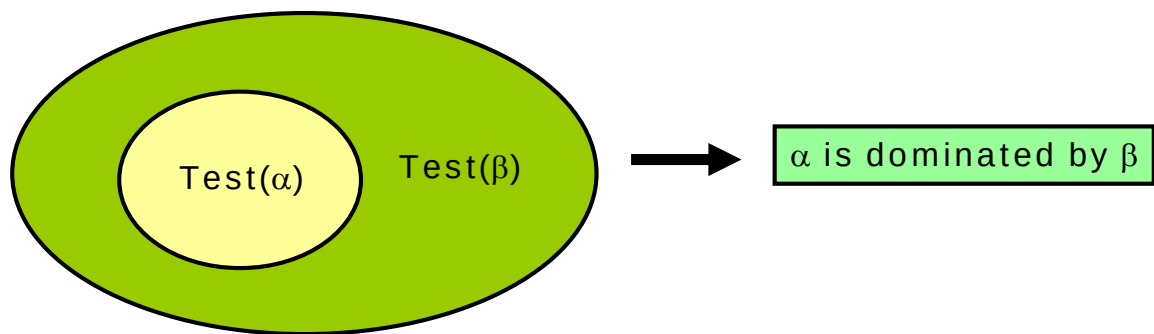- A fault β is said to *dominate* another fault α in an irredundant circuit iff every test (sequence) for α is also a test (sequence) for β , i.e., $\text{test-set}(\alpha) \subseteq \text{test-set}(\beta)$
- No need to consider fault β for fault detection



39

Fault Dominance

□ AND gate

- Output s-a-1 dominates any input s-a-1

□ NAND gate

- Output s-a-0 dominates any input s-a-1

□ OR gate


- Output s-a-0 dominates any input s-a-0

□ NOR gate

- Output s-a-1 dominates any input s-a-0

□ Dominance fault collapsing

 - Reducing the set of faults to be analyzed based on the dominance relation



40


Stem vs. Branch Faults

- Detect A s-a-1:
 $z(t) \oplus z_f(t) = (CD \oplus CE) \oplus (D \oplus CE)$
 $= D \oplus CD \Rightarrow (C=0, D=1)$

- Detect C s-a-1:
 $z(t) \oplus z_f(t) = (CD \oplus CE) \oplus (D \oplus E)$
 $\Rightarrow (C=0, D=1, E=0) \text{ or } (C=0, D=0, E=1)$

- Hence, C s-a-1 does not dominate A s-a-1

 - In general, there might be no equivalence or dominance relations between stem and branch faults




C: stem of a multiple fanout
A, B: branches

41

Analysis of a Single Gate

 - Fault Equivalence Class
 - (A s-a-0, B s-a-0, C s-a-0)
- Fault Dominance Relations
 - (C s-a-1 > A s-a-1) and (C s-a-1 > B s-a-1)
- Faults that can be ignored:
 - A s-a-0, B s-a-0, and C s-a-1




AB	C	A sa1	B sa1	C sa1	A sa0	B sa0	C sa0
00	0			1			
01	0	1		1			
10	0		1	1			
11	1				0	0	0

42

Fault Collapsing

□ Collapse faults by fault equivalence and dominance

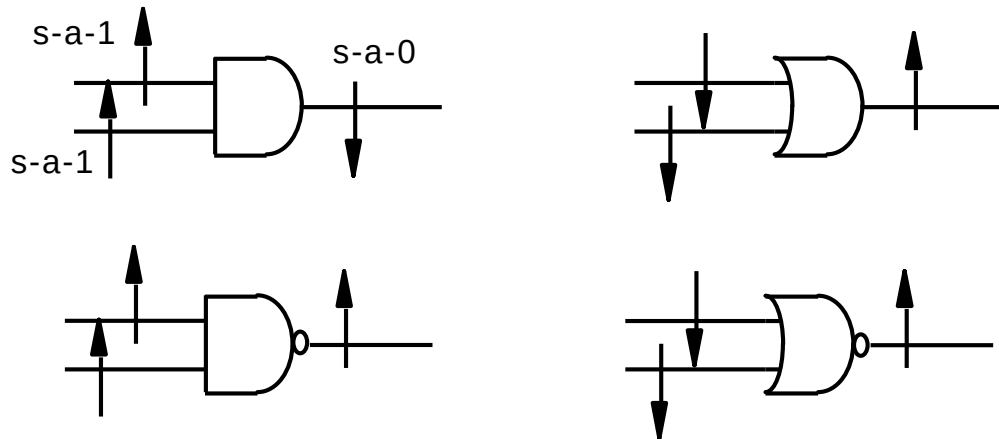- For an n -input gate, we only need to consider $n+1$ faults in test generation



43


Dominance Graph

□ Rule

- When fault α dominates fault β , then an arrow is pointing from α to β


□ Application

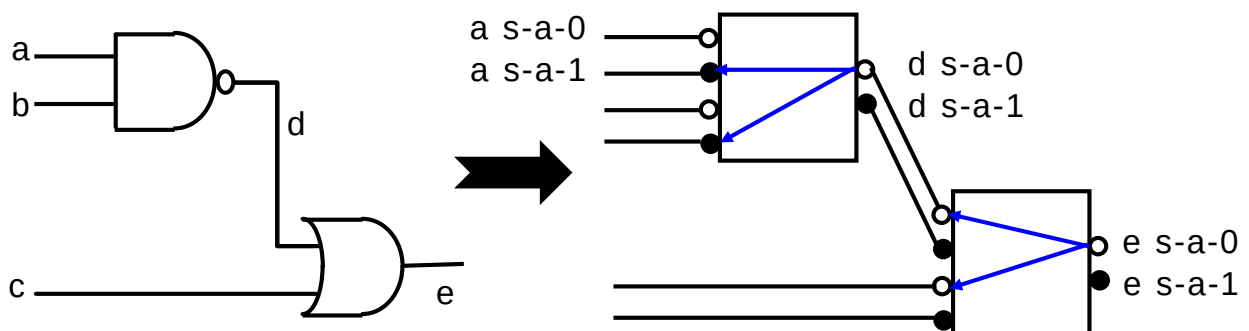- Find out the **transitive dominance relations** among faults



44

Fault Collapsing Flow

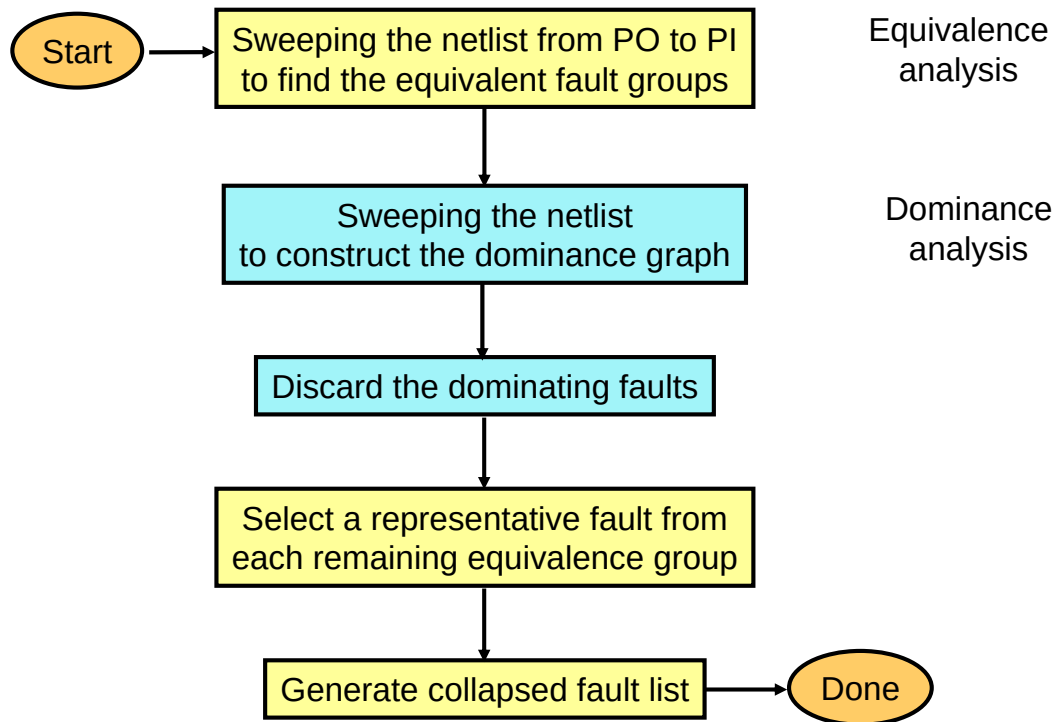

45


Prime Fault

- α is a **prime fault** if every fault that is dominated by α is also equivalent to α
- Representative Set of Prime Fault (RSPF)
 - A set that consists of exactly one prime fault from each equivalence class of prime faults
 - True minimal RSPF is difficult to find

46

Why Fault Collapsing ?

 - Save memory and CPU time
- Ease testing generation and fault simulation
- Exercise




* 30 total faults → 12 prime faults

47

Checkpoint Theorem

- Checkpoints for test generation
 - A test set detects every fault on the **primary inputs** and **fanout branches** is complete
 - I.e., this test set detects all other faults, too
 - Therefore, primary inputs and fanout branches form a **sufficient** set of checkpoints in test generation
 - In fanout-free combinational circuits (i.e., every gate has only one fanout), primary inputs are the checkpoints

 


Stem is not a checkpoint !

48

Why Inputs + Branches Are Enough ?

□ Example

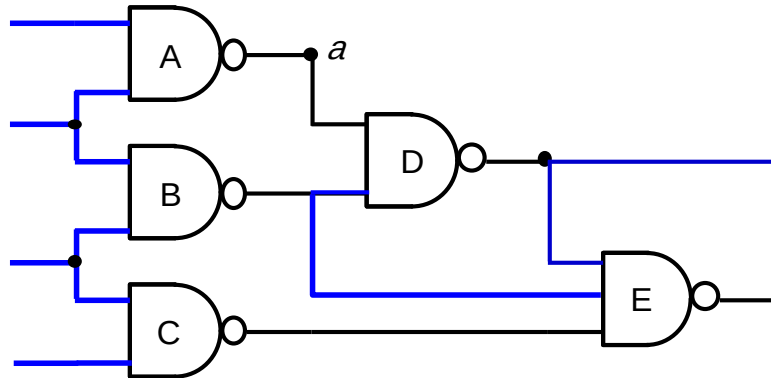- Checkpoints are marked in blue
- Sweeping the circuit from PI to PO to examine every gate, e.g., based on an order of (A->B->C->D->E)
- For each gate, output faults are detected if every input fault is detected




49

Fault Collapsing + Checkpoint

□ Example:

 - 10 checkpoint faults
- $a \text{ s-a-0} \iff d \text{ s-a-0}$, $c \text{ s-a-0} \iff e \text{ s-a-0}$
 $b \text{ s-a-0} > d \text{ s-a-0}$, $b \text{ s-a-1} > d \text{ s-a-1}$
- 6 faults are enough



50

Outline

- Fault Modeling
- Fault Simulation
- Automatic Test Pattern Generation
- Design for Testability


51

Why Fault Simulation ?

- To evaluate the quality of a test set
 - I.e., to compute its fault coverage
- Part of an ATPG program
 - A vector usually detects multiple faults
 - Fault simulation is used to compute the faults that are accidentally detected by a particular vector
- To construct fault-dictionary
 - For post-testing diagnosis

52

Conceptual Fault Simulation

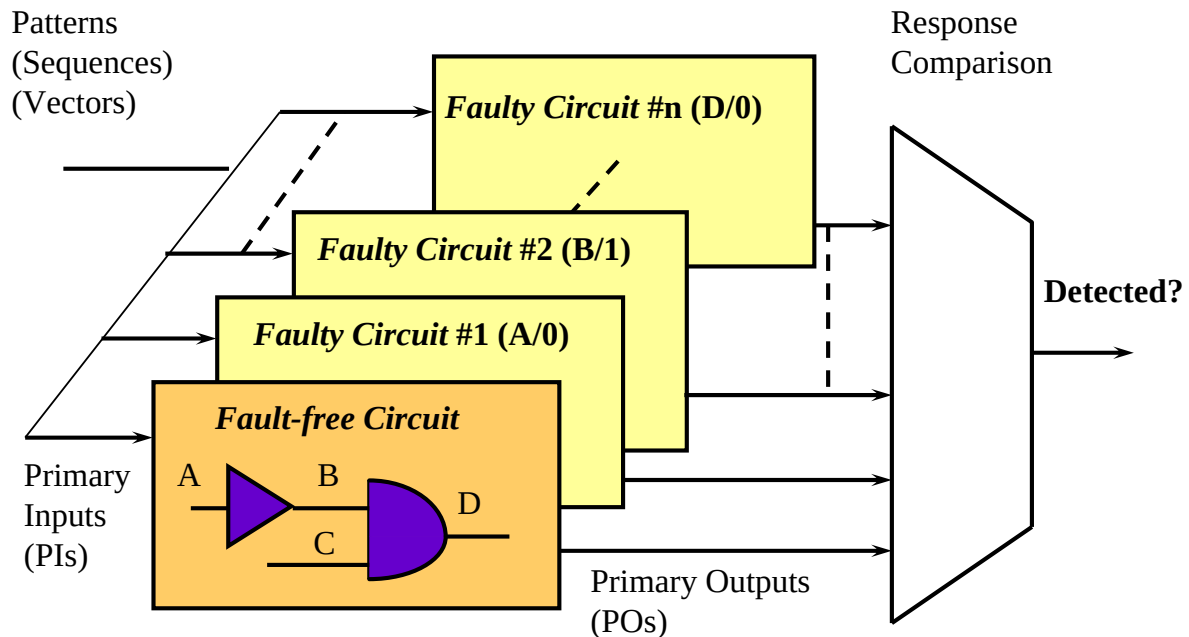

Logic simulation on both good (fault-free) and faulty circuits


53

Some Basics for Logic Simulation

- ❑ In fault simulation, our main concern is functional faults; gate delays are assumed to be **zero** unless delay faults are considered
- ❑ Logic values can be either {0, 1} (for two-value simulation) or {0, 1, X} (for three-value simulation)
- ❑ Two simulation mechanisms:
 - **Compiled-code valuation:**
 - ❑ A circuit is translated into a program and **all** gates are executed for each pattern (may have redundant computation)
 - **Event-driven valuation:**
 - ❑ Simulating a vector is viewed as a sequence of **value-change events** propagating from PIs to POs
 - ❑ Only those logic gates affected by the events are **re-evaluated**


54

Event-Driven Simulation

 

55

Complexity of Fault Simulation

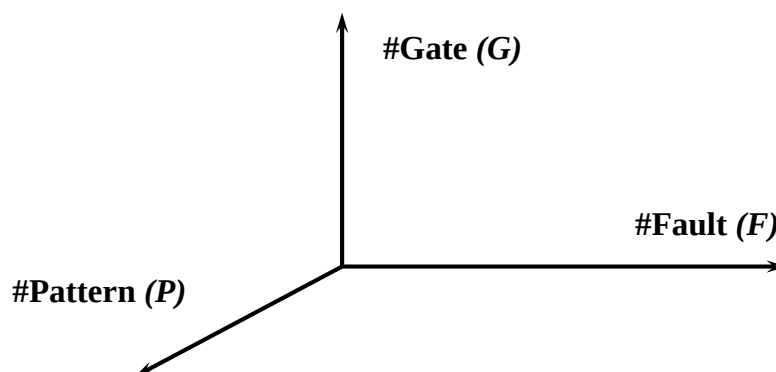


- ❑ Complexity $\sim F \cdot P \cdot G \sim O(G^3)$
- ❑ The complexity is higher than logic simulation by a factor of F , while it is usually much lower than ATPG
- ❑ The complexity can be greatly reduced using
 - fault collapsing and other advanced techniques

56

Characteristics of Fault Simulation

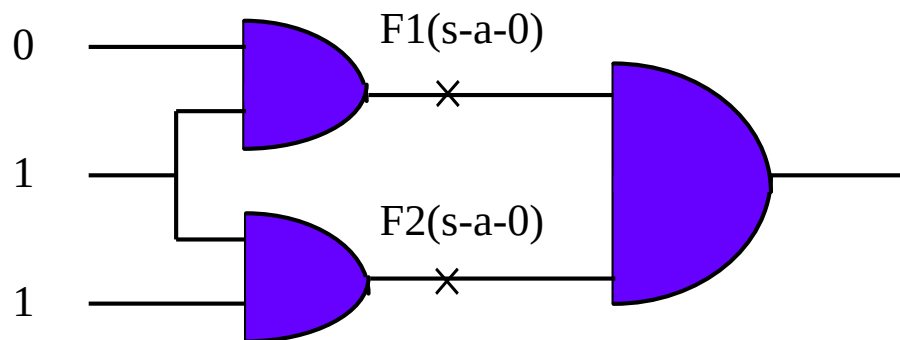- ❑ Fault activity with respect to fault-free circuit
 - is often **sparse** both in **time** and **space**.
- ❑ For example
 - F1 is not activated by the given pattern, while F2 affects only the lower part of this circuit.



57

Fault Simulation Techniques

- ❑ Parallel Fault Simulation
- ❑ Deductive Fault Simulation

58

Parallel Fault Simulation

□ Simulate multiple circuits simultaneously

- The inherent parallel operation of computer words to simulate faulty circuits in parallel with fault-free circuit
- The number of faulty circuits or faults can be processed simultaneously is limited by the word length, e.g., 32 circuits for a 32-bit computer

□ Complication



- An event or a value change of a single faulty or fault-free circuit leads to the computation of an entire word
- The fault-free logic simulation is repeated for each pass

59

Parallel Fault Simulation

□ Example

 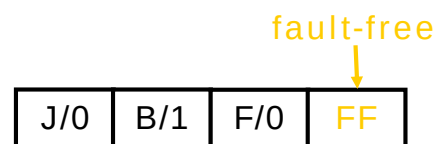- Consider three faults:
(J s-a-0, B s-a-1, and F s-a-0)
- Bit-space: (FF denotes fault-free)



60


Deductive Fault Simulation

- Simulate all faulty circuits in one pass
 - For each pattern, sweep the circuit from PIs to POs.
 - During the process, a list of faults is associated with each wire
 - The list contains faults that would produce a fault effect on this wire
 - The union fault list at every PO contains the detected faults by the simulated input vector
- Main operation is fault list propagation
 - Depending on gate types and values
 - The size of the list may grow dynamically, leading to the potential memory explosion problem

61

Illustration of Fault List Propagation

Consider a two-input AND-gate:

 

Non-controlling case:

Case 1: $A=1, B=1, C=1$ at fault-free,
 $LC = LA \cup LB \cup \{C/0\}$

Controlling cases:

Case 2: $A=1, B=0, C=0$ at fault-free,
 $LC = (\overline{LA} \cap LB) \cup \{C/1\}$

Case 3: $A=0, B=0, C=0$ at fault-free,
 $LC = (LA \cap LB) \cup \{C/1\}$

—
 $\overline{LA}$ is the set of all faults not in LA

62

Rule of Fault List Propagation


	<i>a</i>	<i>b</i>	<i>z</i>	Output fault list
AND	0	0	0	$\{L_a \cap L_b\} \cup z_1$
	0	1	0	$\{L_a - L_b\} \cup z_1$
	1	0	0	$\{L_b - L_a\} \cup z_1$
	1	1	1	$\{L_a \cup L_b\} \cup z_0$
OR	0	0	0	$\{L_a \cup L_b\} \cup z_1$
	0	1	1	$\{L_b - L_a\} \cup z_0$
	1	0	1	$\{L_a - L_b\} \cup z_0$
	1	1	1	$\{L_a \cap L_b\} \cup z_0$
NOT	0		1	$L_a \cup z_0$
	1		0	$L_a \cup z_1$

63

Deductive Fault Simulation

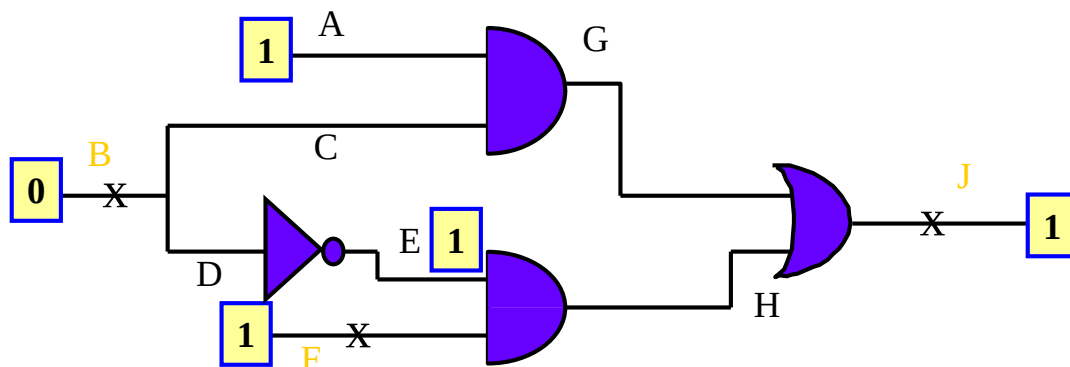Example (1/4)

- Consider 3 faults: B/1, F/0, and J/0 under (A,B,F) = (1,0,1)



Fault list at PIs:


$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC=LD = \{B/1\}$

64

Deductive Fault Simulation

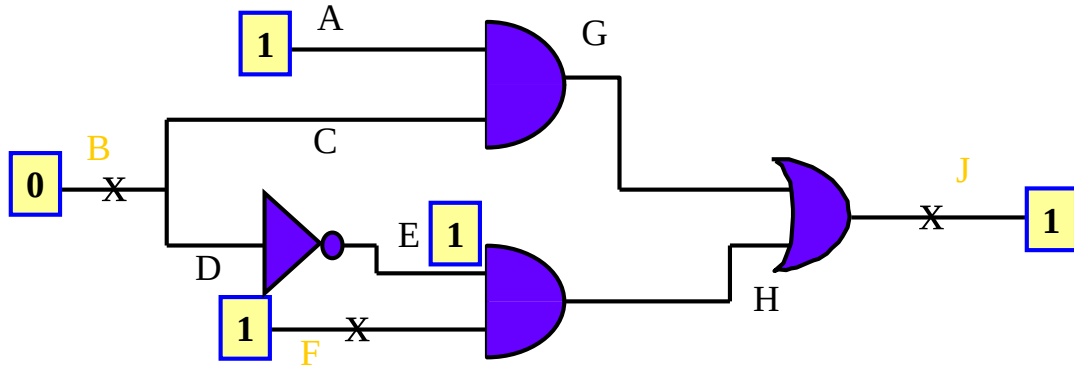Example (2/4)

Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$

Fault lists at G and E:

$LG = (\overline{LA} \cap \overline{LC}) \cup G/1 = \{B/1, G/1\}$


$LE = (\overline{LD}) \cup E/0 = \{B/1, E/0\}$

65

Deductive Fault Simulation

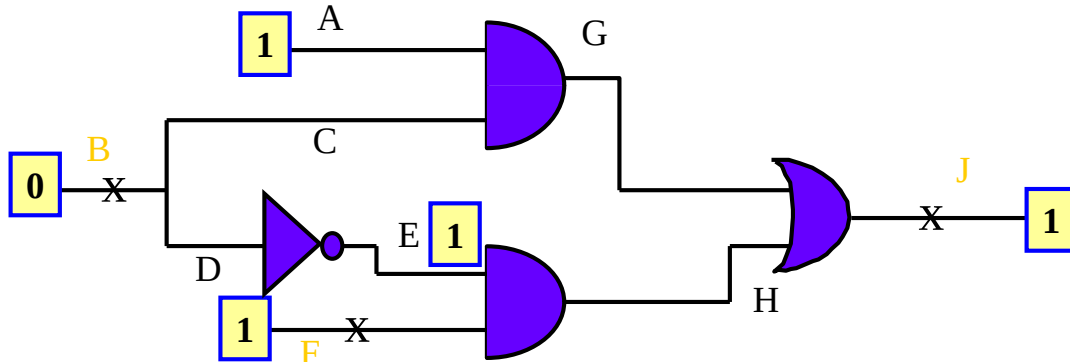Example (3/4)

Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$,

$LG = \{B/1, G/1\}$, $LE = \{B/1, E/0\}$

Fault list at H:


$LH = (LE \cup LF) \cup H/0 = \{B/1, E/0, F/0, H/0\}$

66

Deductive Fault Simulation

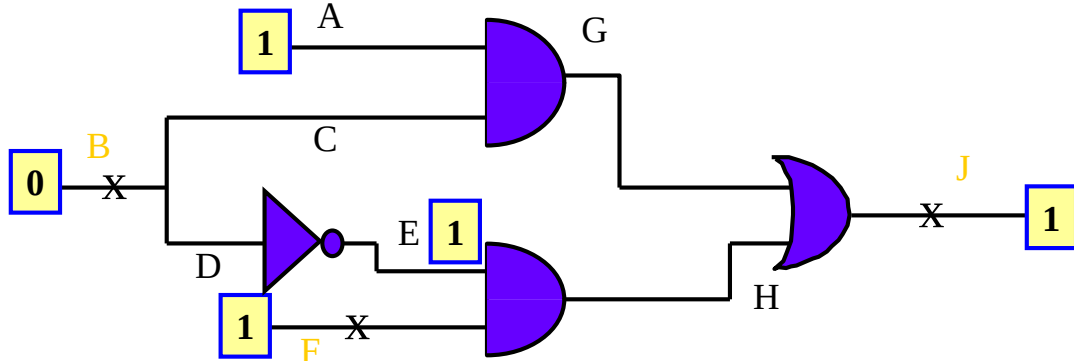Example (4/4)

Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (1,0,1)$



$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = \{B/1\}$, $LG = \{B/1, \text{G/1}\}$, $LE = \{B/1, \text{E/0}\}$, $LH = \{B/1, \text{E/0}, F/0, \text{H/0}\}$

Final fault list at PO J:


$LJ = (LH - LG) \cup LJ = \{\text{E/0}, F/0, J/0\}$

67

Deductive Fault Simulation

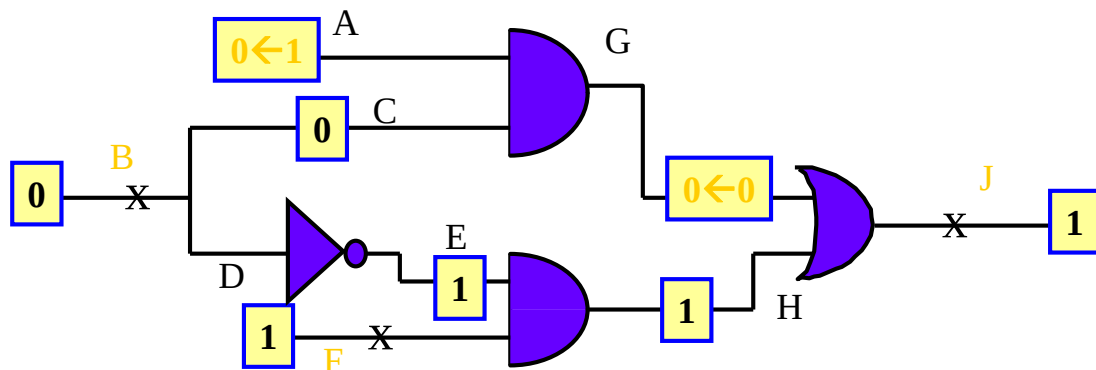Example (cont'd)

Consider 3 faults: B/1, F/0, and J/0 under $(A,B,F) = (0,0,1)$



Event driven updates:

$LB = \{B/1\}$, $LF = \{F/0\}$, $LA = \emptyset$, $LC = LD = LE = \{B/1\}$, $LG = \{G/1\}$, $LH = \{B/1, F/0\}$, $LJ = \{B/1, F/0, J/0\}$

68

Outline

□ Fault Modeling

□ Fault Simulation

□ Automatic Test Pattern Generation (ATPG)

■ Functional approach

□ Boolean difference

■ Structural approach

□ D-algorithm


□ PODEM

□ Design for Testability

69

Typical ATPG Flow

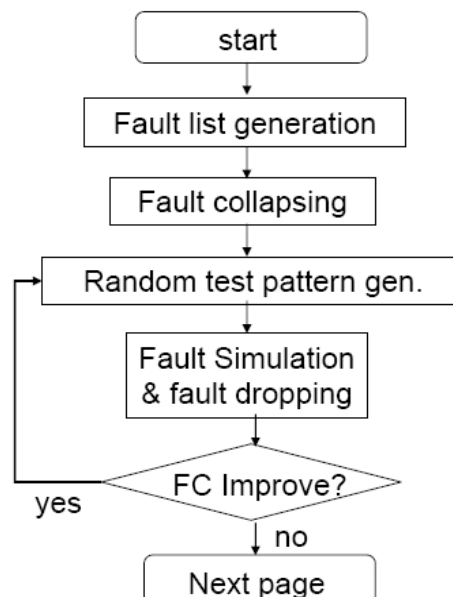
□ 1st phase: random test pattern generation



70

Typical ATPG Flow (cont'd)

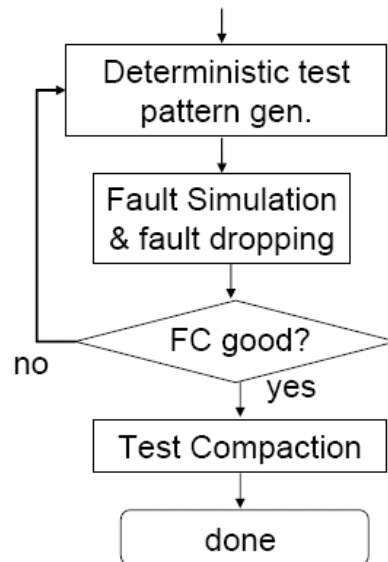- 2nd phase: deterministic test pattern generation



71

Test Pattern Generation

- The test set T of a fault α with respect to some PO z can be computed by

$$T(x) = z(x) \oplus z_{\alpha}(x)$$

- A test pattern can be fully specified or partially specified depending on whether the values of PIs are all assigned

- Example

abc	z	z_{α}
000	0	0
001	0	0
010	0	0
011	0	0
100	0	0
101	1	1
110	1	0
111	1	0


Input vectors (1,1,0) and (1,1,-) are fully and partially specified test patterns of fault α , respectively.

72

Structural Test Generation

D-Algorithm

- Test generation from circuit structure
- Two basic goals
 - (1) **Fault activation** (FA)
 - (2) **Fault propagation** (FP)
 - Both of which requires **Line Justification** (LJ), i.e., finding input combinations that force certain signals to their desired values
- Notations:
 - **1/0 is denoted as D**, meaning that good-value is 1 while faulty value is 0
 - Similarly, **0/1 is denoted as D'**
 - Both D and D' are called **fault effects** (FE)

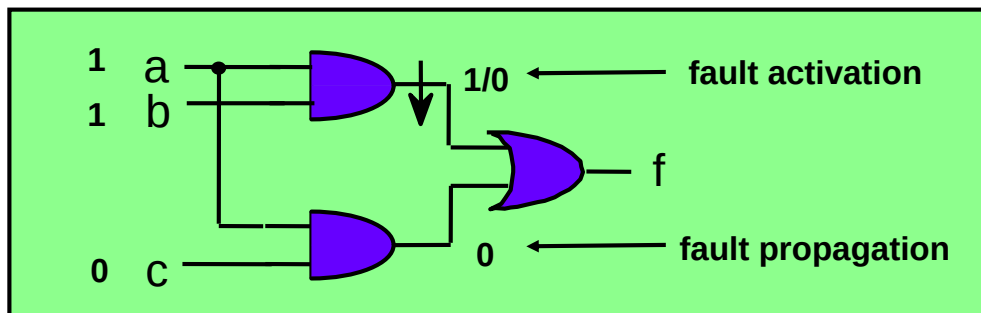


73

Structural Test Generation

D-Algorithm

- **Fault activation**
 - Setting the faulty signal to either 0 or 1 is a **Line Justification** problem
- **Fault propagation**
 1. select a path to a PO → **decisions**
 2. once the path is selected → a set of line justification (LJ) problems are to be solved
- **Line justification**
 - Involves **decisions** or **implications**
 - Incorrect decisions: need **backtracking**

 
To justify $c=1 \rightarrow a=1$ and $b=1$ (implication)
To justify $c=0 \rightarrow a=0$ **or** $b=0$ (decision)



74

Structural Test Generation

D-Algorithm: Fault Propagation

 


- **Fault activation**
 - $G1=0 \rightarrow \{a=1, b=1, c=1\} \rightarrow \{G3=0\}$
- **Fault propagation**: through G5 or G6
- **Decision through G5**:
 - $G2=1 \rightarrow \{d=0, a=0\} \rightarrow$ inconsistency at a $\rightarrow$ backtrack !!
- **Decision through G6**:
 - $\rightarrow G4=1 \rightarrow e=0 \rightarrow$ done !! The resulting test is (111x0)

D-frontiers: are the gates whose output value is x, while one or more inputs are D or D'. For example, initially, the D-frontier is { G5, G6 }.

75

Structural Test Generation

D-Algorithm: Line Justification

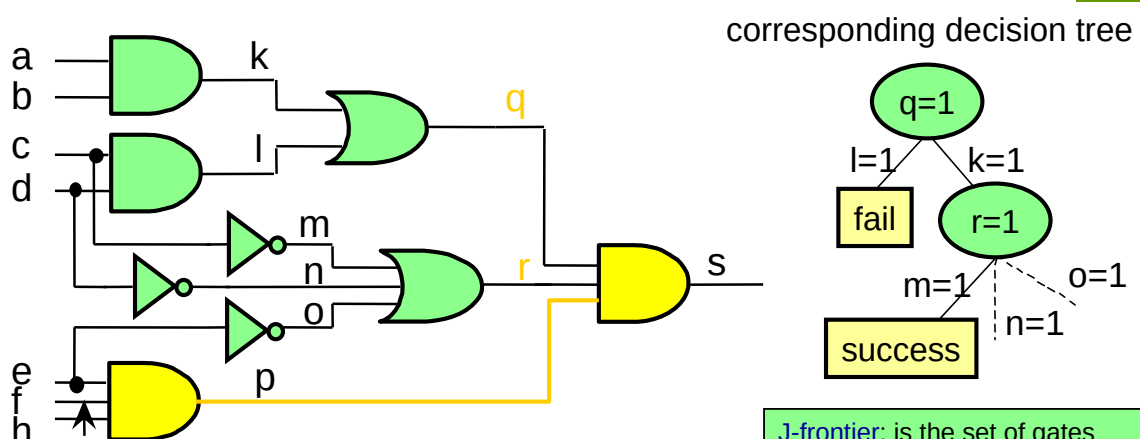

- **FA** $\rightarrow$ set h to 0
- **FP** $\rightarrow e=1, f=1 (\rightarrow o=0)$; **FP** $\rightarrow q=1, r=1$
- **To justify** $q=1 \rightarrow l=1$ or $k=1$
- **Decision**: $l=1 \rightarrow c=1, d=1 \rightarrow m=0, n=0 \rightarrow r=0 \rightarrow$ inconsistency at r $\rightarrow$ backtrack !
- **Decision**: $k=1 \rightarrow a=1, b=1$
- **To justify** $r=1 \rightarrow m=1$ or $n=1 (\rightarrow c=0$ or $d=0) \rightarrow$ Done ! (J-frontier is ϕ)

J-frontier: is the set of gates whose output value is known (i.e., 0 or 1), but is not implied by its input values.
Ex: initially, J-frontier is {q=1, r=1}

76

Test Generation

- ❑ A branch-and-bound search
- ❑ Every decision point is a **branching** point
- ❑ If a set of decisions lead to a **conflict**, a **backtrack** is taken to explore other decisions
- ❑ **A test is found** when
 1. fault effect is propagated to a PO, and
 2. all internal lines are justified
- ❑ No test is found after all possible decisions are tried → Then, target fault is **undetectable**
- ❑ Since the search is **exhaustive**, it will find a test if one exists

For a combinational circuit, an **undetectable** fault is also a **redundant** fault
→ Can be used to simplify circuit.


77

Implication

- ❑ Implication
 - Compute the values that can be uniquely determined
 - ❑ **Local implication**: propagation of values from one line to its immediate successors or predecessors
 - ❑ **Global implication**: the propagation involving a larger area of the circuit and re-convergent fanout
- ❑ Maximum implication principle
 - Perform as many implications as possible
 - It helps to either reduce the number of problems that need decisions or to **reach an inconsistency sooner**


78

Forward Implication

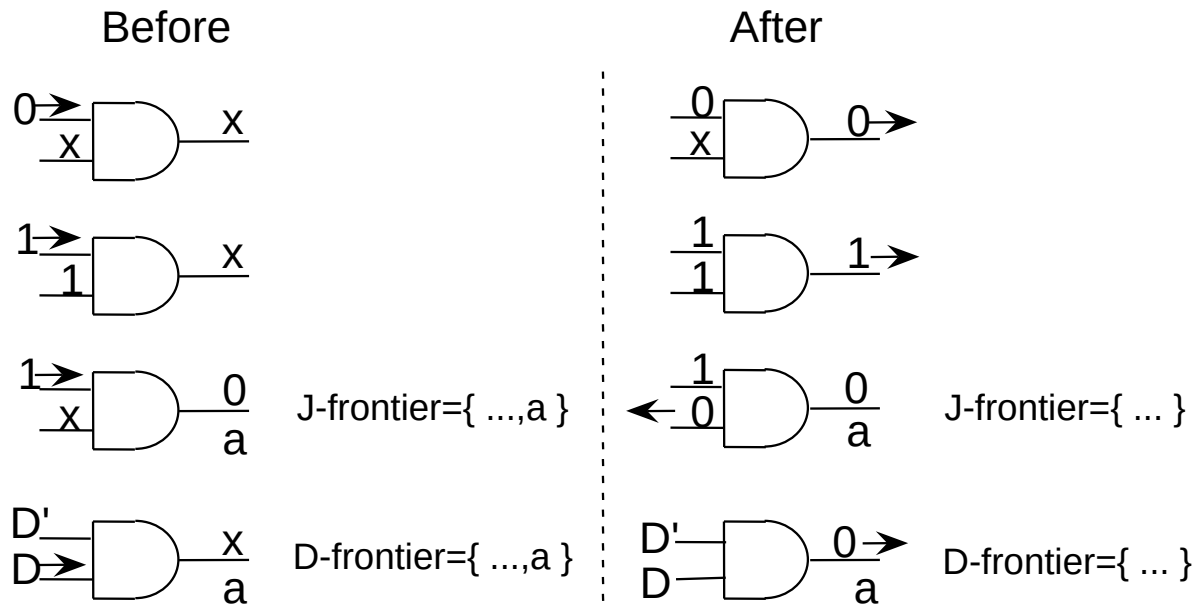

79

Backward Implication

 


80

D-Algorithm (1/4)

Example

- Five logic values {0, 1, x, D, D'}

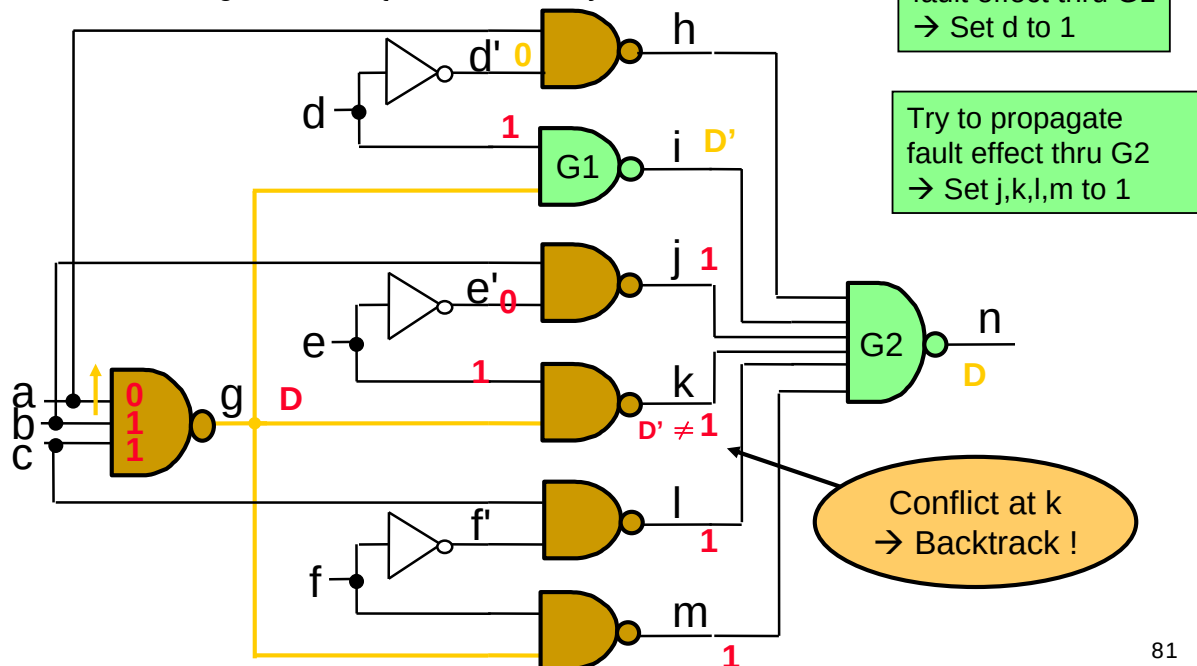


81

D-Algorithm (2/4)

Example

- Five logic values {0, 1, x, D, D'}

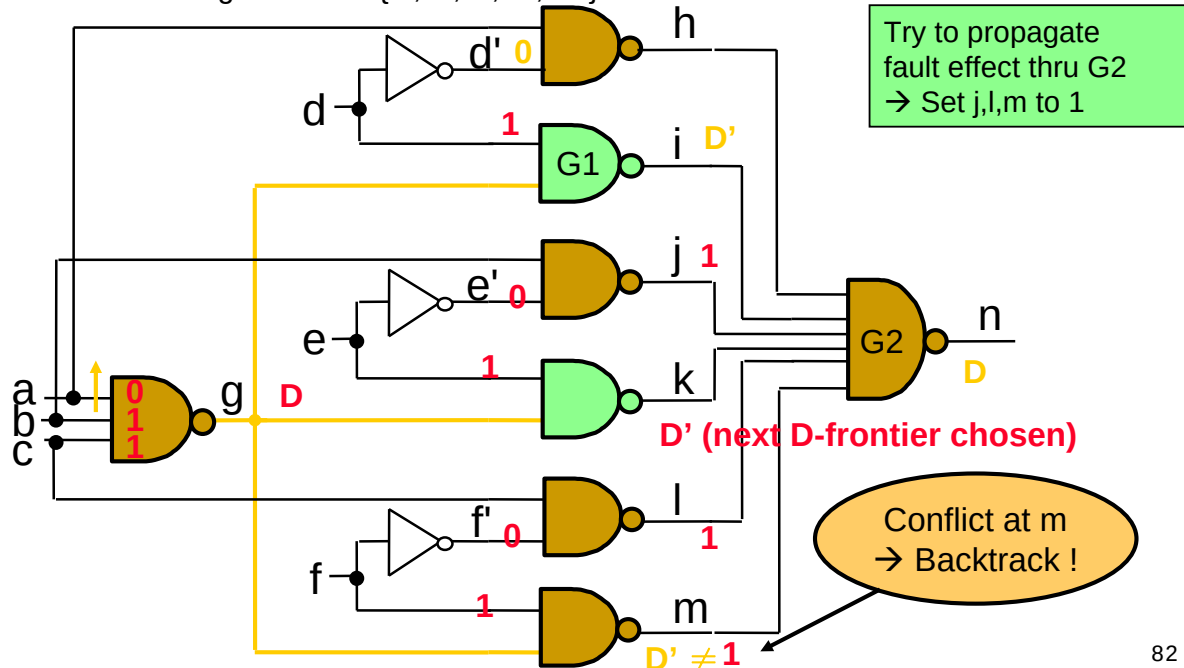


82

D-Algorithm (3/4)

Example

- Five logic values {0, 1, x, D, D'}

 

83

D-Algorithm (4/4)

Decision	Implication	Comments
	a=0 h=1 b=1 c=1 g=D	Active the fault Unique D-drive
d=1	i=D' d'=0	Propagate via i
j=1 k=1 l=1 m=1	n=D e'=0 e=1 k=D'	Propagate via n Contradiction


e=1	k=D' e'=0 j=1	Propagate via k
l=1 m=1	n=D f'=0 f=1 m=D'	Propagate via n Contradiction
f=1	m=D' f'=0 l=1 n=D	Propagate via m

84

Decision Tree on D-Frontier

□ The decision tree

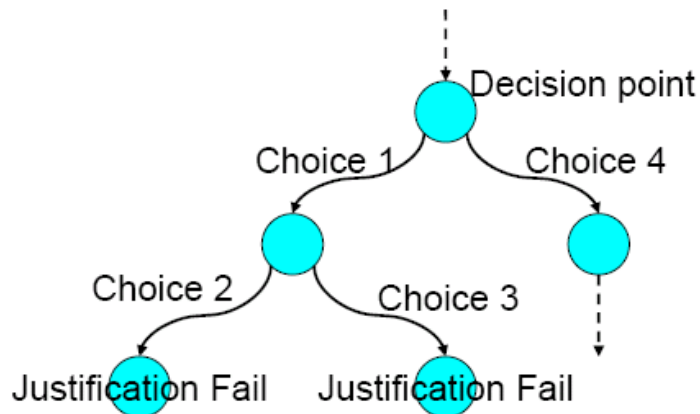- Node → D-frontier
- Branch → decision taken
- A **Depth-First-Search** (DFS) strategy is often used



85

PODEM Algorithm

□ PODEM: Path-Oriented DEcision Making

□ Fault Activation (FA) and Propagation (FP)

- lead to sets of Line Justification (LJ) problems. The LJ problems can be solved via value assignments.

□ In D-algorithm

- TG is done through **indirect signal assignment** for FA, FP, and LJ, that eventually maps into **assignments at PI's**
- The **decision points** are at **internal lines**
- The worst-case number of **backtracks is exponential** in terms of the number of decision points (e.g., at least 2^k for k decision nodes)

□ In PODEM

- The test generation is done through a sequence of **direct assignments at PI's**
- Decision points are at PIs, thus the number of **backtracking** might be **fewer**

86

PODEM Algorithm


Search Space of PODEM

- Complete search space

- A binary tree with 2^n leaf nodes, where n is the number of PIs

- Fast test generation

 - Need to find a path leading to a SUCCESS terminal quickly



87

PODEM Algorithm

Objective and Backtrace

- PODEM

- Also aims at establishing a sensitization path based on **fault activation and propagation** like D-algorithm
 - Instead of justifying the signal values required for sensitizing the selected path, objectives are setup to guide the **decision process at PIs**

- Objective

- is a **signal-value pair** (w, v_w)

- Backtrace

- Backtrace **maps a desired objective into a PI assignment** that is likely to contribute to the achievement of the objective
 - Is a process that traverses the circuit back from the objective signal to PIs
 - The result is a **PI signal-value pair** (x, v_x)
 - No signal value is actually assigned during backtrace (toward PI) !**

88

PODEM Algorithm

Objective

□ Objective routine involves

- selection of a **D-frontier**, G
- selection of an **unspecified input gate** of G

```
Objective() {  
    /* The target fault is w s-a-v */  
    /* Let variable obj be a signal-value pair */  
    if (the value of w is x) obj = ( w, v' );  
    else {  
        select a gate (G) from the D-frontier;  
        select an input (j) of G with value x;  
        c = controlling value of G;  
        obj = (j, c');  
    }  
    return (obj);  
}
```

← fault activation

← fault propagation

89

PODEM Algorithm

Backtrace

□ Backtrace routine involves

- finding an all-x path from objective site to a PI, i.e., every signal in this path has value x


```
Backtrace(w, v_w) {  
    /* Maps objective into a PI assignment */  
    G = w; /* objective node */  
    v = v_w; /* objective value */  
    while (G is a gate output) { /* not reached PI yet */  
        inv = inversion of G;  
        select an input (j) of G with value x;  
        G = j; /* new objective node */  
        v = v  $\oplus$  inv; /* new objective value */  
    }  
    /* G is a PI */ return (G, v);  
}
```

90

PODEM Algorithm

PI Assignment

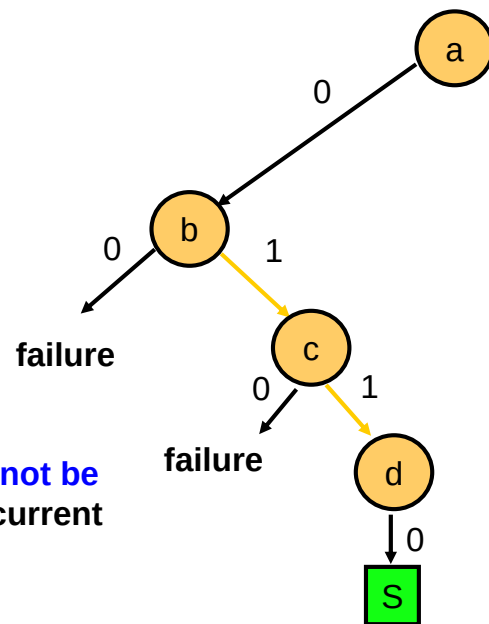PIs: { a, b, c, d }
 Current Assignments: { a=0 }
 Decision: b=0 → objective fails
 Reverse decision: b=1
 Decision: c=0 → objective fails
 Reverse decision: c=1
 Decision: d=0



Failure means **fault effect cannot be propagated** to any PO under current PI assignments

91

PODEM Algorithm

PODEM () /* using depth-first-search */

begin

 If(error at PO) return(SUCCESS);

 If(test not possible) return(FAILURE);

 (k, v_k) = Objective(); /* choose a line to be justified */

 (j, v_j) = Backtrace(k, v_k); /* choose the PI to be assigned */

 Implied (j, v_j); /* make a decision */

 If (PODEM() == SUCCESS) return (SUCCESS);

 Implied (j, v_j); /* reverse decision */

 If (PODEM() == SUCCESS) return(SUCCESS);

 Implied (j, x);


 Return (FAILURE);

end

92

PODEM Algorithm (1/4)


Example

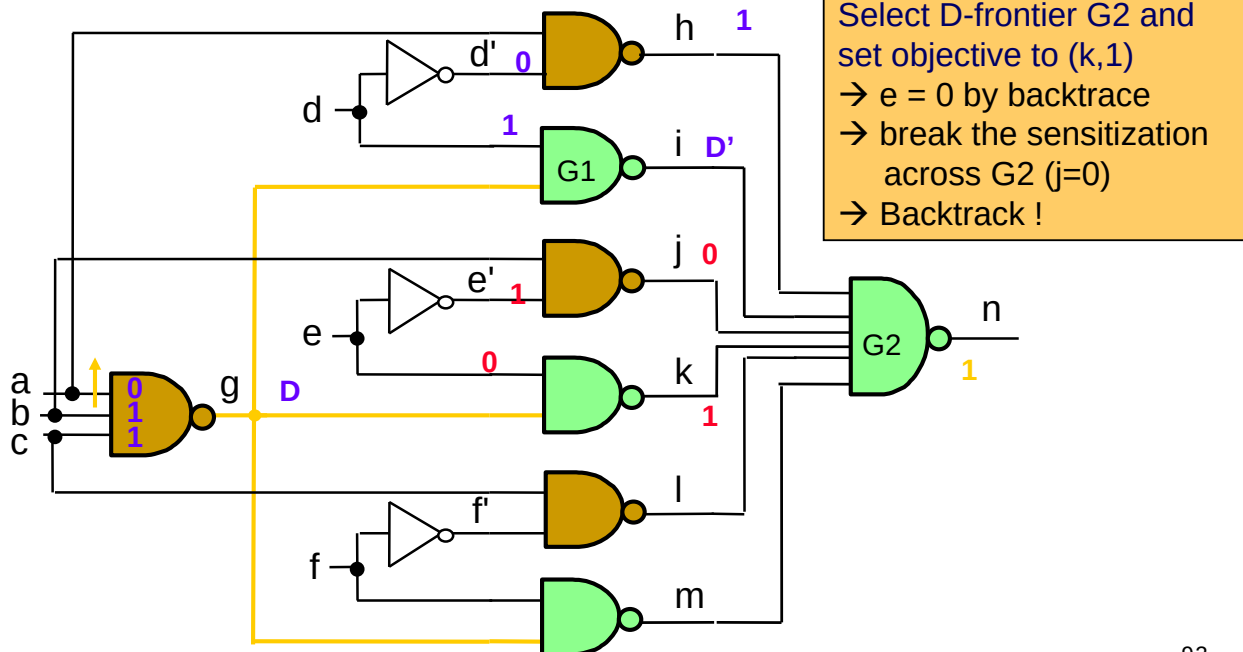

93

PODEM Algorithm (2/4)


Example

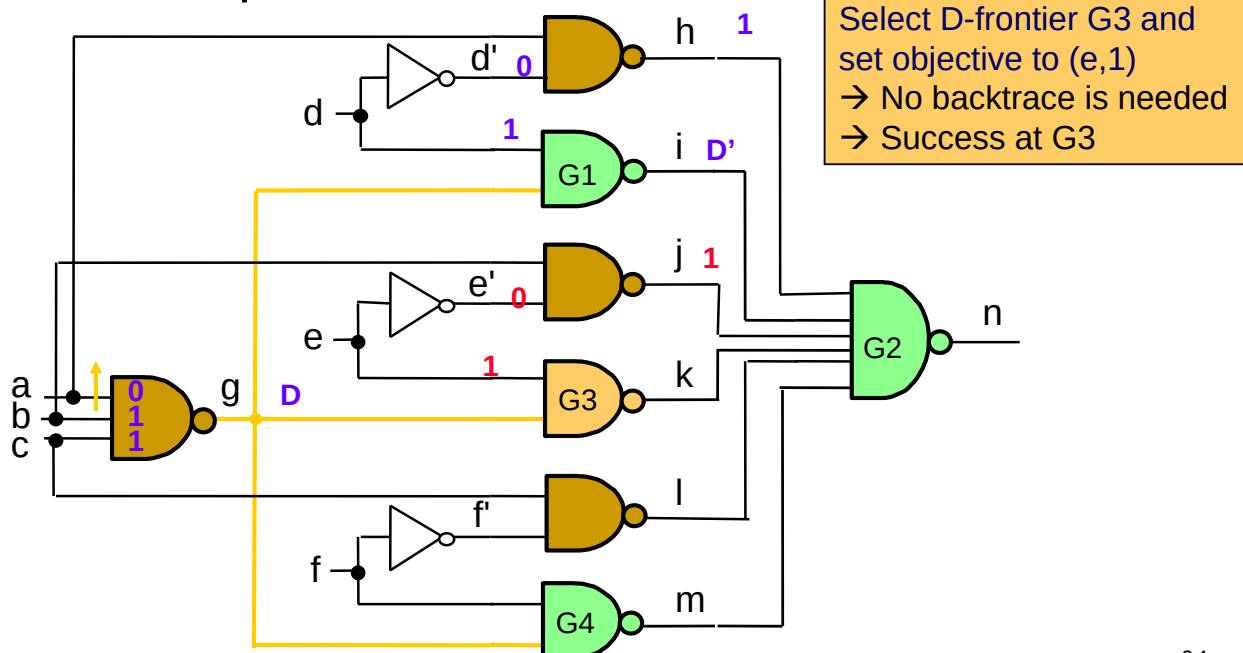

94

PODEM Algorithm (3/4)


Example

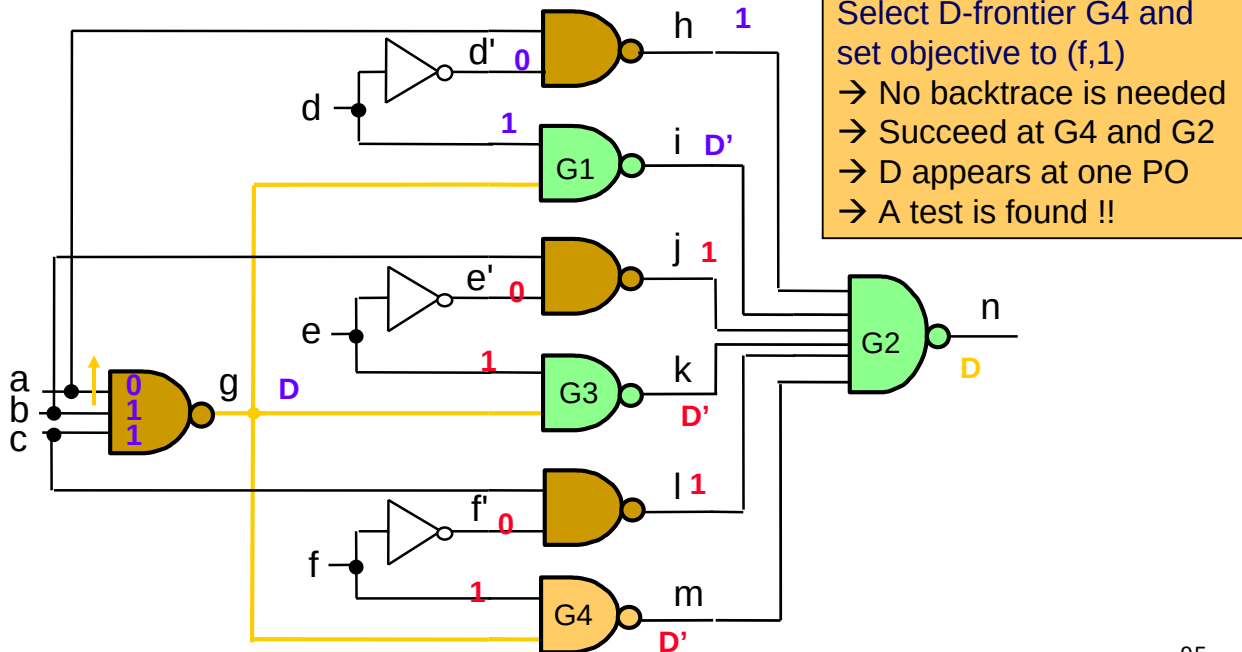

95

PODEM Algorithm (4/4)

Objective	PI assignment	Implications	D-frontier	Comments
a=0	a=0	h=1	g	
b=1	b=1		g	
c=1	c=1	g=D	i,k,m	
d=1	d=1	d'=0		
		i=D'	k,m,n	
k=1	e=0	e'=1 j=0 k=1 n=1	m	no solutions! → backtrack flip PI assignment
	e=1	e'=0 j=1 k=D'	m,n	
l=1	f=1	f'=0 l=1 m=D' n=D		

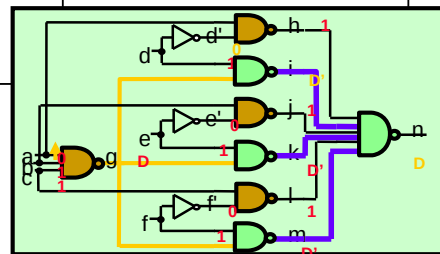


96

PODEM Algorithm

Decision Tree

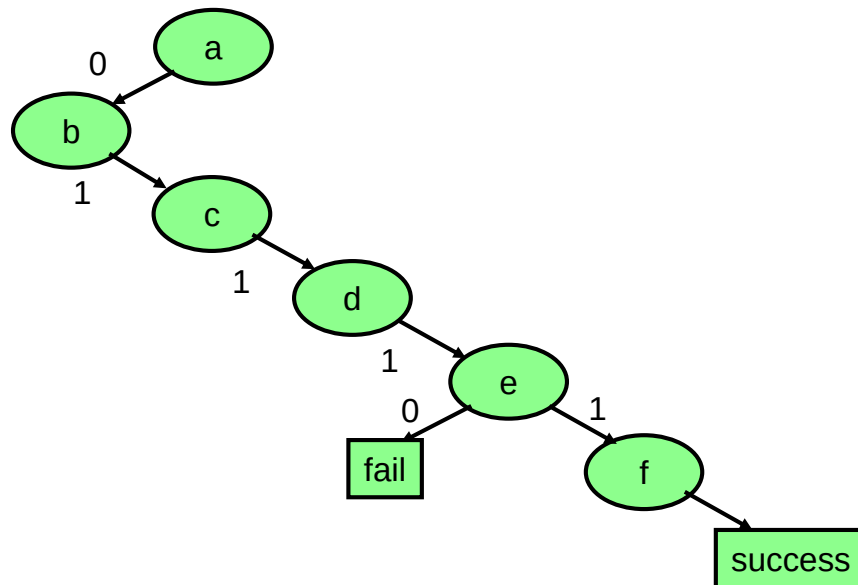- **Decision node:**
PI selected through backtrace for value assignment
- **Branch:**
value assignment to the selected PI



97

Termination Conditions

- **D-algorithm**
 - **Success:**
 - (1) Fault effect at an output (D-frontier may not be empty)
 - (2) J-frontier is empty
 - **Failure:**
 - (1) D-frontier is empty (all possible paths are false)
 - (2) J-frontier is not empty
- **PODEM**
 - **Success:**
 - Fault effect seen at an output
 - **Failure:**
 - Every PI assignment leads to failure, in which D-frontier is empty while fault has been activated

98

PODEM Overview

□ PODEM

- examines all possible input patterns **implicitly** but **exhaustively** (branch-and-bound) for finding a test
- **complete** like D-algorithm (i.e., will find a test if exists)

□ Other key features

- No J-frontier, since there are no values that require justification
- No consistency check, as conflicts can never occur
- No backward implication, because values are propagated only forward
- Backtracking is implicitly done by simulation rather than by an explicit and **time-consuming save/restore process**
- Experiments show that PODEM is **generally faster** than D-algorithm

99

Outline

□ Fault Modeling

□ Fault Simulation

□ Automatic Test Pattern Generation

□ Design for Testability

100

Why DFT ?

- Direct testing is way too difficult !
 - Large number of FFs
 - Embedded memory blocks
 - Embedded analog blocks

101

Design for Testability

- Definition
 - Design for testability (DFT) refers to those design techniques that make test generation and testing cost-effective
- DFT methods
 - Ad-hoc methods, full and partial scan, built-in self-test (BIST), boundary scan
- Cost of DFT
 - Pin count, area, performance, design-time, test-time, etc.

102

Important Factors

□ Controllability

- Measure the ease of controlling a line

□ Observability

- Measure the ease of observing a line at PO

□ DFT deals with ways of improving

- Controllability and observability

103

Test Point Insertion


□ Employ test points to enhance **controllability** and **observability**

- CP: Control Points

- Primary inputs used to enhance controllability


- OP: Observability Points

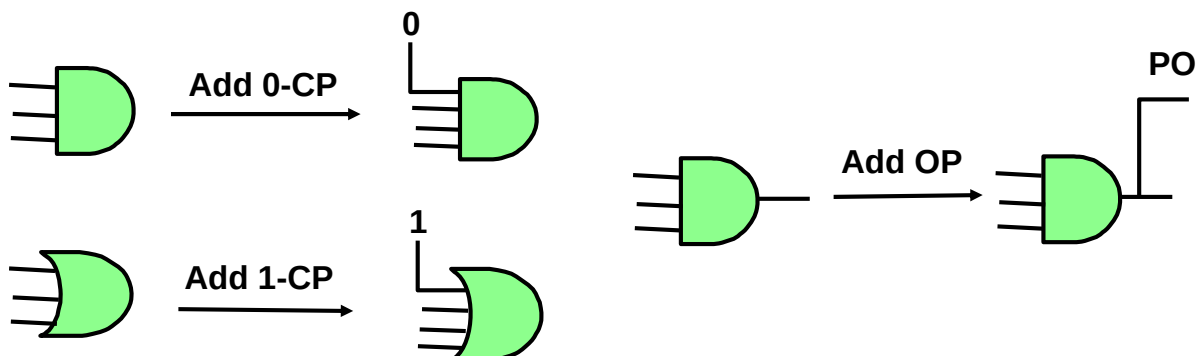- Primary outputs used to enhance observability



104

Control Point Insertion

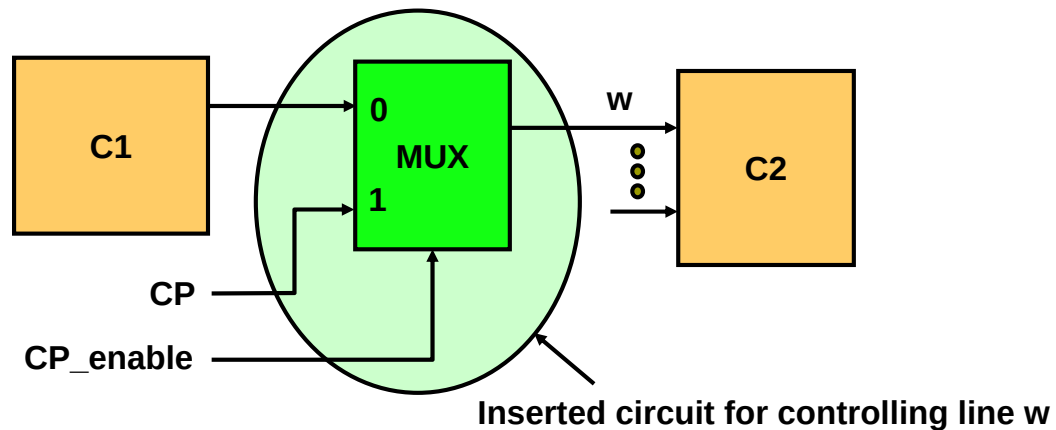

- Normal operation:
When CP_enable = 0
- Inject 0:
Set CP_enable = 1 and CP = 0
- Inject 1:
Set CP_enable = 1 and CP = 1

105

Control Point Selection

- Goal
 - **Controllability** of the fanout-cone of the added point is improved
- Common selections
 - Control, address, and data buses
 - Enable/hold inputs
 - Enable and read/write inputs to memory
 - Clock and preset/clear signals of flip-flops
 - Data select inputs to multiplexers and demultiplexers

106

Observation Point Selection

□ Goal

- **Observability** of the transitive fanins of the added point is improved

□ Common choice


- Stem lines with **more fanouts**
- Global feedback paths
- Redundant signal lines
- Output of logic devices having many inputs
 - MUX, XOR trees
- **Output from state devices**
- Address, control and data buses

107

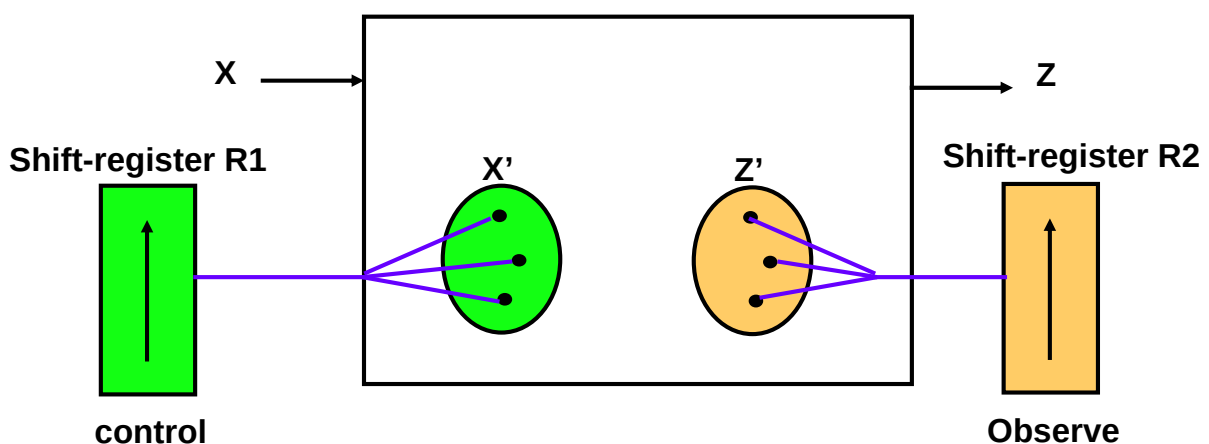Problems with Test Point Insertion

□ Large number of I/O pins

- Can be resolved by adding MUXs to reduce the number of I/O pins, or by adding shift-registers to impose CP values



108

What Is Scan ?

□ Objective

- To provide controllability and observability at **internal state variables** for testing

□ Method


- Add **test mode** control signal(s) to circuit
- Connect **flip-flops to form shift registers** in test mode
- Make inputs/outputs of the flip-flops in the shift register controllable and observable

□ Types

- Internal scan
 - Full scan, partial scan, random access
- Boundary scan


109

Scan Concept

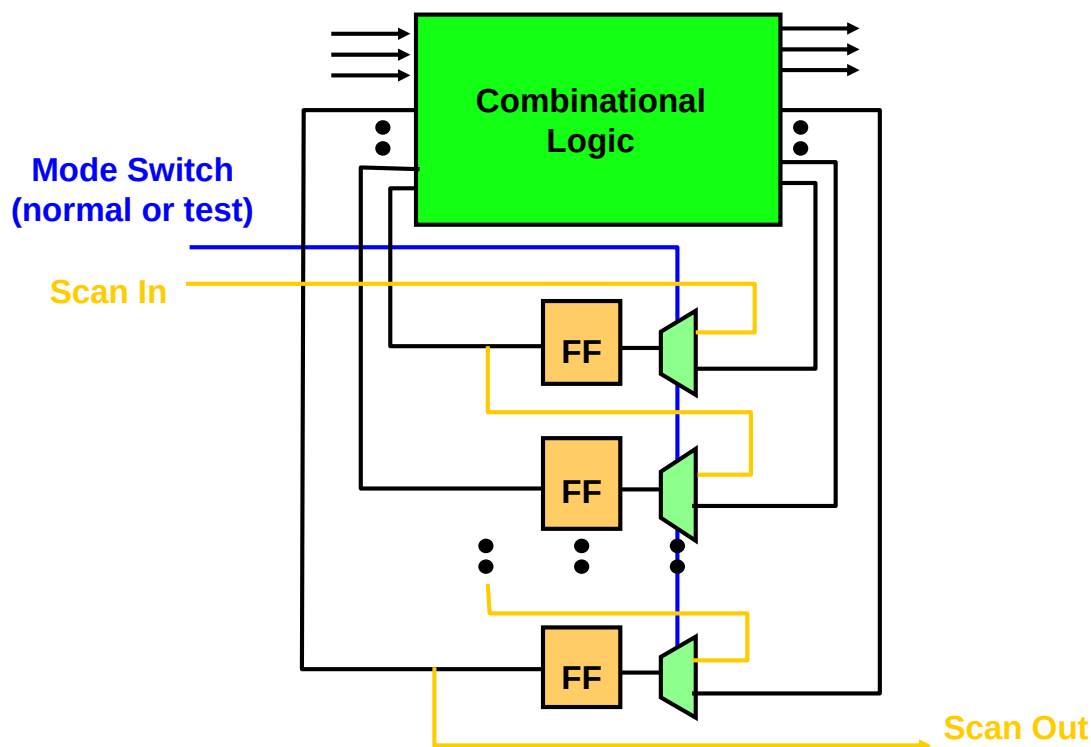

110


Logic Design before Scan Insertion

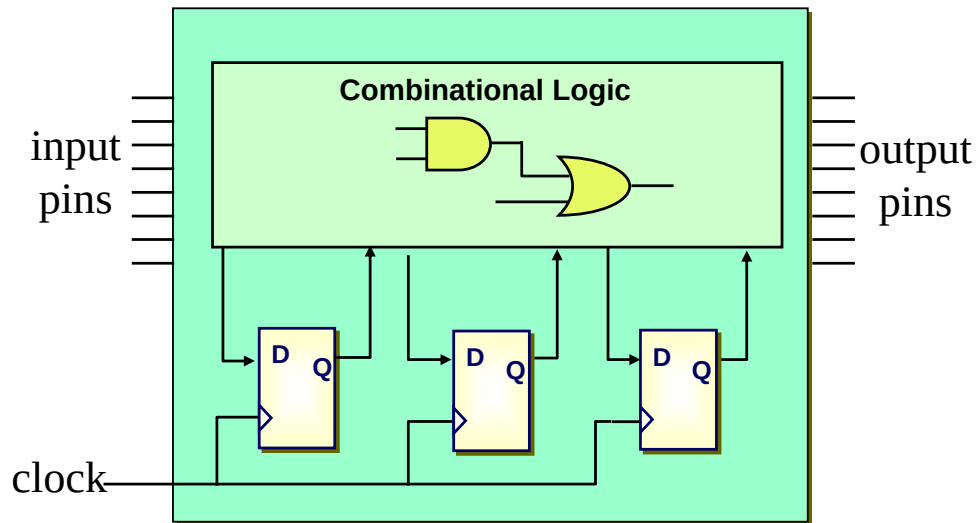

Sequential ATPG is extremely difficult:
due to the lack of controllability and observability at flip-flops.

111

Logic Design after Scan Insertion

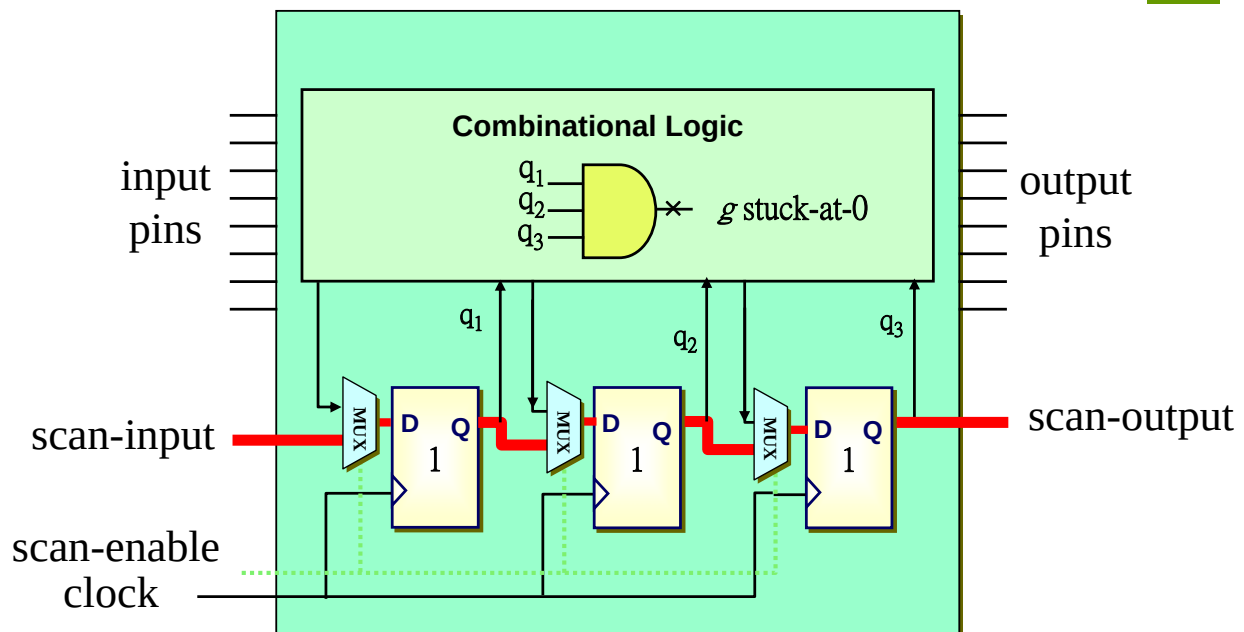


Scan Chain provides an easy access to flip-flops
→ Pattern generation is much easier !!

112

Scan Insertion

Example

3-stage counter

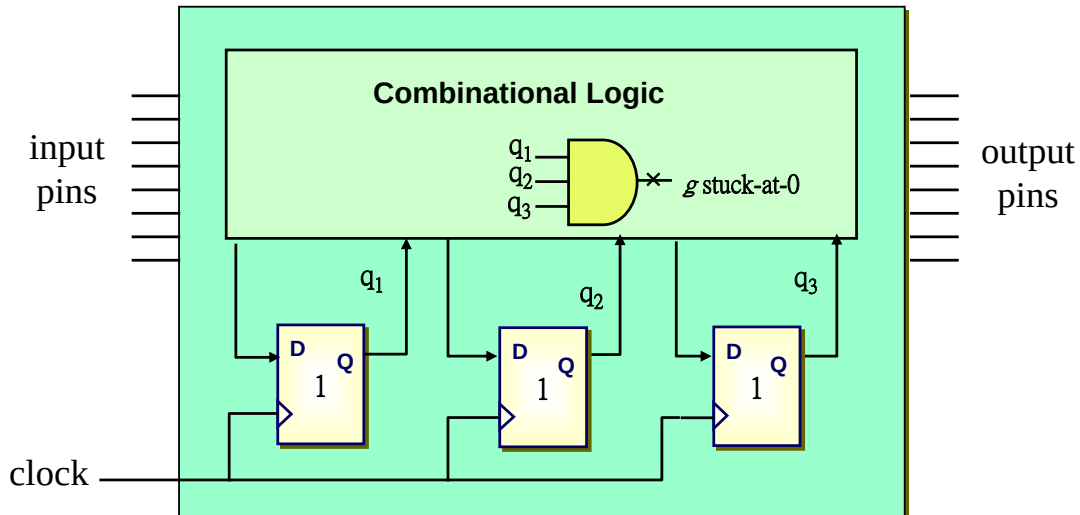

It takes 8 clock cycles to set the flip-flops to be (1, 1, 1), for detecting the target fault g stuck-at-0 fault (2^{20} cycles for a 20-stage counter !)

113

Overhead of Scan Design

Case study

- #CMOS gates = 2000
- Fraction of flip-flops = 0.478
- Fraction of normal routing = 0.471

Scan implementation	Predicted overhead	Actual area overhead	Normalized operating frequency
None	0	0	1.0
Hierarchical	14.05%	16.93%	0.87
Optimized	14.05%	11.9%	0.91

114

Full Scan Problems

□ Problems

- Area overhead
- Possible performance degradation
- High test application time
- Power dissipation


□ Features of commercial tools

- Scan-rule violation check (e.g., DFT rule check)
- Scan insertion (convert a FF to its scan version)
- ATPG (both combinational and sequential)
- Scan chain reordering after layout

115

Scan-Chain Reordering

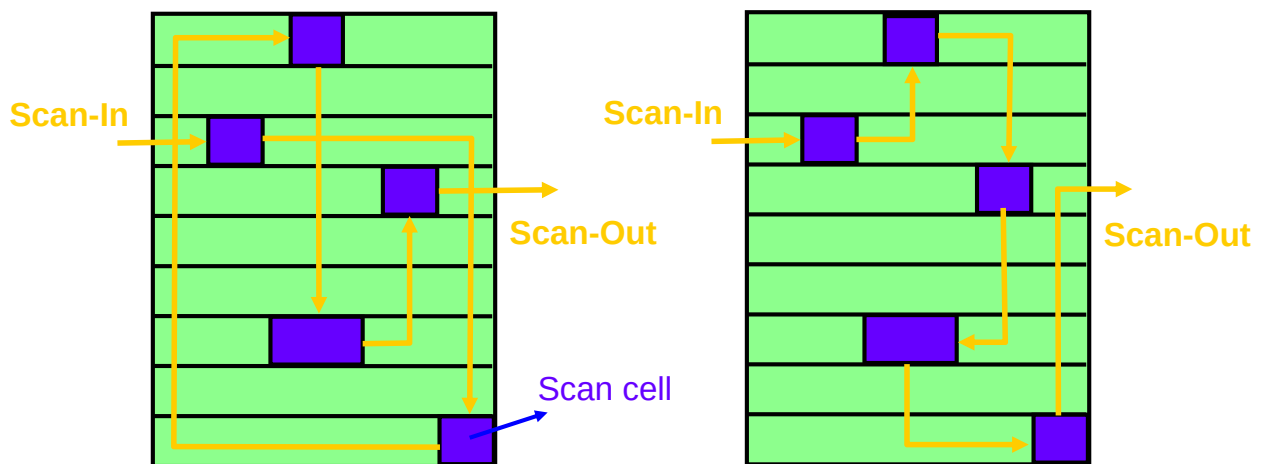- Scan-chain order is often decided at gate-level **without knowing the cell placement**
- Scan-chain consumes a lot of **routing resources**, and could be minimized by **re-ordering the flip-flops** in the chain after layout is done



Layout of a cell-based design

A better scan-chain order

116

Partial Scan

□ Basic idea

- Select a **subset of flip-flops** for scan
- Lower overhead (area and speed)
- Relaxed design rules

□ Cycle-breaking technique


- **Cheng & Agrawal**, IEEE Trans. On Computers, April 1990
- Select scan flip-flops to **simplify sequential ATPG**
- Overhead is about **25% off** than full scan

□ Timing-driven partial scan

- **Jou & Cheng**, ICCAD, Nov. 1991
- Allow optimization of area, timing, and testability simultaneously

117


Full Scan vs. Partial Scan

 

scan time	longer	shorter
hardware overhead	more	less
fault coverage	~100%	unpredictable
ease-of-use	easier	harder

118

Area Overhead vs. Test Effort

 

119

Conclusions

- Testing
 - Conducted after manufacturing
 - Must be considered during the design process
- Major fault models
 - Stuck-at, bridging, stuck-open, delay fault, ...
- Major tools needed
 - Design-for-Testability
 - By scan chain insertion or built-in self-test
 - Fault simulation
 - ATPG
- Other Applications in CAD
 - ATPG is a way of Boolean reasoning and is applicable to many logic-domain CAD problems

120