

CHAPTER 14 SIGNAL GENERATORS AND WAVEFORM-SHAPING CIRCUITS

Chapter Outline

- 14.1 Basic Principles of Sinusoidal Oscillators
- 14.2 Op Amp-RC Oscillators
- 14.3 LC and Crystal Oscillators
- 14.4 Bistable Multivibrators
- 14.5 Generation of Square and Triangular Waveforms using Astable Multivibrators
- 14.6 Generation of a Standardized Pulse-The Monostable Multivibrators
- 14.7 Integrated-Circuit Timers
- 14.8 Nonlinear Waveform-Shaping Circuits

14.1 Basic Principles of Sinusoidal Oscillators

Types of Oscillators

□ Linear oscillator:

- Employs a positive feedback loop consisting of an amplifier and a frequency-selective network
- Some form of nonlinearity has to be employed to provide control of the amplitude of the output

□ Nonlinear oscillator:

- Generates square, triangular, pulse waveforms
- Employs multivibrators: bistable, astable and monostable


The Oscillator Feedback Loop and Oscillation Criterion

□ Positive feedback loop analysis:


$$A_f(s) \equiv \frac{x_o}{x_i} = \frac{A(s)}{1 - A(s)\beta(s)} = \frac{A(s)}{1 - L(s)}, \text{ where } L(s) \text{ is the loop gain}$$

□ Characteristic equation: $1 - L(s) = 0$

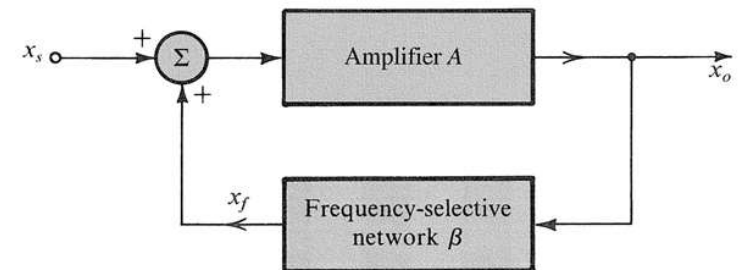
→ Find poles of the closed-loop system by solving $L(s) = 1$




Underdamped

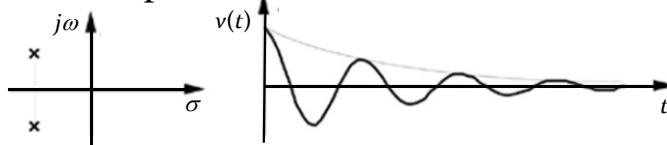

Oscillation

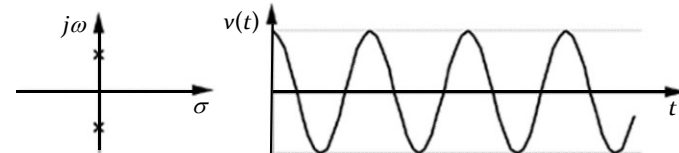

Unstable

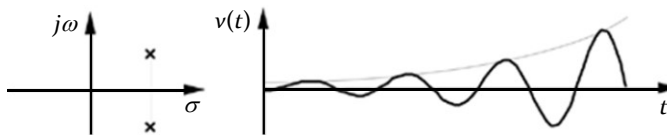

□ Barkhausen criterion:

- The phase of loop gain should be zero at ω_o
- The magnitude of the loop gain should be unity at ω_o
- The characteristic equation has roots at $s = \pm j\omega_o$

$$L(j\omega_o) = A(j\omega_o)\beta(j\omega_o) = 1$$

$$\rightarrow |L(j\omega_o)| = 1$$

$$\rightarrow \angle L(j\omega_o) = 0^\circ$$

□ Stability of oscillation frequency:

- ω_o is determined solely by the phase characteristics
- A steep function $f(\omega)$ results in a more stable frequency


□ Stability of oscillation frequency:

- Oscillation: loop gain $A\beta = 1$
- Growing output: loop gain $A\beta > 1$
- Decaying output: loop gain $A\beta < 1$

Nonlinear Amplitude Control

□ Oscillation mechanism:

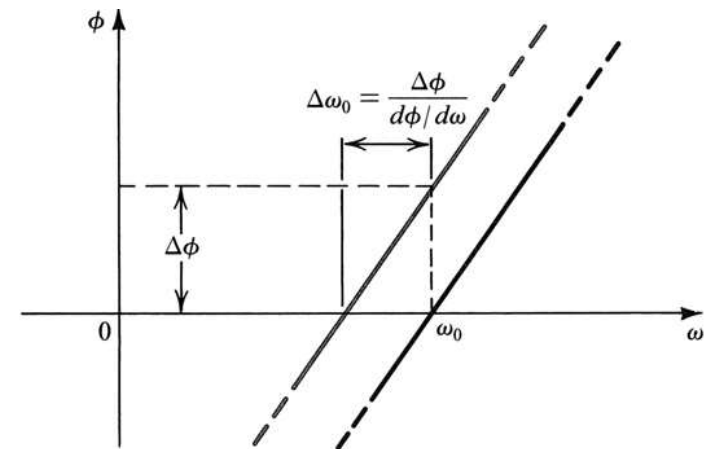- Initiating oscillation: loop gain slightly larger than unity (poles in RHP)
- Gain control: nonlinear network reduces loop gain to unity (poles on $j\omega$ -axis)



Limiter Circuits for Amplitude Control

□ For small output amplitude (D_1 off, D_2 off)

→ incremental gain (slope) = $-R_f/R_1$

□ For large negative output swing (D_1 on, D_2 off)

$$v_A = \frac{R_3 V + R_2 v_O}{R_2 + R_3} = -V_D \rightarrow v_O = -\left(\frac{R_3}{R_2} V + \frac{R_2 + R_3}{R_2} V_D\right) = L_-$$

$$\begin{cases} v_I / R_1 + v_O / R_f = I_{D1} \\ (V + V_D) / R_2 + (v_O + V_D) / R_3 + I_{D1} = 0 \end{cases}$$

$$v_O = -\frac{R_f \parallel R_3}{R_1} v_I - \frac{R_f \parallel R_3}{R_2} V - \frac{R_f \parallel R_3}{R_2 \parallel R_3} V_D$$

→ incremental gain (slope) = $-(R_f \parallel R_4)/R_1$



□ For large positive output swing (D_1 off, D_2 on)

$$v_B = \frac{-R_4 V + R_5 v_O}{R_4 + R_5} = V_D \rightarrow v_O = \frac{R_4}{R_5} V + \frac{R_4 + R_5}{R_5} V_D = L_+$$

$$\begin{cases} v_I / R_1 + v_O / R_f + I_{D2} = 0 \\ (v_O - V_D) / R_4 + (-V - V_D) / R_5 = I_{D2} \end{cases}$$

$$v_O = -\frac{R_f \parallel R_4}{R_1} v_I + \frac{R_f \parallel R_4}{R_5} V + \frac{R_f \parallel R_4}{R_4 \parallel R_5} V_D$$

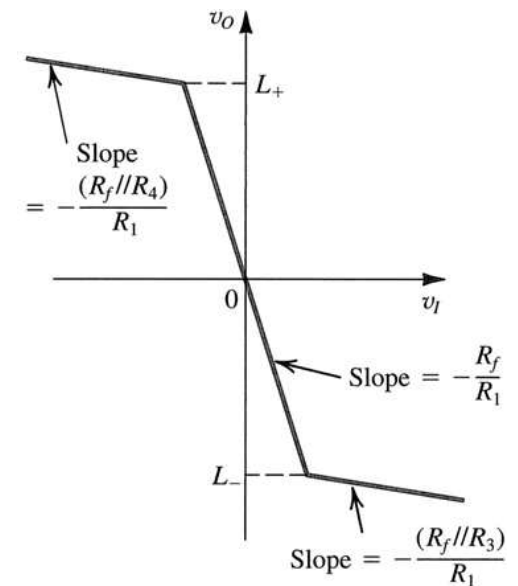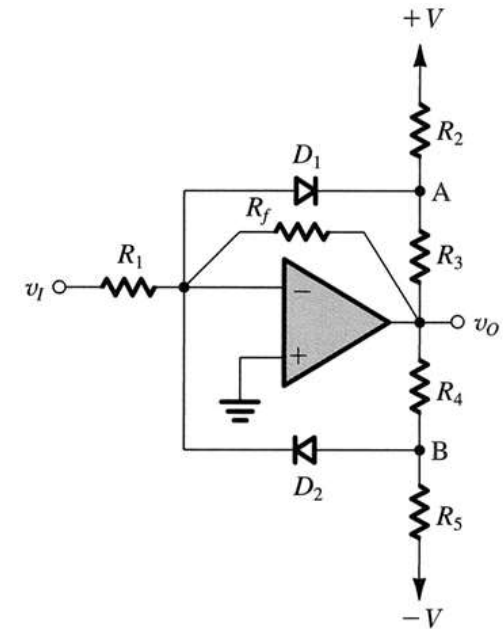→ incremental gain (slope) = $-(R_f \parallel R_3)/R_1$



14.2 OP Amp-RC Oscillator Circuits

Wien-Bridge Oscillator

□ Define the loop gain

$$A(s) = 1 + \frac{R_2}{R_1} \text{ and } \beta(s) = \frac{Z_p}{Z_p + Z_s}$$

$$L(s) = \left[1 + \frac{R_2}{R_1} \right] \frac{Z_p}{Z_p + Z_s} \rightarrow L(s) = \frac{1 + R_2 / R_1}{3 + sRC + 1/sRC}$$

□ Pole locations by solving the characteristic equation

$$L(s) = \frac{1 + R_2 / R_1}{3 + sRC + 1/sRC} = 1 \rightarrow s^2 R^2 C^2 + s \left(2 - \frac{R_2}{R_1} \right) RC + 1 = 0$$

■ Oscillation condition: $2 - R_2/R_1 = 0$ and $s = \pm j\omega_0 = \pm j/RC$

■ Start-up condition: $2 - R_2/R_1 < 0$ (poles at RHP)


□ Barkhausen criterion:

$$L(j\omega) = \frac{1 + R_2 / R_1}{3 + j\omega_0 RC + 1/j\omega_0 RC} = 1 \rightarrow (1 - \omega_0^2 R^2 C^2) + j\omega_0 \left(2 - \frac{R_2}{R_1} \right) RC = 0 \rightarrow 1 - \omega_0^2 R^2 C^2 = 0 \text{ and } 2 - \frac{R_2}{R_1} = 0$$

■ Oscillation condition: $R_2/R_1 = 2$ and $\omega_0 = 1/RC$



■ Start-up condition: $\omega_0 = RC$ and $R_2/R_1 = 2 + \Delta$

□ Limiter is used for amplitude control

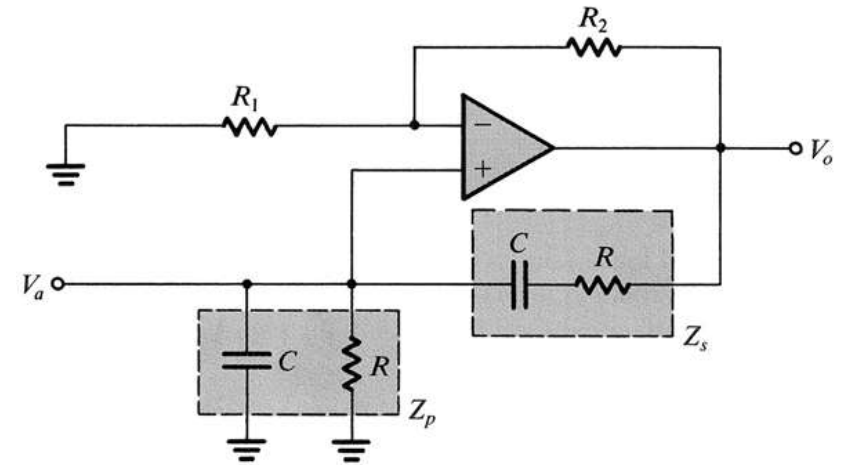



Wien-Bridge Oscillator with Amplitude Control

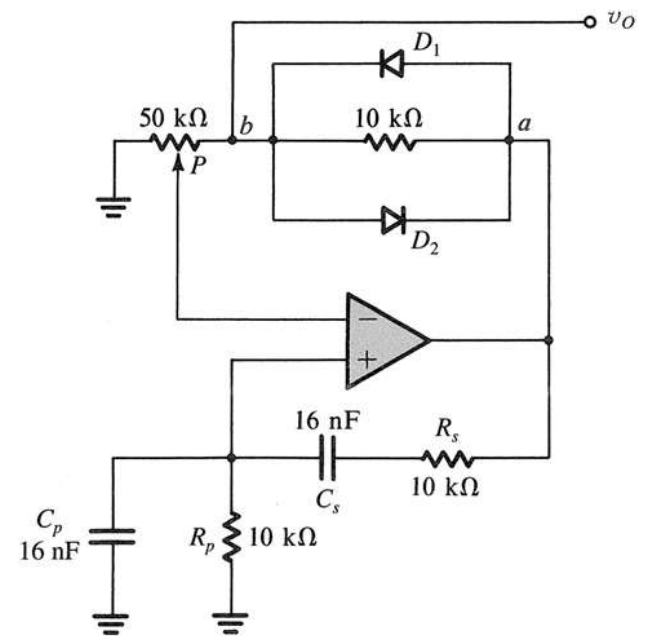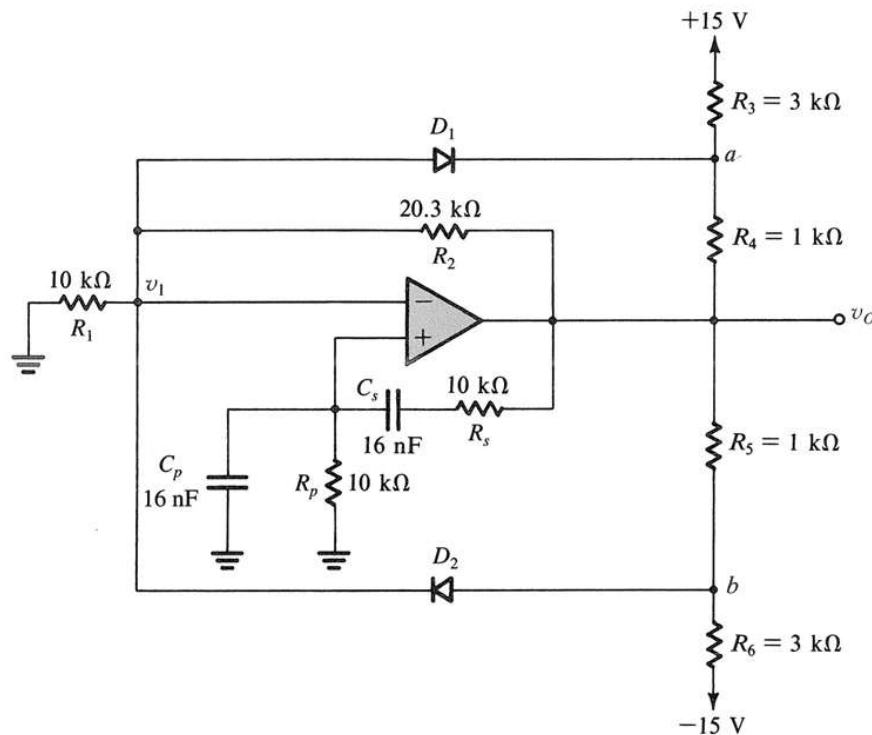- Diodes are used to limit the amplitude of the output swing
- Diodes are off with small-signal operation and can be neglected for analysis of the oscillation condition



Phase-Shift Oscillator

- ❑ The circuit oscillates at the frequency for which the phase shift of the RC network is 180°
- ❑ Only at this frequency will the total phase shift around the loop be 0° or 360°
- ❑ The minimum number of RC sections is three
- ❑ K should be equal to the inverse of the magnitude of the RC network at oscillation frequency
- ❑ Slightly higher K is used to ensure that the oscillation starts
- ❑ Limiter is used for amplitude control

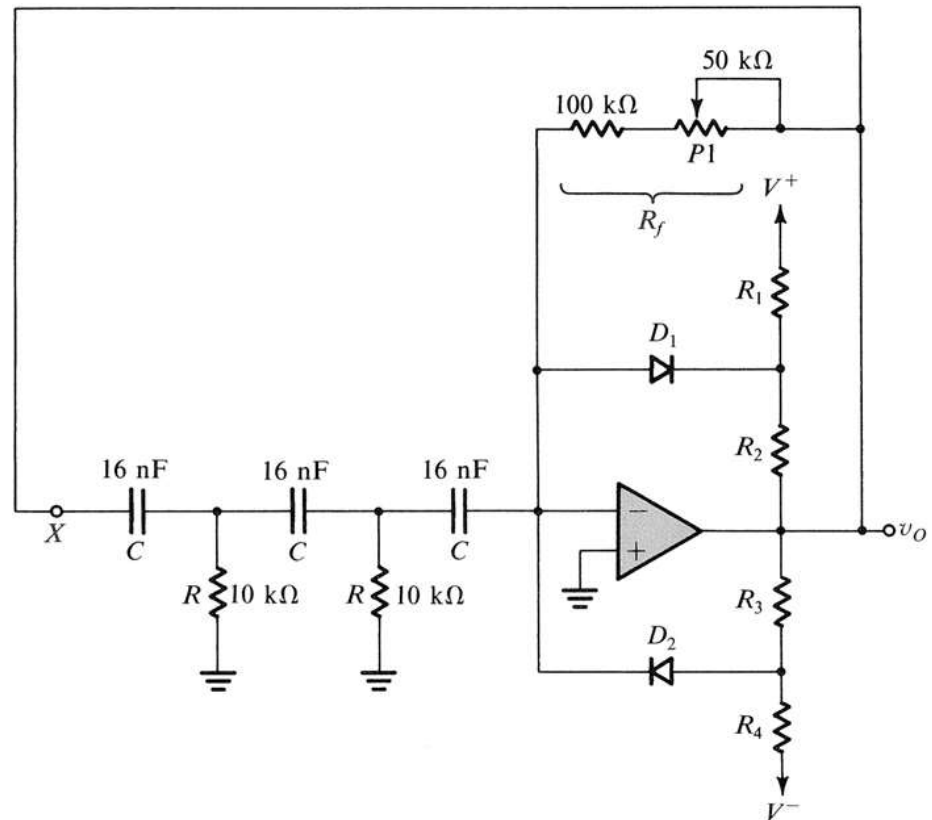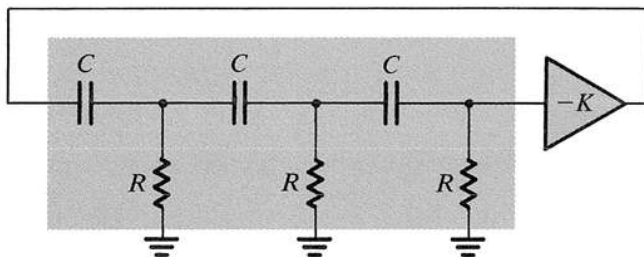

Quadrature Oscillator

❑ Based on the two-integrator loop without damping

❑ Loop gain:

$$L(s) = \frac{v_{O1}}{v_i} \times \frac{v_{O2}}{v_{O1}} = \left(-\frac{1}{sRC} \right) \frac{1}{sRC + \left(\frac{1}{2} - \frac{1}{2} \frac{2R}{R_f} \right)}$$

❑ Oscillation condition:

$$L(s) = -\frac{1}{s^2 R^2 C^2 + sRC \left(\frac{1}{2} - \frac{1}{2} \frac{2R}{R_f} \right)} = 1 \rightarrow s^2 R^2 C^2 + sRC \left(\frac{1}{2} - \frac{R}{R_f} \right) + 1 = 0$$

$$\rightarrow R_f = 2R \text{ and } s = \pm j\omega_0 = \pm j / RC$$


❑ Poles are initially located in RHP (for $R_f < 2R$)

to ensure that oscillation starts


❑ Too much positive feedback results in higher output distortion

❑ v_{O2} is purer than v_{O1} because of the filtering action provided by the second integrator on the peak-limited output of the first integrator

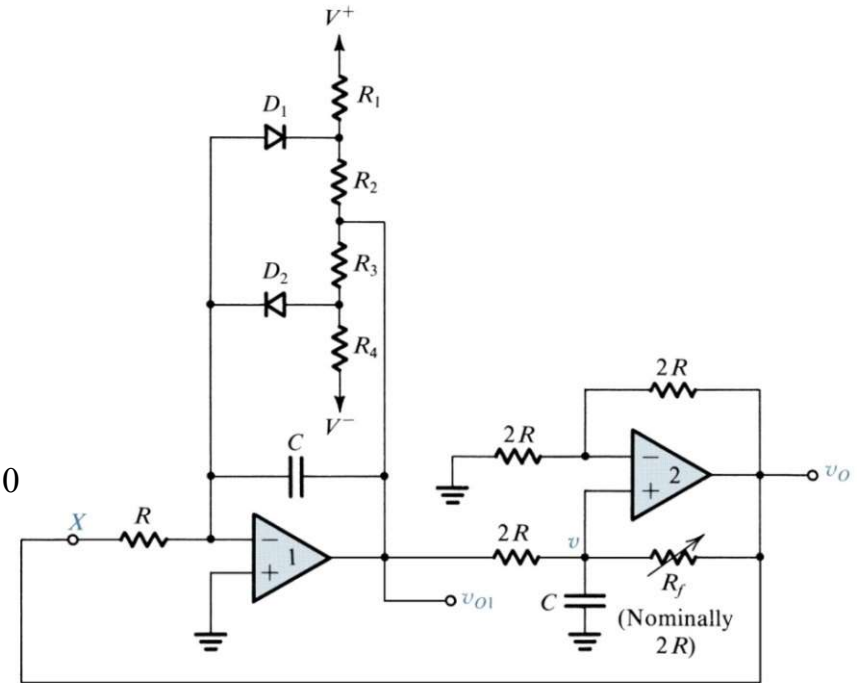❑ v_{O2} and v_{O1} have a phase difference of 90° due to the integrator function




Norton equivalent of the 1st stage

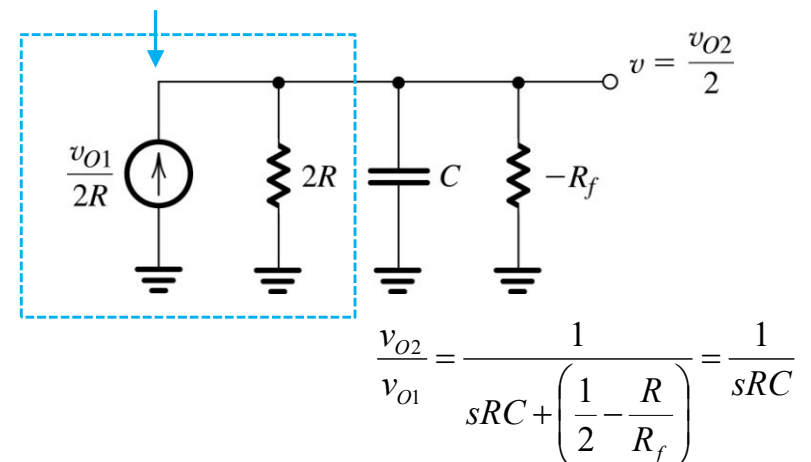


Active-Filter Tuned Oscillator

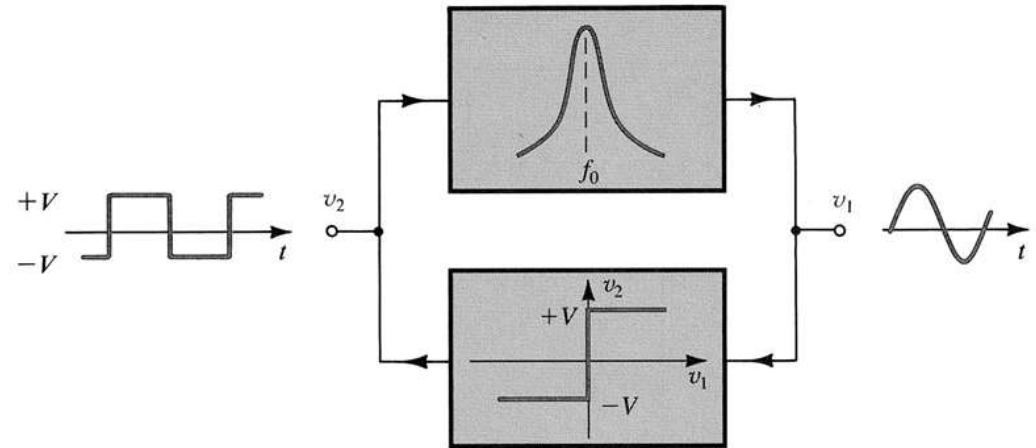- ❑ The circuit consists of a high-Q bandpass filter connected in a positive-feedback loop with a hard limiter
- ❑ Any filter circuit with positive gain can be used to implement the bandpass filter
- ❑ Can generate high-quality output sine waves
- ❑ Have independent control of frequency, amplitude and distortion of the output sinusoid



Final Remark

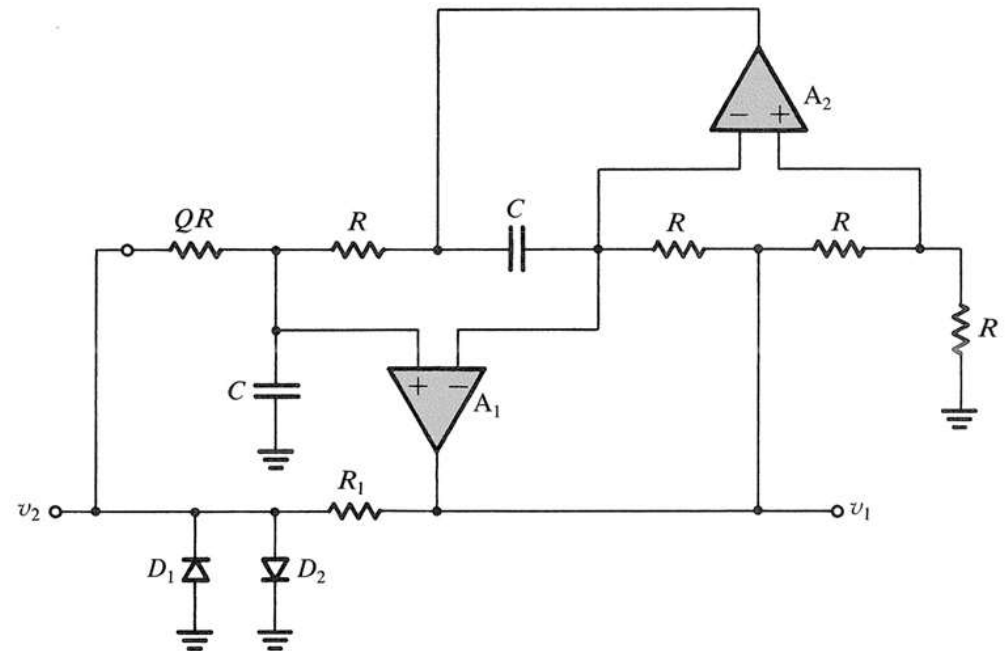
- ❑ Op amp-RF oscillators ~ 10 to 100kHz
- ❑ Lower limit: passive components
- ❑ Upper limit: frequency response and slew rate of op amp



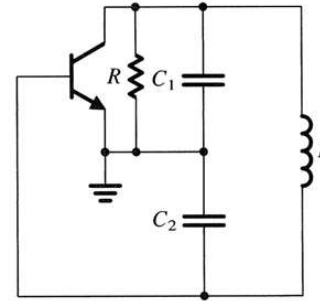
14.3 LC and Crystal Oscillators

LC Tuned Oscillators

- ❑ Colpitts oscillator: capacitive divider
- ❑ Hartley oscillator: inductive divider
- ❑ A parallel LC circuit between base and collector
- ❑ R models the overall losses



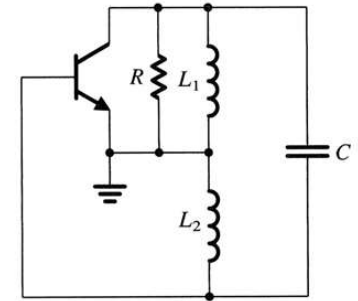
$$\omega_0 = 1 / \sqrt{L(1/C_1 + 1/C_2)}$$



$$\omega_0 = 1 / \sqrt{(L_1 + L_2)C}$$

Analysis of Colpitts Oscillators

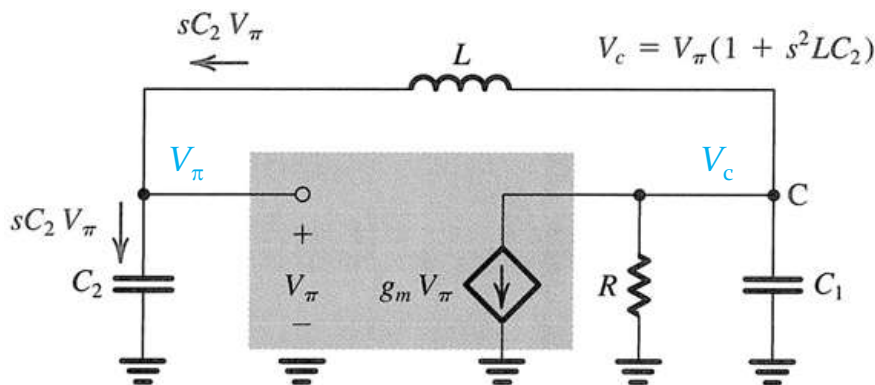

$$\begin{cases} sC_2v_\pi = sL(v_c - v_\pi) \\ sL(v_c - v_\pi) + g_mv_\pi + v_c/R + sC_1v_c = 0 \end{cases}$$

$$\rightarrow s^3LC_1C_2 + s^2\frac{LC_2}{R} + s(C_1 + C_2) + (g_m + \frac{1}{R}) = 0$$


Barkhausen criterion:

$$s = \pm j\omega_0 \rightarrow \left(g_m + \frac{1}{R} - \frac{\omega_0^2 LC_2}{R} \right) + j[\omega_0(C_1 + C_2) - \omega_0^3 LC_1C_2] = 0$$


$$\rightarrow \omega_0 = 1 / \sqrt{LC_1C_2 / (C_1 + C_2)} \text{ and } g_m = \frac{1}{R} \frac{C_2}{C_1}$$

- ❑ Utilize the transistor's nonlinear I - V characteristics for amplitude control (self-limiting)
- ❑ Collector (drain) current waveforms are distorted due to the nonlinear characteristics
- ❑ Output voltage is a sinusoid with high purity because of the filtering action of the LC tuned circuit

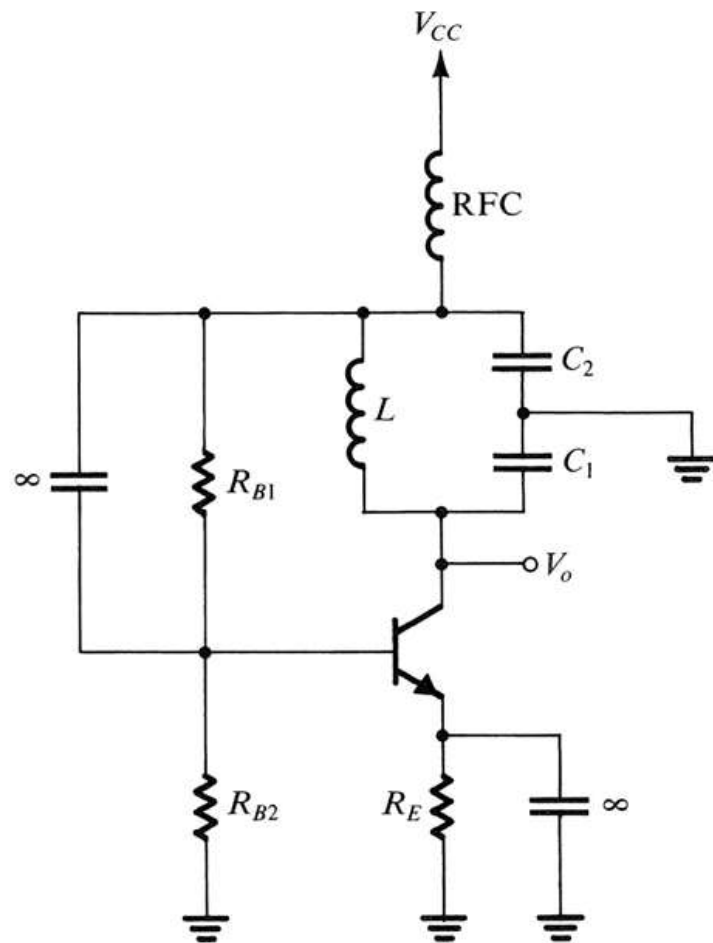
Complete Circuit for a Colpitts Oscillator



DC Analysis


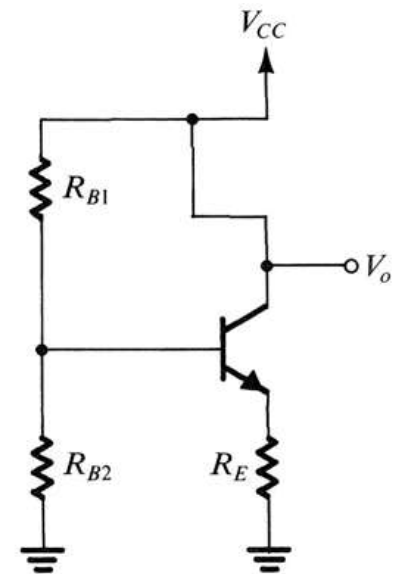


AC Analysis

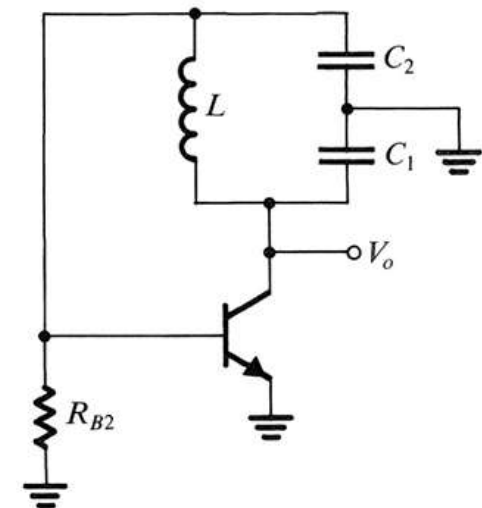

The Cross-Coupled LC Oscillator

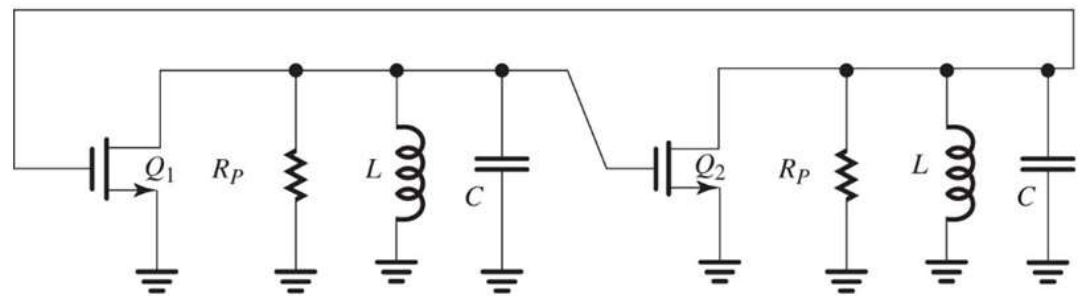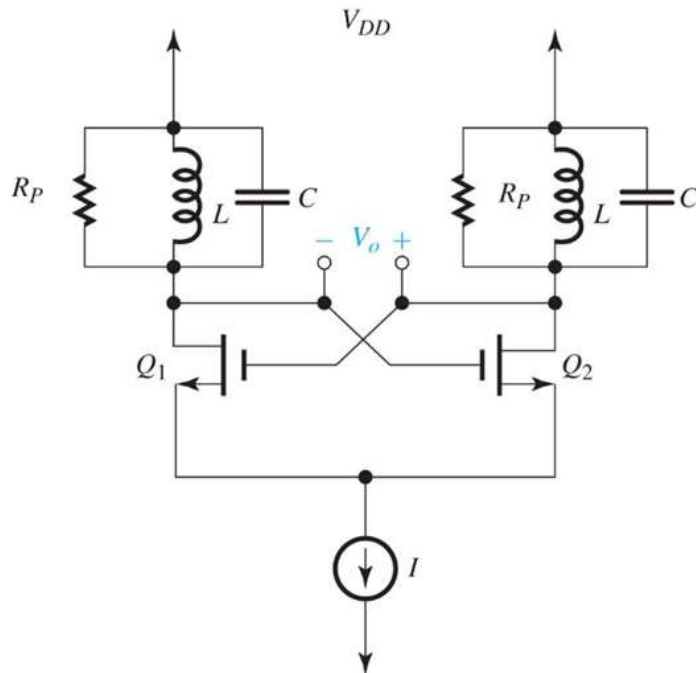- ❑ Popular LC oscillator circuit suitable for IC implementation
- ❑ Capable of operating at high frequencies (up to hundreds of GHz)
- ❑ The oscillation frequency is defined by the LC tank
- ❑ The cross-couple pair is to start up the oscillation
- ❑ Differential oscillation output available



Loop gain:

$$L(s) = \left(\frac{g_m}{1/R + 1/sL + sC} \right)^2$$

Barkhausen criterion:

$$L(j\omega_0) = \left(\frac{g_m}{1/R + 1/j\omega_0 L + j\omega_0 C} \right)^2 = 1 \rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ and } g_m = \frac{1}{R}$$

Crystal Oscillators

□ Crystal impedance:



$$Z(s) = 1 / \left[sC_p + \frac{1}{sL + 1/sC_s} \right]$$

$$Z(s) = \frac{1}{sC_p} \frac{s^2 + 1/LC_s}{s^2 + [(C_p + C_s)/LC_p C_s]}$$

$$\omega_s = 1/\sqrt{LC_s}$$

$$\omega_p = 1/\sqrt{L(1/C_s + 1/C_p)^{-1}}$$
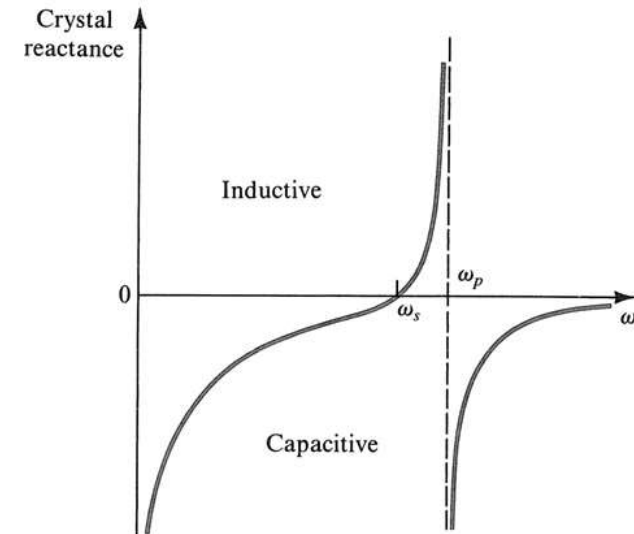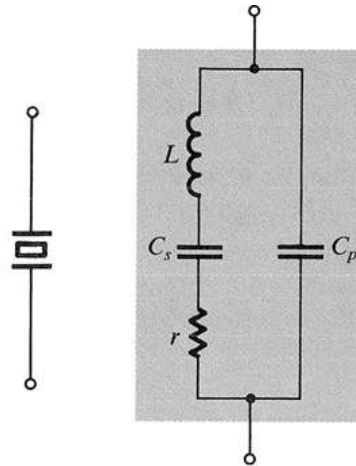
$$Z(j\omega) = -j \frac{1}{\omega C_p} \left(\frac{\omega^2 - \omega_s^2}{\omega^2 - \omega_p^2} \right)$$



□ Crystal reactance is inductive over very narrow frequency (ω_s to ω_p)

□ The frequency band is well defined for a given crystal


□ Use the crystal to replace the inductor of the Colpitts oscillators

□ Oscillation frequency is dominated by C_s (much smaller than other C 's)

$$\omega_0 \approx 1/\sqrt{LC_s} = \omega_s$$

□ Crystals are available with resonance frequencies KHz ~ hundred MHz

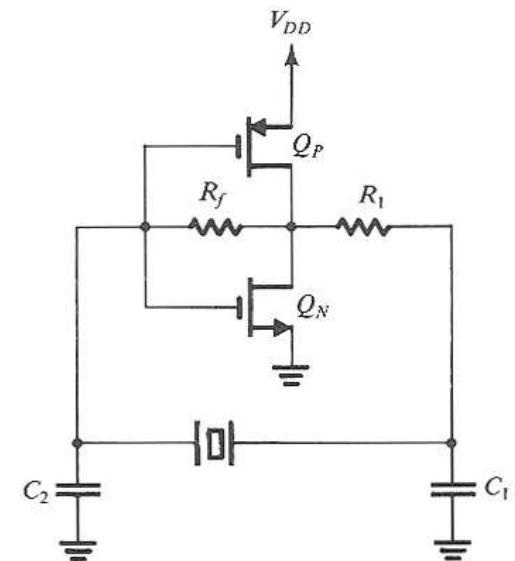□ The oscillation frequency is fixed (tuning is not possible)



14.4 Bistable Multivibrators

Bistable Characteristics



❑ Positive feedback for bistable multivibrator

❑ Stable states:

(1) $v_O = L_+$ and $v_+ = L_+ R_1 / (R_1 + R_2)$

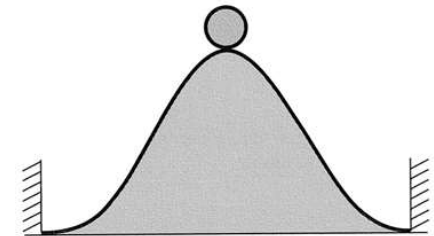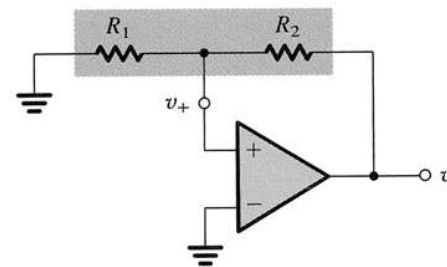(2) $v_O = L_-$ and $v_+ = L_- R_1 / (R_1 + R_2)$

❑ Metastable state: $v_O = 0$ and $v_+ = 0$



Transfer Characteristics of the Inverting Bistable Circuit

❑ Initially $v_I = L_-$, the bistable is in the state of $v_O = L_+$ and $v_+ = L_+ R_1 / (R_1 + R_2)$


→ v_O change state to L_- when v_I increases to a value of $L_+ R_1 / (R_1 + R_2)$

❑ Initially $v_I = L_+$, the bistable is in the state of $v_O = L_-$ and $v_+ = L_- R_1 / (R_1 + R_2)$

→ v_O change state to L_+ when v_I decreases to a value of $L_- R_1 / (R_1 + R_2)$


❑ The circuit exhibits hysteresis with a width of $(V_{TH} - V_{TL})$

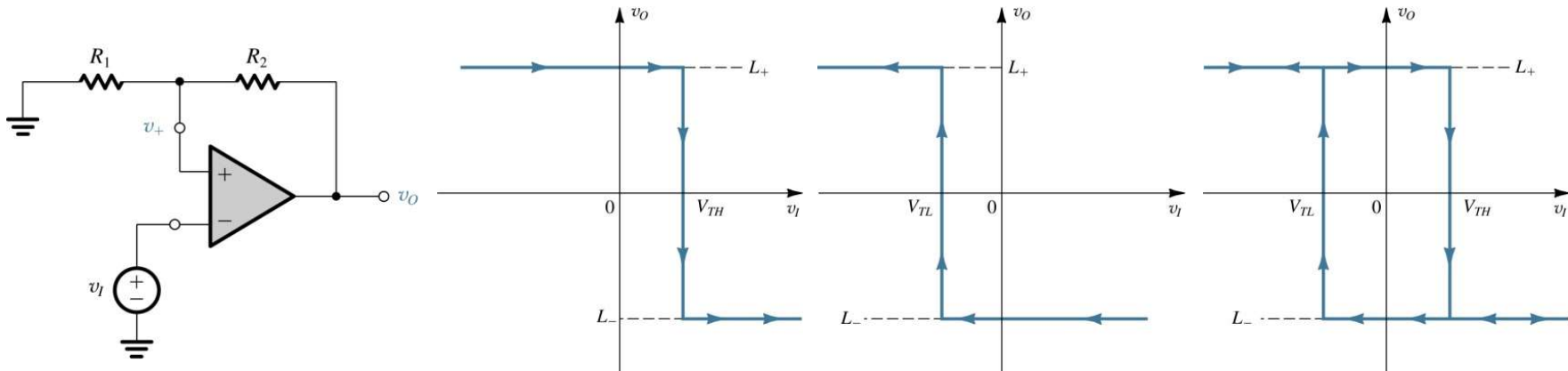❑ Input v_I is referred to as a trigger signal which merely initiates or triggers regeneration




Transfer Characteristics of the Noninverting Bistable Circuit


- Initially $v_I = L_-$, the bistable is in the state of $v_O = L_-$ and $v_+ = v_I R_2 / (R_1 + R_2) + L_- R_1 / (R_1 + R_2) < 0$
 $\rightarrow v_O$ change state to L_+ when v_I increases to a value (V_{TH}) that causes $v_+ = 0 \rightarrow V_{TH} = -L_- (R_1 / R_2) > 0$
- Initially $v_I = L_+$, the bistable is in the state of $v_O = L_+$ and $v_+ = v_I R_2 / (R_1 + R_2) + L_+ R_1 / (R_1 + R_2) > 0$
 $\rightarrow v_O$ change state to L_- when v_I decreases to a value (V_{TL}) that causes $v_+ = 0 \rightarrow V_{TL} = -L_+ (R_1 / R_2) < 0$

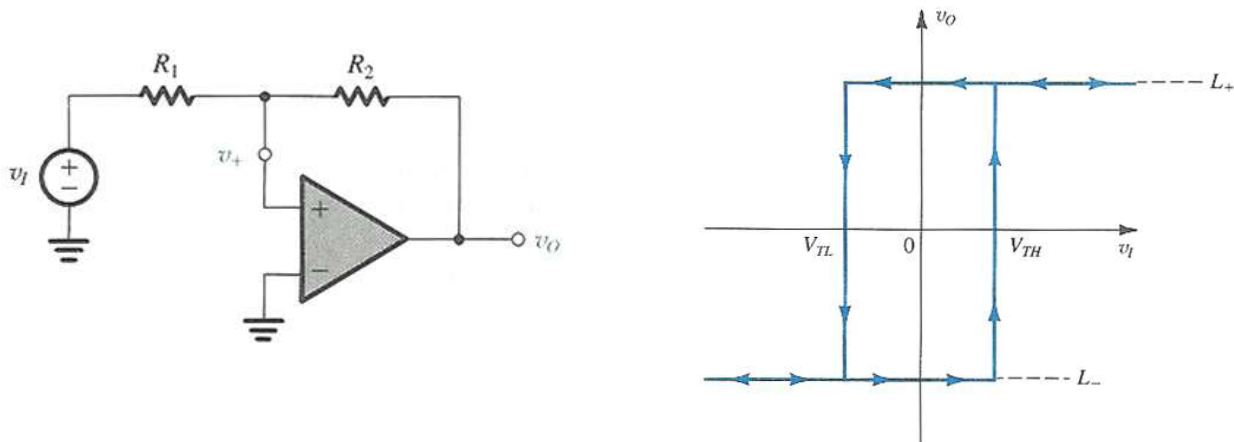

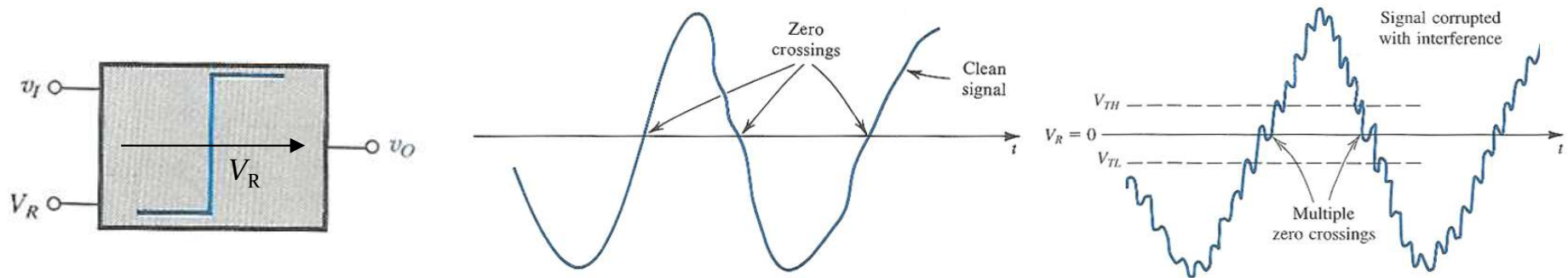Application of the Bistable Circuit as a Comparator




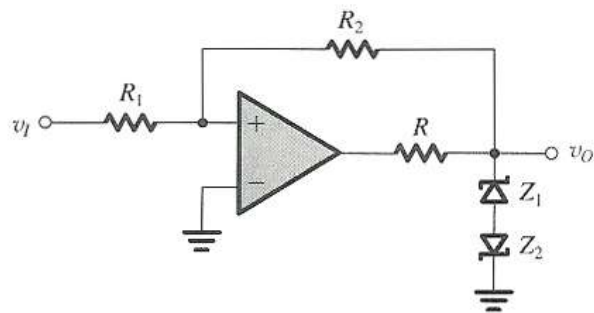Limiter Circuits for Precise Output Levels




$$L_+ = V_{Z1} + V_D$$

$$L_- = -(V_{Z1} + V_D)$$

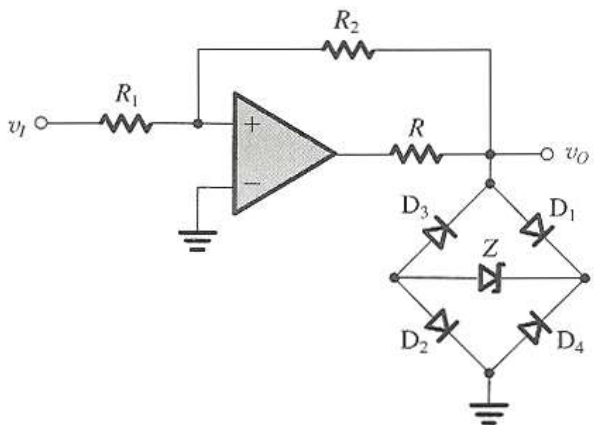




$$L_+ = V_Z + V_{D1} + V_{D2}$$

$$L_- = -(V_Z + V_{D3} + V_{D4})$$

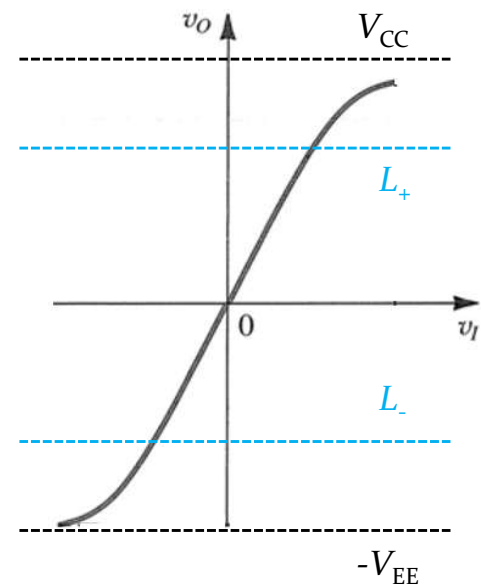

14.5 Generation of Square and Triangular Waveforms using Astable Multivibrators

Operation of the Astable Multivibrator

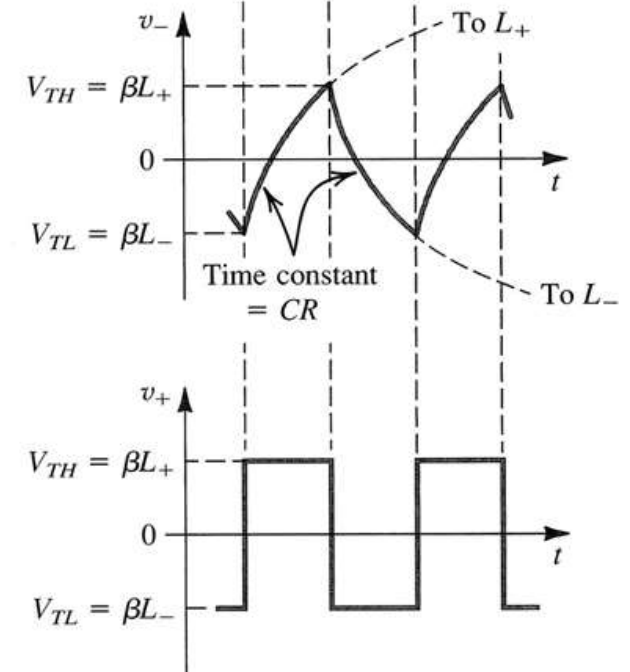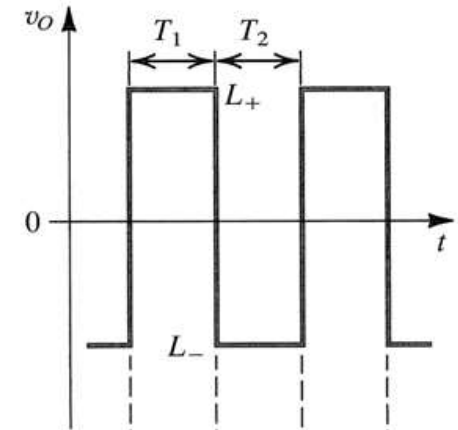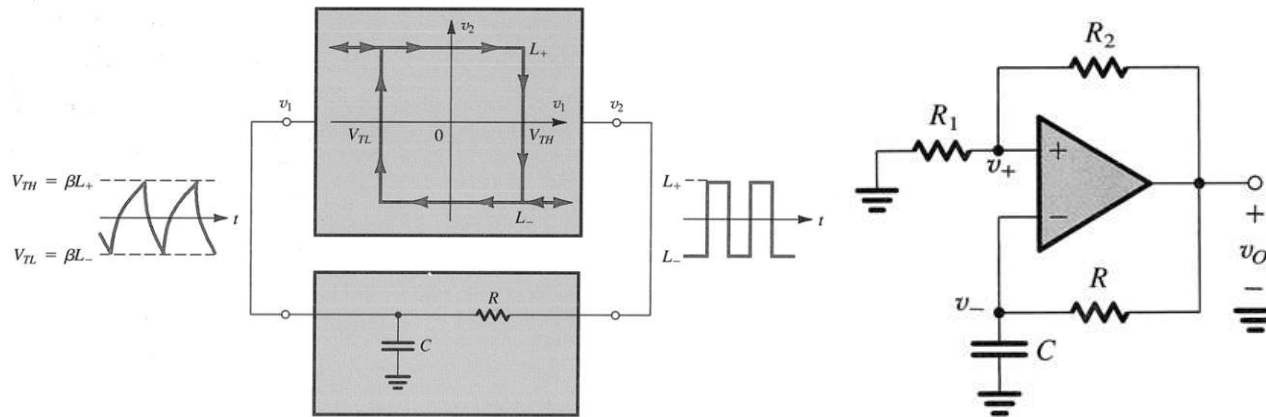

□ RC charge/discharge: $V = V_{\infty} - (V_{\infty} - V_0)e^{-t/RC} \rightarrow \Delta t = RC \ln \left(\frac{V_{\infty} - V_0}{V_{\infty} - V} \right)$

□ For $v_O = L_+$ and $v_+ = v_O R_1 / (R_1 + R_2) > 0$
 $\rightarrow v_-$ is charged toward L_+ through RC
 $\rightarrow v_O$ change stage to L_- when $v_- = v_+$

□ For $v_O = L_-$ and $v_+ = v_O R_1 / (R_1 + R_2) < 0$
 $\rightarrow v_-$ is discharged toward L_- through RC
 $\rightarrow v_O$ change stage to L_+ when $v_- = v_+$




$$v_- = L_+ - (L_+ - \beta \cdot L_-)e^{-t/RC} \rightarrow T_1 = RC \ln \frac{1 - \beta(L_- / L_+)}{1 - \beta}$$

$$v_- = L_- - (L_- - \beta \cdot L_+)e^{-t/RC} \rightarrow T_2 = RC \ln \frac{1 - \beta(L_+ / L_-)}{1 - \beta}$$

□ For $L_- = -L_+$: $T \approx 2RC \ln \frac{1 + \beta}{1 - \beta}$

Generation of Triangular Waveforms

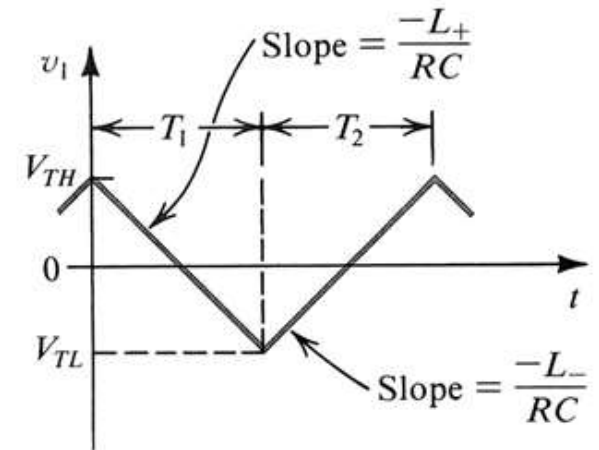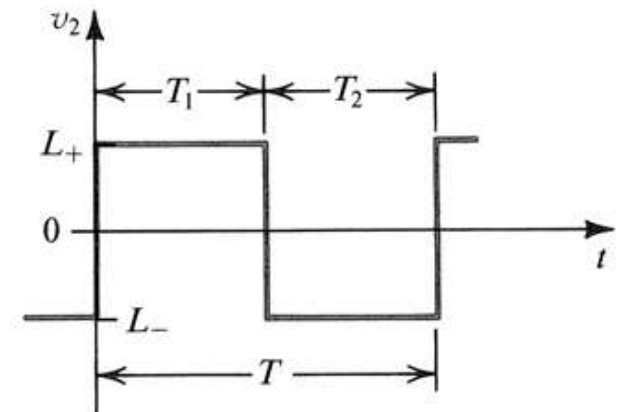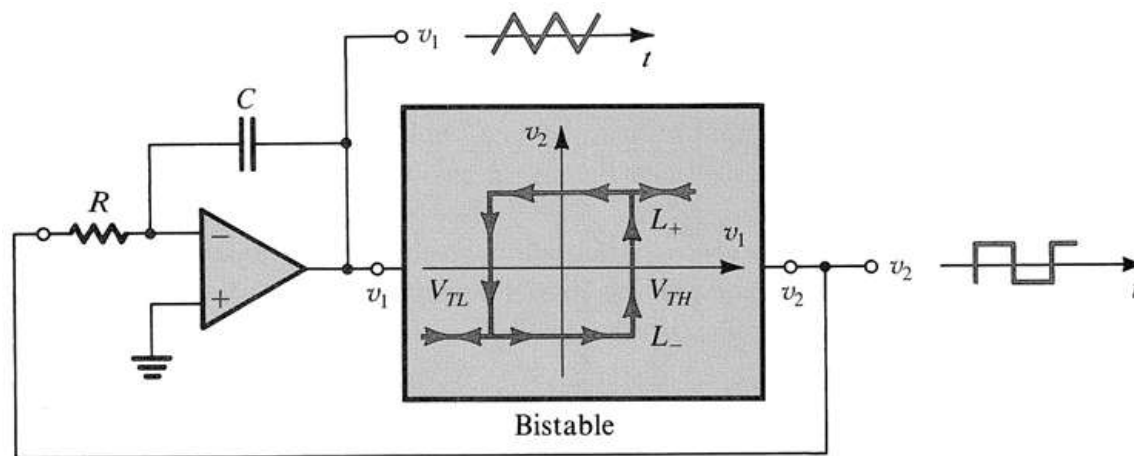- ❑ Triangular can be obtained by replacing the low-pass RC circuit with an integrator
- ❑ The bistable circuit required is of the noninverting type



$$\frac{V_{TH} - V_{TL}}{T_1} = \frac{L_+}{RC} \rightarrow T_1 = RC \frac{V_{TH} - V_{TL}}{L_+}$$

$$\frac{V_{TH} - V_{TL}}{T_2} = \frac{-L_-}{RC} \rightarrow T_2 = RC \frac{V_{TH} - V_{TL}}{-L_-}$$

14.6 Generation of a Standardized Pulse – The Monostable Multivibrators

Op-Amp Monostable Multivibrators

□ Circuit components:


- Trigger: C_2 , R_4 and D_2
- Clamping diode: D_1
- $R_4 \gg R_1 \rightarrow i_{D4} \approx 0$

□ The circuit has one stable state:

- $v_O = L_+$
- $v_B = V_{D1} \approx 0$
- D_1 and D_2 on

□ Operation of monostable multivibrator

- Negative step as the trigger input
- D_2 conducts heavily
- v_C is pulled below v_B for effective trigger
- v_O changes state to L_- and v_C becomes negative
- D_1 and D_2 off and C_1 is discharged toward L_-
- v_O changes state to L_+ as $v_B = v_C = \beta L_-$
- C_1 is charged toward L_+
- v_B is clamped to $V_{D1} \approx 0$ and the circuit is back to its stable state
- Positive trigger step turns off D_2 (invalid trigger)

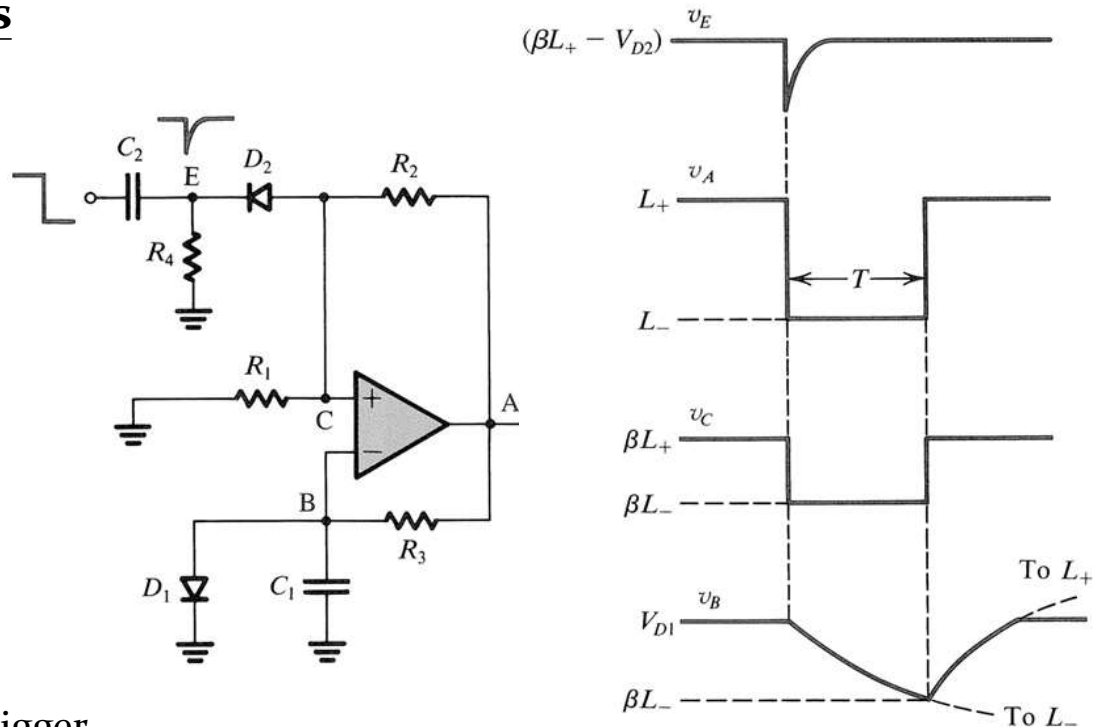


$$v_B(t) = L_- - (L_- - V_{D1})e^{-t/R_3C_1}$$


$$\rightarrow T \approx C_1 R_3 \ln \left(\frac{L_- - V_{D1}}{L_- - \beta \cdot L_-} \right) \approx C_1 R_3 \ln \left(\frac{1}{1 - \beta} \right)$$

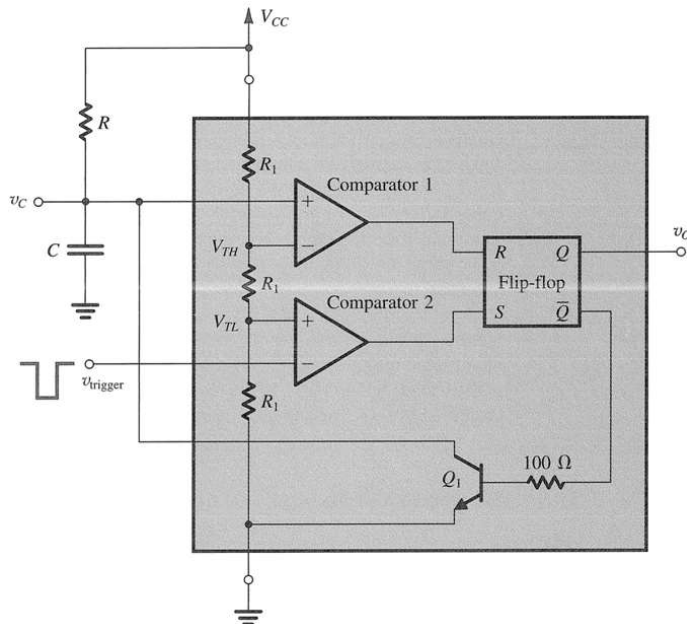14.7 Integrated-Circuit Timers



Monostable Multivibrator using 555 Timer Circuit



- Stable state: $S = R = 0$ and $Q = 0$
 $\rightarrow Q_1$ on and $v_C = 0$
- Trigger ($v_{\text{trigger}} < V_{TL}$): $S = 1$ and $Q = 1$
 $\rightarrow Q_1$ off and v_C is charged toward V_{CC}
- Trigger pulse removal ($v_{\text{trigger}} > V_{TL}$): $S = R = 0$ and $Q = 1$
 $\rightarrow Q_1$ off and v_C is charged toward V_{CC}
- End of recovery period ($v_C = V_{TH}$): $R = 1$ and $Q = 0$
 $\rightarrow Q_1$ on and v_C is discharged toward GND
- Stable state: v_C drops to 0 and $S = R = 0$ and $Q = 0$

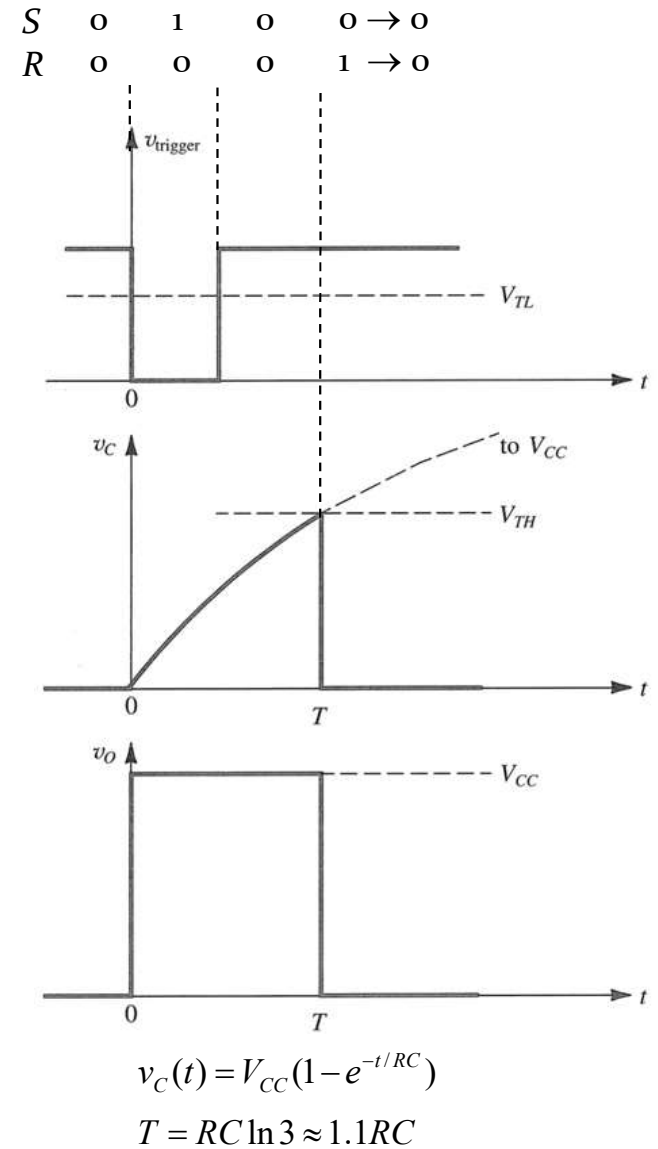

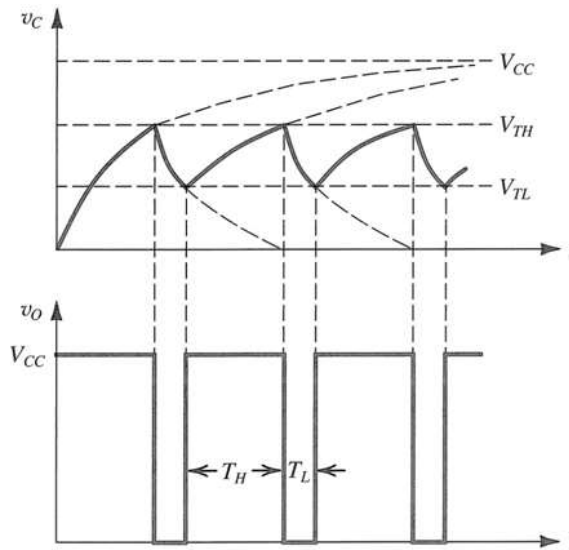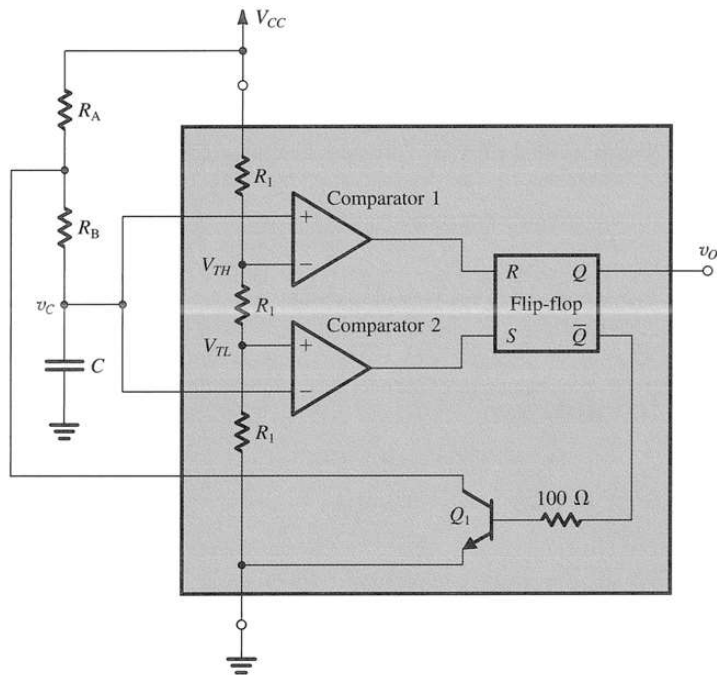Astable Multivibrator using 555 Timer Circuit



$$v_C(t) = V_{CC} - (V_{CC} - V_{TL})e^{-t/C(R_A + R_B)}$$

$$T_H = C(R_A + R_B) \ln 2 \approx 0.69C(R_A + R_B)$$

$$v_C = V_{TH}e^{-t/CR_B}$$

$$T_L = CR_B \ln 3 \approx 0.69CR_B$$

$$T = T_H + T_L = 0.69CR_B$$

$$\text{Duty cycle} \equiv \frac{T_H}{T_H + T_L} = \frac{R_A + R_B}{R_A + 2R_B}$$



□ Operation of astable multivibrator

- Initially $v_C = 0$: $S/R = 1/0$ and $Q = 1 \rightarrow Q_1$ off and v_C is charged toward V_{CC} thru R_A and R_B
- v_C reaches V_{TH} : $S/R = 0/1$ and $Q = 0 \rightarrow Q_1$ on and v_C is discharged toward GND thru R_B
- v_C reaches V_{TL} : $S/R = 1/0$ and $Q = 1 \rightarrow Q_1$ off and v_C is charged toward V_{CC} thru R_A and R_B

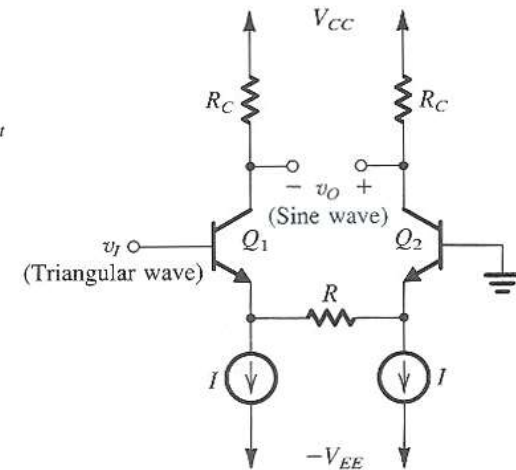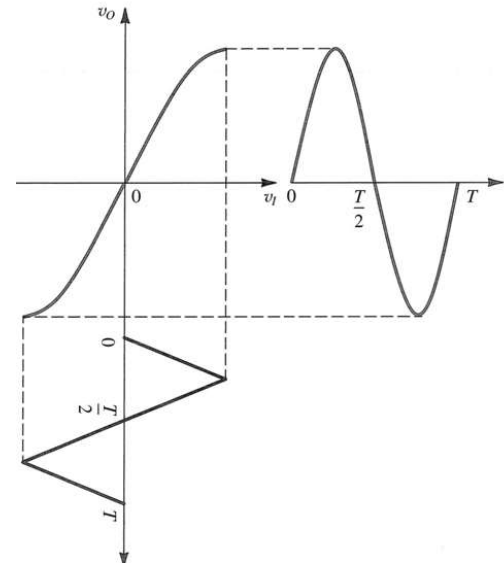14.8 Nonlinear Waveform-Shaping Circuits

Nonlinear Amplification Method

- Use amplifiers with nonlinear transfer characteristics to convert triangular wave to sine wave
- Differential pair with an emitter degeneration resistance can be used as sine-wave shaper



Breakpoint Method

- $R_4, R_5 \gg R_1, R_2$ and R_3 to avoid loading effect

■ $-V_1 < v_{IN} < V_1$:

$\rightarrow v_O = v_{IN}$

■ $-V_2 < v_{IN} < -V_1$ or $V_1 < v_{IN} < V_2$

$\rightarrow v_O = V_1 + (v_{IN} - V_1) R_5 / (R_4 + R_5)$

■ $v_{IN} < -V_2$ or $V_2 < v_{IN}$

$\rightarrow v_O = V_2$

