

CHAPTER 16 ADVANCED MOS AND BIPOLAR LOGIC CIRCUITS


Chapter Outline

- 16.1 Implications of Technology Scaling
- 16.2 Digital IC Technology, Logic-Circuit Family and Design Methodologies
- 16.3 Pseudo-NMOS Logic Circuits
- 16.4 Pass-Transistor Logic Circuits
- 16.5 Dynamic MOS Logic Circuits

 16.1 Implications of Technology Scaling

Moore's Law

- ❑ A new technology is developed for every 2~3 years due to cost and speed requirement
- ❑ The trend was predicted more than 40 years ago by Gordon Moore
- ❑ For every new technology generation:
 - The minimum length is reduced by a factor of 1.414 and the area is reduced by a factor of 2
 - The cost is reduced by half or the circuit complexity is doubled
 - Device scaling generally decreases the parasitics and enhances the operating speed
 - The operating power is reduced
- ❑ The current technology node advances into deep-submicron
- ❑ Issues in deep-submicron technologies have to be taken into account for circuit designs



Scaling Implications

Implications of Device and Voltage Scaling		
Parameter	Relationship	Scaling Factor
1	W, L, t_{ox}	$1/S$
2	V_{DD}, V_t	$1/S$
3	Area/Device	WL
4	C_{ox}	ϵ_{ox}/t_{ox}
5	k'_n, k'_p	$\mu_n C_{ox}, \mu_p C_{ox}$
6	C_{gate}	WLC_{ox}
7	t_p (intrinsic)	$\alpha C/KV_{DD}$
8	Energy/Switching cycle (intrinsic)	CV_{DD}^2
9	P_{dyn}	$f_{max} CV_{DD}^2 = \frac{CV_{DD}^2}{2t_p}$
10	Power density	$P_{dyn}/\text{Device area}$


Velocity Saturation

□ Long-channel devices:

- Drift velocity: $v_n = \mu_n E$
- Electric field in the channel: $E = v_{DS}/L$

□ Short-channel devices:

- Velocity saturates at a critical field E_{cr} with $v_{sat} \cong 10^7$ cm/s
- The v_{DS} at which velocity saturates is denoted by V_{DSsat}
- $V_{DSsat} = E_{cr}L = v_{sat}L/\mu_n$
- V_{DSsat} is a device parameter

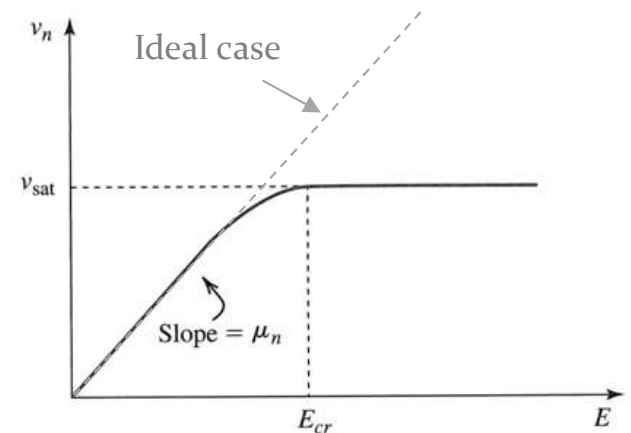

The I-V Characteristics

□ Long-channel devices


- Saturation current: $i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$

□ Short-channel devices

- For $v_{GS} - V_t < V_{DSsat}$: same as long-channel devices
- For $v_{GS} - V_t > V_{DSsat}$:

$$I_{Dsat} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_t) V_{DSsat} - \frac{1}{2} V_{DSsat}^2 \right]$$
 
$$= WC_{ox} v_{sat} \left(V_{GS} - V_t - \frac{1}{2} V_{DSsat} \right)$$




Current Equation for Velocity Saturation

□ For $v_{GS} - V_t \geq V_{DSsat}$ and $v_{DS} \geq V_{DSsat}$, a general expression of the drain current is given by

$$i_D = \mu_n C_{ox} \frac{W}{L} V_{DSsat} \left(v_{GS} - V_t - \frac{1}{2} V_{DSsat} \right) (1 + \lambda V_{DS})$$

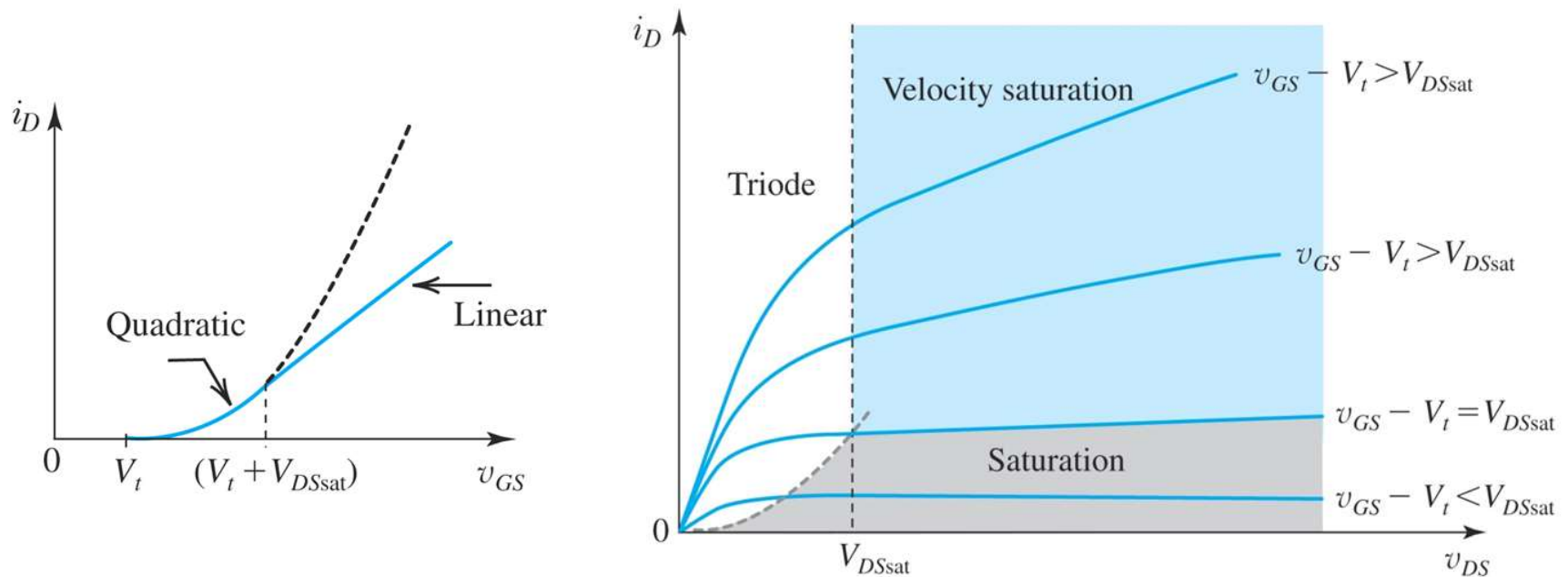- The current is reduced from the prediction of a long-channel device
 - The dependence on v_{GS} is more linear rather than quadratic
- Four regions of operation: cutoff, triode, saturation and velocity saturation
- Short-channel PMOS transistors undergo velocity saturation at the same value of v_{sat}
- The effects on PMOS are less pronounced due to lower mobility and higher V_{DSsat}




Subthreshold Conduction

- ❑ The device is not complete off in deep-submicron devices as $v_{GS} < V_t$
- ❑ The subthreshold current is exponentially proportional to v_{GS} : $i_D = I_s \exp(v_{GS}/nV_T)$
- ❑ It is a problem in digital IC design for two reasons:
 - Such current leads to nonzero static power dissipation for CMOS logics
 - May cause undesirable discharge of capacitors in dynamic CMOS logics

The Interconnect

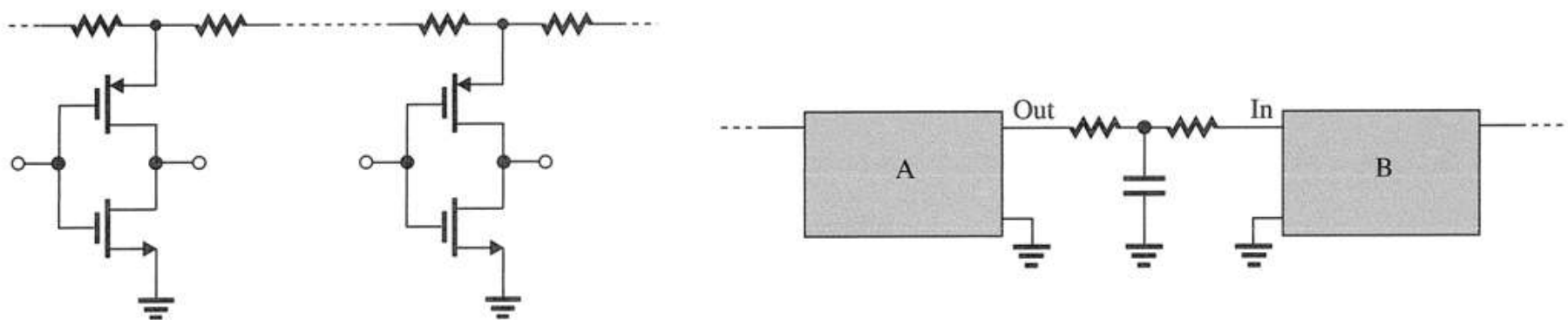
- ❑ The width of the interconnect scales down with the CMOS technology
- ❑ The metal wire is no longer an ideal short
 - Series parasitic resistance may cause undesirable voltage drop and excess delay
 - Parasitic capacitance to ground may lead to speed degradation and additional dynamic power



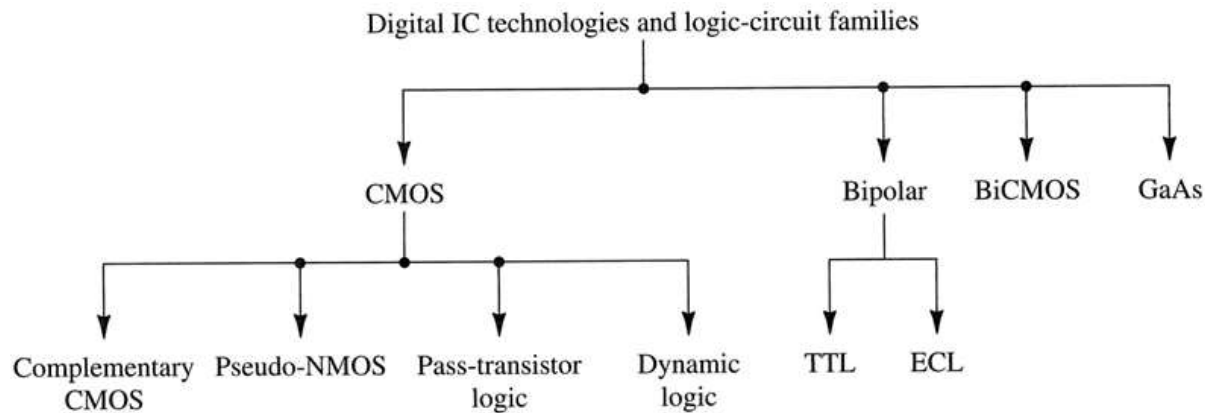16.2 Digital IC Technology, Logic-Circuit Families, and Design Methodologies

Logic-Circuit Families

- ❑ Classified by fabrication technology: CMOS, Bipolar, BiCMOS, GaAs
- ❑ Most widely logic-circuit technology is CMOS
- ❑ Various logic families are implemented in CMOS technology




Styles for Digital System Design

- ❑ Assemble the system using standard IC packages of various levels of complexity
- ❑ Application specific IC (ASIC) with customized digital design when large volume is required
- ❑ Semicustom design:
 - Gate-array (unconnected logic gates) with final customized metallization step
 - Field-programmable gate array (FPGA) can be programmed by the user

 16.3 The Pseudo-NMOS Logic Circuits

The Voltage-Transfer Characteristic (VTC)

- The function of the inverter is to invert the logic value of its input signal
- The voltage-transfer characteristic is used to evaluate the quality of inverter operation




□ VTC parameters

- V_{OH} : output high level
- V_{OL} : output low level
- V_{IH} : the minimum value of input interpreted by the inverter as a logic 1
- V_{IL} : the maximum value of input interpreted by the inverter as a logic 0
- Transition region: input level between V_{IL} and V_{IH}


NMOS Inverter Circuits

- ❑ A simple inverter circuit is composed of a NMOS and a load
- ❑ The load can be realized by a resistor or another NMOS device


Resistive Load
NMOS Inverter

 

Enhancement Load
NMOS Inverter

 


Depletion Load
NMOS Inverter

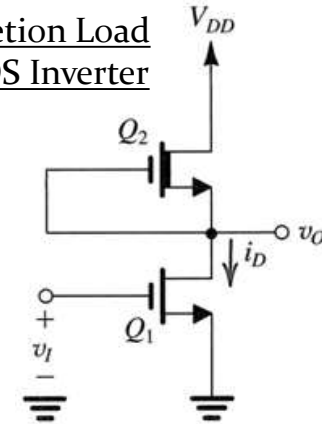

Pseudo-NMOS Inverters

- ❑ Use a PMOS transistor as the load
- ❑ Does not suffer from body effect
- ❑ Directly compatible with complementary CMOS circuits
- ❑ Area and delay penalties arising from the fan-in in complementary CMOS gate is reduced

Pseudo-NMOS Inverter

 

Static Characteristics



- ❑ Load curve represents a much lower saturation current
- ❑ k_n is usually greater than k_p by a factor of 4 to 10
- ❑ A ratioed type logic with $r \equiv k_n/k_p$
- ❑ The logic is typically operated in two extremely cases:
 - $v_I = 0$: $v_O = V_{OH} = V_{DD}$
 - $v_I = V_{DD}$: $v_O = V_{OL} > 0$ (nonzero V_{OL} for pseudo-NMOS)
- ❑ The VTC can be derived based on i_{DN} and i_{DP} :

$$i_{DN} = \frac{1}{2}k_n(v_I - V_t)^2 \quad \text{for } v_O \geq v_I - V_t \quad (\text{saturation})$$

$$i_{DN} = k_n \left[(v_I - V_t)v_O - \frac{1}{2}v_O^2 \right] \quad \text{for } v_O \leq v_I - V_t \quad (\text{triode})$$

$$i_{DP} = \frac{1}{2}k_p(V_{DD} - V_t)^2 \quad \text{for } v_O \leq V_t \quad (\text{saturation})$$
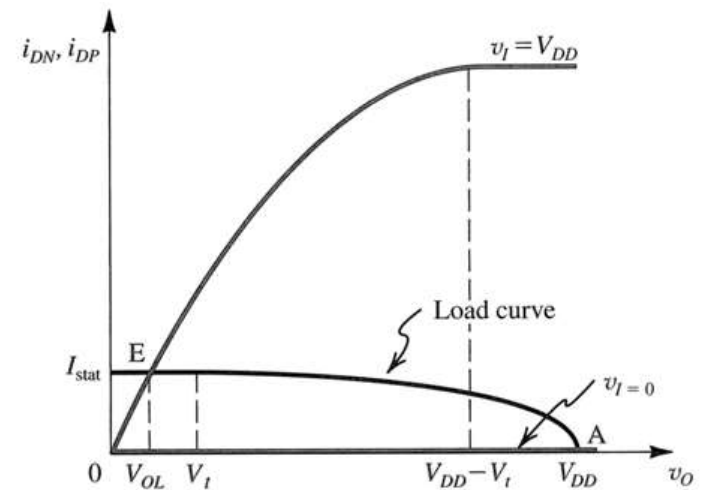 
$$i_{DP} = k_p \left[(V_{DD} - V_t)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right] \quad \text{for } v_O \geq V_t \quad (\text{triode})$$



Derivation of the VTC

□ Assume $V_{tn} = |V_{tp}| = V_t$ for the derivations

□ Region I (Segment AB):

$$v_O = V_{OH} = V_{DD}$$

□ Region II (Segment BC):

$$v_O = V_t + \sqrt{(V_{DD} - V_t)^2 - r(v_I - V_t)^2}$$

□ Region III (Segment CD):

$$r \left[(v_I - V_t)v_O - \frac{1}{2}v_O^2 \right] = \left[(V_{DD} - V_t)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right]$$

□ Region IV (Segment DE):

$$v_O = (v_I - V_t) - \sqrt{(v_I - V_t)^2 - \frac{1}{r}(V_{DD} - V_t)^2}$$

□ Static Characteristics:

$$V_{OH} = V_{DD}$$

$$V_{OL} = (V_{DD} - V_t)(1 - \sqrt{1 - k_p/k_n})$$


$$V_{IH} = V_t + \frac{2}{\sqrt{3k_n/k_p}}(V_{DD} - V_t)$$

$$V_{IL} = V_t + \frac{V_{DD} - V_t}{\sqrt{(k_n/k_p)(k_n/k_p + 1)}}$$

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$
 
$$V_M = V_t + \frac{V_{DD} - V_t}{\sqrt{k_n/k_p + 1}}$$



Region	VTC Segment	Q_N	Q_P	Condition
I	AB	Cut-off	Triode	$v_I < V_t$
II	BC	Saturation	Triode	$v_O > v_I - V_t$
III	CD	Triode	Triode	$V_t < v_O < v_I - V_t$
IV	DE	Triode	Saturation	$v_O < V_t$

Dynamic Operation

□ Determine t_{PLH} :

■ The analysis is identical to the CMOS inverter and the output C is charged by PMOS

$$t_{PLH} = \frac{\alpha_p C}{k_p V_{DD}} \quad \text{where} \quad \alpha_p = 2 / \left[\frac{7}{4} - 3 \left(\frac{V_t}{V_{DD}} \right) + \left(\frac{V_t}{V_{DD}} \right)^2 \right]$$

□ Determine t_{PHL} :

■ The discharge current is $i_{DN} - i_{DP}$ while i_{DP} is typically negligible as r is large

$$t_{PHL} = \frac{\alpha_n C}{k_n V_{DD}} \quad \text{where} \quad \alpha_n = 2 / \left[1 + \frac{3}{4} \left(1 - \frac{1}{r} \right) - \left(3 - \frac{1}{r} \right) \left(\frac{V_t}{V_{DD}} \right) + \left(\frac{V_t}{V_{DD}} \right)^2 \right]$$

□ $\alpha_n \cong \alpha_p$ for a large value of r and t_{PLH} is much larger than t_{PHL}

Design of Pseudo-NMOS Inverter

□ Determine ratio $r = k_n / k_p$

■ The larger the value of r , the lower V_{OL} is and the wider the noise margins are

■ A larger r increases the asymmetry in the dynamic response

■ Usually, r is selected in the range of 4 to 10

□ Determine $(W/L)_n$ and $(W/L)_p$

■ A smaller (W/L) to keep the gate area small and thus obtain a small value for C

■ A smaller (W/L) to keep I_{sat} of Q_p and static power dissipation low

■ Larger (W/L) ratios in order to obtain low t_p and thus fast response

Gate Circuits



- ❑ Identical to PDN of CMOS gate except for the load device
- ❑ The (W/L) ratio of the load device is chosen as the basic inverter
- ❑ The (W/L) ratios of the PDN are chosen for a worst-case gate delay equal to that of the basic inverter (assuming C is constant)

Concluding Remarks

- ❑ In pseudo-NMOS, NOR gates are preferred over NAND gates in order to use minimum-size devices
- ❑ Pseudo-NMOS is particularly suited for applications in which output remains high most of the time
 - Static power dissipation can be reasonably low
 - The output transitions that matter would presumably be high-to-low

Comparison with CMOS Logic

 
 
- ❑ The transistor number is reduced for lower implementation cost
- ❑ The routing complexity is reduced
- ❑ Output capacitance is reduced for higher speed
- ❑ Rationed design
- ❑ Nonzero static power dissipation



  16.4 Pass-Transistor Logic Circuits

Design of Pass-Transistor Logic (PTL) Circuits


- ❑ Using series and parallel combinations of switches
- ❑ The switches are controlled by input logic variables to connect the input and output nodes
- ❑ Can be implemented by a single NMOS transistor or CMOS transmission gate
- ❑ Every circuit node has **at all times** a low-resistance path to V_{DD} or ground



Operation with NMOS Transistor as the Switch


□ Pass-transistor with output high (“poor I ”)

 - The output node refers to the source terminal of the NMOS
- Q is in saturation during the charging process
- V_t increases with v_O due to body effect \rightarrow resulting in a large t_{PLH}
- $V_{OH} = V_{DD} - V_t \rightarrow$ reduced gate noise immunity and possible static power for the following CMOS inverter stage




□ Pass-transistor with output low (“good o ”)

 - The input node refers to the source terminal of the NMOS (Body Effect is neglected)
- The output node can be discharged completely $\rightarrow V_{OL} = 0$











Restoring the Output Level

- The circuit-based approach by adding a feedback loop with Q_R
 - The PMOS Q_R turns on by v_{O2} (= “o”) to restore the signal loss at v_{O1} = “1”
 - The PMOS Q_R is turn off by v_{O2} (= “1”) when v_{O1} = “o”
 - Operation is more involved than it appears due to the positive feedback
 - Q_R has to be a “weak PMOS transistor” in order not to play a major role in the circuit operation
- The alternative approach by process technology
 - The signal loss is due to the threshold voltage of the NMOS devices
 - Threshold adjustment by ion implantation to make zero-threshold devices
 - Subthreshold conduction becomes significant for zero-threshold devices

 

The Use of CMOS Transmission Gates as Switches

        - ❑ PMOS and NMOS are in parallel with complementary control signal
- ❑ Both NMOS and PMOS provide charging/discharging current
- ❑ Good logic level with $V_{OH} = V_{DD}$ and $V_{OL} = 0$
- ❑ The complexity, silicon area and load capacitance are increased
- ❑ Body effect has to be taken into account to evaluate i_{DN} and i_{DP}



The Equivalent Resistance of the Transmission Gate

□ The CMOS transmission gate in charging case is modeled by

□ The equivalent resistance of Q_N :

■ For $v_O \leq V_{DD} - V_{tn}$:

$$i_{DN} = \frac{1}{2}k_n(V_{DD} - V_{tn} - v_O)^2 \quad \text{and} \quad R_{Neq} = \frac{V_{DD} - v_O}{\frac{1}{2}k_n(V_{DD} - V_{tn} - v_O)^2}$$

■ For $v_O > V_{DD} - V_{tn}$:

$$i_{DN} = 0 \quad \text{and} \quad R_{Neq} = \infty$$


□ The equivalent resistance of Q_P :

■ For $v_O \leq |V_{tp}|$:

$$i_{DP} = \frac{1}{2}k_p(V_{DD} - |V_{tp}|)^2 \quad \text{and} \quad R_{Peq} = \frac{V_{DD} - v_O}{\frac{1}{2}k_p(V_{DD} - |V_{tp}|)^2}$$

■ For $v_O > |V_{tp}|$:

$$i_{DP} = k_p \left[(V_{DD} - |V_{tp}|)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right] \quad \text{and} \quad R_{Peq} = \frac{V_{DD} - v_O}{k_p \left[(V_{DD} - |V_{tp}|)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right]}$$

 

□ $R_{TG} = R_{Neq} || R_{Peq}$ remains relatively constant over the full range


□ The case for discharging can be obtained by similar analysis

□ Empirical formula of R_{TG} with $(W/L)_n = (W/L)_p$ for certain CMOS technologies is

$$R_{TG} = \frac{12.5}{(W/L)_n} (k\Omega)$$

Calculation of Propagation Delay in the Signal Path

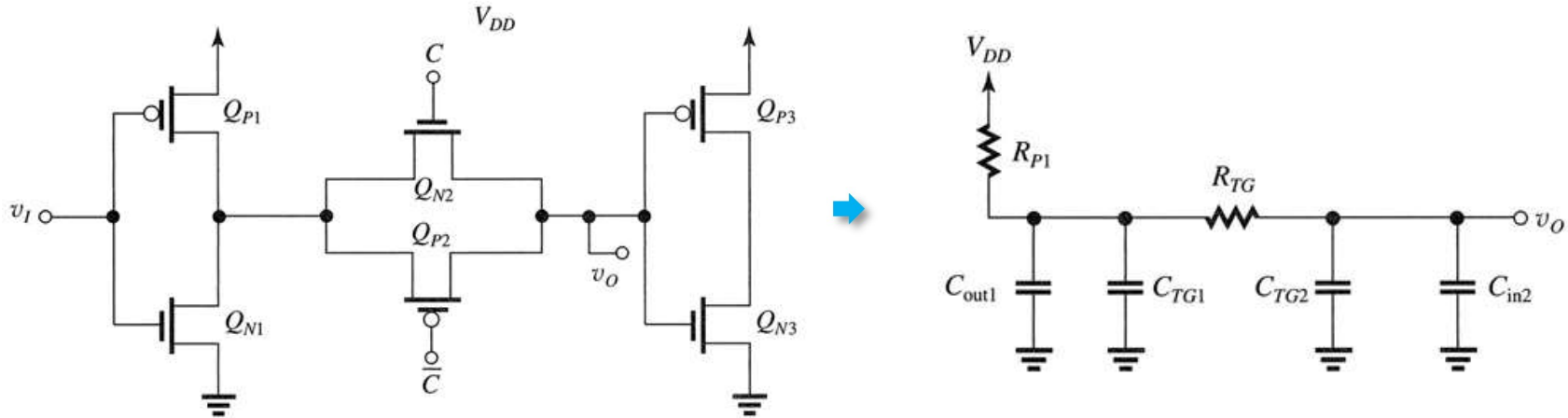- The signal path containing multiple transmission gates can be modeled by resistors and capacitors




- The model is in a form of an RC ladder network
- The propagation delay is given by Elmore delay formula as

$$t_p = 0.69[(C_{out1} + C_{TG1})R_{P1} + (C_{TG2} + C_{in2})(R_{P1} + R_{TG})]$$




- The factor 0.69 is dropped for estimation as the input is not a step function

- *Elmore delay formula is given by
 
$$t_p = 0.69[C_1R_1 + C_2(R_1 + R_2) + C_3(R_1 + R_2 + R_3) + \dots]$$



Pass-Transistor Logic Circuit Examples

   

Final Remarks

- ❑ Advantages of CMOS transmission gate over pass-transistor logic with NMOS devices
 - Logic level: good “1” and “0”
 - No level restoring technique needed
- ❑ Disadvantages of CMOS transmission gate over pass-transistor logic with NMOS devices
 - Silicon area and complexity: an additional input requires one NMOS and one PMOS devices
 - Complementary control signal required
 - Propagation delay: more capacitive loading from the MOSFETs


16.5 Dynamic MOS Logic Circuits

Principle of Dynamic Logic Circuits

- ❑ Rely on the storage of signal voltage on parasitic capacitances at certain circuit nodes
- ❑ The circuits need to be periodically refreshed
- ❑ Maintain the low device count of pseudo-NMOS with zero static power dissipation

Operation of Dynamic Logic Circuits

 - ❑ Precharge phase: Q_p on and Q_e off \rightarrow charge the output node to V_{DD}
- ❑ Evaluation phase: Q_p off and Q_e on \rightarrow selectively discharge the output node through PDN



Nonideal Effects

□ Noise margin:


- Since $V_{IL} \approx V_{IH} \approx V_{tn}$, the resulting noise margins are $NM_L \approx V_{tn}$ and $NM_H \approx V_{DD} - V_{tn}$
- Asymmetric noise immunity (poor NM_L)

□ Output voltage decay due to leakage effects:

- When PDN is off, leakage current will slowly discharge the output node
- The leakage is from the reversed-biased junctions and possibly the subthreshold conduction



□ Charge sharing:

 - Some of the internal nodes in PDN will share the charge in C_L even the PDN path is off
- Can be solved by adding a permanently turn-on transistor Q_L at the cost of static power dissipation




Domino CMOS Logic

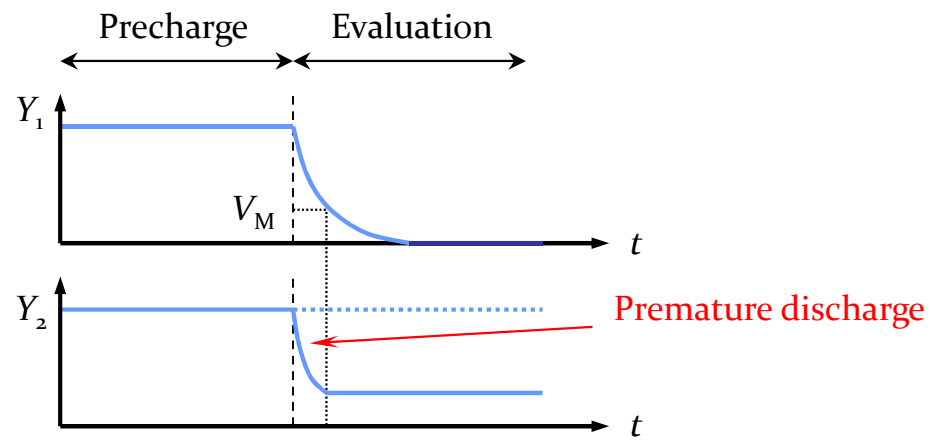 ❑ Problem with cascading dynamic logic gates: errors caused by undesirable premature discharge




❑ Domino CMOS logic:

 - A dynamic logic with a static CMOS inverter connected to its output
- The output to the following stages is 0 during the precharge phase
- Can alleviate the premature discharge problem



□ A cascade of Domino CMOS logic:

 - Each stage has to wait for the rising edge from the preceding stage
- The rising edge propagates through a cascade of gates



Concluding Remarks

- Advantages of Domino logic: small area, high-speed operation, and zero static power dissipation
- Disadvantages of Domino logic:
 - Asymmetric noise margin
 - Leakage issue
 - Charge sharing
 - Dead time: unavailability of output during precharge phase