

Design of a RISC Processor Compatible with ARM Instructions

Ahmet Gürhanlı

Advisor: 陳中平 教授

Lab: BL405



OUTLINE

- Motivation
- Development of the chip
- Architecture
- Synthesis & Optimization
- Place & Route
- Simulation Results
- Conclusion



MOTIVATION


- ARM processors are frequently used in application specific integrated circuits (ASICs).
- Major applications:
 - Telecommunication
 - Data communication
 - Portable Computing
 - Automotive
 - Information Systems
 - Imaging




DEVELOPMENT OF THE CHIP

- Research on ARM processors
- Coding the architecture (Verilog)
- Synthesis with scan chain (Synopsys DC)
- Test pattern generation (Tetramax)
- Place & Route (Astro)
- Post layout verification (Verilog)
- DRC & LVS verification (Calibre)

ARCHITECTURE

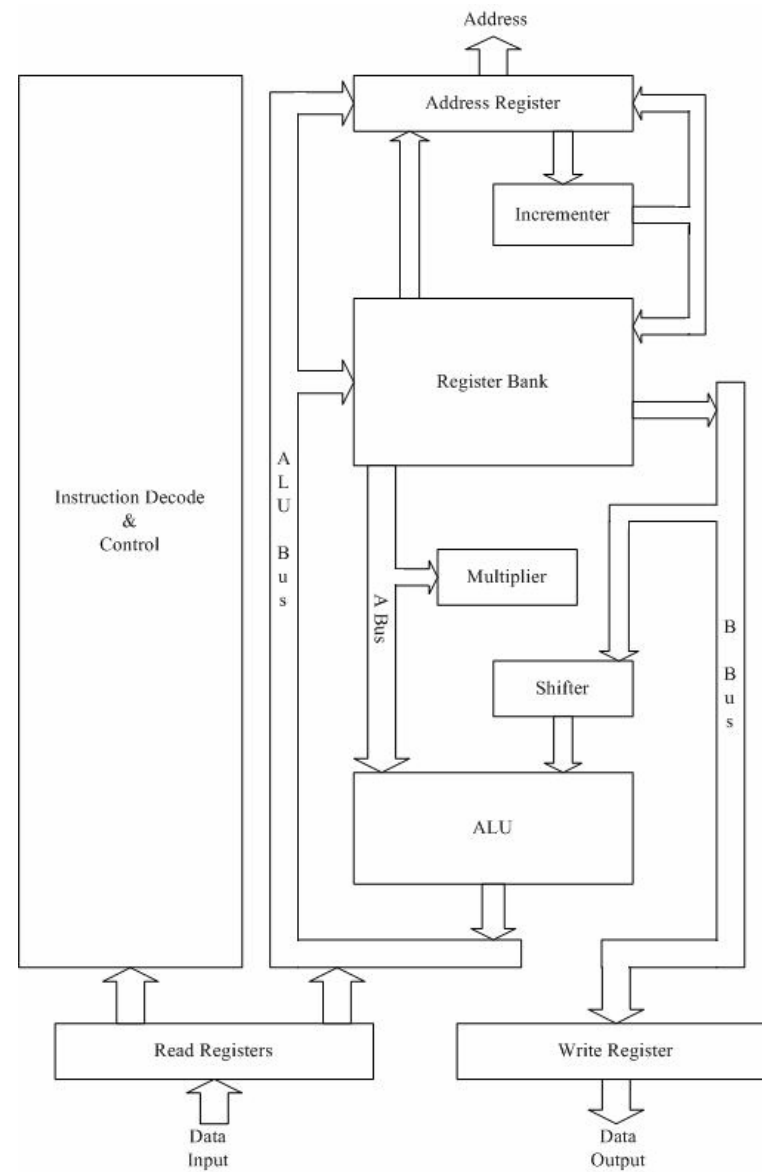

IO Signals

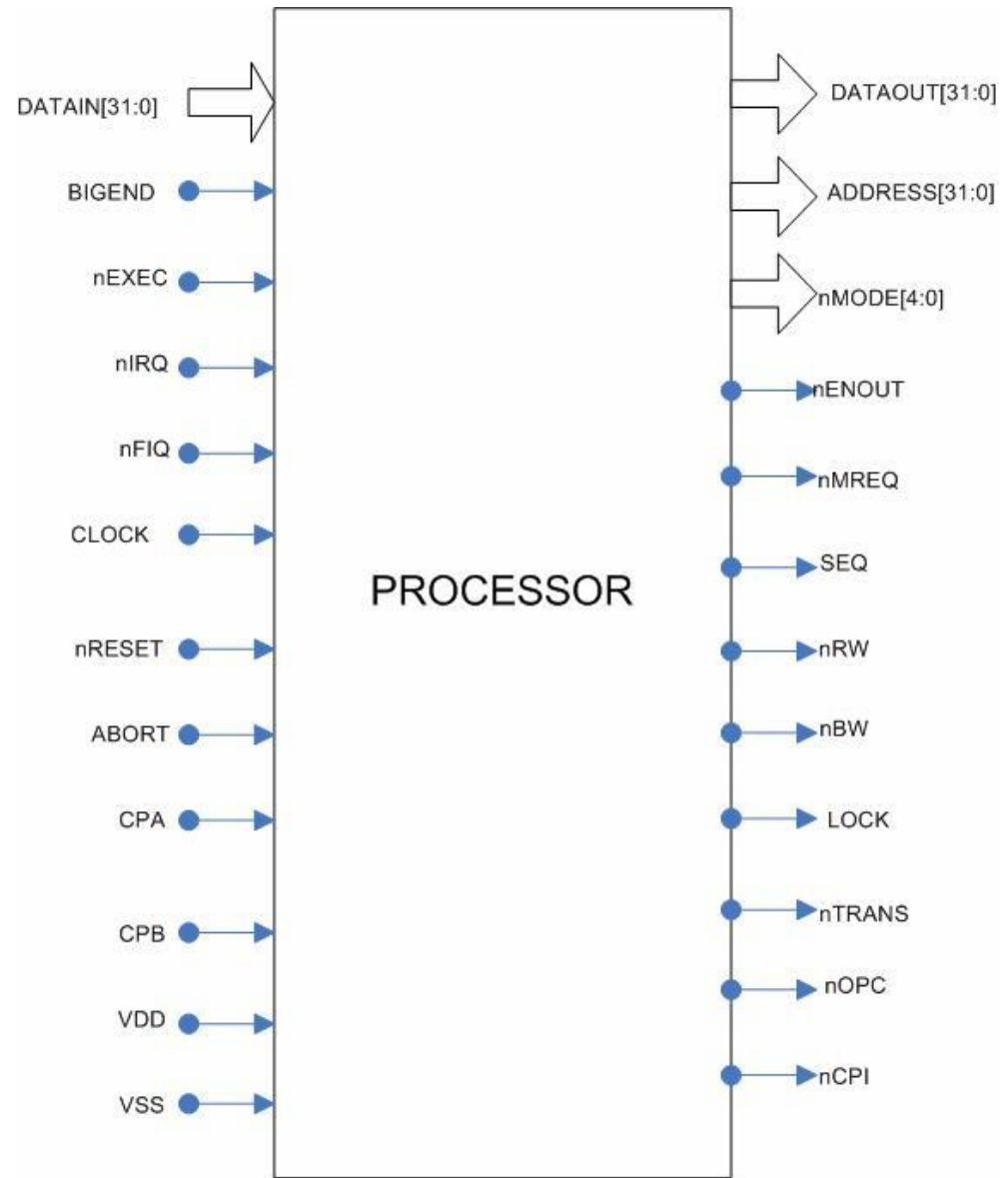




INSTRUCTION SET

Instruction Set is consisted of 34 instructions which can be divided into 12 groups:

- 1. Data processing
- 2. PSR (Program Status Register) transfer
- 3. Multiply
- 4. Single data swap
- 5. Single data transfer
- 6. Undefined Instruction
- 7. Block data transfer
- 8. Branch
- 9. Coprocessor data transfer
- 10. Coprocessor data operation
- 11. Coprocessor register transfer
- 12. Software interrupt

Conditional Execution

 


| Condition Code | Mnemonic Extension | Interpretation | Needed flag state for execution |
|----------------|--------------------|-------------------------------------|---------------------------------|
| 0000 | EQ | Equal / equals zero | Z set |
| 0001 | NE | Not equal | Z clear |
| 0010 | CS/HS | Carry set / unsigned higher or same | C set |
| 0011 | CC/LO | Carry clear / unsigned lower | C clear |
| 0100 | MI | Minus / negative | N set |
| 0101 | PL | Plus / positive | N clear |
| 0110 | VS | Overflow | V set |
| 0111 | VC | No overflow | V clear |
| 1000 | HI | Unsigned higher | C set and Z clear |
| 1001 | LS | Unsigned lower or same | C clear or Z set |
| 1010 | GE | Signed greater than or equal | N equals V |
| 1011 | LT | Signed less than | N is not equal to V |
| 1100 | GT | Signed greater than | Z clear and N equals V |
| 1101 | LE | Signed less than or equal | Z set or N isn't equal to V |
| 1110 | AL | Always | Any |
| 1111 | NV | Never | None |



Components of the Processor

- Read registers
- Write register
- Address register
- Incrementer
- Register bank
- Multiplier
- Shifter
- ALU
- Controller


Read Registers

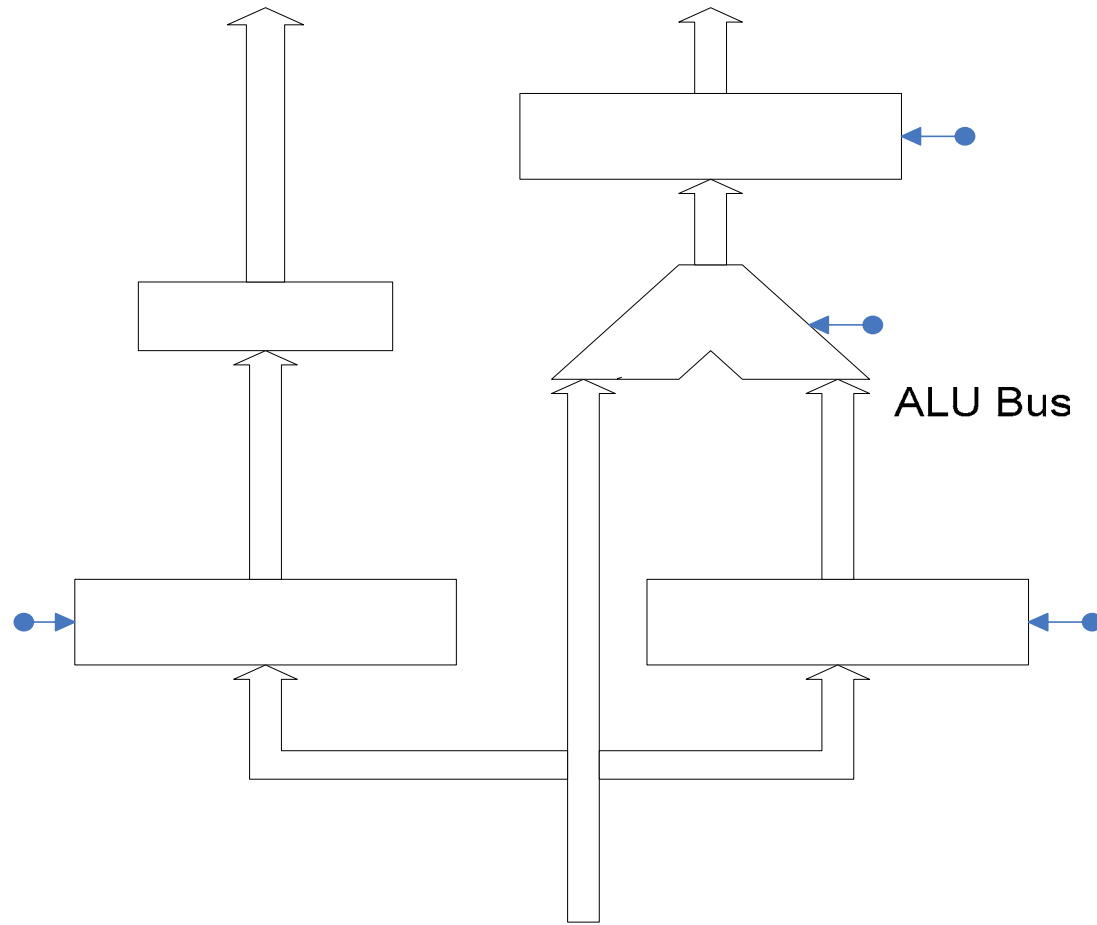


Adjuster

Instru


C

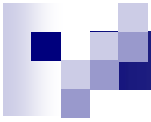

Register Bank

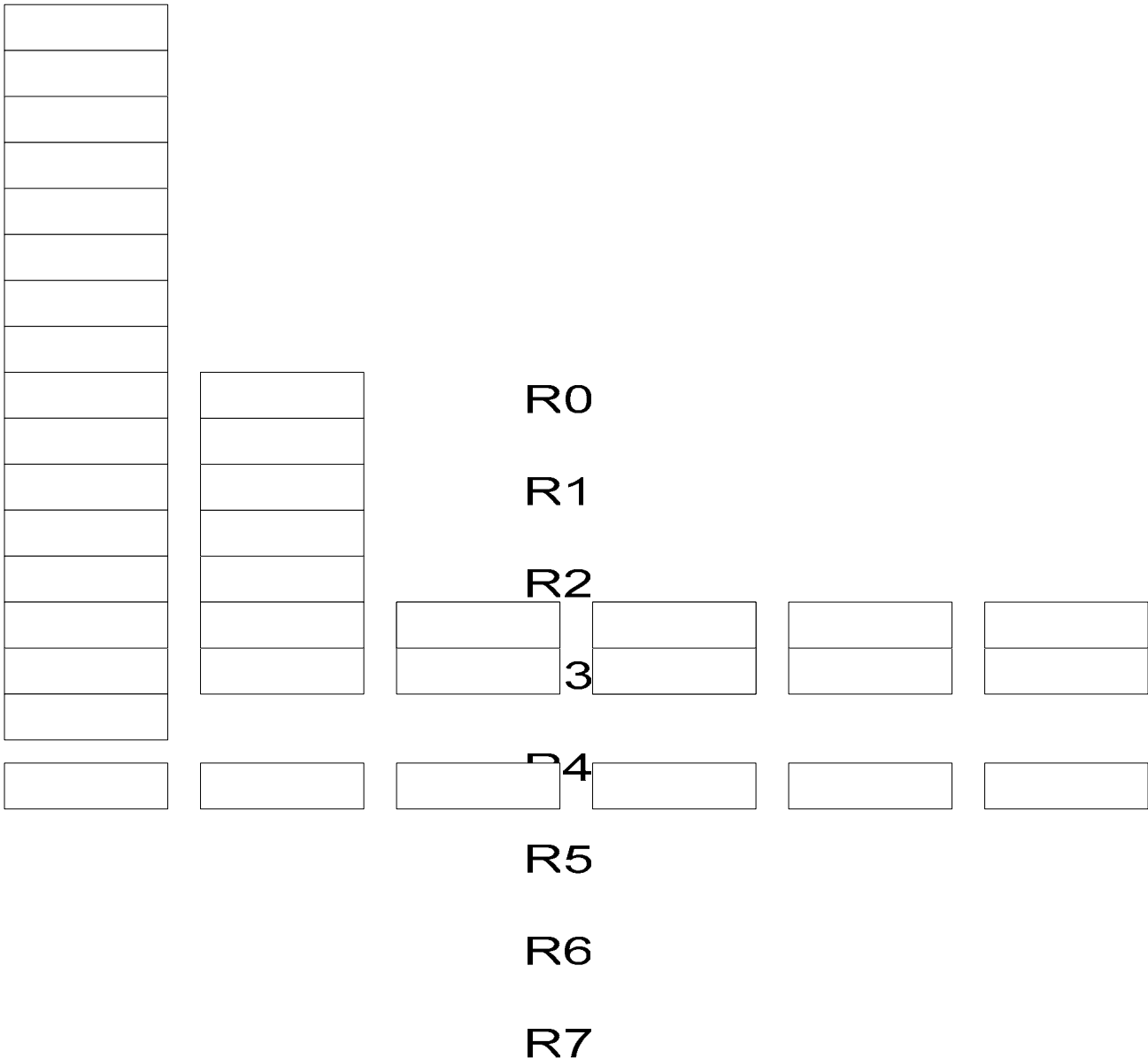

Multiplier

 


| Carry In | Multiplier | Shift | ALU | Carry Out |
|----------|------------|-----------|-----|-----------|
| 0 | 0 | LSL(2N) | A+0 | 0 |
| 0 | 1 | LSL(2N) | A+B | 0 |
| 0 | 2 | LSL(2N+1) | A-B | 1 |
| 0 | 3 | LSL(2N) | A-B | 1 |
| 1 | 0 | LSL(2N) | A+B | 0 |
| 1 | 1 | LSL(2N+1) | A+B | 0 |
| 1 | 2 | LSL(2N) | A-B | 1 |
| 1 | 3 | LSL(2N) | A+0 | 1 |


Multipl

Latch_a_bus


Shifter

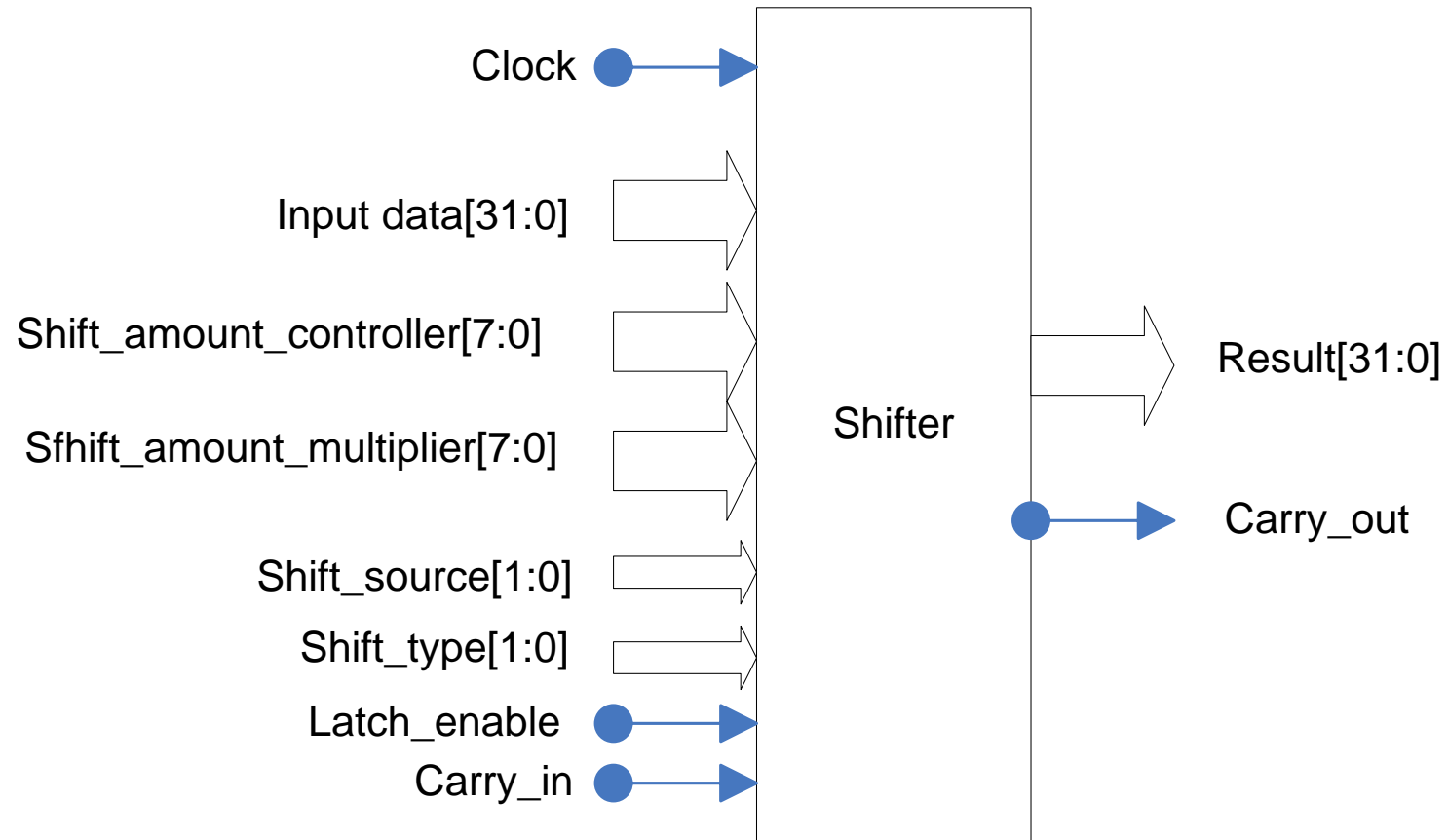

ALU

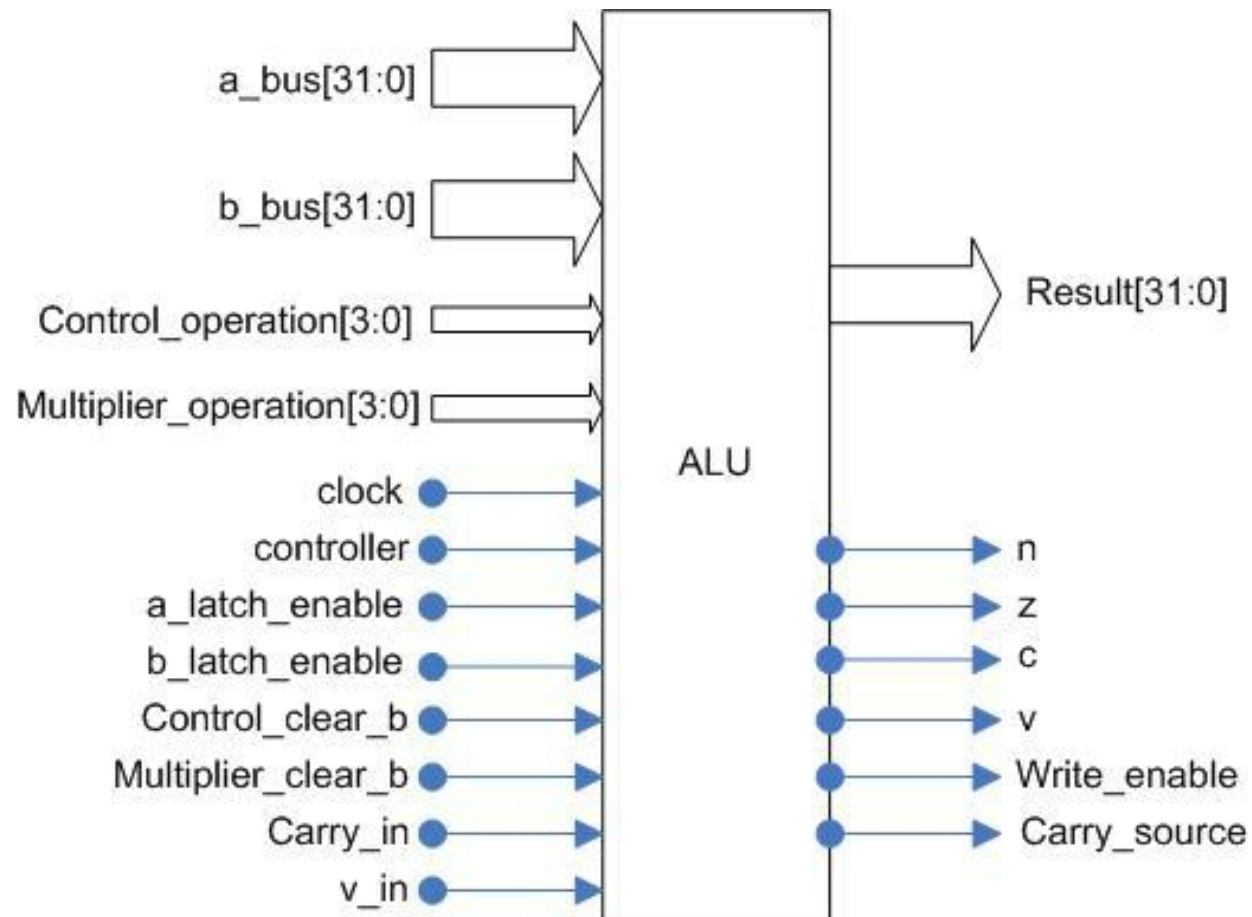

Architecture of the ALU


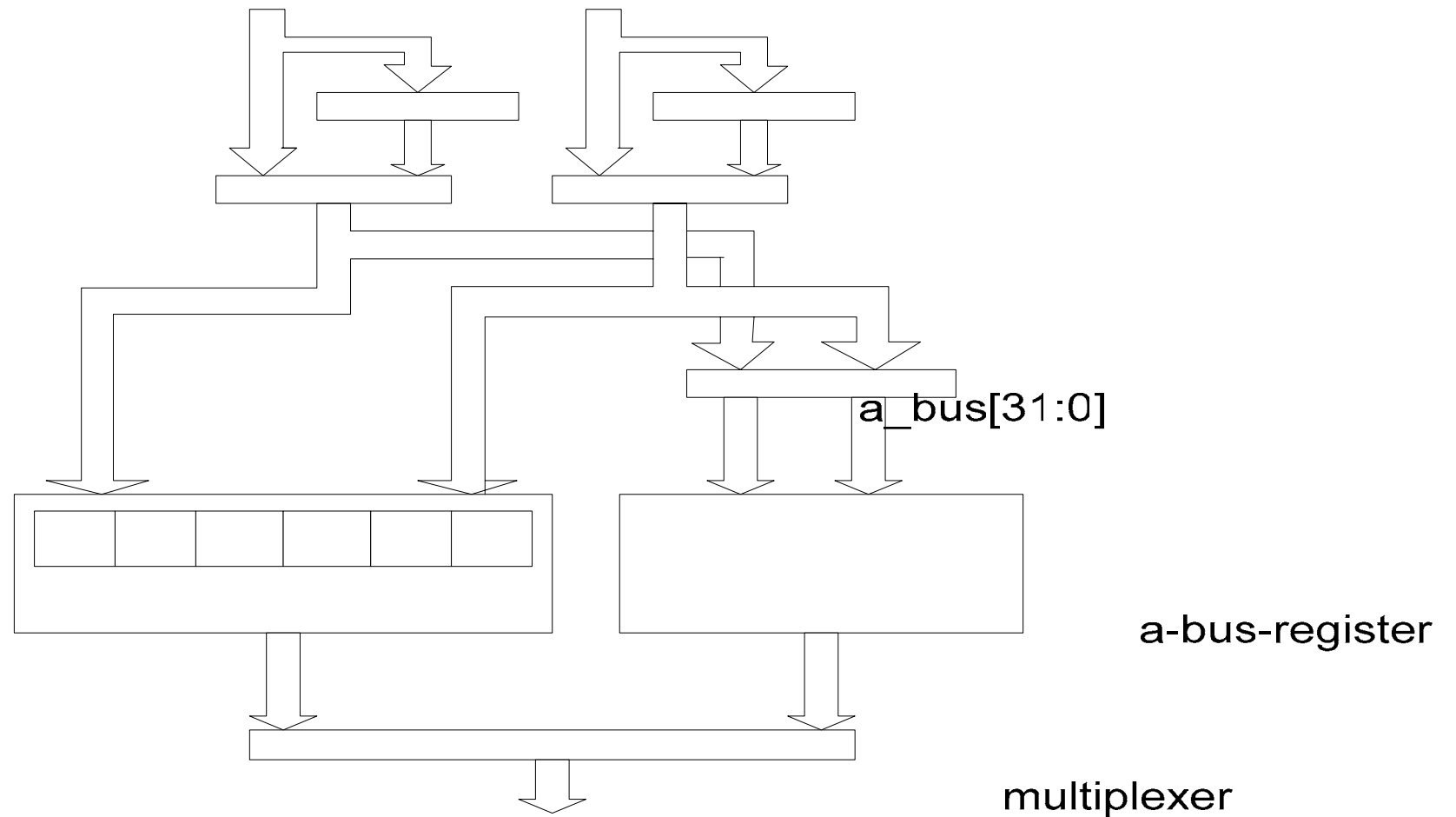




Controller

- Instruction decoding
- FSM
- Interrupt handler
- Pipeline Registers


FSM - Data Processing

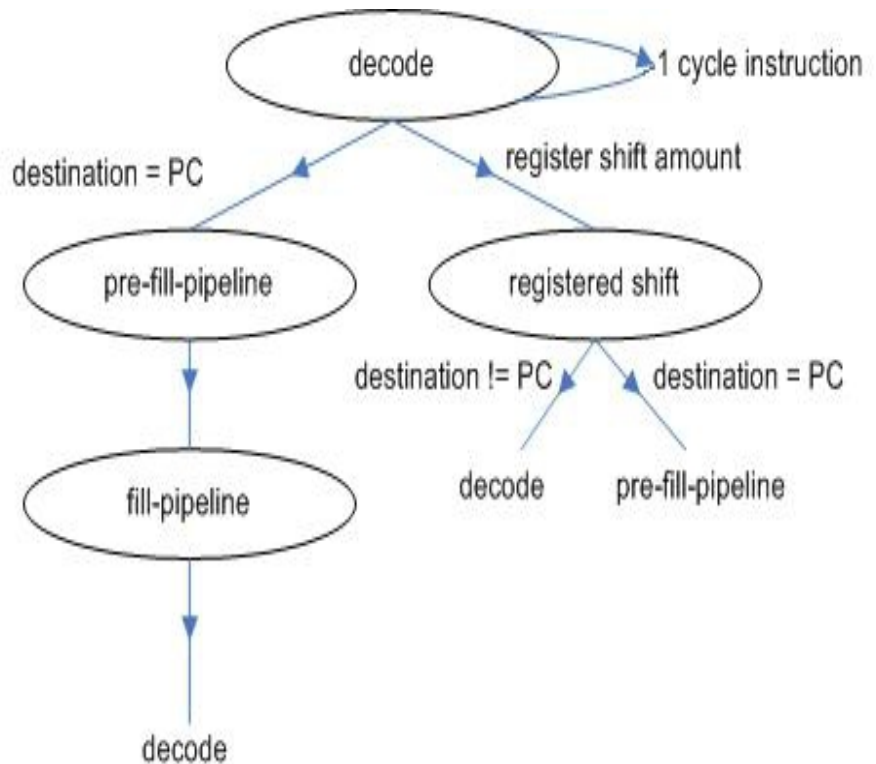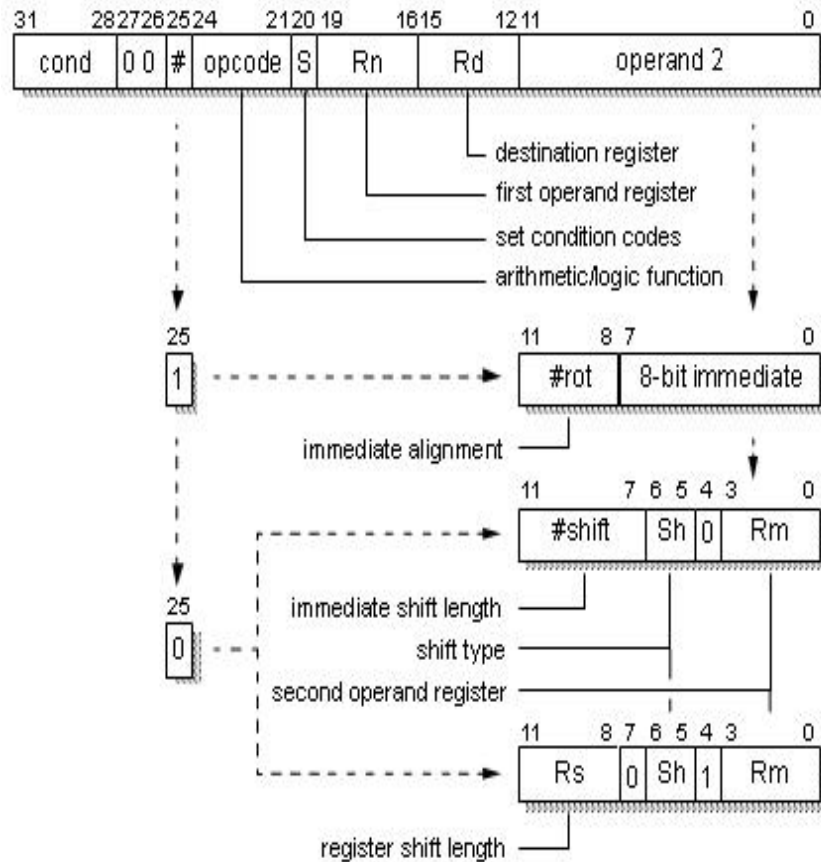



FSM - Multiply




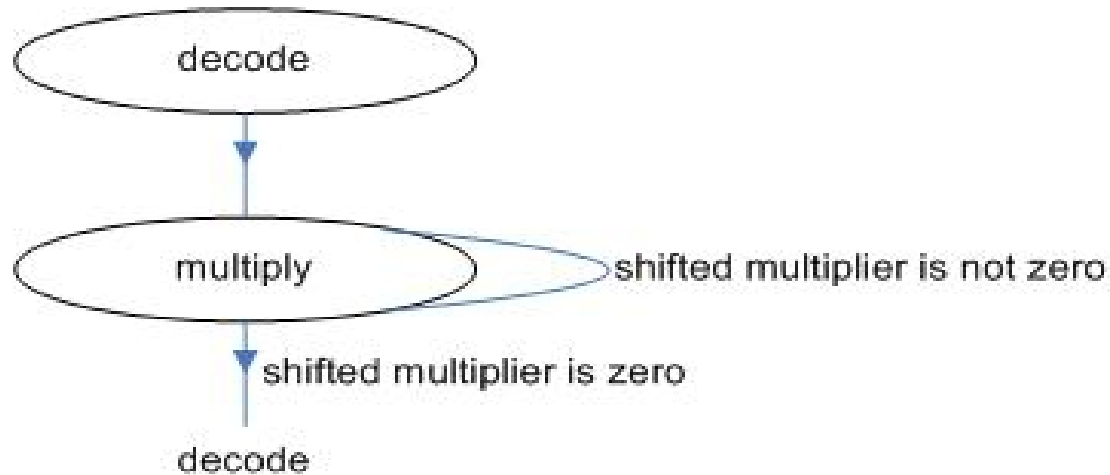
mul = 000; Rd = Rm x Rs
mul = 001; Rd = Rm x Rs + Rn




FSM – Single Load

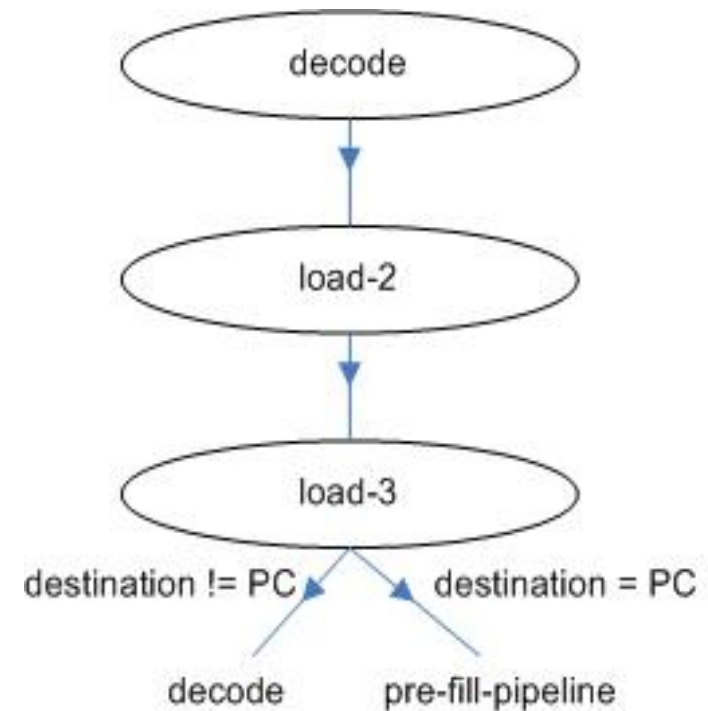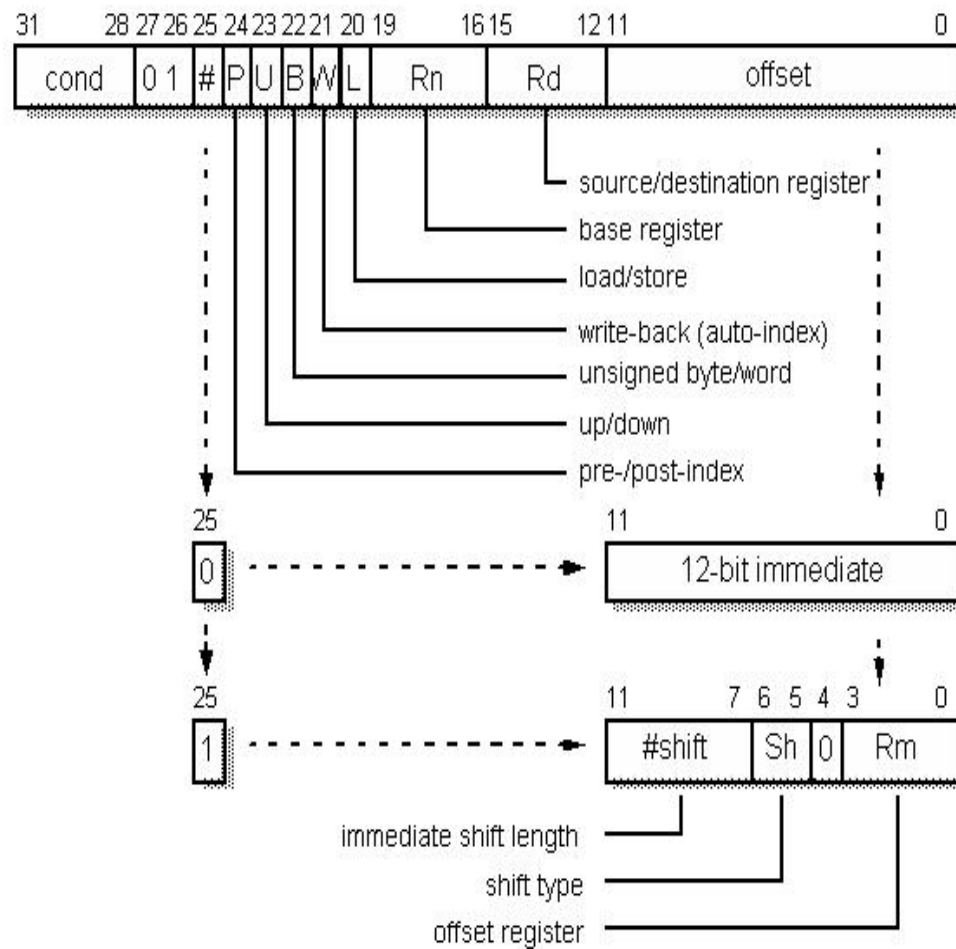


FSM – Multiple Transfer

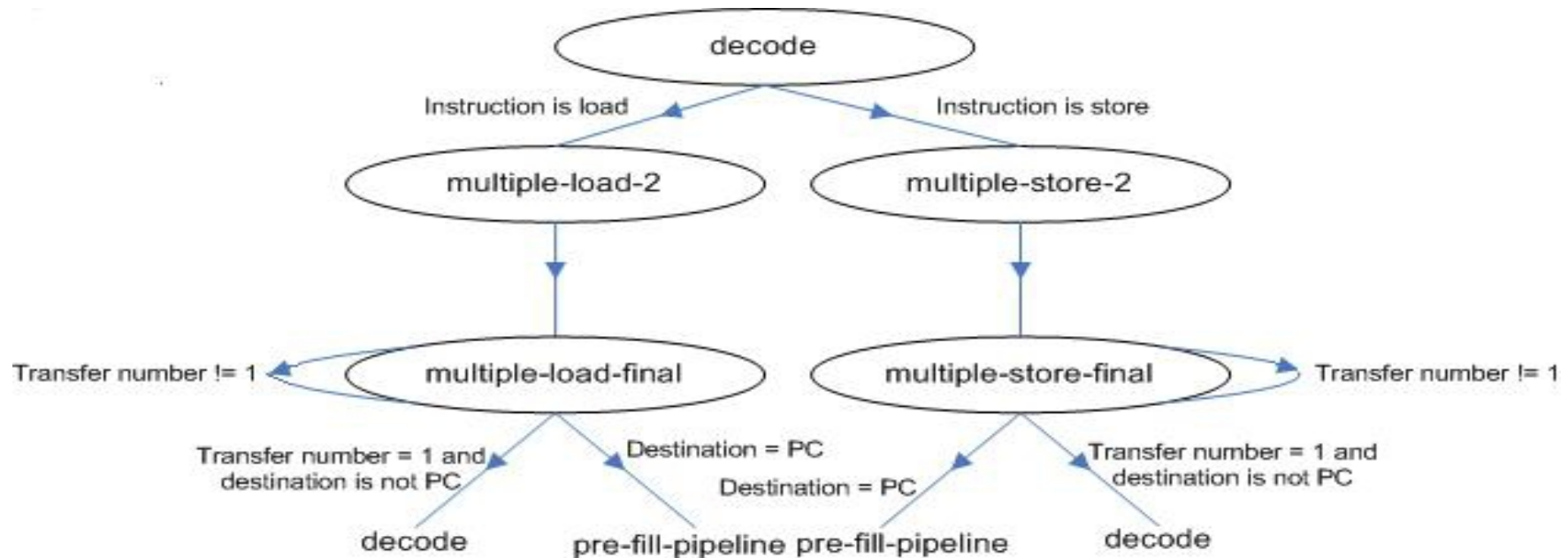 


Coprocessor Register Transfer

 

 load from coprocessor/store to coprocessor




Interrupt Handler

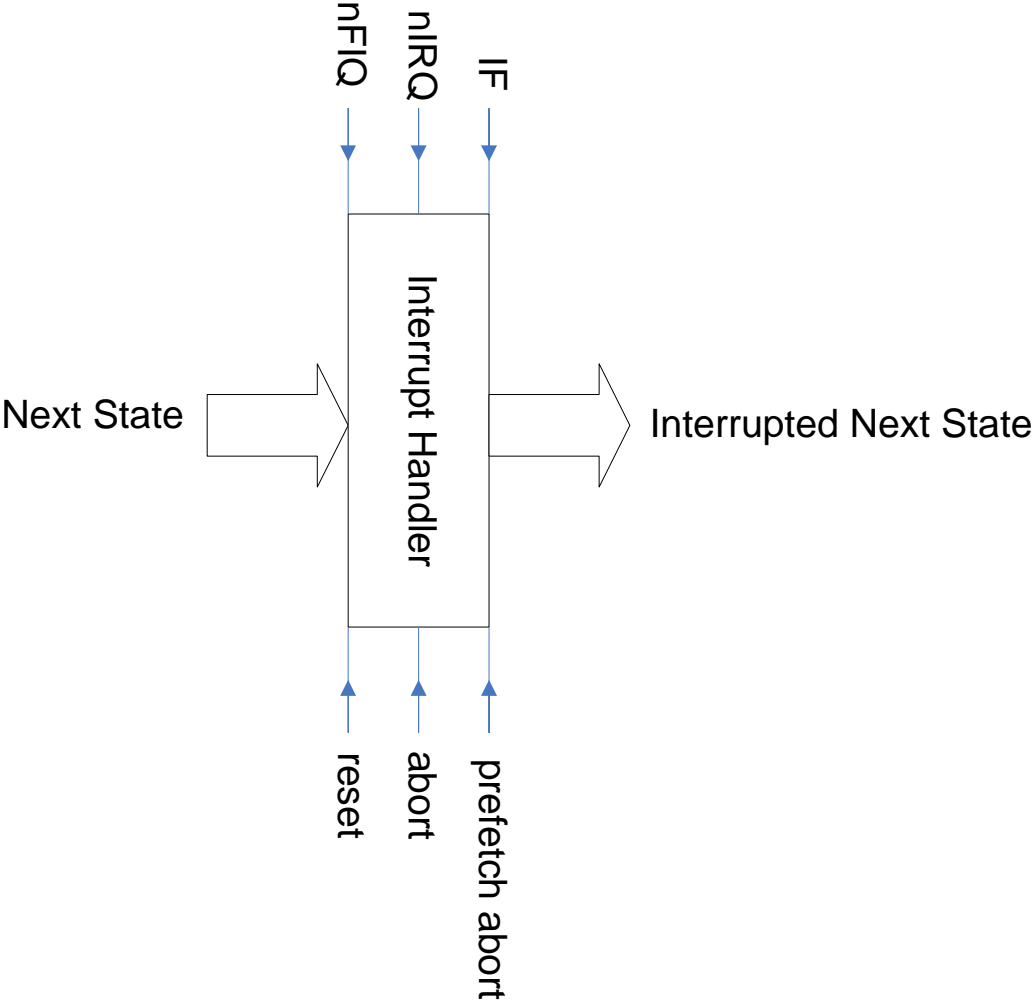




SYNTHESIS


Optimization

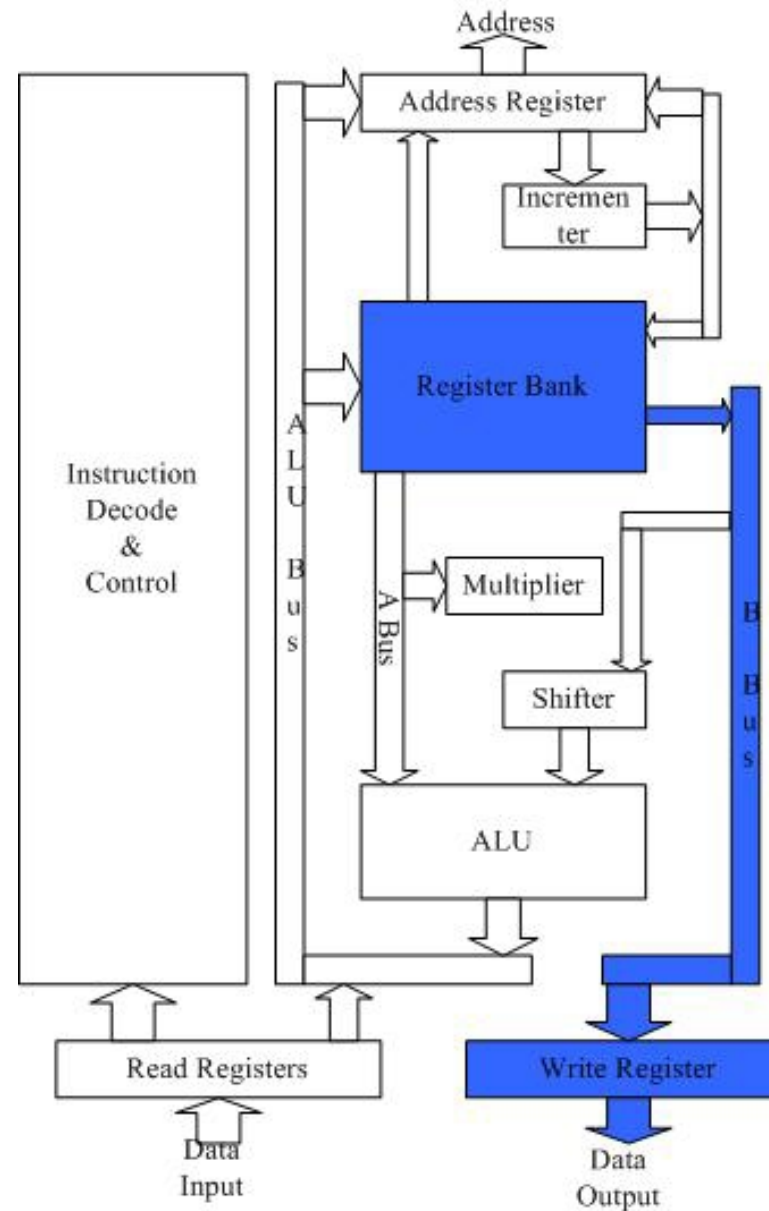


Optimization

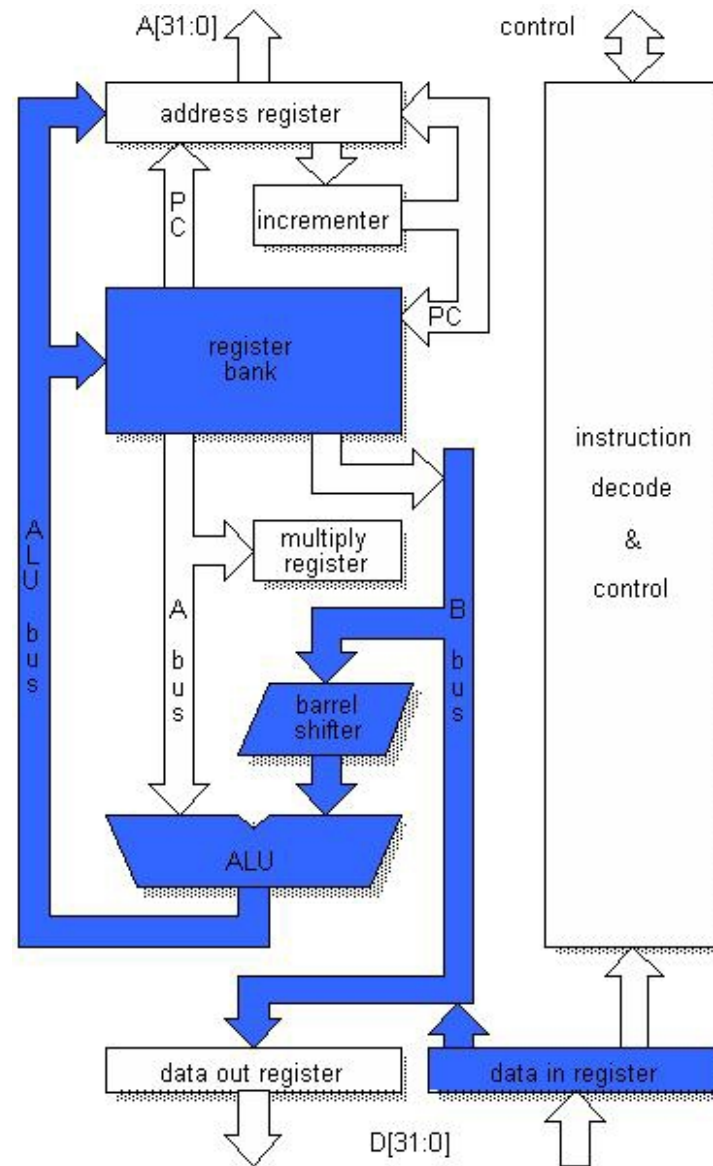


Optimization

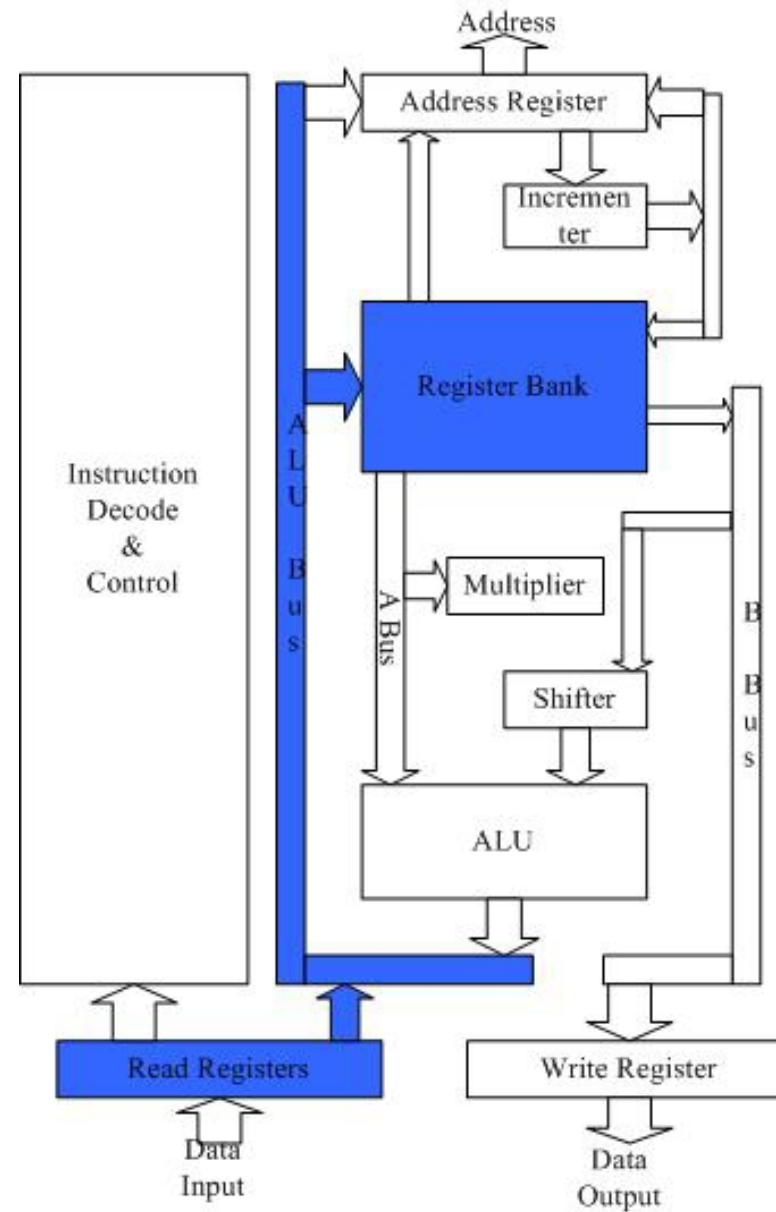


Optimization

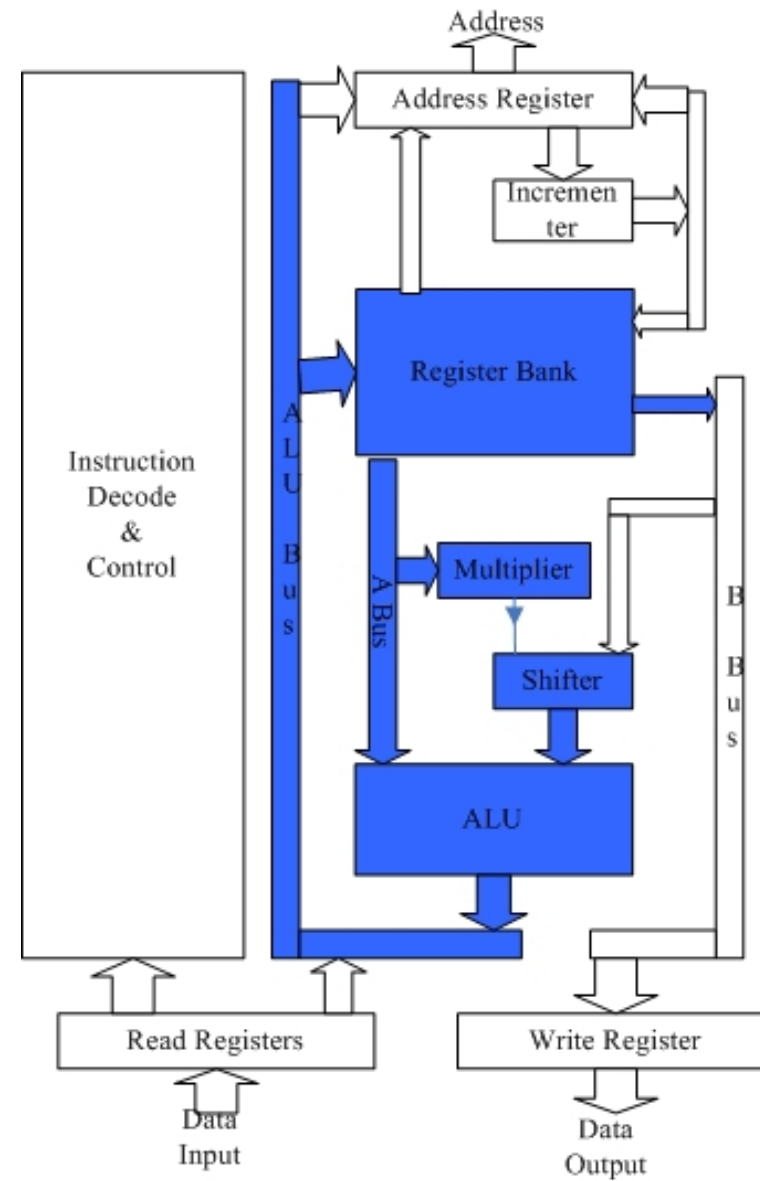

ALU before being modified

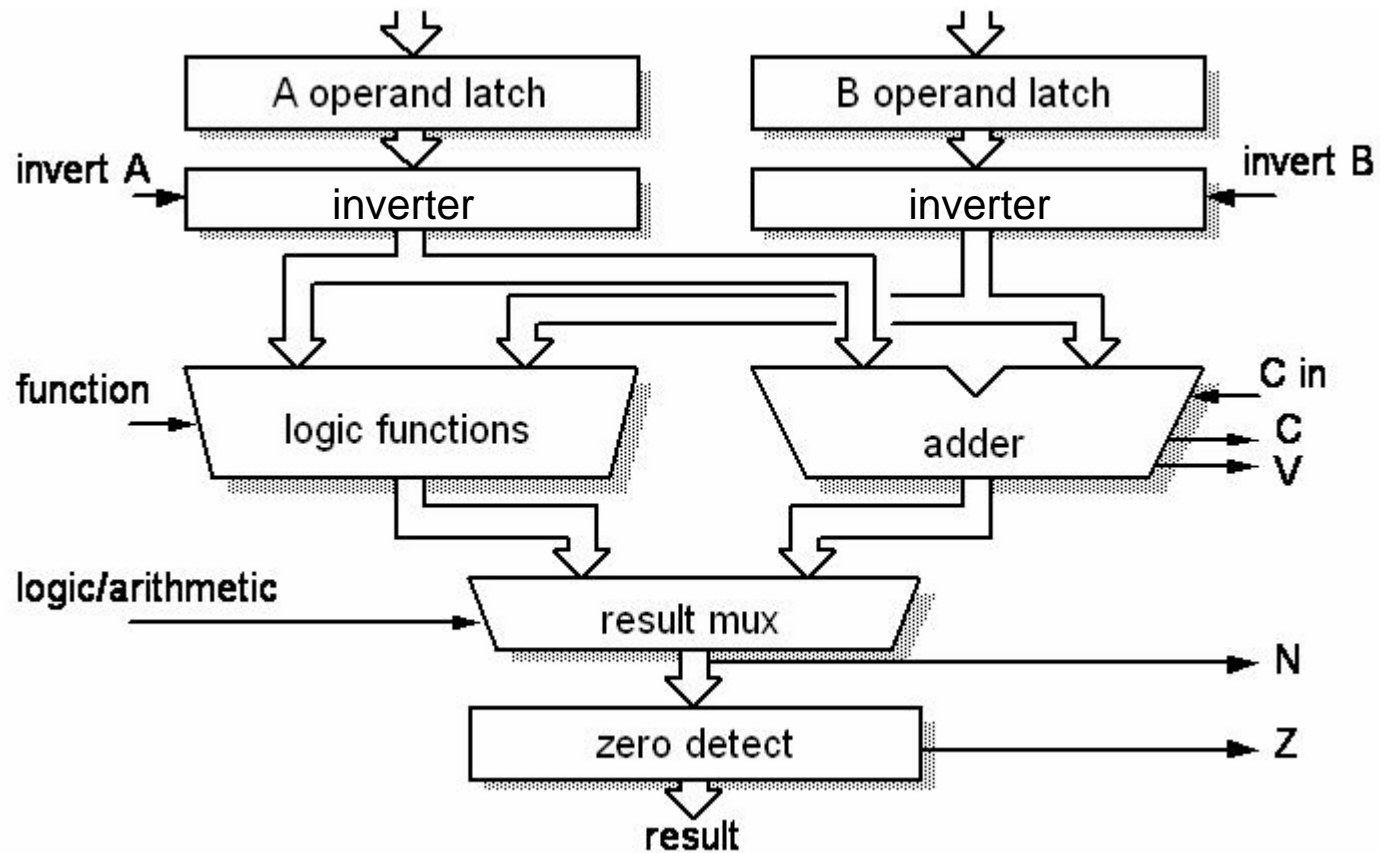

ALU after being modified

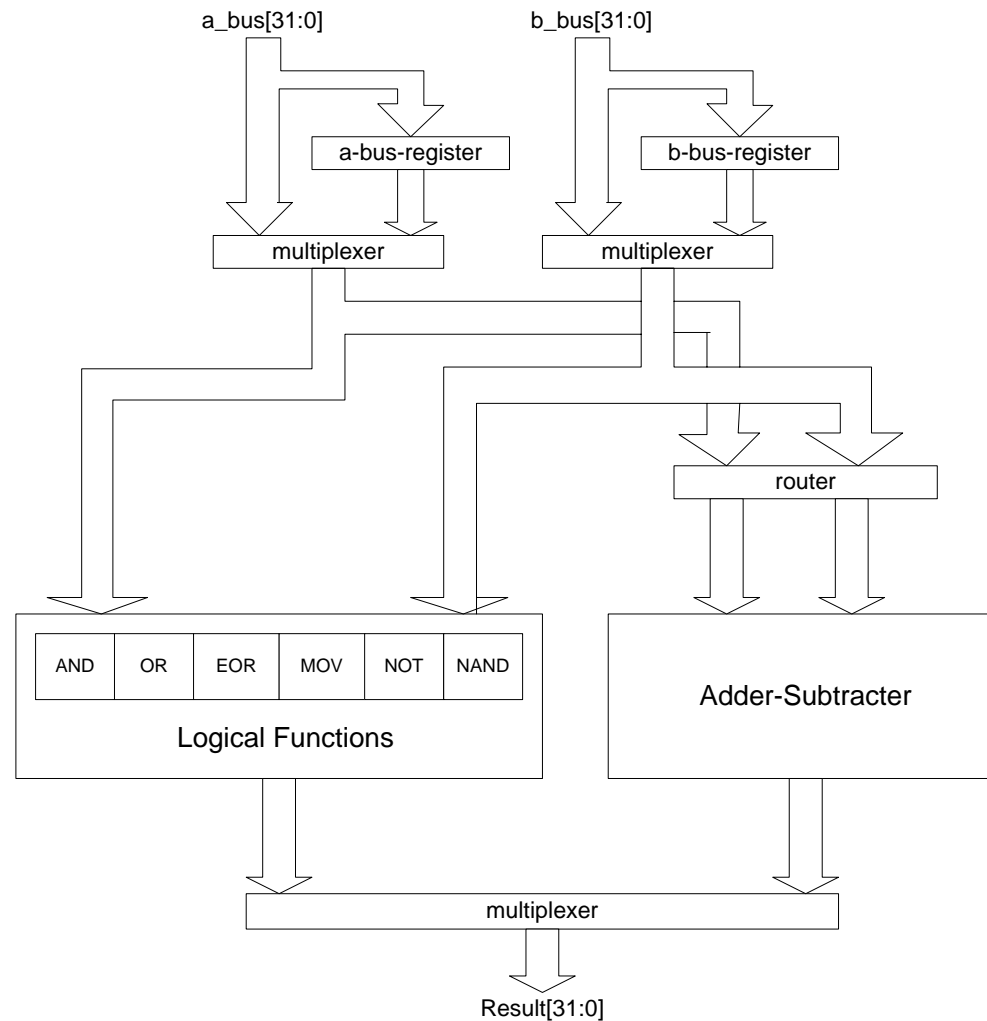




PLACE & ROUTE

- DRC has 0 error count.
- LVS check has passed.
- Post layout simulation has no timing violations.

Layout with Bonding Diagram

 





SIMULATION RESULTS

- Load Instruction
- Multiply Instruction


Load – Instruction decoding

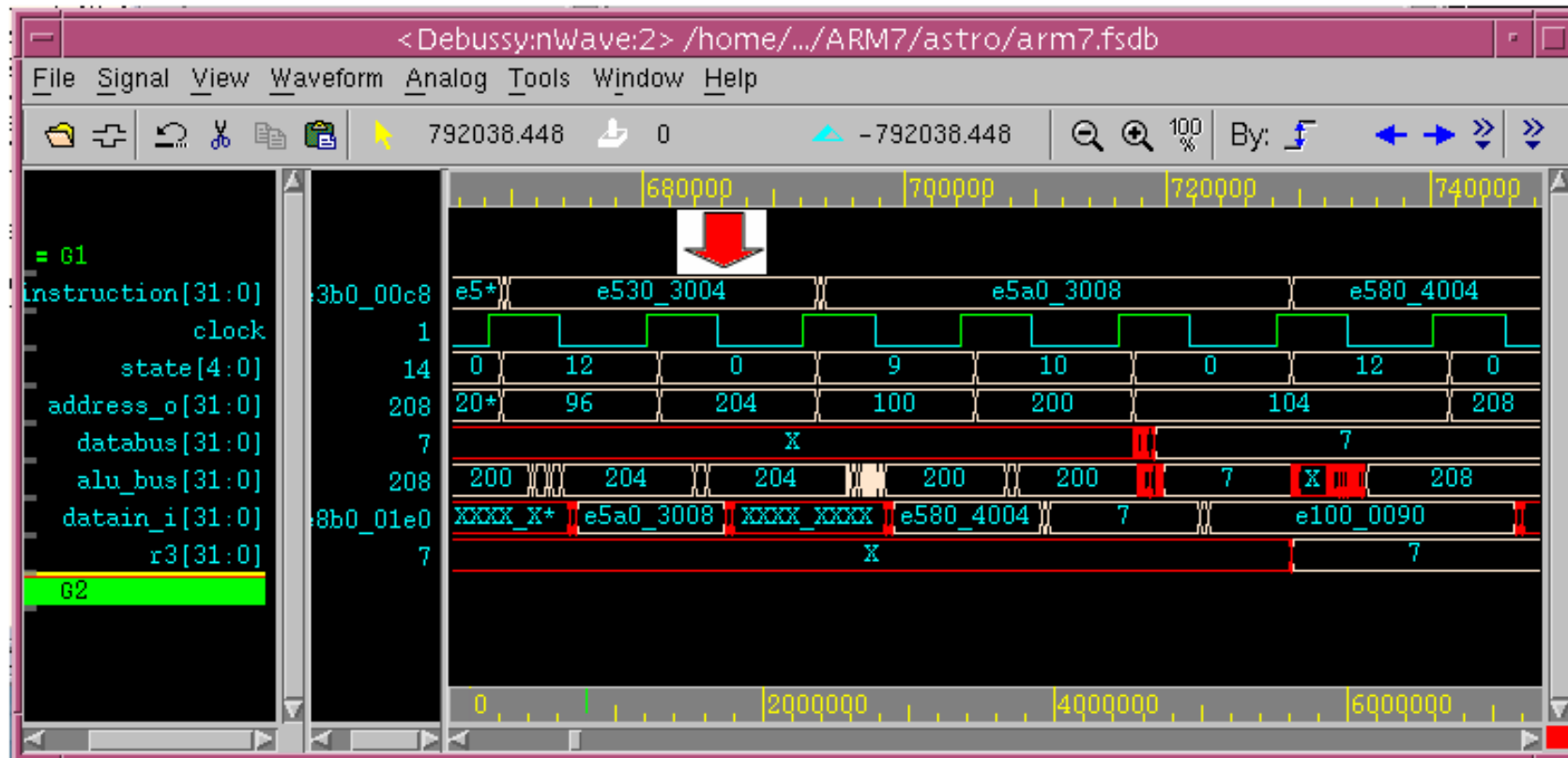


Load – Cycle 1

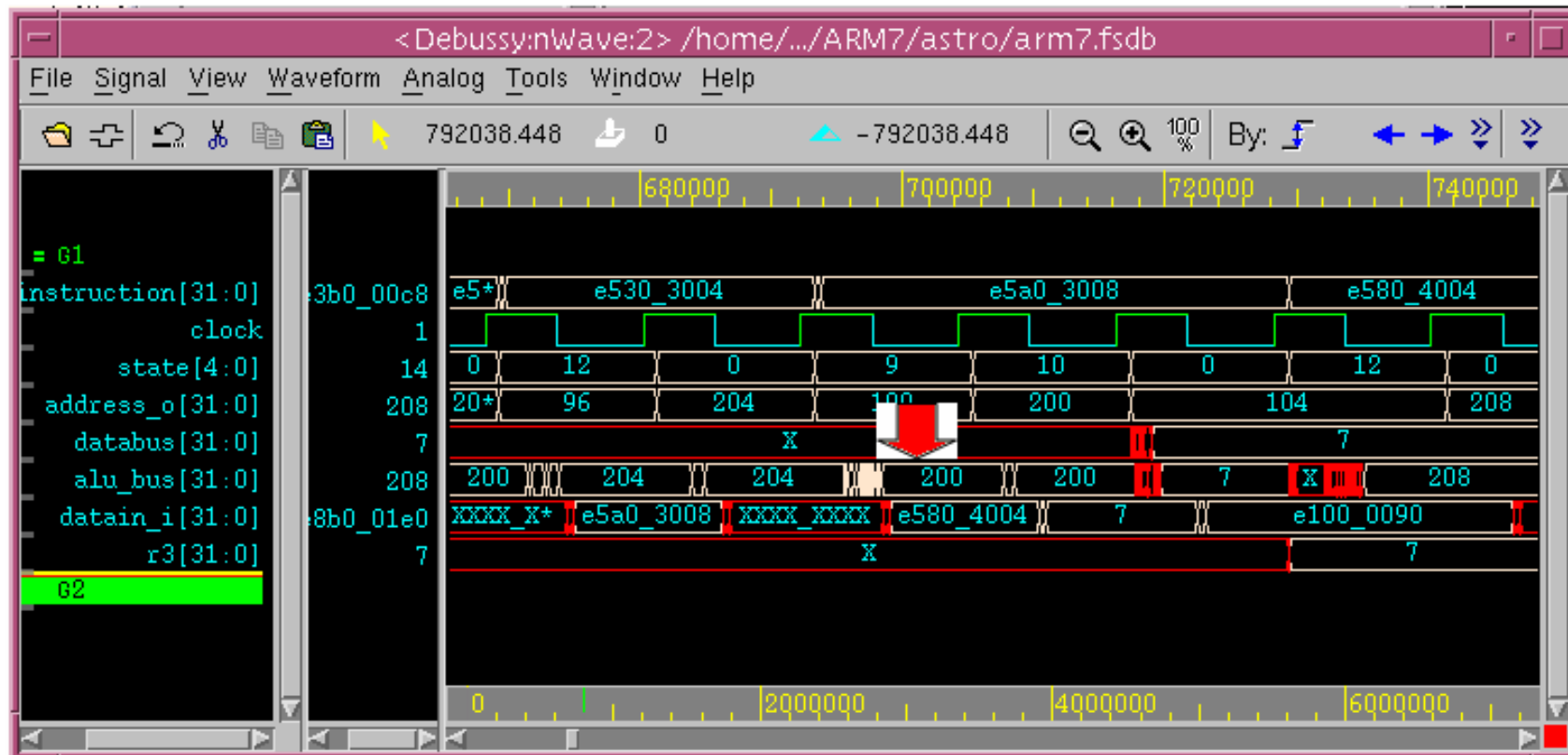


Load – Cycle 2

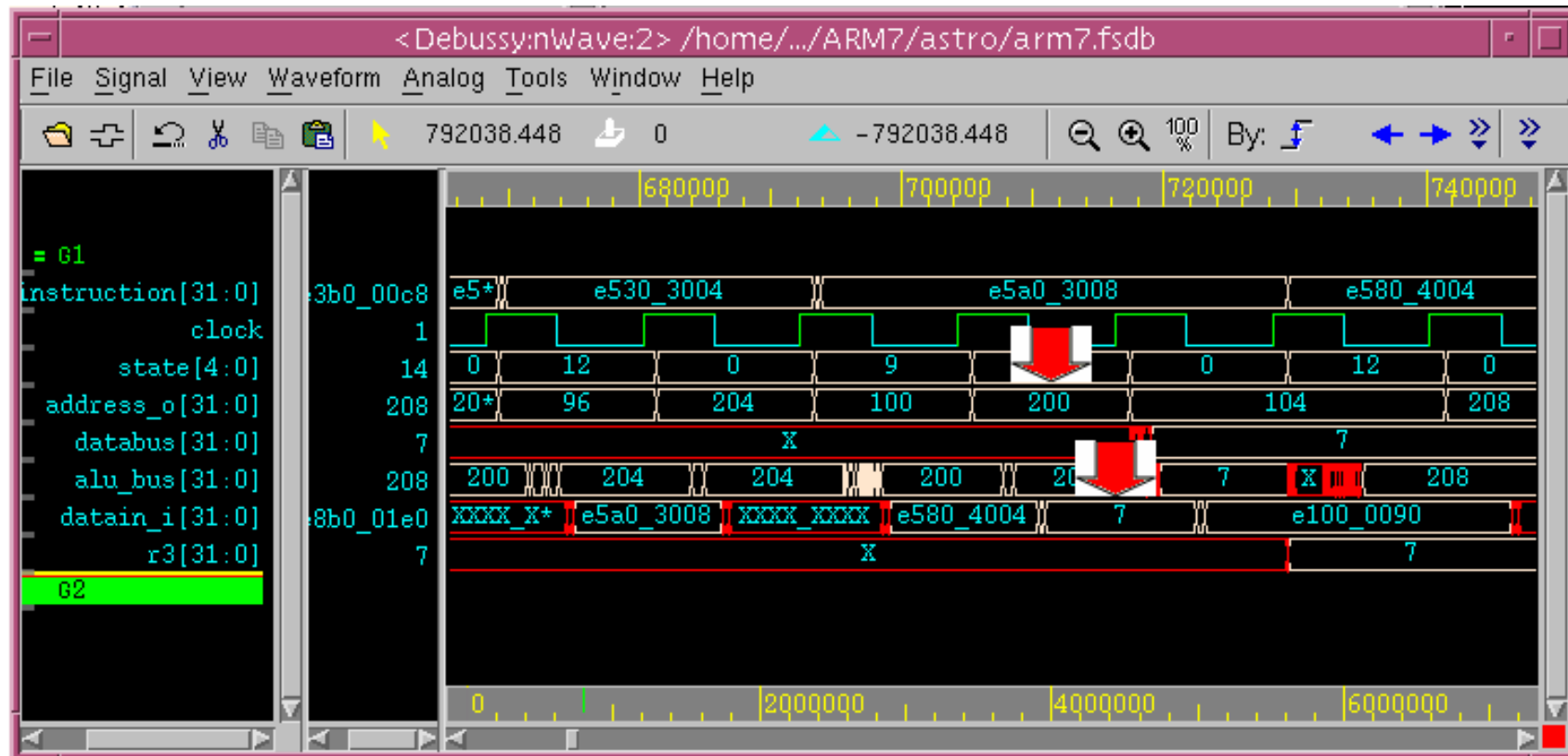


Load – Cycle 3

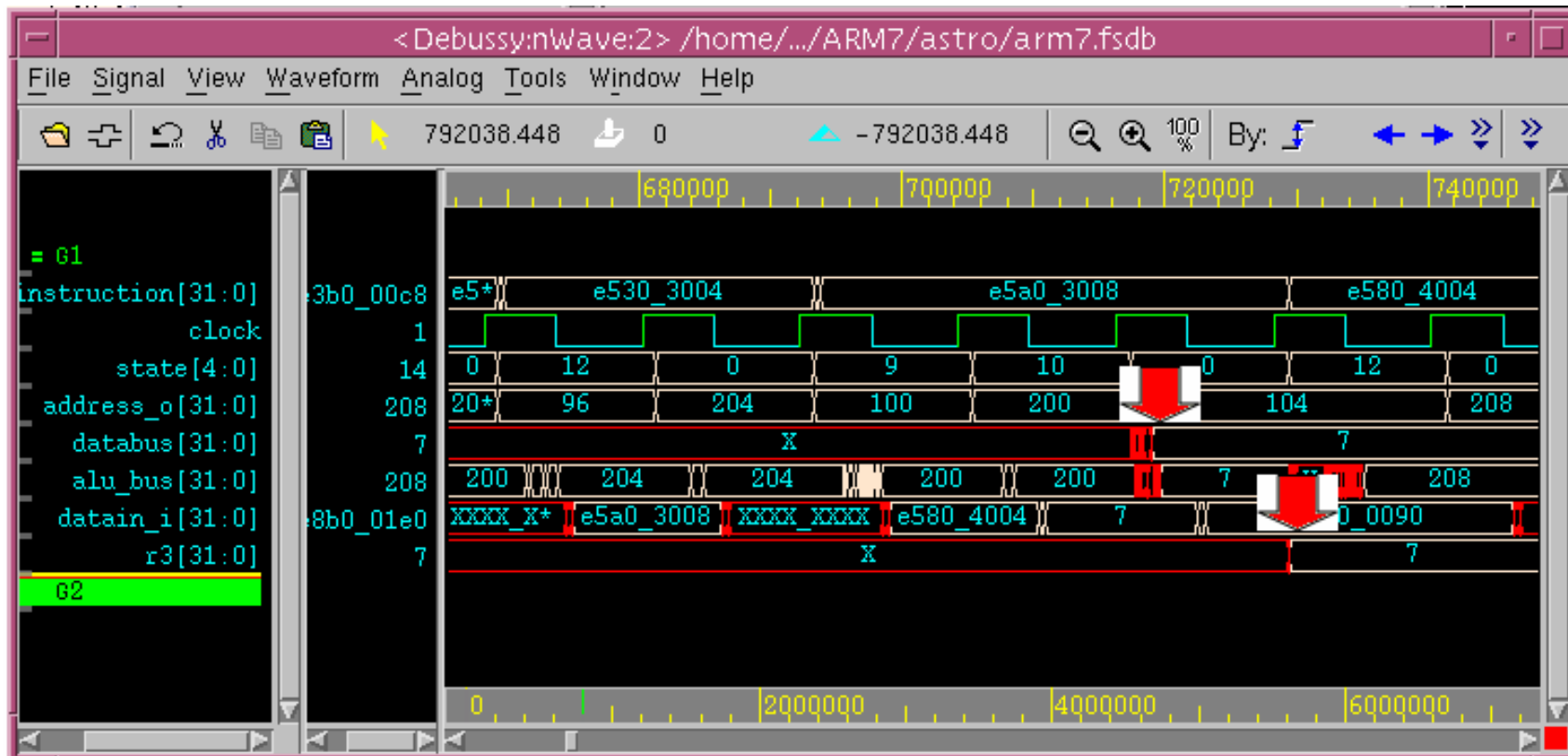

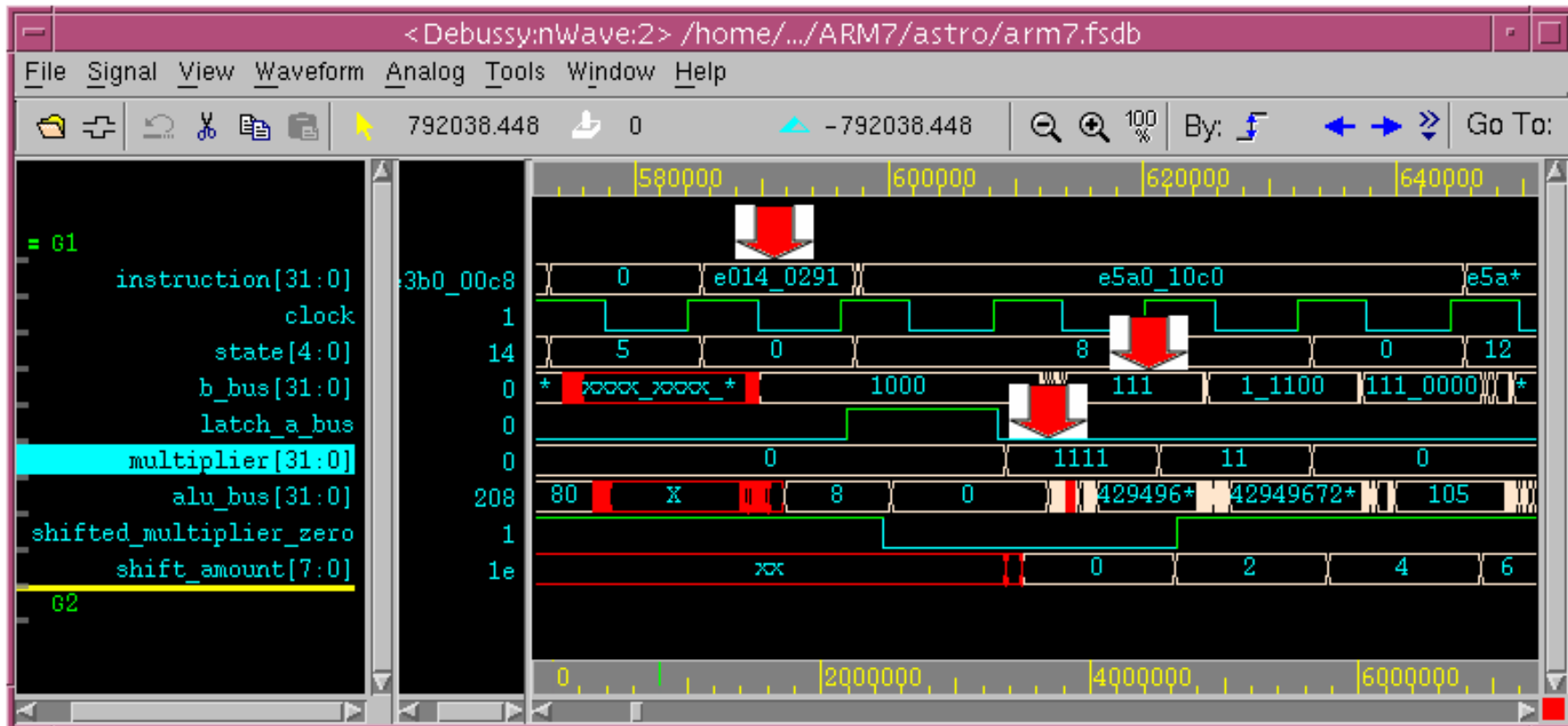
Multiply – Decoding, Multiplier, Multiplicand



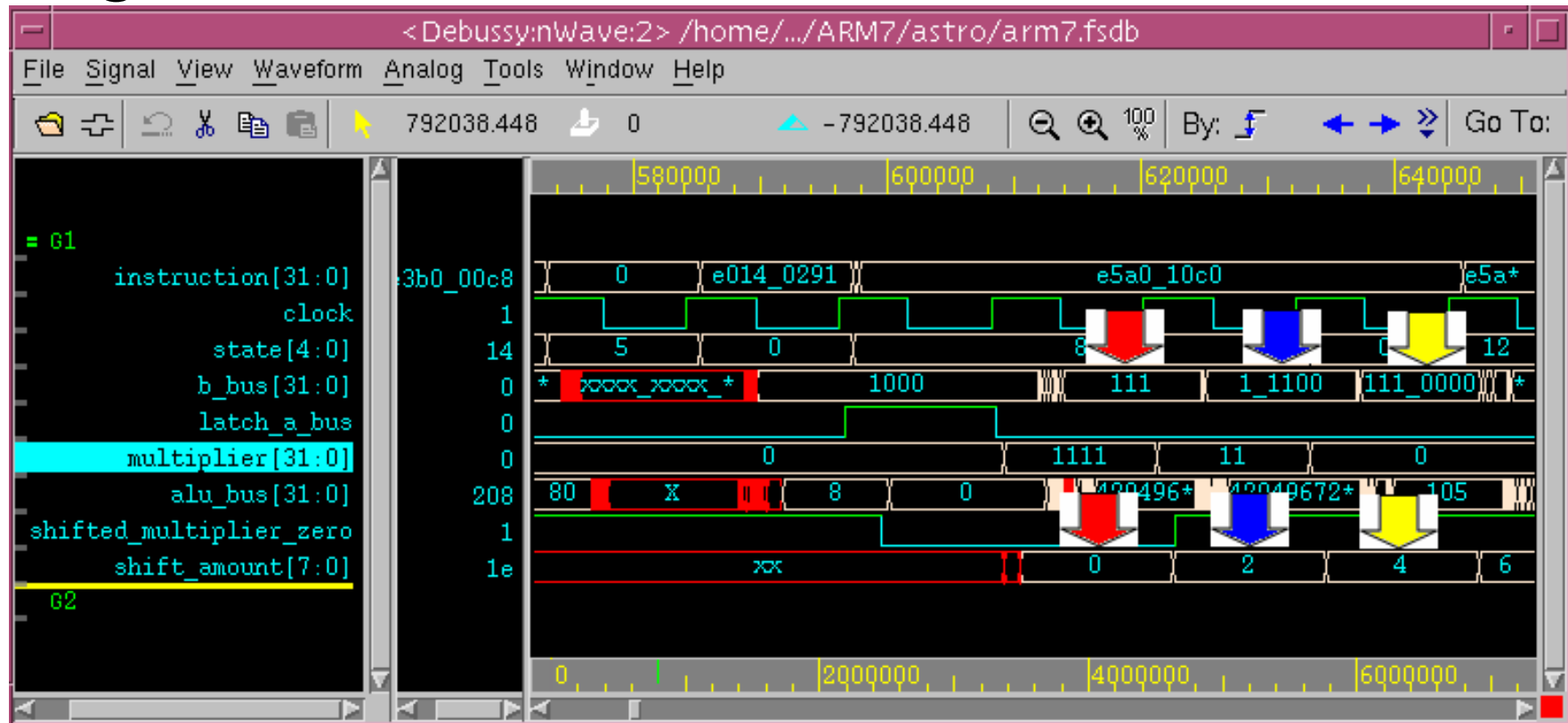
Multiply – Multiplicand is shifted left in each cycle according to Booth's algorithm



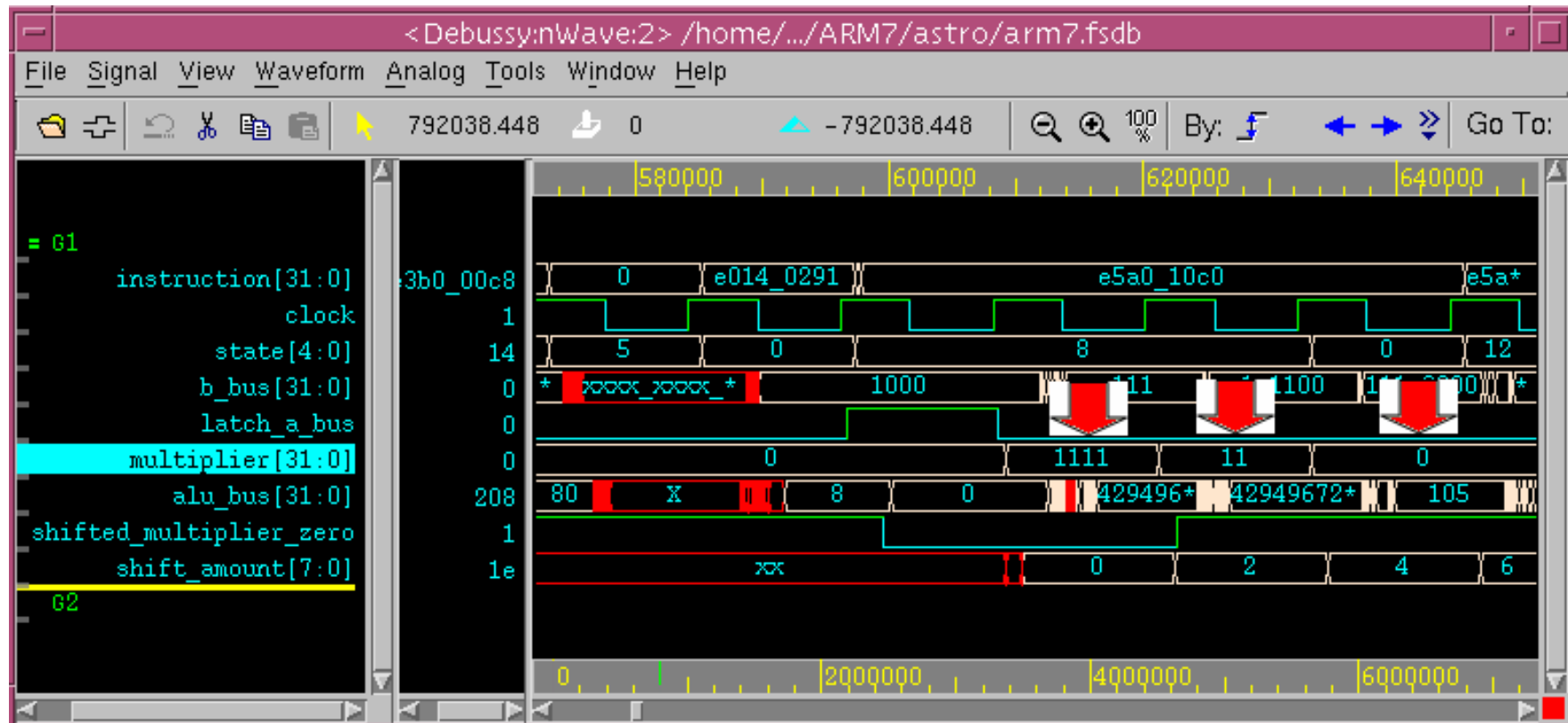
Multiply – Multiplier is shifted right 2 bits in each cycle



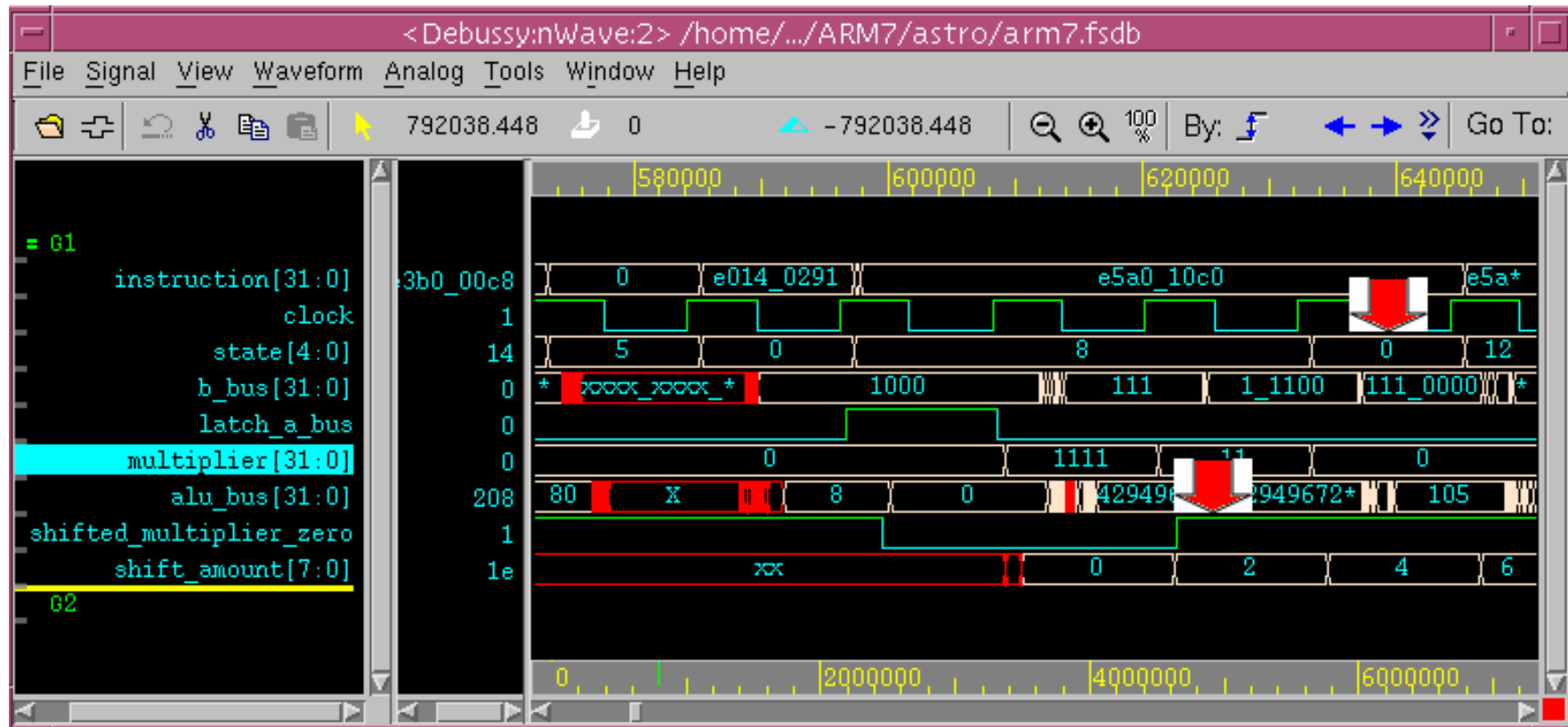Multiply – The instruction completes when the shifted multiplier becomes zero



Multiply – The result is on ALU bus

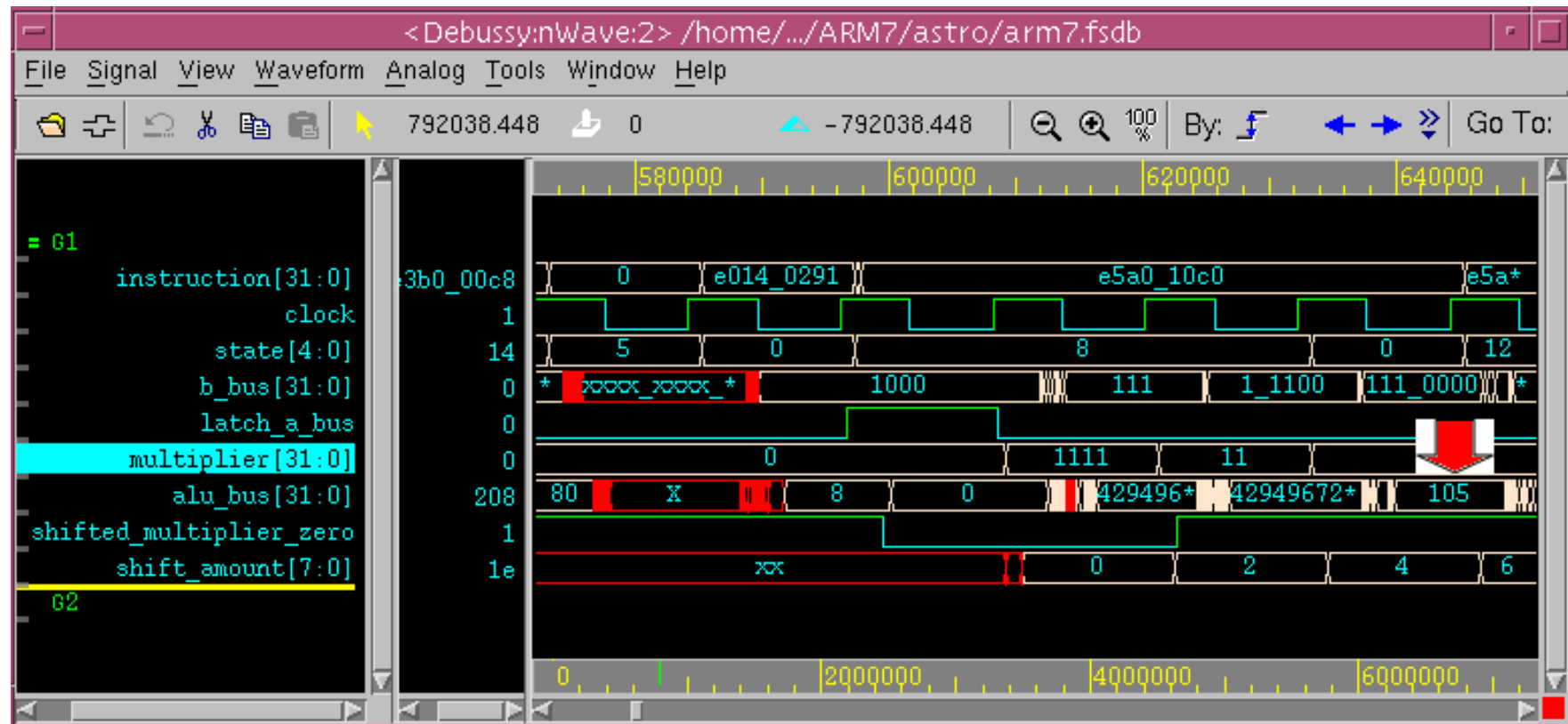




CONCLUSION

(Max frequency before optimizations: 70Mhz)

| Specifications | |
|-----------------------------|---------|
| Maximum operating frequency | 90 MHz |
| Test frequency | 10 MHz |
| Power supply voltage | 1.8V |
| Power | 30.9 mW |
| Gate count | 286547 |
| Area | 7.97 |
| Instruction count | 34 |
| Datapath width | 32 bits |

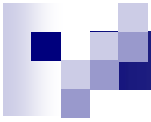

THANK YOU