

Chapter 14 Two-port networks

14.1 Two-ports and impedance parameters

two-port concept, impedance parameters, reciprocal networks

14.2 Admittance, hybrid, and transmission parameters

admittance parameters, hybrid parameters, transmission parameters, parameter conversion

14.3 Circuit analysis with two-ports


terminated two-ports, two-ports in cascade, two-ports in series, two-ports in parallel

14.1 Two-ports and impedance parameters

Basics

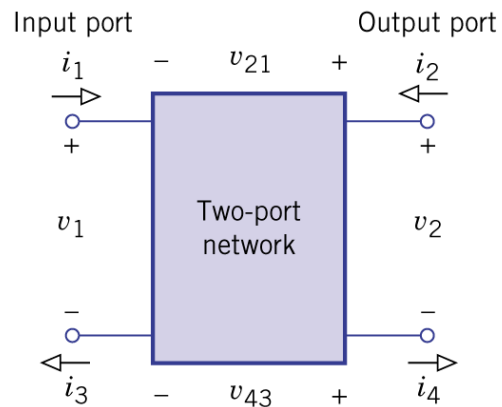
1. Two-port network

- a four-terminal network with input port and output port
- the network characteristics is completely described by v_1, i_1, v_2, i_2
- a useful method to analyze filter, amplifier,....
- can be extended to multi-port networks




$$i_1 = i_3, i_2 = i_4$$

v_{21} and v_{43} are not concerned

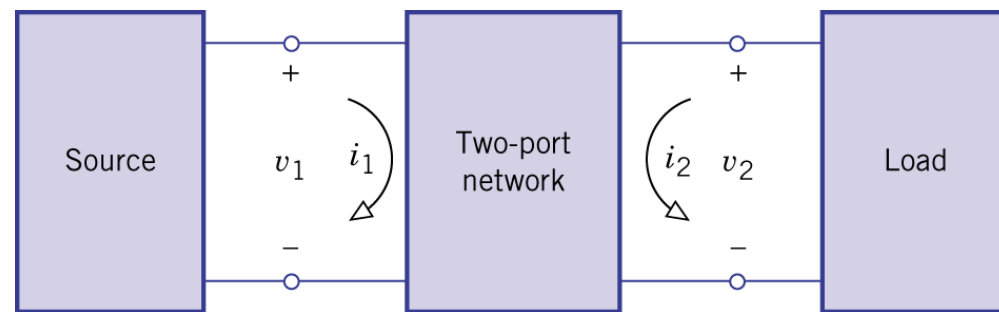

No independent sources are in the two-port network and load.


2. O.C. impedance parameters

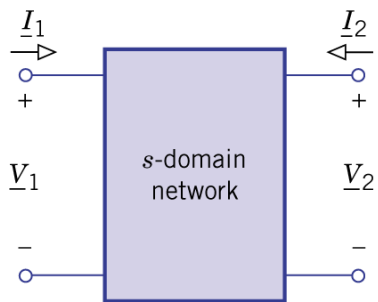

sources : i_1, i_2 , responses : v_1, v_2

in s-domain :
$$\begin{cases} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \\ \underline{V}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2 \end{cases} \rightarrow \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = [\underline{z}] \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$
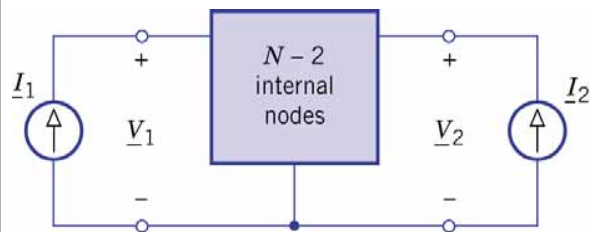
$$[\underline{z}] \equiv \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} : \text{o.c. impedance parameter matrix}$$



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} : \text{input impedance at port 1 with port 2 o.c.}$$


$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} : \text{input impedance at port 2 with port 1 o.c.}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} : \text{reverse transfer impedance with port 1 o.c.}$$


$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} : \text{forward transfer impedance with port 2 o.c.}$$

Discussion

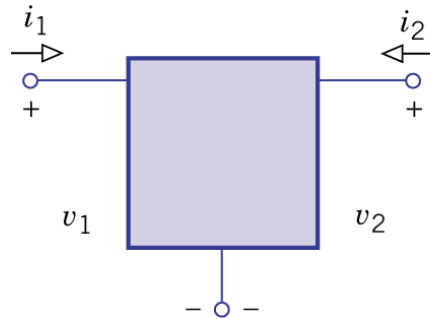1. Most two-port networks are three-terminal networks.



(a) Three-terminal network

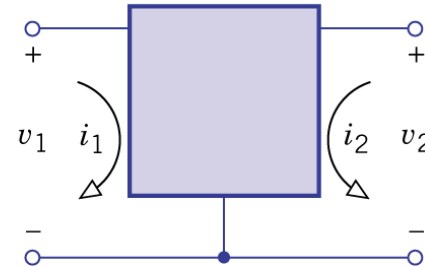


(b) Two-port with common ground

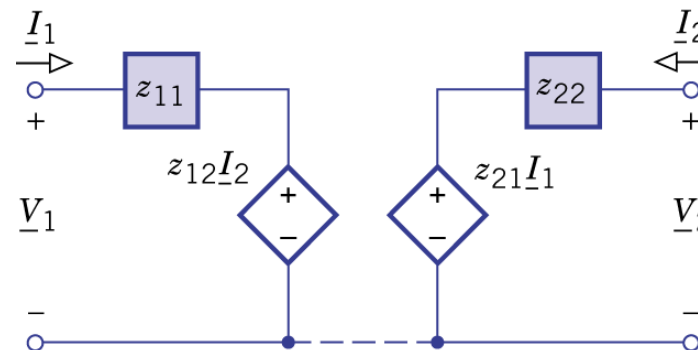2. Equivalent circuit expressed in z-parameters

$$\begin{cases} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \\ \underline{V}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2 \end{cases}$$


$$\begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$




3. Use definition to determine the z-parameter of a two-port network.
 4. Ex. 14.1 find z-parameters of a “symmetrical” network

$$z_{11} = z_{22}$$

$$z_{12} = z_{21}$$

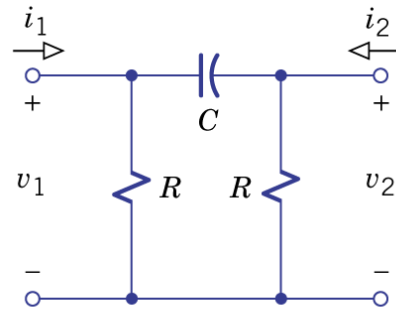

(a) Network for Example 14.1

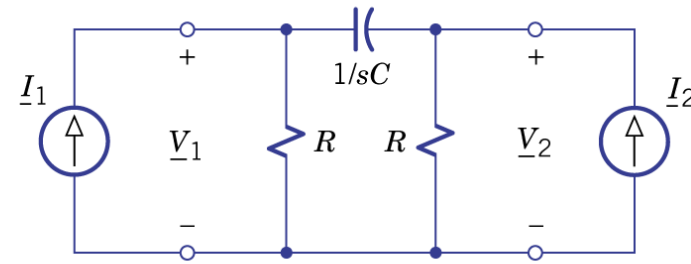

(b) s-domain diagram with current sources

sources: $\underline{I}_1, \underline{I}_2$


$$\begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

$$z_{11} = R // \left(\frac{1}{sC} + R \right) = \frac{1}{\frac{1}{R} + \frac{1}{R + \frac{1}{sC}}} = \frac{1}{\frac{1}{R} + \frac{sC}{1 + sRC}} = \frac{R + sR^2C}{1 + 2sRC} = z_{22}$$


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, \quad \left. V_1 \right|_{I_1=0} = \frac{R}{R + \frac{1}{sC}} \left. V_2 \right|_{I_1=0} = \frac{sRC}{1 + sRC} I_2 z_{22}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \rightarrow z_{12} = \frac{sRC}{1 + sRC} z_{22} = \frac{sRC}{1 + sRC} \frac{R + sR^2C}{1 + 2sRC} = \frac{sR^2C}{1 + 2sRC} = z_{21}$$

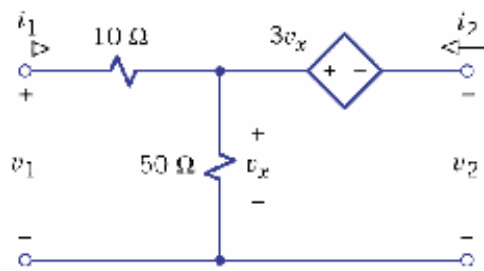
5. Ex. 14.2 find z-parameters of an “active” network



(a) Network for Example 14.2

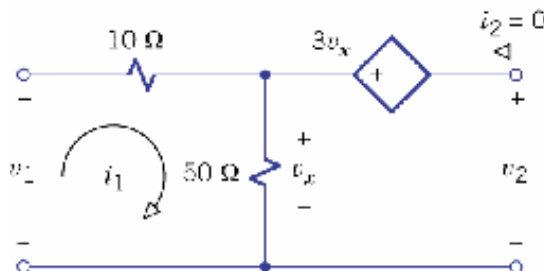

(b) Open-output diagram

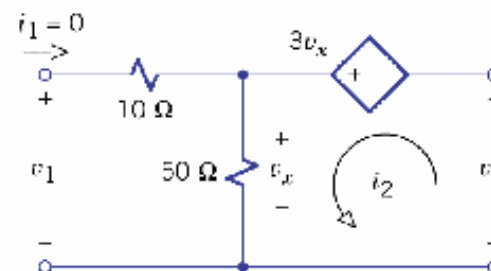

(c) Open-input diagram

sources: i_1, i_2

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$z_{11} = \left. \frac{v_1}{i_1} \right|_{i_2=0}, \quad z_{12} = \left. \frac{v_1}{i_2} \right|_{i_1=0}$$

$$z_{21} = \left. \frac{v_2}{i_1} \right|_{i_2=0}, \quad z_{22} = \left. \frac{v_2}{i_2} \right|_{i_1=0}$$

(1) port - 2 o.c., $i_2 = 0$

$$v_1 = i_1(10 + 50)$$

$$\rightarrow z_{11} = \frac{v_1}{i_1} = 60$$

$$v_x = 50i_1, v_2 = -3v_x + v_x \\ = -2v_x = -100i_1$$

$$\rightarrow z_{21} = \frac{v_2}{i_1} = -100$$

(2) port - 1 o.c., $i_1 = 0$


$$v_2 = -2v_x, v_x = 50i_2$$

$$\rightarrow z_{22} = \frac{v_2}{i_2} = -100 \neq z_{11}$$


$$v_1 = v_x = 50i_2$$

$$\rightarrow z_{12} = \frac{v_1}{i_2} = 50 \neq z_{21}$$

6. Reciprocal circuit

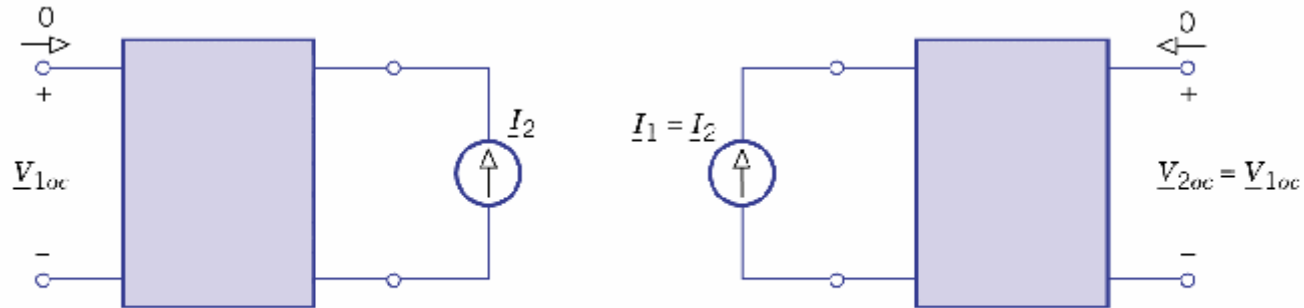

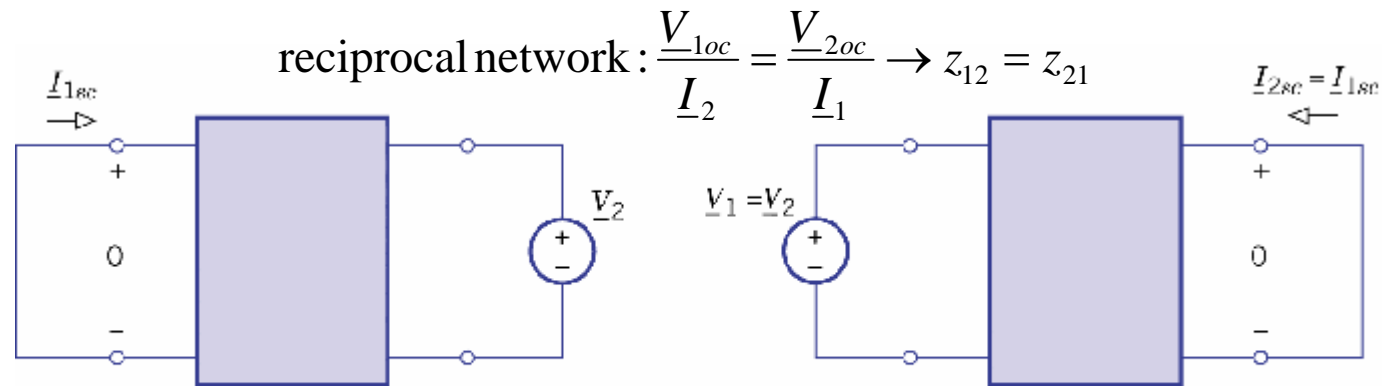(a) Interchanging open circuit and current source



(b) Interchanging short circuit and voltage source

reciprocal network: $\frac{I_{1sc}}{V_2} = \frac{I_{2sc}}{V_1} \rightarrow y_{12} = y_{21}$

7. Any **linear** network containing no controlled sources is a reciprocal network.

∴ node equation and mesh equation have symmetrical forms

8. Ex. 14.3 T-network

$$\text{sources: } \underline{I}_1, \underline{I}_2 \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$(1) I_2 = 0, z_{11} = \frac{V_1}{I_1} = z_{11} - z_{12} + z_{12}, z_{21} = \frac{V_2}{I_1} = z_{12}$$

$$(2) I_1 = 0, z_{22} = \frac{V_2}{I_2} = z_{11} - z_{12} + z_{12}, z_{12} = \frac{V_1}{I_2}$$

$$Z_a = z_{11} - z_{12}, Z_c = z_{12}$$

$$Z_b = z_{22} - z_{12}$$

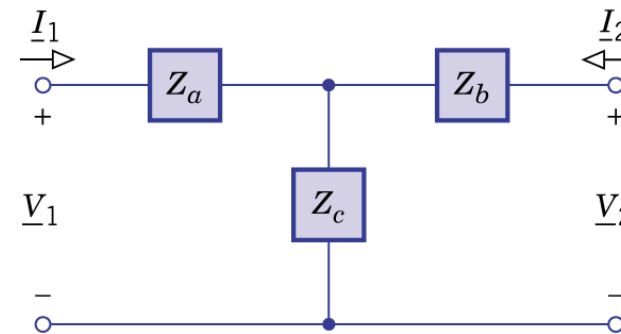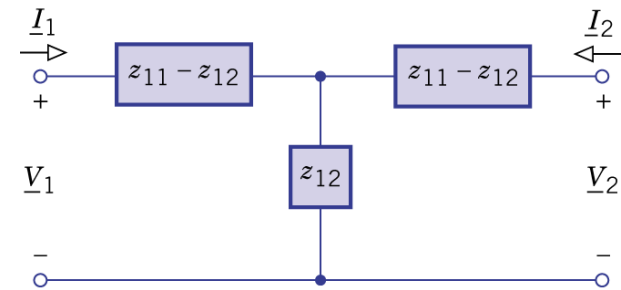


14.2 Admittance, hybrid, and transmission parameters

Basics

1. Not all two-ports possess **meaningful or measurable** z-parameters.

→ other parameters

2. Admittance parameter

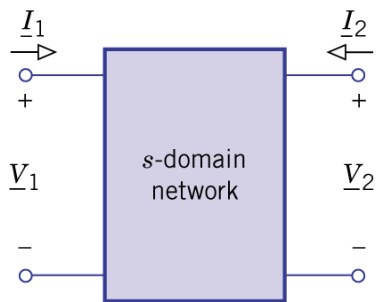

$$[y] \equiv \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} : \text{s.c. admittance parameter matrix}$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} : \text{input admittance at port 1 with port 2 s.c.}$$

sources: $\underline{V}_1, \underline{V}_2$, responses: $\underline{I}_1, \underline{I}_2$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} : \text{input admittance at port 2 with port 1 s.c.}$$


$$\begin{cases} \underline{I}_1 = y_{11}\underline{V}_1 + y_{12}\underline{V}_2 \\ \underline{I}_2 = y_{21}\underline{V}_1 + y_{22}\underline{V}_2 \end{cases}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} : \text{reverse transfer admittance with port 1 s.c.}$$

$$\rightarrow \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = [y] \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} : \text{forward transfer admittance with port 2 s.c.}$$

3. Hybrid parameter

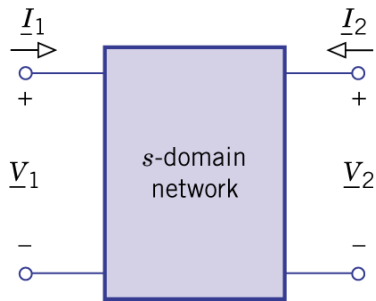

$$[h] \equiv \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} : \text{hybrid parameter matrix}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{1}{y_{11}} : \text{input admittance at port 1 with port 2 s.c.}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{z_{22}} : \text{input impedance at port 2 with port 1 o.c.}$$

sources: I_1, V_2 , responses: V_1, I_2


$$\begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 \\ I_2 = h_{21} I_1 + h_{22} V_2 \end{cases}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} : \text{reverse voltage ratio with port 1 o.c.}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} : \text{forward current ratio with port 2 s.c.}$$

$$\rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

4. Transmission parameter

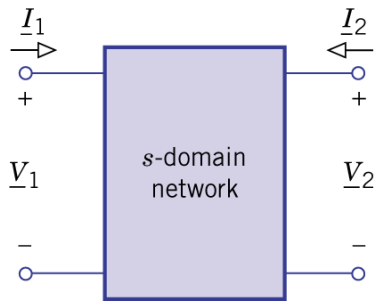

$$[T] \equiv \begin{bmatrix} A & B \\ C & D \end{bmatrix} : \text{transmission parameter matrix}$$

$$A = \left. \frac{\underline{V}_1}{\underline{V}_2} \right|_{\underline{I}_2=0} : \text{reverse voltage ratio with port 2 o.c.}$$

sources: $\underline{V}_2, \underline{I}_2$, responses: $\underline{V}_1, \underline{I}_1$

$$B = \left. \frac{\underline{V}_1}{-\underline{I}_2} \right|_{\underline{V}_2=0} : \text{reverse transfer impedance with port 2 s.c.}$$

$$\begin{cases} \underline{V}_1 = A\underline{V}_2 - B\underline{I}_2 \\ \underline{I}_1 = C\underline{V}_2 - D\underline{I}_2 \end{cases}$$


$$C = \left. \frac{\underline{I}_1}{\underline{V}_2} \right|_{\underline{I}_2=0} : \text{reverse transfer admittance with port 2 o.c.}$$

$$\begin{aligned} \rightarrow \begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix} \\ &= [T] \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix} \end{aligned}$$


$$D = \left. \frac{\underline{I}_1}{-\underline{I}_2} \right|_{\underline{V}_2=0} : \text{forward current ratio with port 2 s.c.}$$

Discussion

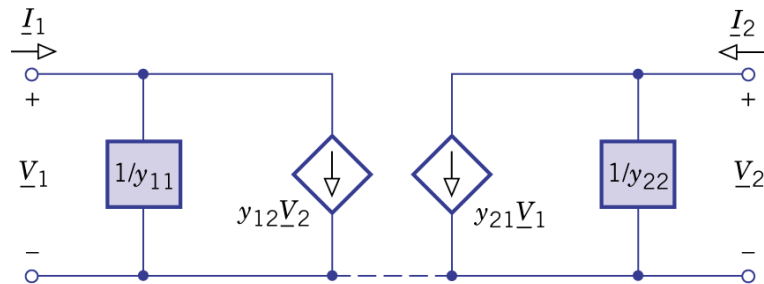1. Equivalent circuit expressed in y-parameters



(a) y-parameter model

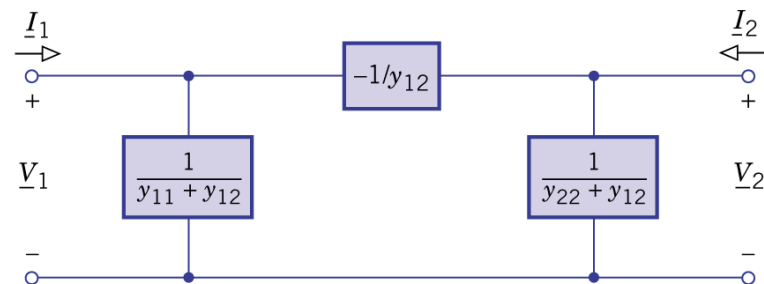

(b) Tee model for reciprocal two-port

sources: $\underline{V}_1, \underline{V}_2$

$$\begin{cases} \underline{I}_1 = y_{11}\underline{V}_1 + y_{12}\underline{V}_2 \\ \underline{I}_2 = y_{21}\underline{V}_1 + y_{22}\underline{V}_2 \end{cases}$$

$$\begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix}$$


$$(1) \underline{V}_2 = 0, \quad y_{11} = \frac{\underline{I}_1}{\underline{V}_1} = y_{11} + y_{12} - y_{12}$$

$$y_{21} = \frac{\underline{I}_2}{\underline{V}_1} = -\frac{1}{-1/y_{12}} = y_{12}$$

$$(2) \underline{V}_1 = 0, \quad y_{22} = \frac{\underline{I}_2}{\underline{V}_2} = y_{22} + y_{12} - y_{12}$$

$$y_{12} = \frac{\underline{I}_1}{\underline{V}_2} = -\frac{1}{-1/y_{12}} = y_{12}$$

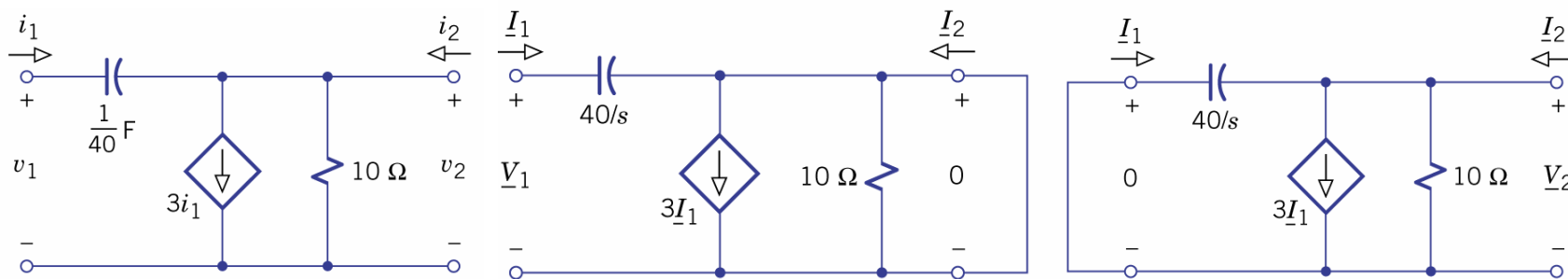2. Ex. 14.5 find y-parameters of an “active” network



(a) Network for Example 14.5

(b) Shorted-output diagram

(c) Shorted-input diagram

sources: $\underline{V}_1, \underline{V}_2$

$$\begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix}$$

(1) port - 2 s.c., $\underline{V}_2 = 0$

$$\underline{I}_1 = \underline{V}_1 \frac{s}{40} \rightarrow y_{11} = \frac{\underline{I}_1}{\underline{V}_1} = \frac{s}{40}$$

$$\underline{I}_2 = 3\underline{I}_1 - \underline{I}_1 = 2\underline{I}_1 = 2 \frac{s}{40} \underline{V}_1$$

$$\rightarrow y_{21} = \frac{\underline{I}_2}{\underline{V}_1} = \frac{s}{20}$$

(2) port - 1 s.c., $\underline{V}_1 = 0$


$$\underline{I}_1 = -\underline{V}_2 \frac{s}{40} \rightarrow y_{12} = \frac{\underline{I}_1}{\underline{V}_2} = -\frac{s}{40} \neq y_{21}$$

$$\underline{I}_2 = 3\underline{I}_1 - \underline{I}_1 + \frac{\underline{V}_2}{10} = 2\underline{I}_1 + \frac{\underline{V}_2}{10}$$

$$= -\frac{s\underline{V}_2}{20} + \frac{\underline{V}_2}{10} = \frac{2-s}{20} \underline{V}_2$$

$$\rightarrow y_{22} = \frac{\underline{I}_2}{\underline{V}_2} = \frac{2-s}{20}$$

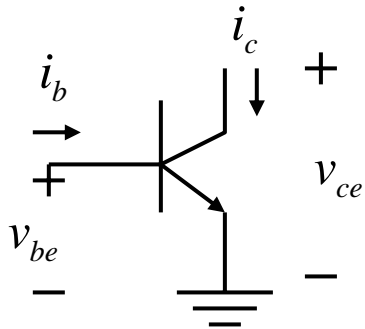3. H-parameters are applied to transistor because they are measured physical quantities.




sources: i_1, v_2 , responses: v_1, i_2


$$\begin{cases} v_1 = h_{11}i_1 + h_{12}v_2 \\ i_2 = h_{21}i_1 + h_{22}v_2 \end{cases} \rightarrow \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

$$CE \rightarrow \begin{bmatrix} v_{be} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$

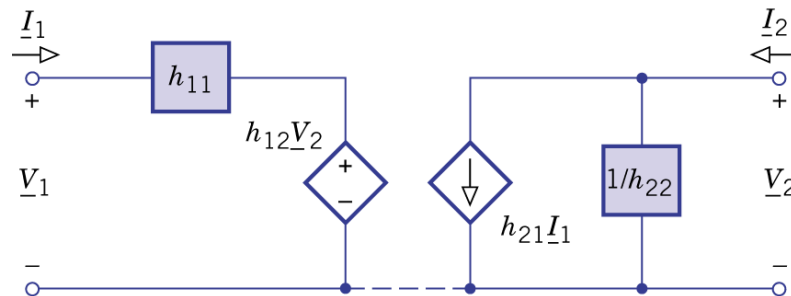
4. Equivalent circuit expressed in h-parameters



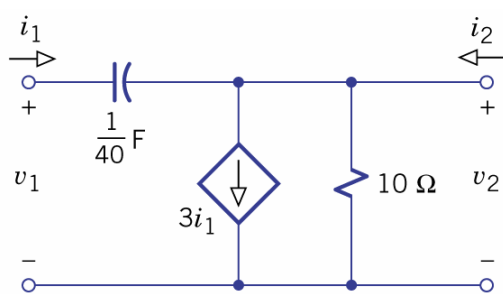
5. Ex. 14.6 find h-parameters of an “active” network



(a) Network for Example 14.5

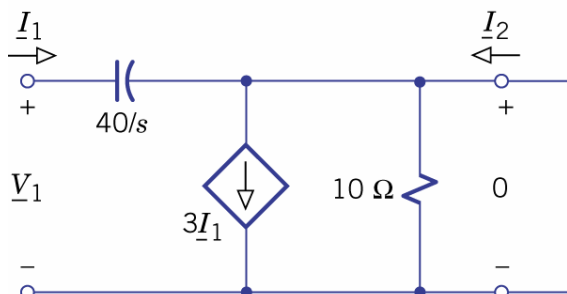

(b) Shorted-output diagram

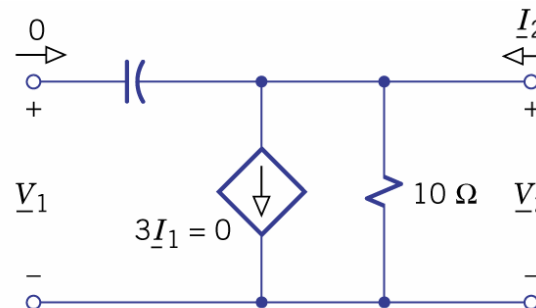

(b) Open input

sources : $\underline{I}_1, \underline{V}_2$

responses : $\underline{V}_1, \underline{I}_2$

$$\begin{cases} \underline{V}_1 = h_{11}\underline{I}_1 + h_{12}\underline{V}_2 \\ \underline{I}_2 = h_{21}\underline{I}_1 + h_{22}\underline{V}_2 \end{cases}$$

$$\rightarrow \begin{bmatrix} \underline{V}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{V}_2 \end{bmatrix}$$

(1) port - 2 s.c., $\underline{V}_2 = 0$

$$\underline{I}_1 = \underline{V}_1 \frac{s}{40}$$

$$\rightarrow h_{11} = \frac{\underline{V}_1}{\underline{I}_1} = \frac{40}{s}$$

$$\underline{I}_2 = 3\underline{I}_1 - \underline{I}_1 = 2\underline{I}_1$$

$$\rightarrow h_{21} = \frac{\underline{I}_2}{\underline{I}_1} = 2$$


(2) port - 1 o.c., $\underline{I}_1 = 0$

$$\underline{V}_1 = \underline{V}_2 \rightarrow h_{12} = \frac{\underline{V}_1}{\underline{V}_2} = 1$$

$$\underline{V}_2 = 10\underline{I}_2$$

$$\rightarrow h_{22} = \frac{\underline{I}_2}{\underline{V}_2} = 0.1$$

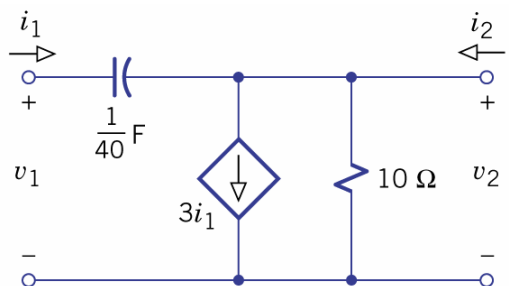6. Ex. 14.7 find ABCD-parameters of an “active” network




(a) Network for Example 14.5

sources: $\underline{V}_2, \underline{I}_2$

responses: $\underline{V}_1, \underline{I}_1$

$$\begin{cases} \underline{V}_1 = A\underline{V}_2 - B\underline{I}_2 \\ \underline{I}_1 = C\underline{V}_2 - D\underline{I}_2 \end{cases}$$
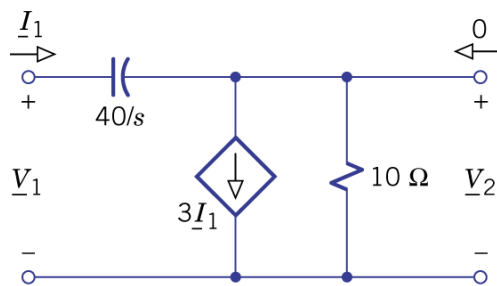
$$\rightarrow \begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix}$$



(a) Open output


(1) port - 2 o.c., $\underline{I}_2 = 0$

$$\underline{I}_1 = 3\underline{I}_1 + \frac{\underline{V}_2}{10}, \underline{I}_1 = -\frac{\underline{V}_2}{20}$$

$$\rightarrow C = \frac{\underline{I}_1}{\underline{V}_2} = -\frac{1}{20}$$

$$\underline{V}_1 = \underline{V}_2 + \frac{40}{s} \underline{I}_1 = \left(1 - \frac{2}{s}\right) \underline{V}_2$$
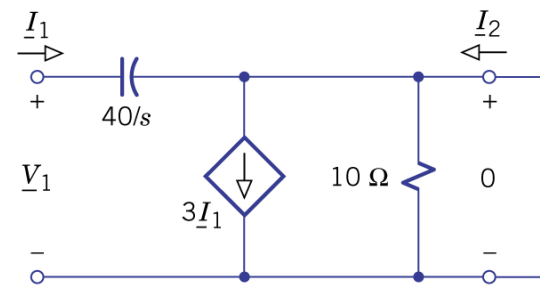
$$\rightarrow A = \frac{\underline{V}_1}{\underline{V}_2} = 1 - \frac{2}{s}$$



(b) Shorted output

(2) port - 2 s.c., $\underline{V}_2 = 0$

$$\underline{I}_1 = 3\underline{I}_1 - \underline{I}_2, 2\underline{I}_1 = \underline{I}_2$$

$$\rightarrow D = \frac{\underline{I}_1}{-\underline{I}_2} = -\frac{1}{2}$$

$$\underline{V}_1 = \frac{40}{s} \underline{I}_1 = \frac{20}{s} \underline{I}_2$$

$$\rightarrow B = \frac{\underline{V}_1}{-\underline{I}_2} = -\frac{20}{s}$$

7. All the 2-port parameters are related as given in Table 14.2.

8. Conversion between z-parameters and y-parameters

$$z\text{-parameter} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow [y] = [z]^{-1} = \begin{bmatrix} \frac{z_{22}}{\Delta_z} & -\frac{z_{12}}{\Delta_z} \\ -\frac{z_{21}}{\Delta_z} & \frac{z_{11}}{\Delta_z} \end{bmatrix}, \Delta_z = |[z]| = z_{11}z_{22} - z_{12}z_{21}$$

$$[z] = [y]^{-1} = \begin{bmatrix} \frac{y_{22}}{\Delta_y} & -\frac{y_{12}}{\Delta_y} \\ -\frac{y_{21}}{\Delta_y} & \frac{y_{11}}{\Delta_y} \end{bmatrix}, \Delta_y = |[y]| = y_{11}y_{22} - y_{12}y_{21}$$

9. Derivation of h-parameters from z-parameters

$$z\text{-parameter} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}, h\text{-parameter} \begin{bmatrix} \underline{V}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{V}_2 \end{bmatrix}$$

$$\begin{cases} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \dots (1) \\ \underline{V}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2 \dots (2) \end{cases} \quad (2) \rightarrow \underline{I}_2 = -\frac{z_{21}}{z_{22}}\underline{I}_1 + \frac{1}{z_{22}}\underline{V}_2 \dots (3)$$

$$(1) \xrightarrow{(3)} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\left(-\frac{z_{21}}{z_{22}}\underline{I}_1 + \frac{1}{z_{22}}\underline{V}_2\right) = \frac{\Delta_z}{z_{22}}\underline{I}_1 + \frac{z_{12}}{z_{22}}\underline{V}_2, \Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

$$[h] = \begin{bmatrix} \frac{\Delta_z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ -\frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$$

10. Derivation of z-parameters from T-parameters

$$T\text{-parameter} \begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix}, z\text{-parameter} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

$$\begin{cases} \underline{V}_1 = A\underline{V}_2 - B\underline{I}_2 \dots (1) \\ \underline{I}_1 = C\underline{V}_2 - D\underline{I}_2 \dots (2) \end{cases} \quad (2) \rightarrow \underline{V}_2 = \frac{1}{C}\underline{I}_1 + \frac{D}{C}\underline{I}_2 \dots (3)$$

$$(1) \xrightarrow{(3)} \underline{V}_1 = A\left(\frac{1}{C}\underline{I}_1 + \frac{D}{C}\underline{I}_2\right) - B\underline{I}_2 = \frac{A}{C}\underline{I}_1 + \frac{\Delta_T}{C}\underline{I}_2, \Delta_T = AD - BC$$

$$[z] = \begin{bmatrix} \frac{A}{C} & \frac{\Delta_T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$

11. For a reciprocal 2-port network,

$$z_{12} = z_{21}, y_{12} = y_{21}, h_{12} = -h_{21}, \Delta_T = AD - BC = 1$$

14.3 Circuit analysis with two-ports

Basics

1. Terminated two-ports using z-parameters

$$\begin{cases} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \dots (1) \\ \underline{V}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2 \dots (2) \end{cases} \begin{cases} \underline{V}_s = Z_s \underline{I}_1 + \underline{V}_1 \dots (3) \\ \underline{V}_2 = -Z_L \underline{I}_2 \dots (4) \end{cases}$$


$$(4) \rightarrow -Z_L \underline{I}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2, z_{21}\underline{I}_1 = -(Z_L + z_{22})\underline{I}_2$$

$$\Rightarrow \text{current transfer function } H_i \equiv \frac{\underline{I}_2}{\underline{I}_1} = \frac{-z_{21}}{Z_L + z_{22}}$$

$$(1) \rightarrow \underline{V}_1 = z_{11}\underline{I}_1 - \frac{z_{12}}{Z_L}\underline{V}_2, \underline{I}_1 = \frac{1}{z_{11}}\underline{V}_1 + \frac{z_{12}}{z_{11}Z_L}\underline{V}_2 \dots (5)$$

$$(2) \rightarrow \underline{V}_2 = z_{21}\left(\frac{1}{z_{11}}\underline{V}_1 + \frac{z_{12}}{z_{11}Z_L}\underline{V}_2\right) - \frac{z_{22}}{Z_L}\underline{V}_2$$
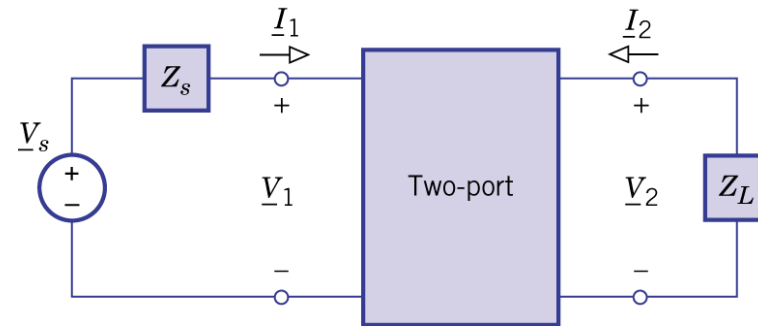
$$\Rightarrow \text{voltage transfer function } H_v \equiv \frac{\underline{V}_2}{\underline{V}_1} = \frac{\frac{z_{21}}{z_{11}}}{1 - \frac{z_{12}z_{21}}{z_{11}Z_L} + \frac{z_{22}}{Z_L}} = \frac{\frac{z_{21}}{z_{11}}Z_L}{z_{11}Z_L - z_{12}z_{21} + z_{11}z_{22}} = \frac{z_{21}Z_L}{\Delta_z + z_{11}Z_L}$$



$$\begin{cases} \underline{V}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \dots (1) \\ \underline{V}_2 = z_{21}\underline{I}_1 + z_{22}\underline{I}_2 \dots (2) \end{cases} \begin{cases} \underline{V}_s = Z_S \underline{I}_1 + \underline{V}_1 \dots (3) \\ \underline{V}_2 = -Z_L \underline{I}_2 \dots (4) \end{cases}$$

$$H_i \equiv \frac{\underline{I}_2}{\underline{I}_1} = \frac{-z_{21}}{Z_L + z_{22}} \dots (6)$$


$$(1) \xrightarrow{(6)} \underline{V}_1 = z_{11}\underline{I}_1 - z_{12} \frac{-z_{21}}{Z_L + z_{22}} \underline{I}_1$$

$$\Rightarrow \text{equivalent input impedance } Z_i \equiv \frac{\underline{V}_1}{\underline{I}_1} = \frac{z_{11}Z_L + z_{11}z_{22} - z_{12}z_{21}}{Z_L + z_{22}} = \frac{\Delta_z + z_{11}Z_L}{Z_L + z_{22}}$$


$$\underline{V}_s = 0, (3) \rightarrow \underline{V}_1 = -Z_S \underline{I}_1 \dots (7), (1) \xrightarrow{(7)} -Z_S \underline{I}_1 = z_{11}\underline{I}_1 + z_{12}\underline{I}_2 \rightarrow \underline{I}_1 = -\frac{z_{12}}{Z_S + z_{11}} \underline{I}_2 \dots (8)$$

$$(2) \xrightarrow{(8)} \underline{V}_2 = z_{21} \left(-\frac{z_{12}}{Z_S + z_{11}} \underline{I}_2 \right) + z_{22}\underline{I}_2$$

$$\Rightarrow \text{equivalent output impedance } Z_o \equiv \left. \frac{\underline{V}_2}{\underline{I}_2} \right|_{\underline{V}_s=0} = \frac{z_{22}Z_S + z_{11}z_{22} - z_{12}z_{21}}{Z_S + z_{11}} = \frac{\Delta_z + z_{22}Z_S}{Z_S + z_{11}}$$

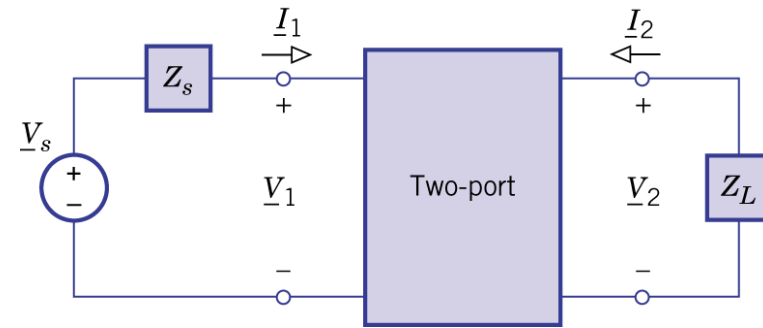


2. Cascade connection using T-parameters

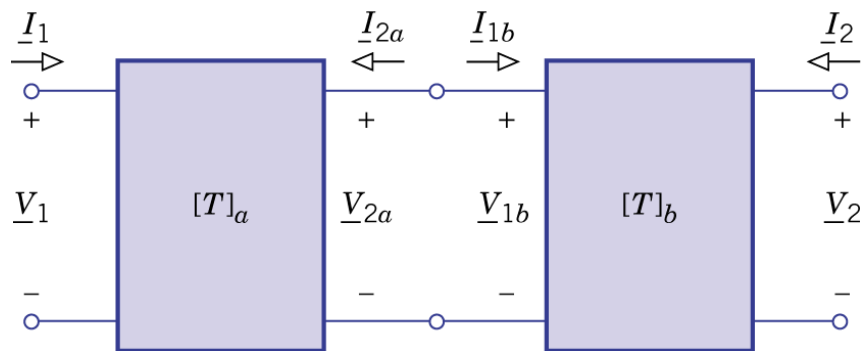


$$\begin{aligned} \begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} &= [T]_a \begin{bmatrix} \underline{V}_{2a} \\ -\underline{I}_{2a} \end{bmatrix} = [T]_a \begin{bmatrix} \underline{V}_{1b} \\ \underline{I}_{1b} \end{bmatrix} \\ &= [T]_a [T]_b \begin{bmatrix} \underline{V}_2 \\ -\underline{I}_2 \end{bmatrix} \\ \Rightarrow [T]_{cas} &= [T]_a [T]_b \end{aligned}$$

3. Series connection using z-parameters

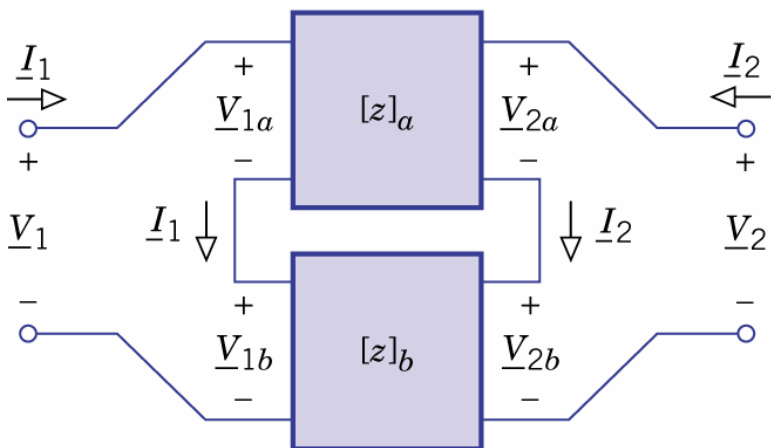

$$\begin{aligned} \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} &= \begin{bmatrix} \underline{V}_{1a} \\ \underline{V}_{2a} \end{bmatrix} + \begin{bmatrix} \underline{V}_{1b} \\ \underline{V}_{2b} \end{bmatrix} \\ &= [z]_a \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} + [z]_b \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} \\ &= ([z]_a + [z]_b) \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} \\ \Rightarrow [z]_{ser} &= [z]_a + [z]_b \end{aligned}$$

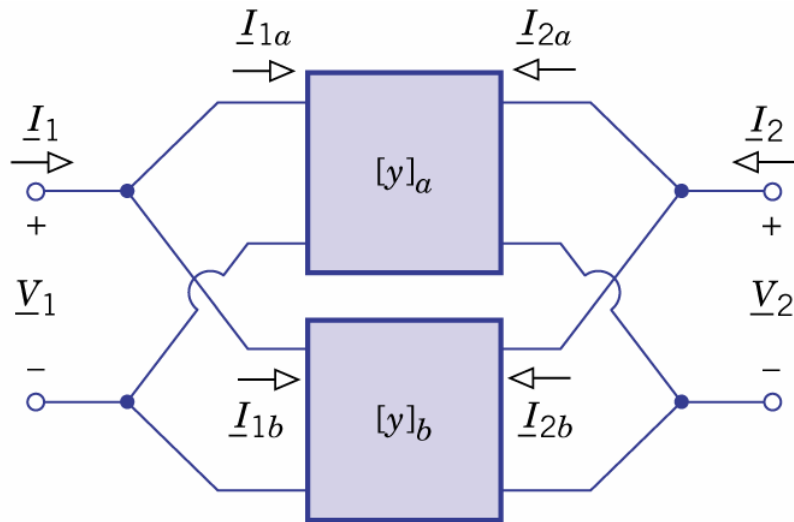
4. Parallel connection using y-parameters



$$\begin{aligned}
 \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} &= \begin{bmatrix} \underline{I}_{1a} \\ \underline{I}_{2a} \end{bmatrix} + \begin{bmatrix} \underline{I}_{1b} \\ \underline{I}_{2b} \end{bmatrix} \\
 &= [\underline{y}]_a \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} + [\underline{y}]_b \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} \\
 &= ([\underline{y}]_a + [\underline{y}]_b) \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} \\
 \Rightarrow [\underline{y}]_{par} &= [\underline{y}]_a + [\underline{y}]_b
 \end{aligned}$$

Discussion

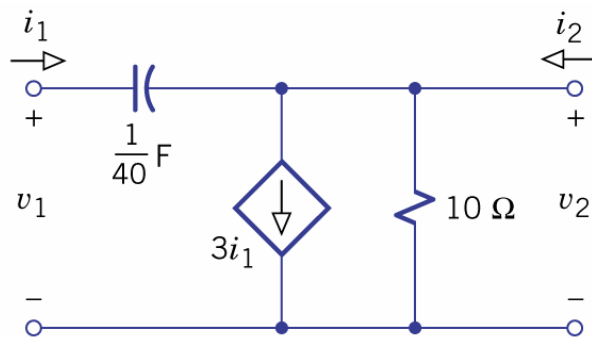1. Relations of terminated two-ports in terms of z- y- h- and T- parameters are given in Table 14.3. They are useful in network analysis.
2. Ex. 14.9 given load be a 2.5H inductor, find I_2/V_1 from T-parameters





(a) Network for Example 14.5

From ex.14.7
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 - \frac{2}{s} & -\frac{20}{s} \\ -\frac{1}{20} & \frac{1}{2} \end{bmatrix}$$

$$\begin{aligned} H(s) &= \frac{I_2}{V_1} = \frac{I_2}{Z_i I_1} = \frac{H_i}{Z_i} \stackrel{\text{Table 14.2}}{=} \frac{-1}{CZ_L + D} \frac{CZ_L + D}{AZ_L + B} \\ &= \frac{-1}{AZ_L + B} = \frac{-1}{\left(1 - \frac{2}{s}\right)2.5s - \frac{20}{s}} = \frac{-0.4s}{s^2 - 2s - 8} \\ &= \frac{-0.4s}{(s - 4)(s + 2)} \end{aligned}$$

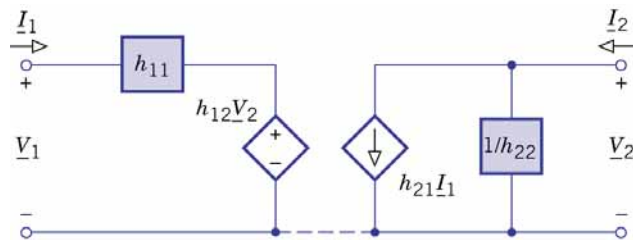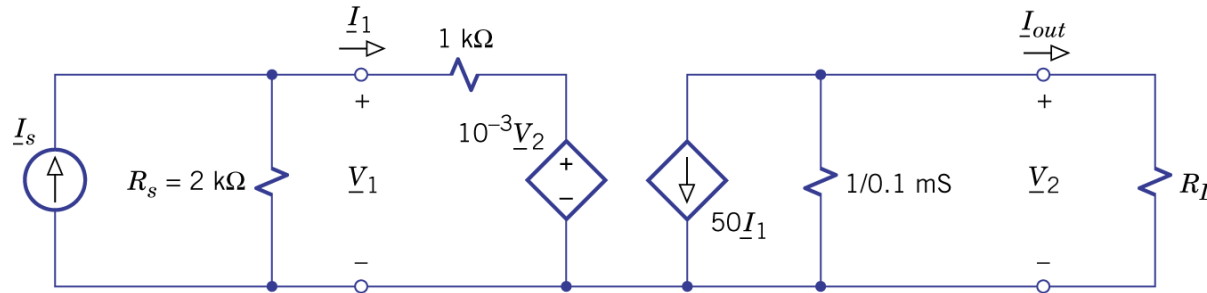3. Ex. 14.10 find R_L to give $A_i = \underline{I}_{out} / \underline{I}_s = -25$ from transistor h-parameters



$$[h] = \begin{bmatrix} 1000 & 10^{-3} \\ 50 & 0.1 \times 10^{-3} \end{bmatrix}$$

$$\Delta_h = 0.05$$

$$Z_i(s) = \frac{V_1}{I_1} = \frac{\Delta_h + h_{11} Y_L}{h_{22} + Y_L}$$


$$H_i(s) = \frac{I_2}{I_1} = \frac{h_{21} Y_L}{h_{22} + Y_L}$$

$$A_i = \frac{I_{out}}{I_s} = \frac{-I_2}{I_1} \frac{I_1}{I_s} = -H_i \frac{R_s}{R_s + Z_i}$$

$$Z_i(s) = \frac{0.05 R_L + 1}{0.1 R_L + 1}, H_i(s) = \frac{50}{0.1 R_L + 1}$$

$$A_i = \frac{-100}{3 + 0.25 R_L} = -25 \rightarrow R_L = 4 k\Omega$$

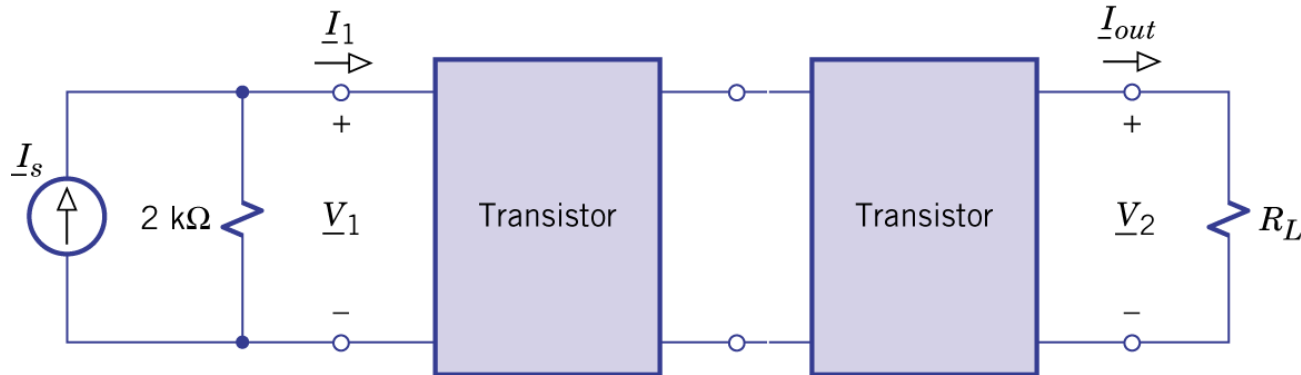4. Ex. 14.11 find A_i of two amplifiers of ex.14.10 in cascade



$$[h] = \begin{bmatrix} 1000 & 10^{-3} \\ 50 & 0.1 \times 10^{-3} \end{bmatrix}, [T]_a = [T]_b = \begin{bmatrix} \frac{-\Delta_h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{bmatrix} = \begin{bmatrix} -10^{-3} & -20 \\ -2 \times 10^{-6} & -0.02 \end{bmatrix}$$

$$\rightarrow [T]_{cas} = [T]_a [T]_b = \begin{bmatrix} 41 \times 10^{-6} & 0.42 \\ 0.042 \times 10^{-6} & 440 \times 10^{-6} \end{bmatrix}$$


$$Z_i(s) = \frac{AR_L + B}{CR_L + D} = 961, H_i(s) = \frac{-1}{CR_L + D} = -1645$$

$$A_i = \frac{I_{out}}{I_s} = \frac{-I_2}{I_1} \frac{I_1}{I_s} = -H_i \frac{R_s}{R_s + Z_i} = 1100$$


14-26

電路學講義第14章

5. Bridged-T connection

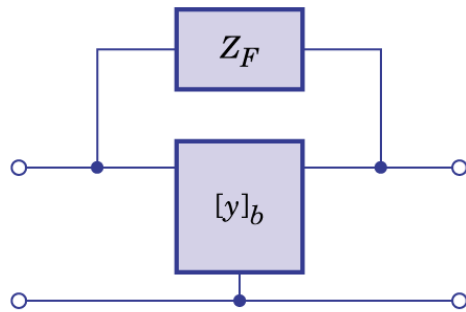

(a) Network with bridging impedance

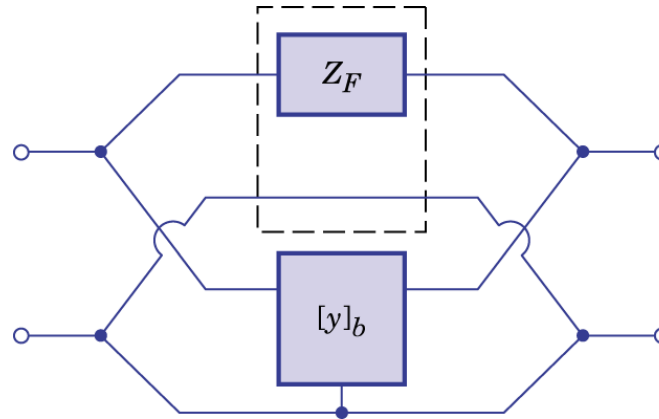



(b) Model as parallel two-ports

$$[y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}, y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}, y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}, y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}, y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{11} = y_{22} = Y_F, y_{12} = y_{21} = -Y_F$$

$$\Rightarrow [y] = \begin{bmatrix} Y_F + y_{11b} & -Y_F + y_{12b} \\ -Y_F + y_{21b} & Y_F + y_{22b} \end{bmatrix}$$

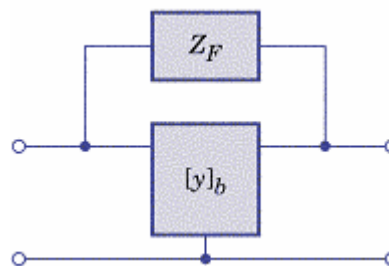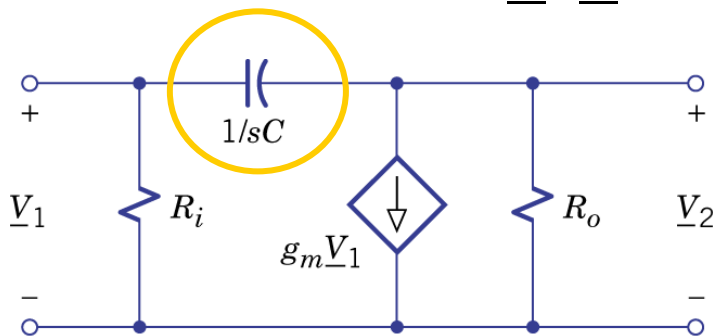6. Ex.14.12 find $H_v = \underline{V}_2 / \underline{V}_1$ of a high frequency transistor



$$Z_F = \frac{1}{sC}, [y]_a = \begin{bmatrix} sC & -sC \\ -sC & sC \end{bmatrix}, [y]_b = \begin{bmatrix} \frac{1}{R_i} & 0 \\ g_m & \frac{1}{R_o} \end{bmatrix} \Rightarrow [y] = \begin{bmatrix} sC + \frac{1}{R_i} & -sC \\ -sCg_m & sC + \frac{1}{R_o} \end{bmatrix}$$

$$H_v = \frac{-y_{21}}{y_{22} + Y_L} = \frac{sC - g_m}{sC + 1/R_o + 1/R_L} = \frac{s - g_m/C}{s + G/C}$$

$$G = 1/R_o + 1/R_L = 1/R_o // R_L$$

