

Chapter 8 Transformers and mutual inductance

-optional-

8.1 Ideal transformers

ideal transformer model, referred source network, referred load network, maximum power transfer

8.2 Magnetic coupling and mutual inductance

self-inductance, mutual inductance, coupling coefficient


8.3 Circuits with mutual inductance

impedance analysis, T- and π -equivalent networks

8.1 Ideal transformers

Basics

1. Ideal transformer model

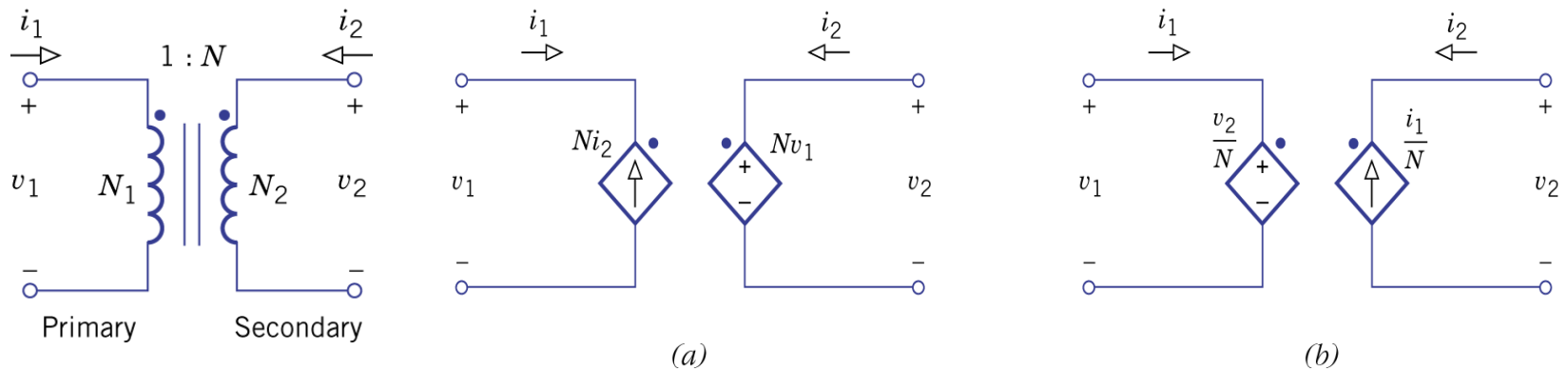


$$\frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2} = \frac{1}{N}, \frac{i_1(t)}{i_2(t)} = -\frac{N_2}{N_1} = -N, N \equiv \frac{N_2}{N_1}$$


$$p(t) = v_1(t)i_1(t) + v_2(t)i_2(t) = v_1(t)i_1(t) + Nv_1(t)\frac{-i_1(t)}{N} = 0$$

“•” means higher potential terminal.

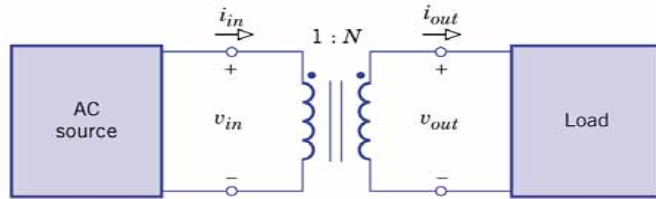
2. Referred load network and referred source network



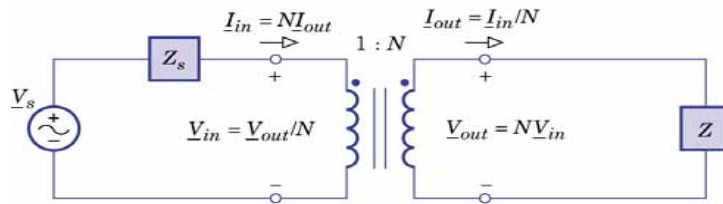
(a) Ideal transformer interfacing a source and a load



(b) Frequency-domain diagram

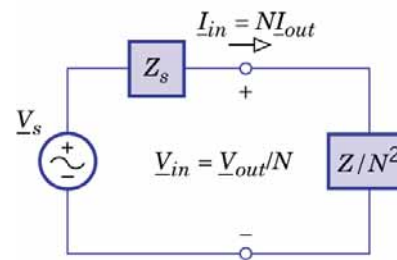

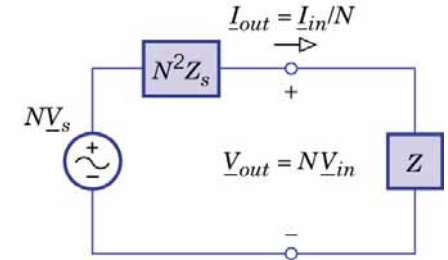(a) Referred load impedance in the primary



(b) Referred source network in the secondary

Maximum power transfer
by impedance matching


$$\frac{Z}{N^2} = Z_s^* = R_s - jX_s$$

referred to the primary $\rightarrow V_{in} = \frac{V_{out}}{N}, I_{in} = NI_{out}, Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{out}}{N} \frac{1}{NI_{out}} = \frac{Z_{out}}{N^2}$


referred to the secondary $\rightarrow V_{out} = NV_{in}, I_{out} = \frac{I_{in}}{N}, Z_{out} = \frac{V_{out}}{I_{out}} = NV_{in} \frac{N}{I_{in}} = N^2 Z_{in}$

Discussion

1. Transformer with taps

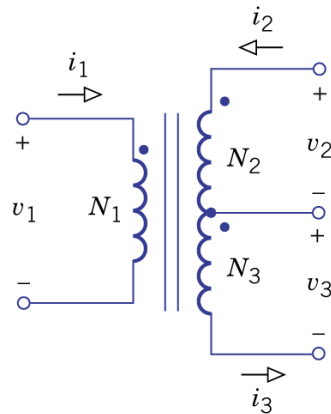

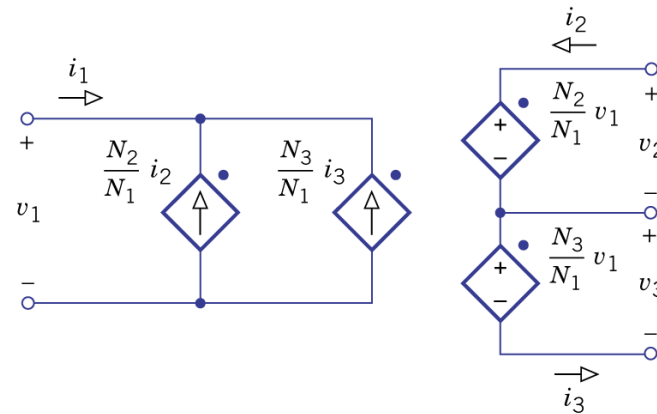(a) Ideal transformer with tapped secondary




(b) Controlled-source model

$$\frac{v_1(t)}{v_2(t)} = \frac{N_1}{N_2}, \frac{v_1(t)}{v_3(t)} = \frac{N_1}{N_3}$$


$$p(t) = v_1(t)i_1(t) + v_2(t)i_2(t) + v_3(t)i_3(t) = 0$$

$$\rightarrow i_1(t) = -\frac{v_2}{v_1}i_2 - \frac{v_3}{v_1}i_3 = -\frac{N_2}{N_1}i_2 - \frac{N_3}{N_1}i_3$$

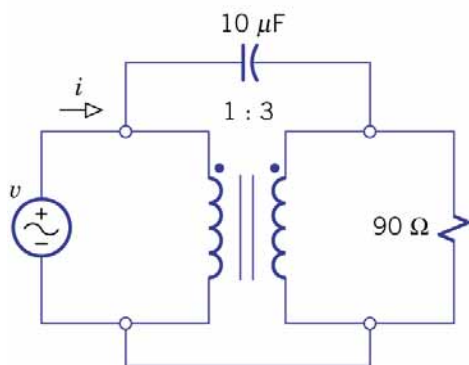2. Ex.8.1 find $\underline{I}$, P from source



(a) Circuit with an ideal transformer

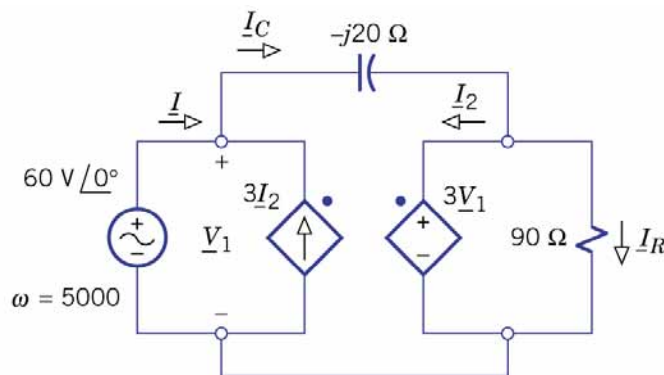

(b) Frequency-domain diagram

$$\underline{I} = \underline{I}_C - 3\underline{I}_2 = \underline{I}_C - 3(\underline{I}_C - \underline{I}_R) = -2 \times \frac{\underline{V}_1 - 3\underline{V}_1}{-j20} + 3 \times \frac{3\underline{V}_1}{90} = 6 + j12 = \sqrt{180} \angle 63.4^\circ$$

$$\underline{Z} = \frac{\underline{V}_1}{\underline{I}} = 2 - j4 \rightarrow P = \frac{1}{2} |\underline{I}|^2 \text{Re}[\underline{Z}] = 180$$

$$P_R = \frac{1}{2} \underline{I}_R^2 R = 180 = P : \text{lossless}$$

3. Ex.8.2 use transformer to improve η

$$(a): P = 15k, P = \frac{1}{2} |\underline{I}_{out}|^2 R$$

$$\rightarrow |\underline{I}_{out}| = 100, |\underline{V}_{out}| = 3 \times |\underline{I}_{out}| = 300$$

$$\rightarrow |\underline{I}| = 100, |\underline{V}_s| = 5 \times |\underline{I}| = 500, \eta = \frac{3}{2+3} = 60\%$$

(b): both ends referred to the middle


$$\begin{cases} \underline{V}_s = 500 \\ \underline{I}_{in} \end{cases} \rightarrow \frac{500 N}{\underline{I}_{in} / N}, \underline{V}_a = N \underline{V}_{in}$$

$$\begin{cases} 3\Omega \\ \underline{I}_{out} = 100 \end{cases} \rightarrow \frac{4^2 \times 3\Omega}{\underline{I}_{out} / 4 = 25}, \underline{V}_b = 4 \underline{V}_{out} = 1200$$


$$\eta = \frac{48}{48+2} = 96\% \quad \text{increases}$$

$$\underline{I} = \frac{500 N}{2+48} = 25 \rightarrow N = 2.5 \quad \text{decreases}$$

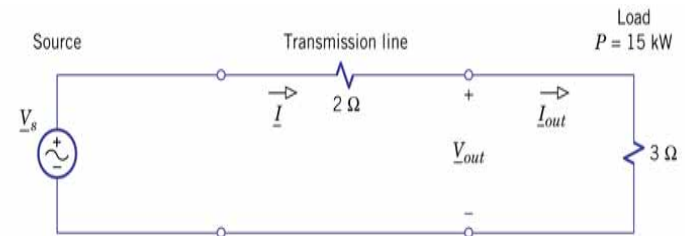
$$\underline{V}_a = 2 \underline{I} + \underline{V}_b = 1250 \quad \text{increases}$$



(a) Power transfer via transmission line

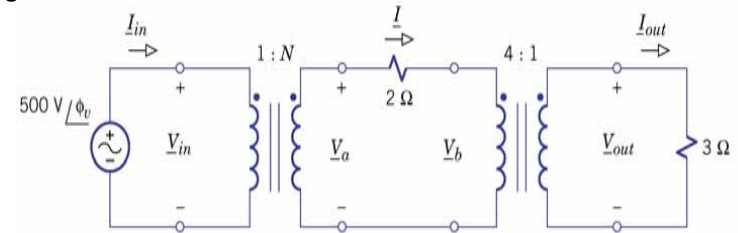

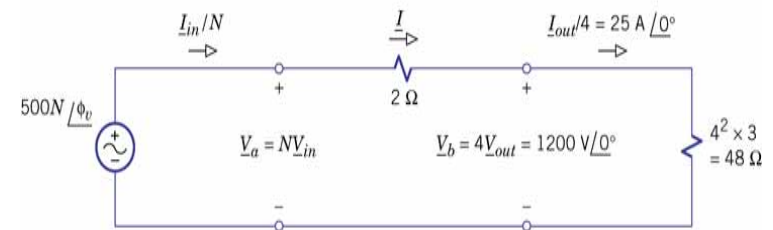(b) Circuit with transformers at each end



(c) Frequency-domain diagram with both ends referred into the middle


4. Ex. 8.3 oscillator application for ac signal coupling

$$N = \frac{1}{2} \rightarrow \text{referred source network}$$


$$KCL \rightarrow \left(\frac{1}{250} + j0.005 + \frac{1}{500} \right) \underline{V}_{out} = 0.024 \quad R_s = 1 \text{ k}\Omega$$

$$\rightarrow \underline{V}_{out} = 3 \angle -40^\circ$$
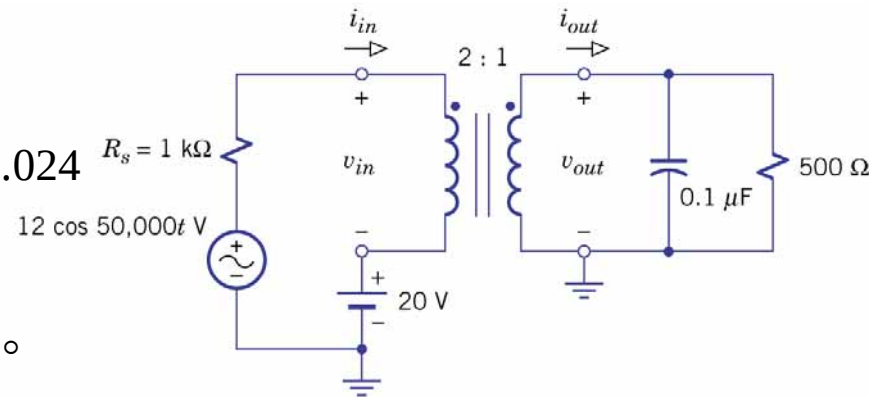
$$\underline{I}_{out} = \left(j0.005 + \frac{1}{500} \right) \underline{V}_{out} = 0.016 \angle 20^\circ$$



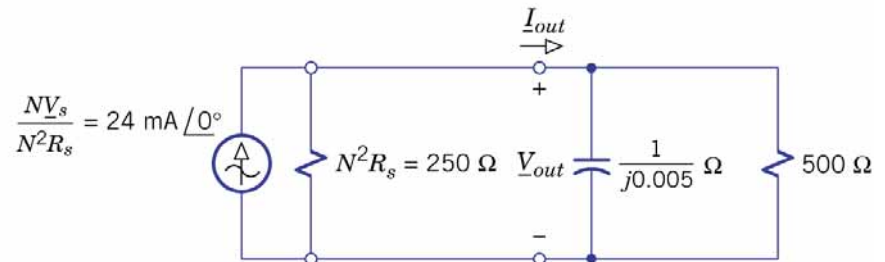(a) Transformer circuit with ac and dc sources



(b) Frequency-domain diagram with referred source network in the secondary

5. Ex. 8.4 use transformer for maximum power transfer, find N and X for P_{max}

$$|V_s| = |I_s Z_s| = 18$$

$$Z_s = 400 // -j200 = 80 - j160$$


$$\frac{Z}{N^2} = \frac{500 + jX}{N^2} = Z_s^* = 80 + j160$$

$$\rightarrow N = \sqrt{\frac{500}{80}} = 2.5$$


$$\frac{\omega L}{2.5^2} = 160, L = 0.01$$

$$P_{max} = \frac{1}{4} \frac{V_{rms}^2}{R} = \frac{1}{4} \frac{\left(\frac{18}{\sqrt{2}}\right)^2}{80} = 0.51$$

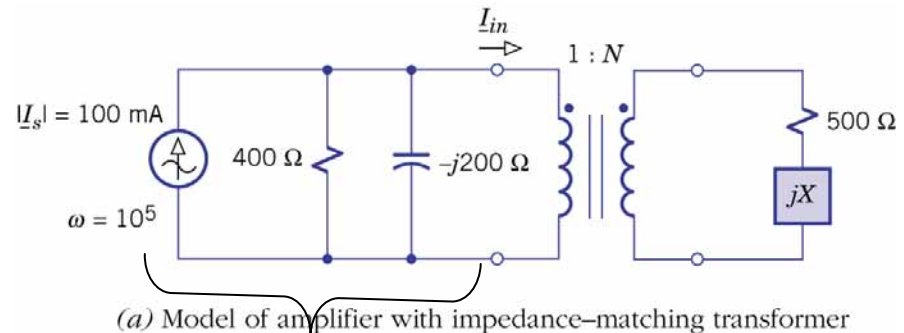Transformer is a practical component as a **lossless** impedance transformer.



output of an amplifier

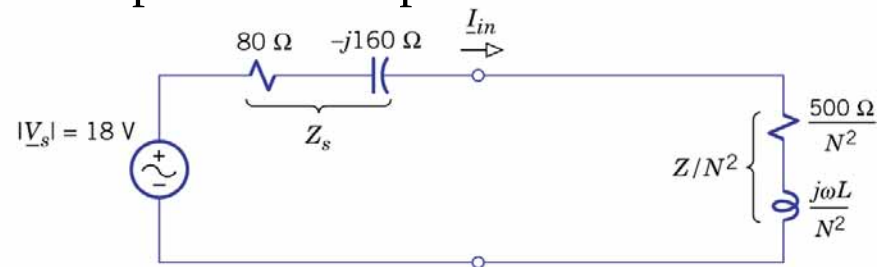


8.2 Magnetic coupling and mutual inductance

Basics

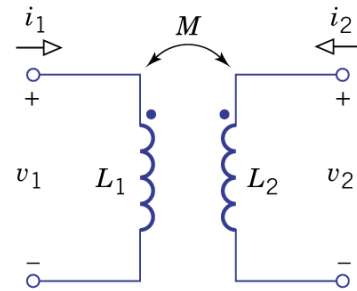
1.

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_1 & \pm M \\ \pm M & L_2 \end{bmatrix} \begin{bmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix}$$

$$\begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = j\omega \begin{bmatrix} L_1 & \pm M \\ \pm M & L_2 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$



(a) The same winding sense

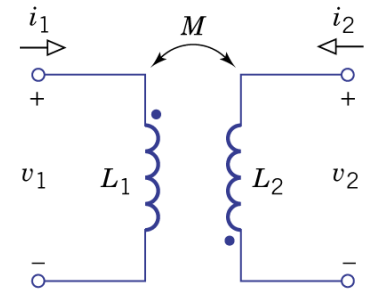

(b) Opposite winding sense

$$\frac{L_2}{L_1} = \left(\frac{N_2}{N_1} \right)^2, M = k\sqrt{L_1 L_2}, 0 \leq k \leq 1, k : \text{coupling coefficient}$$

$$p(t) = v_1 i_1 + v_2 i_2 = L_1 i_1 \frac{di_1}{dt} + M i_1 \frac{di_2}{dt} + M i_2 \frac{di_1}{dt} + L_2 i_2 \frac{di_2}{dt}$$


$$= L_1 i_1 \frac{di_1}{dt} + M \frac{di_1 i_2}{dt} + L_2 i_2 \frac{di_2}{dt}$$

$$w(t) = \int p(t) dt = \frac{1}{2} L_1 i_1^2 + M i_1 i_2 + \frac{1}{2} L_2 i_2^2$$

8.3 Circuits with mutual inductance

Basics

1. Frequency-domain model

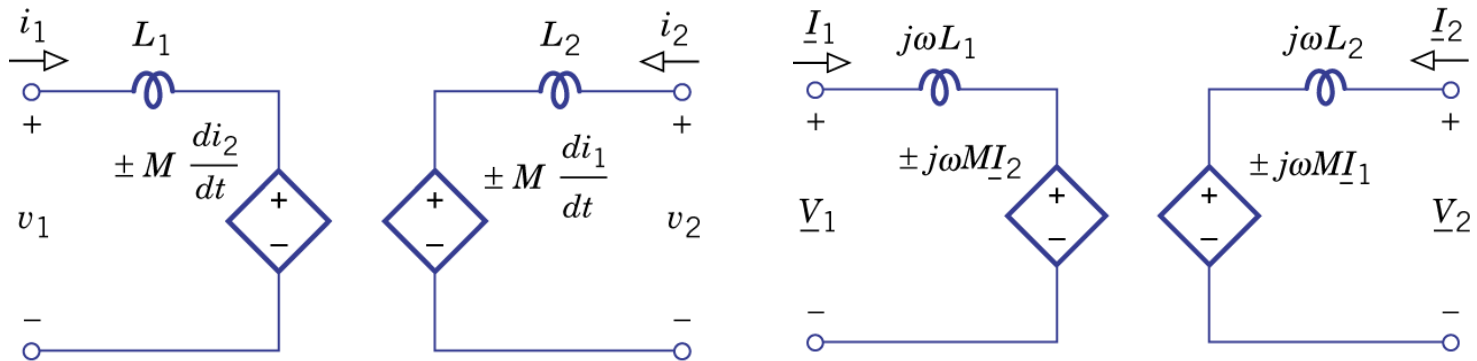

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_1 & \pm M \\ \pm M & L_2 \end{bmatrix} \begin{bmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix} \rightarrow \begin{bmatrix} \underline{V}_1 \\ \underline{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & \pm j\omega M \\ \pm j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix}$$

2. Impedance analysis

$$\underline{I}_2 = -\underline{I}_{out}$$

$$\text{loop 1: } j\omega L_1 \underline{I}_{in} - j\omega M \underline{I}_{out} = \underline{V}_{in}$$

$$\text{loop 2: } (j\omega L_2 + Z) \underline{I}_{out} = j\omega M \underline{I}_{in}$$

$$\rightarrow \frac{\underline{I}_{out}}{\underline{I}_{in}} = \frac{j\omega M}{j\omega L_2 + Z}$$


$$Z_{in} = \frac{\underline{V}_{in}}{\underline{I}_{in}} = j\omega L_1 - j\omega M \frac{\underline{I}_{out}}{\underline{I}_{in}}$$

$$= j\omega L_1 + \frac{(\omega M)^2}{j\omega L_2 + Z}$$


$$= \frac{-\omega^2 L_1 L_2 + j\omega L_1 Z + (\omega M)^2}{j\omega L_2 + Z}$$

$$\frac{\underline{V}_{out}}{\underline{V}_{in}} = \frac{Z \underline{I}_{out}}{Z_{in} \underline{I}_{in}}$$
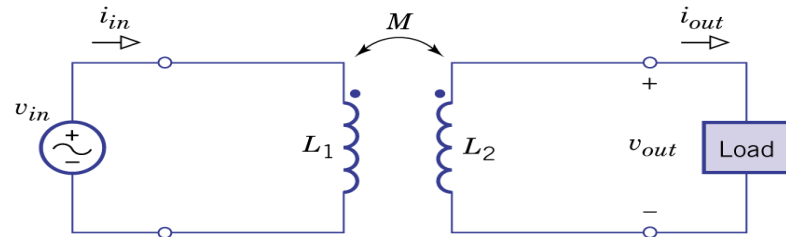
$$= \frac{j\omega M Z}{-\omega^2 L_1 L_2 + j\omega L_1 Z + (\omega M)^2}$$



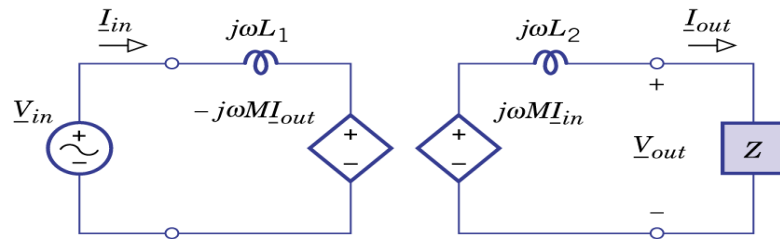(a) Transformer interfacing a source and a load



(b) Frequency-domain diagram with controlled sources


$$\text{if } k = 1, \frac{L_2}{L_1} = \left(\frac{N_2}{N_1} \right)^2 = N^2 \rightarrow M = \sqrt{L_1 L_2} = N L_1 = \frac{L_2}{N}$$

$$\rightarrow \frac{\underline{I}_{out}}{\underline{I}_{in}} = \frac{M}{L_2} \frac{1}{1 + Z / j\omega L_2} = \frac{1}{N} \frac{1}{1 + Z / j\omega L_2} \approx \frac{1}{N}, \text{ if } \omega L_2 \gg Z$$


$$Z_{in} = \frac{j\omega L_1 Z}{j\omega L_2 + Z} = \frac{L_1 Z / L_2}{1 + Z / j\omega L_2} = \frac{1}{N^2} \frac{Z}{1 + Z / j\omega L_2} \approx \frac{Z}{N^2}$$

$$\frac{\underline{V}_{out}}{\underline{V}_{in}} = \frac{j\omega M Z}{j\omega L_1 Z} = \frac{M}{L_1} = \frac{N_2}{N_1} = N, \text{ "ideal transformer"}$$


3. T- and π -equivalent networks

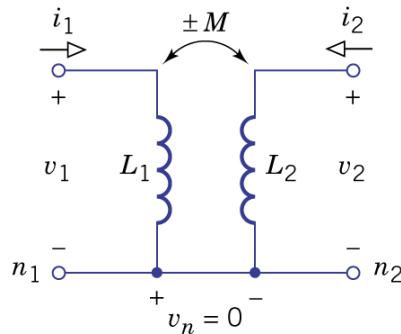

(a) Magnetically coupled coils

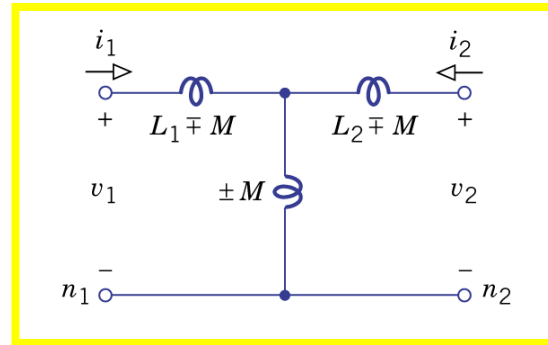

(b) Equivalent tee (T) network

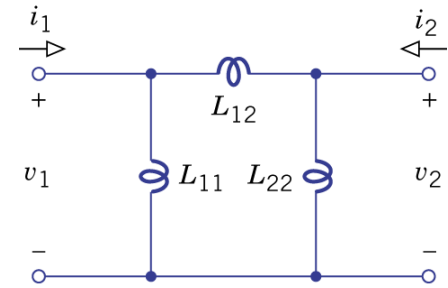

T – network :

$$\begin{aligned} KVL \rightarrow \underline{V}_1 &= j\omega(L_1 \mp M)\underline{I}_1 \pm j\omega M(\underline{I}_1 + \underline{I}_2) = j\omega L_1 \underline{I}_1 \pm j\omega M \underline{I}_2 \\ \underline{V}_2 &= j\omega(L_2 \mp M)\underline{I}_2 \pm j\omega M(\underline{I}_1 + \underline{I}_2) = \pm j\omega M \underline{I}_1 \pm j\omega L_2 \underline{I}_2 \end{aligned}$$

$$Y - \Delta \text{ transformation(4.37) : } R_{ab} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

π – network :


$$(L_1 \mp M)(\pm M) + (\pm M)(L_2 \mp M) + (L_2 \mp M)(L_1 \mp M) = L_1 L_2 - M^2$$

$$L_{11} = \frac{L_1 L_2 - M^2}{L_2 \mp M}, L_{12} = \frac{L_1 L_2 - M^2}{\pm M}, L_{22} = \frac{L_1 L_2 - M^2}{L_1 \mp M}$$

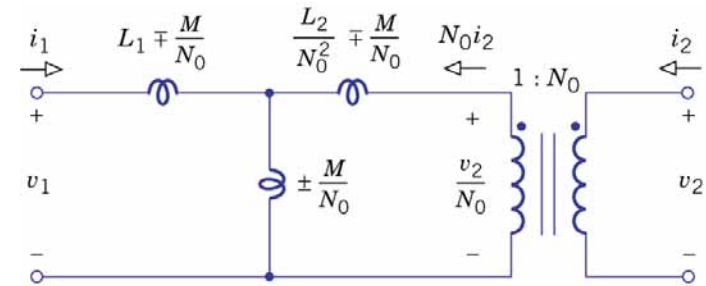
4. Equivalent circuits

$$\begin{aligned} \text{if } N_o &= \pm \frac{L_2}{M} \\ \rightarrow \mp \frac{M}{N_o} &= -\frac{M^2}{L_2} = -k^2 L_1 \Rightarrow \\ \frac{L_2}{N_o^2} \mp \frac{M}{N_o} &= 0 \end{aligned}$$


$$\begin{aligned} \text{if } N_o &= \pm \frac{M}{L_1} \\ L_1 \mp \frac{M}{N_o} &= 0 \Rightarrow \\ \frac{L_2}{N_o^2} &= \frac{L_1}{k^2} \end{aligned}$$



(a)

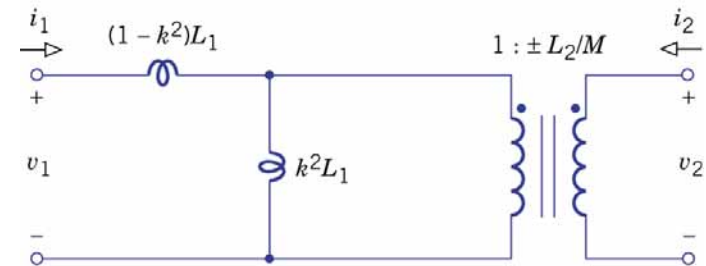


(b)

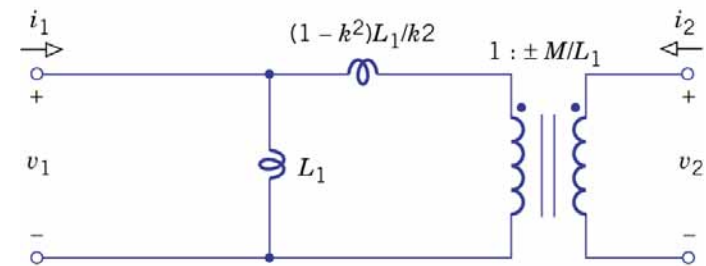


(c)

Discussion

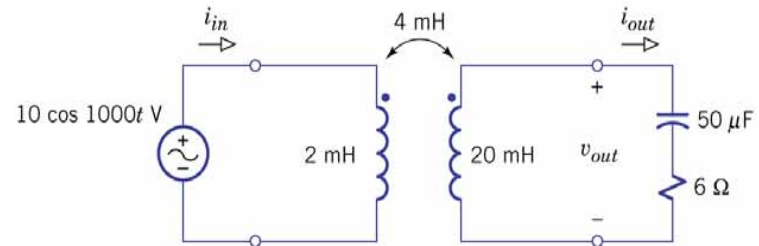1. Ex. 8.7 find $\underline{I}_{in}$, $\underline{I}_{out}$, $\underline{V}_{out}$



(a) Circuit with magnetic coupling

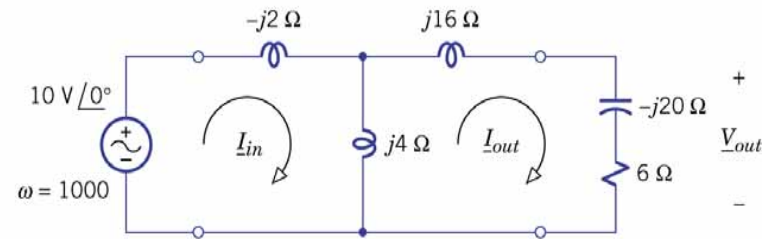

(b) Frequency-domain diagram with the equivalent tee network

$$L_1 - M = -2\text{mH}, L_2 - M = 16\text{mH}$$

$$\text{mesh equation, } \begin{bmatrix} -j2 + j4 & -j4 \\ -j4 & j4 + j16 - j20 + 6 \end{bmatrix} \begin{bmatrix} \underline{I}_{in} \\ \underline{I}_{out} \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$\underline{I}_{in} = 3 \angle -36.9^\circ, \underline{I}_{out} = 2 \angle 53.1^\circ, \underline{V}_{out} = (6 - j20)\underline{I}_{out} = 41.8 \angle -20.2^\circ$$

2. Step-up autotransformer, find $\frac{I_{out}}{I_{in}}, \frac{V_{out}}{V_{in}}$

mesh equation

$$\begin{bmatrix} j\omega L_1 & -j\omega(L_1 + M) \\ -j\omega(L_1 + M) & j\omega(L_1 + 2M + L_2) + Z \end{bmatrix} \begin{bmatrix} I_{in} \\ I_{out} \end{bmatrix} = \begin{bmatrix} V_{in} \\ 0 \end{bmatrix}$$


$$\frac{I_{out}}{I_{in}} = \frac{j\omega(L_1 + M)}{j\omega(L_1 + 2M + L_2) + Z}$$

$$\frac{V_{out}}{V_{in}} = \frac{I_{out} Z}{V_{in}} \frac{j\omega(L_1 + M)}{j\omega L_1 Z - \omega^2(L_1 L_2 - M^2)}$$


if $|j\omega(L_1 + 2M + L_2)| \gg |Z|, k = 1$

$$\frac{I_{out}}{I_{in}} = \frac{L_1 + M}{L_1 + 2M + L_2} = \frac{N_1}{N_1 + N_2} \equiv \frac{1}{N}$$

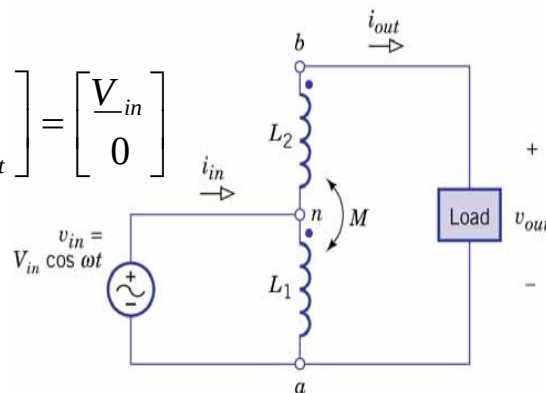
$$\frac{V_{out}}{V_{in}} \approx \frac{L_1 + M}{L_1} = \frac{N_1 + N_2}{N_1} \equiv N$$




(a) Circuit with step-up autotransformer

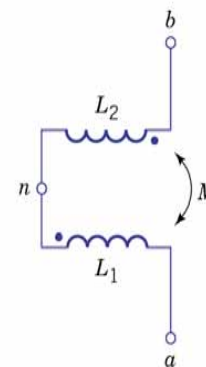

(b) Coils redrawn for clarity

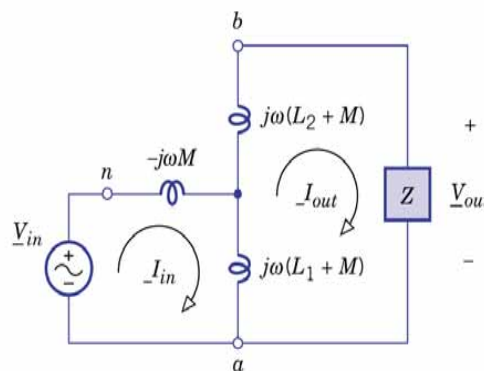

(d) Frequency-domain diagram

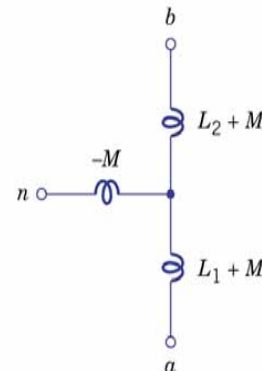

(c) Equivalent tee network

3. Tuned amplifier design


find R, C to give $\omega_o = 10^6$, $Q = 25$

$$k^2 = \frac{M^2}{L_1 L_2} = 0.8$$


$$\rightarrow (1 - k^2)L_1 = 1, k^2 L_1 = 4, \frac{L_2}{M} = 2$$

$$\omega_o = \frac{1}{\sqrt{LC}} = 10^6 \rightarrow C = 62.5 \text{ pF}$$

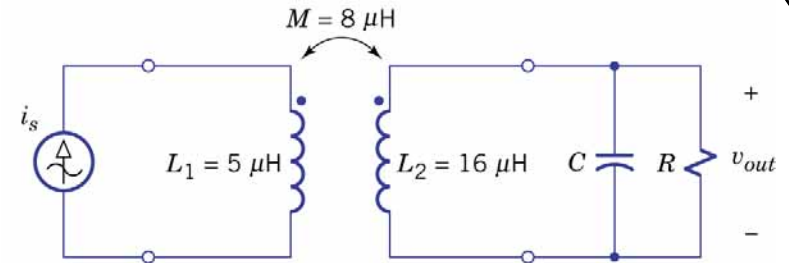
$$Q_{par} = \frac{R}{\omega_o L} = 25 \rightarrow R = 400$$



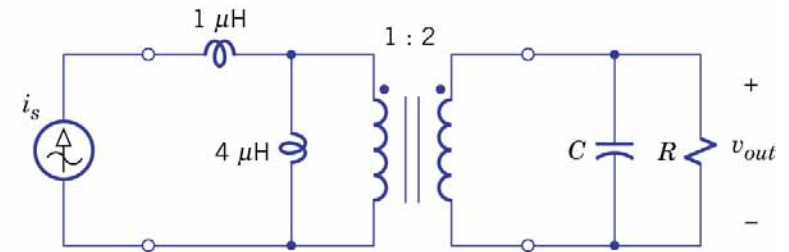(a) Model of "tuned" transistor amplifier



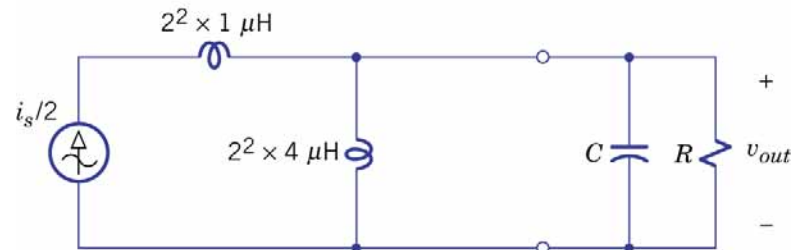(b) Equivalent circuit with an ideal transformer



(c) Referred source network in the secondary