

1. (25%) (a) Find the Thévenin equivalent circuit of the circuit inside the bracket given in Fig.1.
(5%) (b) Use the result of (a) to solve v and i .

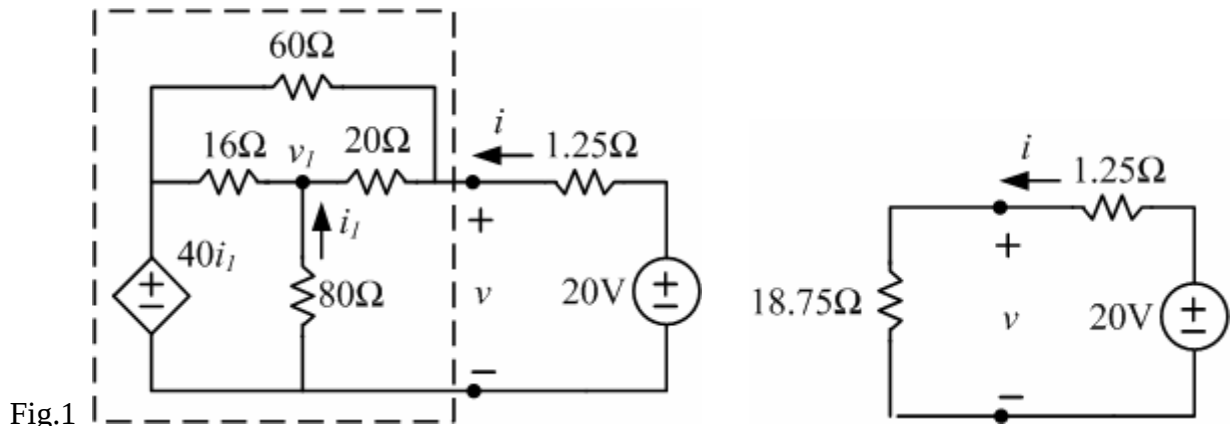


Fig.1

$$i = \frac{v - v_1}{20} + \frac{v - 40i_1}{60} \dots (1), \quad \frac{v_1 - 40i_1}{16} + \frac{v_1}{80} + \frac{v_1 - v}{20} = 0 \dots (2)$$

$$(1) \rightarrow 60i = 3v - 3v_1 + v - 40i_1 = 4v - 3v_1 - 40i_1 \dots (3)$$

$$(2) \rightarrow 5v_1 - 200i_1 + v_1 + 4v_1 - 4v = 0 \rightarrow 10v_1 - 200i_1 - 4v = 0 \dots (4)$$

$$(4) \rightarrow 10v_1 - 200(-\frac{v_1}{80}) = 4v \rightarrow 12.5v_1 = 4v \dots (5)$$

$$\therefore i_1 = -\frac{v_1}{80},$$

$$(3) \rightarrow 60i = 4v - 3v_1 - 40(-\frac{v_1}{80}) = 4v - 2.5v_1 \stackrel{(5)}{=} 4v - 0.8v = 3.2v$$

$$R_{th} = \frac{v}{i} = 18.75$$

$$i = \frac{20}{18.75 + 1.25} = 1A, v = 18.75V$$

2. (30%) For the circuit given in Fig.2, solve v_1 , i_1 , v_2 , and i_2 .

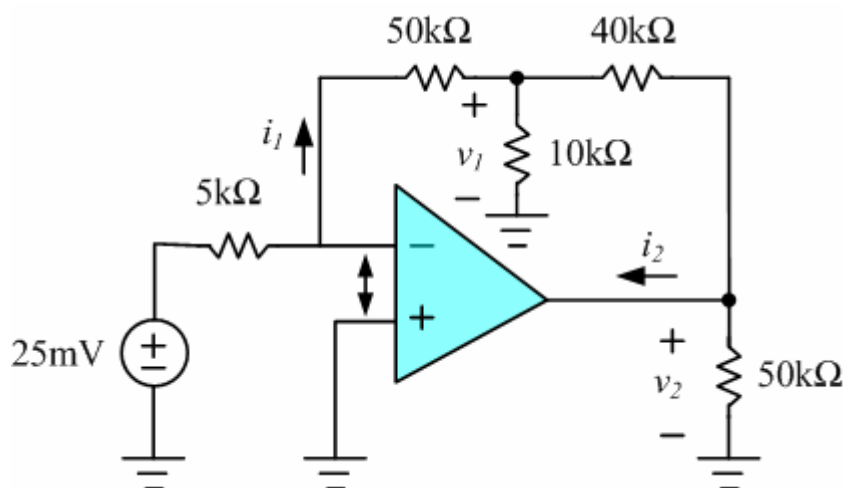


Fig.2

$$i_1 = \frac{25 \times 10^{-3}}{5000} = 5 \mu A$$

$$v_1 = -50 \times 10^3 \times i_1 = -0.25 V$$

$$-5 \times 10^{-6} + \frac{v_1}{10 \times 10^3} + \frac{v_1 - v_2}{40 \times 10^3} = 0 \rightarrow -0.2 + 4v_1 + v_1 - v_2 = 0 \rightarrow v_2 = 5v_1 - 0.2 = -1.45 V$$

$$i_2 = \frac{v_1 - v_2}{40 \times 10^3} - \frac{v_2}{50 \times 10^3} = \frac{1.2}{40 \times 10^3} + \frac{1.45}{50 \times 10^3} = 59 \mu A$$

3. (40%) Use superposition theorem to solve the voltage v given in Fig.3.


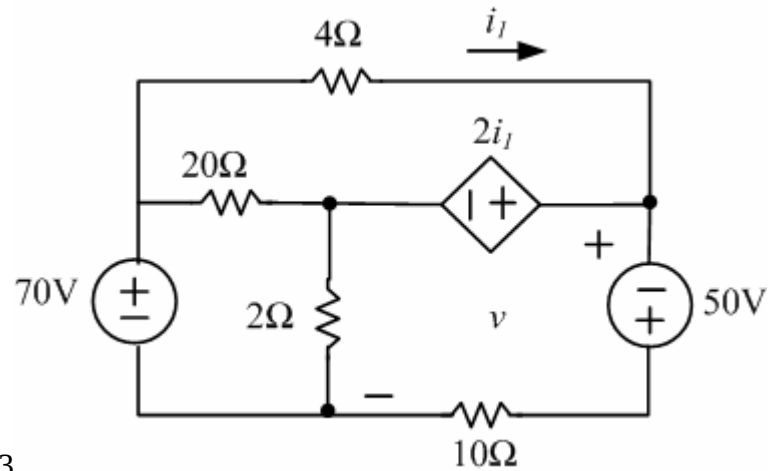


Fig.3

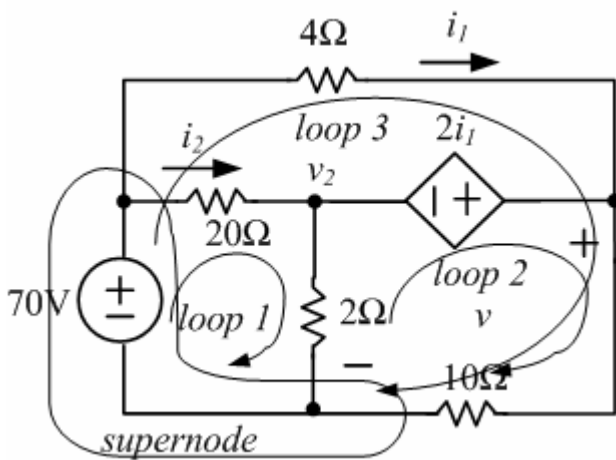


$$\text{loop 1: } 70 = 20i_2 + v_2 \rightarrow i_2 = \frac{70 - v_2}{20} \stackrel{(2)}{=} \frac{7}{2} - \frac{1}{20} \left(\frac{3v}{2} - 35 \right) = -\frac{3v}{40} + \frac{21}{4} \dots (3)$$

$$\text{loop 2: } v_2 + 2i_1 - v = 0 \rightarrow v_2 = v - 2i_1 \stackrel{(1)}{=} v - 2 \left(\frac{35}{2} - \frac{v}{4} \right) = \frac{3v}{2} - 35 \dots (2)$$

$$\text{loop 3: } 70 - 4i_1 - v = 0 \rightarrow i_1 = \frac{35}{2} - \frac{v}{4} \dots (1)$$

$$\text{supernode: } \frac{v_2}{2} + \frac{v}{10} = i_1 + i_2 \stackrel{(1),(2),(3)}{\rightarrow} \frac{1}{2} \left(\frac{3v}{2} - 35 \right) + \frac{v}{10} = \frac{35}{2} - \frac{v}{4} - \frac{3v}{40} + \frac{21}{4}$$
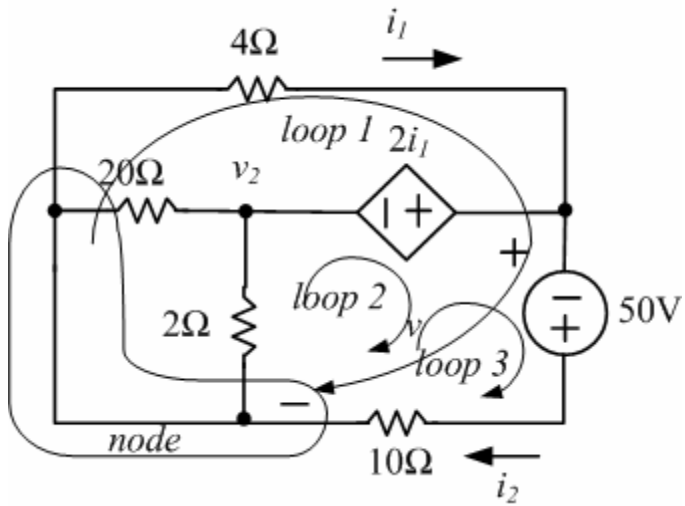
$$\rightarrow \frac{47v}{40} = \frac{161}{4} \rightarrow v = \frac{1610}{47}$$



$$\text{loop1: } 4i_1 + v = 0 \rightarrow i_1 = -\frac{v}{4} \dots (1)$$

$$\text{loop2: } v_2 + 2i_1 - v = 0 \rightarrow v_2 = -2i_1 + v = \frac{3v}{2} \dots (2)$$

$$\text{loop3: } v + 50 - 10i_2 = 0 \rightarrow i_2 = \frac{v}{10} + 5 \dots (3)$$

$$\text{node: } i_1 = \frac{v_2}{20} + \frac{v_2}{2} + i_2 \xrightarrow{(1),(2),(3)} -\frac{v}{4} = \frac{11}{20} \times \frac{3v}{2} + \frac{v}{10} + 5 \Rightarrow -\frac{47}{40}v = 5 \rightarrow v = -\frac{200}{47}$$

$$\text{Total } v = \frac{1610}{47} - \frac{200}{47} = \frac{1410}{47} = 30V$$