
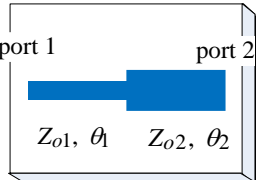
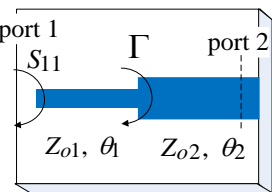
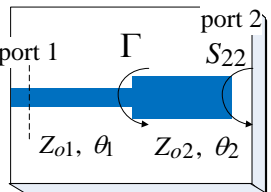
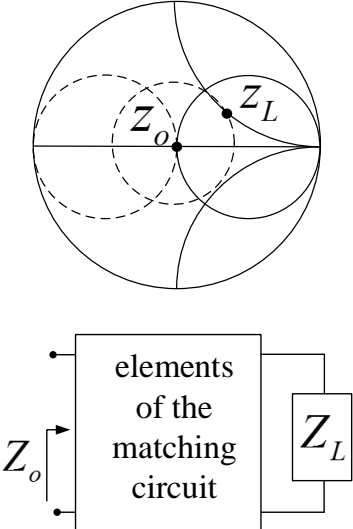
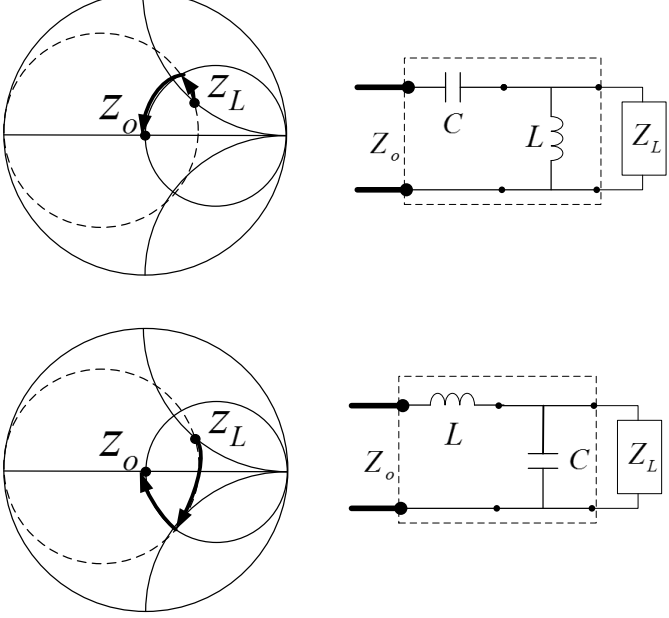


# Microwave Circuits Midterm Examination Solution 2016.11.29


1. Give simplified answer (50%)	(solution)
(1) In case that the load impedance of a double-stub tuner is inside the forbidden region, what does one use a double-stub tuner as a matching circuit?	One can use a transmission line to move the load impedance outside the forbidden region along a VSWR circle.
(2) There are different types of coaxial connectors in page 134 of “point of interest”. Why does a smaller diameter of connector have a higher operating maximum frequency?	Smaller dielectric radial length can increase the maximum frequency of the operating TEM mode.
(3) In case that the input impedance of a microwave device is outside of the Smith chart, what is the physical meaning of this device?	The device has $ \Gamma_{in}  > 1$ or $ R_{in}  < 1$ to be oscillating.
(4) Can you design a lossless matching circuit to match the load impedance of $Z_L = 0$ to be $Z_{in} = Z_o$ ? In case that your answer is “Y”, give an example your lossless matching circuit. In case that your answer is “N”, can you design the matching circuit to be lossy?	A lossless matching circuit cannot change $\text{Re}(Z_L)$ to be $\text{Re}(Z_L) > 0$ . A lossy circuit (or an attenuator) can then increase $\text{Re}(Z_L) > 0$ then a lossless matching circuit can get to be $Z_{in} = Z_o$ .
(5) Calculate the S-matrix of a microwave circuit having two series lossless transmission lines with lengths of $l_1$ and $l_2$ and characteristic impedances of $Z_{o1}$ and $Z_{o2}$ .	<div style="text-align: center;">  </div> <p style="text-align: center;">for <math>S_{11}</math> and <math>S_{21}</math> <span style="margin-left: 200px;">for <math>S_{22}</math> and <math>S_{12}</math></span></p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  </div> <div style="text-align: center;">  </div> </div> $\Gamma = \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}}, T = 1 + \Gamma = \frac{2Z_{o2}}{Z_{o2} + Z_{o1}}$ $\Rightarrow S_{11} = \left. \frac{b_1}{a_1} \right _{a_2=0} = \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}} e^{-j2\beta l_1} = \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}} e^{-j2\theta_1}$ $S_{21} = \left. \frac{b_2}{a_1} \right _{a_2=0} = \frac{2Z_{o2}}{Z_{o2} + Z_{o1}} e^{-j\beta(l_1+l_2)} = \frac{2Z_{o2}}{Z_{o2} + Z_{o1}} e^{-j(\theta_1+\theta_2)}$ $\Rightarrow S_{22} = \frac{Z_{o1} - Z_{o2}}{Z_{o1} + Z_{o2}} e^{-j2\beta l_2} = \frac{Z_{o1} - Z_{o2}}{Z_{o1} + Z_{o2}} e^{-j2\theta_2}$ $S_{12} = \frac{2Z_{o1}}{Z_{o1} + Z_{o2}} e^{-j2\beta(l_1+l_2)} = \frac{2Z_{o1}}{Z_{o1} + Z_{o2}} e^{-j(\theta_1+\theta_2)}$

<p>(6) The quality factor <math>Q_u</math> of a microstrip resonator is smaller than those of coaxial resonator and rectangular cavity resonator. What can you provide two approaches to give higher <math>Q_u</math> value of microwave resonator?</p>	<p>One can reduce <math>\alpha_d</math> and <math>\alpha_c</math> to get the equivalent resistor <math>R</math> to be smaller.</p>
<p>(7) Explain four reasons to use S-matrix for microwave circuits.</p>	<ol style="list-style-type: none"> <li>(1) The match load has a broadband range.</li> <li>(2) The measurable S-matrix are in terms of incident, reflected and transmitted waves.</li> <li>(3) The termination of <math>Z_o</math> causes no oscillation.</li> <li>(4) It is convenient to use microwave network analysis.</li> </ol>
<p>(8) Describe five approaches to reduce the characteristic impedance <math>Z_o</math> of a microstrip line.</p>	<ol style="list-style-type: none"> <li>(1) microstrip width <math>W \uparrow (C \uparrow, Z_o \downarrow)</math></li> <li>(2) substrate dielectric constant <math>\uparrow (C \uparrow, Z_o \downarrow)</math></li> <li>(3) substrate thickness <math>\downarrow (C \uparrow, Z_o \downarrow)</math></li> <li>(4) top metal thickness <math>\uparrow (W \uparrow, C \uparrow, Z_o \downarrow)</math></li> <li>(5) top metal cover distance <math>\downarrow (C \uparrow, Z_o \downarrow)</math></li> <li>(6) additional dielectric material on a microstrip line (<math>C \uparrow, Z_o \downarrow</math>)</li> <li>(7) additional a parallel microstrip line (<math>C \uparrow, Z_o \downarrow</math>)</li> </ol>
<p>(9) Explain the physical use of <math>\epsilon_{eff}</math> for a microstrip line.</p>	<p>One can then use a quasi-TEM line in terms of <math>\epsilon_{eff}</math> to calculate <math>\alpha_d</math>, <math>\beta</math> and <math>Z_o</math> for a microstrip line.</p>
<p>(10) Design two matching circuits from <math>Z_L</math> to <math>Z_o</math> by plotting the moving traces in the Smith chart and related elements.</p> 	

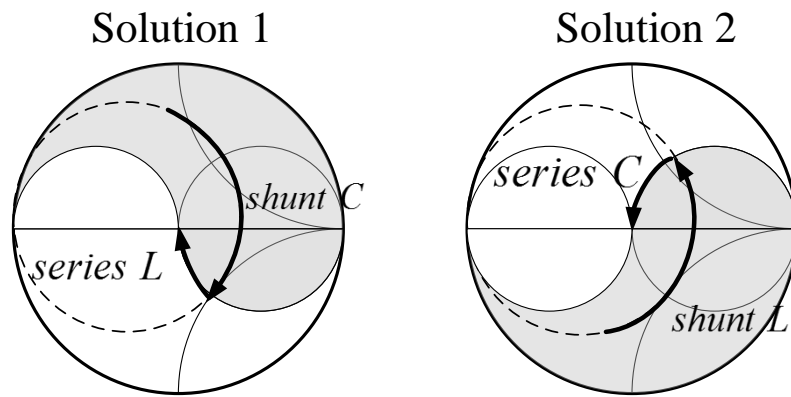2. (20%) For the Example 5.1 in page 231, two L-section matching circuits in Fig.5.3(b) are shunt-series matching circuits. Solution 1 is a shunt C-series L matching circuit and solution 2 is a shunt L-series C matching circuit. In Note slide 5-8, it is not able to design a series-shunt matching circuit. It indicates that the load is in a certain region of the Smith chart to give a related L-section matching circuit. Try plot and identify the available region for the load of this example in Smith charts for (1) a shunt C-series L matching circuit for solution 1 and (2) a shunt L-series C matching circuit for solution 2.



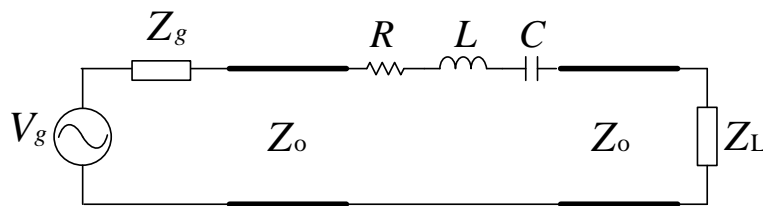3. (30%) A series RLC resonator with  $R=1\Omega$ ,  $L=\frac{150}{\pi}$  nH,  $C=\frac{5}{3\pi}$  pF in series with a transmission line with  $V_g=1V$ ,  $Z_g=Z_o=Z_L=50\Omega$  is shown as the following circuit.



Calculate

(1) the resonant frequency $f_o$ ,	$f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{\frac{150}{\pi}10^{-9} \frac{5}{3\pi}10^{-12}}} = 1GHz$
(2) the unloaded $Q_U(f_o)$ ,	$Q_U(\omega_o) = \frac{\omega_o L}{R} = \frac{2\pi10^9 \frac{150}{\pi}10^{-9}}{1} = 300$
(3) the external $Q_e(f_o)$ ,	$Q_e(\omega_o) = \frac{\omega_o L}{2Z_o} = \frac{2\pi10^9 \frac{150}{\pi}10^{-9}}{2 \times 50} = 3$
(4) the loaded $Q_L(f_o)$ ,	$Q_L(\omega_o) = \frac{\omega_o L}{R + 2Z_o} = \frac{2\pi10^9 \frac{150}{\pi}10^{-9}}{1 + 2 \times 50} = 2.97$
(5) the coefficient of coupling $g$ of the resulting circuit,	$g = \frac{Q_U}{Q_e} = 100$

(6) the 3dB bandwidth of the resulting circuit,	$BW_{3dB} = \frac{f_o}{Q_L} = \frac{1}{2.97} GHz \approx 337 MHz$
(7) the power generated from the source,	$P_{inc} = P_{avs} = \frac{1}{2} \left  \frac{V_g}{Z_g + Z_g^*} \right ^2 R_g = \frac{1}{2} \frac{ V_g ^2}{4R_g^2} R_g = \frac{1}{2} \frac{ V_g ^2}{4R_g}$ $= \frac{1}{2} \frac{1}{4 \times 50} W = 2.5mW = 3.98dBm$
(8) the power delivered to the load at $f_o$ ,	$P_L = \frac{1}{2} \left  \frac{V_g}{Z_g + Z_L + R} \right ^2 R_L = \frac{1}{2} \left  \frac{1}{50 + 50 + 10} \right ^2 50$ $= 2.45mW = 3.89dBm$ $= P_{inc} \left( \frac{2Z_o}{2Z_o + R} \right)^2 = P_{inc} \left( \frac{Q_L}{Q_E} \right)^2$
(9) the insertion loss of the RLC resonator.	$IL = 3.98 - 3.89 = 0.09dB$
(10) What type of this circuit with specific values?	It is a bandpass filter with its center frequency at $1GHz$ with $Q_L = 2.97$ , $BW_{3dB} = 337MHz$ and $IL = 0.09dB$ .