

微波電路講義

Microwave Circuits Notes

瞿大雄 教授
國立臺灣大學電機工程學系

微波電路講義

General Information

1. Class: EE5009(921U0560) Tue. 9:10-12:10, EE-II 144
2. Textbook: *Microwave Engineering*, 4th ed., D.M. Pozar, John Wiley & Sons, 2011
3. Scopes: basic principles and design formula of passive and active microwave linear circuits using transmission line theory in terms of $V(z)$ and $I(z)$ ($V^+(z)$, $V^-(z)$, $I^+(z)$, $I^-(z)$) representation and microwave network analysis in terms of S-parameters
4. Contents:
 - Ch.2 Transmission line theory, 2.1, 2.3-2.7
 - Ch.3 Transmission lines and waveguides, 3.1, 3.5, 3.7, 3.8, 3.11
 - Ch.4 Microwave network analysis, 4.1-4.6
 - Ch.5 Impedance matching and tuning, 5.1-5.9
 - Ch.6 Microwave resonators, 6.1, 6.2, 6.5, 6.6
 - Ch.7 Power dividers and directional couplers, 7.1-7.3, 7.5-7.9

Ch.8 Microwave filters, 8.3-8.8

Ch.9 Theory and design of ferrimagnetic components, 9.6

Ch.10 Noise and nonlinear distortion, 10.1-10.4

Ch.11 Active RF and microwave devices, 11.1-11.4

Ch.12 Microwave amplifier design, 12.1-12.5

Ch.13 Oscillators and mixers, 13.2, 13.5

Ch.14 Introduction to microwave systems, 14.1-14.6

5. Estimated time table: 48hrs

	Date	Notes		Date	Notes
1	9/13	~2-9	10	11/15	university carnival
2	9/20	~2-34	11	11/22	~8-53
3	9/27	~4-11, Quiz#1(ch.2)	12	11/29	~10-16, Quiz#4(ch.7)
4	10/4	~4-27, Quiz#2(ch.3)	13	12/6	APMC
5	10/11	~5-5	14	12/13	~11-11. Quiz#5(ch.8)
6	10/18	~5-36, Quiz#3(ch.4)	15	12/20	~11-38
7	10/25	~6-20	16	12/27	~12-36, Quiz#6(ch.10,11)
8	11/1	~7-25	17	1/3	~14-14
9	11/8	Midterm Exam (~ch.6)	18	1/10	Final Exam

6. Grades: review quiz 15%, midterm exam. (Ch.2-Ch.6) 40%, final exam. (Ch.7-Ch.14) 45%

7. Office hour: Tue. 14:00~16:00 @room 541, or thc@ntu.edu.tw

8. Related readings:

(1) *Foundations of interconnect and microstrip design*, 3rd ed., T.C. Edwards, M.B. Steer, John Wiley & Sons, 2000.

(2) *Microwave engineering using microstrip circuits*, Fooks and Zakarevicius, Prentice Hall, 1990.

(3) *RF/microwave circuit design for wireless applications*, U.L. Rohde and D.P. Newkirk, John Wiley & Sons, 2000.

(4) *Microwave and rf design*, 2nd ed., M. Steer, Scitech, 2013.

(5) *Radio frequency and microwave electronics*, M. M. Radmanesh, Prentice Hall, 2001.

(6) *Microwave and RF engineering*, R. Sorrentino and G. Bianchi, John Wiley & Sons, 2009.

*(7) *Foundations for microwave engineering*, R.E. Collin, McGraw-Hill, 2nd ed., 1992.

9. Notes (including solved problems and ADS examples) are available at <http://cc.ee.ntu.edu.tw/~thc/> or comm.ntu.edu.tw/faculty.htm

Chapter 1 Introduction

1. Definition

Microwave: designating or of that part of the electromagnetic spectrum between the far infrared and some lower frequency limit: commonly regarded as extending from 300,000 to 300 megahertz. (Webster's dictionary)

f: 300MHz - 300GHz $\Rightarrow \lambda$: 100cm - 0.1cm
electromagnetic spectrum (p.2, Fig.1.1)

2. Why use microwaves?

(1) Antenna gain is proportional to the electric size of the antenna.

$\Rightarrow f \uparrow$, gain \uparrow (p.665, eq.(14.12))

miniature microwave system possible

$$D_{\max} = \frac{4\pi A}{\lambda^2}$$

(2) $f \uparrow \Rightarrow$ available bandwidth \uparrow (p.671, Sec.14.2)

e.g., TV BW=6MHz

10% BW of VHF @60MHz for 1channel

1% BW of U-band @60GHz for 100 channels

(3) Line of sight propagation and not affected by cloud, fog, ...
⇒ frequency reuse in satellite and terrestrial communications
(frequency division duplexing, FDD)

(4) Radar cross section (RCS) is proportional to the target electrical size.
⇒ frequency ↑, RCS ↑ (p.696, Table 14.3) $\sigma = \frac{P_s}{S_t}$ (14.39)
radar application, see p.690

(5) Molecular, atomic and nuclear resonances occur at microwave frequencies (p.703, Fig.14.29)
⇒ astronomy, medical diagnostics and treatment, remote sensing and industrial heating applications

3. Biological effects and safety

non-ionized radiation ⇒ thermal effect

IEEE standard C95.1-2005 (p.707, Fig. 14.32)

Excessive radiation may be dangerous to brain, eye, genital, stomach organs, ⇒ cataract, sterility, cancer,

<http://www.fda.gov/Radiation-EmittingProducts/RadiationEmittingProductsandProcedures/HomeBusinessandEntertainment/CellPhones/default.htm>


Chapter 2 Transmission Line Theory

- 2.1 The lumped-element circuit model for a transmission line
transmission line or telegrapher equation,
traveling wave solution
- 2.3 The terminated lossless transmission line
 Z_{in} , Γ , VSWR
time-average power flow
- 2.4 The Smith chart
 Z_{in} -plot conformal mapped on Γ -plot
- 2.5 The quarter-wave transformer
frequency response, TDR
- 2.6 Generator and load mismatches
impedance match, conjugate match
- 2.7 Lossy transmission lines
low loss line, distortionless line
perturbation method

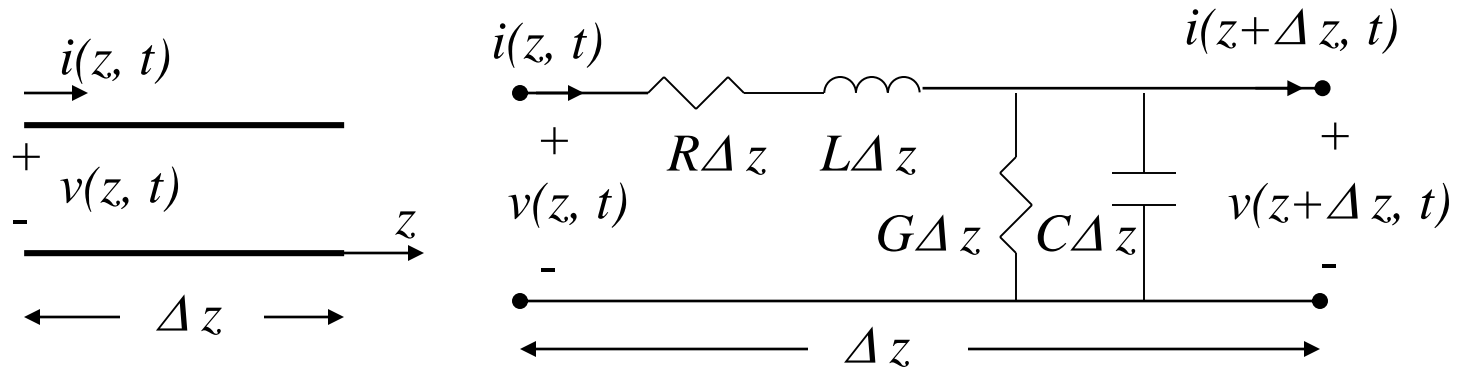2.1 The lumped-element circuit model for a transmission line

- Transmission line equation

TEM lines: coaxial line, parallel line and stripline



R, L: conductor resistance, inductance/unit length (series elements)

G, C: dielectric conductance, capacitance/unit length (parallel elements)

$$\frac{\partial v(z, t)}{\partial z} = -Ri(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\text{KVL, KCL (2.1)} \Rightarrow \frac{\partial i(z, t)}{\partial z} = -Gv(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

time-domain form of transmission line equation, or telegrapher equation

微波電路講義

⇒ time-harmonic form $e^{j\omega t}$

$$v(z,t) = \text{Re}[V(z)e^{j\omega t}], i(z,t) = \text{Re}[I(z)e^{j\omega t}]$$

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z)$$

• Traveling wave solution

$$V(z) \equiv V^+(z) + V^-(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

$$I(z) \equiv I^+(z) + I^-(z) = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z} = \frac{1}{Z_o} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z})$$

$$\Rightarrow Z_o \equiv \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} : \text{characteristic impedance}$$

(derivation)

$$\frac{dV(z)}{dz} = -\gamma V_o^+ e^{-\gamma z} + \gamma V_o^- e^{\gamma z} = -(R + j\omega L)I(z) \rightarrow I(z) = \frac{\gamma}{R + j\omega L} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}) = \sqrt{\frac{G + j\omega C}{R + j\omega L}} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z})$$


$$= \frac{1}{Z_o} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}) = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z} \equiv I^+(z) + I^-(z) \Rightarrow Z_o \equiv \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

⇒ wave equation

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0, \quad \frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0$$

$$\gamma \equiv \sqrt{(R + j\omega L)(G + j\omega C)} \equiv \alpha + j\beta$$

propagation constant

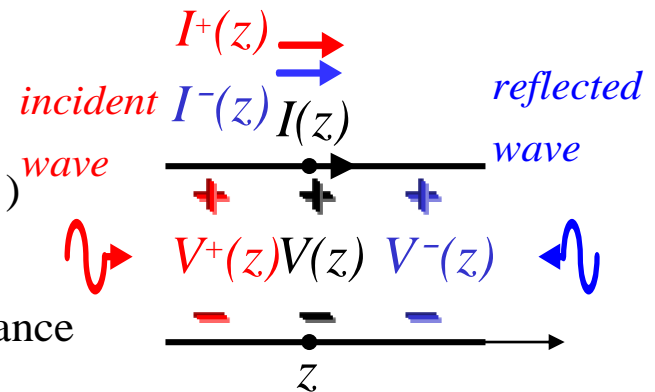

time-domain solution

$$v(z,t) = |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \angle V_o^+) + |V_o^-| e^{\alpha z} \cos(\omega t + \beta z + \angle V_o^-)$$


$$i(z,t) = |I_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \angle I_o^+) + |I_o^-| e^{\alpha z} \cos(\omega t + \beta z + \angle I_o^-)$$

Discussion:

1. attenuation constant

$$|V^+(1m)| = |V^+(0m)| e^{-\alpha}$$

$$\alpha = \ln \frac{|V^+(0m)|}{|V^+(1m)|} \text{ (Neper)} = 20 \log \frac{|V^+(0m)|}{|V^+(1m)|} \text{ (dB)}, 1 \text{ Np} = 20 \log e \text{ dB} = 8.68 \text{ dB}$$

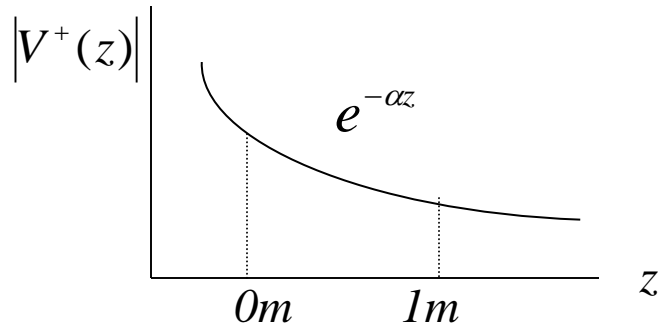

$$|P^+(z)| = |P^+(0)| e^{-2\alpha z}$$

2. phase constant $\beta = \frac{2\pi}{\lambda} = \frac{\omega}{v_p}$

wavelength $\lambda = \frac{2\pi}{\beta}$

phase velocity $v_p = \frac{\omega}{\beta}$

group velocity $v_g = \left(\frac{d\beta}{d\omega}\right)^{-1}$

3. characteristic impedance (wave impedance)

$$Z_o \equiv \frac{V_o^+}{I_o^+} (= \frac{V^+(z)}{I^+(z)}) = -\frac{V_o^-}{I_o^-} (= -\frac{V^-(z)}{I^-(z)})$$

input impedance

$$Z_{in}(z) \equiv \frac{V(z)}{I(z)} (= \frac{V^+(z) + V^-(z)}{I^+(z) + I^-(z)}) = \frac{V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}}{I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z}}$$


4.

$$P^+(z) \equiv V^+(z)I^{+*}(z) = V_o^+ e^{-\alpha z} I_o^{+*} e^{-\alpha z} = V_o^+ e^{-\alpha z} \frac{V_o^{+*}}{Z_o} e^{-\alpha z} = \frac{|V_o^+|^2}{Z_o} e^{-2\alpha z}$$

$$P^-(z) \equiv V^-(z)I^{-*}(z) = V_o^- e^{\alpha z} I_o^{-*} e^{\alpha z} = V_o^- e^{\alpha z} \left(-\frac{V_o^{-*}}{Z_o}\right) e^{\alpha z} = -\frac{|V_o^-|^2}{Z_o} e^{2\alpha z}$$

5. Transmission line equation can be derived from the Maxwell's equations (Sec. 2.2 on coaxial line example).

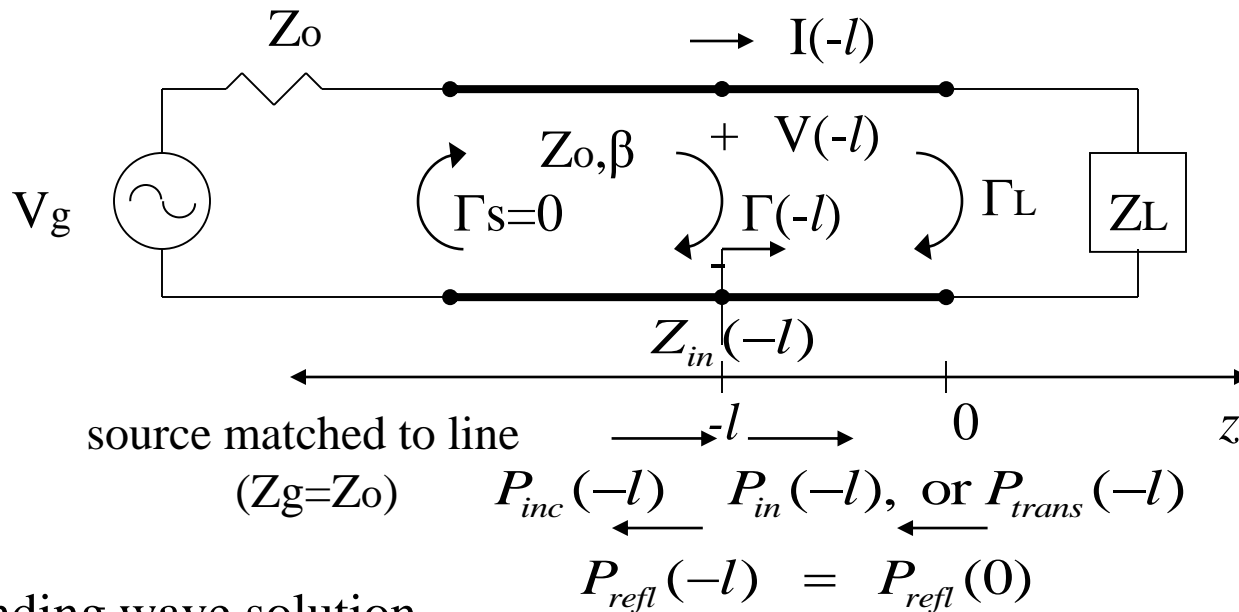2.3 The terminated lossless transmission line



standing wave solution

$$V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z}$$

$$I(z) = I_o^+ e^{-j\beta z} + I_o^- e^{j\beta z} = \frac{V_o^+}{Z_o} e^{-j\beta z} - \frac{V_o^-}{Z_o} e^{j\beta z}$$

- Reflection coefficient (applications in measurement, radar, and remote sensing)

$$\Gamma(-l) \equiv \frac{V^-(-l)}{V^+(-l)} = \frac{V_o^- e^{-j\beta l}}{V_o^+ e^{j\beta l}} = \Gamma_L e^{-j2\beta l} = e^{-j\beta l} \Gamma_L e^{-j\beta l}$$

$$\therefore \Gamma(0) = \frac{V_o^-}{V_o^+} \equiv \Gamma_L$$

- Input impedance (application in circuit design)

$$Z_{in}(-l) \equiv \frac{V(-l)}{I(-l)} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l}$$

(derivation)

$$Z_{in}(-l) = \frac{V(-l)}{I(-l)} = Z_o \frac{V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l}}{V_o^+ e^{j\beta l} - V_o^- e^{-j\beta l}} = Z_o \frac{V_o^+ e^{j\beta l} (1 + \Gamma_L e^{-2j\beta l})}{V_o^+ e^{j\beta l} (1 - \Gamma_L e^{-2j\beta l})} = Z_o \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}}$$

$$\xrightarrow{l=0} Z_{in}(0) = \frac{V(0)}{I(0)} \equiv Z_L = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$$\begin{aligned} Z_{in}(-l) &= Z_o \frac{e^{j\beta l} + \Gamma_L e^{-j\beta l}}{e^{j\beta l} - \Gamma_L e^{-j\beta l}} = Z_o \frac{(Z_L + Z_o)e^{j\beta l} + (Z_L - Z_o)e^{-j\beta l}}{(Z_L + Z_o)e^{j\beta l} - (Z_L - Z_o)e^{-j\beta l}} = Z_o \frac{Z_L(e^{j\beta l} + e^{-j\beta l}) + Z_o(e^{j\beta l} - e^{-j\beta l})}{Z_L(e^{j\beta l} - e^{-j\beta l}) + Z_o(e^{j\beta l} + e^{-j\beta l})} \\ &= Z_o \frac{Z_L \cos \beta l + jZ_o \sin \beta l}{jZ_L \sin \beta l + Z_o \cos \beta l} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \end{aligned}$$

- Voltage standing wave ratio

$$\text{VSWR} \equiv \frac{|V_{max}|}{|V_{min}|} = \frac{|1 + |\Gamma_L||}{|1 - |\Gamma_L||}$$

(derivation)

$$V(-l) = V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l} = V_o^+ e^{j\beta l} (1 + \Gamma_L e^{-j2\beta l}) = |V_o^+| e^{j\angle V_o^+} e^{j\beta l} (1 + |\Gamma_L| e^{j\angle \Gamma_L} e^{-j2\beta l})$$

$$|V(-l)| = |V_o^+| |1 + |\Gamma_L| e^{j\angle \Gamma_L} e^{-j2\beta l}|$$

$$\angle \Gamma_L - 2\beta l = \begin{cases} 2n\pi & \rightarrow |V_{max}| = |V_o^+| |1 + |\Gamma_L|| \\ (2n+1)\pi & \rightarrow |V_{min}| = |V_o^+| |1 - |\Gamma_L|| \end{cases}, 2\beta \Delta l = \pi \rightarrow \Delta l = \frac{\pi}{2(2\pi/\lambda)} = \frac{\lambda}{2}$$

- Time-average input or transmitted power flow

$$P_{in}(z) \equiv \frac{1}{T} \int_0^T v(z,t) i(z,t) dt = \frac{1}{2} \text{Re} [V(z) I^*(z)] = \frac{1}{2} \frac{|V_o^+|^2}{Z_o} (1 - |\Gamma_L|^2) = P_{inc} - P_{refl} = P_{trans}$$

constant

time-average incident power

time-average reflected power

(lossless line)

(derivation)

$$\begin{aligned}
 P_{in}(z) &\equiv \frac{1}{T} \int_0^T v(z,t)i(z,t)dt = \frac{1}{T} \int_0^T \text{Re}[V(z)e^{j\omega t}] \text{Re}[I(z)e^{j\omega t}] dt \\
 &= \frac{1}{T} \int_0^T \frac{1}{2} [V(z)e^{j\omega t} + V^*(z)e^{-j\omega t}] \frac{1}{2} [I(z)e^{j\omega t} + I^*(z)e^{-j\omega t}] dt \\
 &= \frac{1}{4T} \int_0^T [V(z)I(z)e^{j2\omega t} + V^*(z)I^*(z)e^{-j2\omega t} + V(z)I^*(z) + V^*(z)I(z)] dt \\
 &= \frac{1}{4T} [V(z)I^*(z) + V^*(z)I(z)] \int_0^T dt = \frac{1}{4T} 2 \text{Re}[V(z)I^*(z)] T \\
 &= \frac{1}{2} \text{Re}[V(z)I^*(z)] \\
 &= \frac{1}{2} \text{Re}\{(V^+ + V^-)(I^+ + I^-)^*\} = \frac{1}{2} \text{Re}\{V^+I^{+*} + V^+I^{-*} + V^-I^{+*} + V^-I^{-*}\} \\
 &= \frac{1}{2} \text{Re}\{V^+I^{+*} - \frac{V^+V^{-*}}{Z_o} + \frac{V^-V^{+*}}{Z_o} + V^-I^{-*}\} = \frac{1}{2} \text{Re}\{V^+I^{+*} + V^-I^{-*}\} = \frac{1}{2} \text{Re}\{P^+ + P^-\} \\
 &= \frac{|V_o^+|^2}{2Z_o} - \frac{|V_o^-|^2}{2Z_o} = \frac{|V_o^+|^2}{2Z_o} (1 - |\Gamma_L|^2) = P_{inc} - P_{refl}, |\Gamma_L| = \frac{|V_o^-|}{|V_o^+|} = \left| \frac{Z_L - Z_o}{Z_L + Z_o} \right|
 \end{aligned}$$

lossless line

• Discussion

1. $Z_{in} \longleftrightarrow \Gamma$ $Z_{in}(z) = Z_o \frac{1+\Gamma(z)}{1-\Gamma(z)}$, $\Gamma(z) = \frac{Z_{in}(z) - Z_o}{Z_{in}(z) + Z_o}$

2. Return loss $RL \equiv -20 \log |\Gamma_L| (dB) = -20 \log \left| \frac{V_o^-}{V_o^+} \right| = -10 \log \left| \frac{P_o^-}{P_o^+} \right|$

<i>e.g.</i> , $ \Gamma_L =$	1	0.1	0
$RL =$	$0dB$	$20dB$	∞dB
VSWR	∞	1.22	1

all incident power is reflected

matched load

"no return loss"

" ∞ return loss"

3. $1 \leq VSWR \leq \infty$

matched load $|\Gamma_L| = 0 \rightarrow VSWR = 1$

Q: VSWR for a lossy line?

"N"

4. passive load $0 \leq |\Gamma_L| \leq 1$, eg. *o.c.* $\Gamma_L = 1$, *s.c.* $\Gamma_L = -1$, matched load $\Gamma_L = 0$
 active load $|\Gamma_L| > 1$



5. Impedance match

$Z_{in}(z)=Z_o \Rightarrow$ no reflected wave $\Gamma(z)=0$, $VSWR=1$, $R_L = \infty$ dB

$P_{in}=P_{in,max}$: maximum power delivered to the load

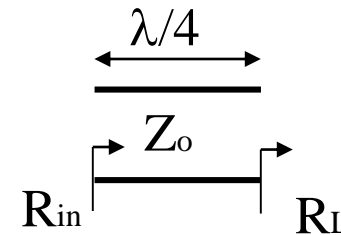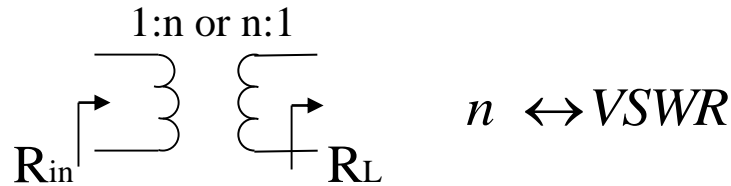6. $l=\lambda/2$, $Z_{in}(l)=Z_L$,

$l=\lambda/4$, $Z_{in}(l)=Z_o^2/Z_L$ impedance inverter or quarter-wave “transformer”



$$1:n \rightarrow R_{in} = \frac{R_L}{n^2}, n:1 \rightarrow R_{in} = n^2 R_L$$

$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + \left| \frac{R_L - Z_o}{R_L + Z_o} \right|}{1 - \left| \frac{R_L - Z_o}{R_L + Z_o} \right|} \begin{cases} \begin{matrix} R_L > Z_o \\ = \frac{R_L}{Z_o} \end{matrix}, R_{in} = \frac{Z_o^2}{R_L} = \frac{R_L}{R_L^2 / Z_o^2} = \frac{R_L}{VSWR^2} \\ \begin{matrix} R_L < Z_o \\ = \frac{Z_o}{R_L} \end{matrix}, R_{in} = \frac{Z_o^2}{R_L} = \frac{R_L}{R_L^2 / Z_o^2} = VSWR^2 R_L \end{cases}$$

7. Mismatch loss (ML)

$$@ z = 0, V_o^+ + V_o^- = V_L$$

$$\Gamma_L \equiv \frac{V_o^-}{V_o^+}, T \equiv \frac{V_L}{V_o^+}$$

$$\rightarrow V_o^+ (1 + \Gamma_L) = V_o^+ T \rightarrow 1 + \Gamma_L = T$$

$$P_{inc} = \frac{1}{2} \frac{|V_o^+|^2}{Z_o}, P_{refl} = \frac{1}{2} \frac{|V_o^-|^2}{Z_o} = \frac{|V_o^-|^2}{|V_o^+|^2} \frac{1}{2} \frac{|V_o^+|^2}{Z_o} = |\Gamma_L|^2 P_{inc} \rightarrow |\Gamma_L|^2 = \frac{P_{refl}}{P_{inc}}$$

$$P_{trans} = \frac{1}{2} \frac{|V_L|^2}{R_L} = \frac{Z_o}{R_L} \frac{|V_L|^2}{2} \frac{1}{Z_o} \frac{|V_o^+|^2}{2} = \frac{Z_o}{R_L} |T|^2 P_{inc} \equiv |T_P|^2 P_{inc} \rightarrow |T_P|^2 = \frac{P_{trans}}{P_{inc}} = \frac{Z_o}{R_L} |T|^2$$

$$P_{inc} = P_{refl} + P_{trans} \rightarrow P_{inc} = |\Gamma_L|^2 P_{inc} + |T_P|^2 P_{inc} \rightarrow 1 = |\Gamma_L|^2 + |T_P|^2 = |\Gamma_L|^2 + \frac{Z_o}{R_L} |T|^2$$

$$ML(\text{mismatch loss}) \equiv -10 \log \frac{P_{trans}}{P_{inc}} = -20 \log |T_P|$$

$$RL(\text{return loss}) \equiv -10 \log \frac{P_{refl}}{P_{inc}} = -20 \log |\Gamma_L|$$


$$R_L = \infty, \Gamma_L = 1, RL = 0dB, T = 2, T_P = 0, ML = \infty dB$$

$$R_L = 0, \Gamma_L = -1, RL = 0dB, T = 0, T_P = 0, ML = \infty dB$$


$$R_L = 150\Omega, Z_o = 50\Omega, \Gamma_L = \frac{1}{2}, RL = 6dB, T = \frac{3}{2}, |T_P|^2 = \frac{50}{150} \frac{9}{4} = \frac{3}{4}, ML = 1.25dB$$

$$R_L = \frac{50}{3}\Omega, Z_o = 50\Omega, \Gamma_L = -\frac{1}{2}, RL = 6dB, T = \frac{1}{2}, |T_P|^2 = \frac{50}{50/3} \frac{1}{4} = \frac{3}{4}, ML = 1.25dB$$

$$R_L = 50\Omega, Z_o = 50\Omega, \Gamma_L = 0, RL = \infty dB, T = 1, |T_P|^2 = 1, ML = 0dB$$

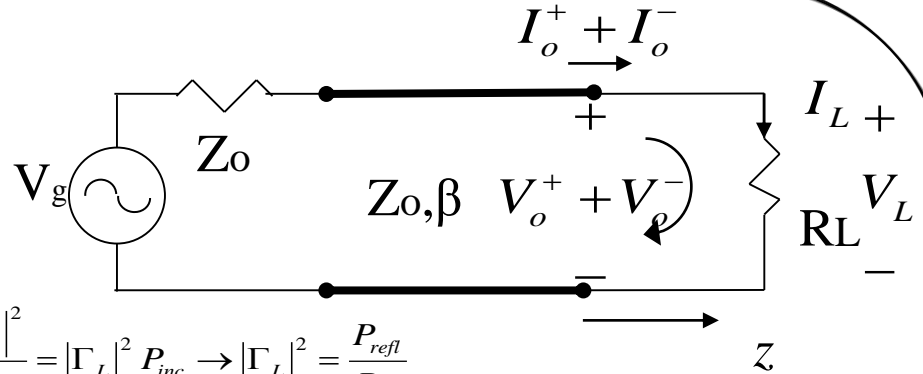

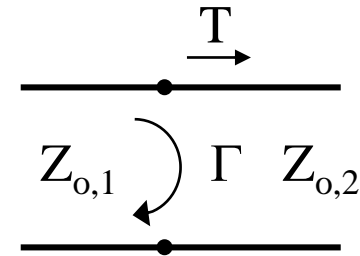e.g. transmission line junction
(p.62, Fig.2.9)



@ junction, $V_1 = V_2 \rightarrow V_{o,1}^+ + V_{o,1}^- = V_{o,2}^+$

$$\Gamma \equiv \frac{V_{o,1}^-}{V_{o,1}^+}, T \equiv \frac{V_{o,2}^+}{V_{o,1}^+} \rightarrow V_{o,1}^+(1 + \Gamma) = V_{o,2}^+ = V_{o,1}^+ T \rightarrow 1 + \Gamma = T$$

$$P_{inc} = \frac{1}{2} \frac{|V_{o,1}^+|^2}{Z_{o,1}}, P_{refl} = \frac{1}{2} \frac{|V_{o,1}^-|^2}{Z_{o,1}} = \frac{|V_{o,1}^-|^2}{|V_{o,1}^+|^2} \frac{1}{2} \frac{|V_{o,1}^+|^2}{Z_{o,1}} = |\Gamma|^2 P_{inc}, |\Gamma|^2 = \frac{P_{refl}}{P_{inc}}$$


$$P_{trans} = \frac{1}{2} \frac{|V_{o,2}^+|^2}{Z_{o,2}} = \frac{Z_{o,1}}{Z_{o,2}} \frac{|V_{o,2}^+|^2}{|V_{o,1}^+|^2} \frac{1}{2} \frac{|V_{o,1}^+|^2}{Z_{o,1}} = \frac{Z_{o,1}}{Z_{o,2}} |T|^2 P_{inc} = |T_P|^2 P_{inc}, |T_P|^2 \equiv \frac{P_{trans}}{P_{inc}} = \frac{Z_{o,1}}{Z_{o,2}} |T|^2$$

$$P_{inc} = P_{refl} + P_{trans} \rightarrow P_{inc} = |\Gamma|^2 P_{inc} + |T_P|^2 P_{inc} \rightarrow 1 = |\Gamma|^2 + |T_P|^2 = |\Gamma|^2 + \frac{Z_{o,1}}{Z_{o,2}} |T|^2$$

$$Z_{o,1} = 50\Omega, Z_{o,2} = 50\Omega, \Gamma = 0, RL = \infty dB, T = 1, |T_P|^2 = 1, ML = 0dB$$

$$Z_{o,1} = 50\Omega, Z_{o,2} = 150\Omega, \Gamma = \frac{1}{2}, RL = 6dB, T = \frac{3}{2}, |T_P|^2 = \frac{3}{4}, ML = 1.25dB$$

8. Open-circuited line

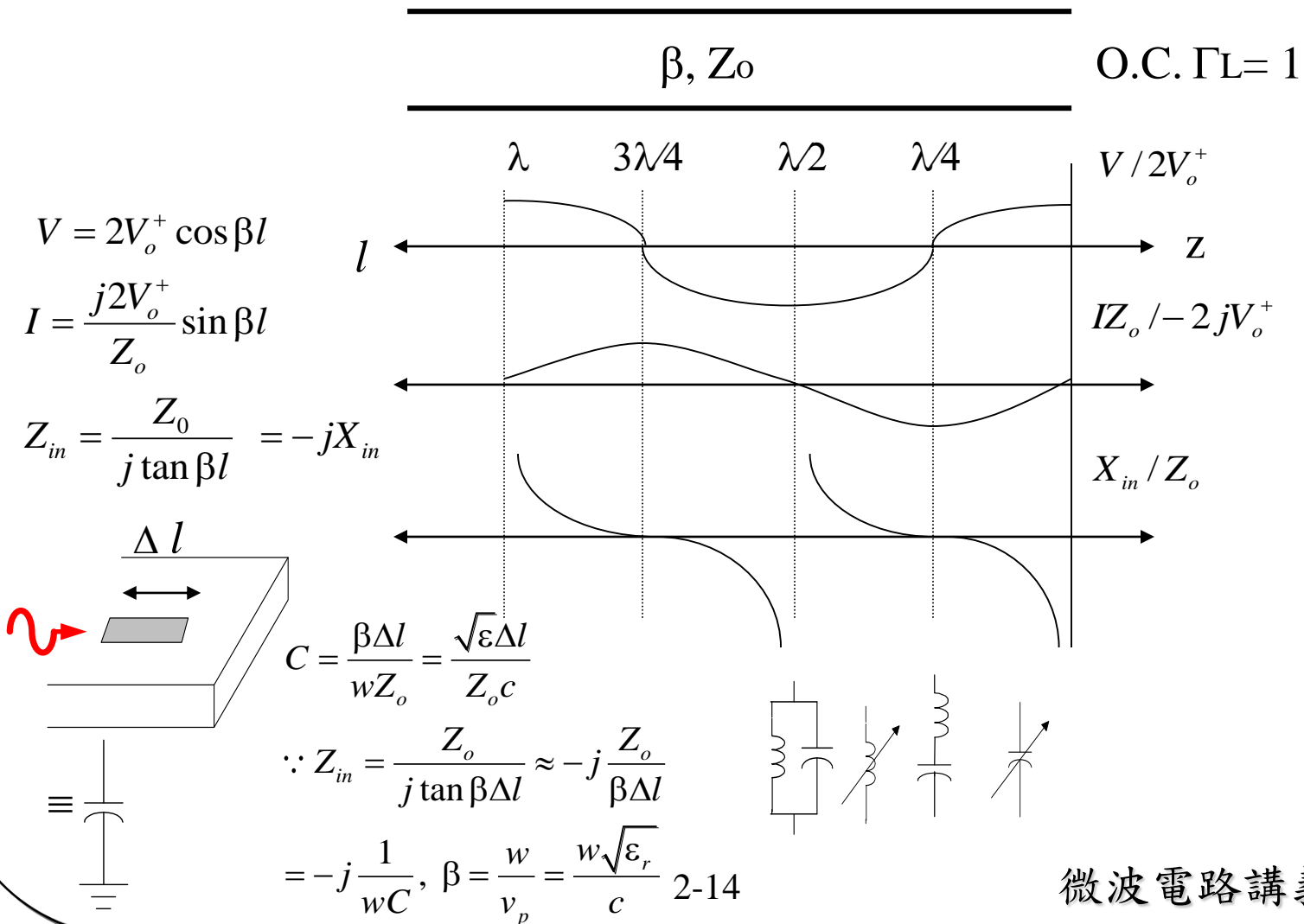



9. Short-circuited line



$$V = j2V_o^+ \sin \beta l$$

$$I = \frac{2V_o^+}{Z_o} \cos \beta l$$


$$Z_{in} = jZ_o \tan \beta l = jX_{in}$$

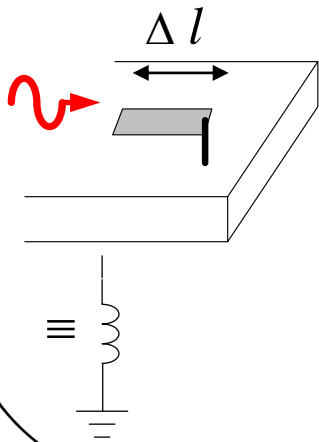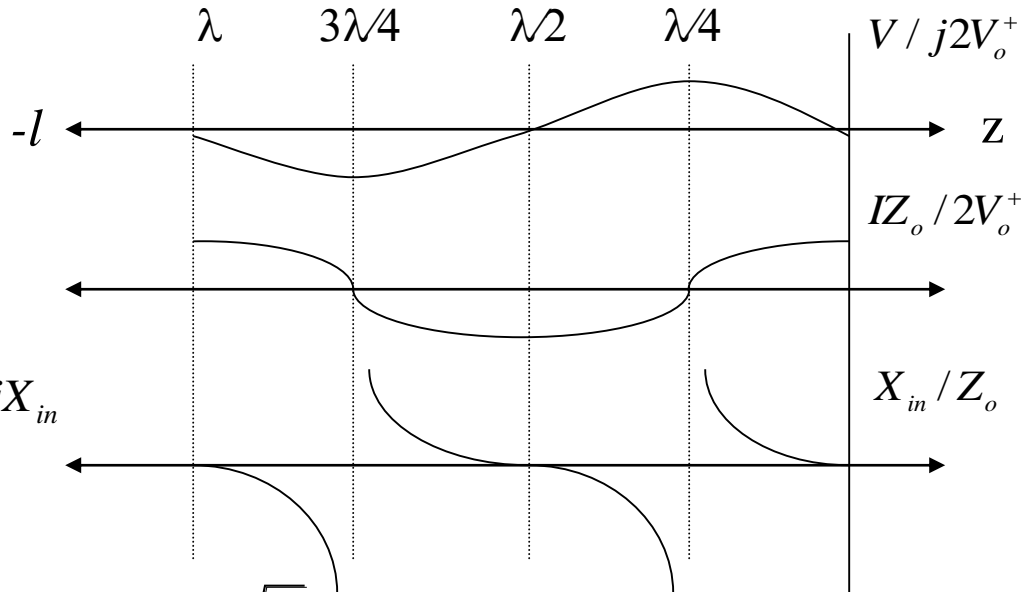

$$L \approx \frac{Z_o \beta \Delta l}{w} = \frac{Z_o \sqrt{\epsilon_r} \Delta l}{c}$$

$$\therefore Z_{in} = j\omega L = jZ_o \tan \beta \Delta l$$
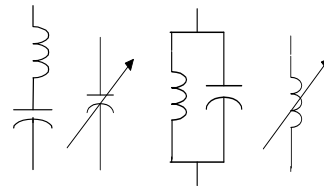
$$\approx jZ_o \beta \Delta l, \quad \beta = \frac{w}{v_p} = \frac{w \sqrt{\epsilon_r}}{c}$$



(derivation of the y-axis scales in Figs.2-6 and 2-8)

open – circuited transmission line

$$V = V_o^+ (e^{-j\beta z} + e^{j\beta z}) = 2V_o^+ \cos \beta z \quad z < 0$$

$$\because z = -l, V = 2V_o^+ \cos \beta l, \text{ or } \frac{V}{2V_o^+} = \cos \beta l$$

$$I = \frac{V_o^+}{Z_o} (e^{-j\beta z} - e^{j\beta z}) = \frac{-j2V_o^+}{Z_o} \sin \beta z = \frac{j2V_o^+}{Z_o} \sin \beta l, \text{ or } \frac{IZ_o}{-j2V_o^+} = -\sin \beta l$$

$$Z_{in} = \frac{Z_o}{j \tan \beta l} = -jX_{in}, \text{ or } \frac{X_{in}}{Z_o} = \frac{1}{\tan \beta l}$$

similarly, for short – circuited transmission line

$$V = V_o^+ (e^{-j\beta z} - e^{j\beta z}) = -j2V_o^+ \sin \beta z = j2V_o^+ \sin \beta l, \text{ or } \frac{V}{j2V_o^+} = \sin \beta l$$

$$I = \frac{V_o^+}{Z_o} (e^{-j\beta z} + e^{j\beta z}) = \frac{2V_o^+}{Z_o} \cos \beta z = \frac{2V_o^+}{Z_o} \cos \beta l, \text{ or } \frac{IZ_o}{2V_o^+} = \cos \beta l$$

$$Z_{in} = jZ_o \tan \beta l = jX_{in}, \text{ or } \frac{X_{in}}{Z_o} = \tan \beta l$$

10. Standing wave expression

$$V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z} = V_o^+ e^{-j\beta z} (1 + \Gamma_L e^{j2\beta z}) = |V_o^+| e^{j\angle V_o^+} e^{-j\beta z} (1 + |\Gamma_L| e^{j\angle \Gamma_L + j2\beta z})$$

$$|V(z)| = |V_o^+| |1 + |\Gamma_L| e^{j\angle \Gamma_L + j2\beta z}|$$

$$= |V_o^+| \sqrt{[1 + |\Gamma_L| \cos(\angle \Gamma_L + 2\beta z)]^2 + |\Gamma_L|^2 \sin^2(\angle \Gamma_L + 2\beta z)}$$

$$= |V_o^+| \sqrt{(1 + |\Gamma_L|)^2 - 2|\Gamma_L| [1 - \cos(\angle \Gamma_L + 2\beta z)]}$$

$$= |V_o^+| \sqrt{(1 + |\Gamma_L|)^2 - 4|\Gamma_L| \sin^2(\beta z + \frac{\angle \Gamma_L}{2})}$$

$$|V(z)| = \begin{cases} |V_{\max}| = |V_o^+| (1 + |\Gamma_L|) \\ |V_{\min}| = |V_o^+| (1 - |\Gamma_L|) \end{cases}, \beta z + \frac{\angle \Gamma_L}{2} = \begin{cases} n\pi \\ (n + \frac{1}{2})\pi \end{cases}$$

$$\rightarrow \angle \Gamma_L + 2\beta z = \angle \Gamma_L - 2\beta l = \begin{cases} 2n\pi \\ (2n + 1)\pi \end{cases}, \Delta l = \frac{\pi}{2\beta} = \frac{\pi}{2(2\pi/\lambda)} = \frac{\lambda}{2}$$

An ADS example of a terminated transmission line is given in Ex1 in Ch2_prj.

11. Measurable quantities

eg. an open – circuited transmission line

$$V(-l) = V_o^+ e^{j\beta l} + V_o^+ e^{-j\beta l} = 2V_o^+ \cos \beta l \rightarrow v(-l, t) = \text{Re}[Ve^{j\omega t}] = 2|V_o^+| \cos \beta l \cos(\omega t + \angle V_o^+)$$

$$I(-l) = \frac{j2V_o^+}{Z_o} \sin \beta l \rightarrow i(-l, t) = \text{Re}[Ie^{j\omega t}] = -\frac{2|V_o^+|}{Z_o} \sin \beta l \sin(\omega t + \angle V_o^+) = \frac{2|V_o^+|}{Z_o} \sin \beta l \cos(\omega t + \angle V_o^+ + \frac{\pi}{2})$$

(1) $Z_{in}(-l)$: most difficult

$$\text{measure } v(-l, t) \text{ and } i(-l, t) \rightarrow V(-l) \text{ and } I(-l) \rightarrow Z_{in}(-l) = \frac{V(-l)}{I(-l)}$$

(2) $\Gamma_{in}(-l)$: less difficult

$$\text{separate } v(-l, t) \text{ into } v^+(-l, t) \text{ and } v^-(-l, t) \rightarrow \text{measure } V^+(-l) \text{ and } V^-(-l) \rightarrow \Gamma_{in}(-l) = \frac{V^-(-l)}{V^+(-l)} = 1e^{-j2\beta l}$$


(3) VSWR: least difficult

$$\text{measure } |v_{amp, \max}|, |v_{amp, \min}|, |v_{amp}(-l)| = 2|V_o^+| |\cos \beta l| \rightarrow VSWR = \frac{|V_{\max}|}{|V_{\min}|} = \frac{|v_{amp, \max}|}{|v_{amp, \min}|}$$

2.4 The Smith chart

Map rectangular plot of $z = Z/Z_o = r + jx$ onto the polar plot of

$$\Gamma = |\Gamma|e^{j\angle\Gamma} (= \Gamma_r + j\Gamma_i), |\Gamma| \leq 1, -180^\circ \leq \angle\Gamma \leq 180^\circ$$

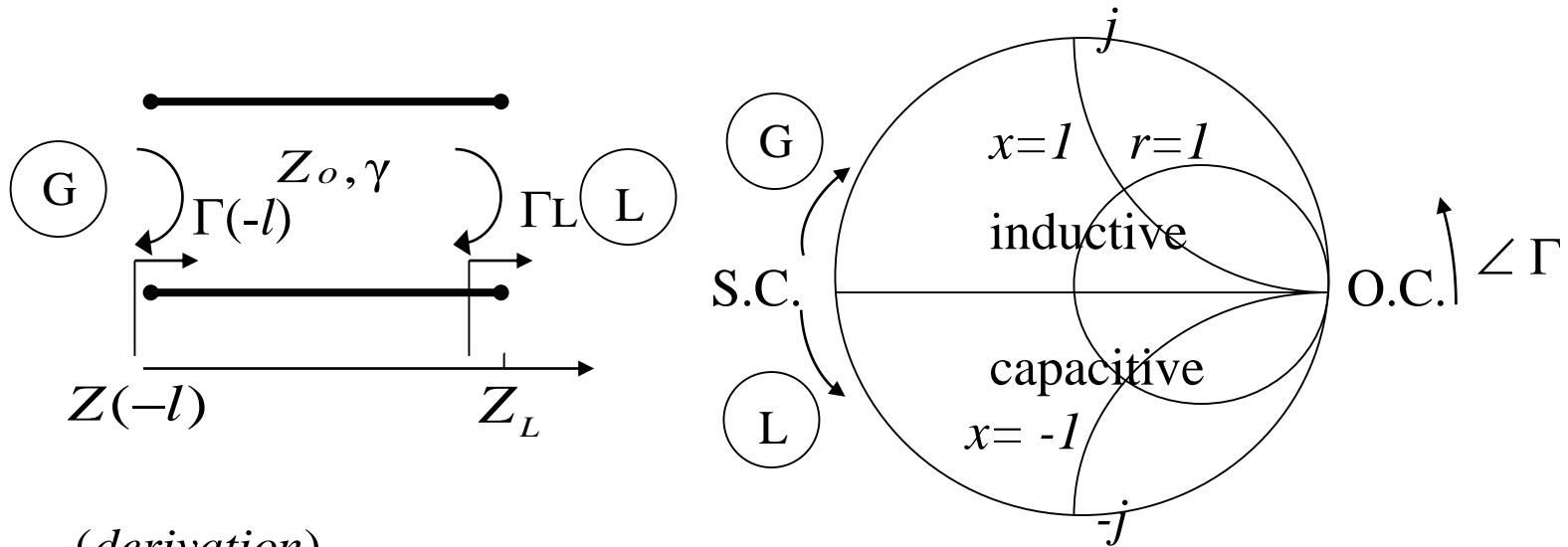


(derivation)

$$\Gamma = \frac{Z - Z_o}{Z + Z_o} = \frac{z - 1}{z + 1} \rightarrow z = r + jx = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} = \frac{1 - \Gamma_r^2 - \Gamma_i^2 + j2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\Rightarrow \left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2, (\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

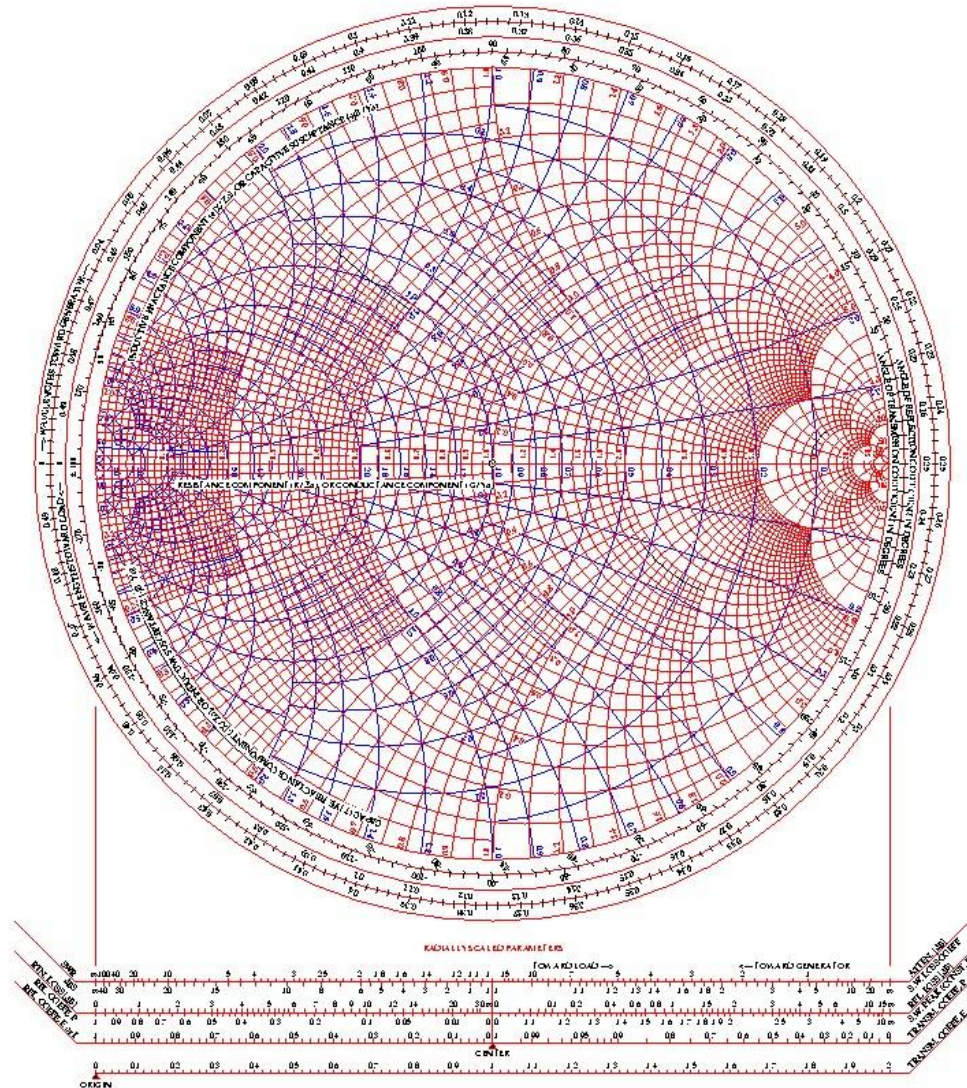NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Discussion

$$1. Z_L \rightarrow z_L \rightarrow \Gamma_L \xrightarrow{\Gamma(-l)=\Gamma_L e^{-j2\beta l}} \Gamma(-l) \rightarrow z(-l) \rightarrow Z(-l)$$

2. r-circle \perp x-circle

3. $VSWR = r_{\max}$


(derivation)

$$VSWR = \frac{|V_{\max}|}{|V_{\min}|} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}, r_{\max} = \frac{R_{\max}}{Z_o} = \frac{|V_{\max}|}{|I_{\min}| Z_o} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$\because V(-l) = V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l} = V_o^+ e^{j\beta l} (1 + \Gamma_L e^{-j2\beta l}) = |V_o^+| e^{j\Delta V_o^+} e^{j\beta l} (1 + |\Gamma_L| e^{j\Delta \Gamma_L} e^{-j2\beta l})$$

$$|V(-l)| = |V_o^+| |1 + |\Gamma_L| e^{j\Delta \Gamma_L - j2\beta l}|, |I(-l)| = \frac{|V_o^+|}{Z_o} |1 - |\Gamma_L| e^{j\Delta \Gamma_L - j2\beta l}|$$

$$\angle \Gamma_L - 2\beta l = \begin{cases} 0 \rightarrow |V_{\max}| = |V_o^+| (1 + |\Gamma_L|), |I_{\min}| = \frac{|V_o^+|}{Z_o} (1 - |\Gamma_L|) \\ \pi \rightarrow |V_{\min}| = |V_o^+| (1 - |\Gamma_L|), |I_{\max}| = \frac{|V_o^+|}{Z_o} (1 + |\Gamma_L|) \end{cases}$$

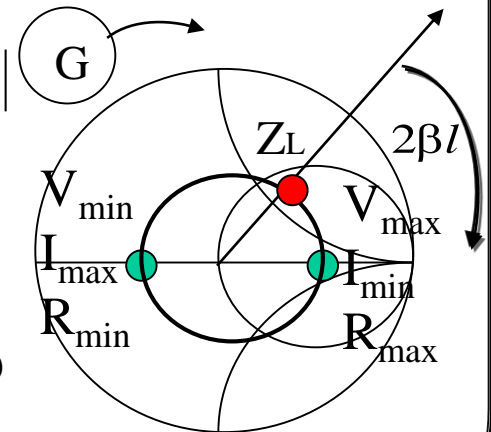


4. $\Delta l = \lambda/2 \rightarrow \Delta \angle \Gamma = 360^\circ$


$$5. z^{-1} (= y = \frac{Y}{Y_o} = YZ_o) \rightarrow \angle \Gamma + 180^\circ$$

(derivation)
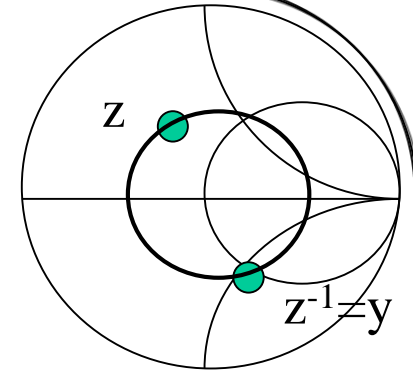
$$z = \frac{1+\Gamma}{1-\Gamma}, z^{-1} = \frac{1}{z} = \frac{1-\Gamma}{1+\Gamma} = \frac{1+\Gamma e^{j\angle 180^\circ}}{1-\Gamma e^{j\angle 180^\circ}} = \frac{1+\Gamma'}{1-\Gamma'}, \Gamma' = \Gamma e^{j\angle 180^\circ}$$


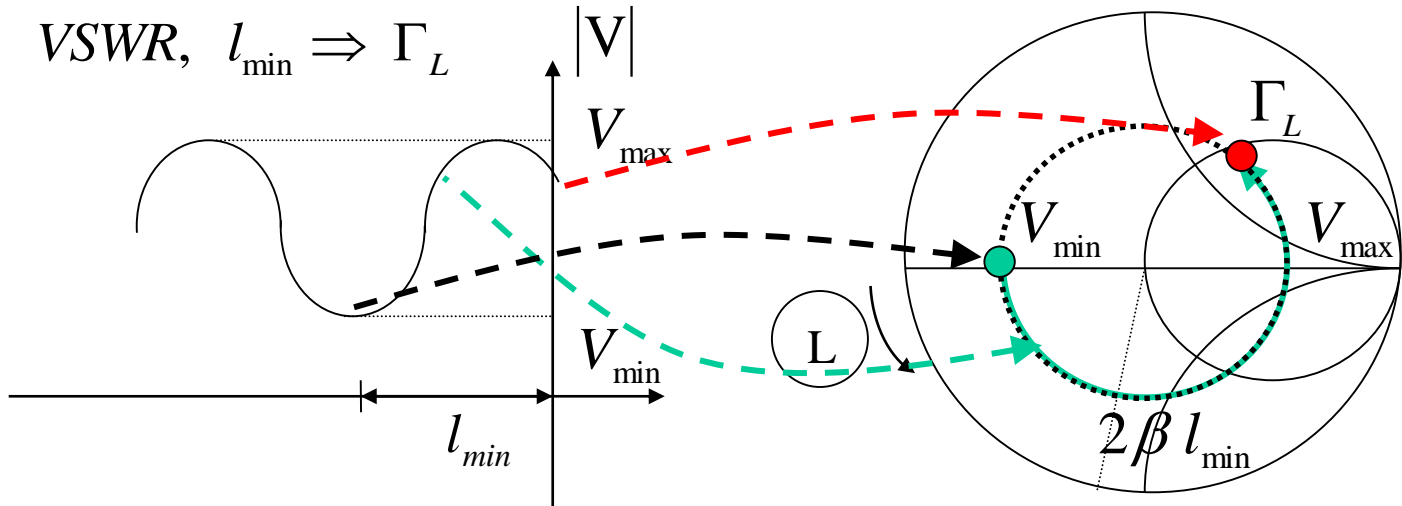
$$6. VSWR, l_{\min} \Rightarrow \Gamma_L$$




$$VSWR = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} \rightarrow |\Gamma_L| = \frac{VSWR-1}{VSWR+1}$$

$$180^\circ + 2\beta l_{\min} = \angle \Gamma_L$$

微波电路讲义

7. Ex. 2.4 $VSWR=1.5$, find Γ_L

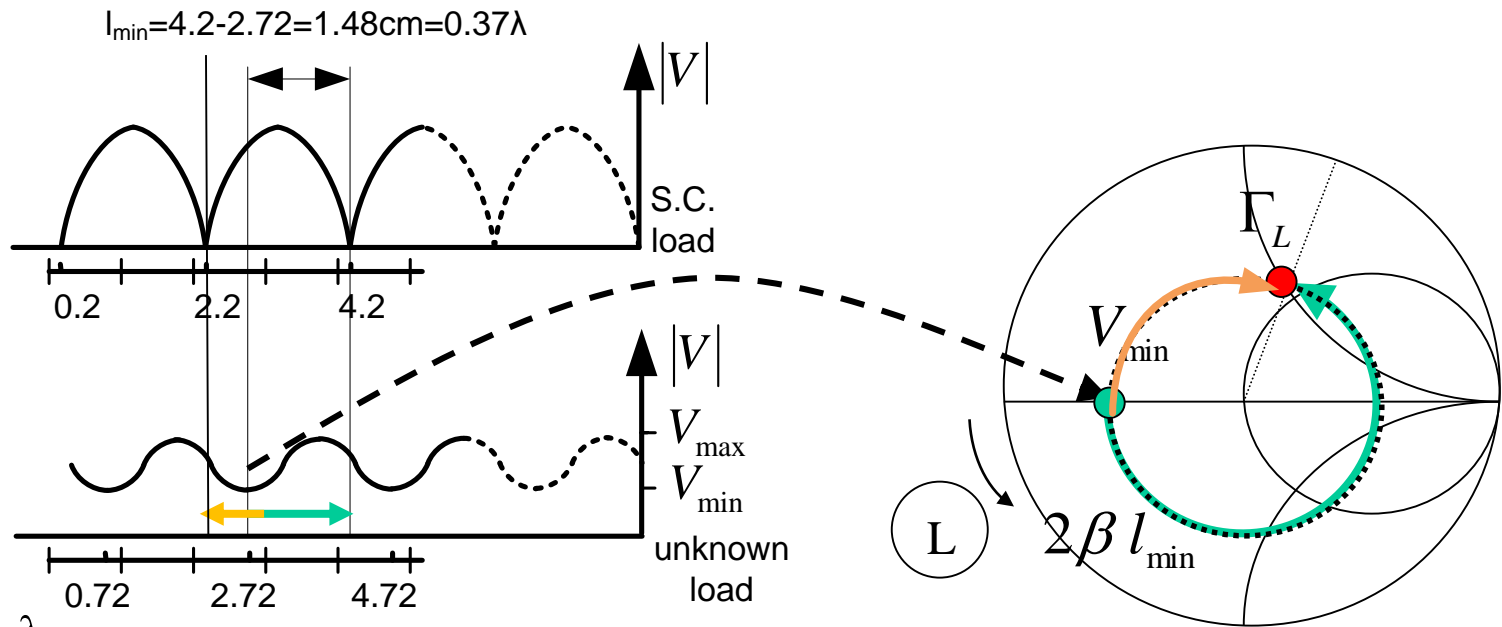



$$\frac{\lambda}{2} = 2 \text{ cm} \rightarrow \lambda = 4 \text{ cm}$$

$$VSWR = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \rightarrow |\Gamma_L| = \frac{VSWR - 1}{VSWR + 1} = \frac{1.5 - 1}{1.5 + 1} = 0.2$$

$$\angle \Gamma_L = 180^\circ + 2\beta l_{\min} = 180^\circ + 2 \frac{2 \times 180^\circ}{4} \times 1.48 - 360^\circ$$

$$= 180^\circ + 266.4^\circ - 360^\circ = 86.4^\circ$$

2.5 The quarter-wave transformer

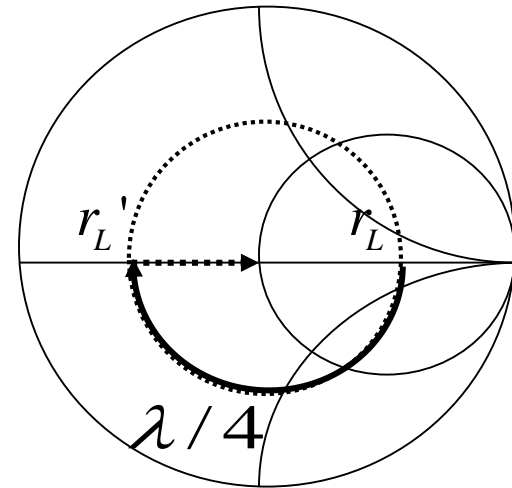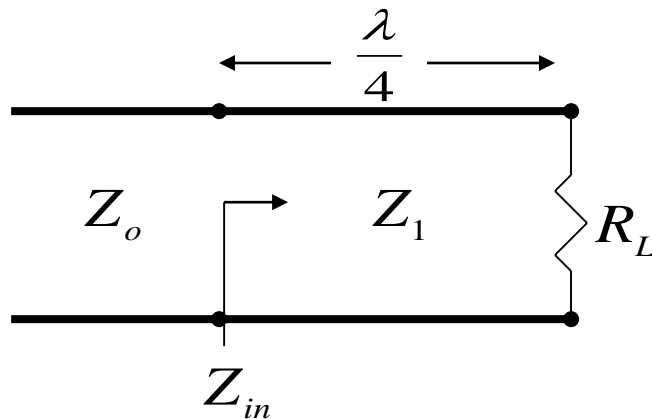

matched condition: $Z_{in}(f_o) = \frac{Z_1^2}{R_L} = Z_o$


$$r_L = \frac{R_L}{Z_1} \rightarrow r_L' = r_L^{-1} \rightarrow R_L' = r_L' Z_1$$

$$\rightarrow \frac{R_L'}{Z_o} = \frac{r_L' Z_1}{Z_o} = \frac{Z_1}{Z_o r_L} = \frac{Z_1^2}{Z_o R_L} = 1$$

Discussion

1. Ex.2.5, frequency response (p.73, Fig.2.17)
2. Analysis from multiple-reflection viewpoint (slide 2-28)

2.6 Generator and load mismatches

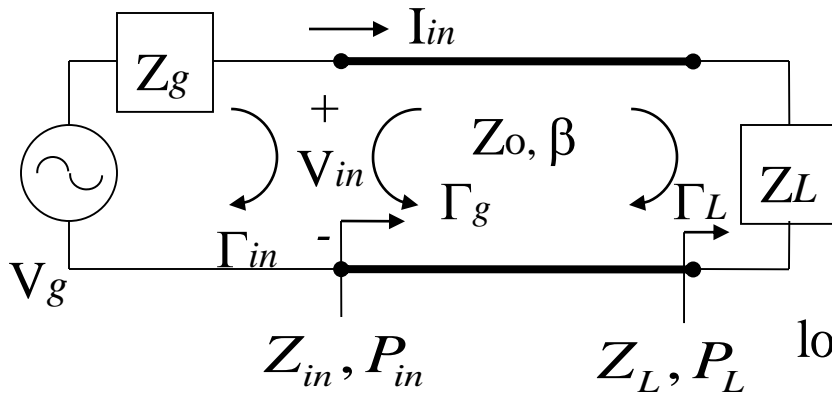

$$P_{in} = \frac{1}{2} \text{Re}(V_{in} I_{in}^*)$$

$$= \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2}$$

lossless line \rightarrow power delivered to the load

$$P_L = P_{in}$$

Discussion

1. Impedance match

load matched to the line $Z_L = Z_o$ ($\Gamma_L = 0$) $\Rightarrow Z_{in} = Z_o$

$$P_{in} = \frac{1}{2} |V_g|^2 \frac{Z_o}{(Z_o + R_g)^2 + X_g^2}$$

source matched to the loaded line $Z_g = Z_{in}$ ($\Gamma_{in} = 0$)

$$P_{in} = \frac{1}{2} |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)}$$

(derivation)

time – average input power

$$\begin{aligned} P_{in} &= \frac{1}{2} \operatorname{Re}(V_{in} I_{in}^*) = \frac{1}{2} \operatorname{Re}\left(V_{in} \frac{V_{in}^*}{Z_{in}^*}\right) = \frac{1}{2} |V_{in}|^2 \operatorname{Re}\left(\frac{1}{Z_{in}^*}\right) \\ &= \frac{1}{2} |V_g|^2 \frac{|Z_{in}|^2}{|Z_{in} + Z_g|^2} \operatorname{Re}\left(\frac{Z_{in}}{|Z_{in}|^2}\right) = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \end{aligned}$$

load matched to the line ($Z_L = Z_o$)

$$Z_{in} = Z_o, P_{in} = \frac{1}{2} |V_g|^2 \frac{R_{in}}{(Z_o + R_g)^2 + X_g^2}$$

source matched to the loaded line ($Z_g = Z_{in}$)

$$P_{in} = \frac{1}{2} |V_g|^2 \frac{R_g}{(R_g + R_g)^2 + (X_g + X_g)^2} = \frac{1}{2} |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)}$$

2. Conjugate match


(given a fixed Z_g)

$$Z_{in} = Z_g^* (\Gamma_g \neq 0, \Gamma_{in} \neq 0) \Rightarrow \text{maximum power transfer from source}$$


$$\left(\frac{\partial P_{in}}{\partial R_{in}} = 0, \quad \frac{\partial P_{in}}{\partial X_{in}} = 0 \right)$$

$$P_{in,max} = \frac{1}{2} |V_g|^2 \frac{1}{4R_g} \quad (12.9)$$

$$\equiv P_{avs} (P_{inc}) = P_{in} |_{Z_{in}=Z_g^*} : \text{maximum available power from source}$$

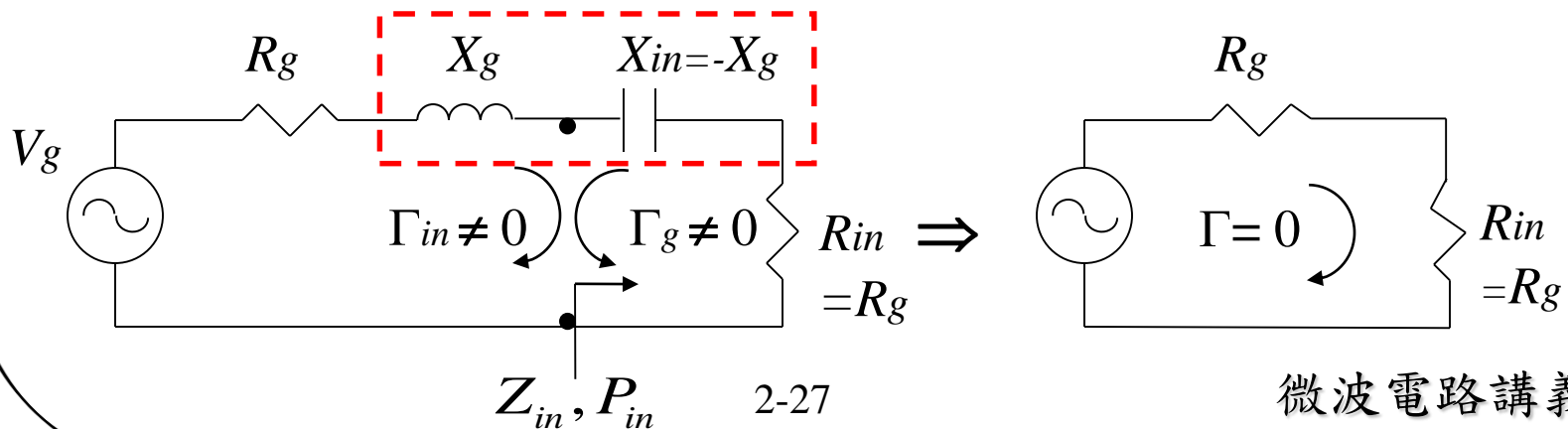

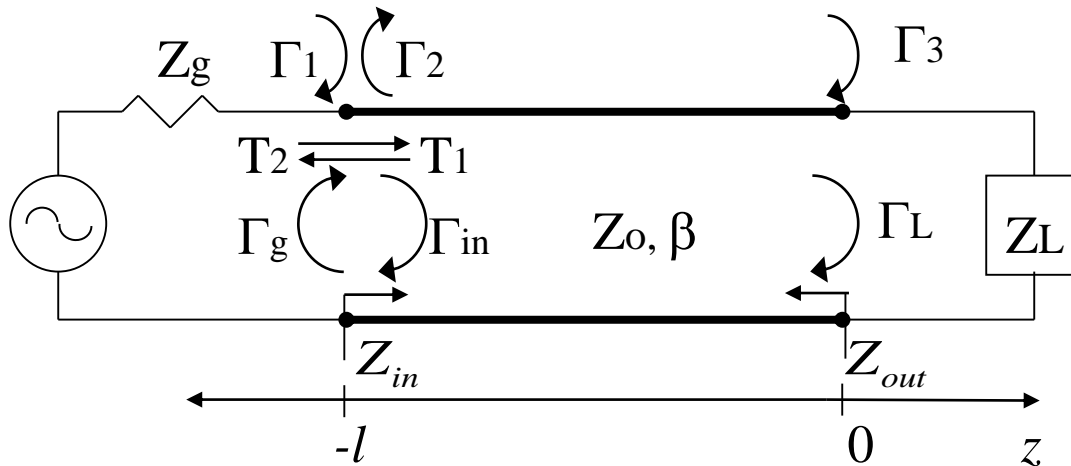3. Reflection coefficient (from multiple-reflection viewpoint)



$$\Gamma_1 = \frac{Z_o - Z_g}{Z_o + Z_g}$$

$$T_1 = 1 + \Gamma_1$$

$$\Gamma_2 = \frac{Z_g - Z_0}{Z_g + Z_0} = -\Gamma_1$$

$$T_2 = 1 + \Gamma_2$$

$$\Gamma_3 = \frac{Z_L - Z_0}{Z_L + Z_0} \neq \Gamma_L$$

$$\Gamma_{in} = \Gamma_1 + \underline{T_1 e^{-j2\beta l} \Gamma_3 T_2} + \underline{T_1 e^{-j2\beta l} \Gamma_3 \Gamma_2 e^{-j2\beta l} \Gamma_3 T_2} + \underline{T_1 e^{-j2\beta l} \Gamma_3 \Gamma_2 e^{-j2\beta l} \Gamma_3 \Gamma_2 e^{-j2\beta l} \Gamma_3 T_2} + \dots$$

$$= \Gamma_1 + T_1 e^{-j2\beta l} \Gamma_3 T_2 \sum (e^{-j2\beta l} \Gamma_2 \Gamma_3)^n = \Gamma_1 + \frac{T_1 \Gamma_3 T_2 e^{-j2\beta l}}{1 - \Gamma_2 \Gamma_3 e^{-j2\beta l}}$$

$$= \Gamma_1 + \frac{(1 + \Gamma_1) \Gamma_3 (1 - \Gamma_1) e^{-j2\beta l}}{1 + \Gamma_1 \Gamma_3 e^{-j2\beta l}} = \frac{\Gamma_1 + \Gamma_3 e^{-j2\beta l}}{1 + \Gamma_1 \Gamma_3 e^{-j2\beta l}}$$

$$\begin{aligned}
\underline{\Gamma_{in}} &= \frac{\Gamma_1 + \Gamma_3 e^{-j2\beta l}}{1 + \Gamma_1 \Gamma_3 e^{-j2\beta l}} = \frac{\frac{Z_o - Z_g}{Z_o + Z_g} + \frac{Z_L - Z_o}{Z_L + Z_o} e^{-j2\beta l}}{1 + \frac{Z_o - Z_g}{Z_o + Z_g} \frac{Z_L - Z_o}{Z_L + Z_o} e^{-j2\beta l}} \\
&= \frac{(Z_o - Z_g)(Z_L + Z_o)e^{j\beta l} + (Z_o + Z_g)(Z_L - Z_o)e^{-j\beta l}}{(Z_o + Z_g)(Z_L + Z_o)e^{j\beta l} + (Z_o - Z_g)(Z_L - Z_o)e^{-j\beta l}} \\
&= \frac{Z_o Z_L \cos \beta l + Z_o^2 j \sin \beta l - Z_g Z_L j \sin \beta l - Z_g Z_o \cos \beta l}{Z_o Z_L \cos \beta l + Z_o^2 j \sin \beta l + Z_g Z_L j \sin \beta l + Z_g Z_o \cos \beta l} \times \frac{1 / \cos \beta l}{1 / \cos \beta l} \\
&= \frac{Z_o(Z_L + jZ_o \tan \beta l) - Z_g(Z_o + jZ_L \tan \beta l)}{Z_o(Z_L + jZ_o \tan \beta l) + Z_g(Z_o + jZ_L \tan \beta l)} \\
&= \frac{Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} - Z_g}{Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} + Z_g} = \frac{Z_{in} - Z_g}{Z_{in} + Z_g}, Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \\
\underline{\Gamma_L} &= \frac{Z_L - Z_{out}}{Z_L + Z_{out}}, Z_{out} = Z_o \frac{Z_g + jZ_o \tan \beta l}{Z_o + jZ_g \tan \beta l}
\end{aligned}$$

4. Impedance match (source is matched to the loaded line)

$Z_{in}(z) = Z_g(z)$: no reflected wave, $\Gamma_{in}(z) = 0$, VSWR = 1, RL = ∞ dB

2.7 Lossy transmission lines

- low-loss line, $R \ll \omega L$, $G \ll \omega C$

$$\alpha \approx \frac{1}{2} \left(\frac{R}{Z_o} + GZ_o \right), \beta \approx \omega \sqrt{LC}, Z_o \approx \sqrt{\frac{L}{C}}$$

- distortionless line $RC = LG$

$$\alpha = R \sqrt{\frac{C}{L}} : \text{constant}, \beta = \omega \sqrt{LC} \rightarrow v_p = \frac{1}{\sqrt{LC}} : \text{constant}, \Delta t = \frac{\Delta l}{v_p} : \text{constant}$$

$$Z_o = \sqrt{\frac{L}{C}}$$

- perturbation method

low-loss line (assume $\Gamma(z) = 0$)

$$P(z) = P_o e^{-2\alpha z} \rightarrow \text{power loss per unit length: } P_l \equiv -\frac{\partial P}{\partial z} = 2\alpha P(z)$$

$$\Rightarrow \alpha = \frac{P_l(z)}{2P(z)} = \frac{P_l(z=0)}{2P_o}$$

Discussion

1. $\alpha = \alpha_c + \alpha_d$ (Ex. 2.6, 2.7 for a coaxial line, p.721 Appendix J)

a coaxial line

$$\alpha = \frac{1}{2} \left(R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right) = \frac{R_s}{2\eta \ln \frac{b}{a}} \left(\frac{1}{a} + \frac{1}{b} \right) + \frac{\omega \epsilon'' \eta}{2} = \alpha_c + \alpha_d$$


2. Wheeler incremental inductance rule

$\alpha_c \rightarrow$ conductor loss \rightarrow current flow inside conductor
 $\rightarrow \Delta H$ in the conductor $\rightarrow \Delta L \rightarrow \Delta Z_o$

$$\alpha_c = \frac{\omega \Delta L}{2Z_o} = \frac{R_s}{2Z_o \eta} \frac{dZ_o}{dl}$$

Solved Problems

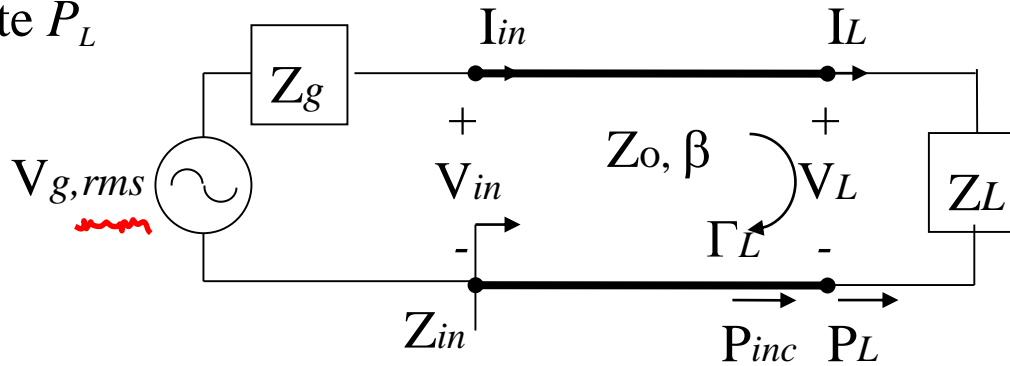Prob. 2.16 $V_{g,rms} = 15V, Z_g = 75\Omega, Z_o = 75\Omega, Z_L = 60 - j40\Omega, l = 0.7\lambda$
 calculate P_L




$$(1) P_L = P_{inc} (1 - |\Gamma_L|^2), P_{inc} = \frac{(V_g / 2)^2}{Z_o}, \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} (\because Z_g = Z_o)$$

$$(2) P_L = |I_{in}|^2 R_{in} = \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 \text{Re}(Z_{in}), Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l}$$

$$(3) P_L = |I_L|^2 R_L = \left| \frac{V_L}{Z_L} \right|^2 \text{Re}(Z_L), V_L = V_0^+ (1 + \Gamma_L), V_0^+ = \frac{V_g}{2} (\because Z_g = Z_o)$$

for a lossy line: $V_{in} = V_0^+ (e^{\gamma l} + \Gamma_L e^{-\gamma l}) = V_g \frac{Z_{in}}{Z_{in} + Z_g}, Z_{in} = Z_o \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \rightarrow V_0^+ \xrightarrow{(3)} V_L \rightarrow P_L$

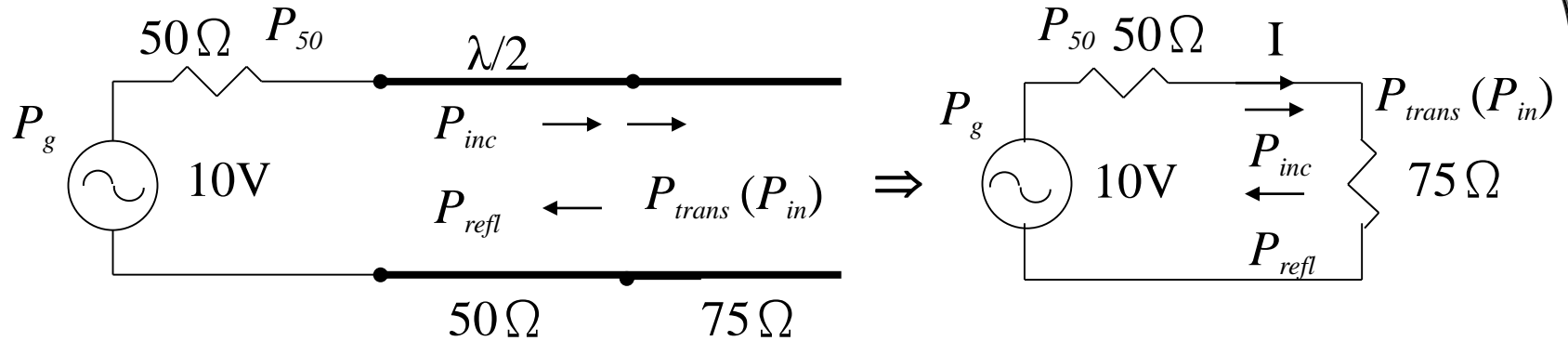Prob. 2.18 Calculate P_{inc} , P_{refl} , P_{trans}



$$P_g = \frac{1}{2} \frac{10}{50 + 75} 10 = 0.4W, P_{inc} = \frac{1}{2} \left(\frac{10}{50 + 50} \right)^2 50 = 0.25W$$

$$P_{50\Omega} = \frac{1}{2} \left(\frac{10}{50 + 75} \right)^2 50 = 0.16W, P_{trans} = P_{in} = \frac{1}{2} \left(\frac{10}{50 + 75} \right)^2 75 = 0.24W$$

$$P_{refl} = P_{inc} |\Gamma|^2 = 0.25 \left| \frac{75 - 50}{75 + 50} \right|^2 = 0.01W$$

$$P_{inc} = P_{refl} + P_{trans}, P_g = P_{50\Omega} + P_{trans} (P_{in}) = P_{50\Omega} + P_{inc} - P_{refl} \Rightarrow P_g > P_{inc} \geq P_{in}$$

For conjugate match: $Z_{in} = Z_g^*$, ($R_{in} = R_g$, impedance match)

$$P_{avs} = P_{in}|_{Z_{in}=Z_g^*} = 0.25W (> 0.24W) \rightarrow P_{50\Omega} = 0.25W, P_g = 0.5W, P_{refl} = 0W$$


Prob. 2.27 Find b/a and Z_o for a coaxial line to have minimal α_c

$$\alpha_c = \frac{R_s}{2\eta \ln b/a} \left(\frac{1}{a} + \frac{1}{b} \right)$$

$$\frac{\partial \alpha_c}{\partial a} = \frac{R_s}{2\eta} \left[\frac{1}{a} \left(\frac{1}{\ln b/a} \right)^2 \left(\frac{1}{a} + \frac{1}{b} \right) + \frac{1}{\ln b/a} \left(-\frac{1}{a^2} \right) \right] = 0$$

$$a \left(\frac{1}{a} + \frac{1}{b} \right) = \ln \frac{b}{a}, 1 + \frac{b}{a} = \frac{b}{a} \ln \frac{b}{a} \rightarrow \frac{b}{a} = 3.59$$
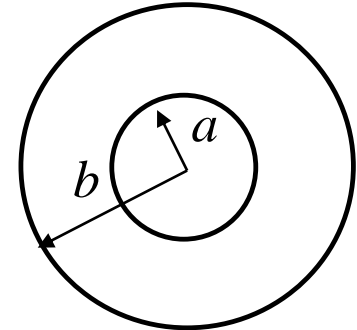
$$Z_o = \frac{\eta}{2\pi} \ln \frac{b}{a} \approx 77\Omega, \text{ for } \epsilon_r = 1$$



ADS examples: Ch2_prj