

Chapter 4 Microwave network analysis

- 4.1 Impedance and equivalent voltages and currents
equivalent transmission line model (β , Z_0)
- 4.2 Impedance and admittance matrices
not applicable in microwave circuits
- 4.3 The scattering matrix
properties, generalized scattering parameters, VNA measurement
- 4.4 The transmission (ABCD) matrix
cascade network
- 4.5 Signal flow graph
2-port circuit, TRL calibration
- 4.6 Discontinuities and modal analysis
microstrip discontinuities and compensation

4.1 Impedance and equivalent voltages and currents

- Equivalent voltages and currents

Microwave circuit approach

Interest: voltage and current at a set of terminals (ports), power flow through a device, and how to find the response of a network

For a certain mode in the line, the line characteristics are represented by its global quantities Z_0 , β , l .

Define: equivalent voltage (wave) \propto transverse electric field

equivalent current (wave) \propto transverse magnetic field

\Rightarrow voltage (wave)/current (wave) = characteristic impedance or wave impedance of the line

and voltage \times current = power flow of the mode

\rightarrow use transmission line theory to analyze microwave circuit performance at the interested ports

- Impedance

characteristic impedance of the medium $\eta = \sqrt{\frac{\mu}{\epsilon}}$


wave impedance of the particular mode of wave $Z_w = \frac{E_t^+}{H_t^+}$

characteristic impedance of the line $Z_o = \frac{V^+}{I^+}$

input impedance at a port of circuit $Z_{in}(z) = \frac{V(z)}{I(z)}$

Discussion

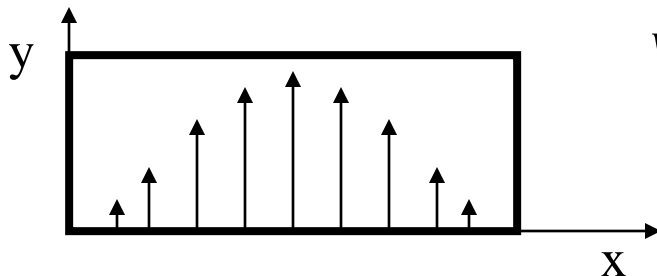1. Transmission line model for the TE₁₀ mode of a rectangular waveguide



transverse fields (Table 3.2, p.117)

$$V(x, z) \equiv \int \bar{E} \cdot d\bar{l} = \int E_y dy$$

: x - dependent , non - unique value

transmission line model

$$E_y = (A^+ e^{-j\beta z} + A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_1 V \sin \frac{\pi x}{a}$$

$$H_x = -\frac{1}{Z_{TE_{10}}} (A^+ e^{-j\beta z} - A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_2 I \sin \frac{\pi x}{a}$$

$$Z_{TE_{10}} = -\frac{E_y^+}{H_x^+} = \frac{k\eta}{\beta} \equiv Z_o$$

$$P^+ = -\frac{1}{2} \int E_y^+ H_x^{+*} dx dy$$

$$V = V_{o^+} e^{-j\beta z} + V_{o^-} e^{j\beta z}$$

$$I = I_{o^+} e^{-j\beta z} - I_{o^-} e^{j\beta z}$$

$$= \frac{V_{o^+}}{Z_o} e^{-j\beta z} - \frac{V_{o^-}}{Z_o} e^{j\beta z}$$

$$Z_o = \frac{V_{o^+}}{I_{o^+}} = \frac{V_{o^-}}{I_{o^-}}$$

$$P^+ = \frac{1}{2} V_{o^+} I_{o^+}^*$$

(derivation of C_1 and C_2)

$$E_y = (A^+ e^{-j\beta z} + A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_1 (V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z}) \sin \frac{\pi x}{a}$$

$$\rightarrow V_o^+ = \frac{A^+}{C_1}, V_o^- = \frac{A^-}{C_1}$$

$$H_x = -\frac{1}{Z_{TE_{10}}} (A^+ e^{-j\beta z} - A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_2 (I_o^+ e^{-j\beta z} - I_o^- e^{j\beta z}) \sin \frac{\pi x}{a}$$

$$\rightarrow I_o^+ = -\frac{A^+}{C_2 Z_{TE_{10}}}, I_o^- = -\frac{A^-}{C_2 Z_{TE_{10}}}$$


$$P^+ = -\frac{1}{2} \int_0^a \int_0^b E_y^+ H_x^{+*} dx dy = \frac{ab}{4Z_{TE_{10}}} |A^+|^2 \equiv \frac{1}{2} V_o^+ I_o^{+*} = -\frac{|A^+|^2}{2C_1 C_2^* Z_{TE_{10}}} \rightarrow C_1 C_2^* = -\frac{2}{ab}$$

$$Z_{TE_{10}} \equiv Z_o = \frac{V_o^+}{I_o^+} = -\frac{A^+ C_2 Z_{TE_{10}}}{C_1 A^+} \rightarrow \frac{C_2}{C_1} = -1$$

$$\Rightarrow C_1 = \sqrt{\frac{2}{ab}}, C_2 = -\sqrt{\frac{2}{ab}}$$

2. Ex.4.2

incident
wave

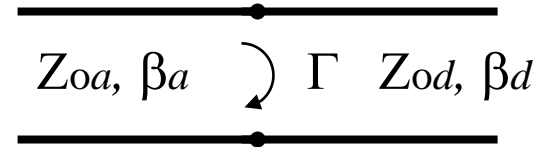

$$\Gamma = \frac{Z_{od} - Z_{oa}}{Z_{od} + Z_{oa}}$$

$$Z_{oa} = \frac{k_o \eta_o}{\beta_a}, Z_{od} = \frac{k \eta}{\beta_d}, k_o \eta_o = k \eta, k = \sqrt{\epsilon_r} k_o$$

$$\beta_a^2 + k_c^2 = k_o^2, \beta_d^2 + k_c^2 = k^2, k_c = \frac{\pi}{a} = \frac{2\pi}{\lambda_c} = \frac{2\pi f_c}{v_p} = \frac{2\pi f_c}{c/\sqrt{\epsilon_r}}$$

$$X \text{ - band: } a = 2.286 \text{ cm} \rightarrow \lambda_c = 2a = 4.472 \text{ cm} \rightarrow k_c = 137 \text{ m}^{-1} \rightarrow f_{c,a} = 6.56 \text{ GHz}, f_{c,\epsilon_r} = 4.17 \text{ GHz}$$

$$\text{if } f = 10 \text{ GHz} \rightarrow k_o = 2\pi f / c = 209 \text{ m}^{-1}, \beta_a = 158 \text{ m}^{-1}, \epsilon_r = 2.54 \rightarrow k = 333 \text{ m}^{-1}, \beta_d = 304 \text{ m}^{-1}$$


$$Z_{oa} = 500 \Omega, Z_{od} = 259.6 \Omega, \Gamma = -0.316$$

$$\text{if } f = 6 \text{ GHz} \rightarrow k = \sqrt{\epsilon_r} k_o = 201 \text{ m}^{-1} > k_c \text{ in } \epsilon_r, \beta_d = 147 \text{ m}^{-1},$$

$$k_o = 126 \text{ m}^{-1} < k_c \text{ in air}, \beta_a = j54 \text{ m}^{-1}, TE_{10} \text{ "non-exist"}$$

Q: What if the incident wave is from the other direction? **“N”**

4.2 Impedance and admittance matrices

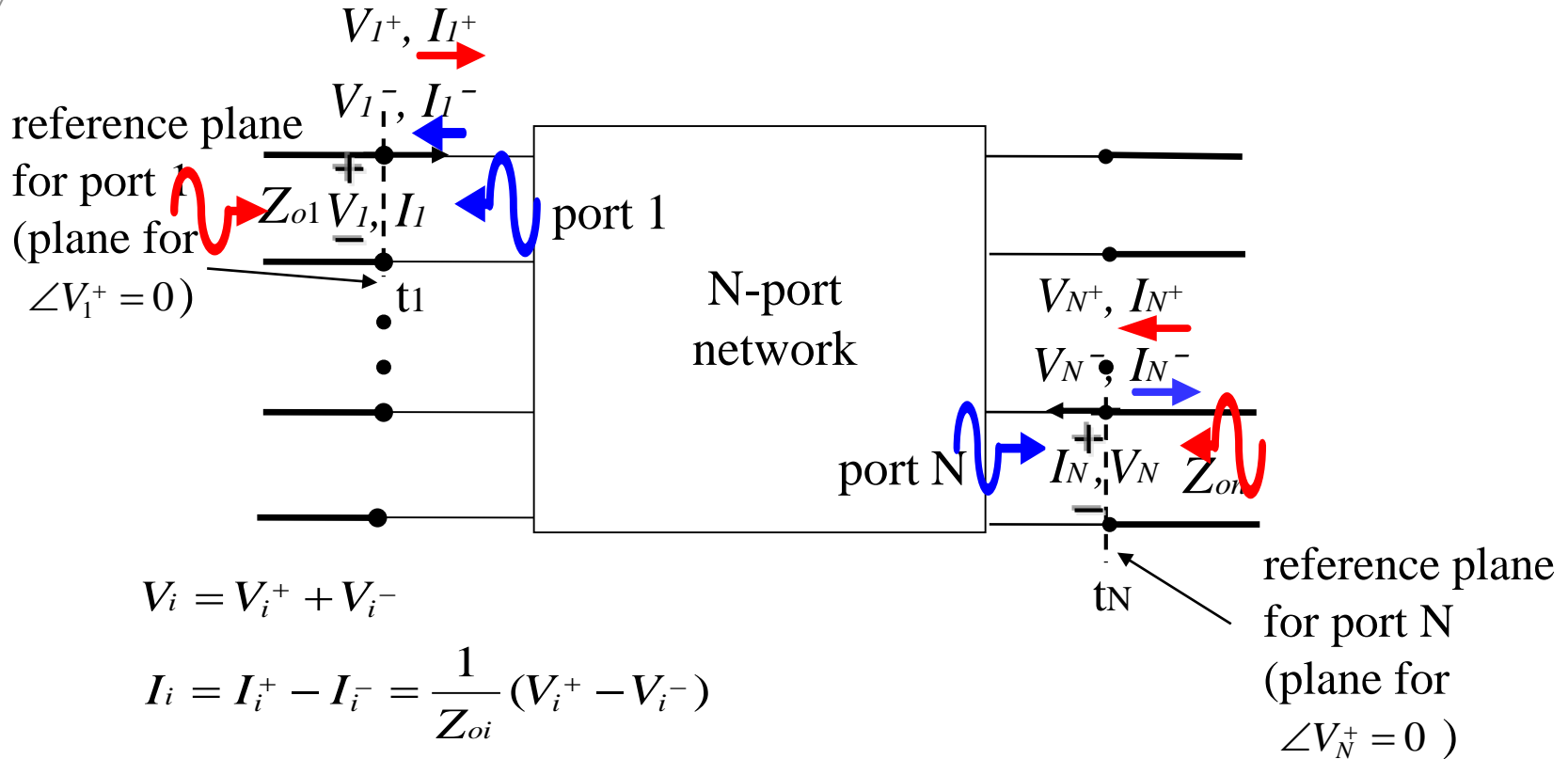

$$V_i = V_i^+ + V_i^-$$

$$I_i = I_i^+ - I_i^- = \frac{1}{Z_{oi}} (V_i^+ - V_i^-)$$

$$Z_{oi} = \frac{V_i^+}{I_i^+} = \frac{V_i^-}{I_i^-}$$

$$P_{inc,i} = \frac{1}{2} \text{Re}\{V_i^+ I_i^{+*}\}, P_{in,i} = \frac{1}{2} \text{Re}\{V_i I_i^*\}$$

- Impedance matrix

$$[V] = [Z] [I], \quad \begin{bmatrix} V_1 \\ V_2 \\ \bullet \\ \bullet \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \bullet & \bullet & Z_{1N} \\ Z_{21} & \bullet & \bullet & \bullet & Z_{2N} \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ Z_{N1} & Z_{N2} & \bullet & \bullet & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \bullet \\ \bullet \\ I_N \end{bmatrix}, \quad Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0, k \neq j} = \left. \frac{\text{response}_i}{\text{source}_j} \right|_{I_k=0, k \neq j}$$

- Admittance matrix

$$[I] = [Y] [V], \quad \begin{bmatrix} I_1 \\ I_2 \\ \bullet \\ \bullet \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \bullet & \bullet & Y_{1N} \\ Y_{21} & \bullet & \bullet & \bullet & Y_{2N} \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ Y_{N1} & Y_{N2} & \bullet & \bullet & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \bullet \\ \bullet \\ V_N \end{bmatrix}, \quad Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0, k \neq j} = \left. \frac{\text{response}_i}{\text{source}_j} \right|_{V_k=0, k \neq j}$$

Discussion

1. Reciprocal network

$$[Z] = [Z]^t, \quad Z_{ij} = Z_{ji}, \quad [Z] \text{ and } [Y] : \text{symmetric matrix}$$

$$[Y] = [Y]^t, \quad Y_{ij} = Y_{ji}$$

(derivation)

| | | | | | |
|--|--------|-------------------|------------------|--|------------------|
| | source | | port 1 | | port 2 |
| | a | \longrightarrow | V_{1a}, I_{1a} | | V_{2a}, I_{2a} |
| | b | \longrightarrow | V_{1b}, I_{1b} | | V_{2b}, I_{2b} |

reciprocity theorem: $V_{1a}I_{1b} + V_{2a}I_{2b} = V_{1b}I_{1a} + V_{2b}I_{2a}$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$(\cancel{Z_{11}I_{1a}} + Z_{12}I_{2a})I_{1b} + (Z_{21}I_{1a} + \cancel{Z_{22}I_{2a}})I_{2b} = (\cancel{Z_{11}I_{1b}} + Z_{12}I_{2b})I_{1a} + (Z_{21}I_{1b} + \cancel{Z_{22}I_{2b}})I_{2a}$$

$$Z_{12}I_{2a}I_{1b} + Z_{21}I_{1a}I_{2b} = Z_{12}I_{2b}I_{1a} + Z_{21}I_{1b}I_{2a}$$

$$(Z_{12} - Z_{21})(I_{2a}I_{1b} - I_{2b}I_{1a}) = 0 \Rightarrow Z_{12} = Z_{21}$$

2. T and Π networks

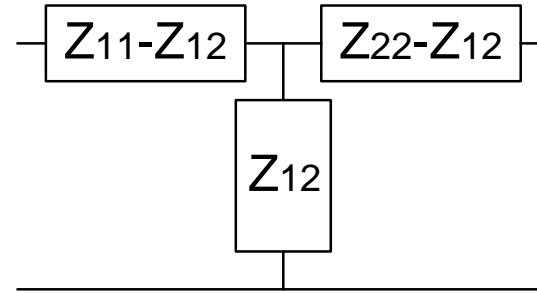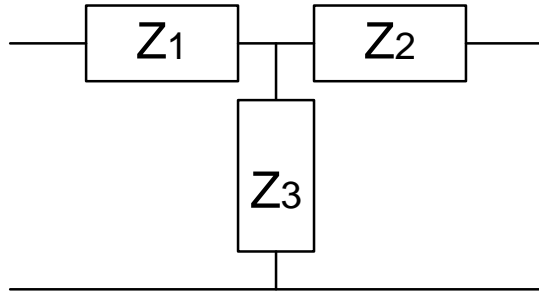



(derivation)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 + Z_3, Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_3 = Z_{12}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_2 + Z_3$$
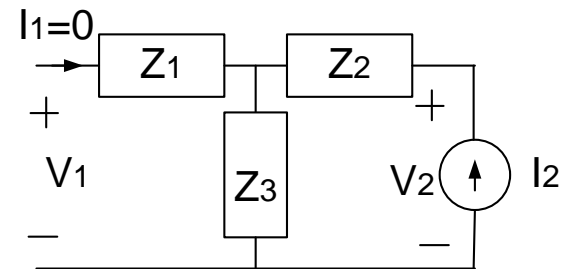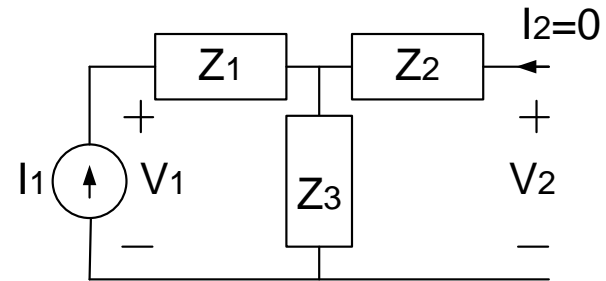
$$\rightarrow Z_3 = Z_{12}, Z_1 = Z_{11} - Z_{12}, Z_2 = Z_{22} - Z_{12}$$



微波電路講義

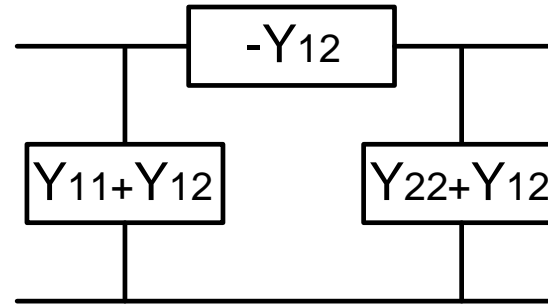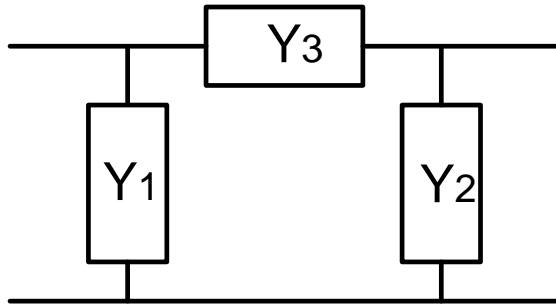



(derivation)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_1 + Y_3, Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -Y_3 = Y_{12}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_2 + Y_3$$
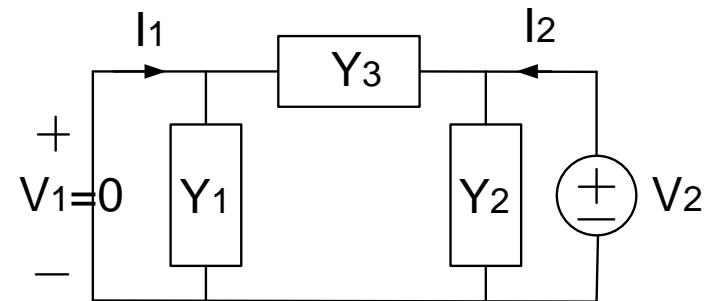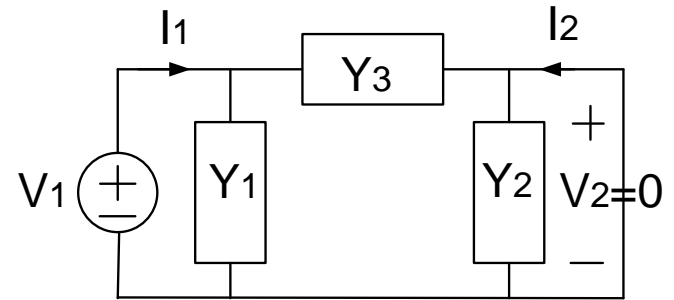
$$\rightarrow Y_1 = Y_{11} + Y_{12}, Y_3 = -Y_{12}, Y_2 = Y_{22} + Y_{12}$$



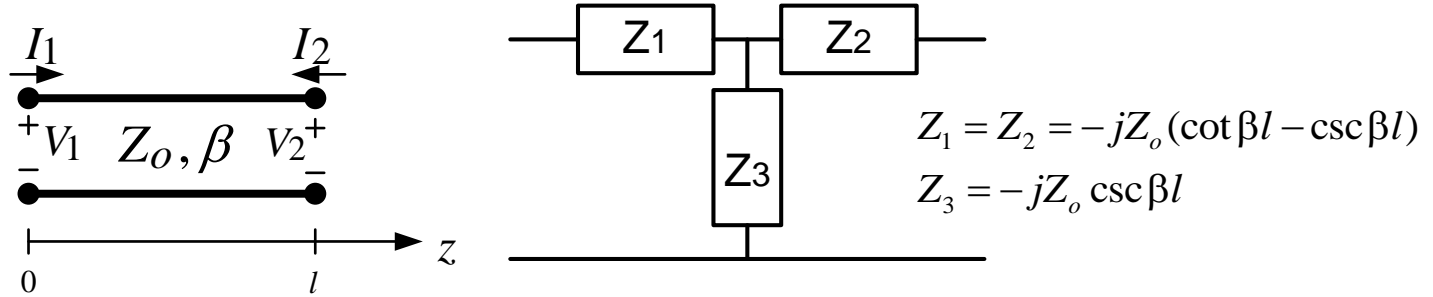3. Z- and Y- matrices of a lossless transmission line section



(derivation)

$$V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z}, I(z) = Y_o(V_o^+ e^{-j\beta z} - V_o^- e^{j\beta z}), \text{B.C. } V_1 = V(0), I_1 = I(0), V_2 = V(l), I_2 = -I(l)$$

$$V_1 = V_o^+ + V_o^-, I_1 = Y_o(V_o^+ - V_o^-) \rightarrow V_o^\pm = \frac{1}{2}(V_1 \pm Z_o I_1)$$

$$V_2 = V_o^+ e^{-j\beta l} + V_o^- e^{j\beta l} = \frac{1}{2}(V_1 + Z_o I_1)e^{-j\beta l} + \frac{1}{2}(V_1 - Z_o I_1)e^{j\beta l} = V_1 \cos \beta l - jZ_o I_1 \sin \beta l \dots (1)$$

$$I_2 = -Y_o(V_o^+ e^{-j\beta l} - V_o^- e^{j\beta l}) = -Y_o \left[\frac{1}{2}(V_1 + Z_o I_1)e^{-j\beta l} - \frac{1}{2}(V_1 - Z_o I_1)e^{j\beta l} \right] = jY_o V_1 \sin \beta l - I_1 \cos \beta l \dots (2)$$

$$(2) \rightarrow V_1 = -jZ_o I_1 \cot \beta l - jZ_o I_2 \csc \beta l \dots (3)$$

$$(1) \rightarrow V_2 = -jZ_o I_1 \cos \beta l \cot \beta l - jZ_o I_2 \cot \beta l - jZ_o I_1 \sin \beta l \Rightarrow [Z] = -jZ_o \begin{bmatrix} \cot \beta l & \csc \beta l \\ \csc \beta l & \cot \beta l \end{bmatrix}$$

$$= -jZ_o I_1 \csc \beta l - jZ_o I_2 \cot \beta l$$


$$Z_1 = Z_{11} - Z_{12} = -jZ_o(\cot \beta l - \csc \beta l) = Z_2, Z_3 = Z_{12} = -jZ_o \csc \beta l$$

$$(1) V_2 = V_1 \cos \beta l - jZ_o I_1 \sin \beta l \rightarrow I_1 = -jY_o \cot \beta l V_1 + jY_o \csc \beta l V_2 \dots (3)$$

$$\begin{aligned} \xrightarrow{(3)} (2) I_2 &= jY_o V_1 \sin \beta l - I_1 \cos \beta l = jY_o V_1 \sin \beta l - (-jY_o \cot \beta l V_1 + jY_o \csc \beta l V_2) \cos \beta l \\ &= jY_o \csc \beta l V_1 - jY_o \cot \beta l V_2 \end{aligned}$$

$$[Y] = -jY_o \begin{bmatrix} \cot \beta l & -\csc \beta l \\ -\csc \beta l & \cot \beta l \end{bmatrix}$$
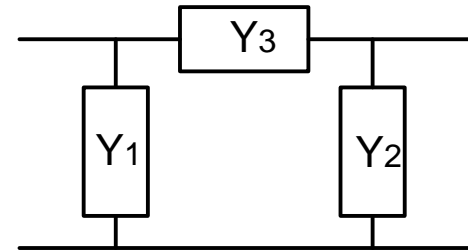
$$\rightarrow Y_1 = Y_{11} + Y_{12} = -jY_o (\cot \beta l - \csc \beta l) = Y_2, Y_3 = jY_o \csc \beta l$$



$$Y_1 = Y_2 = -jY_o (\cot \beta l - \csc \beta l)$$

$$Y_3 = jY_o \csc \beta l$$


4. Reciprocal lossless network

$$\text{Re}\{Z_{ij}\} = 0$$

5. Problems to use Z- or Y-matrix in microwave circuits

- 1) difficult in defining voltage and current for non-TEM lines
- 2) no equipment available to measure voltage and current in complex value (eg. sampling scope in microwave range, impedance meter <3GHz)
- 3) difficult to make open and short circuits over broadband
- 4) active devices not stable as terminated with open or short circuit


4.3 The scattering matrix

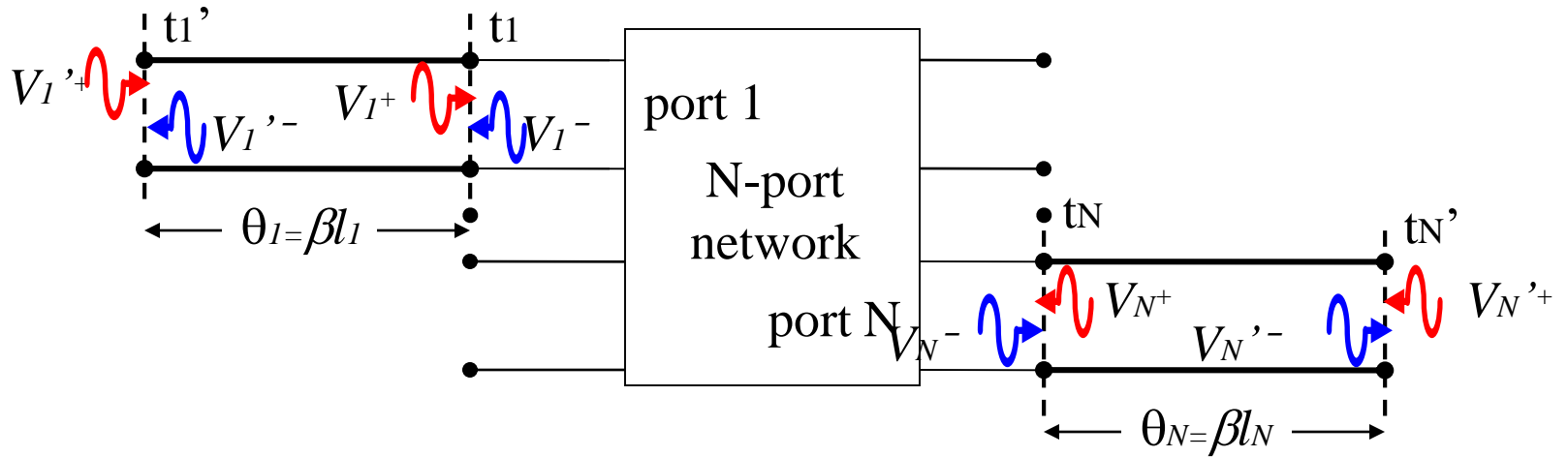

$$[V^-] = [S] [V^+], \quad \begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & \cdots & S_{1N} \\ S_{21} & \cdots & \cdots & \cdots & S_{2N} \\ \vdots & \vdots & \vdots & \vdots & \vdots \\ S_{N1} & S_{N2} & \cdots & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}, \quad S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0, k \neq j} = \frac{\text{response}_i}{\text{source}_j} \Big|_{V_k^+ = 0, k \neq j}$$

Discussion

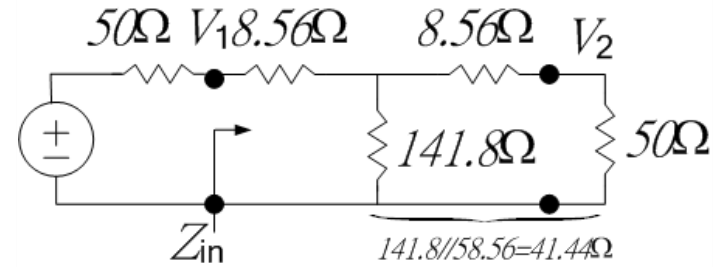1. Ex 4.4 a 3dB attenuator ($Z_o=50\Omega$)



$$Z_{in} = 8.56 + 41.44 = 50$$

$$S_{11} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = 0 \left(= \frac{V_1^-}{V_1^+} \right) \rightarrow V_1^- = 0 \rightarrow V_1 = V_1^+ + V_1^- = V_1^+$$

$$V_2^+ = 0, V_2^- = V_2 = V_1 \frac{41.44}{41.44 + 8.56} \frac{50}{50 + 8.56} = 0.707V_1 = \frac{1}{\sqrt{2}}V_1 = \frac{1}{\sqrt{2}}V_1^+ = S_{21}V_1^+$$

reciprocal $\rightarrow S_{21} = S_{12}$
 symmetric $\rightarrow S_{11} = S_{22}$


$$\rightarrow [S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & 0 \end{bmatrix} : \text{lossy}$$

incident power to port 1: $P_{inc,1} = \frac{1}{2} \frac{|V_1^+|^2}{Z_o}$

transmitted power from port 2: $P_{trans,2} = \frac{1}{2} \frac{|V_2^-|^2}{Z_o} = \frac{1}{2} \frac{\left| \frac{1}{\sqrt{2}} V_1^+ \right|^2}{Z_o} = \frac{1}{2} \times \frac{1}{2} \frac{|V_1^+|^2}{Z_o} : 3\text{dB attenuation}$

attenuator design $\left\{ \begin{array}{l} \text{input match} \\ \text{attenuation value} \end{array} \right. \rightarrow R_1, R_2$

2. T-type attenuator design

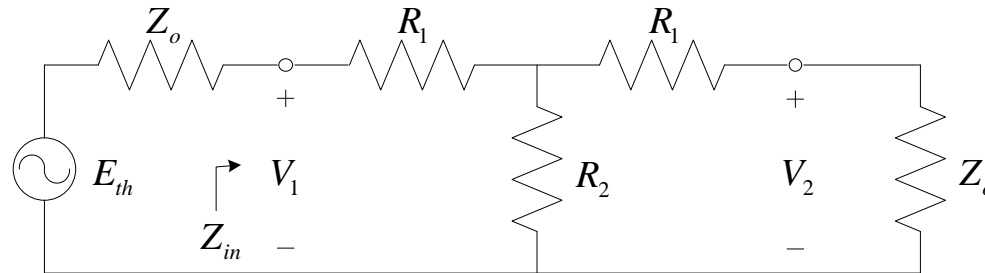

$$\left\{ \begin{array}{l} Z_{in} = (R_1 + Z_o) // R_2 + R_1 = Z_o \\ S_{21} = \frac{V_2}{V_1} = \frac{R_2 // (R_1 + Z_o)}{R_1 + R_2 // (R_1 + Z_o)} \frac{Z_o}{R_1 + Z_o} = \alpha \end{array} \right. \Rightarrow \left\{ \begin{array}{l} R_1 = \frac{1-\alpha}{1+\alpha} Z_o \\ R_2 = \frac{2\alpha}{1-\alpha^2} Z_o \end{array} \right.$$

$$3dB \text{ attenuator } \alpha = \frac{1}{\sqrt{2}} \Rightarrow \left\{ \begin{array}{l} R_1 = \frac{1-\alpha}{1+\alpha} Z_o = \frac{\sqrt{2}-1}{\sqrt{2}+1} Z_o \\ R_2 = \frac{2\alpha}{1-\alpha^2} Z_o = 2\sqrt{2} Z_o \end{array} \right.$$

3. Relation of [Z], [Y], and [S]

$$[S] = ([Z] + [U])^{-1} ([Z] - [U]), \quad [Y] = [Z]^{-1}$$

(derivation)

$$\text{Let } Z_{on} = 1, \quad \begin{aligned} V_n &= V_n^+ + V_n^- \\ I_n &= V_n^+ - V_n^- \end{aligned}$$

$$[V] = [Z][I] \rightarrow [V^+] + [V^-] = [Z]([V^+] - [V^-])$$

$$\rightarrow [Z][V^-] + [V^-] = [Z][V^+] - [V^+]$$

$$([Z] + [U])[V^-] = ([Z] - [U])[V^+]$$

$$\therefore [V^-] = [S][V^+] \rightarrow ([Z] + [U])[S][V^+] = ([Z] - [U])[V^+]$$

$$[S] = ([Z] + [U])^{-1} ([Z] - [U])$$

4. Reciprocal network

$$[S] = [S]^t, \quad [S]: \text{symmetric matrix}$$

(derivation)

$$\text{Let } Z_{on} = 1, \quad \begin{array}{l} V_n = V_n^+ + V_n^- \\ I_n = V_n^+ - V_n^- \end{array} \rightarrow \begin{array}{l} V_n^+ = (V_n + I_n) / 2 \\ V_n^- = (V_n - I_n) / 2 \end{array}$$

$$[V^+] = \frac{1}{2}([V] + [I]) = \frac{1}{2}([Z] + [U])[I]$$

$$[V^-] = \frac{1}{2}([V] - [I]) = \frac{1}{2}([Z] - [U])[I]$$

$$[V^-] = ([Z] - [U])([Z] + [U])^{-1} [V^+] \rightarrow [S] = ([Z] - [U])([Z] + [U])^{-1}$$

$$[S]^t = (([Z] + [U])^{-1})^t ([Z] - [U])^t = ([Z] + [U])^{-1} ([Z] - [U]) \stackrel{\text{from 3}}{=} [S]$$

5. Lossless network (unitary property)

$$[S]^t [S]^* = [U], \quad \sum_{k=1}^N S_{ki} S_{kj}^* = \begin{cases} 1 & i = j \\ 0 & i \neq j \end{cases}$$

(derivation)

Let $Z_{on} = 1$

lossless (incident power = transmitted power) \rightarrow net averaged input power $\sum_i P_{in,i} = 0$

$$\begin{aligned} P_{in} &= \frac{1}{2} \operatorname{Re}([V]^t [I]^*) = \frac{1}{2} \operatorname{Re}([V^+] + [V^-])^t ([V^+]^* - [V^-]^*) \\ &= \frac{1}{2} \operatorname{Re}([V^+]^t [V^+]^* - [V^-]^t [V^-]^* + \underbrace{[V^-]^t [V^+]^* - [V^+]^t [V^-]^*}_{Im}) = 0 \end{aligned}$$

$$[V^+]^t [V^+]^* = [V^-]^t [V^-]^* \stackrel{[V^-] = [S][V^+]}{=} [V^+]^t [S]^t [S]^* [V^+]^*$$

$$\rightarrow [S]^t [S]^* = [U]$$

6. Lossy network $\sum_{k=1}^N S_{ki} S_{ki}^* < 1$

7. Ex.4.5

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

$[S]$: not symmetric \rightarrow a non-reciprocal network

$|S_{11}|^2 + |S_{21}|^2 = 0.745 \neq 1 \rightarrow$ a lossy network

port 1 $RL = -20 \log |S_{11}| = 16.5 dB$

port 2 $RL = -20 \log |S_{22}| = 14 dB$

$IL = -20 \log |S_{21}| = 1.4 dB$


port 2 terminated with a matched load $\Gamma_L = 0 \rightarrow$

$$\Gamma_{in} = |S_{11}| = 0.15, RL = -20 \log 0.15 = 16.5 dB$$

port 2 terminated with a short circuit $\Gamma_L = -1 \rightarrow$

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = -0.452, RL = 6.9 dB$$

8. Shift property

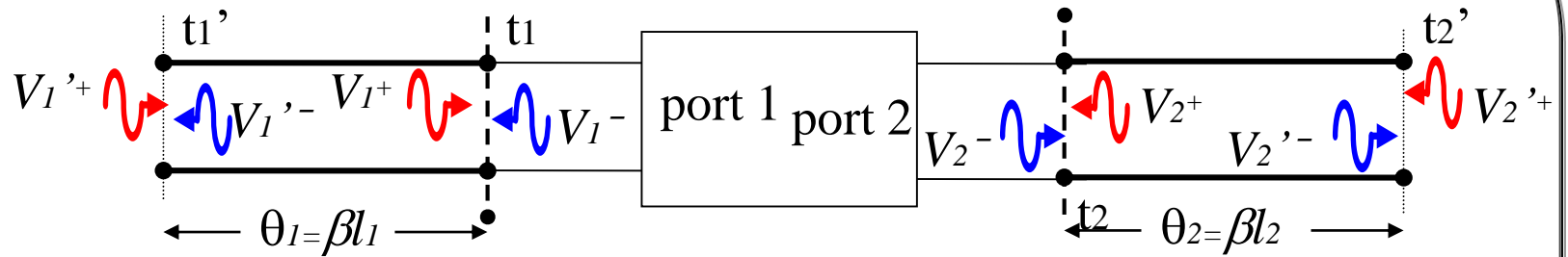

$$S'_{11} = e^{-j2\theta_1} S_{11}, S'_{21} = e^{-j\theta_1} S_{21} e^{-j\theta_2}, S'_{12} = e^{-j\theta_2} S_{12} e^{-j\theta_1}, S'_{22} = e^{-j2\theta_2} S_{22}$$

n-port network: $[S'] = \begin{bmatrix} e^{-j\theta_1} & 0 & \bullet & 0 \\ 0 & e^{-j\theta_2} & \bullet & 0 \\ \bullet & \bullet & \bullet & \bullet \\ 0 & 0 & \bullet & e^{-j\theta_N} \end{bmatrix} [S] \begin{bmatrix} e^{-j\theta_1} & 0 & \bullet & 0 \\ 0 & e^{-j\theta_2} & \bullet & 0 \\ \bullet & \bullet & \bullet & \bullet \\ 0 & 0 & \bullet & e^{-j\theta_N} \end{bmatrix}$


9. S-matrix is not effected by the network arrangement.

10. Power waves on a lossless transmission line with Z_{oi}

incident (power) wave : $a_i \equiv \frac{V_i^+}{\sqrt{Z_{oi}}} = \frac{V_i + Z_{oi}I_i}{2\sqrt{Z_{oi}}}$

reflected (power) wave : $b_i \equiv \frac{V_i^-}{\sqrt{Z_{oi}}} = \frac{V_i - Z_{oi}I_i}{2\sqrt{Z_{oi}}}$

$$[V^-] = [S][V^+] \Rightarrow [b] = [S][a], S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, k \neq j} = \frac{V_i^- \sqrt{Z_{oj}}}{V_j^+ \sqrt{Z_{oi}}} \Big|_{V_k^+=0, k \neq j}$$

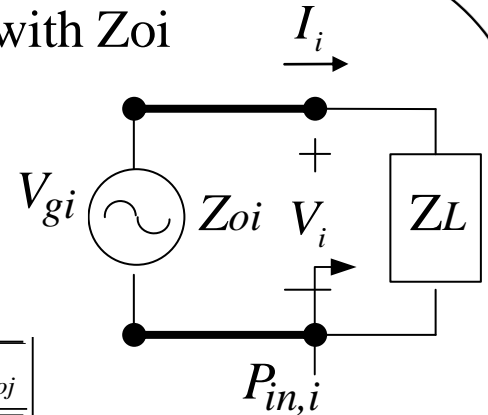

$$P_{in,i} = \frac{1}{2} \text{Re}\{V_i I_i^*\} = \frac{1}{2} |a_i|^2 - \frac{1}{2} |b_i|^2 = P_{inc,i} - P_{refl,i} = P_{inc,i} (1 - |S_{ii}|^2) = P_L$$

(derivation)

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}, b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}, V_i = V_i^+ + V_i^- = \sqrt{Z_{oi}}(a_i + b_i), I_i = \frac{V_i^+ - V_i^-}{Z_{oi}} = \frac{a_i - b_i}{\sqrt{Z_{oi}}}$$

$$P_{in,i} = \frac{1}{2} \text{Re}\{V_i I_i^*\} = \frac{1}{2} \text{Re}\{(a_i + b_i)(a_i - b_i)^*\} = \frac{1}{2} \text{Re}\{|a_i|^2 - |b_i|^2 + \underbrace{a_i^* b_i - a_i b_i^*}_{\text{Im}}\}$$

$$= \frac{1}{2} |a_i|^2 - \frac{1}{2} |b_i|^2 = P_{inc,i} - P_{refl,i} = P_{inc,i} (1 - |S_{ii}|^2), S_{ii} = \left. \frac{b_i}{a_i} \right|_{a_k=0, k \neq i}$$

$$= \frac{1}{2} \text{Re}\{P_i^+ - P_i^-\} \rightarrow P_i^+ = \frac{|V_i^+|^2}{Z_{oi}} = |a_i|^2, P_i^- = \frac{|V_i^-|^2}{Z_{oi}} = |b_i|^2$$

11. Two-port device with its S-matrix

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad : \text{reflection coefficient at port 1 with port 2 matched}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad : \text{forward transmission coefficient with port 2 matched}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad : \text{reverse transmission coefficient with port 1 matched}$$


$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \quad : \text{reflection coefficient at port 2 with port 1 matched}$$

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$


$$b_1 = a_1 S_{11} + a_2 S_{12}$$

$$b_2 = a_1 S_{21} + a_2 S_{22}$$

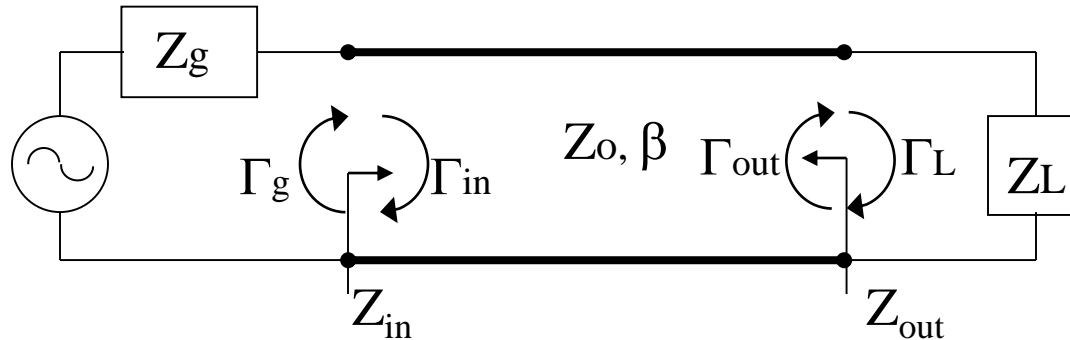
12. Reflection coefficient and S_{11} , S_{22}


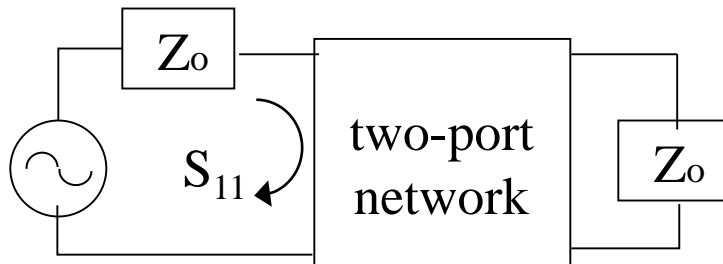
$$\Gamma_{in} = \frac{Z_{in} - Z_g}{Z_{in} + Z_g} = -\Gamma_g, \Gamma_{out} = \frac{Z_{out} - Z_L}{Z_{out} + Z_L} = -\Gamma_L, \text{ if } Z_g = Z_o \text{ then } \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$


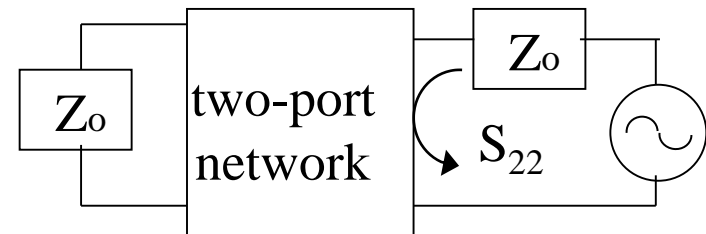
$$S_{11} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o}$$





$$S_{22} = \frac{Z_{out} - Z_o}{Z_{out} + Z_o}$$

13. RL and IL

$$RL \text{ at port 1: } -20 \log \left| \frac{b_1}{a_1} \right| = -20 \log |S_{11}|$$


$$IL \text{ from port 1 to port 2: } -20 \log \left| \frac{b_2}{a_1} \right| = -20 \log |S_{21}|$$
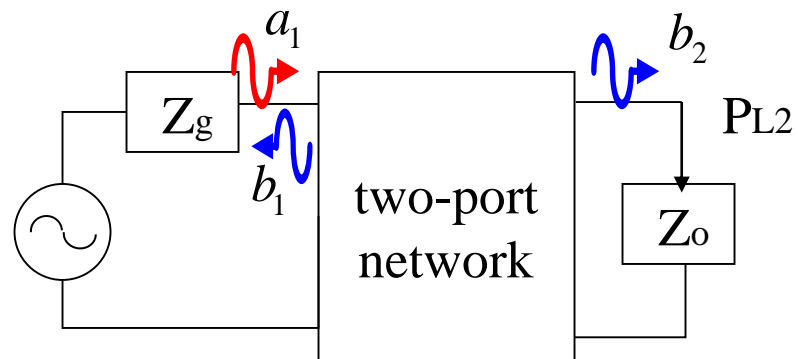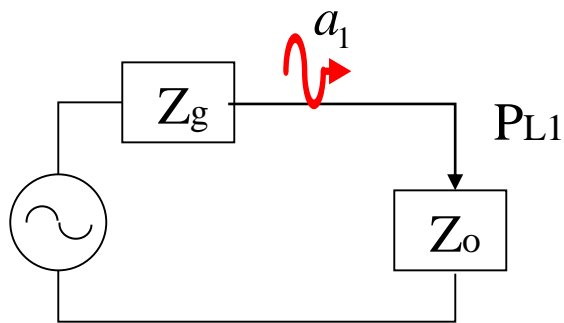
$$\text{insertion loss } IL(dB) \equiv 10 \log \frac{P_{L1}}{P_{L2}}$$



usually $Z_g = Z_o$

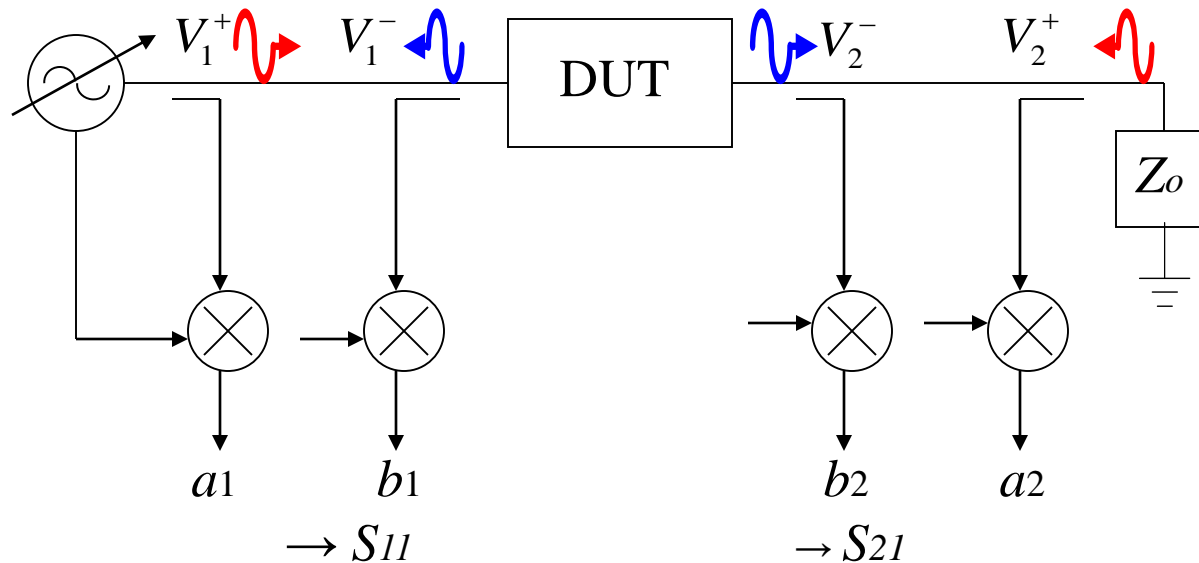14. Two-port S-matrix measurement using VNA



15. Advantages to use S-matrix in microwave circuit

- 1) matched load available in broadband application
- 2) measurable quantity in terms of incident, reflected and transmitted waves
- 3) termination with Z_0 causes no oscillation
- 4) convenient in the use of microwave network analysis

16. Generalized scattering parameters

incident power wave $a_i \equiv \frac{V_i + Z_{ri} I_i}{2\sqrt{|\operatorname{Re} Z_{ri}|}}$, Z_{ri} : reference impedance

reflected power wave $b_i \equiv \frac{V_i - Z_{ri}^* I_i}{2\sqrt{|\operatorname{Re} Z_{ri}|}}$

→ power wave reflection coefficient $S_{ii} \equiv \frac{b_i}{a_i} = \frac{V_i - Z_{ri}^* I_i}{V_i + Z_{ri} I_i} = \frac{Z_L - Z_{ri}^*}{Z_L + Z_{ri}}$

power reflection coefficient $|S_{ii}|^2 = \left| \frac{b_i}{a_i} \right|^2 = \left| \frac{Z_L - Z_{ri}^*}{Z_L + Z_{ri}} \right|^2$, conjugate match $Z_L = Z_{ri}^* \rightarrow |S_{ii}|^2 = 0$

$$P_{in,i} = \frac{1}{2} \operatorname{Re}\{V_i I_i^*\} = \frac{1}{2} (|a_i|^2 - |b_i|^2) = P_L$$



Ref: K.Kurokawa, "Power waves and the scattering matrix", IEEE-MTT, pp.194-201, March 1965

⇔ traveling wave along a lossless line with real Z_0

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}, b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}, V_i = V_i^+ + V_i^- = \sqrt{Z_{oi}}(a_i + b_i), I_i = \frac{V_i^+ - V_i^-}{Z_{oi}} = \frac{a_i - b_i}{\sqrt{Z_{oi}}}$$

$$\rightarrow a_i + b_i = \frac{V_i}{\sqrt{Z_{oi}}}, a_i - b_i = I_i \sqrt{Z_{oi}} \rightarrow a_i = \frac{V_i + Z_0 I_i}{2\sqrt{Z_0}}, b_i = \frac{V_i - Z_0 I_i}{2\sqrt{Z_0}}$$

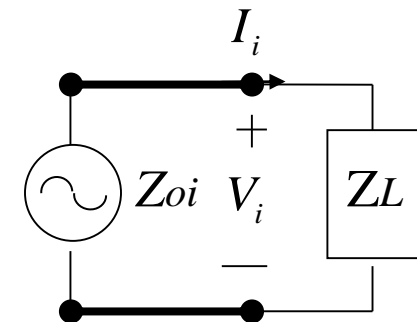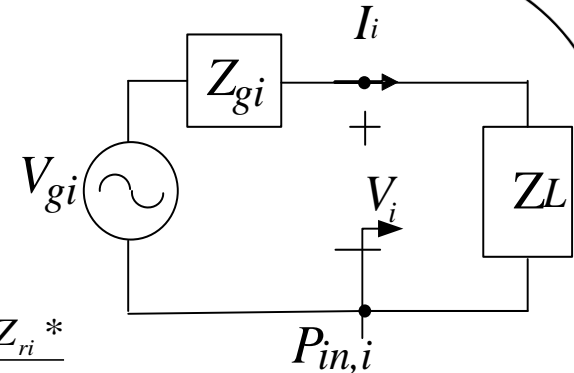
$$S_{ii} = \frac{b_i}{a_i} = \frac{V_i - Z_0 I_i}{V_i + Z_0 I_i} = \frac{Z_L - Z_0}{Z_L + Z_0}, \text{ impedance match } Z_L = Z_0 \rightarrow S_{ii} = 0$$



微波電路講義

$$V_i = V_{gi} \frac{Z_L}{Z_L + Z_{gi}}, I_i = \frac{V_{gi}}{Z_L + Z_{gi}}$$

$$P_L = \frac{1}{2} \operatorname{Re}\{V_i I_i^*\} = \frac{V_{gi}^2}{2} \frac{\operatorname{Re} Z_L}{|Z_L + Z_{gi}|^2}$$

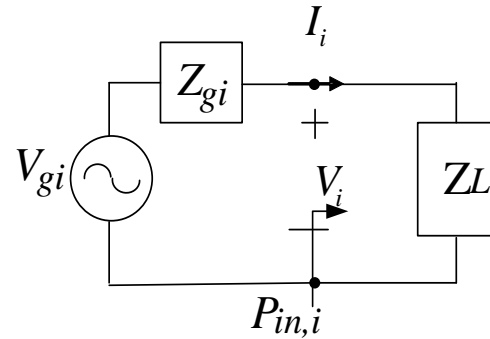

$$a_i \equiv \frac{V_i + Z_{ri} I_i}{2\sqrt{|\operatorname{Re} Z_{ri}|}} = V_{gi} \frac{\frac{Z_L}{Z_L + Z_{gi}} + Z_{ri} \frac{1}{Z_L + Z_{gi}}}{2\sqrt{|\operatorname{Re} Z_{ri}|}} \stackrel{Z_L = Z_{ri}^*}{=} V_{gi} \frac{\sqrt{|\operatorname{Re} Z_{ri}|}}{Z_L + Z_{gi}}$$

if $Z_L = Z_{ri}^* \rightarrow$

$$b_i \equiv \frac{V_i - Z_{ri}^* I_i}{2\sqrt{|\operatorname{Re} Z_{ri}|}} = V_{gi} \frac{\frac{Z_L}{Z_L + Z_{gi}} - Z_{ri}^* \frac{1}{Z_L + Z_{gi}}}{2\sqrt{|\operatorname{Re} Z_{ri}|}} = 0 \rightarrow S_{ii} = 0$$

$$\rightarrow P_L = P_{in,i} = \frac{1}{2} |a_i|^2 = P_{inc,i} = \frac{V_{gi}^2}{2} \frac{\sqrt{|\operatorname{Re} Z_{ri}|}}{|Z_L + Z_{gi}|^2}$$

if $Z_L = Z_g^* \rightarrow P_L = \frac{1}{8} \frac{V_{gi}^2}{\operatorname{Re} Z_L}$: maximum power transfer from source

$$[a] = [F]([V] + [Z_r][I])$$


$$[b] = [F]([V] - [Z_r]^*[I])$$

$$[Z_r] = \begin{bmatrix} Z_{r1} & 0 & \cdot & 0 \\ 0 & \cdot & 0 & 0 \\ 0 & 0 & \cdot & 0 \\ 0 & 0 & 0 & Z_{rN} \end{bmatrix}$$

$$[F] = \frac{1}{2} \begin{bmatrix} \sqrt{\operatorname{Re} Z_{r1}} & 0 & \cdot & 0 \\ 0 & \cdot & 0 & 0 \\ 0 & 0 & \cdot & 0 \\ 0 & 0 & 0 & \sqrt{\operatorname{Re} Z_{rN}} \end{bmatrix},$$


$$[V] = [Z][I] \Rightarrow [b] = [F]([Z] - [Z_r]^*)([Z] + [Z_r])^{-1}[F]^{-1}[a]$$
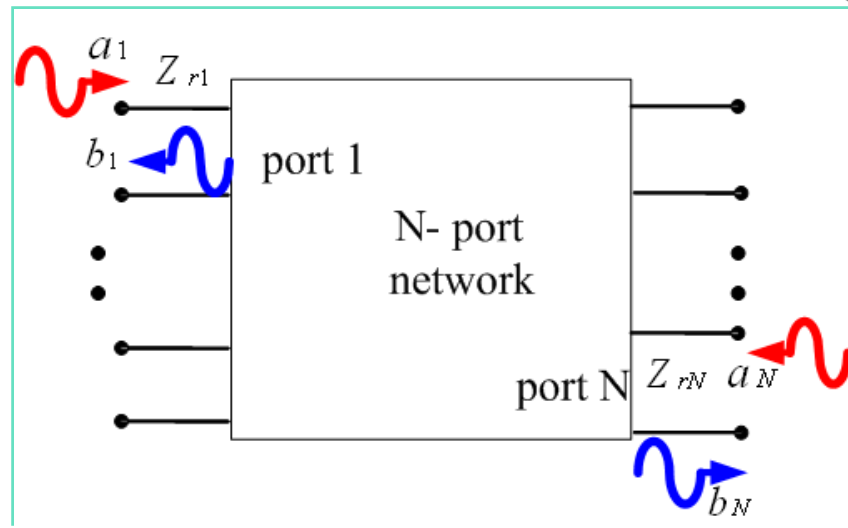
$$\Rightarrow [S] = [F]([Z] - [Z_r]^*)([Z] + [Z_r])^{-1}[F]^{-1}$$



4.4 The transmission (ABCD) matrix

- Cascade network

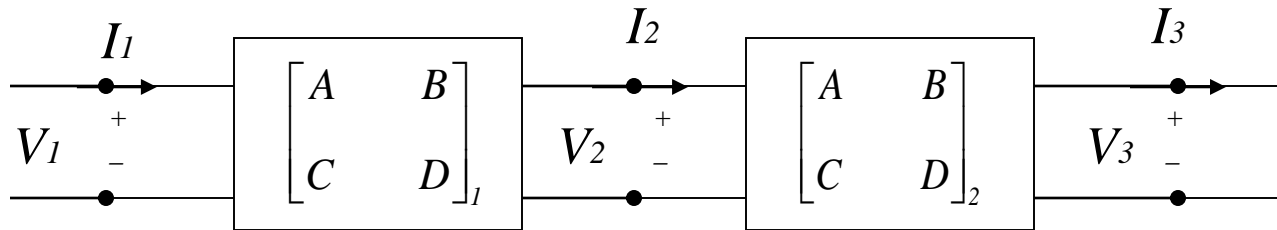

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \begin{bmatrix} A & B \\ C & D \end{bmatrix}_2 \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Discussion

1. ABCD matrix of two-port circuits (p.190, Table 4.1)
2. Reciprocal network $AD-BC=1$
3. S-, Z-, Y-, ABCD-matrix relation of 2-port network (p.192, Table 4.2)
4. Ex. 4.6 ABCD(Z)

(derivation) Z (ABCD)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}, \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{AV_2}{CV_2} = \frac{A}{C}$$

$$Z_{12} = \left. \frac{V_1}{-I_2} \right|_{I_1=0} = \left. \frac{AV_2 + BI_2}{-I_2} \right|_{I_1=0} = -A \left. \frac{V_2}{I_2} \right|_{I_1=0} - B, I_1 = 0 = CV_2 + DI_2 \rightarrow -\frac{V_2}{I_2} = \frac{D}{C}$$

$$= -A\left(-\frac{D}{C}\right) - B = \frac{AD - BC}{C}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{CV_2 + DI_2} \right|_{I_2=0} = \frac{1}{C}$$

$$Z_{22} = -\left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{D}{C}, \because I_1 = 0 = CV_2 + DI_2$$

symmetrical network

$$Z_{11} = Z_{22} \rightarrow A = D$$

reciprocal network

$$Z_{12} = Z_{21}$$


$$\frac{AD - BC}{C} = \frac{1}{C} \rightarrow AD - BC = 1$$

(derivation) S (ABCD)

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}, \begin{matrix} V_1 = V_1^+ + V_1^- \\ I_1 = (V_1^+ - V_1^-)/Z_o \end{matrix} \rightarrow \begin{matrix} V_1^+ = (V_1 + Z_o I_1)/2 \\ V_1^- = (V_1 - Z_o I_1)/2 \end{matrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \left. \frac{V_1 - Z_o I_1}{V_1 + Z_o I_1} \right|_{V_2^+=0} = \left. \frac{AV_2 + BI_2 - Z_o CV_2 - Z_o DI_2}{AV_2 + BI_2 + Z_o CV_2 + Z_o DI_2} \right|_{V_2^+=0}$$
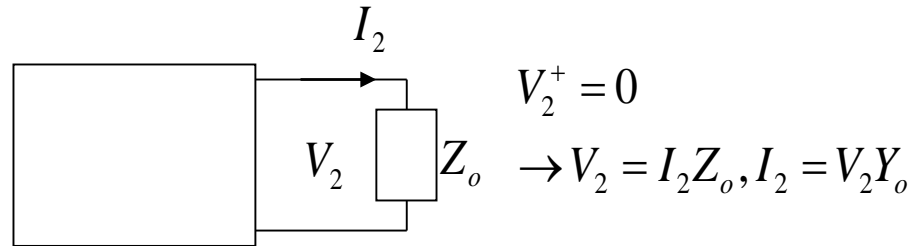
$$= \frac{A + BY_o - CZ_o - D}{A + BY_o + CZ_o + D}$$



$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0} \stackrel{V_2=V_2^-}{=} \frac{V_2}{(V_1 + Z_o I_1)/2} = \frac{2V_2}{AV_2 + BI_2 + Z_o CV_2 + Z_o DI_2}$$


$$= \frac{I_2 = V_2 Y_o \quad 2}{A + BY_o + CZ_o + D}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+=0}, \quad V_2 = V_2^+ + V_2^-, \quad -I_2 = (V_2^+ - V_2^-)/Z_o \rightarrow \begin{cases} V_2^+ = (V_2 - Z_o I_2)/2 \\ V_2^- = (V_2 + Z_o I_2)/2 \end{cases}$$

$$V_1^- = V_1 = \frac{V_1}{(V_2 - Z_o I_2)/2}, \quad \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}, \quad \Delta = AD - BC$$

$$= \frac{2V_1}{(DV_1 - BI_1 + Z_o CV_1 - Z_o AI_1)/\Delta} = \frac{2\Delta V_1}{DV_1 + BY_o V_1 + CZ_o V_1 + AV_1}$$
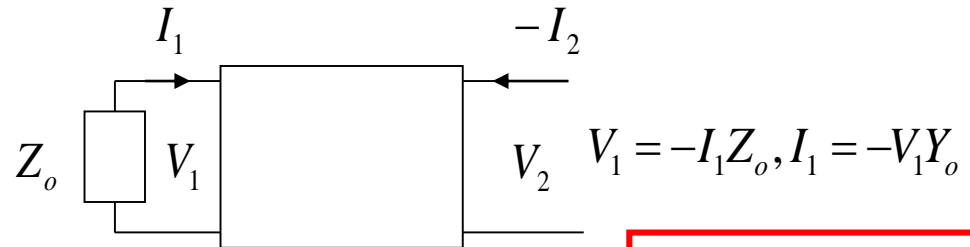
$$= \frac{2\Delta}{A + BY_o + CZ_o + D}$$




$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+=0} = \frac{V_2 + Z_o I_2}{V_2 - Z_o I_2} = \frac{DV_1 - BI_1 + Z_o(-CV_1 + AI_1)}{DV_1 - BI_1 - Z_o(-CV_1 + AI_1)}$$


$$\stackrel{I_1 = -V_1 Y_o}{=} \frac{DV_1 + BY_o V_1 + Z_o(-CV_1 + AY_o V_1)}{DV_1 + BY_o V_1 - Z_o(-CV_1 + AY_o V_1)} = \frac{-A + BY_o - CZ_o + D}{A + BY_o + CZ_o + D}$$

symmetrical
 $S_{11} = S_{22}, A = D$
 reciprocal
 $S_{12} = S_{21}, \Delta = 1$


5. Example

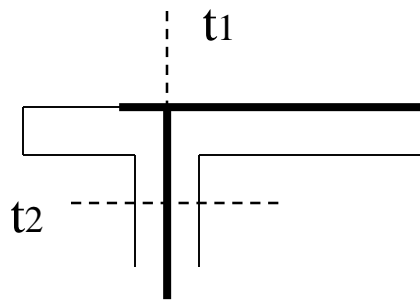

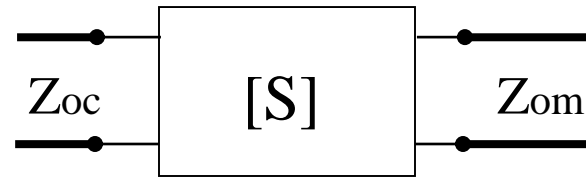coaxial-microstrip transition
(a linear circuit)




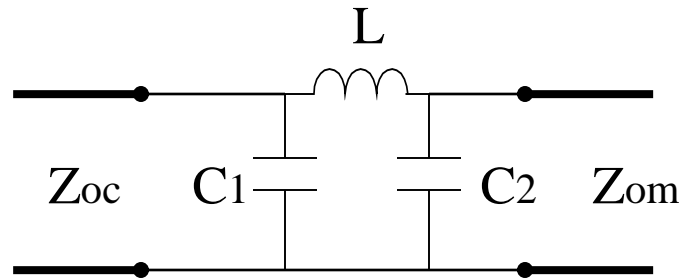
[S] representation can be obtained from
measurement or calculation.



one possible equivalent circuit

4.5 Signal flow graphs

- 2-port representation

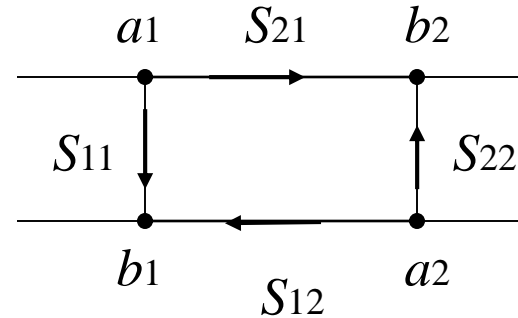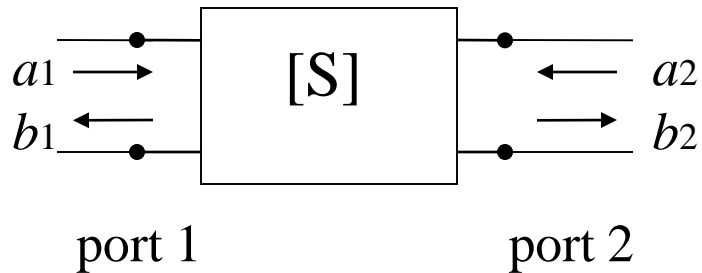

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$b_1 = a_1 S_{11} + a_2 S_{12}$$


$$b_2 = a_1 S_{21} + a_2 S_{22}$$

$$RL \text{ at port 1: } -20 \log \left| \frac{b_1}{a_1} \right| = -20 \log |S_{11}|$$


$$IL \text{ from port 1 to port 2: } -20 \log \left| \frac{b_2}{a_1} \right| = -20 \log |S_{21}|$$

Discussion



1. Source representation

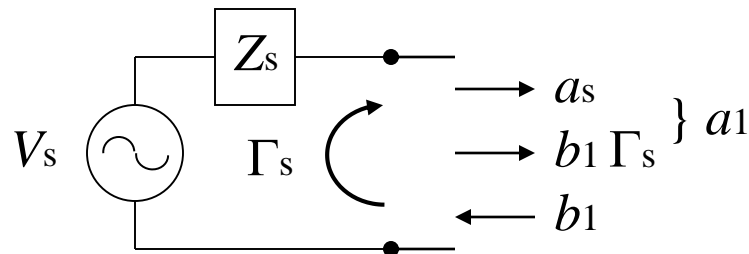
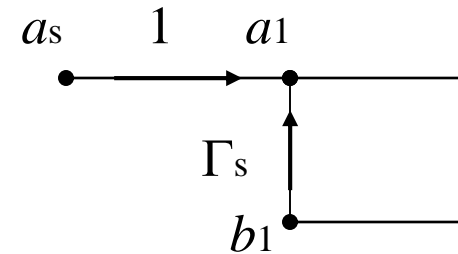
$$e_s = V_s \frac{Z_o}{Z_o + Z_s}, a_s \equiv \frac{e_s}{\sqrt{Z_o}}$$




2. Load representation

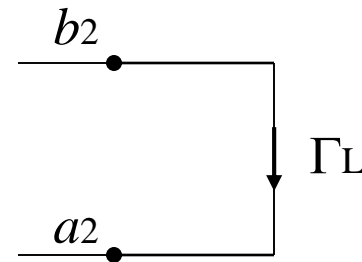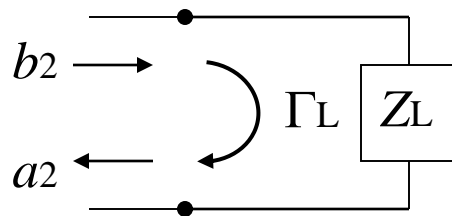

3. Series, parallel, self-loop, splitting rules (p.196, Fig.4.16)

4. 2-port circuit representation


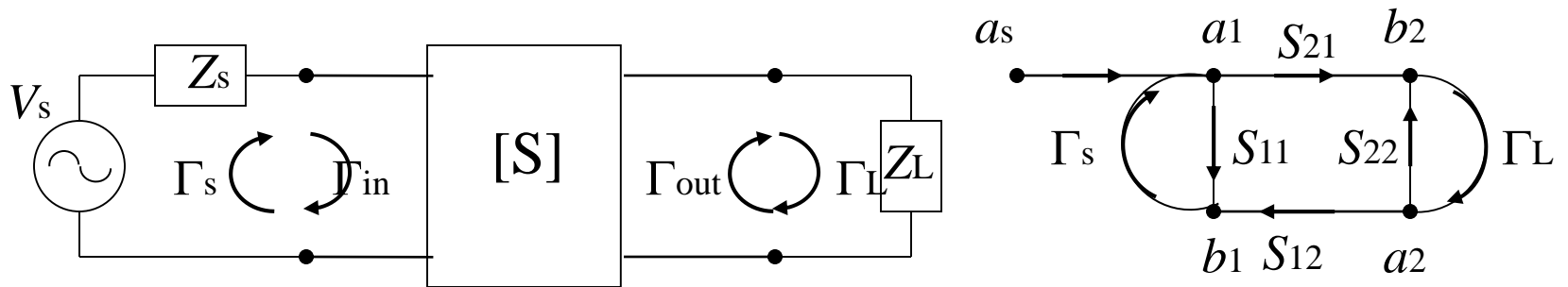


$$b_1 = a_1 S_{11} + a_1 S_{21} \Gamma_L S_{12} (1 + S_{22} \Gamma_L + \dots) = a_1 S_{11} + a_1 \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\rightarrow \Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$


$$b_2 = a_2 S_{22} + a_2 S_{12} \Gamma_S S_{21} (1 + S_{11} \Gamma_S + \dots) = a_2 S_{22} + a_2 \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$
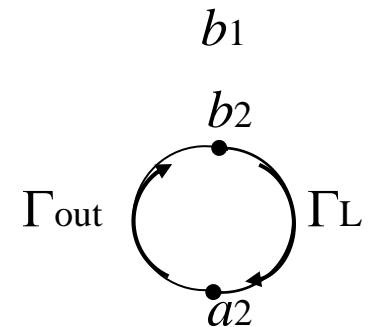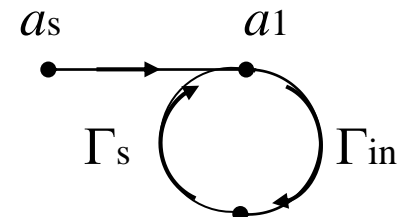
$$\Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$



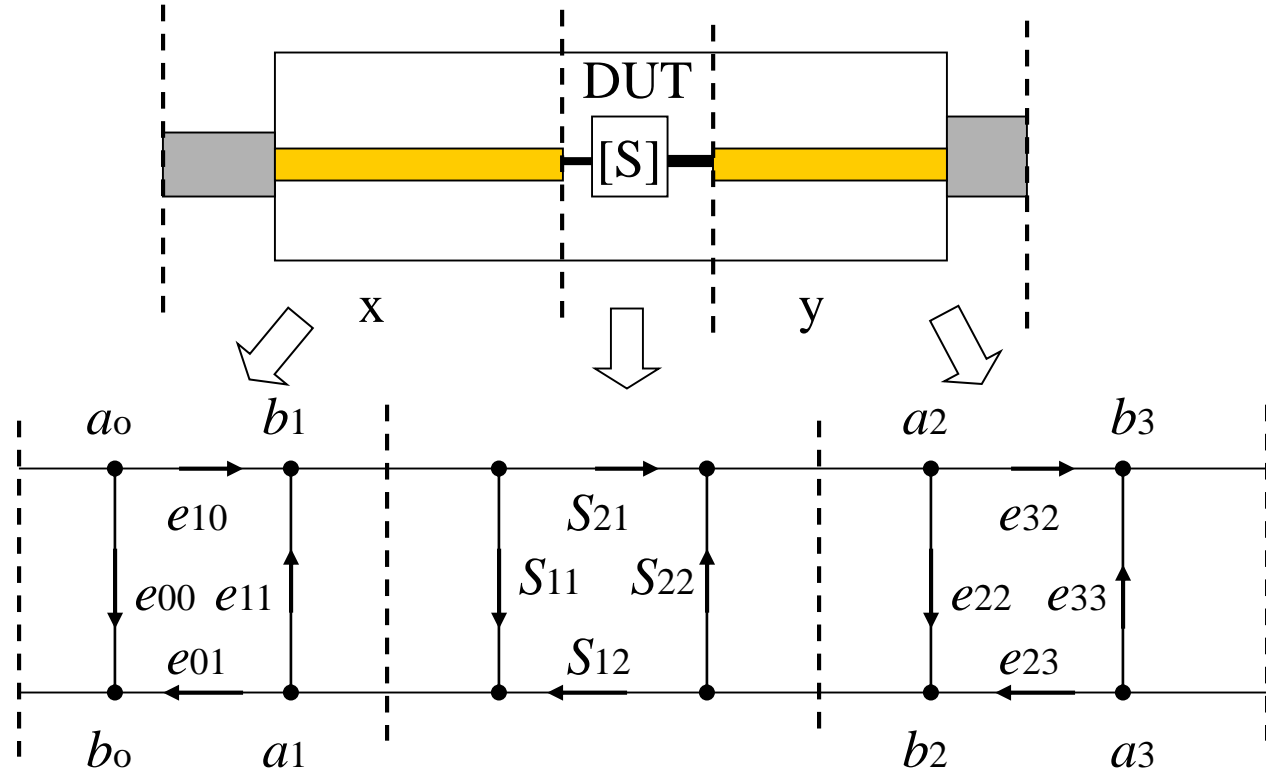5. TRL (Thru-Reflect-Line) calibration

Find $[S]_{\text{DUT}}$ from 2-port measurement using three calibrators



6 unknowns of $[S]_x$ and $[S]_y$ to be calibrated to acquire $[S]_{\text{DUT}}$


T: Through \rightarrow 3 eqs., R: Reflection \rightarrow 2 eqs., L: Line \rightarrow 3 eqs.

\Rightarrow R (Γ) and line length (γl) can be unknown

Calibrators


T: Through

→ 3 eqs.

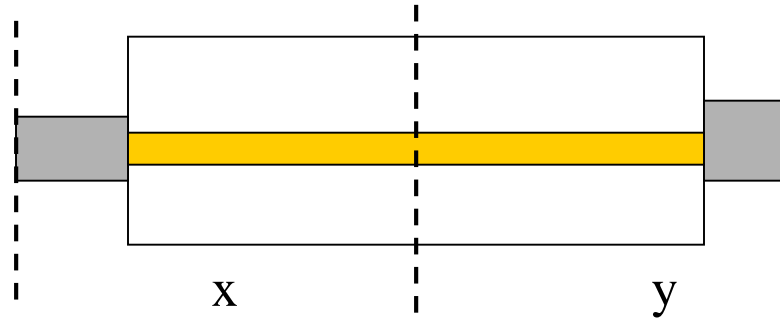


R: Reflection

→ 2 eqs.

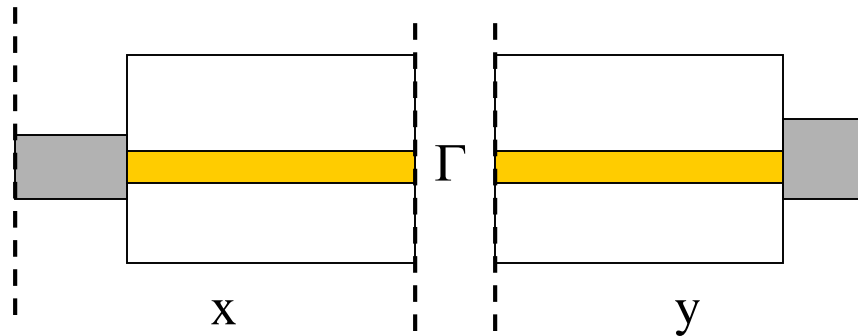

L: Line

→ 3 eqs.

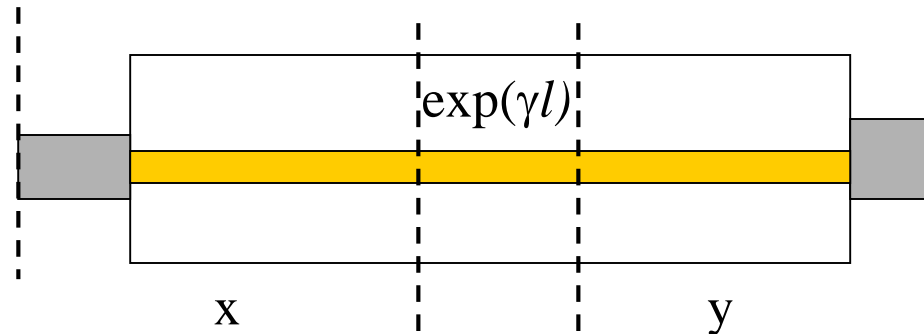

Requirement: connectors and line have same characteristics for 3 calibrators

Limitation: operation bandwidth $20^\circ \leq \beta l \leq 160^\circ$

(brief derivation)

R – matrix (wave cascade matrix)

$$\begin{bmatrix} \mathbf{b}_1 \\ \mathbf{a}_1 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} \mathbf{a}_2 \\ \mathbf{b}_2 \end{bmatrix}$$

$$[R] = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} = \frac{1}{S_{21}} \begin{bmatrix} S_{12}S_{21} - S_{11}S_{22} & S_{11} \\ -S_{22} & 1 \end{bmatrix}$$

error matrices $[R_x] = \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix}$, $[R_y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

Through: $[S_T] = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \rightarrow [R_T] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

Line: $[S_L] = \begin{bmatrix} 0 & e^{-\gamma l} \\ e^{-\gamma l} & 0 \end{bmatrix} \rightarrow [R_L] = \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix}$

Reflection: Γ

Thru measurement: $[R_{mT}] = [R_x] [R_T] [R_y] = [R_x] [R_y]$

Line measurement: $[R_{mL}] = [R_x] [R_L] [R_y]$

$$\Rightarrow [M] [R_x] = [R_x] [R_L], \quad [M] \equiv [R_{mL}] [R_{mT}]^{-1} \quad \Rightarrow \quad e_{00}, \frac{e_{01}e_{10}}{e_{11}}$$

$$[R_y] [N] = [R_L] [R_y], \quad [N] \equiv [R_{mT}]^{-1} [R_{mL}] \quad \Rightarrow \quad e_{33}, \frac{e_{23}e_{32}}{e_{22}}$$

reflection measurement at port 1 $\Gamma_{mx} = e_{00} + \frac{e_{10}e_{01}\Gamma}{1 - e_{11}\Gamma}$

reflection measurement at port 2 $\Gamma_{my} = e_{33} + \frac{e_{23}e_{32}\Gamma}{1 - e_{22}\Gamma}$

$$\left. \begin{array}{l} \Gamma_{mx} \\ \Gamma_{my} \\ \Gamma_{mT} \end{array} \right\} \Rightarrow e_{11}, e_{22}, e_{10}e_{01}, e_{23}e_{32} \quad \left. \begin{array}{l} S_{21mT} \\ S_{12mT} \end{array} \right\} \Rightarrow e_{10}e_{32}, e_{23}e_{01}$$

$$\Rightarrow e_{10}, e_{01}, e_{23}, e_{32}$$

$$\Rightarrow \Gamma, e^{-\gamma l}$$

(detailed derivation)

$$[M][R_x] = [R_x][R_L] \rightarrow \begin{bmatrix} m_{11} & m_{12} \\ m_{21} & m_{22} \end{bmatrix} \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix} = \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix} \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix}$$

$$\rightarrow \begin{cases} m_{11}x_{11} + m_{12}x_{21} = x_{11}e^{-\gamma l} \\ m_{21}x_{11} + m_{22}x_{21} = x_{21}e^{-\gamma l} \\ m_{11}x_{12} + m_{12}x_{22} = x_{12}/e^{-\gamma l} \\ m_{21}x_{12} + m_{22}x_{22} = x_{22}/e^{-\gamma l} \end{cases} \rightarrow \begin{cases} m_{21}\left(\frac{x_{11}}{x_{21}}\right)^2 + (m_{22} - m_{11})\frac{x_{11}}{x_{21}} - m_{12} = 0 \\ m_{21}\left(\frac{x_{12}}{x_{22}}\right)^2 + (m_{22} - m_{11})\frac{x_{12}}{x_{22}} - m_{12} = 0 \end{cases} \rightarrow \begin{cases} a = \frac{x_{11}}{x_{21}} = e_{00} - \frac{e_{10}e_{01}}{e_{11}} \\ b = \frac{x_{12}}{x_{22}} = e_{00} \end{cases}$$

root choice : $e_{10}e_{01} \neq 0 \rightarrow a \neq b, |e_{00}| \approx |e_{11}| \ll 1 \rightarrow |a| > |b|$

$$[R_y][N] = [R_L][R_y] \rightarrow \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} n_{11} & n_{12} \\ n_{21} & n_{22} \end{bmatrix} = \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix} \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$\rightarrow \begin{cases} y_{11}n_{11} + y_{12}n_{21} = y_{11}e^{-\gamma l} \\ y_{21}n_{11} + y_{22}n_{21} = y_{12}e^{-\gamma l} \\ y_{11}n_{12} + y_{12}n_{22} = y_{12}/e^{-\gamma l} \\ y_{21}n_{12} + y_{22}n_{22} = y_{22}/e^{-\gamma l} \end{cases} \rightarrow \begin{cases} n_{12}\left(\frac{y_{11}}{y_{12}}\right)^2 + (n_{22} - n_{11})\frac{y_{11}}{y_{12}} - n_{21} = 0 \\ n_{12}\left(\frac{y_{21}}{y_{22}}\right)^2 + (n_{22} - n_{11})\frac{y_{21}}{y_{22}} - n_{21} = 0 \end{cases} \rightarrow \begin{cases} c = \frac{y_{11}}{y_{12}} = -e_{33} + \frac{e_{23}e_{32}}{e_{22}} \\ d = \frac{y_{21}}{y_{22}} = -e_{33} \end{cases}$$

root choice : $e_{23}e_{32} \neq 0 \rightarrow c \neq d, |e_{22}| \approx |e_{33}| \ll 1 \rightarrow |c| > |d|$

$$\left\{ \begin{array}{l} \Gamma_{mx} = e_{00} + \frac{e_{10}e_{01}\Gamma}{1 - e_{11}\Gamma} \rightarrow \Gamma = \frac{1}{e_{11}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \\ \Gamma_{my} = e_{33} + \frac{e_{23}e_{32}\Gamma}{1 - e_{22}\Gamma} \rightarrow \Gamma = \frac{1}{e_{22}} \frac{d + \Gamma_{my}}{c + \Gamma_{my}} \\ \Gamma_{mT} = e_{00} + \frac{e_{10}e_{01}e_{22}}{1 - e_{11}e_{22}} \rightarrow e_{11} = \frac{1}{e_{22}} \frac{b - \Gamma_{mT}}{a - \Gamma_{mT}} \end{array} \right.$$

$$\Rightarrow e_{11}^2 = \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \frac{c + \Gamma_{my}}{d + \Gamma_{my}} \frac{b - \Gamma_{mT}}{a - \Gamma_{mT}}, e_{22} = \frac{1}{e_{11}} \frac{b - \Gamma_{mT}}{a - \Gamma_{mT}}, e_{10}e_{01} = (b - a)e_{11}, e_{23}e_{32} = (c - d)e_{22}$$

$$\left\{ \begin{array}{l} S_{21mT} = \frac{e_{10}e_{32}}{1 - e_{11}e_{22}} \\ S_{12mT} = \frac{e_{23}e_{01}}{1 - e_{11}e_{22}} \end{array} \right. \Rightarrow e_{10}e_{32} = S_{21mT}(1 - e_{11}e_{22}), e_{23}e_{01} = S_{12mT}(1 - e_{11}e_{22}) \Rightarrow e_{10}, e_{01}, e_{23}, e_{32}$$

$$\Rightarrow \Gamma = \frac{1}{e_{11}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \dots (\text{also for } e_{11} \text{ selection}), e^{-\gamma l} = m_{11} + \frac{m_{12}}{a}$$

4.6 Discontinuities and modal analysis

- equivalent circuit components

$$\Delta E \Rightarrow C, \quad \Delta H \Rightarrow L$$

constant E (V) \Rightarrow parallel connection



constant H (I) \Rightarrow serial connection

Discussion


1. Microstrip discontinuities





open-end

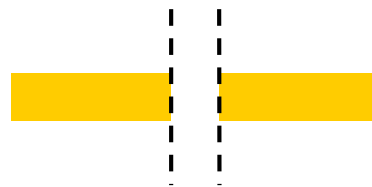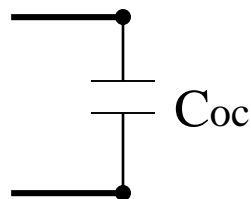


gap

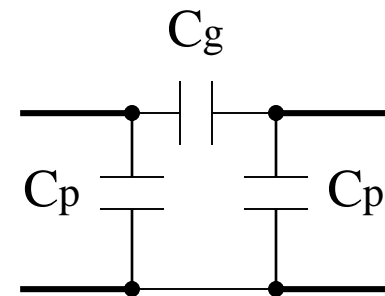


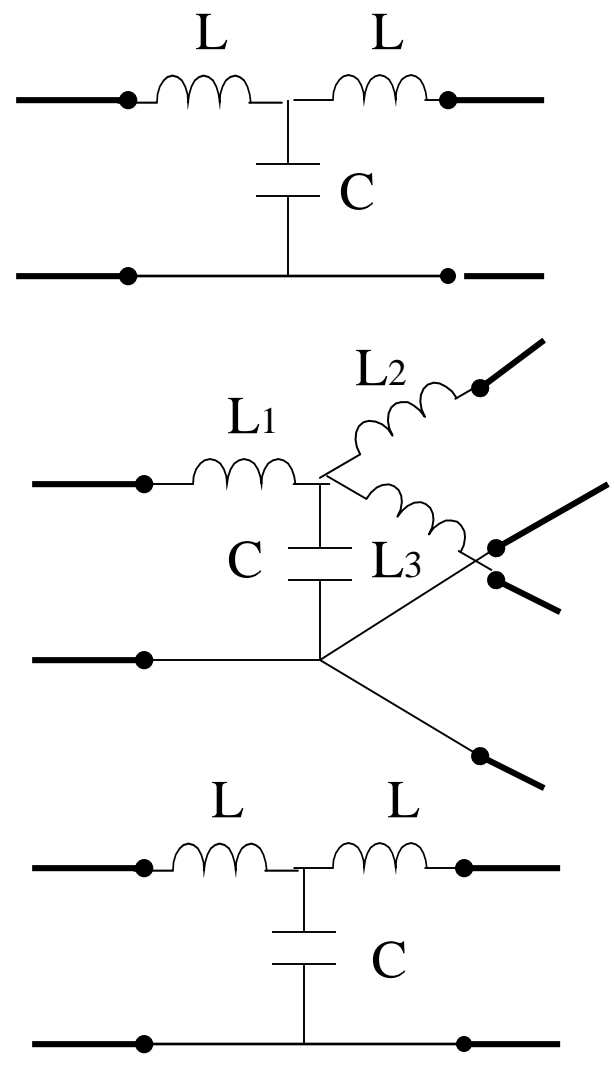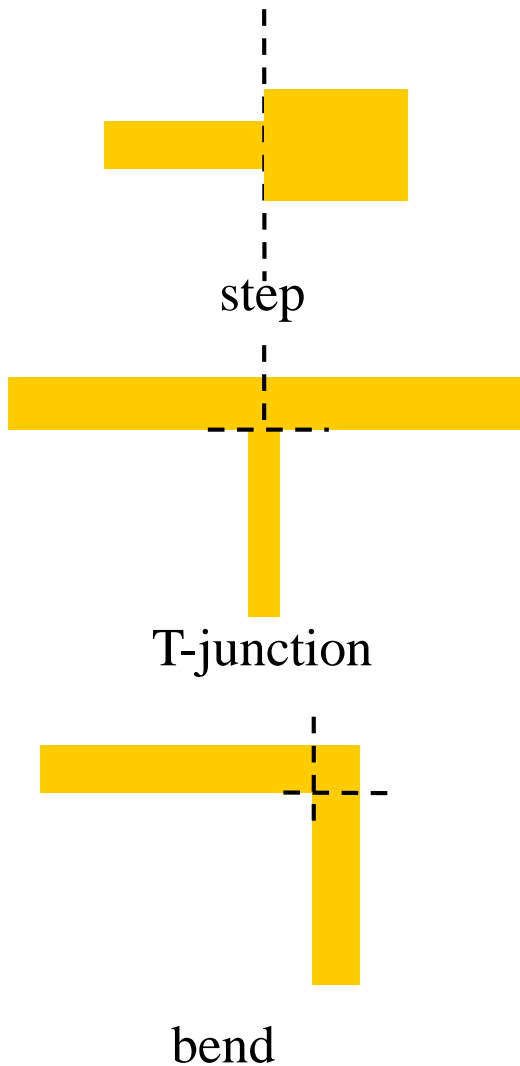

2. Microstrip discontinuity compensation

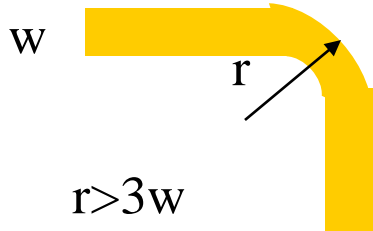

swept bend

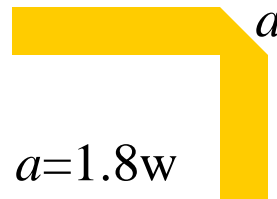

$$a = 1.8w$$



mitered bends




mitered step



mitered T-junction

Solved Problems


Prob. 4.11 Find [S] relative to Z_o

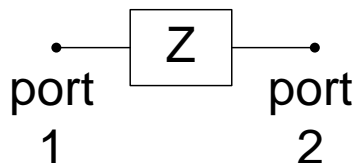

$$[Y] = \begin{bmatrix} 1/Z & -1/Z \\ -1/Z & 1/Z \end{bmatrix}, DY = (Y_o + Y_{11})(Y_o + Y_{22}) + Y_{12}Y_{21} = \frac{Z + 2Z_o}{ZZ_o^2}$$

$$[S] = \begin{bmatrix} \frac{(Y_o - Y_{11})(Y_o + Y_{22}) + Y_{12}Y_{21}}{DY} & \frac{-2Y_{12}Y_o}{DY} \\ \frac{-2Y_{21}Y_o}{DY} & \frac{(Y_o + Y_{11})(Y_o - Y_{22}) + Y_{12}Y_{21}}{DY} \end{bmatrix}$$
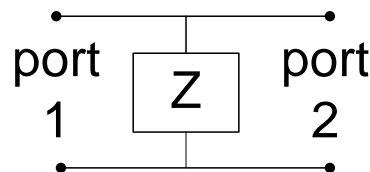
$$= \begin{bmatrix} \frac{1/Z_o^2}{DY} & \frac{2/ZZ_o}{DY} \\ \frac{2/ZZ_o}{DY} & \frac{1/Z_o^2}{DY} \end{bmatrix} = \begin{bmatrix} \frac{Z}{Z + 2Z_o} & \frac{2Z_o}{Z + 2Z_o} \\ \frac{2Z_o}{Z + 2Z_o} & \frac{Z}{Z + 2Z_o} \end{bmatrix}, 1 - S_{11} = S_{21}$$




$$[Z] = \begin{bmatrix} Z & Z \\ Z & Z \end{bmatrix}, \Delta Z = (Z_o + Z_{11})(Z_o + Z_{22}) - Z_{12}Z_{21} = 2Z_oZ + Z_o^2$$

$$[S] = \begin{bmatrix} \frac{(Z_{11} - Z_o)(Z_{22} + Z_o) - Z_{12}Z_{21}}{\Delta Z} & \frac{2Z_{12}Z_o}{\Delta Z} \\ \frac{2Z_{21}Z_o}{\Delta Z} & \frac{(Z_{11} + Z_o)(Z_{22} - Z_o) - Z_{12}Z_{21}}{\Delta Z} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{-Z_o^2}{\Delta Z} & \frac{2ZZ_o}{\Delta Z} \\ \frac{2ZZ_o}{\Delta Z} & \frac{-Z_o^2}{\Delta Z} \end{bmatrix} = \begin{bmatrix} \frac{-Z_o}{Z_o + 2Z} & \frac{2Z}{Z_o + 2Z} \\ \frac{2Z}{Z_o + 2Z} & \frac{-Z_o}{Z_o + 2Z} \end{bmatrix}, 1 + S_{11} = S_{21}$$

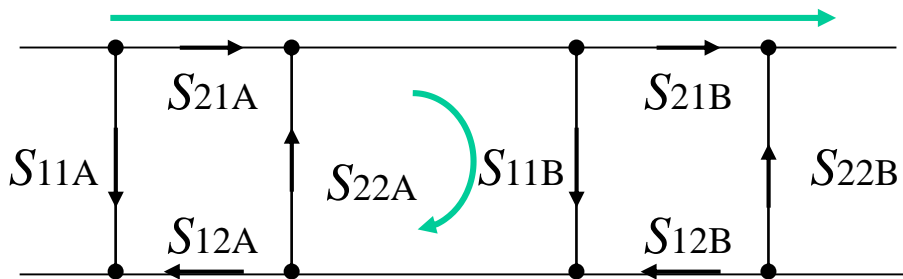Prob. 4.12 Find S_{21} of $[S_A]$ in cascade of $[S_B]$



$$S_{21} = \frac{S_{21A}S_{21B}}{1 - S_{22A}S_{11B}}$$

微波電路講義

Prob. 4.14

$$\begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix}$$

(1) $|S_{12}|^2 + |S_{42}|^2 = 0.8 \neq 1 \rightarrow \text{lossy}$

(2) $[S]$ symmetrical $\rightarrow \text{reciprocal}$

(3) return loss at port 1 = $-20 \log |S_{11}| = -20 \log 0.1 = 20 \text{dB}$

(4) insertion loss between port 2 and port 4 = $-20 \log |S_{24}| = -20 \log 0.4 = 8 \text{dB}$

phase delay between port 2 and port 4 = 45°

(5) reflection at port 1 as port 3 is connected to a short circuit

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} 0.178\angle 90^\circ & 0.6\angle 45^\circ & 0.4\angle 45^\circ & 0 \\ 0.6\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0.4\angle 45^\circ & 0 & 0 & 0.5\angle -45^\circ \\ 0 & 0.3\angle -45^\circ & 0.5\angle -45^\circ & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ 0 \\ -b_3 \\ 0 \end{bmatrix}$$

$$b_3 = 0.4\angle 45^\circ a_1$$

$$b_1 = 0.178\angle 90^\circ a_1 - 0.4\angle 45^\circ b_3 = 0.178\angle 90^\circ a_1 - 0.16\angle 90^\circ a_1 = 0.018\angle 90^\circ a_1$$

$$S_{11} = \frac{b_1}{a_1} = 0.018j$$

Prob. 4.19 given $[S_{ij}]$ of a two-port network normalized to Z_o , find its generalized $[S'_{ij}]$ in terms of Z_{o1} and Z_{o2}



$$\text{incident (power) wave : } a_i \equiv \frac{V_i^+}{\sqrt{Z_{oi}}} = \frac{V_i + Z_{oi}I_i}{2\sqrt{Z_{oi}}}$$

$$\text{reflected (power) wave : } b_i \equiv \frac{V_i^-}{\sqrt{Z_{oi}}} = \frac{V_i - Z_{oi}I_i}{2\sqrt{Z_{oi}}}$$

$$[V^-] = [S][V^+] \Rightarrow [b] = [S][a], \quad S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, k \neq j} = \left. \frac{V_i^- \sqrt{Z_{oj}}}{V_j^+ \sqrt{Z_{oi}}} \right|_{V_k^+=0, k \neq j}$$

$$\Rightarrow S'_{11} = S_{11}, S'_{12} = S_{12} \frac{\sqrt{Z_{o2}}}{\sqrt{Z_{o1}}}, S'_{21} = S_{21} \frac{\sqrt{Z_{o1}}}{\sqrt{Z_{o2}}}, S'_{22} = S_{22}$$

Prob. 4.28 find P_2/P_1 and P_3/P_1

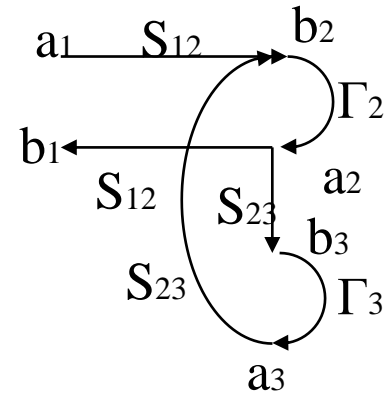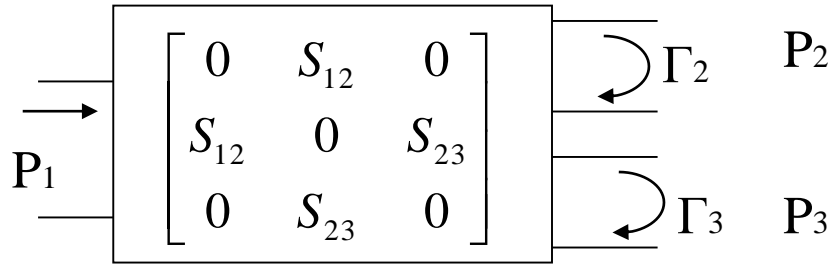

$$b_1 = a_1 \frac{S_{12}^2 \Gamma_2}{1 - \Gamma_2 \Gamma_3 S_{23}^2} = a_1 \Gamma_{in}, b_2 = a_1 \frac{S_{12}}{1 - \Gamma_2 \Gamma_3 S_{23}^2}, b_3 = a_1 \frac{S_{12} \Gamma_2 S_{23}}{1 - \Gamma_2 \Gamma_3 S_{23}^2}$$

$$\frac{P_2}{P_1} = \frac{|b_2|^2 - |a_2|^2}{|a_1|^2 - |b_1|^2} = \frac{|b_2|^2 (1 - |\Gamma_2|^2)}{|a_1|^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 \left(1 - \frac{|S_{12}^2 \Gamma_2|^2}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2}\right)} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 - |S_{12}^2 \Gamma_2|^2}$$

$$\frac{P_3}{P_1} = \frac{|b_3|^2 - |a_3|^2}{|a_1|^2 - |b_1|^2} = \frac{|b_3|^2 (1 - |\Gamma_3|^2)}{|a_1|^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 |\Gamma_2|^2 |S_{23}|^2 (1 - |\Gamma_3|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 \left(1 - \frac{|S_{12}^2 \Gamma_2|^2}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2}\right)} = \frac{|S_{12}|^2 |\Gamma_2|^2 |S_{23}|^2 (1 - |\Gamma_3|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 - |S_{12}^2 \Gamma_2|^2}$$

ADS examples: Ch4_prj