

Chapter 4 Microwave network analysis

- 4.1 Impedance and equivalent voltages and currents
equivalent transmission line model (β , Z_0)
- 4.2 Impedance and admittance matrices
not applicable in microwave circuits
- 4.3 The scattering matrix
properties, VNA measurement
- 4.4 The transmission (ABCD) matrix
cascade network
- 4.5 Signal flow graph
2-port circuit, TRL calibration
- 4.6 Discontinuities and modal analysis
microstrip discontinuities and compensation

4.1 Impedance and equivalent voltages and currents

- Equivalent voltages and currents

Microwave circuit approach

Interest: voltage and current at a set of terminals (ports), power flow through a device, and how to find the response of a network

For a certain mode in the line, the line characteristics are represented by its global quantities Z_0 , β , l .

Define: equivalent voltage (wave) \propto transverse electric field

equivalent current (wave) \propto transverse magnetic field

\ni voltage (wave)/current (wave) = characteristic impedance or wave impedance of the line

and voltage \times current = power flow of the mode

→ use transmission line theory to analyze microwave circuit performance at the interested ports

- Impedance

characteristic impedance of the medium $\eta = \sqrt{\frac{\mu}{\epsilon}}$


wave impedance of the particular mode of wave $Z_w = \frac{E_t^+}{H_t^+}$

characteristic impedance of the line $Z_o = \frac{V^+}{I^+}$

input impedance at a port of circuit $Z_{in}(z) = \frac{V(z)}{I(z)}$

Discussion

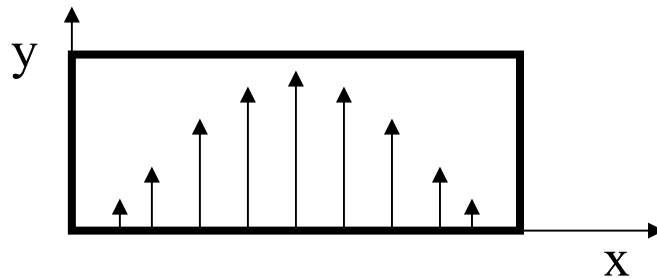1. Transmission line model for the TE₁₀ mode of a rectangular waveguide



$$V(x, z) \equiv \int \bar{E} \cdot d\bar{l} = \int E_y dy$$

: x - dependent , non - unique value

transverse fields

transmission line model

$$E_y = (A^+ e^{-j\beta z} + A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_1 V \sin \frac{\pi x}{a}$$

$$V = V_{o^+} e^{-j\beta z} + V_{o^-} e^{j\beta z}$$

$$I = I_{o^+} e^{-j\beta z} + I_{o^-} e^{j\beta z}$$

$$H_x = -\frac{1}{Z_{TE_{10}}} (A^+ e^{-j\beta z} - A^- e^{j\beta z}) \sin \frac{\pi x}{a} \equiv C_2 I \sin \frac{\pi x}{a}$$

$$= \frac{V_{o^+}}{Z_o} e^{-j\beta z} - \frac{V_{o^-}}{Z_o} e^{j\beta z}$$

$$Z_{TE_{10}} = -\frac{E_y^+}{H_x^+} = \frac{k\eta}{\beta} \equiv Z_o$$

$$Z_o = \frac{V_{o^+}}{I_{o^+}} = -\frac{V_{o^-}}{I_{o^-}}$$

$$P^+ = -\frac{1}{2} \int E_y^+ H_x^{+*} dx dy$$


$$P^+ = \frac{1}{2} V_{o^+} I_{o^+}^*$$

微波電路講義

$$P^+ = \frac{ab}{4Z_{TE_{10}}} |A^+|^2 \equiv \frac{1}{2} V_o^+ I_o^{+*} = \frac{1}{2} C_1 C_2^* |A^+|^2$$

$$Z_{TE_{10}} \equiv Z_o = \frac{C_1}{C_2} \Rightarrow C_1 = \sqrt{\frac{ab}{2}}, \quad C_2 = \frac{1}{Z_{TE_{10}}} \sqrt{\frac{ab}{2}}$$

2. Ex.4.2

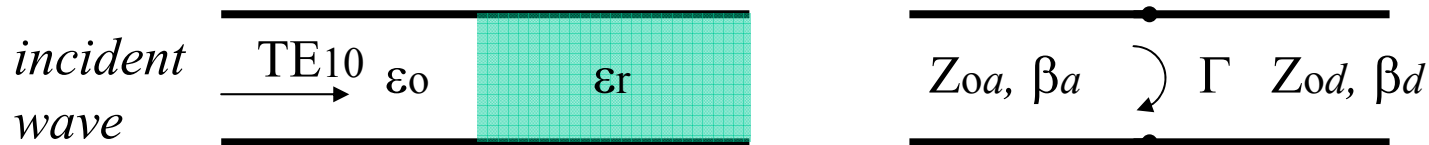

$$\Gamma = \frac{Z_{od} - Z_{oa}}{Z_{od} + Z_{oa}}$$

$$Z_{oa} = \frac{k_o \eta_o}{\beta_a}, \quad Z_{od} = \frac{k \eta}{\beta_d}, \quad k_o \eta_o = k \eta, \quad k = \sqrt{\epsilon_r} k_o$$

$$\beta_a^2 + k_c^2 = k_o^2, \quad \beta_d^2 + k_c^2 = k^2, \quad k_c = \frac{\pi}{a}$$

$$a = 2.286 \text{ cm} \rightarrow \lambda_c = 2a = 4.472 \text{ cm} \rightarrow k_c = 137 \text{ m}^{-1}, \quad f_c = 6.56 \text{ GHz}$$

$$\text{if } f = 10 \text{ GHz} \rightarrow k_o = 209 \text{ m}^{-1}, \beta_a = 158 \text{ m}^{-1}, \epsilon_r = 2.54 \rightarrow k = 333 \text{ m}^{-1}, \beta_d = 304 \text{ m}^{-1}$$

$$\text{if } f = 6 \text{ GHz} \rightarrow k = 201 \text{ m}^{-1} > k_c, k_o = 126 \text{ m}^{-1} < k_c$$

Q: What if the incident wave is from the other direction? **“N”**


4.2 Impedance and admittance matrices

reference plane

for port 1

(plane

for $\angle V_1^+ = 0$)

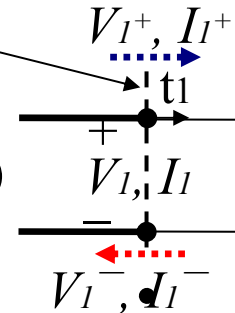

port 1

N-port
network


port N

reference plane

for port N

(plane

for $\angle V_N^+ = 0$)

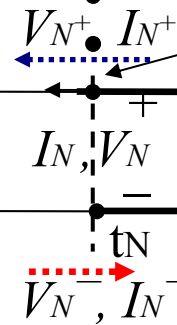

$$V_i = V_i^+ + V_i^-$$

$$I_i = I_i^+ + I_i^- = \frac{V_i^+ - V_i^-}{Z_{oi}}$$

$$Z_{oi} = \frac{V_i^+}{I_i^+} = -\frac{V_i^-}{I_i^-}$$

$$P_{inc,i} = \frac{1}{2} \text{Re} \{V_i^+ I_i^{+*}\}, P_{in,i} = \frac{1}{2} \text{Re} \{V_i I_i^*\}$$

• Impedance matrix

$$[V] = [Z] [I], \quad \begin{bmatrix} V_1 \\ V_2 \\ \bullet \\ \bullet \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \bullet & \bullet & Z_{1N} \\ Z_{21} & \bullet & \bullet & \bullet & Z_{2N} \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ Z_{N1} & Z_{N2} & \bullet & \bullet & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \bullet \\ \bullet \\ I_N \end{bmatrix}, \quad Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0, k \neq j} = \left. \frac{\text{response}_i}{\text{source}_j} \right|_{I_k=0, k \neq j}$$

• Admittance matrix

$$[I] = [Y] [V], \quad \begin{bmatrix} I_1 \\ I_2 \\ \bullet \\ \bullet \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \bullet & \bullet & Y_{1N} \\ Y_{21} & \bullet & \bullet & \bullet & Y_{2N} \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ Y_{N1} & Y_{N2} & \bullet & \bullet & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \bullet \\ \bullet \\ V_N \end{bmatrix}, \quad Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0, k \neq j} = \left. \frac{\text{response}_i}{\text{source}_j} \right|_{V_k=0, k \neq j}$$

Discussion

1. Reciprocal network

$$\begin{aligned} [Z] &= [Z]^t, & Z_{ij} &= Z_{ji}, & [Z] \text{ and } [Y] &: \text{ symmetric matrix} \\ [Y] &= [Y]^t, & Y_{ij} &= Y_{ji} \end{aligned}$$

(derivation)

source		port 1	port 2
a	→	V_{1a}, I_{1a}	V_{2a}, I_{2a}
b	→	V_{1b}, I_{1b}	V_{2b}, I_{2b}

reciprocity theorem: $V_{1a}I_{1b} + V_{2a}I_{2b} = V_{1b}I_{1a} + V_{2b}I_{2a}$


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$(\cancel{Z_{11}I_{1a}} + Z_{12}I_{2a})I_{1b} + (Z_{21}I_{1a} + \cancel{Z_{22}I_{2a}})I_{2b} = (\cancel{Z_{11}I_{1b}} + Z_{12}I_{2b})I_{1a} + (Z_{21}I_{1b} + \cancel{Z_{22}I_{2b}})I_{2a}$$

$$Z_{12}I_{2a}I_{1b} + Z_{21}I_{1a}I_{2b} = Z_{12}I_{2b}I_{1a} + Z_{21}I_{1b}I_{2a}$$

$$(Z_{12} - Z_{21})(I_{2a}I_{1b} - I_{2b}I_{1a}) = 0 \Rightarrow Z_{12} = Z_{21}$$

2. T and Π networks

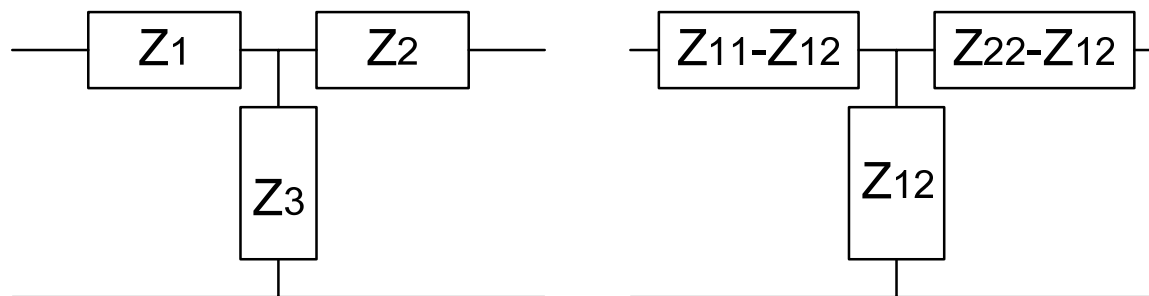



(derivation)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_1 + Z_3, \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_3 = Z_{12}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_2 + Z_3$$
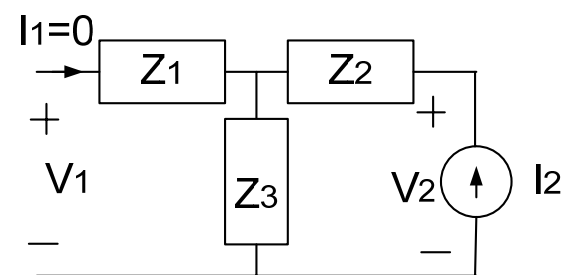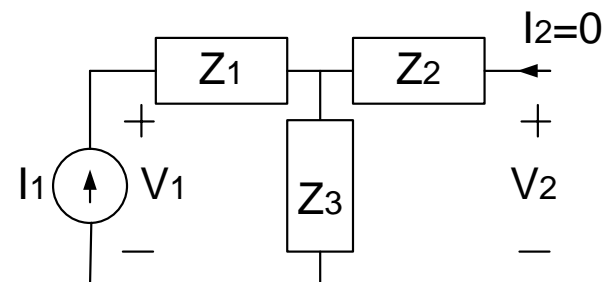
$$\rightarrow Z_3 = Z_{12}, \quad Z_1 = Z_{11} - Z_{12}, \quad Z_2 = Z_{22} - Z_{12}$$



微波電路講義

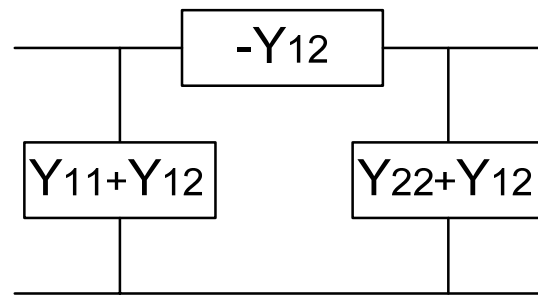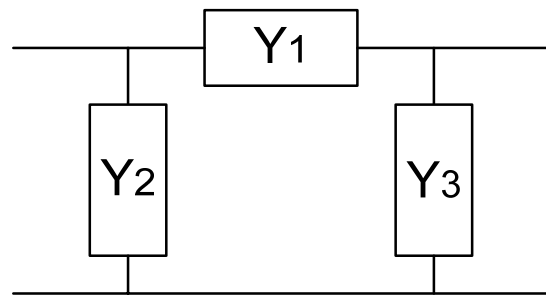



(derivation)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = Y_1 + Y_2, Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -Y_1 = Y_{12}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = Y_1 + Y_3$$
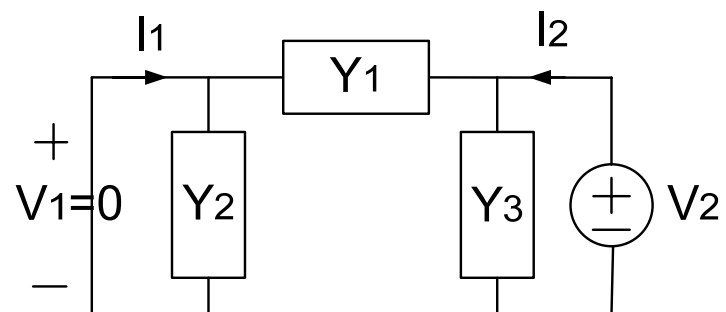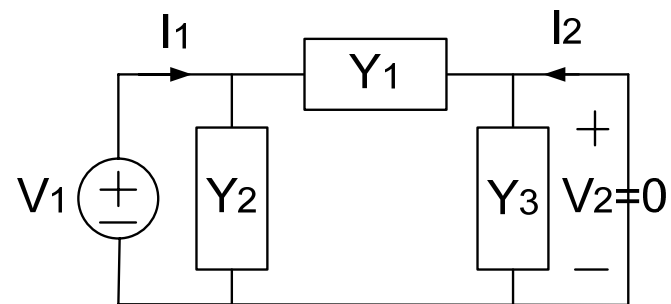
$$\rightarrow Y_1 = -Y_{12}, Y_2 = Y_{11} + Y_{12}, Y_3 = Y_{22} + Y_{12}$$




3. Reciprocal lossless network

$$\operatorname{Re}\{Z_{ij}\} = 0$$

4. Problems to use Z- or Y-matrix in microwave circuits

- 1) difficult in defining voltage and current for non-TEM lines
- 2) no equipment available to measure voltage and current in complex value (eg. sampling scope in microwave range, impedance meter <3GHz)
- 3) difficult to make open and short circuits over broadband
- 4) active devices not stable as terminated with open or short circuit

4.3 The scattering matrix

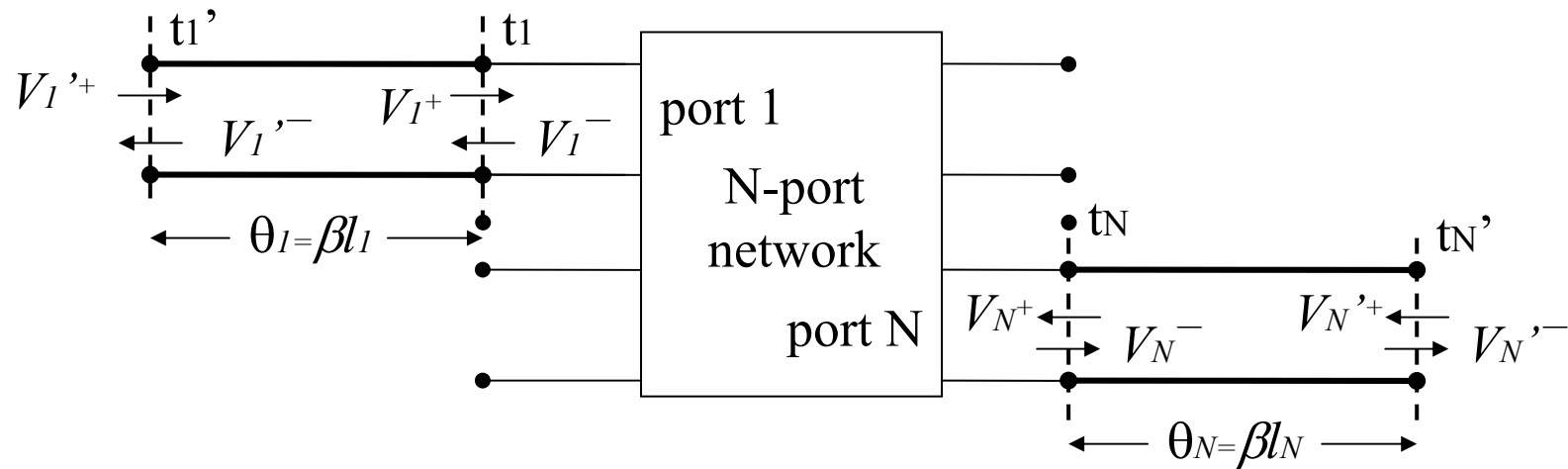

$$[V^-] = [S] [V^+], \quad \begin{bmatrix} V_1^- \\ V_2^- \\ \bullet \\ \bullet \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \bullet & \bullet & S_{1N} \\ S_{21} & \bullet & \bullet & \bullet & S_{2N} \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ \bullet & \bullet & \bullet & \bullet & \bullet \\ S_{N1} & S_{N2} & \bullet & \bullet & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \bullet \\ \bullet \\ V_N^+ \end{bmatrix}, \quad S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0, k \neq j} = \left. \frac{\text{response}_i}{\text{source}_j} \right|_{V_k^+ = 0, k \neq j}$$

Discussion

1. Ex 4.4 a 3dB attenuator

$$Z_{in} = 8.56 + 41.44 = 50$$

$$S_{11} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = 0 = S_{22}$$


$$V_2^- = V_2 = V_1 \frac{41.44}{41.44 + 8.56} \frac{50}{50 + 8.56} = 0.707V_1 = \frac{1}{\sqrt{2}}V_1 = \frac{1}{\sqrt{2}}V_1^+ = S_{21}V_1^+$$

$$\rightarrow [S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & 0 \end{bmatrix} : \text{lossy, reciprocal, symmetric}$$


$$\text{incident power to port 1: } \frac{1}{2} \frac{|V_1^+|^2}{Z_o}$$

$$\text{transmitted power from port 2: } \frac{1}{2} \frac{|V_2^-|^2}{Z_o} = \frac{1}{2} \frac{\left| \frac{1}{\sqrt{2}} V_1^+ \right|^2}{Z_o} = \frac{1}{2} \times \frac{1}{2} \frac{|V_1^+|^2}{Z_o} : 3\text{dB attenuation}$$
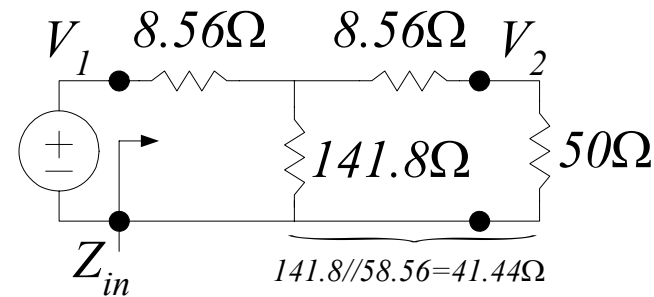
$$\text{attenuator design} \begin{cases} \text{input match} \\ \text{attenuation value} \end{cases} \rightarrow R_1, R_2$$



2. T-type attenuator design

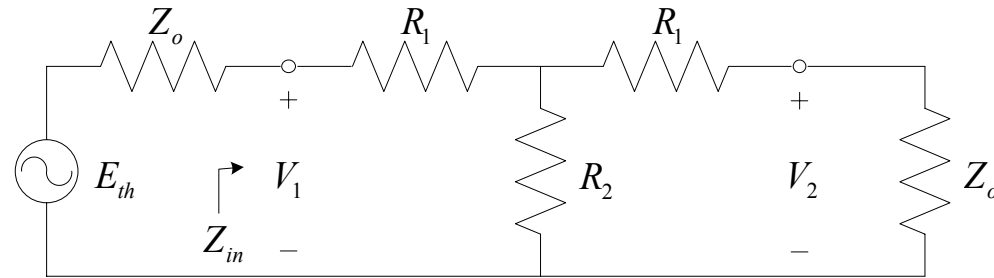

$$\left\{ \begin{array}{l} Z_{in} = (R_1 + Z_o) // R_2 + R_1 = Z_o \\ S_{21} = \frac{V_2}{V_1} = \frac{R_2 // (R_1 + Z_o)}{R_1 + R_2 // (R_1 + Z_o)} \frac{Z_o}{R_1 + Z_o} = \alpha \end{array} \right. \Rightarrow \left\{ \begin{array}{l} R_1 = \frac{1-\alpha}{1+\alpha} Z_o \\ R_2 = \frac{2\alpha}{1-\alpha^2} Z_o \end{array} \right.$$

$$3dB \text{ attenuator } \alpha = \frac{1}{\sqrt{2}} \Rightarrow \left\{ \begin{array}{l} R_1 = \frac{1-\alpha}{1+\alpha} Z_o = \frac{\sqrt{2}-1}{\sqrt{2}+1} Z_o \\ R_2 = \frac{2\alpha}{1-\alpha^2} Z_o = 2\sqrt{2} Z_o \end{array} \right.$$

3. Relation of [Z], [Y], and [S]

$$[S] = ([Z] + [U])^{-1} ([Z] - [U]), \quad [Y] = [Z]^{-1}$$

(*derivation*)

$$\text{Let } Z_{on} = 1, \quad \begin{aligned} V_n &= V_n^+ + V_n^- \\ I_n &= V_n^+ - V_n^- \end{aligned}$$

$$[V] = [Z][I] \rightarrow [V^+] + [V^-] = [Z]([V^+] - [V^-])$$

$$\rightarrow [Z][V^-] + [V^-] = [Z][V^+] - [V^+]$$

$$([Z] + [U])[V^-] = ([Z] - [U])[V^+]$$

$$\because [V^-] = [S][V^+] \rightarrow ([Z] + [U])[S][V^+] = ([Z] - [U])[V^+]$$

$$[S] = ([Z] + [U])^{-1} ([Z] - [U])$$

4. Reciprocal network

$$[S] = [S]^t, \quad [S]: \text{symmetric matrix}$$

(derivation)

$$\text{Let } Z_{on} = 1, \quad \begin{aligned} V_n &= V_n^+ + V_n^- & \rightarrow & V_n^+ = (V_n + I_n) / 2 \\ I_n &= V_n^+ - V_n^- & & V_n^- = (V_n - I_n) / 2 \end{aligned}$$

$$[V^+] = \frac{1}{2}([V] + [I]) = \frac{1}{2}([Z] + [U])[I]$$

$$[V^-] = \frac{1}{2}([V] - [I]) = \frac{1}{2}([Z] - [U])[I]$$

$$[V^-] = ([Z] - [U])([Z] + [U])^{-1} [V^+] \rightarrow [S] = ([Z] - [U])([Z] + [U])^{-1}$$

$$[S]^t = (([Z] + [U])^{-1})^t ([Z] - [U])^t = ([Z] + [U])^{-1} ([Z] - [U]) \stackrel{\text{from 3}}{=} [S]$$

5. Lossless network (unitary property)

$$[S]^t [S]^* = [U], \quad \sum_{k=1}^N S_{ki} S_{kj}^* = \begin{cases} 1 & i = j \\ 0 & i \neq j \end{cases}$$

(derivation)

Let $Z_{on} = 1$

lossless (incident power = emitted power) \rightarrow net averaged input power $\sum_i P_{in,i} = 0$

$$\begin{aligned} P_{in} &= \frac{1}{2} \operatorname{Re}([V]^t [I]^*) = \frac{1}{2} \operatorname{Re}([\mathcal{V}^+] + [\mathcal{V}^-])^t ([\mathcal{V}^+]^* - [\mathcal{V}^-]^*) \\ &= \frac{1}{2} \operatorname{Re}([\mathcal{V}^+]^t [\mathcal{V}^+]^* - [\mathcal{V}^-]^t [\mathcal{V}^-]^* + [\mathcal{V}^-]^t [\mathcal{V}^+]^* - [\mathcal{V}^+]^t [\mathcal{V}^-]^*) = 0 \end{aligned}$$

\swarrow Im

$$[\mathcal{V}^+]^t [\mathcal{V}^+]^* = [\mathcal{V}^-]^t [\mathcal{V}^-]^* \stackrel{[\mathcal{V}^-] = [S][\mathcal{V}^+]}{=} [\mathcal{V}^+]^t [S]^t [S]^* [\mathcal{V}^+]^*$$

$$\rightarrow [S]^t [S]^* = [U]$$

6. Lossy network $\sum_{k=1}^N S_{ki} S_{ki}^* < 1$

7. Ex.4.5

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

$[S]$: not symmetric \rightarrow a non-reciprocal network

$|S_{11}|^2 + |S_{21}|^2 = 0.745 \neq 1 \rightarrow$ a lossy network

port 1 $RL = -20 \log |S_{11}| = 16.5 dB$

port 2 $RL = -20 \log |S_{22}| = 14 dB$

$IL = -20 \log |S_{21}| = 1.4 dB$


port 2 terminated with a matched load $\Gamma_L = 0 \rightarrow$

$$\Gamma_{in} = |S_{11}| = 0.15, RL = -20 \log 0.15 = 16.5 dB$$

port 2 terminated with a short circuit $\Gamma_L = -1 \rightarrow$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = -0.452, RL = 6.9 dB$$

8. Shift property

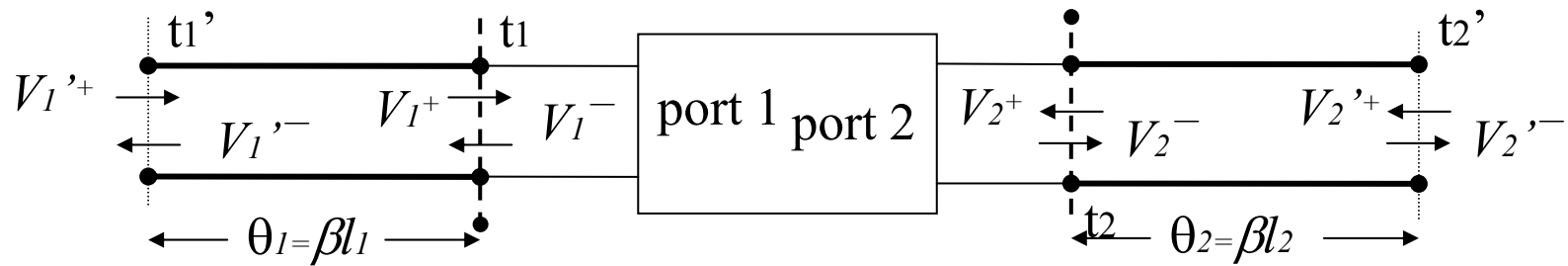

$$S'_{11} = e^{-j2\theta_1} S_{11}, S'_{21} = e^{-j\theta_1} S_{21} e^{-j\theta_2}, S'_{12} = e^{-j\theta_2} S_{12} e^{-j\theta_1}, S'_{22} = e^{-j2\theta_2} S_{22}$$

n-port network: $[S'] = \begin{bmatrix} e^{-j\theta_1} & 0 & \bullet & 0 \\ 0 & e^{-j\theta_2} & \bullet & 0 \\ \bullet & \bullet & \bullet & \bullet \\ 0 & 0 & \bullet & e^{-j\theta_N} \end{bmatrix} [S] \begin{bmatrix} e^{-j\theta_1} & 0 & \bullet & 0 \\ 0 & e^{-j\theta_2} & \bullet & 0 \\ \bullet & \bullet & \bullet & \bullet \\ 0 & 0 & \bullet & e^{-j\theta_N} \end{bmatrix}$

9. S-matrix is not effected by the network arrangement.

10. Generalized S-matrix

$a_i \equiv \frac{V_i^+}{\sqrt{Z_{oi}}}$: incident (power) wave, $b_i \equiv \frac{V_i^-}{\sqrt{Z_{oi}}}$: reflected (power) wave

$$[V^-] = [S][V^+] \Rightarrow [b] = [S][a], S_{ij} = \left. \frac{b_i}{a_j} \right|_{a_k=0, k \neq j} = \left. \frac{V_i^- \sqrt{Z_{oj}}}{V_j^+ \sqrt{Z_{oi}}} \right|_{V_k^+=0, k \neq j}$$

$$P_{in,i} = \frac{1}{2} \operatorname{Re} \{ V_i I_i^* \} = \frac{1}{2} |a_i|^2 - \frac{1}{2} |b_i|^2 = P_{inc,i} - P_{ref,i} = P_{inc,i} (1 - |S_{ii}|^2)$$

(derivation)

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}, b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}, V_i = V_i^+ + V_i^- = \sqrt{Z_{oi}} (a_i + b_i), I_i = \frac{V_i^+ - V_i^-}{Z_{oi}} = \frac{a_i - b_i}{\sqrt{Z_{oi}}} \quad \swarrow \operatorname{Im}$$

$$P_{in,i} = \frac{1}{2} \operatorname{Re} \{ V_i I_i^* \} = \frac{1}{2} \operatorname{Re} \{ (a_i + b_i)(a_i - b_i)^* \} = \frac{1}{2} \operatorname{Re} \{ |a_i|^2 - |b_i|^2 + a_i^* b_i - a_i b_i^* \}$$

$$= \frac{1}{2} |a_i|^2 - \frac{1}{2} |b_i|^2$$

11. Two-port device with its S-matrix

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad : \text{reflection coefficient at port 1 with port 2 matched}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad : \text{forward transmission coefficient with port 2 matched}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad : \text{reverse transmission coefficient with port 1 matched}$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \quad : \text{reflection coefficient at port 2 with port 1 matched}$$

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$b_1 = a_1 S_{11} + a_2 S_{12}$$


$$b_2 = a_1 S_{21} + a_2 S_{22}$$

12. RL and IL

$$RL \text{ at port 1: } -20 \log \left| \frac{b_1}{a_1} \right| = -20 \log |S_{11}|$$


$$IL \text{ from port 1 to port 2: } -20 \log \left| \frac{b_2}{a_1} \right| = -20 \log |S_{21}|$$
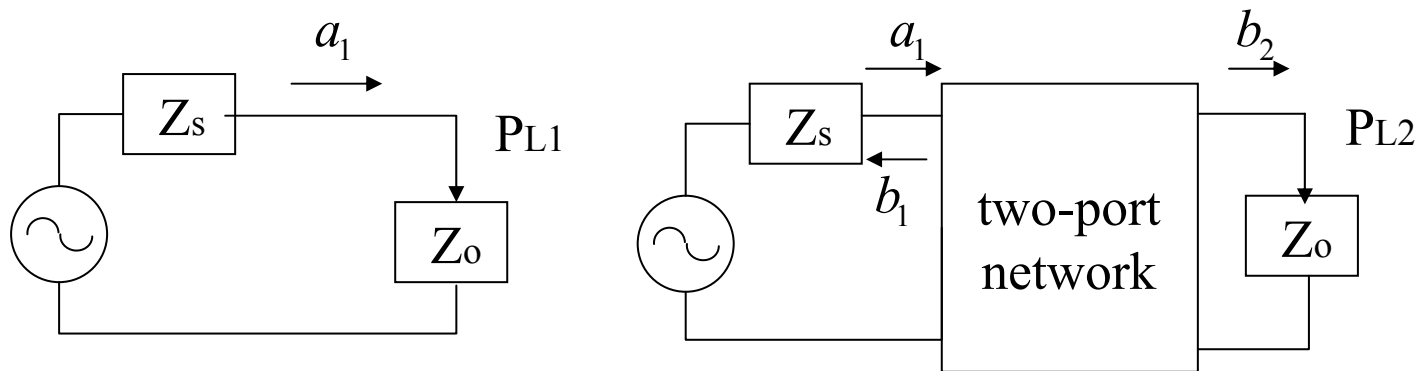
$$\text{insertion loss } IL(dB) \equiv 10 \log \frac{P_{L1}}{P_{L2}}$$



usually $Z_s \neq Z_o$

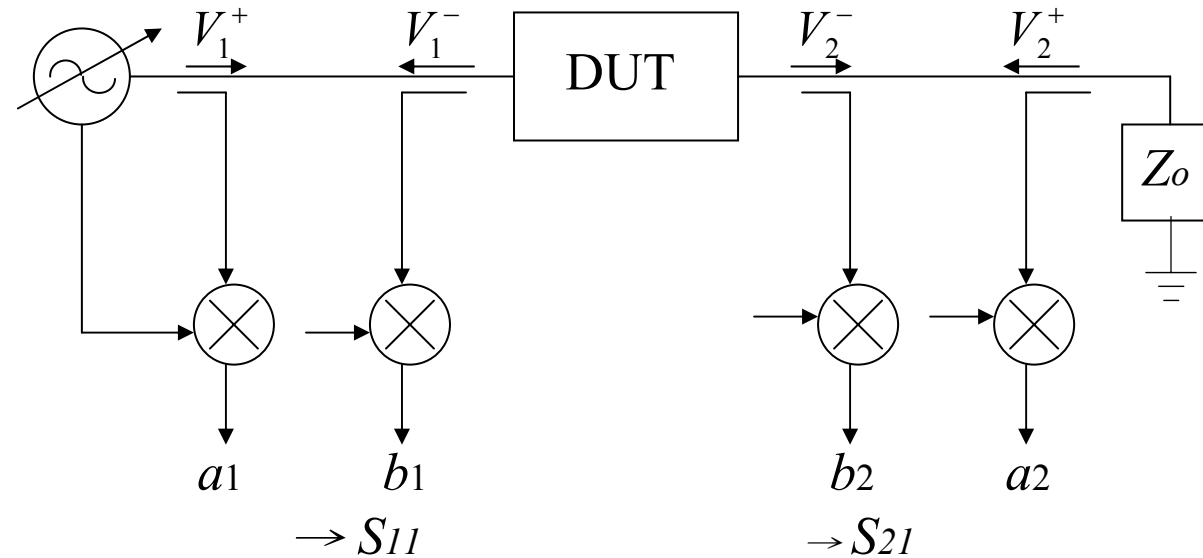13. Two-port S-matrix measurement using VNA



14. Advantages to use S-matrix in microwave circuit

- 1) matched load available in broadband application
- 2) measurable quantity in terms of incident, reflected and transmitted waves
- 3) termination with Z_o causes no oscillation
- 4) convenient in the use of microwave network analysis

15. ADS S-parameter calculation

$$\text{incident power wave } a_i \equiv \frac{V_i + Z_i I_i}{\sqrt{|\operatorname{Re} Z_i|}},$$

$$\text{reflected power wave } b_i \equiv \frac{V_i - Z_i^* I_i}{\sqrt{|\operatorname{Re} Z_i|}}$$

$$\rightarrow \text{power wave reflection coefficient } S_{ii} \equiv \frac{b_i}{a_i} = \frac{V_i - Z_i^* I_i}{V_i + Z_i I_i} = \frac{Z_L - Z_i^*}{Z_L + Z_i}$$

$$\text{power reflection coefficient } |S_{ii}|^2 = \left| \frac{b_i}{a_i} \right|^2 = \left| \frac{Z_L - Z_i^*}{Z_L + Z_i} \right|^2, \text{ conjugate match } Z_L = Z_i^* \rightarrow |S_{ii}|^2 = 0$$



$$P_{in,i} = \frac{1}{2} \operatorname{Re} \{V_i I_i^*\} = \frac{1}{2} (|a_i|^2 - |b_i|^2)$$

⇔ traveling wave along the line with real Z_0

$$a_i = \frac{V_i^+}{\sqrt{Z_{oi}}}, b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}, V_i = V_i^+ + V_i^- = \sqrt{Z_{oi}} (a_i + b_i), I_i = \frac{V_i^+ - V_i^-}{Z_{oi}} = \frac{a_i - b_i}{\sqrt{Z_{oi}}}$$

$$\rightarrow a_i + b_i = \frac{V_i}{\sqrt{Z_{oi}}}, a_i - b_i = I_i \sqrt{Z_{oi}} \rightarrow a_i = \frac{V_i + Z_0 I_i}{\sqrt{Z_0}}, b_i = \frac{V_i - Z_0 I_i}{\sqrt{Z_0}}$$

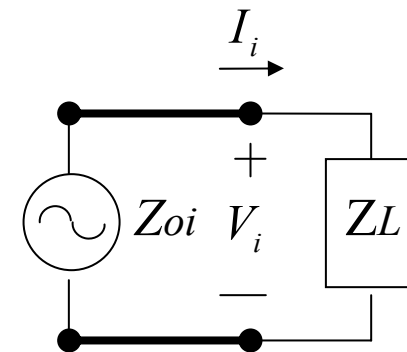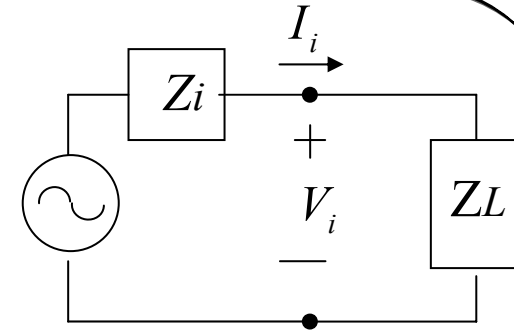
$$S_{ii} = \frac{b_i}{a_i} = \frac{V_i - Z_0 I_i}{V_i + Z_0 I_i} = \frac{Z_L - Z_0}{Z_L + Z_0}, \text{ impedance match } Z_L = Z_0 \rightarrow S_{ii} = 0$$



微波電路講義

4.4 The transmission (ABCD) matrix

- Cascade network

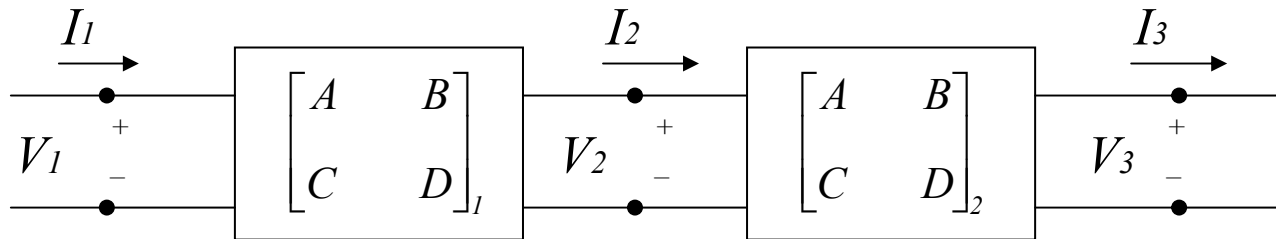

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \begin{bmatrix} A & B \\ C & D \end{bmatrix}_2 \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Discussion

1. ABCD matrix of two-port circuits (p.185, Table 4.1)
2. Reciprocal network $AD-BC=1$
3. S-, Z-, Y-, ABCD-matrix relation of 2-port network (p.187, Table 4.2)
4. Ex. 4.6

(derivation) Z (ABCD)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}, \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{AV_2}{CV_2} = \frac{A}{C}$$

$$Z_{12} = \left. \frac{V_1}{-I_2} \right|_{I_1=0} = \left. \frac{AV_2 + BI_2}{-I_2} \right|_{I_1=0} = -A \left. \frac{V_2}{I_2} \right|_{I_1=0} - B, I_1 = 0 = CV_2 + DI_2 \rightarrow -\frac{V_2}{I_2} = \frac{D}{C}$$

$$= -A\left(-\frac{D}{C}\right) - B = \frac{AD - BC}{C}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \left. \frac{V_2}{CV_2 + DI_2} \right|_{I_2=0} = \frac{1}{C}$$

$$Z_{22} = \left. -\frac{V_2}{I_2} \right|_{I_1=0} = \frac{D}{C}, \because I_1 = 0 = CV_2 + DI_2$$

symmetrical network

$$Z_{11} = Z_{22} \rightarrow A = D$$

reciprocal network

$$Z_{12} = Z_{21}$$


$$\frac{AD - BC}{C} = \frac{1}{C} \rightarrow AD - BC = 1$$

(derivation) S (ABCD)

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}, \begin{matrix} V_1 = V_1^+ + V_1^- \\ I_1 = (V_1^+ - V_1^-)/Z_o \end{matrix} \rightarrow \begin{matrix} V_1^+ = (V_1 + Z_o I_1)/2 \\ V_1^- = (V_1 - Z_o I_1)/2 \end{matrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \left. \frac{V_1 - Z_o I_1}{V_1 + Z_o I_1} \right|_{V_2^+=0} = \left. \frac{AV_2 + BI_2 - Z_o CV_2 - Z_o DI_2}{AV_2 + BI_2 + Z_o CV_2 + Z_o DI_2} \right|_{V_2^+=0}$$
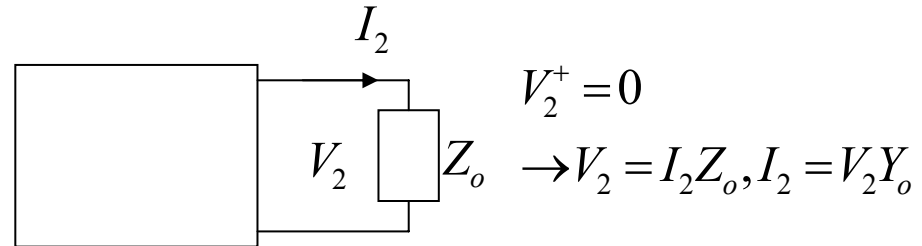
$$= \frac{A + BY_o - CZ_o - D}{A + BY_o + CZ_o + D}$$



$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0} \stackrel{V_2^-=V_2}{=} \frac{V_2}{(V_1 + Z_o I_1)/2} = \frac{2V_2}{AV_2 + BI_2 + Z_o CV_2 + Z_o DI_2}$$


$$\stackrel{I_2 = V_2 Y_o}{=} \frac{2}{A + BY_o + CZ_o + D}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+=0}, \quad \begin{matrix} V_2 = V_2^+ + V_2^- \\ -I_2 = (V_2^+ - V_2^-)/Z_o \end{matrix} \rightarrow \begin{matrix} V_2^+ = (V_2 - Z_o I_2)/2 \\ V_2^- = (V_2 + Z_o I_2)/2 \end{matrix}$$

$$V_1^- = V_1 = \frac{V_1}{(V_2 - Z_o I_2)/2}, \quad \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}, \quad \Delta = AD - BC$$

$$= \frac{2V_1}{(DV_1 - BI_1 + Z_o CV_1 - Z_o AI_1)/\Delta} = \frac{2\Delta V_1}{DV_1 + BY_o V_1 + CZ_o V_1 + AV_1}$$
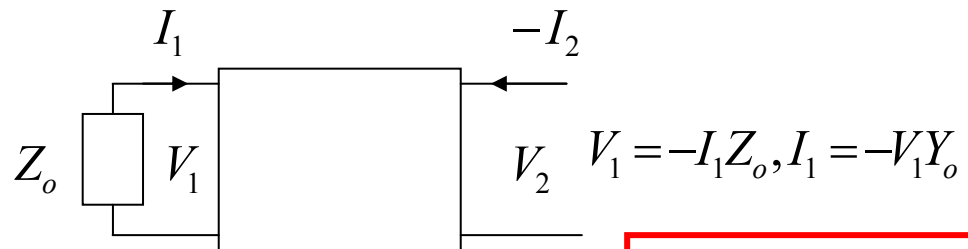
$$= \frac{2\Delta}{A + BY_o + CZ_o + D}$$




$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+=0} = \frac{V_2 + Z_o I_2}{V_2 - Z_o I_2} = \frac{DV_1 - BI_1 + Z_o(-CV_1 + AI_1)}{DV_1 - BI_1 - Z_o(-CV_1 + AI_1)}$$

$$\stackrel{I_1 = -V_1 Y_o}{=} \frac{DV_1 + BY_o V_1 + Z_o(-CV_1 + AY_o V_1)}{DV_1 + BY_o V_1 - Z_o(-CV_1 + AY_o V_1)} = \frac{-A + BY_o - CZ_o + D}{A + BY_o + CZ_o + D}$$

symmetrical
 $S_{11} = S_{22}, A = D$
 reciprocal
 $S_{12} = S_{21}, \Delta = 1$


5. Example

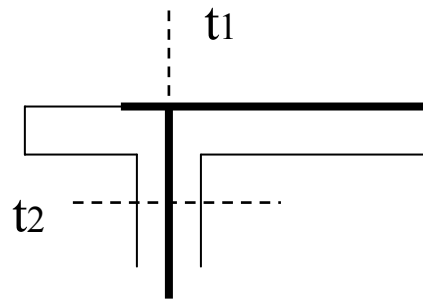

coaxial-microstrip transition
(a linear circuit)




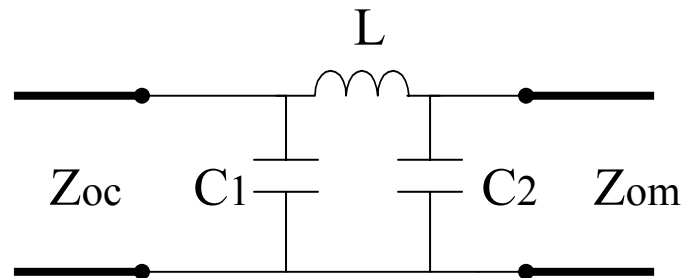
[S] representation can be obtained from
measurement or calculation.



one possible equivalent circuit

4.5 Signal flow graphs

- 2-port representation

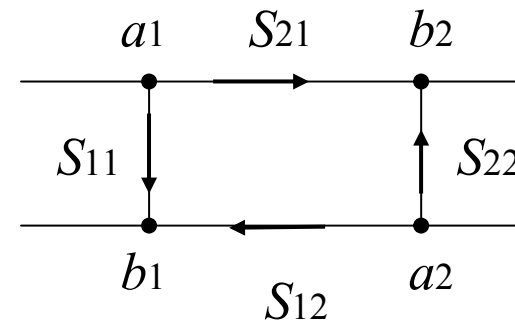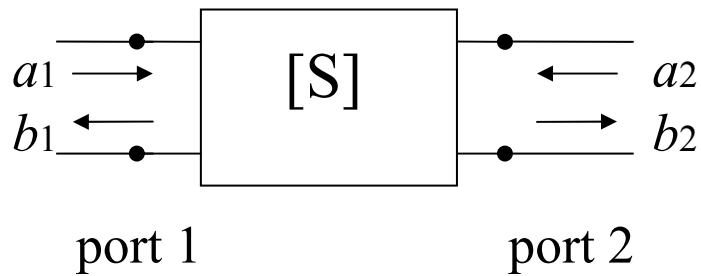

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$b_1 = a_1 S_{11} + a_2 S_{12}$$


$$b_2 = a_1 S_{21} + a_2 S_{22}$$

$$RL \text{ at port 1: } -20 \log \left| \frac{b_1}{a_1} \right| = -20 \log |S_{11}|$$


$$IL \text{ from port 1 to port 2: } -20 \log \left| \frac{b_2}{a_1} \right| = -20 \log |S_{21}|$$

Discussion



1. Source representation

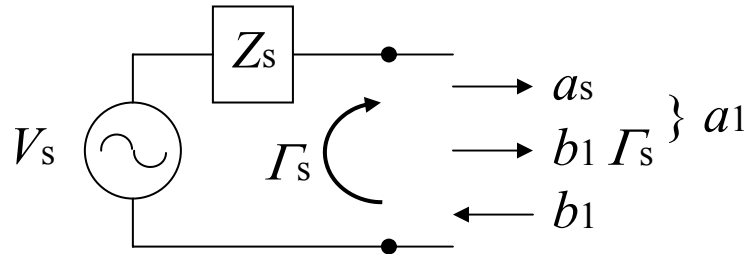
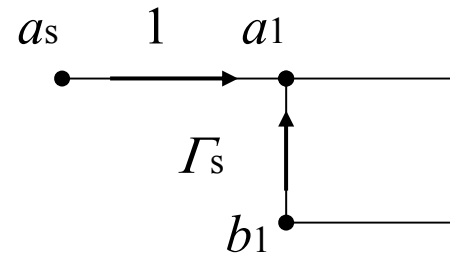
$$e_s = V_s \frac{Z_o}{Z_o + Z_s}, a_s \equiv \frac{e_s}{\sqrt{Z_o}}$$





2. Load representation

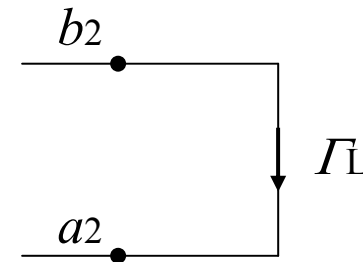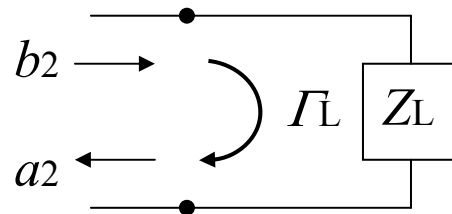

3. Series, parallel, self-loop, splitting rules (p.191, Fig.4.16)

4. 2-port circuit representation

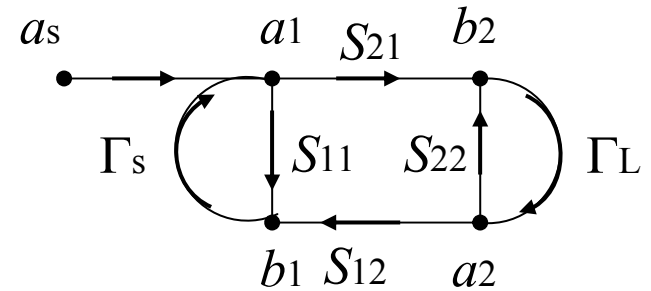
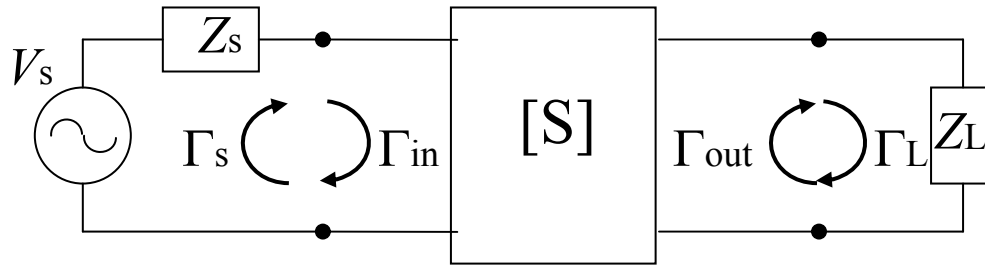


$$b_1 = a_1 S_{11} + a_1 S_{21} \Gamma_L S_{12} (1 + S_{22} \Gamma_L + \dots) = a_1 S_{11} + a_1 \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\rightarrow \Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$


$$b_2 = a_2 S_{22} + a_2 S_{12} \Gamma_s S_{21} (1 + S_{11} \Gamma_s + \dots) = a_2 S_{22} + a_2 \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s}$$
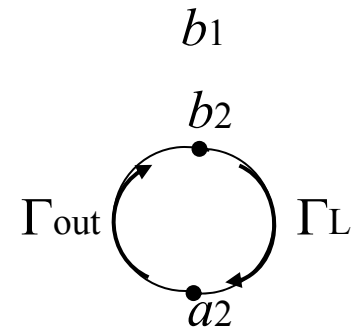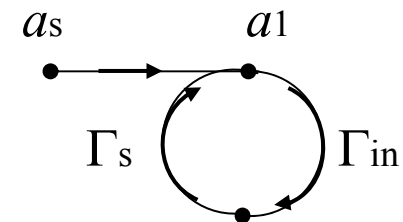
$$\Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s}$$



微波電路講義

5. TRL (Thru-Reflect-Line) calibration

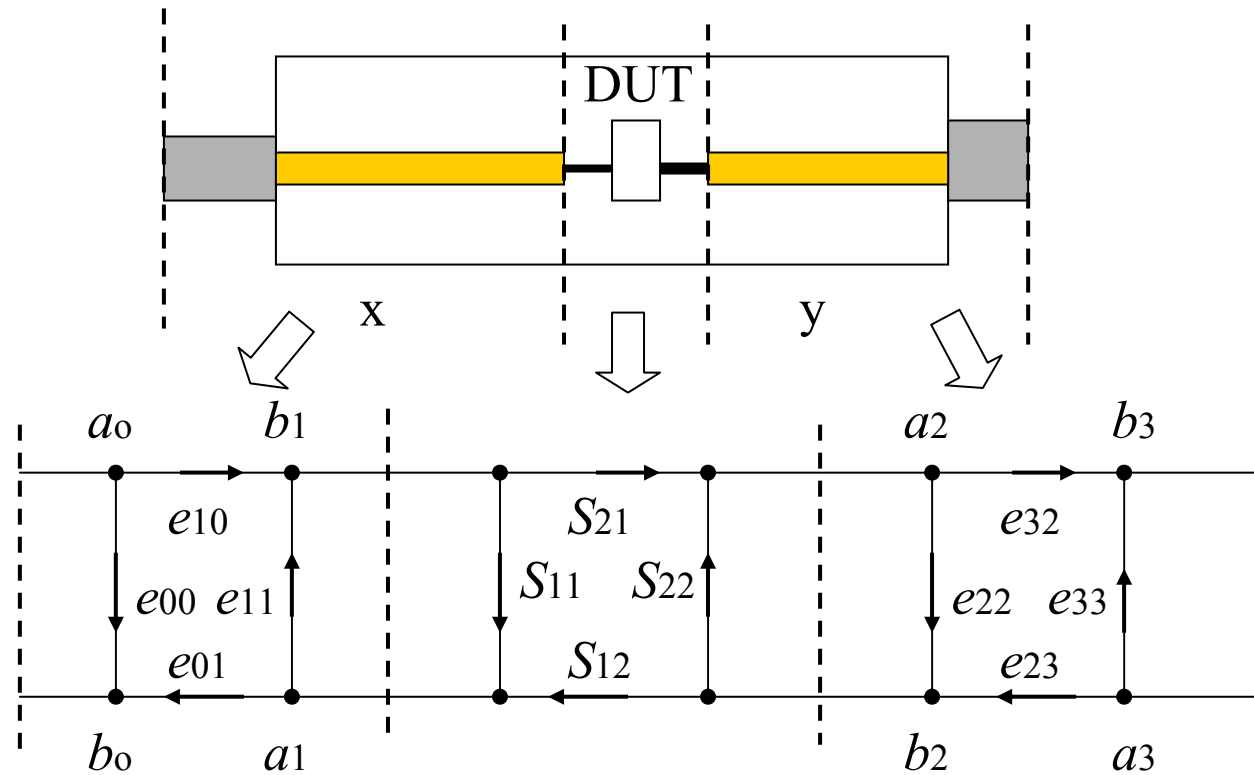

6 unknowns to be solved


T: Through \rightarrow 3 eqs., R: Reflection \rightarrow 2 eqs., L: Line \rightarrow 3 eqs.

\Rightarrow R (Γ) and line length (γl) can be unknown

Calibrators


T: Through

→ 3 eqs.

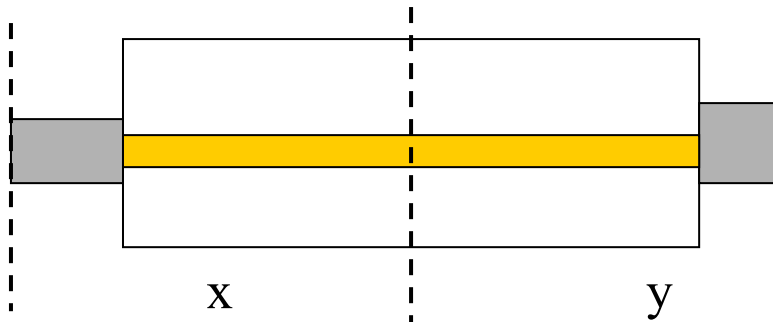


R: Reflection

→ 2 eqs.

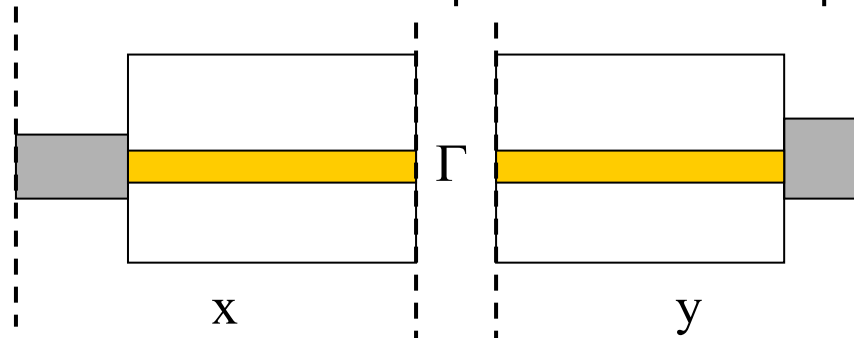

L: Line

→ 3 eqs.

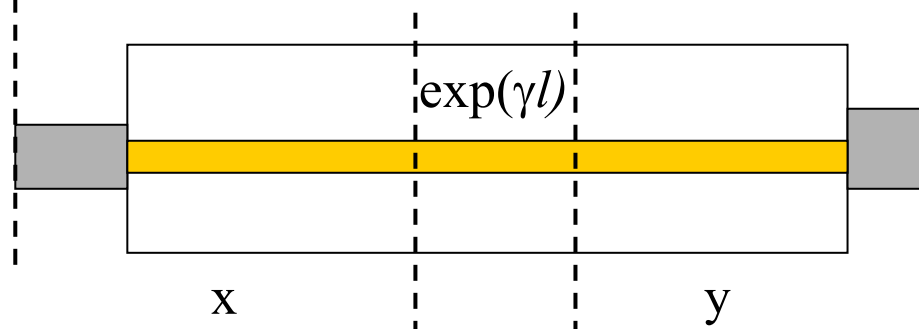

Requirement: connectors and line have same characteristics for 3 calibrators

Limitation: operation bandwidth $20^\circ \leq \beta l \leq 340^\circ$

R – matrix (wave cascade matrix)

$$\begin{bmatrix} b_1 \\ a_1 \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} a_2 \\ b_2 \end{bmatrix}$$

$$[R] = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} = \frac{1}{S_{21}} \begin{bmatrix} S_{12}S_{21} - S_{11}S_{22} & S_{11} \\ -S_{22} & 1 \end{bmatrix}$$

error matrices $[R_x] = \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix}$, $[R_y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

Through: $[S_T] = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \rightarrow [R_T] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$

Line: $[S_L] = \begin{bmatrix} 0 & e^{-\gamma l} \\ e^{-\gamma l} & 0 \end{bmatrix} \rightarrow [R_L] = \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix}$ Reflection: Γ

Thru measurement: $[R_{mT}] = [R_x] [R_T] [R_y] = [R_x] [R_y]$

Line measurement: $[R_{mL}] = [R_x] [R_L] [R_y]$

$$\Rightarrow [M] [R_x] = [R_x] [R_L], \quad [M] \equiv [R_{mL}] [R_{mT}]^{-1} \quad \Rightarrow \quad e_{00}, \frac{e_{01}e_{10}}{e_{11}}$$

$$[R_y] [N] = [R_L] [R_y], \quad [N] \equiv [R_{mT}]^{-1} [R_{mL}] \quad \Rightarrow \quad e_{33}, \frac{e_{23}e_{32}}{e_{22}}$$

reflection measurement at port 1 $\Gamma_{mx} = e_{00} + \frac{e_{10}e_{01}\Gamma}{1 - e_{11}\Gamma}$

reflection measurement at port 2 $\Gamma_{my} = e_{33} + \frac{e_{23}e_{32}\Gamma}{1 - e_{22}\Gamma}$

$$\left. \begin{array}{l} \Gamma_{mx} \\ \Gamma_{my} \\ \Gamma_{mT} \end{array} \right\} \Rightarrow e_{11}, e_{22}, e_{10}e_{01}, e_{23}e_{32} \quad \left. \begin{array}{l} S_{21mT} \\ S_{12mT} \end{array} \right\} \Rightarrow e_{10}e_{32}, e_{23}e_{01}$$

$$\Rightarrow e_{10}, e_{01}, e_{23}, e_{32}$$

$$\Rightarrow \Gamma, e^{-\gamma l}$$

(detailed derivation)

$$[M][R_x] = [R_x][R_L] \rightarrow \begin{bmatrix} m_{11} & m_{12} \\ m_{21} & m_{22} \end{bmatrix} \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix} = \begin{bmatrix} x_{11} & x_{12} \\ x_{21} & x_{22} \end{bmatrix} \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix}$$

$$\rightarrow \begin{cases} m_{11}x_{11} + m_{12}x_{21} = x_{11}e^{-\gamma l} \\ m_{21}x_{11} + m_{22}x_{21} = x_{21}e^{-\gamma l} \\ m_{11}x_{12} + m_{12}x_{22} = x_{12}/e^{-\gamma l} \\ m_{21}x_{12} + m_{22}x_{22} = x_{22}/e^{-\gamma l} \end{cases} \rightarrow \begin{cases} m_{21}\left(\frac{x_{11}}{x_{21}}\right)^2 + (m_{22} - m_{11})\frac{x_{11}}{x_{21}} - m_{12} = 0 \\ m_{21}\left(\frac{x_{12}}{x_{22}}\right)^2 + (m_{22} - m_{11})\frac{x_{12}}{x_{22}} - m_{12} = 0 \end{cases} \rightarrow \begin{cases} \frac{x_{11}}{x_{21}} = e_{00} - \frac{e_{10}e_{01}}{e_{11}} \\ \frac{x_{12}}{x_{22}} = e_{00} \end{cases}$$

$$[R_y][N] = [R_L][R_y] \rightarrow \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} n_{11} & n_{12} \\ n_{21} & n_{22} \end{bmatrix} = \begin{bmatrix} e^{-\gamma l} & 0 \\ 0 & 1/e^{-\gamma l} \end{bmatrix} \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$\rightarrow \begin{cases} y_{11}n_{11} + y_{12}n_{21} = y_{11}e^{-\gamma l} \\ y_{21}n_{11} + y_{22}n_{21} = y_{21}e^{-\gamma l} \\ y_{11}n_{12} + y_{12}n_{22} = y_{12}/e^{-\gamma l} \\ y_{21}n_{12} + y_{22}n_{22} = y_{22}/e^{-\gamma l} \end{cases} \rightarrow \begin{cases} n_{21}\left(\frac{y_{11}}{y_{12}}\right)^2 + (n_{22} - n_{11})\frac{y_{11}}{y_{12}} - n_{12} = 0 \\ n_{21}\left(\frac{y_{21}}{y_{22}}\right)^2 + (n_{22} - n_{11})\frac{y_{21}}{y_{22}} - n_{21} = 0 \end{cases} \rightarrow \begin{cases} \frac{y_{11}}{y_{12}} = -e_{33} + \frac{e_{23}e_{32}}{e_{22}} \\ \frac{y_{21}}{y_{22}} = -e_{33} \end{cases}$$

$$\left\{ \begin{array}{l} \Gamma_{mx} = e_{00} + \frac{e_{10}e_{01}\Gamma}{1-e_{11}\Gamma} \rightarrow \Gamma = \frac{1}{e_{11}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}}, (b = e_{00}, a = e_{00} - \frac{e_{10}e_{01}}{e_{11}}) \\ \Gamma_{my} = e_{33} + \frac{e_{23}e_{32}\Gamma}{1-e_{22}\Gamma} \rightarrow \Gamma = \frac{1}{e_{22}} \frac{d + \Gamma_{mx}}{c + \Gamma_{mx}}, (d = -e_{33}, c = -e_{33} + \frac{e_{23}e_{32}}{e_{22}}) \\ \Gamma_{mT} = e_{00} + \frac{e_{10}e_{01}e_{22}}{1-e_{11}e_{22}} \rightarrow e_{11} = \frac{1}{e_{22}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \end{array} \right.$$

$$\Rightarrow e_{11}^2 = \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \frac{c + \Gamma_{mx}}{d + \Gamma_{mx}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}}, e_{22} = \frac{1}{e_{11}} \frac{b - \Gamma_{mT}}{a - \Gamma_{mT}}, e_{10}e_{01} = (b - a)e_{11}, e_{23}e_{32} = (c - d)e_{11}$$

$$\left\{ \begin{array}{l} S_{21mT} = \frac{e_{10}e_{32}}{1 - e_{11}e_{22}} \\ S_{12mT} = \frac{e_{23}e_{01}}{1 - e_{11}e_{22}} \end{array} \right. \Rightarrow e_{10}e_{32} = S_{21mT}(1 - e_{11}e_{22}), e_{23}e_{01} = S_{12mT}(1 - e_{11}e_{22}) \Rightarrow e_{10}, e_{01}, e_{23}, e_{32}$$

$$\Rightarrow \Gamma = \frac{1}{e_{11}} \frac{b - \Gamma_{mx}}{a - \Gamma_{mx}} \dots (\text{also for } e_{11} \text{ selection}), e^{-\gamma l} = m_{11} + \frac{m_{12}}{a}$$

4.6 Discontinuities and modal analysis

- equivalent circuit components


$$\Delta E \Rightarrow C, \quad \Delta H \Rightarrow L$$



constant E (V) \Rightarrow parallel connection

constant H (I) \Rightarrow serial connection


Discussion

1. Microstrip discontinuities

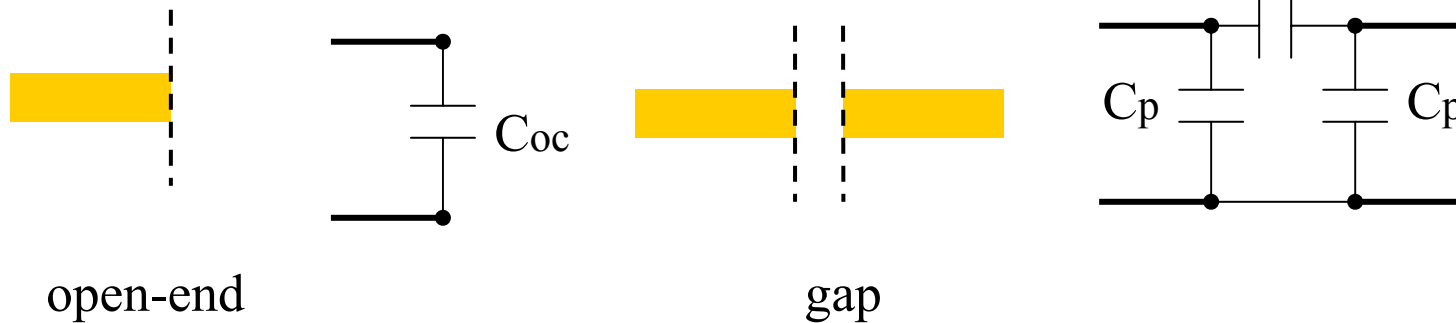


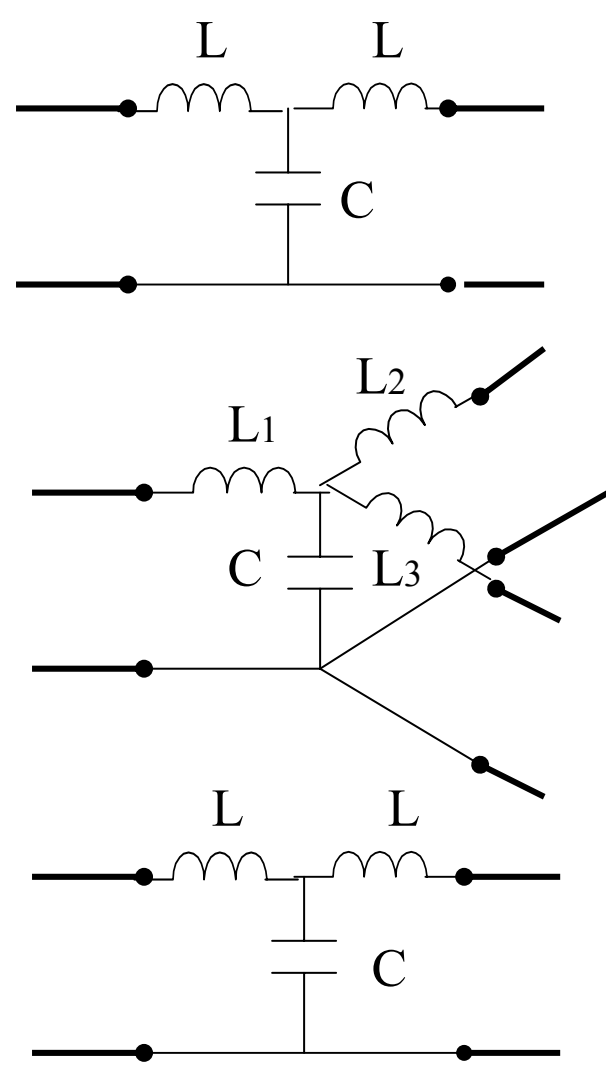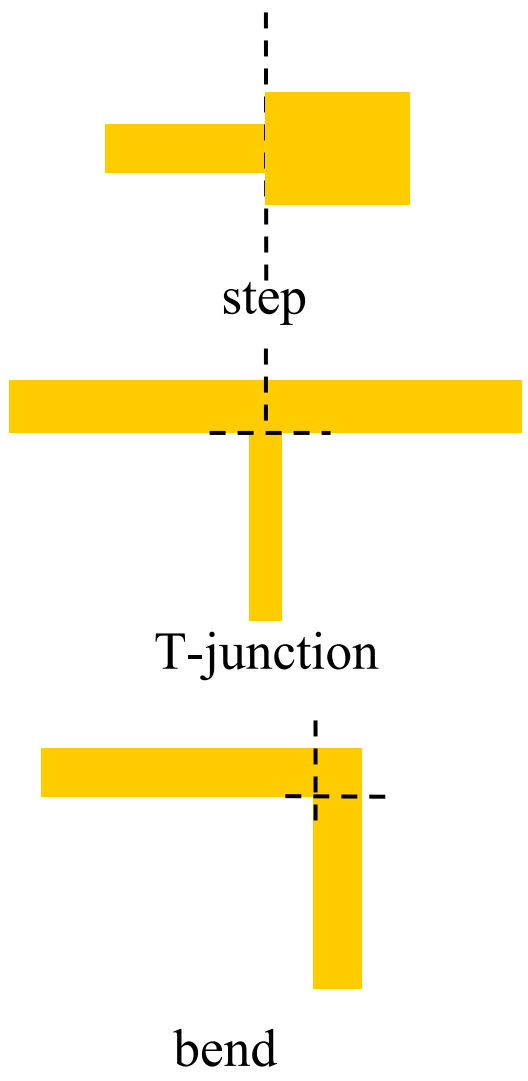

2. Microstrip discontinuity compensation

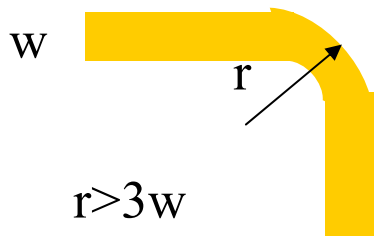

swept bend

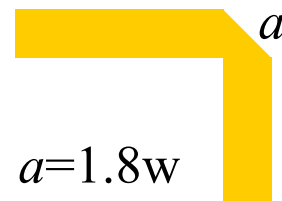

mitered bends




mitered step



mitered T-junction

Solved Problems


Prob. 4.10 Find [S] relative to Z_0

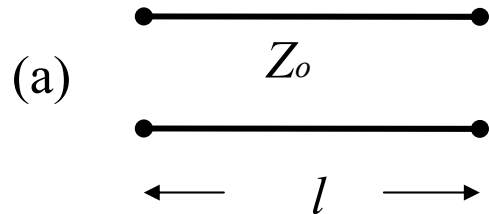


$$S_{11} = S_{22} = 0$$

$$S_{12} = S_{21} = e^{-j\beta l}$$

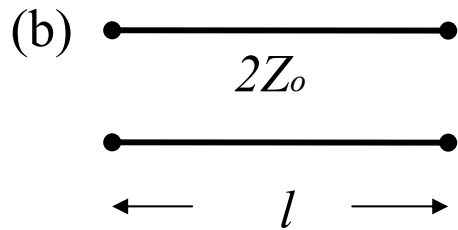
$$Z_{in} = \frac{V_1}{I_1} = \frac{V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l}}{\frac{1}{2Z_0} (V_o^+ e^{j\beta l} - V_o^- e^{-j\beta l})} = 2Z_0 \frac{1 + \Gamma(0)e^{-j2\beta l}}{1 - \Gamma(0)e^{-j2\beta l}}$$


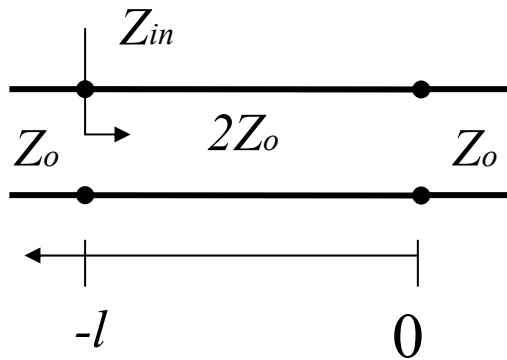
$$\Gamma(0) = \frac{Z_0 - 2Z_0}{Z_0 + 2Z_0} = -\frac{1}{3}$$


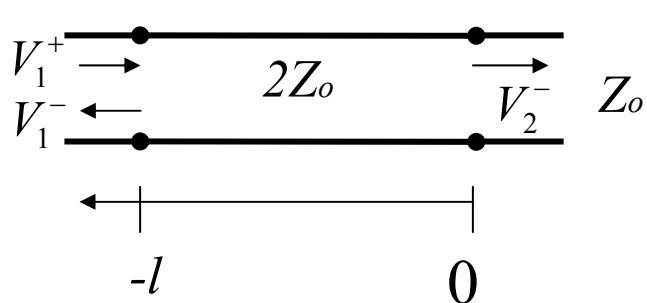
$$S_{11} = S_{22} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{2 \frac{1 - \frac{1}{3} e^{-j2\beta l}}{1 + \frac{1}{3} e^{-j2\beta l}} - 1}{2 \frac{1 - \frac{1}{3} e^{-j2\beta l}}{1 + \frac{1}{3} e^{-j2\beta l}} + 1} = \frac{1 - e^{-j2\beta l}}{3 - \frac{1}{3} e^{-j2\beta l}}$$



$$V_1 = V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l}, \frac{V_o^-}{V_o^+} = \Gamma(0) = -\frac{1}{3}$$

$$= V_1^+ + V_1^- = V_1^+ (1 + S_{11})$$


$$V_2 = V_o^+ + V_o^- = V_o^+ (1 + \Gamma(0))$$

$$= V_2^-$$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{V_o^+ (1 - \frac{1}{3})}{V_o^+ (e^{j\beta l} - \frac{1}{3} e^{-j\beta l})} = \frac{\frac{2}{3} (1 + \frac{1 - e^{-j2\beta l}}{3 - \frac{1}{3} e^{-j2\beta l}})}{e^{j\beta l} - \frac{1}{3} e^{-j\beta l}} = \frac{\frac{2}{3} \frac{4 - \frac{4}{3} e^{-j2\beta l}}{3 - \frac{1}{3} e^{-j2\beta l}}}{e^{j\beta l} - \frac{1}{3} e^{-j\beta l}}$$

$$= \frac{8}{3} \frac{1 - \frac{1}{3} e^{-j2\beta l}}{3 - \frac{1}{3} e^{-j2\beta l}} \frac{1}{e^{j\beta l} - \frac{1}{3} e^{-j\beta l}} = \frac{8}{3} \frac{e^{j\beta l}}{3 - \frac{1}{3} e^{-j2\beta l}}$$

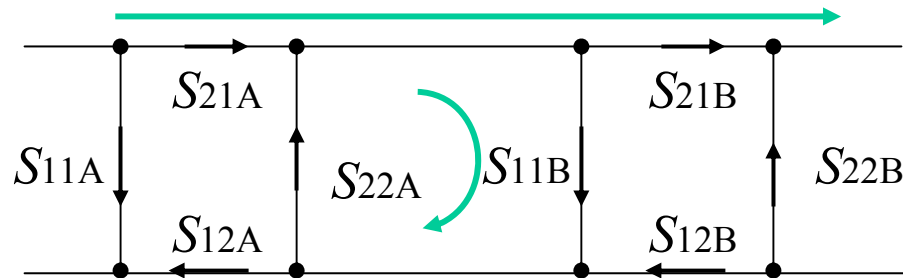Prob. 4.11 Find S_{21} of $[S_A]$ in cascade of $[S_B]$



$$S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$$

Prob. 4.16

$$\begin{bmatrix} 0.1 \angle 90^\circ & 0.8 \angle -45^\circ & 0.3 \angle -45^\circ & 0 \\ 0.8 \angle -45^\circ & 0 & 0 & 0.4 \angle 45^\circ \\ 0.3 \angle -45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.4 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

(1) $|S_{12}|^2 + |S_{42}|^2 = 0.8 \neq 1 \rightarrow \text{lossy}$

(2) $[S]$ symmetric $\rightarrow \text{reciprocal}$

(3) return loss at port 1 = $-20 \log |S_{11}| = -20 \log 0.1 = 20 \text{ dB}$

(4) insertion loss between port 2 and port 4 = $-20 \log |S_{24}| = -20 \log 0.4 = 8 \text{ dB}$

phase delay between port 2 and port 4 = 45°

(5) Reflection at port 1 as port 3 is connected to a short circuit


$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} 0.1\angle 90^\circ & 0.8\angle -45^\circ & 0.3\angle -45^\circ & 0 \\ 0.8\angle -45^\circ & 0 & 0 & 0.4\angle 45^\circ \\ 0.3\angle -45^\circ & 0 & 0 & 0.6\angle -45^\circ \\ 0 & 0.4\angle 45^\circ & 0.6\angle -45^\circ & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ 0 \\ -b_3 \\ 0 \end{bmatrix}$$

$$b_3 = 0.3\angle -45^\circ a_1$$

$$b_1 = 0.1\angle 90^\circ a_1 - 0.3\angle -45^\circ b_3 = 0.1\angle 90^\circ a_1 - 0.09\angle -90^\circ a_1$$

$$S_{11} = \frac{b_1}{a_1} = 0.09j + 0.1j = 0.19j$$

Prob. 4.18 find [S] of the junction

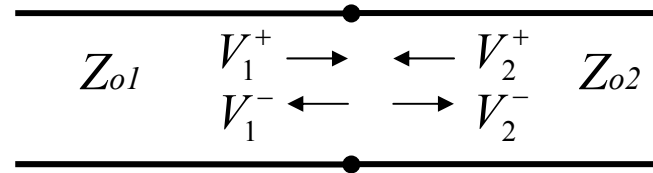

$$S_{11} = \frac{V_1^- / \sqrt{Z_{o1}}}{V_1^+ / \sqrt{Z_{o1}}} = \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}}, S_{22} = \frac{V_2^- / \sqrt{Z_{o2}}}{V_2^+ / \sqrt{Z_{o2}}} = \frac{Z_{o1} - Z_{o2}}{Z_{o1} + Z_{o2}}$$



$$S_{21} = \frac{V_2^- / \sqrt{Z_{o2}}}{V_1^+ / \sqrt{Z_{o1}}} = \frac{2Z_{o2}}{Z_{o1} + Z_{o2}} \frac{\sqrt{Z_{o1}}}{\sqrt{Z_{o2}}} = \frac{2\sqrt{Z_{o1}Z_{o2}}}{Z_{o1} + Z_{o2}} \quad (\text{p.63 (2.51)?)}$$

$$\because V_1^+ + V_1^- = V_2^- \rightarrow \frac{V_2^-}{V_1^+} = 1 + S_{11} = 1 + \frac{Z_{o2} - Z_{o1}}{Z_{o2} + Z_{o1}} = \frac{2Z_{o2}}{Z_{o1} + Z_{o2}}$$

$$S_{12} = \frac{V_1^- / \sqrt{Z_{o1}}}{V_2^+ / \sqrt{Z_{o2}}} = \frac{2Z_{o1}}{Z_{o1} + Z_{o2}} \frac{\sqrt{Z_{o2}}}{\sqrt{Z_{o1}}} = \frac{2\sqrt{Z_{o1}Z_{o2}}}{Z_{o1} + Z_{o2}} = S_{21}$$

$$\because V_2^+ + V_2^- = V_1^- \rightarrow \frac{V_1^-}{V_2^+} = 1 + S_{22} = 1 + \frac{Z_{o1} - Z_{o2}}{Z_{o1} + Z_{o2}} = \frac{2Z_{o1}}{Z_{o1} + Z_{o2}}$$

Prob. 4.30 find P_2/P_1 and P_3/P_1

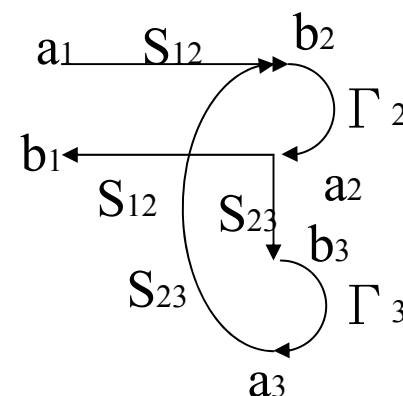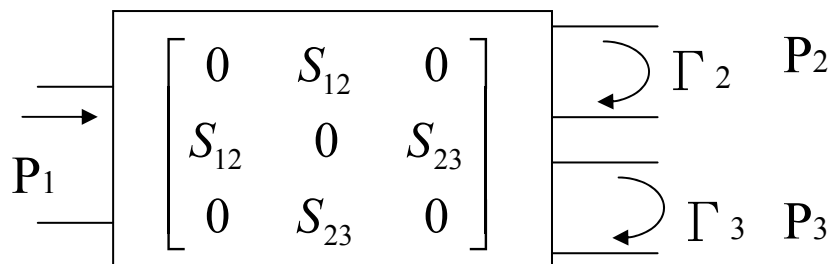

$$b_1 = a_1 \frac{S_{12}^2 \Gamma_2}{1 - \Gamma_2 \Gamma_3 S_{23}^2} = a_1 \Gamma_{in}, b_2 = a_1 \frac{S_{12}}{1 - \Gamma_2 \Gamma_3 S_{23}^2}, b_3 = a_1 \frac{S_{12} \Gamma_2 S_{23}}{1 - \Gamma_2 \Gamma_3 S_{23}^2}$$

$$\frac{P_2}{P_1} = \frac{|b_2|^2 - |a_2|^2}{|a_1|^2 - |b_1|^2} = \frac{|b_2|^2 (1 - |\Gamma_2|^2)}{|a_1|^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 \left(1 - \frac{|S_{12}^2 \Gamma_2|^2}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2}\right)} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 - |S_{12}^2 \Gamma_2|^2}$$

$$\frac{P_3}{P_1} = \frac{|b_3|^2 - |a_3|^2}{|a_1|^2 - |b_1|^2} = \frac{|b_3|^2 (1 - |\Gamma_3|^2)}{|a_1|^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 |\Gamma_2|^2 |S_{23}|^2 (1 - |\Gamma_3|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 \left(1 - \frac{|S_{12}^2 \Gamma_2|^2}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2}\right)} = \frac{|S_{12}|^2 |\Gamma_2|^2 |S_{23}|^2 (1 - |\Gamma_3|^2)}{|1 - \Gamma_2 \Gamma_3 S_{23}^2|^2 - |S_{12}^2 \Gamma_2|^2}$$

Suggested homework (due 2 weeks): 9, 21, 25, 28, 29

ADS examples: Ch4_prj