

Chapter 7 Power dividers and directional couplers

- 7.1 Basic properties of dividers and couplers
three-port network (T-junction), four-port network
(directional coupler), directivity measurement
- 7.2 The T-junction power divider
lossless divider, lossy divider
- 7.3 The Wilkinson power divider
even-odd mode analysis, unequal power division divider,
n-way Wilkinson divider
- 7.5 The quadrature (90°) hybrid
branch-line coupler
- 7.6 Coupled line directional couplers
even- and odd-mode Z_o , single-section and multisection
coupled line couplers

7.7 The Lange coupler

7.8 The 180° hybrid


rat-race hybrid, tapered coupled line hybrid

7.9 Other couplers

reflectometer

7.1 Basic properties of dividers and couplers

- N-port network

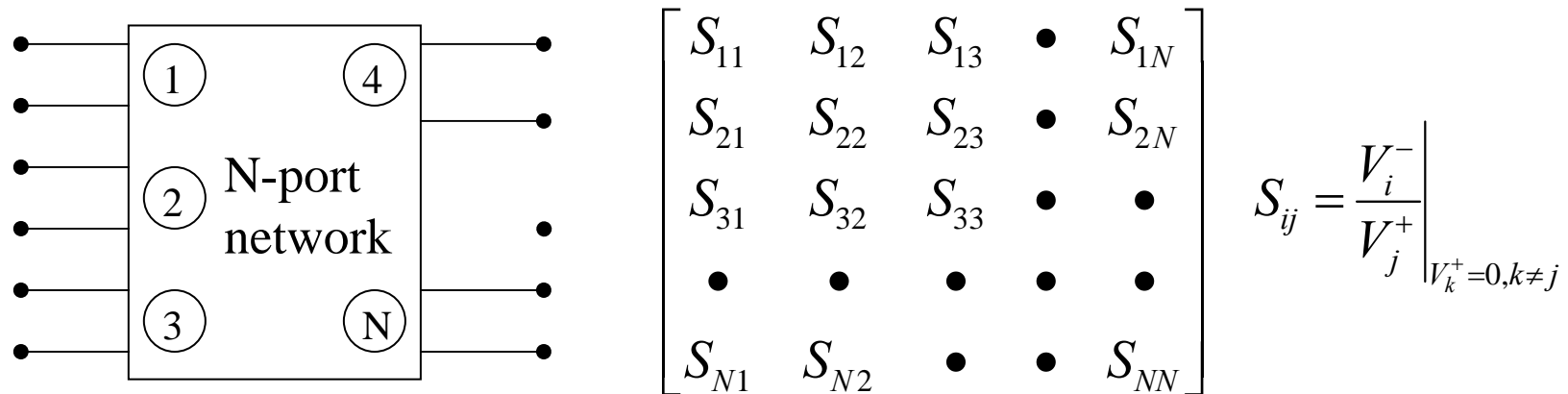


Discussion

1. matched ports $\rightarrow S_{ii} = 0$
2. reciprocal network \rightarrow symmetric property $S_{ij} = S_{ji}$
3. lossless network \rightarrow unitary property


$$\sum_{i=1}^N |S_{ij}|^2 = 1 \quad \forall j, \quad \sum_{i=1}^N S_{ik} S_{kj}^* = 0 \quad k \neq j$$

- three-port network (T-junction)

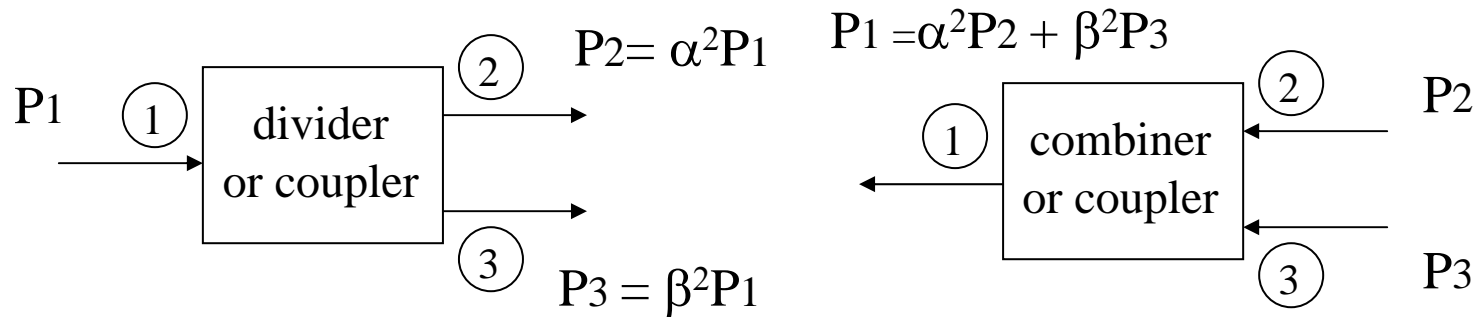


Discussion

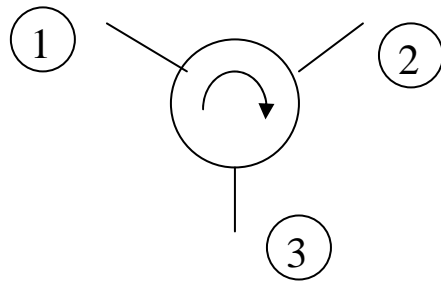1. Three-port network **cannot** be lossless, reciprocal and matched at all ports.
2. A lossless and matched three-port network is nonreciprocal
→ circulator


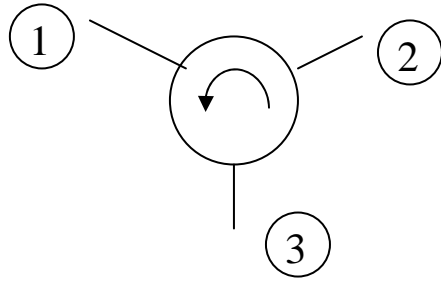
$$\begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$



$$\begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$

3. A matched and reciprocal three-port network is lossy \rightarrow resistive divider.
4. A matched and lossy three-port network can have ∞ isolation at two output ports ($S_{23}=S_{32}=0$) \rightarrow Wilkinson power divider .

(derivation of 1)

For a matched, reciprocal three-port network


$$\begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} \xrightarrow{\text{lossless}} \begin{cases} |S_{12}|^2 + |S_{13}|^2 = 1 & S_{13}^* S_{23} = 0 & |S_{12}| = 1 \\ |S_{12}|^2 + |S_{23}|^2 = 1 & S_{12}^* S_{13} = 0 \rightarrow \text{if } S_{13} = 0, & |S_{23}| = 0 \rightarrow \text{lossy} \\ |S_{13}|^2 + |S_{23}|^2 = 1 & S_{12}^* S_{23} = 0 & |S_{13}| = 1 \neq 0 \end{cases}$$

(derivation of 2)


For a matched, lossless, nonreciprocal three-port network

$$\begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix} \xrightarrow{\text{lossless}} \begin{cases} |S_{21}|^2 + |S_{31}|^2 = 1 & S_{31}^* S_{32} = 0 \\ |S_{12}|^2 + |S_{32}|^2 = 1 & S_{12}^* S_{13} = 0 \\ |S_{13}|^2 + |S_{23}|^2 = 1 & S_{21}^* S_{23} = 0 \end{cases} \rightarrow \begin{cases} \text{if } S_{21} = 1 \rightarrow S_{31} = 0, S_{32} = 1, S_{23} = 0, S_{13} = 1, S_{12} = 0 \\ \text{if } S_{21} = 0 \rightarrow S_{31} = 1, S_{32} = 0, S_{23} = 1, S_{13} = 0, S_{12} = 1 \end{cases}$$

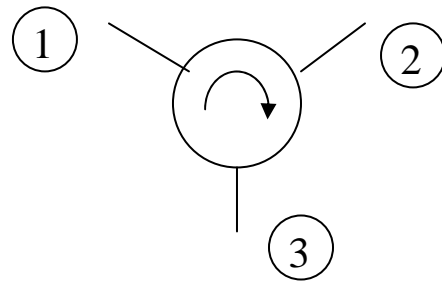
$$\begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$



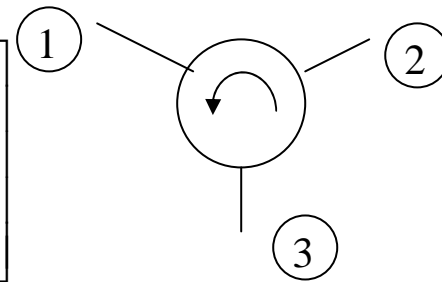
$$\begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



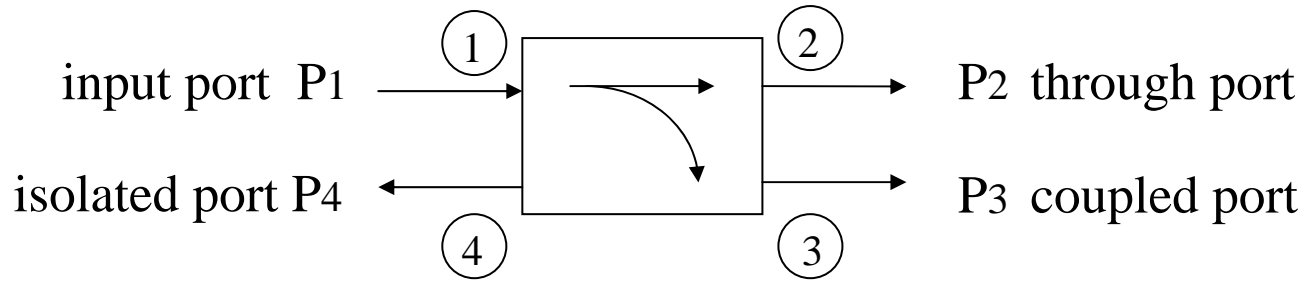• four-port network (directional coupler)




$$\text{coupling } C(dB) \equiv 10 \log \frac{P_1}{P_3} = -20 \log |S_{31}|$$

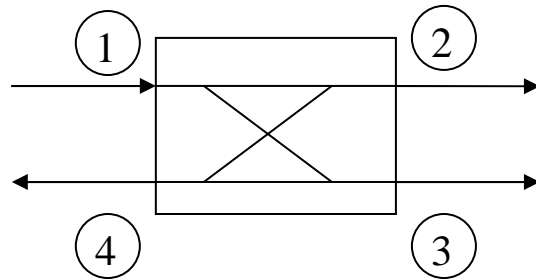

$$\text{directivity } D(dB) \equiv 10 \log \frac{P_3}{P_4} = 10 \log \frac{P_3}{P_1} \frac{P_1}{P_4} = 20 \log \frac{|S_{31}|}{|S_{41}|}$$

$$\text{isolation } I(dB) \equiv 10 \log \frac{P_1}{P_4} = C + D = -20 \log |S_{41}|$$

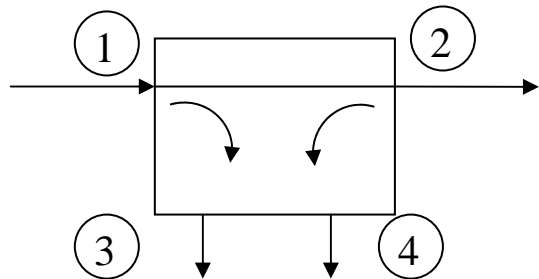

$$\text{voltage coupling factor } C = 10^{-C(dB)/20} = \left| \frac{V_3^-}{V_1^+} \right| < 1$$

$$\text{directivity } D = 10^{D(dB)/20} = \left| \frac{V_3^-}{V_4^-} \right| > 1$$

Discussion

1. Matched, reciprocal and lossless four-port network \rightarrow symmetrical (90°) directional coupler or antisymmetrical (180°) directional coupler

$$\begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix} \quad \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

2. $C=3\text{dB}$ \rightarrow 90° hybrid (quadrature hybrid, symmetrical coupler),
 180° hybrid (magic-T hybrid, rat-race hybrid)

$$\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix} \quad \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

(derivation of 1)

For a matched, reciprocal and lossless four-port network

$$\begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix} \rightarrow \begin{array}{l} \text{row 1}^*, 2: S_{13}^* S_{23} + S_{14}^* S_{24} = 0 \dots (1) \\ \text{row 3, 4}^*: S_{14}^* S_{13} + S_{24}^* S_{23} = 0 \dots (2) \\ \text{row 1}^*, 3: S_{12}^* S_{23} + S_{14}^* S_{34} = 0 \dots (3) \\ \text{row 2, 4}^*: S_{14}^* S_{12} + S_{34}^* S_{23} = 0 \dots (4) \end{array}$$

$$\begin{array}{l} \xrightarrow{(1)S_{24}^* - (2)S_{13}^*} S_{14}^* (|S_{13}|^2 - |S_{24}|^2) = 0 \\ \xrightarrow{(3)S_{12}^* - (4)S_{34}^*} S_{23}^* (|S_{12}|^2 - |S_{34}|^2) = 0 \end{array}$$

case 1: $S_{14} = S_{23} = 0 \rightarrow$

$$\begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix} \rightarrow \begin{array}{l} |S_{12}|^2 + |S_{13}|^2 = 1 \\ |S_{12}|^2 + |S_{24}|^2 = 1 \\ |S_{13}|^2 + |S_{34}|^2 = 1 \\ |S_{24}|^2 + |S_{34}|^2 = 1 \end{array} \rightarrow \begin{array}{l} S_{12} = S_{34} = \alpha \\ |S_{13}| = |S_{24}| \text{ choose } S_{13} = \beta e^{j\theta} \\ |S_{12}| = |S_{34}| \rightarrow S_{24} = \beta e^{j\phi} \\ \alpha^2 + \beta^2 = 1 \end{array}$$

row 2*, 3 $\rightarrow S_{12}^* S_{13} + S_{24}^* S_{34} = 0 \rightarrow e^{j\theta} + e^{-j\phi} = 0 \rightarrow \theta + \phi = \pi$

(a) 90° directional coupler with $\theta = \phi = \frac{\pi}{2}$ (b) 180° directional coupler with $\theta = 0, \phi = \pi$

$$\begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$


$$\begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix} \rightarrow \begin{array}{l} \text{row 1}^*, 2: S_{13}^* S_{23} + S_{14}^* S_{24} = 0 \dots (1) \\ \text{row 3, 4}^*: S_{14}^* S_{13} + S_{24}^* S_{23} = 0 \dots (2) \\ \text{row 1}^*, 3: S_{12}^* S_{23} + S_{14}^* S_{34} = 0 \dots (3) \\ \text{row 2, 4}^*: S_{14}^* S_{12} + S_{34}^* S_{23} = 0 \dots (4) \end{array}$$

$$\text{case 2: if } \begin{array}{l} |S_{13}| = |S_{24}| \\ |S_{12}| = |S_{34}| \end{array} \xrightarrow{\text{choose}} \begin{array}{l} S_{13} = S_{24} = j\beta \\ S_{12} = S_{34} = \alpha \end{array} \rightarrow \begin{array}{l} (1): j\beta(-S_{23} + S_{14}^*) = 0 \\ (3): \alpha(S_{23} + S_{14}^*) = 0 \end{array}$$

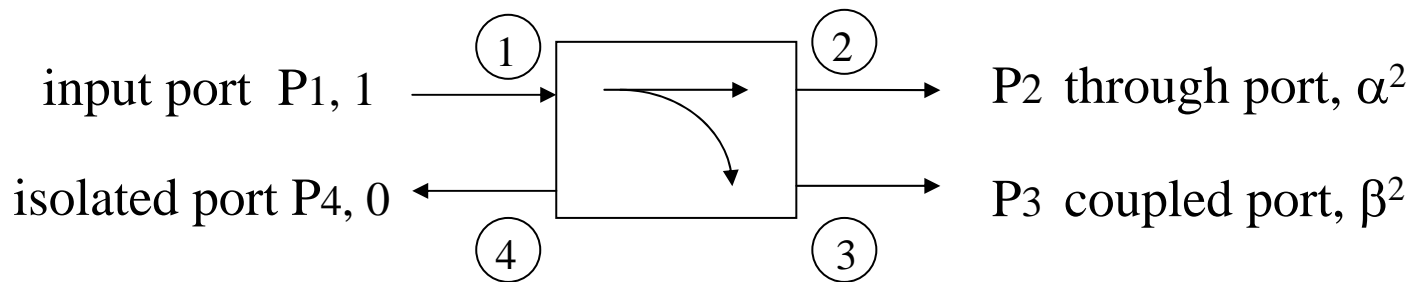
(a) $S_{14} = S_{23} = 0 \rightarrow$ directional coupler as case 1

$$(b) \alpha = \beta = 0 \rightarrow \begin{bmatrix} 0 & 0 & 0 & S_{14} \\ 0 & 0 & S_{23} & 0 \\ 0 & S_{23} & 0 & 0 \\ S_{14} & 0 & 0 & 0 \end{bmatrix}, \text{ two decoupled two-port networks}$$



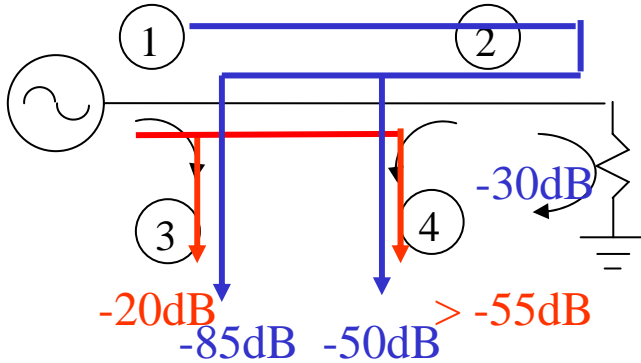3. directivity measurement

If $C=20\text{dB}$, $D=35\text{dB}$, $RL=30\text{dB}$ (require $<35\text{dB}$)




1→3 (C, -20dB) → 4 (C/D, -55dB)

$$V_3^- = C V_1^+, D = \frac{V_3^-}{V_4^-} \rightarrow V_4^- = \frac{C}{D} V_1^+$$

1→2→4 (CΓ, -85dB) → 3 (CΓ/D, -55dB)
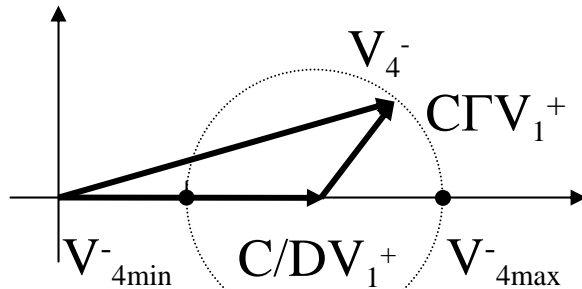
$$V_4^- \approx C\Gamma V_1^+ (= C\Gamma \sqrt{1-C^2} V_1^+), V_3^- \approx \frac{C\Gamma}{D} V_1^+$$



$$\text{For } |\Gamma| < \frac{1}{D}$$

with the use of a sliding load $|\Gamma| e^{j\angle\Gamma}$

$$P_{4\max} = P_1 \left(\frac{C}{D} + C|\Gamma| \right)^2$$

$$P_{4\min} = P_1 \left(\frac{C}{D} - C|\Gamma| \right)^2$$



$$P_3 = C^2 P_1, M = \sqrt{\frac{P_3}{P_{4\max}}} = \frac{D}{1 + |\Gamma|D}$$

$$m = \sqrt{\frac{P_{4\max}}{P_{4\min}}} = \frac{1 + |\Gamma|D}{1 - |\Gamma|D}$$

$$\Rightarrow D = M \frac{2m}{m+1}$$

7.2 The T-junction power divider

- lossless divider

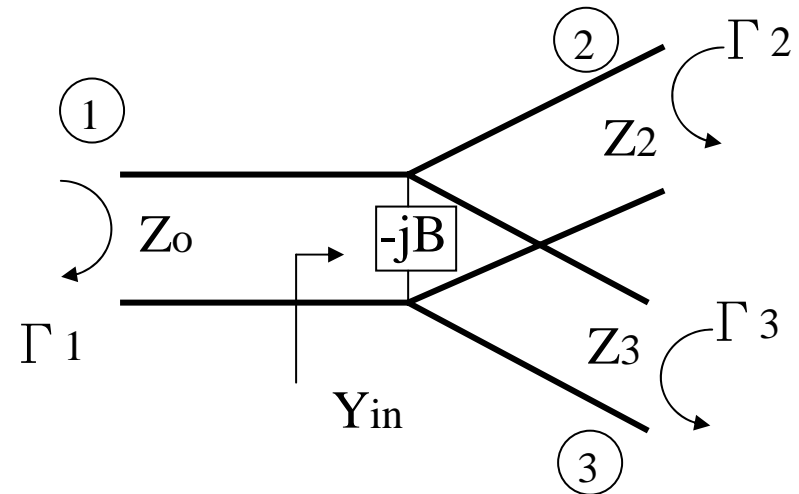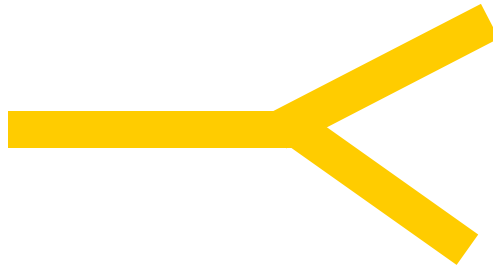

$$Y_{in} = jB + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{Z_0} \quad \rightarrow \quad B = 0 \quad \text{"not practical"}$$

\Rightarrow A lossless divider has mismatched ports.

Discussion

1. Ex. 7.1 $Z_o=50\Omega$, $P_2:P_3=1:2$, calculate Γ_2 and Γ_3 .

$$P_1 : P_2 : P_3 = 1 : \frac{1}{3} : \frac{2}{3} = \frac{1}{Z_o} : \frac{1}{Z_2} : \frac{1}{Z_3}$$


$$\rightarrow Z_2 = 3Z_o = 150\Omega, \quad Z_3 = \frac{3}{2}Z_o = 75\Omega$$

$$Z_{in} = Z_2 // Z_3 = 50\Omega$$

$$\Gamma_2 = \frac{50 // 75 - Z_2}{50 // 75 + Z_2} = -0.666, \quad \Gamma_3 = \frac{50 // 150 - Z_3}{50 // 150 + Z_3} = -0.333$$

2. It's a lossless and mismatched three-port divider, but not good in isolation.

- resistive (lossy) divider

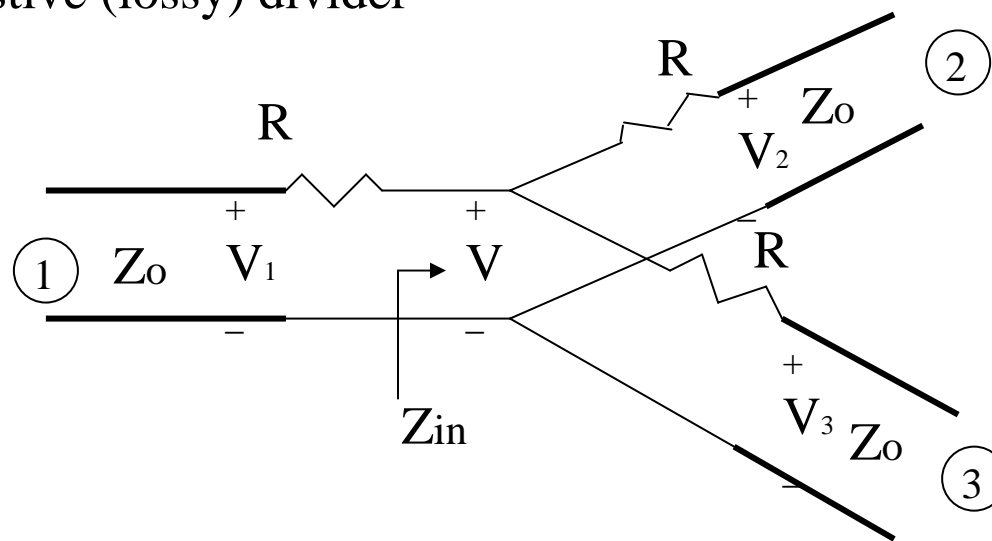

matched ports $\Rightarrow (R + Z_o) \parallel (R + Z_o) + R = Z_o \rightarrow R = \frac{Z_o}{3}$

Discussion

1. $[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} \therefore Z_{in} = \frac{R + Z_o}{2} = \frac{2}{3} Z_o, V = V_1 \frac{\frac{2}{3} Z_o}{R + \frac{2}{3} Z_o} = \frac{2}{3} V_1$

$V_2, V_3 = V \frac{Z_o}{\frac{Z_o}{3} + Z_o} = \frac{3}{4} V = \frac{1}{2} V_1$


2. $P_{in} = \frac{1}{2} \frac{V_1^2}{Z_o}$, $P_2 = P_3 = \frac{1}{8} \frac{V_1^2}{Z_o} = \frac{P_{in}}{4}$, $P_{loss} = \frac{P_{in}}{4}$ for each R

→ lossy divider

3. It's a lossy and matched three-port divider, but not good in isolation.

7.3 The Wilkinson power divider

- basic concept

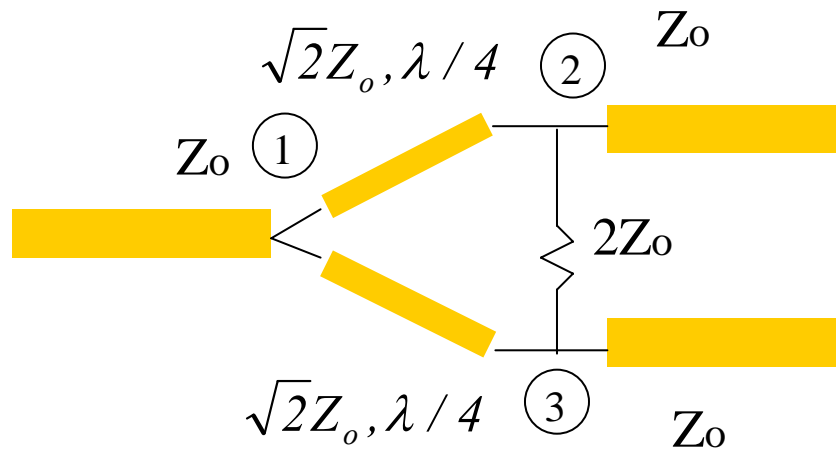

$$\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & -j & -j \\ -j & 0 & 0 \\ -j & 0 & 0 \end{bmatrix}$$


Input port 1 matched, port 2 and port 3 have equal potential

$$\rightarrow \sqrt{2}Z_0, \lambda/4$$


Input port 2, port 2 and port 3 have perfect isolation

=> a **lossy, matched and good isolation (equal phase)** three-port divider

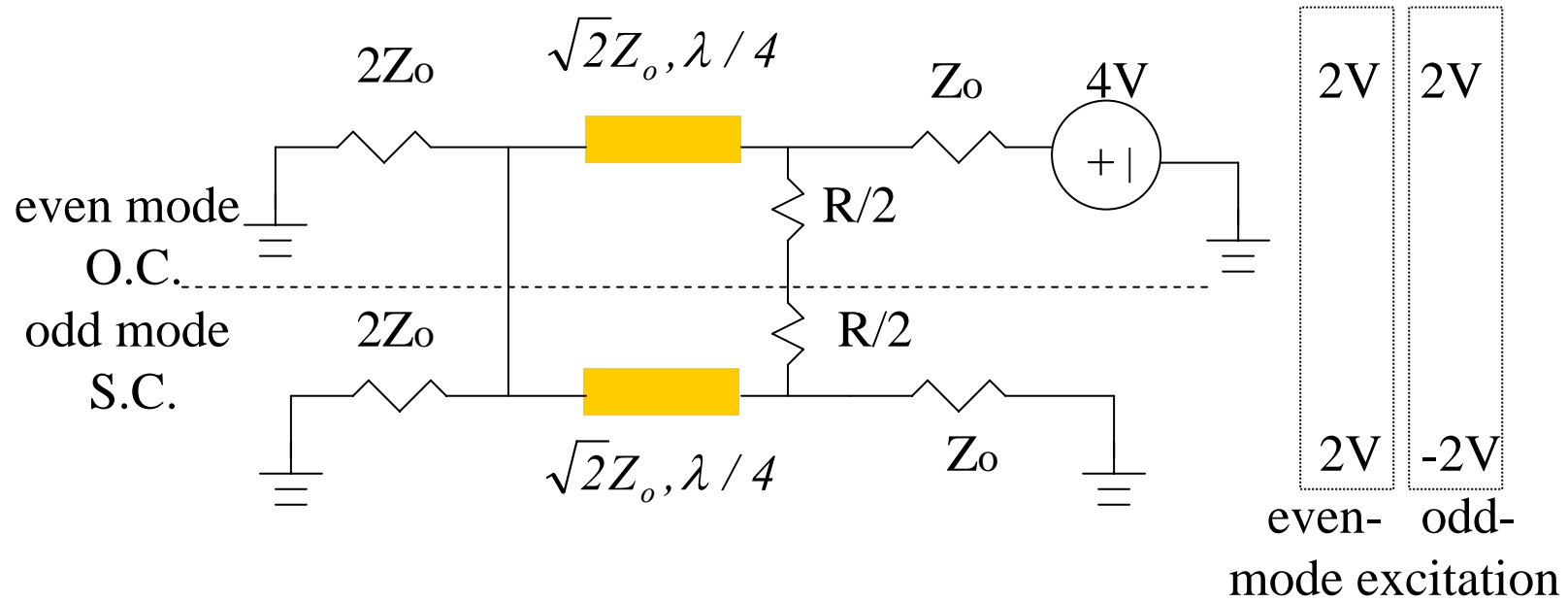- even-odd mode analysis
A linear, symmetric network



even-mode

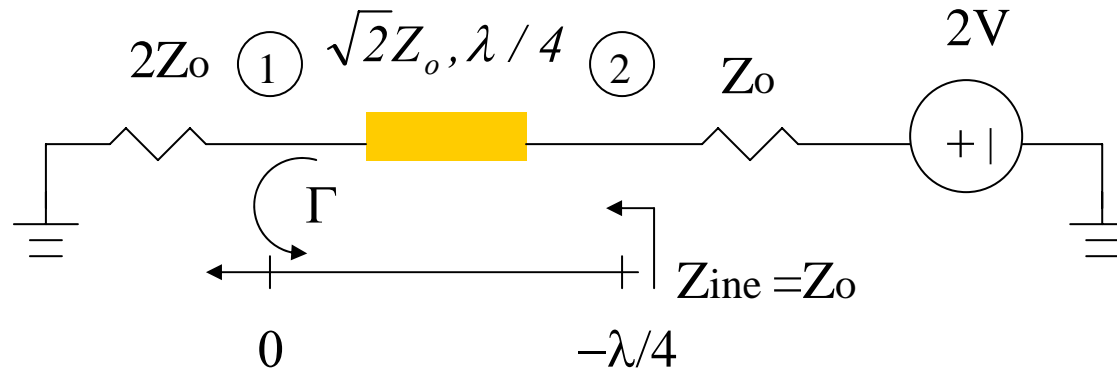

ports 2, 3 matched, $V_{2e} = V$, symmetry of ports 2 and 3 $\rightarrow V_{3e} = V$


$$\Gamma = \frac{2 - \sqrt{2}}{2 + \sqrt{2}} \rightarrow V_{1e} = jV \frac{\Gamma + 1}{\Gamma - 1} = -j\sqrt{2}V$$

(derivation of V_{1e}) $V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$

$$V_{2e} = V^+ e^{-j\frac{2\pi - \lambda}{\lambda} \frac{\lambda}{4}} + V^- e^{j\frac{2\pi - \lambda}{\lambda} \frac{\lambda}{4}} = V^+ e^{j\frac{\pi}{2}} + V^- e^{-j\frac{\pi}{2}} = jV^+ (1 - \Gamma) \equiv V$$

$$V_{1e} = V^+ + V^- = V^+ (1 + \Gamma) = -j \frac{1 + \Gamma}{1 - \Gamma} V = -j \frac{1 + \frac{2 - \sqrt{2}}{2 + \sqrt{2}}}{1 - \frac{2 - \sqrt{2}}{2 + \sqrt{2}}} V = -j \frac{4}{2\sqrt{2}} V = -j\sqrt{2}V$$

odd-mode

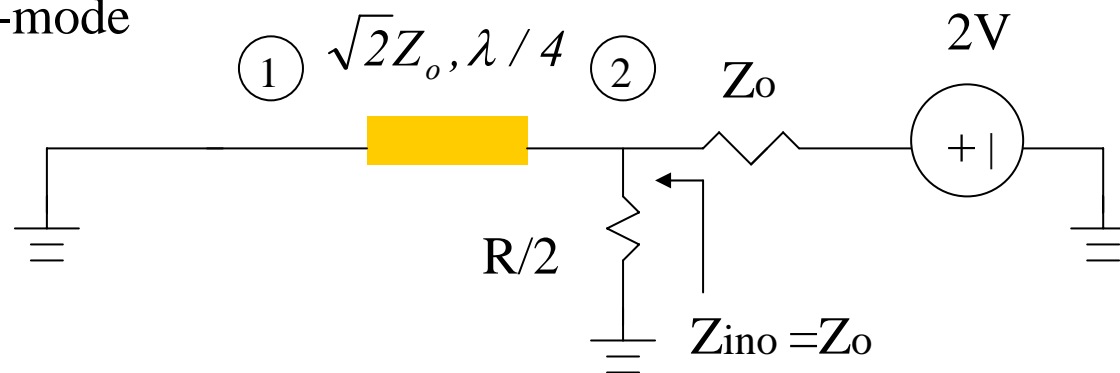

$\frac{R}{2} = Z_o \rightarrow R = 2Z_o \rightarrow$ ports 2 and 3 matched, $V_{2o} = V, V_{3o} = -V$, symmetry of ports 2 and 3

$$\left. \begin{array}{l} V_{2e} = V \\ V_{2o} = V \end{array} \right\} \rightarrow V_2 = V_{2e} + V_{2o} = 2V, \quad \left. \begin{array}{l} V_{1e} = -j\sqrt{2}V \\ V_{1o} = 0 \end{array} \right\} \rightarrow V_1 = V_{1e} + V_{1o} = -j\sqrt{2}V$$


$$\left. \begin{array}{l} V_{3e} = V \\ V_{3o} = -V \end{array} \right\} \rightarrow V_3 = V_{3e} + V_{3o} = 0$$

$$\Rightarrow S_{12} = \frac{V_1^-}{V_2^+} = \frac{V_1}{V_2} \Big|_{S_{11}=S_{22}=0} = \frac{-j\sqrt{2}V}{2V} = -j\frac{1}{\sqrt{2}} = S_{21} = S_{31} = S_{13}$$

$$\Rightarrow S_{32} = \frac{V_3^-}{V_2^+} = \frac{V_3}{V_2} \Big|_{S_{11}=S_{33}=0} = \frac{0}{2V} = 0 = S_{23}$$

Discussion

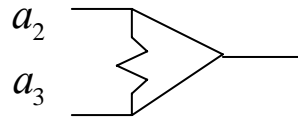1. 3dB Wilkinson power divider has equal amplitude and phase outputs at port 2 and port 3.
2. Ex. 7.2 3dB Wilkinson power divider $Z_0=70.7\Omega$, $R=100\Omega$. frequency response (p.322, Fig. 7.12)
3. 3dB Wilkinson power combiner




$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & -j & -j \\ -j & 0 & 0 \\ -j & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ a_2 \\ a_3 \end{bmatrix} = \begin{bmatrix} -j \frac{1}{\sqrt{2}} (a_2 + a_3) \\ 0 \\ 0 \end{bmatrix}$$

$$\text{if } a_2 = a_3 \rightarrow P_1 = \frac{1}{2} \left(\frac{1}{2} |a_2 + a_3|^2 \right) = \frac{1}{2} (|a_2|^2 + |a_3|^2) = P_2 + P_3$$

$$\text{if } a_2 \neq a_3, P_1 = \frac{1}{2} \left(\frac{1}{2} |a_2 + a_3|^2 \right) \neq \frac{1}{2} (|a_2|^2 + |a_3|^2)$$

$$\rightarrow \begin{matrix} \text{even} & \frac{\frac{a_2 + a_3}{2}}{2} \\ \text{odd} & \frac{\frac{a_2 - a_3}{2}}{2} \end{matrix} \Rightarrow 2 \times \frac{1}{2} \left| \frac{a_2 + a_3}{2} \right|^2$$

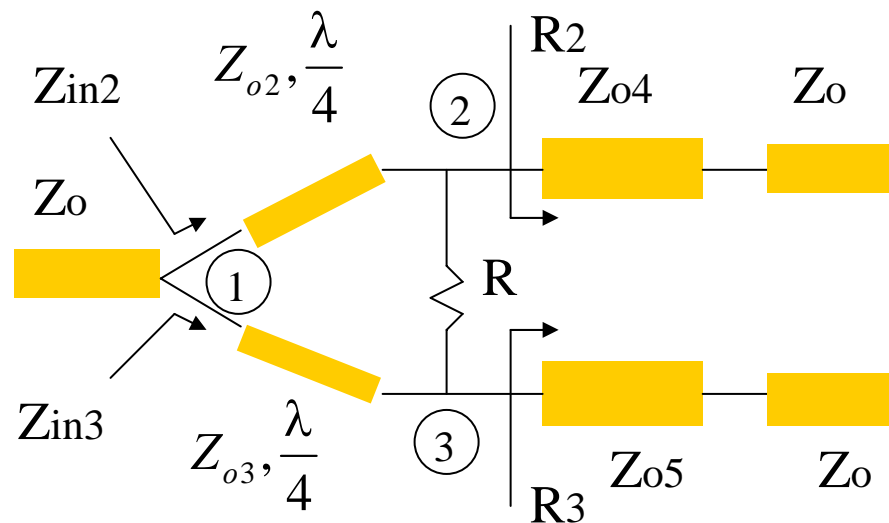4. unequal power division (Wilkinson power divider)



(1) port 1 match $\rightarrow Z_o = Z_{in2} // Z_{in3}$



(2) $\frac{P_3}{P_2} = K^2 \rightarrow \frac{V_3^2}{Z_{in3}} = K^2 \frac{V_2^2}{Z_{in2}}$

(3) $V_2 = V_3 \rightarrow Z_{in2} = K^2 Z_{in3}$

$$(1), (3) \rightarrow Z_{in2} = (1 + K^2)Z_o, Z_{in3} = \frac{1 + K^2}{K^2} Z_o$$

$$R_2 = K^2 R_3, R_2 = KZ_o \rightarrow R_3 = \frac{Z_o}{K}, Z_{o4} = \sqrt{K}Z_o, Z_{o5} = \frac{Z_o}{\sqrt{K}}$$
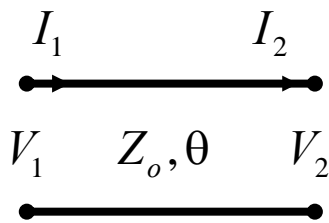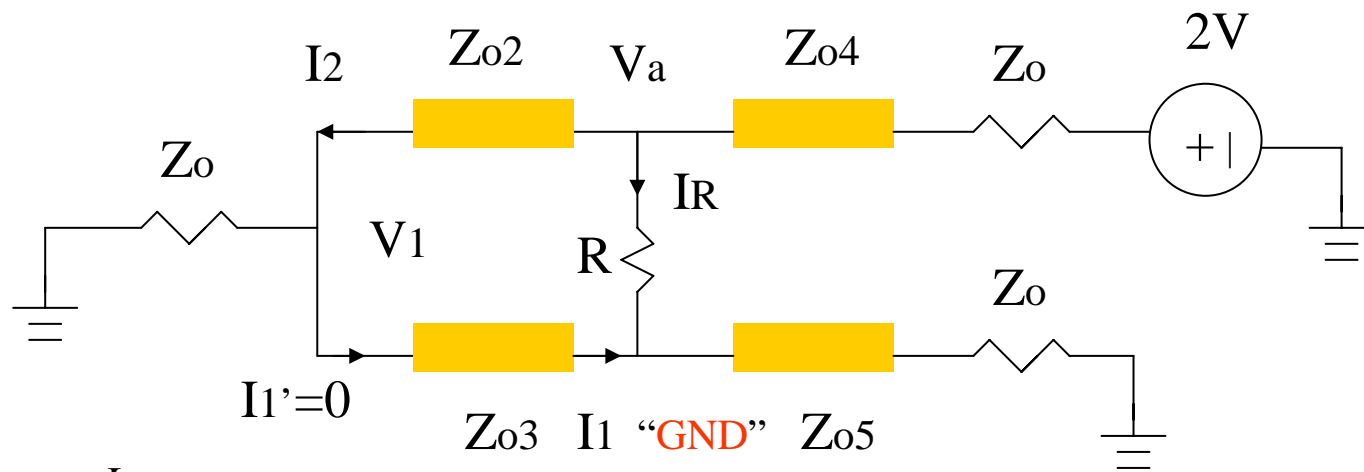
$$Z_{o2} = \sqrt{Z_{in2}R_2} = \sqrt{K(1 + K^2)}Z_o, Z_{o3} = \sqrt{Z_{in3}R_3} = \sqrt{\frac{1 + K^2}{K^3}}Z_o$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_o \sin \theta \\ \frac{j \sin \theta}{Z_o} & \cos \theta \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & jZ_o \\ \frac{j}{Z_o} & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \rightarrow \begin{aligned} V_1 &= jZ_o I_2 \\ I_1 &= \frac{j}{Z_o} V_2 \end{aligned}$$

$$I_1 = \frac{V_1}{jZ_{o3}}, I_2 = \frac{V_a}{jZ_{o2}}, \frac{V_1}{I_2} = Z_o$$

$$I_R + I_1 = 0 = \frac{V_a}{R} + \frac{V_1}{jZ_{o3}} = \frac{jZ_{o2}I_2}{R} + \frac{Z_o I_2}{jZ_{o3}} = jI_2 \left(\frac{Z_{o2}}{R} - \frac{Z_o}{Z_{o3}} \right)$$

$$\rightarrow R = \frac{Z_{o2}Z_{o3}}{Z_o} = \frac{1+K^2}{K} Z_o, K = 1 \text{ for a 3dB Wilkinson divider}$$

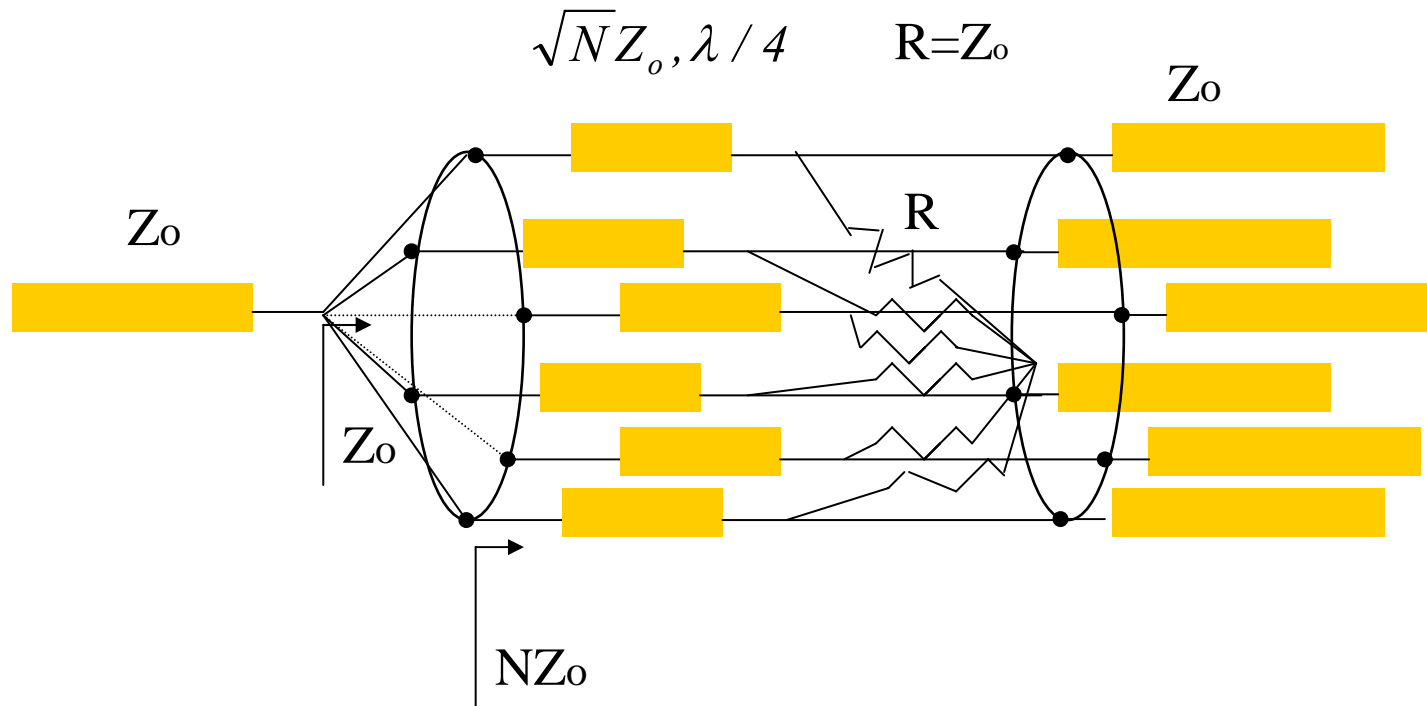
5. N-way Wilkinson power divider (not in planar shape)



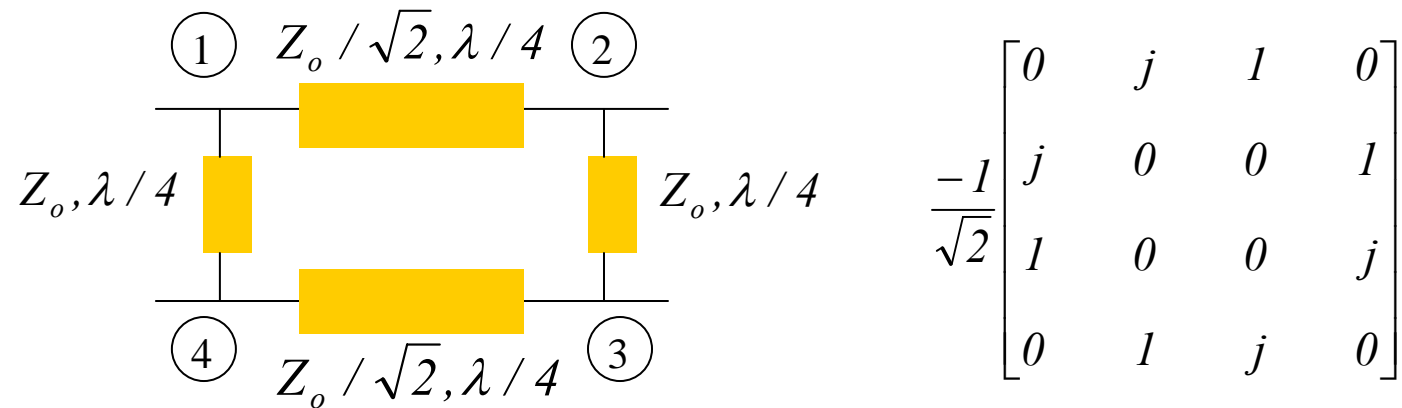
7.5 The quadrature (90°) hybrid

- branch-line coupler


Port 2 and port 3 have equal amplitude and 90° phase difference




- even-odd mode analysis

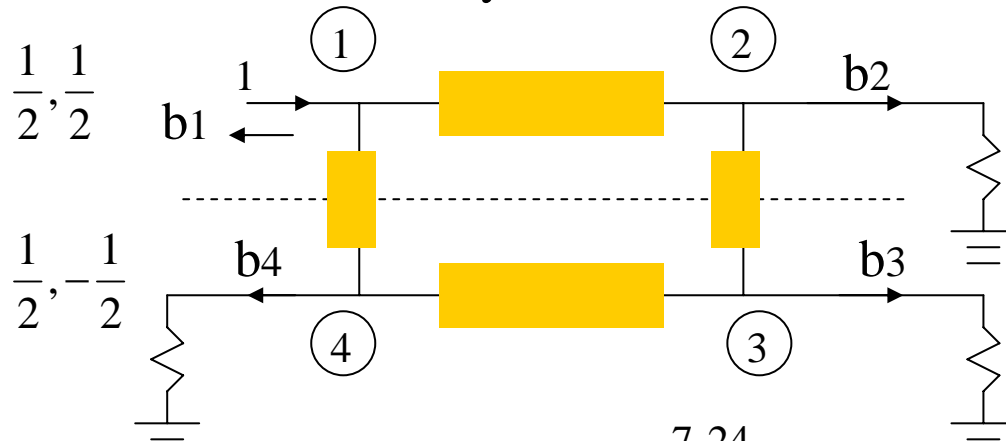

even-mode

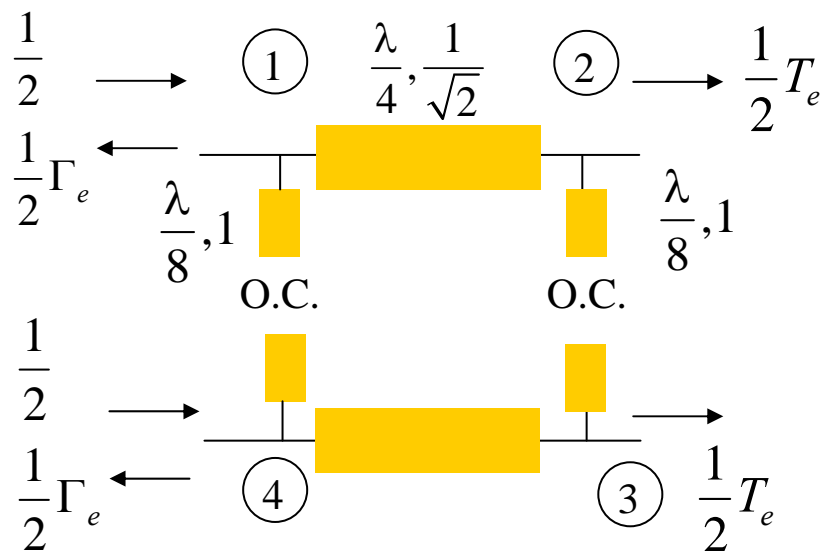


odd-mode

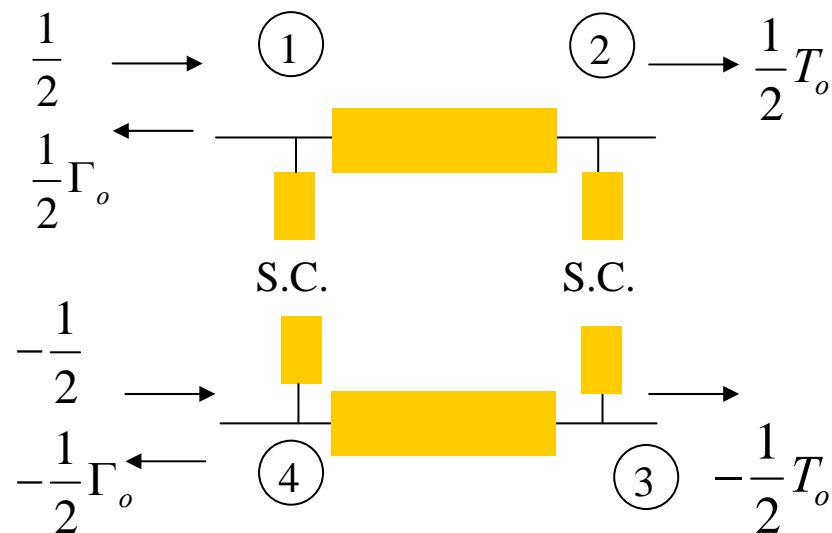


$$b_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o = S_{11}, b_2 = \frac{1}{2}T_e + \frac{1}{2}T_o = S_{21}$$

$$b_3 = \frac{1}{2}T_e - \frac{1}{2}T_o = S_{31}, b_4 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o = S_{41}$$
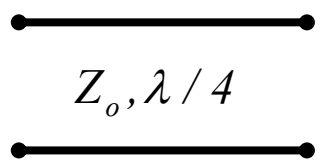
$$\begin{bmatrix} b_1 & b_2 & b_3 & b_4 \\ b_2 & b_1 & b_4 & b_3 \\ b_3 & b_4 & b_1 & b_2 \\ b_4 & b_3 & b_2 & b_1 \end{bmatrix}$$


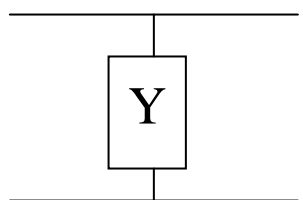
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_o \sin \theta \\ jY_o \sin \theta & \cos \theta \end{bmatrix}_{\theta=\frac{\pi}{2}} = \begin{bmatrix} 0 & jZ_o \\ jY_o & 0 \end{bmatrix}$$



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$\Rightarrow \text{even-mode: } \frac{\lambda}{8} \text{ open-circuit stub } \begin{bmatrix} 1 & 0 \\ jY_o & 1 \end{bmatrix}$$

$$\text{odd-mode: } \frac{\lambda}{8} \text{ short-circuit stub } \begin{bmatrix} 1 & 0 \\ -jY_o & 1 \end{bmatrix}$$


$$\Gamma = S_{11} = \frac{AZ_o + B - CZ_o^2 - DZ_o}{AZ_o + B + CZ_o^2 + DZ_o}, T = S_{21} = \frac{2Z_o}{AZ_o + B + CZ_o^2 + DZ_o}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} \begin{bmatrix} 0 & \frac{j}{\sqrt{2}} \\ j\sqrt{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} -1 & j \\ j & -1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} \begin{bmatrix} 0 & \frac{j}{\sqrt{2}} \\ j\sqrt{2} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j & 1 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & j \\ j & 1 \end{bmatrix}$$

$$\rightarrow \Gamma_e = 0, \Gamma_o = 0, T_e = \frac{-1}{\sqrt{2}}(1+j), T_o = \frac{1}{\sqrt{2}}(1-j)$$

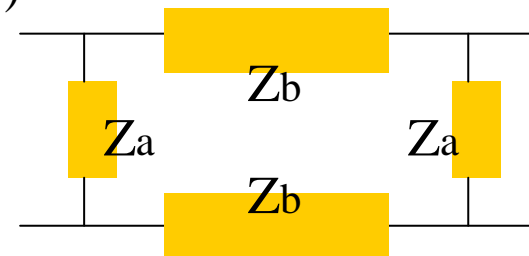
$$\Rightarrow b_1 = 0, b_2 = \frac{-j}{\sqrt{2}}, b_3 = \frac{-1}{\sqrt{2}}, b_4 = 0$$





Discussion

1. Unequal power division branch-line coupler uses $Z_a, Z_b \lambda/4$ lines (prob. 7.17).
2. Ex. 7.5, frequency response (p.336, Fig. 7.25), BW: 10% ~ 20%
3. Multisection branch-line couplers can increase the operation BW.


4. Smith chart consideration

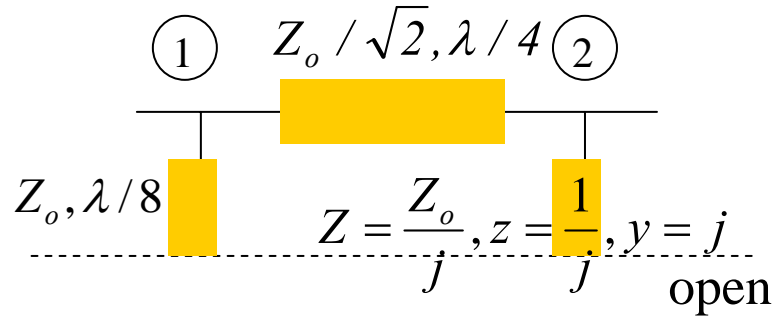

even-mode

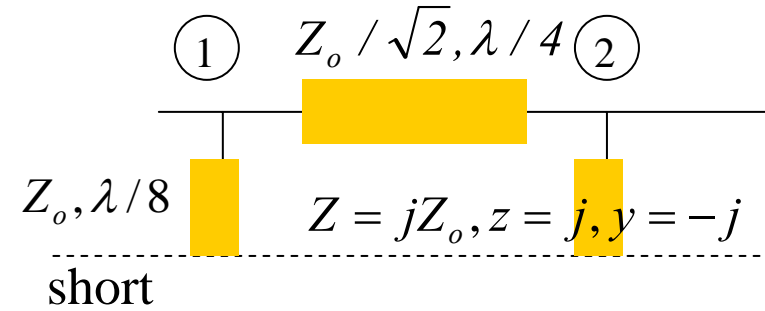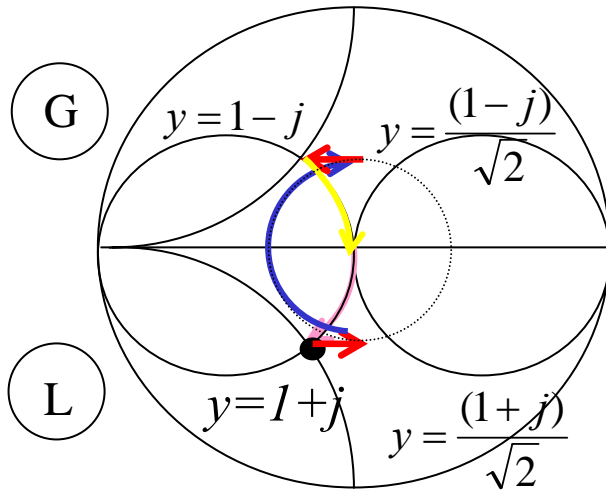


odd-mode

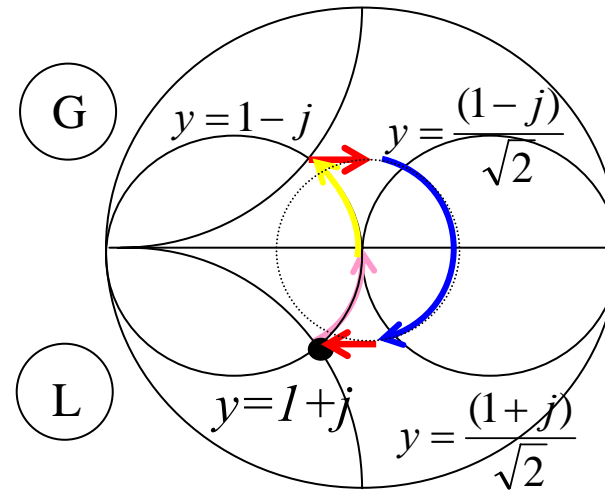


7.6 Coupled line directional couplers




- coupled line theory

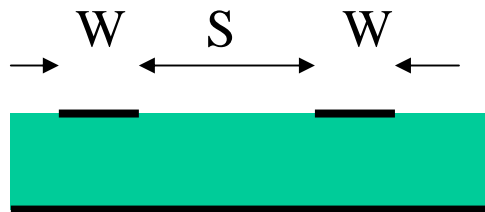

even-mode excitation

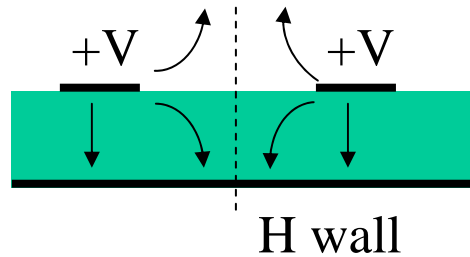

odd-mode excitation

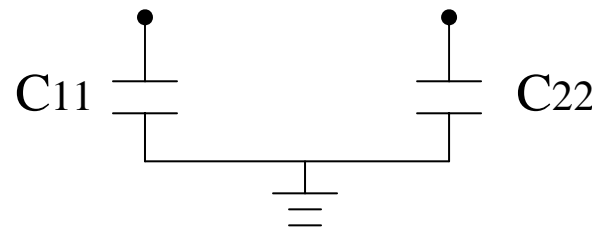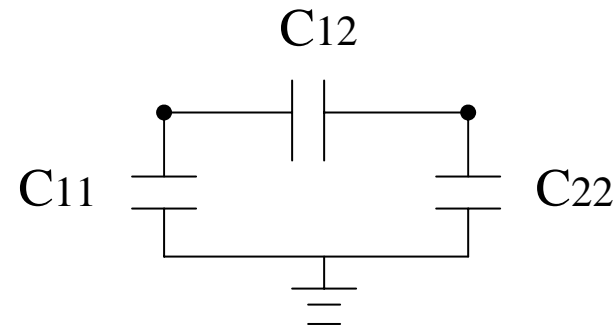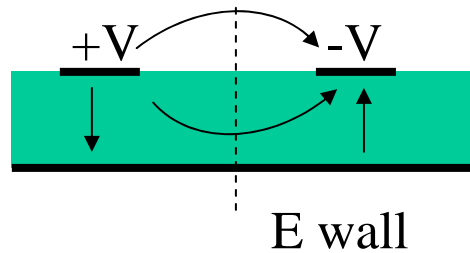


$$C_e = C_{11} = C_{22}$$

$$Z_{oe} = \frac{1}{v_e C_e}$$


$$C_o = C_{11} + 2C_{12}$$

$$Z_{oo} = \frac{1}{v_o C_o}$$

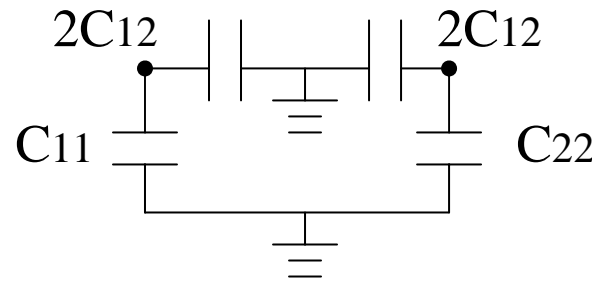

Discussion

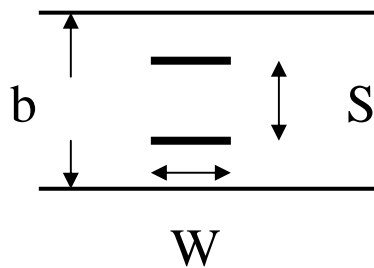1. In general $v_e \neq v_o$ ($\because \epsilon_{effe} > \epsilon_{effo}$), for TEM mode $v_e = v_o = v$.
2. Z_{oe}, Z_{oo} (W/b, S/b) (p.339, Fig. 7.29 and p.340, Fig. 7.30) for coupled striplines and microstrip lines.
3. $Z_{oe} > Z_{oo}$, W/b $\uparrow \rightarrow Z_{oe} \downarrow$, Z_{oo} \downarrow , S/b $\uparrow \rightarrow Z_{oe} \downarrow$, Z_{oo} \uparrow and $Z_{oe}, Z_{oo} \rightarrow Z_o$.
4. Ex.7.6 derive Z_{oe}, Z_{oo} of coupled striplines (p.337, Fig.7.26(b))



$$C_{11} = \frac{\epsilon W}{(b-S)/2} + \frac{\epsilon W}{(b+S)/2} = \frac{4b\epsilon W}{b^2 - S^2}, C_{12} = \frac{\epsilon W}{S}$$

$$C_e = C_{11}, C_o = C_{11} + 2C_{12}$$

$$Z_{oe} = \frac{1}{vC_e} = Z_o \frac{b^2 - S^2}{4bW\sqrt{\epsilon_r}}$$

$$Z_{oo} = \frac{1}{vC_o} = Z_o \frac{1}{2W\sqrt{\epsilon_r}[2b/(b^2 - S^2) + 1/S]}$$


- coupled line coupler

matched port $\rightarrow Z_o = \sqrt{Z_{oe}Z_{oo}}$

$$C \equiv \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}}, \theta = \frac{\pi}{2} \Rightarrow$$


$$\begin{bmatrix} 0 & -j\sqrt{1-C^2} & C & 0 \\ -j\sqrt{1-C^2} & 0 & 0 & C \\ C & 0 & 0 & -j\sqrt{1-C^2} \\ 0 & C & -j\sqrt{1-C^2} & 0 \end{bmatrix}$$

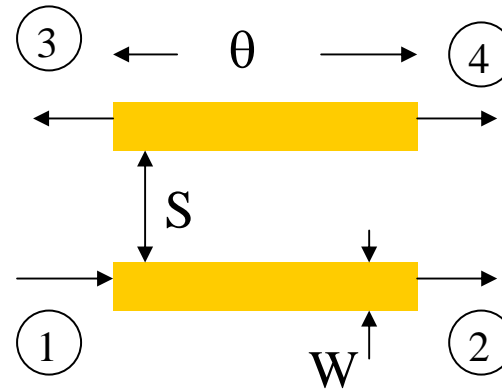design equations: $Z_{oe} = Z_o \sqrt{\frac{1+C}{1-C}}, Z_{oo} = Z_o \sqrt{\frac{1-C}{1+C}} \Rightarrow S, W$



Discussion

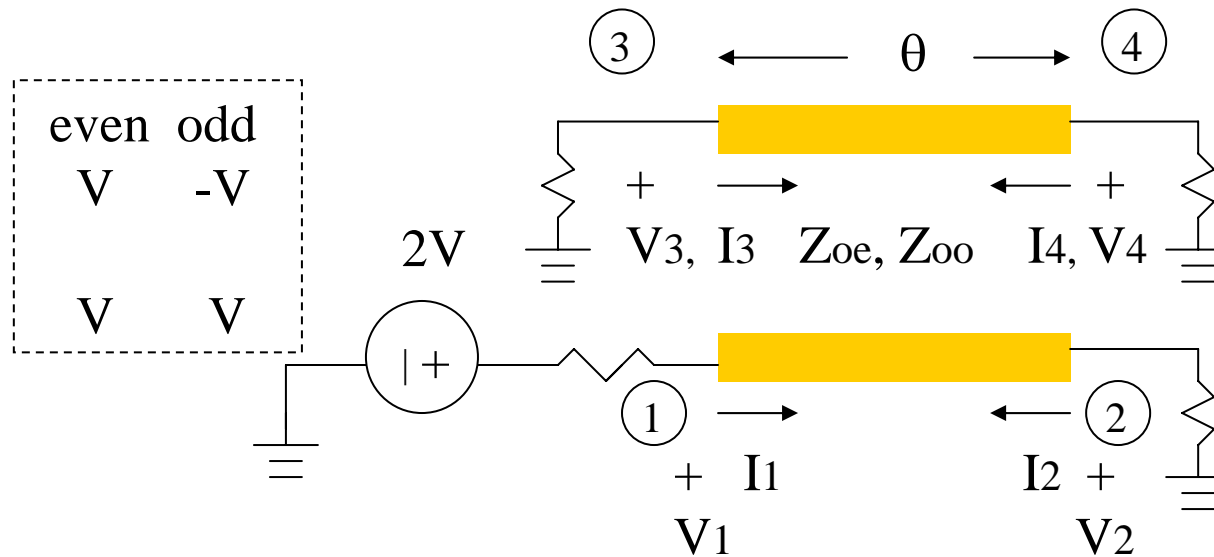1. Design procedure: given C and Z_o , calculate Z_{oe} and Z_{oo} , then use Fig. 7.29 or 7.30 to find W/b and S/b for stripline or microstrip.
2. even-odd mode analysis



even mode: $I_1^e = I_3^e, I_2^e = I_4^e, V_1^e = V_3^e, V_2^e = V_4^e$

odd mode: $I_1^o = -I_3^o, I_2^o = -I_4^o, V_1^o = -V_3^o, V_2^o = -V_4^o$

$$I_1 = I_1^e + I_1^o, I_2 = I_2^e + I_2^o, I_3 = I_1^e - I_1^o, I_4 = I_2^e - I_2^o$$

$$V_1 = V_1^e + V_1^o, V_2 = V_2^e + V_2^o, V_3 = V_1^e - V_1^o, V_4 = V_2^e - V_2^o$$

$$Z_{in}^{e,o} = Z_{oe,o} \frac{Z_o + jZ_{oe,o} \tan \theta}{Z_{oe,o} + jZ_o \tan \theta} \quad V_1^{e,o} = V \frac{Z_{in}^{e,o}}{Z_{in}^{e,o} + Z_o}, I_1^{e,o} = \frac{V}{Z_{in}^{e,o} + Z_o}$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o} = Z_o + \frac{2(Z_{in}^e Z_{in}^o - Z_o^2)}{Z_{in}^e + Z_{in}^o + 2Z_o} \dots(1)$$

$$= Z_o \Leftarrow \text{if } Z_o^2 (= Z_{in}^e Z_{in}^o) = Z_{oe} Z_{oo} \dots(2)$$

$$\rightarrow V_1^{e,o} = V \frac{Z_o + jZ_{oe,o} \tan \theta}{2Z_o + j(Z_{oe} + Z_{oo}) \tan \theta} \dots(3)$$

$$V_3 = V_1^e - V_1^o = V \frac{j(Z_{oe} - Z_{oo}) \tan \theta}{2Z_o + j(Z_{oe} + Z_{oo}) \tan \theta}$$

$$C \equiv \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \rightarrow V_3 = V \frac{jC \tan \theta}{\sqrt{1 - C^2} + j \tan \theta} \dots(4)$$

$$\begin{aligned}
\text{derivation of (1): } Z_{in} &= \frac{V_1}{I_1} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o} = \frac{V \frac{Z_{in}^e}{Z_{in}^e + Z_o} + V \frac{Z_{in}^o}{Z_{in}^o + Z_o}}{\frac{V}{Z_{in}^e + Z_o} + \frac{V}{Z_{in}^o + Z_o}} \\
&= \frac{Z_{in}^e (Z_{in}^o + Z_o) + Z_{in}^o (Z_{in}^e + Z_o)}{Z_{in}^e + Z_{in}^o + 2Z_o} = \frac{Z_o (Z_{in}^e + Z_{in}^o + 2Z_o) + 2Z_{in}^e Z_{in}^o - 2Z_o^2}{Z_{in}^e + Z_{in}^o + 2Z_o} \\
&= Z_o + \frac{2(Z_{in}^e Z_{in}^o - Z_o^2)}{Z_{in}^e + Z_{in}^o + 2Z_o}
\end{aligned}$$

$$\begin{aligned}
\text{derivation of (2): } Z_{in}^e Z_{in}^o &= Z_{oe} \frac{Z_o + jZ_{oe} \tan \theta}{Z_{oe} + jZ_o \tan \theta} Z_{oo} \frac{Z_o + jZ_{oo} \tan \theta}{Z_{oo} + jZ_o \tan \theta} \\
&\stackrel{Z_{oe} Z_{oo} = Z_o^2}{=} Z_{oe} Z_{oo} \frac{\sqrt{Z_{oe} Z_{oo}} + jZ_{oe} \tan \theta}{Z_{oe} + j\sqrt{Z_{oe} Z_{oo}} \tan \theta} \times \frac{1/\sqrt{Z_{oe}}}{1/\sqrt{Z_{oe}}} \frac{\sqrt{Z_{oe} Z_{oo}} + jZ_{oo} \tan \theta}{Z_{oo} + j\sqrt{Z_{oe} Z_{oo}} \tan \theta} \times \frac{1/\sqrt{Z_{oo}}}{1/\sqrt{Z_{oo}}} \\
&= Z_{oe} Z_{oo} \frac{\sqrt{Z_{oo}} + j\sqrt{Z_{oe}} \tan \theta}{\sqrt{Z_{oe}} + j\sqrt{Z_{oo}} \tan \theta} \frac{\sqrt{Z_{oe}} + j\sqrt{Z_{oo}} \tan \theta}{\sqrt{Z_{oo}} + j\sqrt{Z_{oe}} \tan \theta} = Z_{oe} Z_{oo} = Z_o^2 \rightarrow Z_{in} = Z_o : \text{i/p match}
\end{aligned}$$

$$\text{derivation of (3): } V_1^e = V \frac{Z_{in}^e}{Z_{in}^e + Z_o} = V \frac{Z_{oe} \frac{Z_o + jZ_{oe} \tan \theta}{Z_{oe} + jZ_o \tan \theta}}{Z_{oe} \frac{Z_o + jZ_{oe} \tan \theta}{Z_{oe} + jZ_o \tan \theta} + Z_o}$$

$$= V \frac{Z_{oe} Z_o + jZ_{oe}^2 \tan \theta}{2Z_{oe} Z_o + jZ_{oe}^2 \tan \theta + jZ_o^2 \tan \theta} \times \frac{1/Z_{oe}}{1/Z_{oe}} = V \frac{Z_o + jZ_{oe} \tan \theta}{2Z_o + jZ_{oe} \tan \theta + jZ_{oo} \tan \theta}$$

$$V_3 = V_1^e - V_1^o = V \frac{j(Z_{oe} - Z_{oo}) \tan \theta}{2Z_o + j(Z_{oe} + Z_{oo}) \tan \theta}$$

$$\text{derivation of (4): } C \equiv \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \rightarrow V_3 = V \frac{j \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \tan \theta}{\frac{2Z_o}{Z_{oe} + Z_{oo}} + j \tan \theta} = V \frac{jC \tan \theta}{\frac{2Z_o}{Z_{oe} + Z_{oo}} + j \tan \theta}$$

$$\sqrt{1-C^2} = \sqrt{1 - \left(\frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}}\right)^2} = \frac{\sqrt{(Z_{oe} + Z_{oo})^2 - (Z_{oe} - Z_{oo})^2}}{Z_{oe} + Z_{oo}} = \frac{2\sqrt{Z_{oe}Z_{oo}}}{Z_{oe} + Z_{oo}} = \frac{2Z_o}{Z_{oe} + Z_{oo}}$$

$$\rightarrow V_3 = V \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta}$$


$$\begin{bmatrix} V_1^{e,o} \\ I_1^{e,o} \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_{oe,o} \sin \theta \\ jY_{oe,o} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2^{e,o} \\ I_2^{e,o} \end{bmatrix}$$

$$\rightarrow V_2^{e,o} = V \frac{Z_o}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta} \dots\dots(5)$$

$$V_2 = V_2^e + V_2^o = V \frac{2Z_o}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta} = V \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta}$$

$$V_4 = V_2^e - V_2^o = 0$$

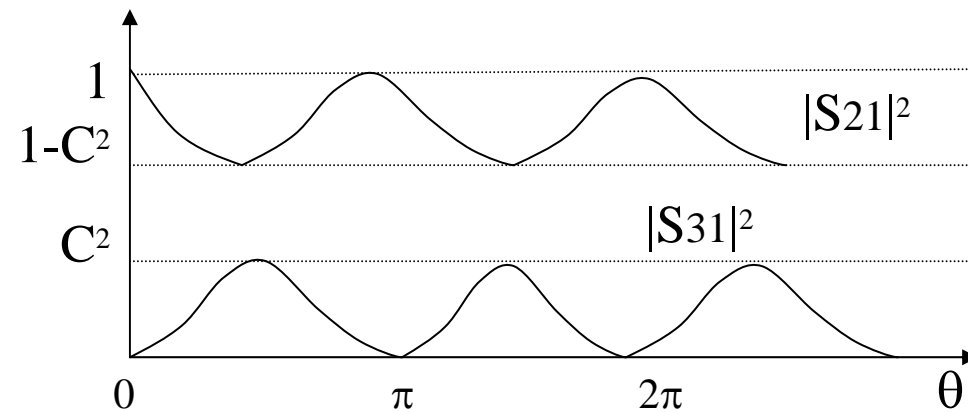3. frequency response at port 2 and port 3



derivation of (5)

$$\begin{bmatrix} V_1^{e,o} \\ I_1^{e,o} \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_{oe,o} \sin \theta \\ jY_{oe,o} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2^{e,o} \\ I_2^{e,o} \end{bmatrix} \rightarrow \begin{bmatrix} V_2^{e,o} \\ I_2^{e,o} \end{bmatrix} = \begin{bmatrix} \cos \theta & -jZ_{oe,o} \sin \theta \\ -jY_{oe,o} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_1^{e,o} \\ I_1^{e,o} \end{bmatrix}$$

$$V_1^{e,o} = V \frac{Z_o + jZ_{oe,o} \tan \theta}{2Z_o + j(Z_{oe} + Z_{oo}) \tan \theta} = V \frac{Z_o \cos \theta + jZ_{oe,o} \sin \theta}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

$$I_1^e = \frac{V}{Z_{in}^e + Z_o}, Z_{in}^e = Z_{oe} \frac{Z_o + jZ_{oe} \tan \theta}{Z_{oe} + jZ_o \tan \theta}$$

$$I_1^e = \frac{V}{Z_{in}^e + Z_o} = \frac{V}{Z_{oe} \frac{Z_o + jZ_{oe} \tan \theta}{Z_{oe} + jZ_o \tan \theta} + Z_o} = V \frac{Z_{oe} + jZ_o \tan \theta}{Z_{oe}(Z_o + jZ_{oe} \tan \theta) + Z_o(Z_{oe} + jZ_o \tan \theta)}$$

$$= V \frac{Z_{oe} + jZ_o \tan \theta}{2Z_{oe}Z_o + j(Z_{oe}^2 + Z_o^2) \tan \theta} \times \frac{1/Z_{oe}}{1/Z_{oe}} = V \frac{1 + j\sqrt{Z_{oo}/Z_{oe}} \tan \theta}{2Z_o + j(Z_{oe} + Z_{oo}) \tan \theta} = V \frac{\cos \theta + j\sqrt{Z_{oo}/Z_{oe}} \sin \theta}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

$$\rightarrow I_1^{e,o} = V \frac{\cos \theta + j\sqrt{Z_{oo,e}/Z_{oe,o}} \sin \theta}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

$$\Rightarrow V_2^{e,o} = \cos \theta V_1^{e,o} - jZ_{oe,o} \sin \theta I_1^{e,o}$$

$$= V \frac{(Z_o \cos \theta + jZ_{oe,o} \sin \theta) \cos \theta}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta} - V \frac{jZ_{oe,o} \sin \theta (\cos \theta + j\sqrt{Z_{oo,e}/Z_{oe,o}} \sin \theta)}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

$$= V \frac{Z_o \cos^2 \theta + jZ_{oe,o} \sin \theta - jZ_{oe,o} \sin \theta + \sqrt{Z_{oe}Z_{oo}} \sin^2 \theta}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

$$= V \frac{Z_o}{2Z_o \cos \theta + j(Z_{oe} + Z_{oo}) \sin \theta}$$

4. selection of line length

$$\theta = \frac{\pi}{2} \rightarrow l = \frac{\lambda}{4}$$

$$V_1 = 1$$

$$V_2 = -j\sqrt{1-C^2}, P_2 = (1-C^2)P_1$$

$$V_3 = C, P_2 = C^2 P_1$$

$$V_4 = 0$$

$$\theta = \pi \rightarrow l = \frac{\lambda}{2}$$

$$V_1 = 1$$

$$V_2 = 1$$

$$V_3 = 0$$

$$V_4 = 0$$

$\theta = \frac{\pi}{2}$, V_2 and V_3 have 90° phase difference \rightarrow quadrature coupler


5. In general $v_e \neq v_o \rightarrow \theta_e \neq \theta_o$, coupled line coupler is suited for a weakly coupled coupler.
6. $C=3\text{dB} \rightarrow Z_{oe}=120.7\Omega$, $Z_{oo}=20.7\Omega \rightarrow S$ becomes not practical and coupled line theory is not applicable \rightarrow Lange coupler

7. Ex.7.7 design a 20dB coupled stripline coupler, $b=0.32\text{cm}$,
 $\epsilon_r=2.2$, $Z_0=50\Omega$, $f=3\text{GHz}$.

$$C = 10^{-20/20} = 0.1 \rightarrow Z_{oe} = 55.28\Omega, Z_{oo} = 45.23\Omega$$

from p.339, Fig. 7.29, $W/b = 0.809$, $S/b = 0.306 \rightarrow S = 0.098\text{cm}$
 frequency response (p.346, Fig. 7.34)

- multisection coupled line coupler

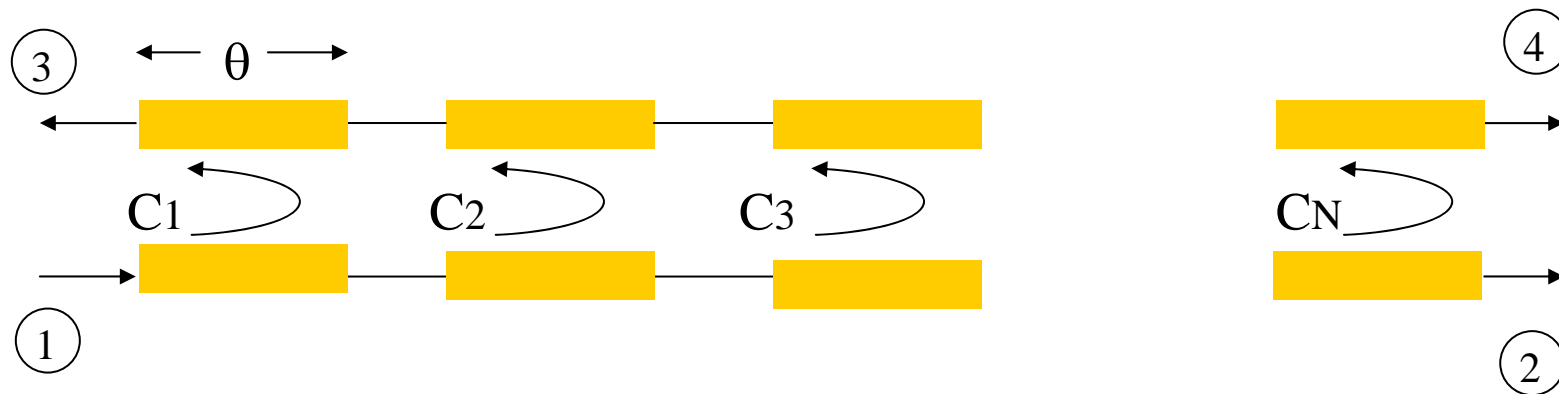

$C \ll 1, N : \text{odd}$

$$\text{single section } \frac{V_3}{V_1} = \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta} \approx \frac{jC \tan \theta}{1 + j \tan \theta} = jC \sin \theta e^{-j\theta}$$

$$\frac{V_2}{V_1} = \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta} \approx \frac{1}{\cos \theta + j \sin \theta} = e^{-j\theta}$$

$$\text{multisection } \frac{V_3}{V_1} = jC_1 \sin \theta e^{-j\theta} + jC_2 \sin \theta e^{-j\theta} e^{-j2\theta} + \dots + jC_N \sin \theta e^{-j\theta} e^{-j2(N-1)\theta}$$

if $C_1 = C_N, C_2 = C_{N-1}, \dots$

$$\frac{V_3}{V_1} = j2 \sin \theta e^{-jN\theta} [C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots + \frac{1}{2} C_M], M = \frac{N+1}{2}$$

$$C = \frac{V_3}{V_1} \left(\theta = \frac{\pi}{2} \right), \frac{V_3}{V_1}(\theta) \rightarrow C_n \Rightarrow S_n, W_n$$

Discussion

1. Ex. 7.8 design a 20dB coupler with binomial response, $N=3$,
 $Z_0=50\Omega$, $f_0=3\text{GHz}$.


$$C = \left| \frac{V_3}{V_1} \right| = 2 \sin \theta \left[C_1 \cos 2\theta + \frac{1}{2} C_2 \right] = C_1 \sin 3\theta + (C_2 - C_1) \sin \theta$$

$$\left. \frac{dC}{d\theta} \right|_{\theta=\frac{\pi}{2}} = 0, \quad \left. \frac{d^2C}{d\theta^2} \right|_{\theta=\frac{\pi}{2}} = 10C_1 - C_2 = 0, \quad C\left(\frac{\pi}{2}\right) = C_2 - 2C_1 = 10^{-20/20} = 0.1$$

$$\begin{aligned} \rightarrow C_1 = C_3 = 0.0125 &\rightarrow Z_{oe}^1 = Z_{oe}^3 = 50.63\Omega, Z_{oo}^1 = Z_{oo}^3 = 49.38\Omega \\ C_2 = 0.125 &\rightarrow Z_{oe}^2 = 56.69\Omega, Z_{oo}^2 = 44.1\Omega \end{aligned}$$


frequency response (p.348, Fig. 7.37)

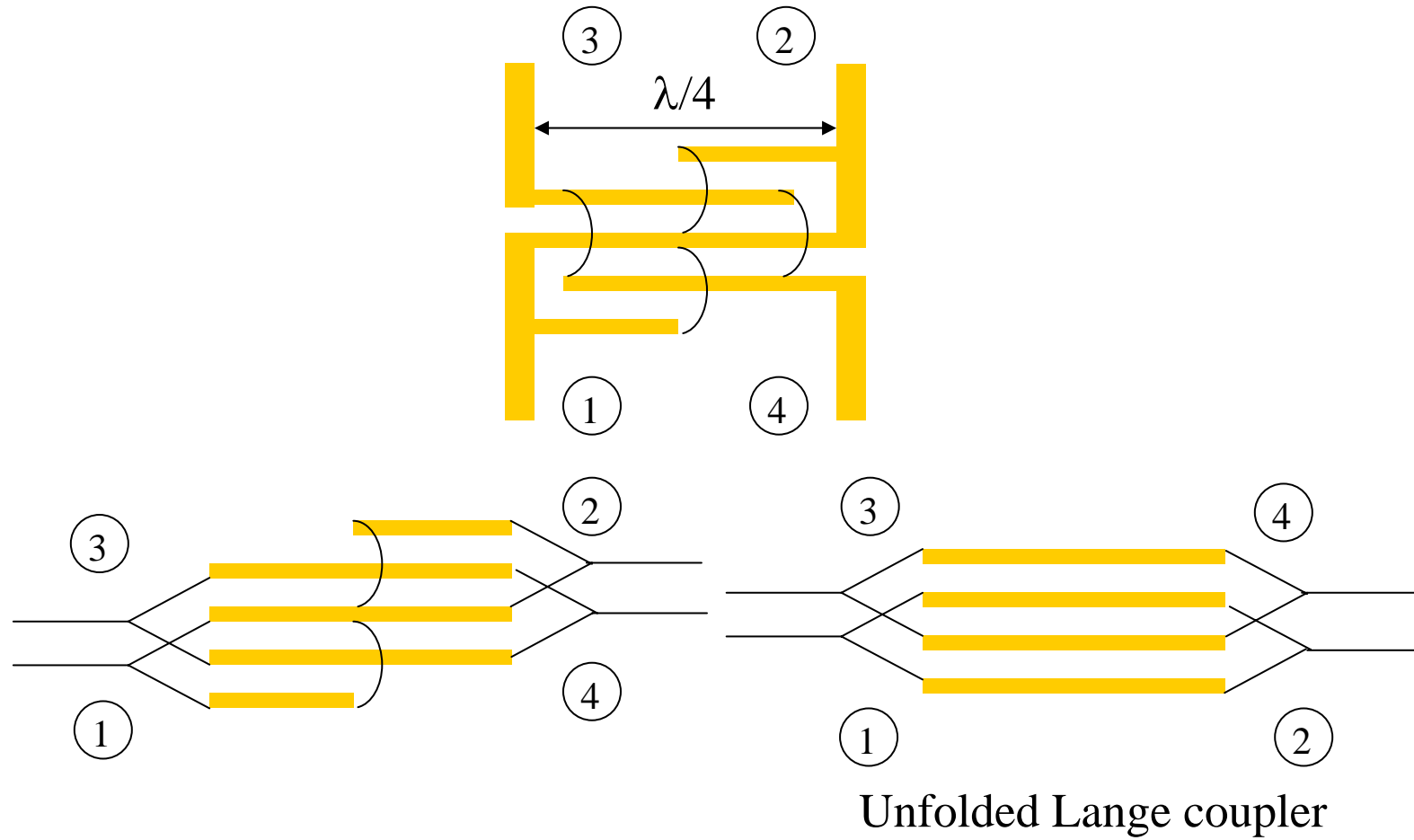7.7 The Lange coupler (interdigitated coupler)




Unfolded Lange coupler


four-wire coupled line model

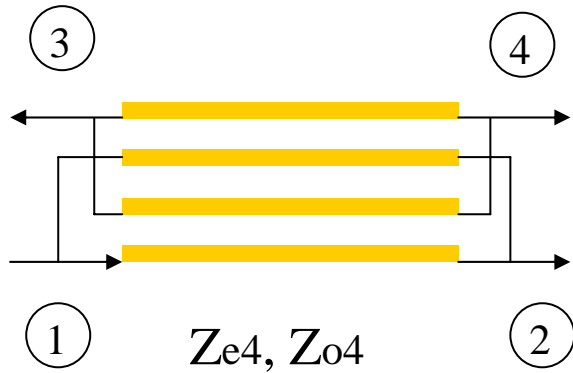

even + + + +
 odd + - + -

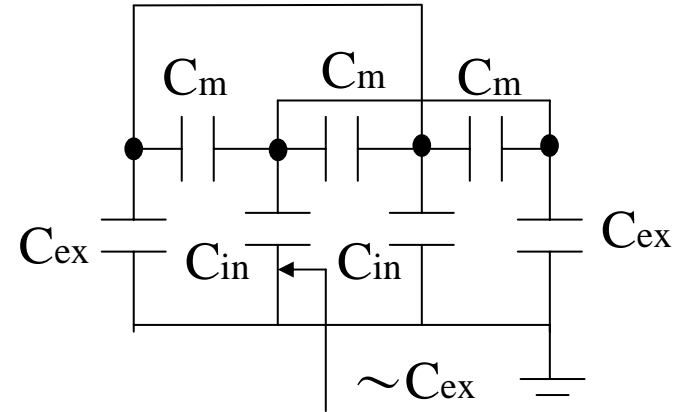

approximate two-wire coupled line model

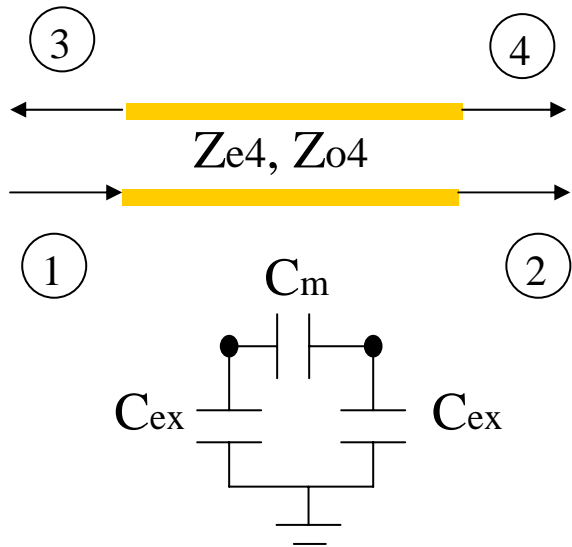

nearest neighbor coupling

$$C_{ex} \approx C_{in} + C_m \text{ in series with } C_{ex}$$

$$\rightarrow C_{in} \approx C_{ex} - \frac{C_{ex} C_m}{C_{ex} + C_m}$$

$$C_{e4} = C_{ex} + C_{in}$$

$$C_{o4} = C_{ex} + C_{in} + 3 \times 2C_m$$

$$C_e = C_{ex}$$

$$C_o = C_{ex} + 2C_m$$

$$\text{4-line model: } C_{e4} = C_{ex} + C_{in}, C_{o4} = C_{ex} + C_{in} + 6C_m$$

$$\text{2-line model: } C_e = C_{ex}, C_o = C_{ex} + 2C_m$$

$$\rightarrow C_{e4} = \frac{C_e(3C_e + C_o)}{C_e + C_o}, C_{o4} = \frac{C_o(3C_o + C_e)}{C_e + C_o} \dots (1)$$

$$Z_o = \frac{1}{vC} \Rightarrow Z_{e4} = \frac{Z_{oo} + Z_{oe}}{3Z_{oo} + Z_{oe}} Z_{oe}, Z_{o4} = \frac{Z_{oo} + Z_{oe}}{3Z_{oe} + Z_{oo}} Z_{oo} \dots (2)$$

$$Z_o = \sqrt{Z_{e4} Z_{o4}}, C \equiv \frac{Z_{e4} - Z_{o4}}{Z_{e4} + Z_{o4}} \rightarrow \begin{aligned} Z_{oe} &= \frac{4C - 3 + \sqrt{9 - 8C^2}}{2C \sqrt{(1-C)/(1+C)}} Z_o \\ Z_{oo} &= \frac{4C - 3 - \sqrt{9 - 8C^2}}{2C \sqrt{(1+C)/(1-C)}} Z_o \end{aligned} \Rightarrow W, S$$

Discussion

1. Lange coupler is suitable for wideband 3dB 90° hybrid, and MMIC design uses air bridges instead of bond wires.

$$\text{derivation of (1): 4-line: } C_{e4} = C_{ex} + C_{in} \quad C_{in} \approx C_{ex} - \frac{C_{ex}C_m}{C_{ex}+C_m} = 2C_{ex} - \frac{C_{ex}C_m}{C_{ex}+C_m}$$

$$\text{2-line: } C_e = C_{ex}, C_o = C_{ex} + 2C_m \rightarrow C_m = \frac{C_o - C_e}{2}$$

$$C_{e4} = 2C_e - \frac{C_e \frac{C_o - C_e}{2}}{C_e + \frac{C_o - C_e}{2}} = 2C_e - \frac{C_e C_o - C_e^2}{C_e + C_o} = \frac{2C_e^2 + 2C_e C_o - C_e C_o + C_e^2}{C_e + C_o} = \frac{C_e(3C_e + C_o)}{C_e + C_o}$$

$$C_{o4} = C_{ex} + C_{in} + 6C_m = \frac{C_e(3C_e + C_o)}{C_e + C_o} + 3(C_o - C_e) = \frac{3C_e^2 + C_e C_o + 3C_o^2 - 3C_e^2}{C_e + C_o} = \frac{C_o(3C_o + C_e)}{C_e + C_o}$$


$$\text{derivation of (2): } Z_o = \frac{1}{vC}$$

$$\Rightarrow Z_{e4} = \frac{1}{vC_{e4}} = \frac{1}{v \frac{C_e(3C_e + C_o)}{C_e + C_o}} = \frac{1}{vC_e} \frac{C_e + C_o}{3C_e + C_o} \times \frac{1/vC_e C_o}{1/vC_e C_o} = \frac{1}{vC_e} \frac{1/vC_o + 1/vC_e}{3/vC_o + 1/vC_e} = Z_{oe} \frac{Z_{oo} + Z_{oe}}{3Z_{oo} + Z_{oe}}$$

$$Z_{o4} = \frac{1}{vC_{o4}} = \frac{1}{v \frac{C_o(3C_o + C_e)}{C_e + C_o}} = \frac{1}{vC_o} \frac{C_e + C_o}{3C_o + C_e} \times \frac{1/vC_e C_o}{1/vC_e C_o} = \frac{1}{vC_o} \frac{1/vC_o + 1/vC_e}{3/vC_e + 1/vC_o} = Z_{oo} \frac{Z_{oo} + Z_{oe}}{3Z_{oe} + Z_{oo}}$$

7.8 The 180° hybrid

- rat-race coupler

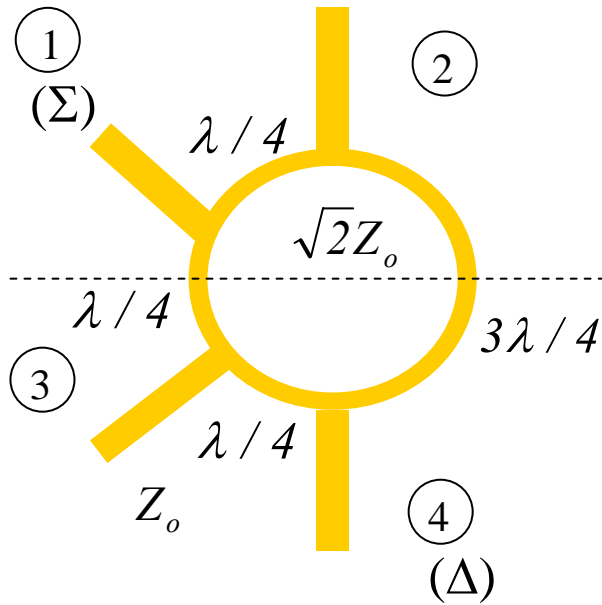

(1) input port 1

port 1 match $\rightarrow \sqrt{2Z_o Z_o} = \sqrt{2}Z_o$

$\frac{3}{4}\lambda - \frac{1}{4}\lambda = \frac{\lambda}{2} \rightarrow$ port 4 "GND"

or isolated port


(2) input ports 2 and 3

\rightarrow port 1 : Σ port, port 4 : Δ port

$$-\frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

Discussion

1. even-odd mode analysis


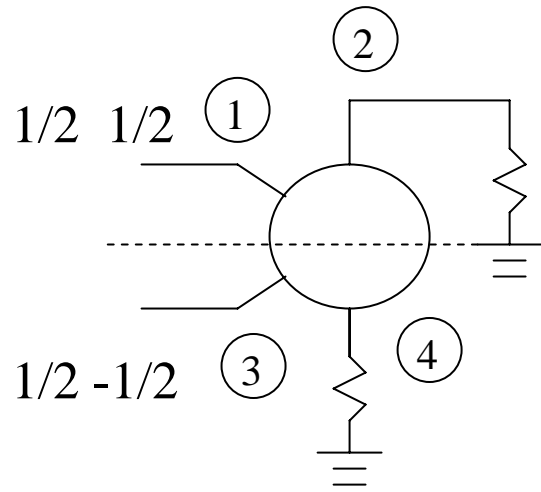



$$b_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o,$$

$$b_2 = \frac{1}{2}T_e + \frac{1}{2}T_o$$


$$b_3 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o,$$
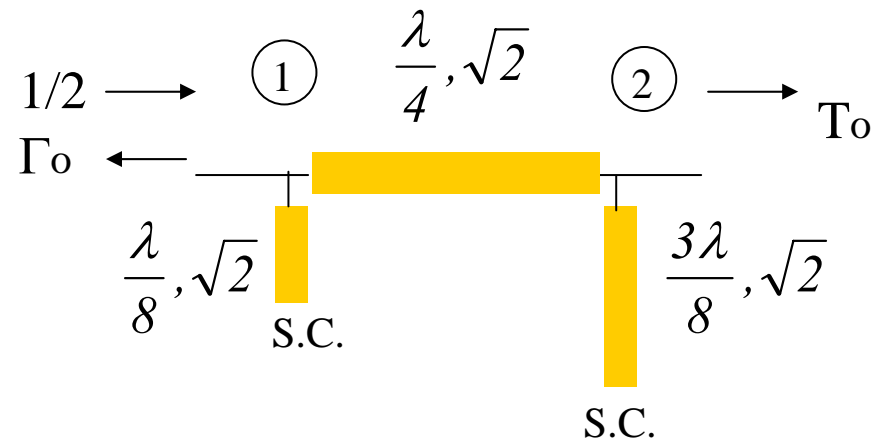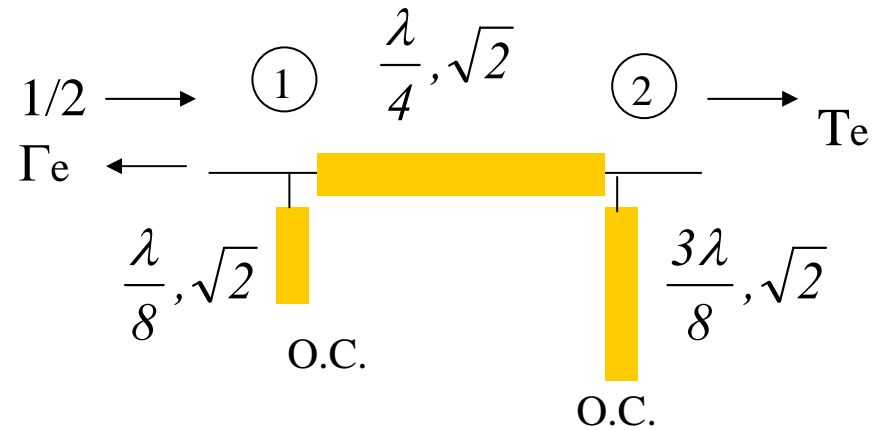
$$b_4 = \frac{1}{2}T_e - \frac{1}{2}T_o$$



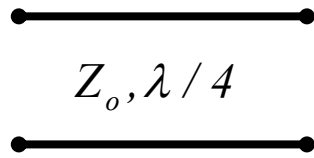
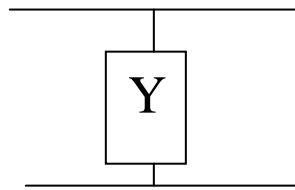
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & jZ_o \\ jY_o & 0 \end{bmatrix}$$



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{cases} \begin{bmatrix} 1 & 0 \\ jY_o & 1 \end{bmatrix} & \text{even - mode open - circuit } \lambda/8 \text{ stub} \\ \begin{bmatrix} 1 & 0 \\ -jY_o & 1 \end{bmatrix} & \text{even - mode open - circuit } 3\lambda/8 \text{ stub} \\ \begin{bmatrix} 1 & 0 \\ -jY_o & 1 \end{bmatrix} & \text{odd - mode short - circuit } \lambda/8 \text{ stub} \\ \begin{bmatrix} 1 & 0 \\ jY_o & 1 \end{bmatrix} & \text{odd - mode short - circuit } 3\lambda/8 \text{ stub} \end{cases}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} 1 & 0 \\ \frac{j}{\sqrt{2}} & 1 \end{bmatrix} \begin{bmatrix} 0 & j\sqrt{2} \\ \frac{j}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -\frac{j}{\sqrt{2}} & 1 \end{bmatrix} = \begin{bmatrix} 1 & j\sqrt{2} \\ j\sqrt{2} & -1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} 1 & 0 \\ -\frac{j}{\sqrt{2}} & 1 \end{bmatrix} \begin{bmatrix} 0 & j\sqrt{2} \\ \frac{j}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{j}{\sqrt{2}} & 1 \end{bmatrix} = \begin{bmatrix} -1 & j\sqrt{2} \\ j\sqrt{2} & 1 \end{bmatrix}$$

$$\rightarrow \Gamma_e = -\frac{j}{\sqrt{2}}, \Gamma_o = \frac{j}{\sqrt{2}}, T_e = -\frac{j}{\sqrt{2}}, T_o = -\frac{j}{\sqrt{2}}$$

$$\Rightarrow b_1 = 0, b_2 = -\frac{j}{\sqrt{2}}, b_3 = -\frac{j}{\sqrt{2}}, b_4 = 0$$


2. input port 2 \rightarrow ports 1, 4 180° phase difference, port 3 isolated port
input port 4 \rightarrow ports 2, 3 180° phase difference, port 1 isolated port

3. Ex. 7.9 3dB rat-race hybrid $Z_o=70.7\Omega$, BW 20~30% (p.357, Fig.7.46)


4.

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = -\frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ a_2 \\ a_3 \\ 0 \end{bmatrix} = -\frac{j}{\sqrt{2}} \begin{bmatrix} a_2 + a_3 \\ 0 \\ 0 \\ -a_2 + a_3 \end{bmatrix}$$

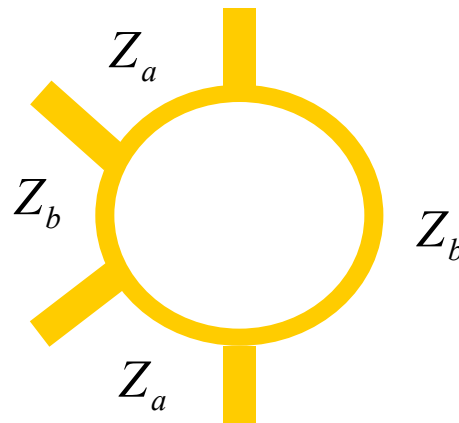5. Unequal power division rat-race coupler uses Z_a , Z_b lines



• tapered coupled line hybrid

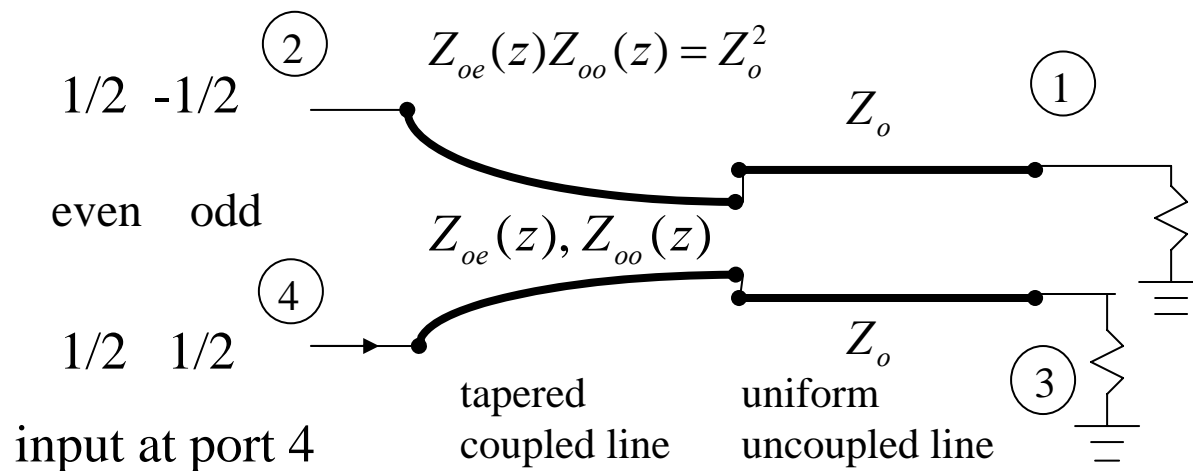


$$b_1 = \frac{1}{2}T_e - \frac{1}{2}T_o$$



$$b_2 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o$$

$$b_3 = \frac{1}{2}T_e + \frac{1}{2}T_o$$
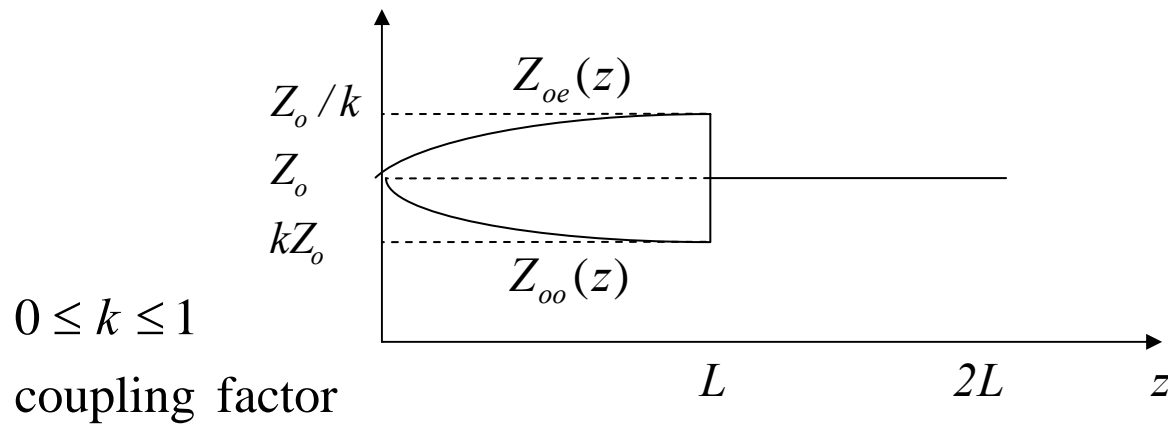
$$b_4 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o$$



b_1	b_2	b_3	b_4
b_2	b_1	b_4	b_3
b_3	b_4	b_1	b_2
b_4	b_3	b_2	b_1

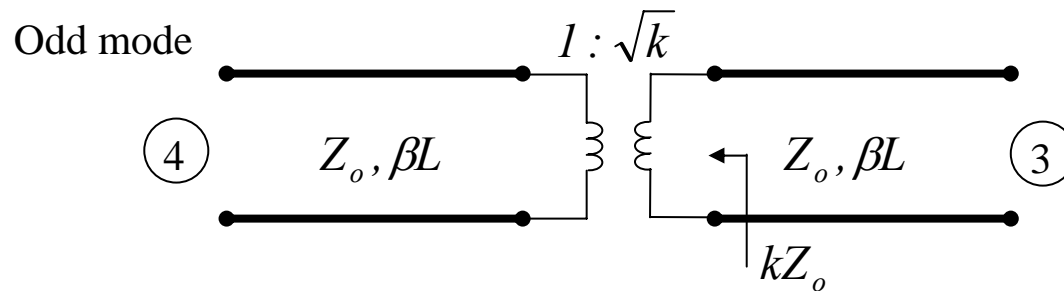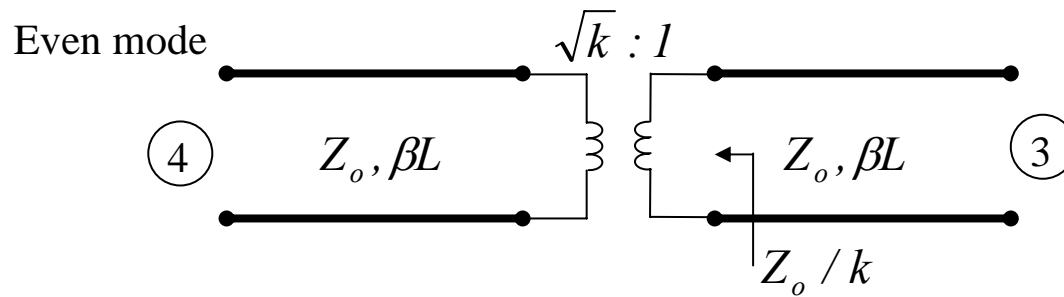

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} \cos \theta & j \sin \theta \\ j \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} \sqrt{k} & 0 \\ 0 & \frac{1}{\sqrt{k}} \end{bmatrix} \begin{bmatrix} \cos \theta & j \sin \theta \\ j \sin \theta & \cos \theta \end{bmatrix} \quad (\text{p.185, Table 4.1})$$

$$= \begin{bmatrix} \sqrt{k} \cos^2 \theta - \frac{1}{\sqrt{k}} \sin^2 \theta & j(\sqrt{k} + \frac{1}{\sqrt{k}}) \sin \theta \cos \theta \\ j(\sqrt{k} + \frac{1}{\sqrt{k}}) \sin \theta \cos \theta & -\sqrt{k} \sin^2 \theta + \frac{1}{\sqrt{k}} \cos^2 \theta \end{bmatrix} \rightarrow \begin{aligned} \Gamma_e &= \frac{A + B - C - D}{A + B + C + D} \\ T_e &= \frac{2}{A + B + C + D} \end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} \cos \theta & j \sin \theta \\ j \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} \frac{1}{\sqrt{k}} & 0 \\ 0 & \sqrt{k} \end{bmatrix} \begin{bmatrix} \cos \theta & j \sin \theta \\ j \sin \theta & \cos \theta \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{\sqrt{k}} \cos^2 \theta - \sqrt{k} \sin^2 \theta & j(\sqrt{k} + \frac{1}{\sqrt{k}}) \sin \theta \cos \theta \\ j(\sqrt{k} + \frac{1}{\sqrt{k}}) \sin \theta \cos \theta & -\frac{1}{\sqrt{k}} \sin^2 \theta + \sqrt{k} \cos^2 \theta \end{bmatrix} \rightarrow \begin{cases} \Gamma_o = \frac{A+B-C-D}{A+B+C+D} \\ T_o = \frac{2}{A+B+C+D} \end{cases}$$

$$\rightarrow \Gamma_e = \frac{k-1}{k+1} e^{-j2\theta}, \Gamma_o = \frac{1-k}{k+1} e^{-j2\theta}, T_e = \frac{2\sqrt{k}}{k+1} e^{-j2\theta}, T_o = \frac{2\sqrt{k}}{k+1} e^{-j2\theta}$$

$$\Rightarrow b_1 = 0 = S_{14}, b_2 = \frac{k-1}{k+1} e^{-j2\theta} \equiv -\alpha e^{-j2\theta} = S_{24},$$

$$b_3 = \frac{2\sqrt{k}}{k+1} e^{-j2\theta} \equiv \beta e^{-j2\theta} = S_{34}, b_4 = 0 = S_{44}$$

$$|\alpha|^2 + |\beta|^2 = 1$$

$$b_1 = \frac{1}{2} T_e - \frac{1}{2} T_o$$

$$b_2 = \frac{1}{2} \Gamma_e - \frac{1}{2} \Gamma_o$$

$$b_3 = \frac{1}{2} T_e + \frac{1}{2} T_o$$

$$b_4 = \frac{1}{2} \Gamma_e + \frac{1}{2} \Gamma_o$$

input at port 2 = input at port 4 $\rightarrow S_{12} = S_{34}, S_{22} = S_{44}, S_{32} = S_{14}, S_{42} = S_{24}$

reciprocal $\rightarrow S_{23} = S_{32}, S_{41} = S_{14}$



input at port 1 $\rightarrow \Gamma_e = \frac{1-k}{k+1} e^{-j2\theta}, \Gamma_o = \frac{k-1}{k+1} e^{-j2\theta}$

$\Rightarrow b_1 = \frac{1}{2}(\Gamma_e + \Gamma_o) = 0 = S_{11}, b_3 = \frac{1}{2}(\Gamma_e - \Gamma_o) = \frac{1-k}{k+1} e^{-j2\theta} \equiv \alpha e^{-j2\theta} = S_{31}$


input at port 3 = input at port 1 $\rightarrow S_{13} = S_{31}$

$$\Rightarrow [S] = e^{-j2\theta} \begin{bmatrix} 0 & \beta & \alpha & 0 \\ \beta & 0 & 0 & -\alpha \\ \alpha & 0 & 0 & \beta \\ 0 & -\alpha & \beta & 0 \end{bmatrix}$$

• waveguide magic-T

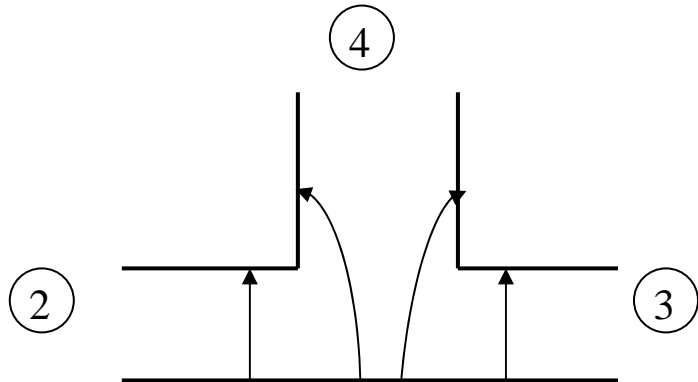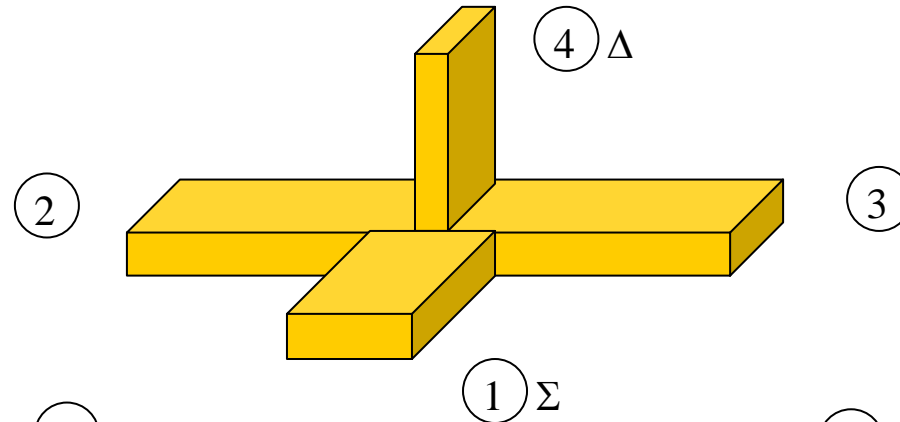

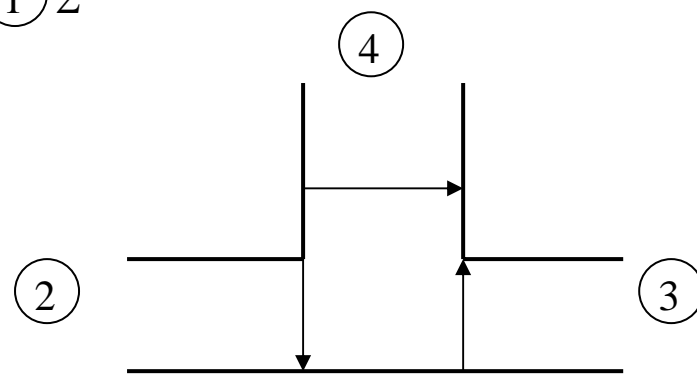
input at port 1
 port 4: 0
 port 2 and port 3: equal
 amplitude and phase



input at port 4
 port 1: 0
 port 2 and port 3: 180° phase
 difference

7.9 Other couplers


- reflectometer

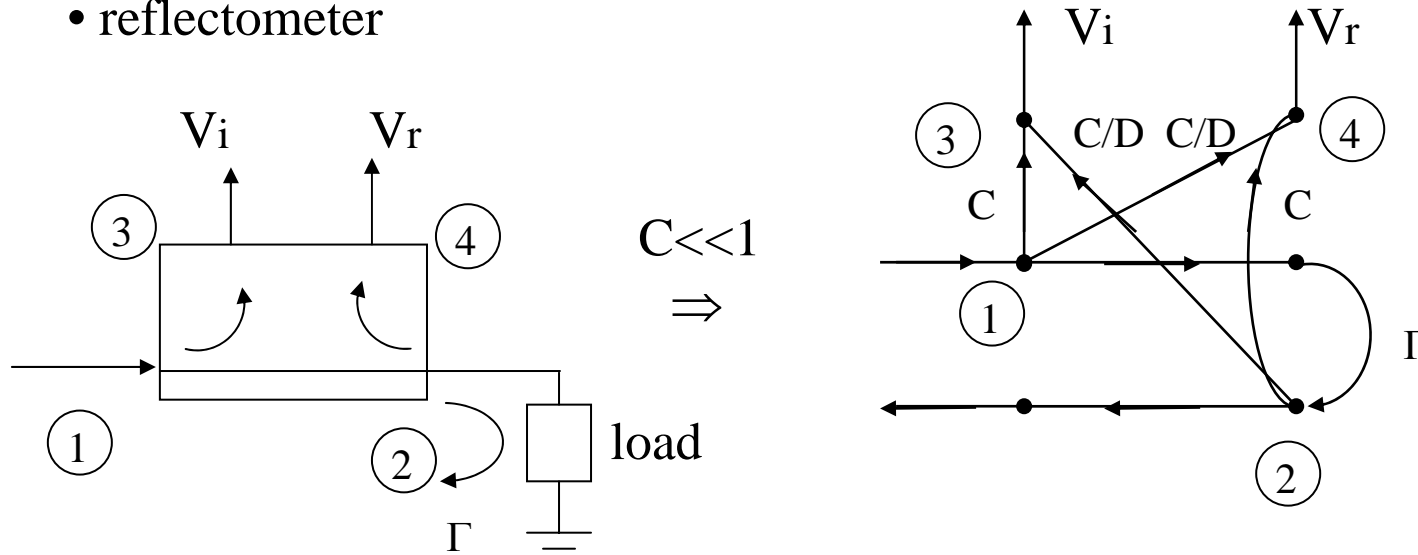

$$V_i = C + \frac{C}{D} \Gamma e^{j\theta}, V_r = \frac{C}{D} + C \Gamma e^{j\phi}$$

$$\left| \frac{V_r}{V_i} \right|_{\max, \min} = \frac{|\Gamma| \pm \frac{1}{D}}{1 \mp \frac{|\Gamma|}{D}}, \text{ as } D \rightarrow \infty \left| \frac{V_r}{V_i} \right| \rightarrow \Gamma$$

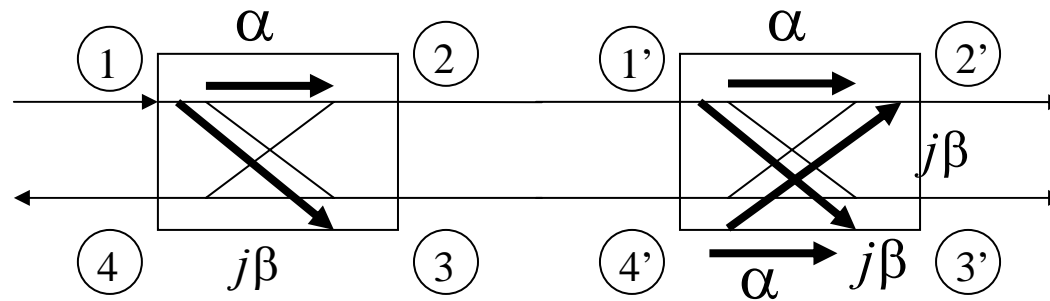Prob. 7.3 Two 90° 8.34dB couplers are connected in cascade, find $S_{2'1}, S_{3'1}$



$$C = 8.34 \text{ dB} = -20 \log \beta \rightarrow \beta = 0.383, \alpha^2 + \beta^2 = 1 \rightarrow \alpha = 0.924$$


$$V_{3'}^- = \alpha V_{4'}^+ + j\beta V_{1'}^+ = \alpha V_3^- + j\beta V_2^- = \alpha(j\beta V_1^+) + j\beta(\alpha V_1^+) \\ = 2j\alpha\beta V_1^+ = 0.707 \angle 90^\circ V_1^+$$

$$V_{2'}^- = \alpha V_{1'}^+ + j\beta V_{4'}^+ = \alpha V_2^- + j\beta V_3^- = \alpha(\alpha V_1^+) + j\beta(j\beta V_1^+) \\ = (\alpha^2 - \beta^2)V_1^+ = 0.707 V_1^+$$


$$V_{4'}^- = 0$$

\Rightarrow 3dB quadrature coupler

connection problem in microstrip circuits

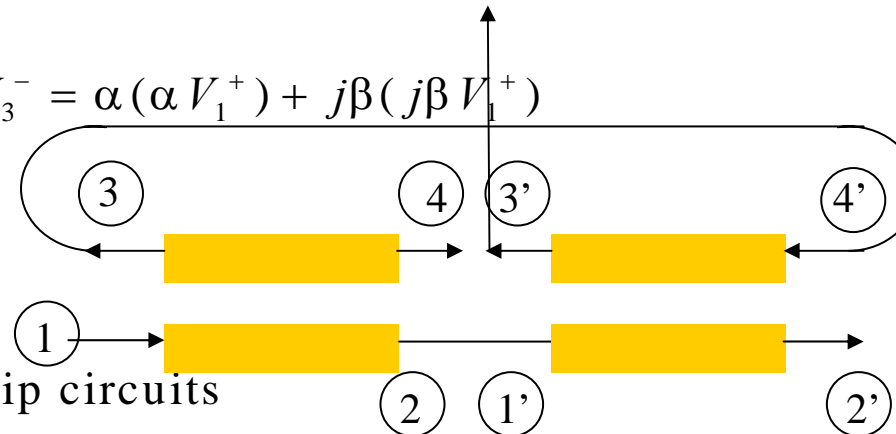

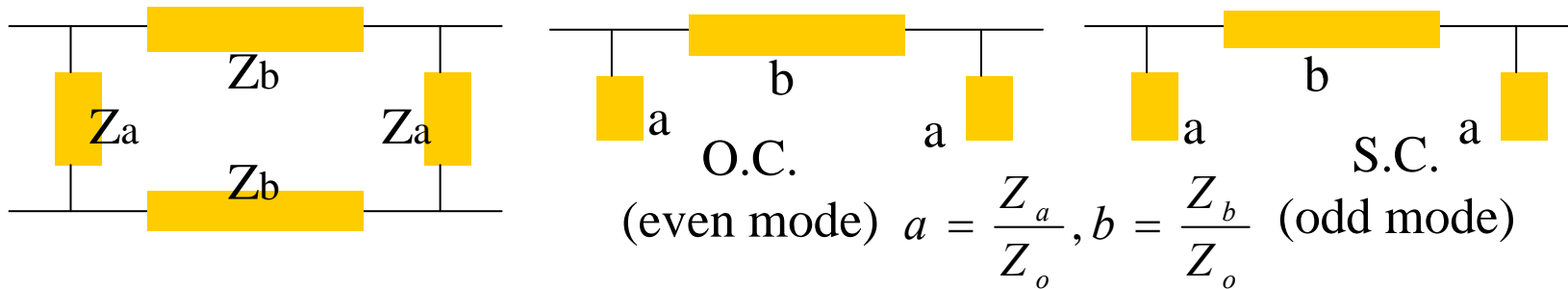Prob. 7.17 Design an unequal power branch-line coupler



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} 1 & 0 \\ j/a & 1 \end{bmatrix} \begin{bmatrix} 0 & jb \\ j/b & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j/a & 1 \end{bmatrix} = \begin{bmatrix} -b/a & jb \\ j/b - jb/a^2 & -b/a \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} 1 & 0 \\ -j/a & 1 \end{bmatrix} \begin{bmatrix} 0 & jb \\ j/b & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j/a & 1 \end{bmatrix} = \begin{bmatrix} b/a & jb \\ j/b - jb/a^2 & b/a \end{bmatrix}$$

$$\rightarrow \Gamma_e = \frac{j(b-1/b+b/a^2)}{-2b/a+j(b+1/b-b/a^2)}, \Gamma_o = \frac{j(b-1/b+b/a^2)}{2b/a+j(b+1/b-b/a^2)}, T_e = \frac{1}{-b/a+jb}, T_o = \frac{1}{b/a+jb}$$

input match $b_1 = \frac{1}{2}(\Gamma_e + \Gamma_o) = 0 \rightarrow 1 - \frac{1}{b^2} + \frac{1}{a^2} = 0 \dots (1)$

$$b_2 = \frac{1}{2}(T_e + T_o) = \frac{-j}{b(1+1/a^2)}, b_3 = \frac{1}{2}(T_e - T_o) = \frac{-1/a}{b(1+1/a^2)}, P_2 = \alpha P_3 \rightarrow |b_2|^2 = \alpha |b_3|^2 \Rightarrow 1 = \frac{\alpha}{a^2} \rightarrow a = \sqrt{\alpha}$$

$$(1) \rightarrow b = \frac{a}{\sqrt{1+a^2}} = \sqrt{\frac{\alpha}{1+\alpha}} \Rightarrow Z_a = \sqrt{\alpha} Z_o, Z_b = \sqrt{\frac{\alpha}{1+\alpha}} Z_o$$

Suggested homework (due 2 weeks): 4, 6, 8, 28, 29, 33

ADS examples: Ch7_prj