

Chapter 8 Microwave filters

8.3 Filter design by the insertion loss method

power loss ratio, maximally flat and equal-ripple LPF
prototypes

8.4 Filter transformations

impedance and frequency scaling, LPF \rightarrow HPF, BPF, BSF

8.5 Filter implementation

Richard's transformation, Kuroda's identities

8.6 Stepped-impedance low-pass filters

microstrip LPF

8.7 Coupled line filters


Z- and Y-inverters, microstrip BPF

8.8 Filters using coupled resonators

BSF, BPF

8.3 Filter design by the insertion loss method

- Power loss ratio (insertion loss)

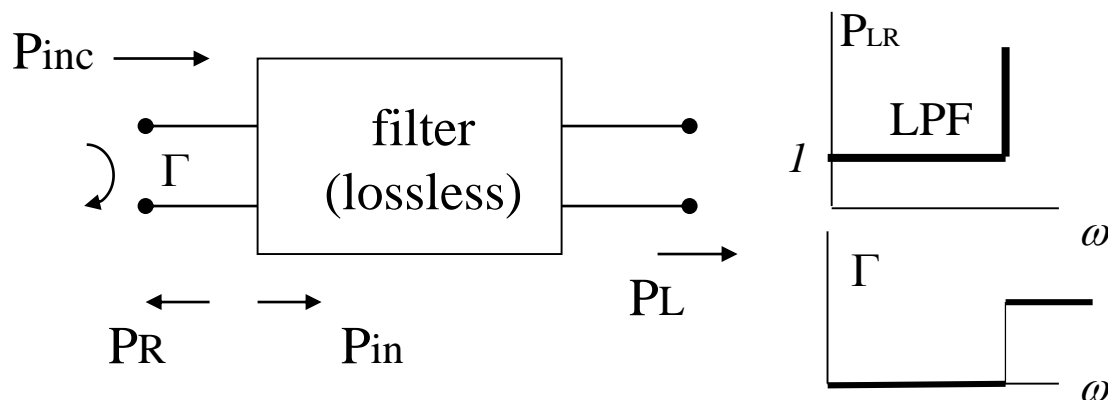

$$\begin{aligned}
 P_{LR} &\equiv \frac{P_{inc}}{P_L} = \frac{P_{inc}}{P_{inc} - P_R} \\
 &= \frac{1}{1 - |\Gamma(\omega)|^2} \\
 &= \frac{1}{1 - \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)}} \\
 &= 1 + \frac{M(\omega^2)}{N(\omega^2)}
 \end{aligned}$$

Discussion

1. P_{inc} ($= P_{avs}$, available power from source) $= P_{in} + P_R$

$P_{in} = P_L$ for a lossless filter

insertion loss $IL \equiv 10 \log P_{LR} = 10 \log \frac{P_{inc}}{P_L}$ ($= -10 \log G_T$) (12.13)

($= -20 \log |S_{21}|$, if $\Gamma_S = \Gamma_L = 0$)

return loss $RL \equiv 10 \log \frac{P_{inc}}{P_R} = -20 \log |\Gamma|$

2. $|\Gamma(w)|^2$ is an even function of $w \rightarrow |\Gamma(w)|^2 = \frac{M(w^2)}{M(w^2) + N(w^2)}$ (p.173)

$\because v(t) : \text{real} \rightarrow \text{Re}V(w) : \text{even}, \text{Im}V(w) : \text{odd} \rightarrow V(-w) = V^*(w)$

$I(-w) = I^*(w), Z(-w) = Z^*(w), \Gamma(-w) = \Gamma^*(w)$

$|\Gamma(w)|^2 = \Gamma(w)\Gamma^*(w) = \Gamma(w)\Gamma(-w), |\Gamma(-w)|^2 = \Gamma(-w)\Gamma^*(-w) = \Gamma(-w)\Gamma(w)$

3. Maximally flat (Butterworth, binomial) LPF

$P_{LR}(w) = 1 + \varepsilon \left(\frac{w}{w_c}\right)^{2N}, w_c : \text{cutoff frequency}, \varepsilon = 1 \rightarrow P_{LR}(w_c) = 2 = 3dB$

stopband attenuation $20NdB / \text{decade}$

4. Equal ripple (Chebyshev, optimal) LPF

$P_{LR}(w) = 1 + \varepsilon T_N^2\left(\frac{w}{w_c}\right)^{2N}, P_{LR}(w_c) = 1 + \varepsilon$

ripple $10^{\log(1+\varepsilon)}$ in passband, stopband attenuation $20NdB / \text{decade}$

frequency responses (p.400, Fig. 8.21)


5. Filter design procedure:


specification \rightarrow LPF prototype \rightarrow LPF, HPF, BPF, or BSF
transformation \rightarrow microstrip realization

6. Filter specification:

frequency range, BW, IL, stopband attenuation and frequencies,
input and output impedances, VSWR, group delay, phase
linearity, temperature range, and transient response.

• LPF prototype

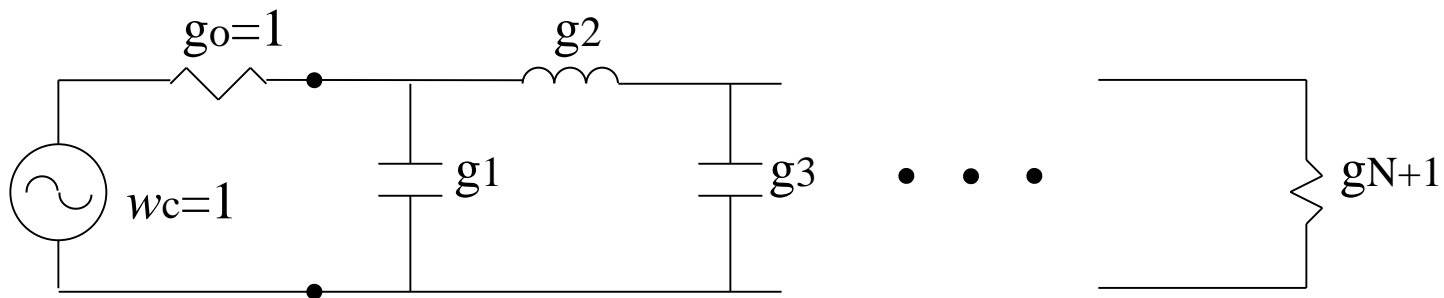

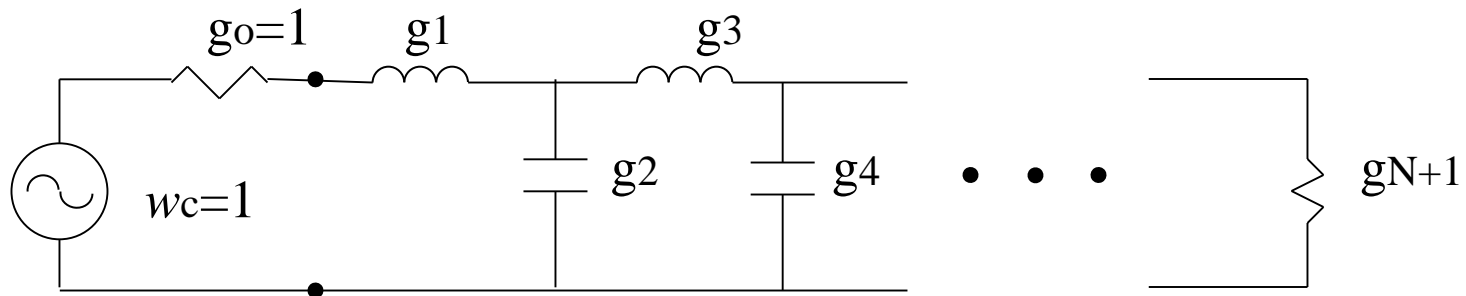

Discussion

1. Maximally flat LPF prototype design equations

$$IL = 10 \log \left[1 + \left(\frac{w}{w_c} \right)^{2N} \right]$$

$$w_c = 1, g_o = g_{N+1} = 1, g_k = 2 \sin \frac{(2k-1)\pi}{2N} \quad k = 1, 2, \dots, N$$

$$N = \frac{\log(10^{IL(w)/10} - 1)}{2 \log \frac{w}{w_c}}$$

2. Element values for maximally flat LPF prototype are given in Table 8.3 of p.404, frequency response given in Fig. 8.26 of p.405.
3. Equal-ripple LPF prototype design equations

$$IL = 10 \log \left[1 + \varepsilon T_N^2 \left(\frac{w}{w_c} \right) \right]$$

$$\varepsilon = 10^{\frac{\text{ripple}(dB)}{10}} - 1$$

$$T_N(w) = \begin{cases} \cos \left(N \cos^{-1} \frac{w}{w_c} \right) & 0 \leq w \leq w_c \\ \cosh \left(N \cosh^{-1} \frac{w}{w_c} \right) & w > w_c \end{cases}$$

$$N = \frac{\cosh^{-1} \left[10^{IL(w)/10} - 1 \right] / \left[10^{\frac{\text{ripple}(dB)}{10}} - 1 \right]}{\cos^{-1} \left(\frac{w}{w_c} \right)}$$

$$w_c = 1, g_o = 1, g_1 = \frac{2a_1}{\gamma}, g_{N+1} = \begin{cases} 1, & N \text{ odd} \\ \coth^2 \frac{\beta}{4}, & N \text{ even} \end{cases}$$

$$\gamma = \sinh \frac{\beta}{2N}$$

$$\beta = \ln \left[\coth \frac{10 \log(\epsilon + 1)}{17.37} \right]$$

$$g_k = \frac{4a_{k-1}a_k}{b_{k-1}b_k}, \quad k = 2, 3, \dots, N$$

$$a_k = \sin \frac{(2k-1)\pi}{2N}, \quad b_k = \gamma^2 + \sin^2 \frac{k\pi}{N}, \quad k = 1, 2, \dots, N$$

4. Element values for equal-ripple LPF prototype (p.406, Table 8.4) and frequency response (p.407, Fig. 8.27)

8.4 Filter transformations

- Impedance scaling $g_o = 1 \rightarrow R_o \Rightarrow \text{impedance} \times R_o$

$$\text{scaled values: } R_S' = R_o, R_L' = R_o R_L, L' = R_o L, C' = \frac{C}{R_o}$$

- Frequency scaling

$$w: 1 \rightarrow w_c \Rightarrow P'_{LR}(w) = P_{LR}\left(\frac{w}{w_c}\right) \Rightarrow \text{same impedance, } w \leftarrow \frac{w}{w_c}$$

$$jX_L = j \frac{w}{w_c} L = jwL' \rightarrow L' = \frac{L}{w_c}$$

scaled values:

$$jB_C = j \frac{w}{w_c} C = jwC' \rightarrow C' = \frac{C}{w_c}$$

- Impedance and frequency scaling


$$\text{scaled values: } R_S' = R_o, R_L' = R_o R_L, L' = \frac{R_o L}{w_c}, C' = \frac{C}{R_o w_c}$$

- Frequency scaling for HPF, BPF and BSF


LPF








HPF

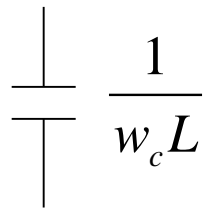

BPF

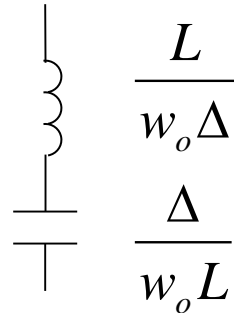

BSF

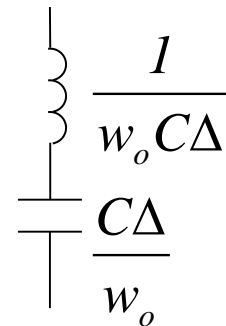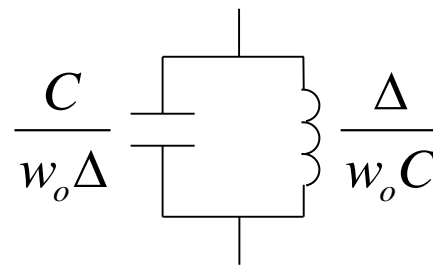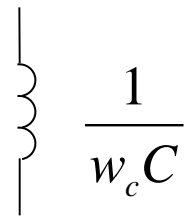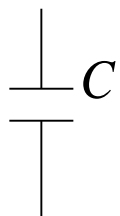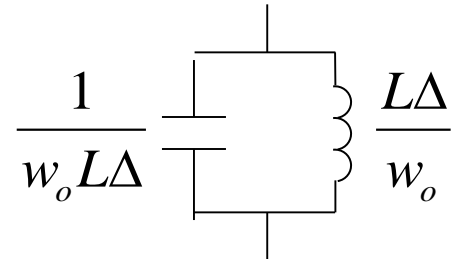

$$\Delta = \frac{w_2 - w_1}{w_o} : \text{fractional BW}$$

Discussion

1. Ex. 8.3 design a maximally flat LPF, $f_c=2\text{GHz}$, $Z_0=50\Omega$, $IL(3\text{GHz})=15\text{dB}$

from Fig.8.26, $IL = 15\text{dB}$ for $\left| \frac{w}{w_c} \right| - 1 = 0.5 @ 3\text{GHz} \rightarrow N = 5$

from Table 8.3, $C_1 = C_5 = 0.618$, $L_2 = L_4 = 1.618$, $C_3 = 2$


$$\rightarrow C_1' = C_5' = \frac{C_1}{50w_c} = 0.984\text{pF}$$

$$L_2' = L_4' = \frac{50L_2}{w_c} = 6.438\text{nH}$$

$$C_3' = \frac{C_3}{50w_c} = 3.183\text{pF}$$

frequency response (p.412, Fig. 8.30) with the comparison of equal-ripple LPF and linear phase LPF


2. LPF \rightarrow HPF frequency scaling

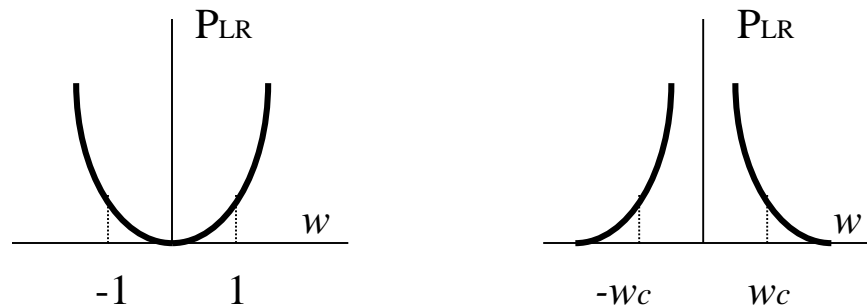

$$0 \rightarrow \pm\infty, 1 \rightarrow -w_c, -1 \rightarrow w_c \Rightarrow w \leftarrow -\frac{w_c}{w}$$

$$LPF \left\{ \begin{array}{l} \frac{1}{jwC} \rightarrow \frac{1}{-j\frac{w_c C}{w}} = jwL' \\ jwL \rightarrow -j\frac{w_c L}{w} = \frac{1}{jwC'} \end{array} \right. \Rightarrow HPF \left\{ \begin{array}{l} L' = \frac{1}{w_c C} \\ C' = \frac{1}{w_c L} \end{array} \right.$$


3. LPF \rightarrow BPF frequency scaling

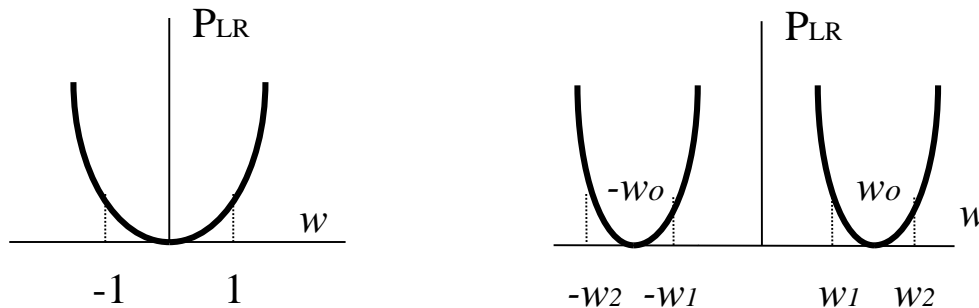

$$0 \rightarrow w_o, 1 \rightarrow w_2, -1 \rightarrow w_1 \Rightarrow w \leftarrow \frac{1}{\Delta} \left(\frac{w}{w_o} - \frac{w_o}{w} \right), \quad w_o = \sqrt{w_1 w_2}, \quad \Delta = \frac{w_2 - w_1}{w_o}$$

$$LPF \left\{ \begin{array}{l} \frac{1}{j\omega C} \rightarrow \frac{1}{j \frac{C}{\Delta} \left(\frac{w}{w_o} - \frac{w_o}{w} \right)} = \frac{1}{j\omega \frac{C}{w_o \Delta} + \frac{C w_o}{j\omega \Delta}} \Rightarrow BPF \left\{ \begin{array}{l} C' = \frac{C}{w_o \Delta}, L' = \frac{\Delta}{w_o C} \\ L' = \frac{L}{w_o \Delta}, C' = \frac{\Delta}{w_o L} \end{array} \right. \\ j\omega L \rightarrow j \frac{L}{\Delta} \left(\frac{w}{w_o} - \frac{w_o}{w} \right) = j\omega \frac{L}{w_o \Delta} + \frac{L w_o}{j\omega \Delta} \end{array} \right.$$

4. LPF → BSF frequency scaling

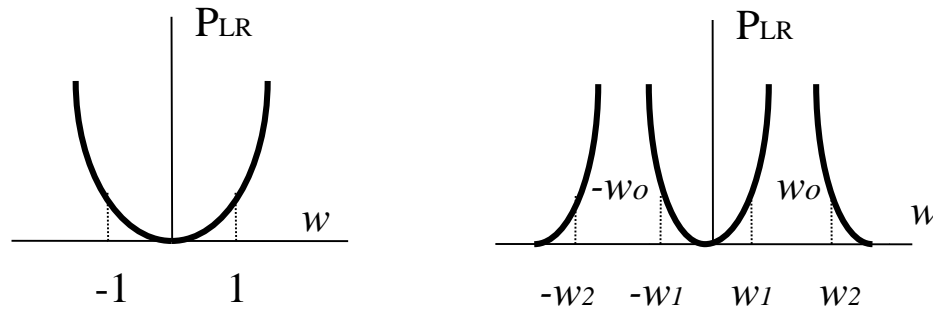

$$0 \rightarrow \pm\infty, 1 \rightarrow -w_1, -1 \rightarrow w_2 \Rightarrow w \leftarrow \frac{\Delta}{\frac{w_o}{w} - \frac{w}{w_o}}$$

$$\begin{aligned}
 \left. \begin{aligned}
 LPF \left\{ \begin{aligned}
 \frac{1}{jwC} &\rightarrow \frac{1}{jC\left(\frac{\Delta}{\frac{w_o}{w} - \frac{w}{w_o}}\right)} = \frac{w_o}{jwC\Delta} + \frac{jw}{C\Delta w_o} \\
 jwL &\rightarrow jL\left(\frac{\Delta}{\frac{w_o}{w} - \frac{w}{w_o}}\right) = \frac{1}{\frac{w_o}{jwL\Delta} + \frac{jw}{Lw_o\Delta}}
 \end{aligned} \right. &\Rightarrow BSF \left\{ \begin{aligned}
 C' &= \frac{C\Delta}{w_o}, L' = \frac{1}{w_o C\Delta} \\
 L' &= \frac{L\Delta}{w_o}, C' = \frac{1}{w_o L\Delta}
 \end{aligned} \right.
 \end{aligned}
 \right.
 \end{aligned}$$

5. Ex. 8.4 design a $N=3$, 0.5dB equal-ripple BPF, $f_0=1\text{GHz}$, $Z_0=50\Omega$, $\text{BW}=10\%$

from Table 8.4, $L_1 = L_3 = 1.5963$, $C_2 = 1.0967$, $R_L = 1$

$$\rightarrow L_1' = L_3' = \frac{L_1 50}{\omega_0 \Delta} = 127 \text{ nH}$$

$$C_1' = C_3' = \frac{\Delta}{\omega_0 L_1 50} = 0.199 \text{ pF}$$

$$L_2' = \frac{50 \Delta}{\omega_0 C_2} = 0.726 \text{ nH}$$

$$C_2' = \frac{C_2}{50 \omega_0 \Delta} = 34.91 \text{ pF}$$


frequency response (p.415, Fig. 8.33)

8.5 Filter implementation

- Richards' transformation

$$\omega \rightarrow \Omega, \Omega \equiv \tan \beta l = \tan (\omega l / v_p)$$

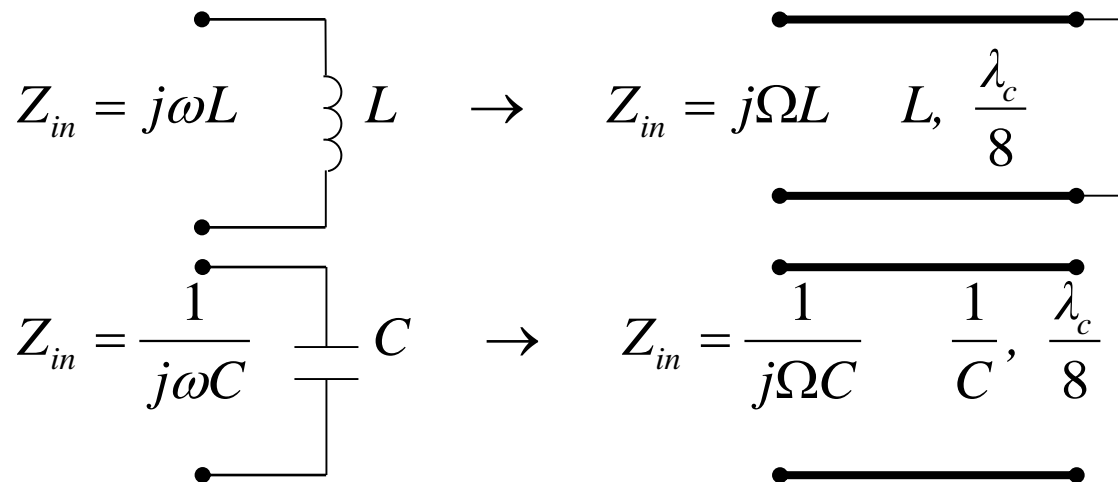lumped elements \rightarrow commensurate lines with S.C. or O.C. stub




Discussion

$$1. \omega_c = 1 \rightarrow \Omega_c = \tan \beta_c l = \tan \frac{2\pi}{\lambda_c} \frac{\lambda_c}{8} = \tan \frac{\pi}{4} = 1$$


$$2. \beta \frac{\lambda_c}{8} = \pi \rightarrow \frac{\omega}{c} \frac{\lambda_c}{8} = \pi \rightarrow \omega = 8\pi f_c = 4\omega_c \Rightarrow \text{stub response repeats every } 4\omega_c.$$

• Kuroda's identities

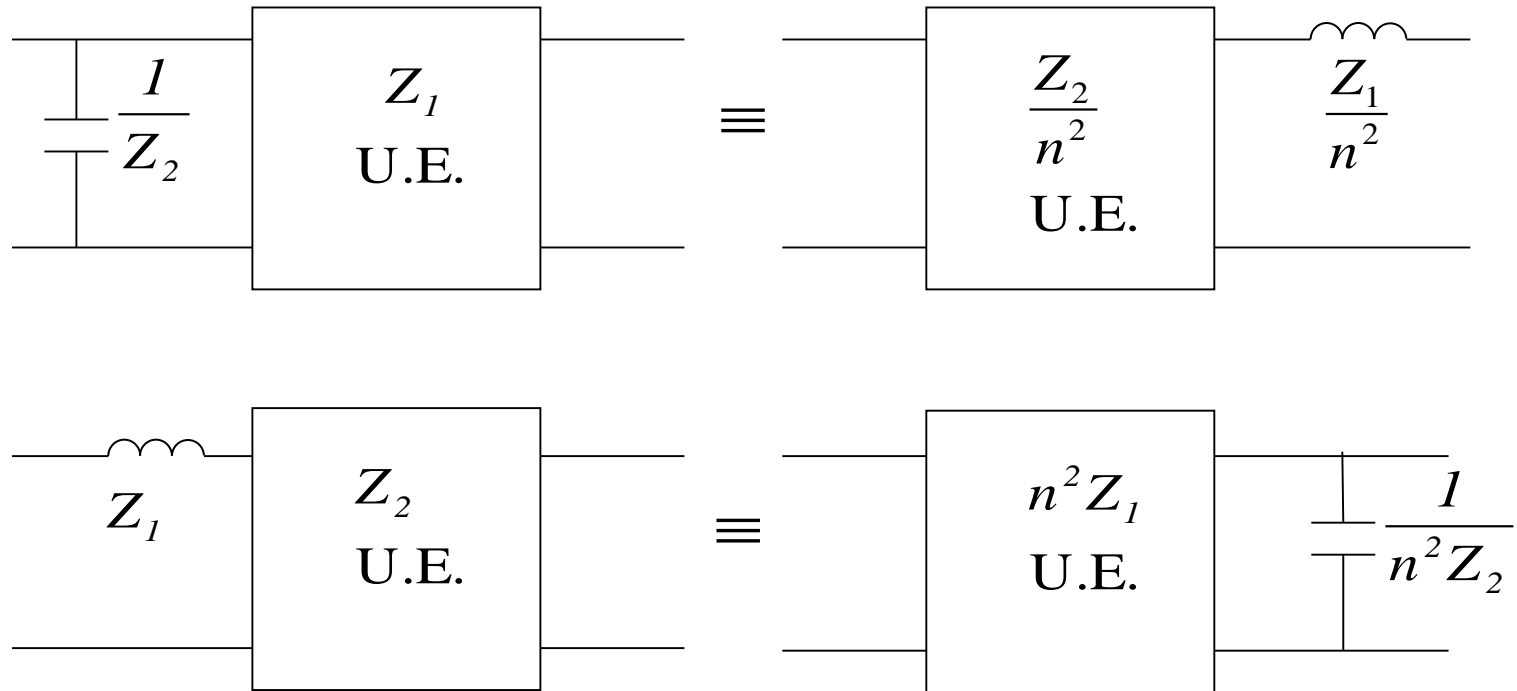

U.E. (unit element) : $\lambda_c/8$ line

$$n^2 = 1 + \frac{Z_2}{Z_1}$$

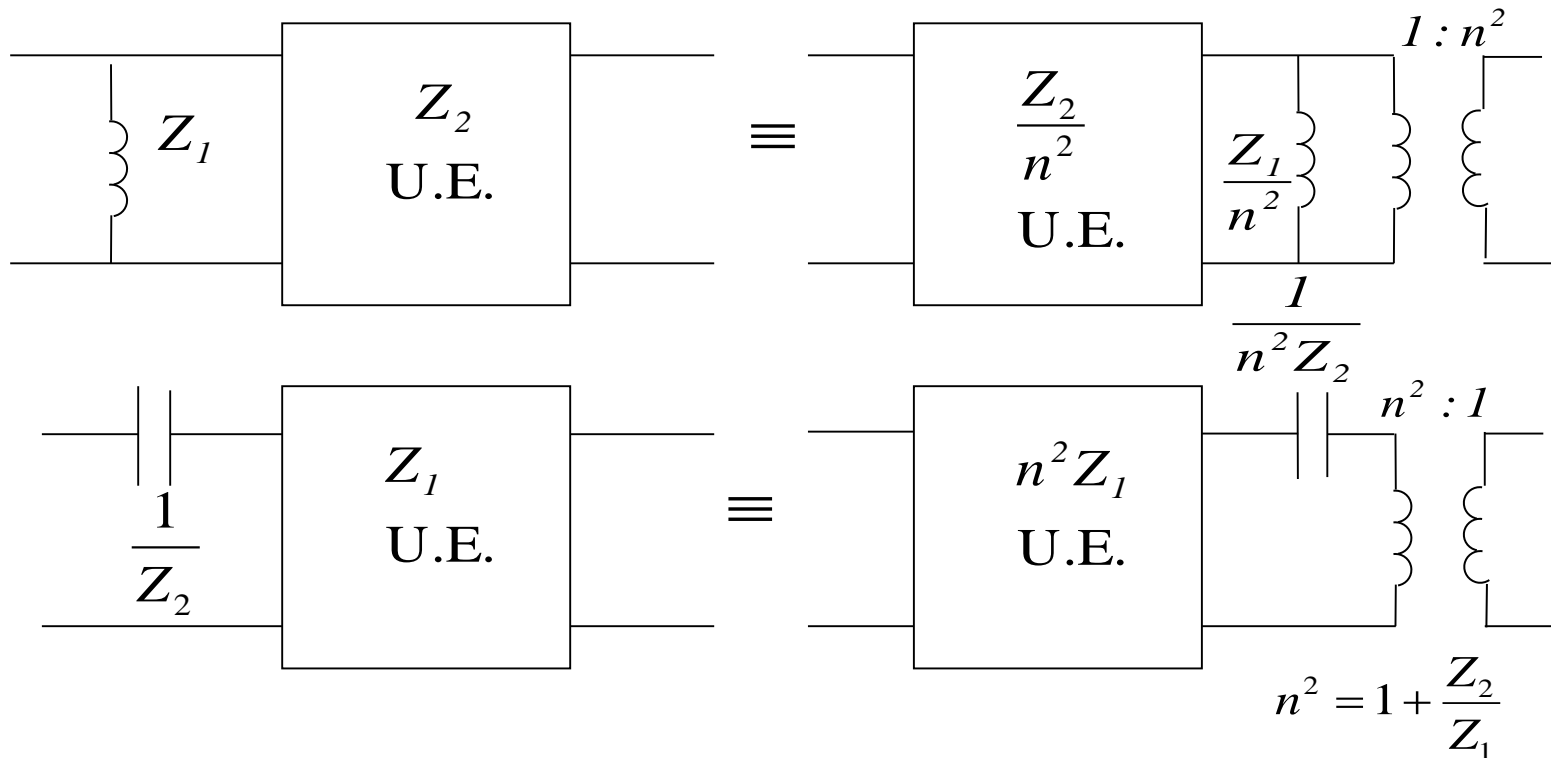

Discussion

1. Use $\lambda_c/8$ redundant lines to separate stubs.
2. series L (short stub) \leftrightarrow shunt C (open stub)
series C and shunt L change positions

3. derivation of (a)



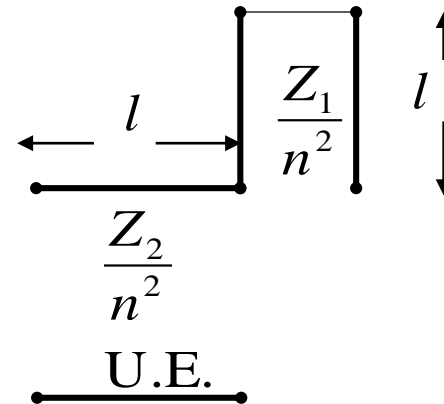
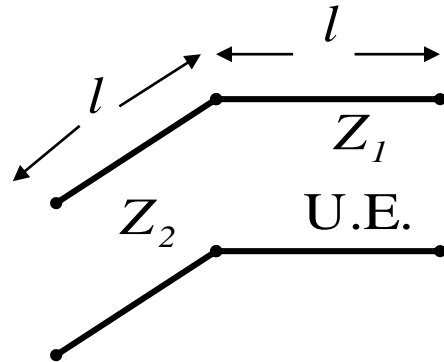


Diagram showing a transmission line of length l and characteristic impedance Z_o .
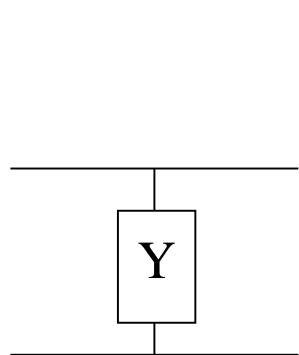
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_o \sin \beta l \\ jY_o \sin \beta l & \cos \beta l \end{bmatrix} = \frac{1}{\sqrt{1+\Omega^2}} \begin{bmatrix} 1 & j\Omega Z_o \\ \frac{j\Omega}{Z_o} & 1 \end{bmatrix}$$


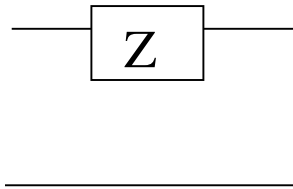
$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{cases} \begin{bmatrix} 1 & 0 \\ \frac{j\Omega}{Z_o} & 1 \end{bmatrix} & \text{open-circuited shunt stub} \\ \begin{bmatrix} 1 & 0 \\ \frac{1}{j\Omega Z_o} & 1 \end{bmatrix} & \text{short-circuited shunt stub} \end{cases}$$



$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} = \begin{cases} \begin{bmatrix} 1 & \frac{Z_o}{j\Omega} \\ 0 & 1 \end{bmatrix} & \text{open-circuited series stub} \\ \begin{bmatrix} 1 & j\Omega Z_o \\ 0 & 1 \end{bmatrix} & \text{short-circuited series stub} \end{cases}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_L = \frac{1}{\sqrt{1+\Omega^2}} \begin{bmatrix} 1 & 0 \\ \frac{j\Omega}{Z_2} & 1 \end{bmatrix} \begin{bmatrix} 1 & j\Omega Z_1 \\ \frac{j\Omega}{Z_1} & 1 \end{bmatrix}$$

$$= \frac{1}{\sqrt{1+\Omega^2}} \begin{bmatrix} 1 & j\Omega Z_1 \\ j\Omega \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) & 1 - \Omega^2 \frac{Z_1}{Z_2} \end{bmatrix}$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_R = \frac{1}{\sqrt{1+\Omega^2}} \begin{bmatrix} 1 & \frac{j\Omega Z_2}{n^2} \\ \frac{j\Omega n^2}{Z_2} & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{j\Omega Z_1}{n^2} \\ 0 & 1 \end{bmatrix}$$

$$= \frac{1}{\sqrt{1+\Omega^2}} \begin{bmatrix} 1 & \frac{j\Omega}{n^2} (Z_1 + Z_2) \\ \frac{j\Omega n^2}{Z_2} & 1 - \Omega^2 \frac{Z_1}{Z_2} \end{bmatrix} \rightarrow n^2 = 1 + \frac{Z_2}{Z_1}$$


4. Microstrip LPF design procedure




series L, shunt C $\rightarrow \lambda_c/8$ series short stub, $\lambda_c/8$ shunt open stub
 \rightarrow add redundant $\lambda_c/8 Z_0$ lines $\rightarrow \lambda_c/8$ shunt open stubs
 \rightarrow consider discontinuity effects

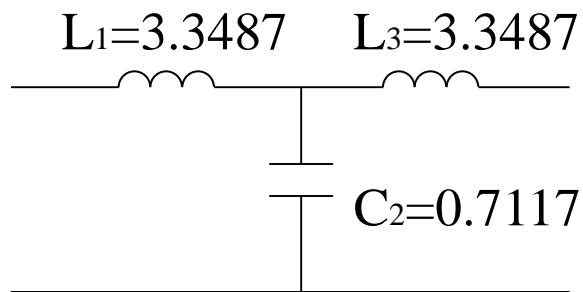5. Ex.8.5 design a 3dB equal-ripple LPF with $f_c=4\text{GHz}$, $N=3$,
 $Z_{in}, Z_{out}=50\Omega$







$Z_0=3.3487$ $Z_0=3.3487$

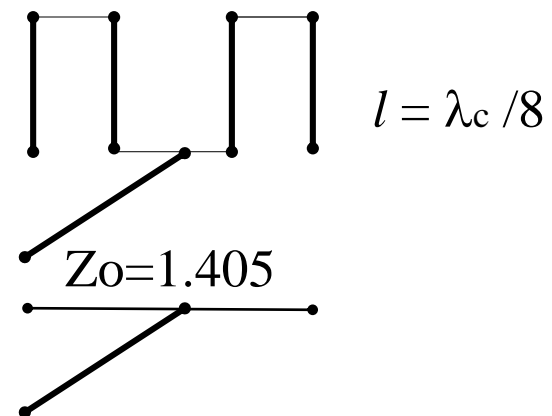

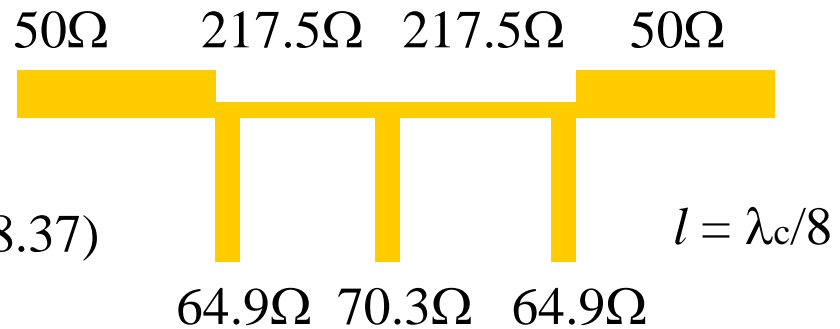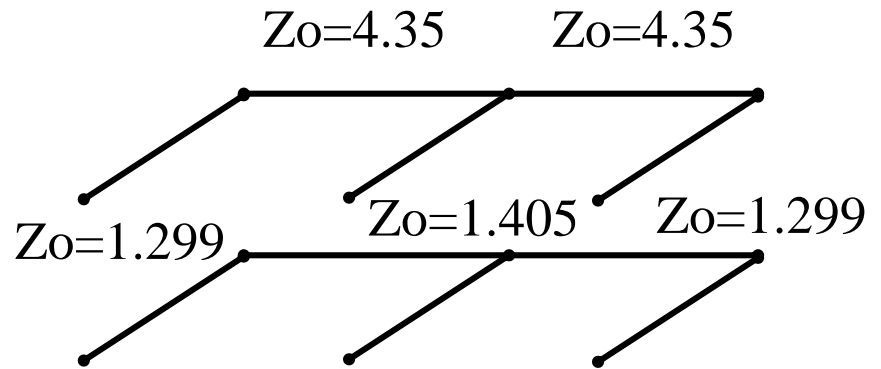
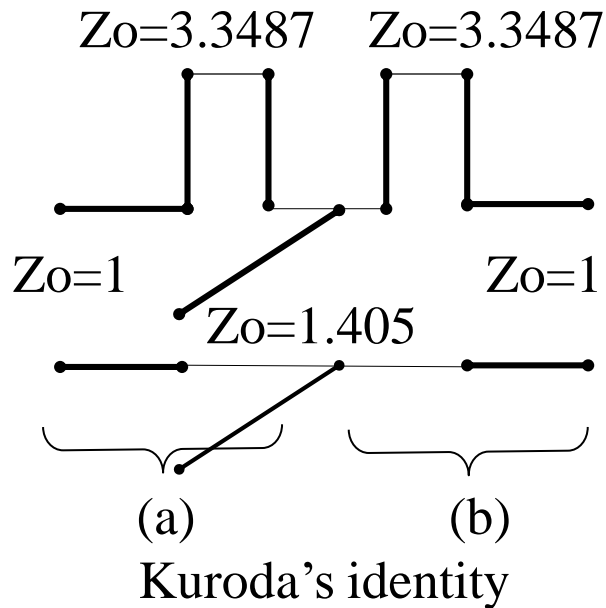


frequency response (p.421, Fig.8.37)
frequency repeats every 16GHz
 S_{21} @8GHz, 24GHz ($l=\lambda'/4, 3\lambda'/4, \dots$)

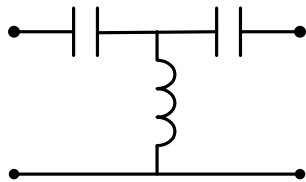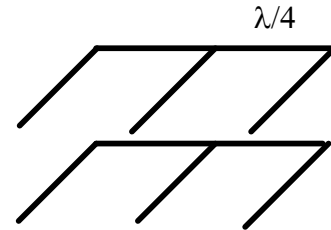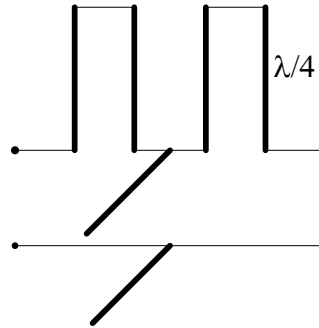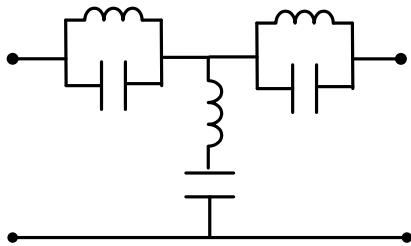6. Similar procedures can be used for bandstop filters, but Kuroda identities are not useful for highpass or bandpass filters. (p.421)




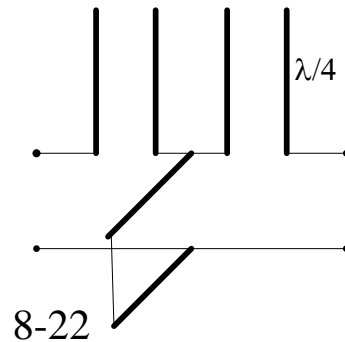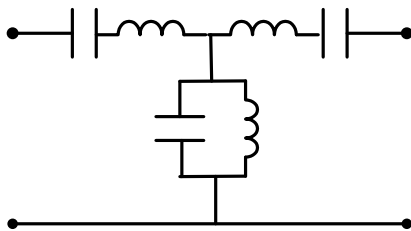Series capacitor transformation is not available in Kuroda identities.




8.6 Stepped-impedance LPF

- Short transmission line section

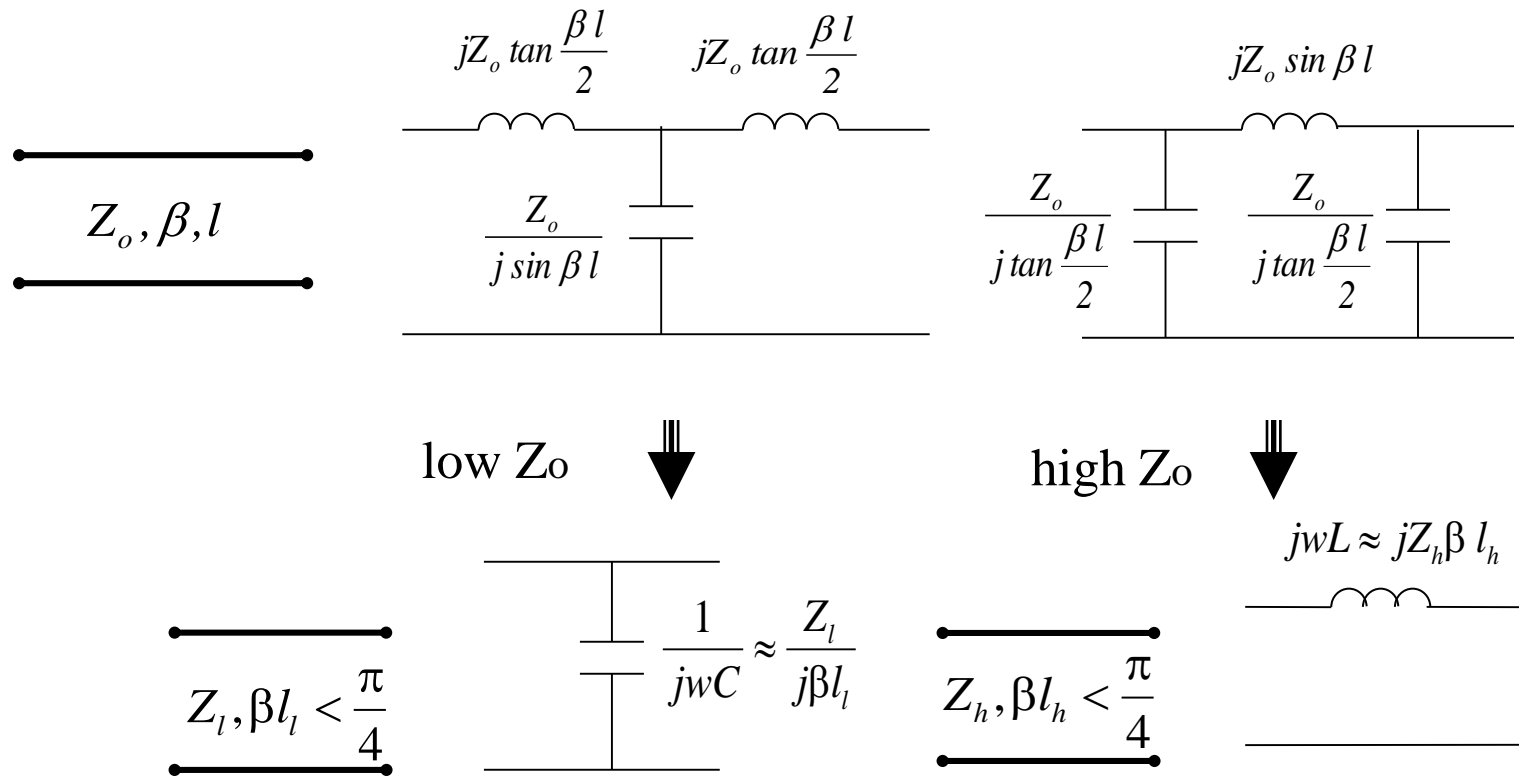


Discussion

1. (derivation from notes 4-12, 13)

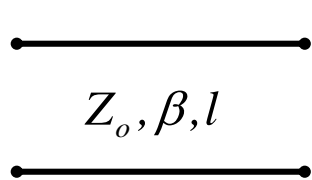

$$\theta = \beta l$$

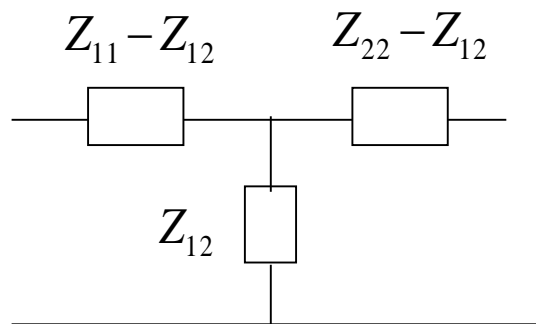
$$[Z] = -jZ_o \begin{bmatrix} \cot \theta & \csc \theta \\ \csc \theta & \cot \theta \end{bmatrix}, [Y] = -jY_o \begin{bmatrix} \cot \theta & -\csc \theta \\ -\csc \theta & \cot \theta \end{bmatrix}$$



$$Z_{12} = -jZ_o \csc \theta$$

$$Z_{11} - Z_{12} = -jZ_o (\cot \theta - \csc \theta) = -jZ_o \left(\frac{\cos \theta}{\sin \theta} - \frac{1}{\sin \theta} \right)$$
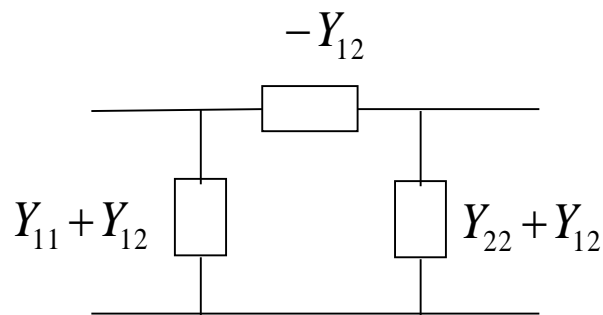
$$= -jZ_o \frac{-2 \sin^2 \frac{\theta}{2}}{2 \sin \frac{\theta}{2} \cos \frac{\theta}{2}} = jZ_o \tan \frac{\theta}{2}$$



$$Y_{12} = jY_o \csc \theta$$

$$Y_{11} + Y_{12} = \frac{1}{jZ_o} \left[\frac{\cos \theta}{\sin \theta} - \frac{1}{\sin \theta} \right] = \frac{j \tan \frac{\theta}{2}}{Z_o}$$

2. Microstrip LPF design procedure

L, C \rightarrow select proper $Z_h, Z_l \rightarrow$ at cutoff frequency $R_oL = Z_h\beta l_h,$
 $R_o/C = Z_l/\beta l_l \rightarrow l_h, l_l \rightarrow$ consider parasitics of L,C and discontinuity effects


3. Considerations of Z_l

$$\frac{Z_l}{j \sin \beta l_l} = \frac{1}{j\omega C} \rightarrow \sin \beta l_l = \omega C Z_l \stackrel{\beta l \leq \frac{\pi}{4}}{\leq} \frac{1}{\sqrt{2}} \rightarrow Z_l \leq \frac{1}{\omega C \sqrt{2}}$$
$$l_l = \frac{1}{\beta} \sin^{-1} \omega C Z_l \rightarrow \text{open stubs?}$$

4. Considerations of Z_h

$$jZ_h \sin \beta l_h = j\omega L \rightarrow \sin \beta l_h = \frac{\omega L}{Z_h} \stackrel{\beta l \leq \frac{\pi}{4}}{\leq} \frac{1}{\sqrt{2}} \rightarrow Z_h \geq \sqrt{2}\omega L \rightarrow \text{fabrication?}$$
$$l_h = \frac{1}{\beta} \sin^{-1} \frac{\omega L}{Z_h} \rightarrow \text{capacitor coupling?}$$

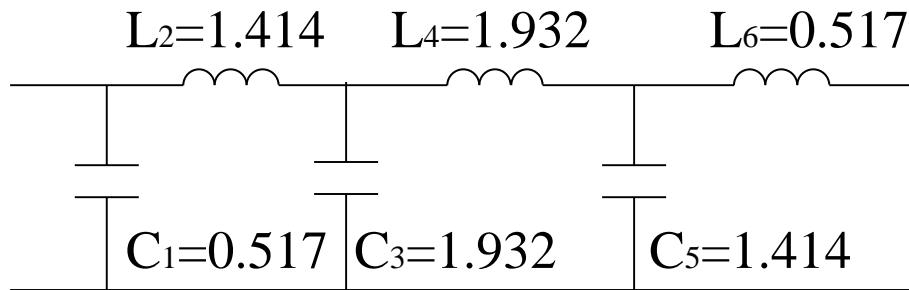5. Ex.8.6 design a maximally flat LPF with $f_c=2.5\text{GHz}$, $IL(4\text{GHz})=20\text{ dB}$, $Z_{in}, Z_{out}=50\Omega$, $Z_h=120\Omega$, $Z_l=20\Omega \rightarrow N=6$



$$l_h = R_o L / \beta Z_h,$$


$$l_l = C Z_l / \beta R_o$$



frequency response (p.425, Fig.8.41)
no repetition of frequency response

8.7 Coupled line filters

• Coupled line BPF element


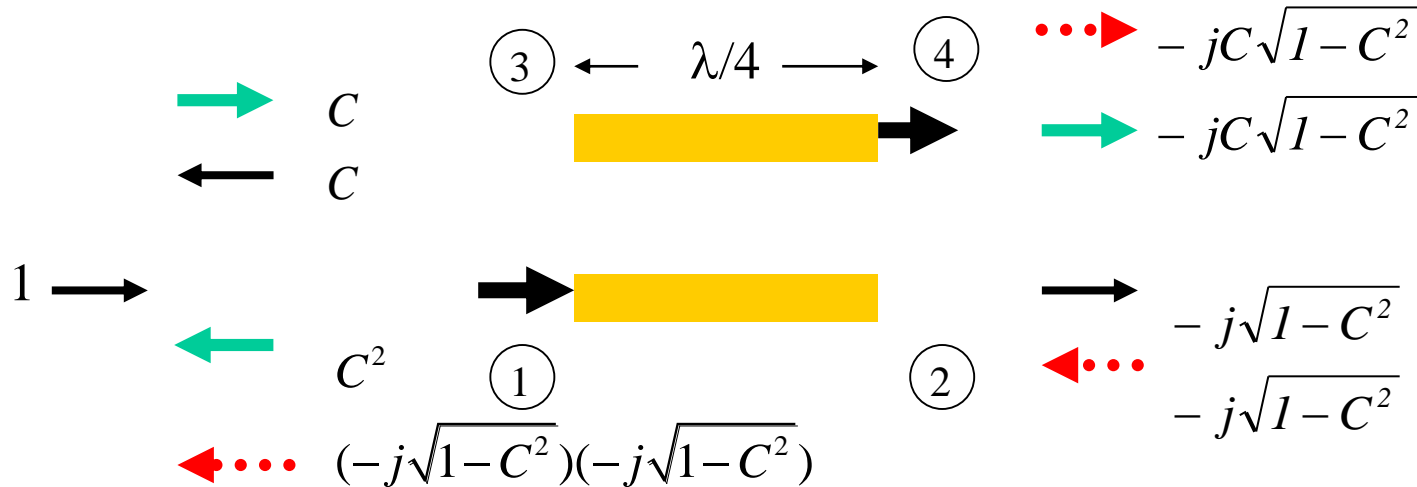


$$\textcircled{1} [C^2 - (1 - C^2)]^2 = 4C^4 - 4C^2 + 1$$

$$\textcircled{4} [-j2C\sqrt{1 - C^2}]^2 = 4C^2(1 - C^2) = -4C^4 + 4C^2$$

$$\textcircled{1} + \textcircled{4} = 1$$
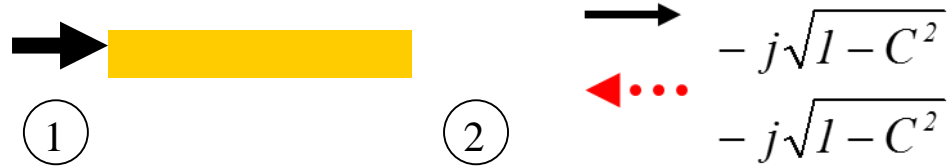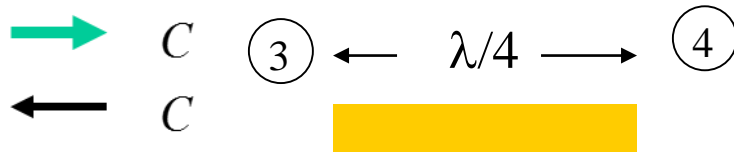
$$\text{if } C = \frac{1}{\sqrt{2}}, \rightarrow \textcircled{1} = 0, \textcircled{4} = 1$$



$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} 0 & -j\sqrt{1-C^2} & C & 0 \\ -j\sqrt{1-C^2} & 0 & 0 & C \\ C & 0 & 0 & -j\sqrt{1-C^2} \\ 0 & C & -j\sqrt{1-C^2} & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ -j\sqrt{1-C^2}a_1 \\ Ca_1 \\ 0 \end{bmatrix}$$



$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} 0 & -j\sqrt{1-C^2} & C & 0 \\ -j\sqrt{1-C^2} & 0 & 0 & C \\ C & 0 & 0 & -j\sqrt{1-C^2} \\ 0 & C & -j\sqrt{1-C^2} & 0 \end{bmatrix} \begin{bmatrix} 0 \\ -j\sqrt{1-C^2}a_1 \\ Ca_1 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} [-(1-C^2)+C^2]a_1 \\ 0 \\ 0 \\ [-j\sqrt{1-C^2}C - j\sqrt{1-C^2}C]a_1 \end{bmatrix} \stackrel{C=\frac{1}{\sqrt{2}}}{=} \begin{bmatrix} 0 \\ 0 \\ 0 \\ -ja_1 \end{bmatrix}$$

• Impedance and admittance inverters (p.422, Fig. 8.38)






impedance inverter

admittance inverter

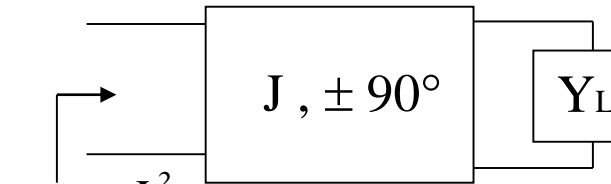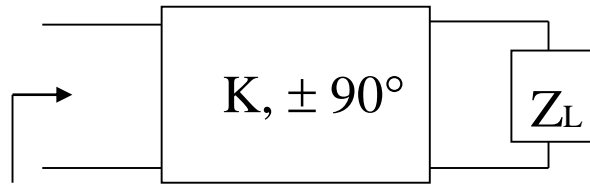


$$Z_{in} = \frac{K^2}{Z_L}$$

$$Y_{in} = \frac{J^2}{Y_L}$$

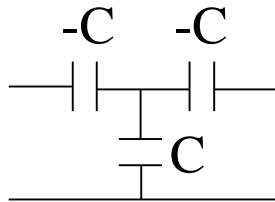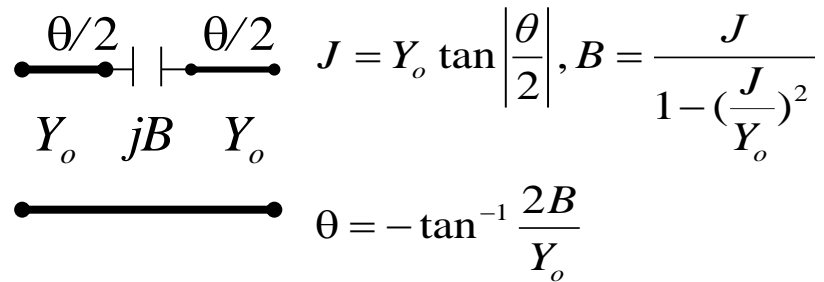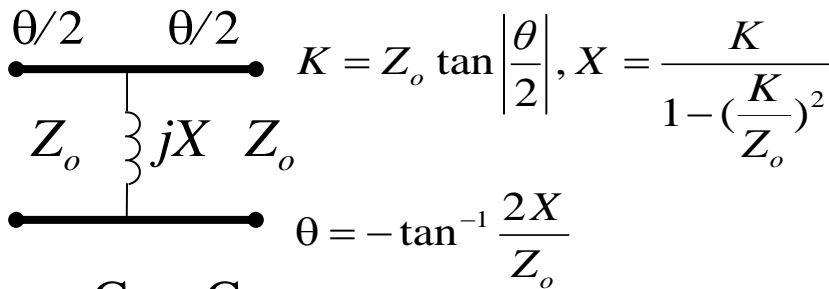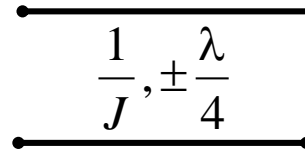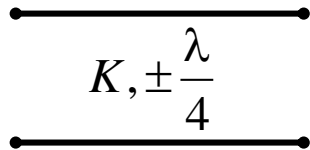


$$K = \frac{1}{\omega C}$$

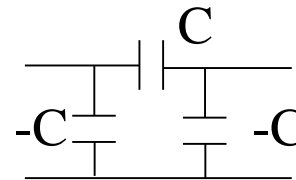

$$J = \omega C$$

(derivation of impedance inverter)

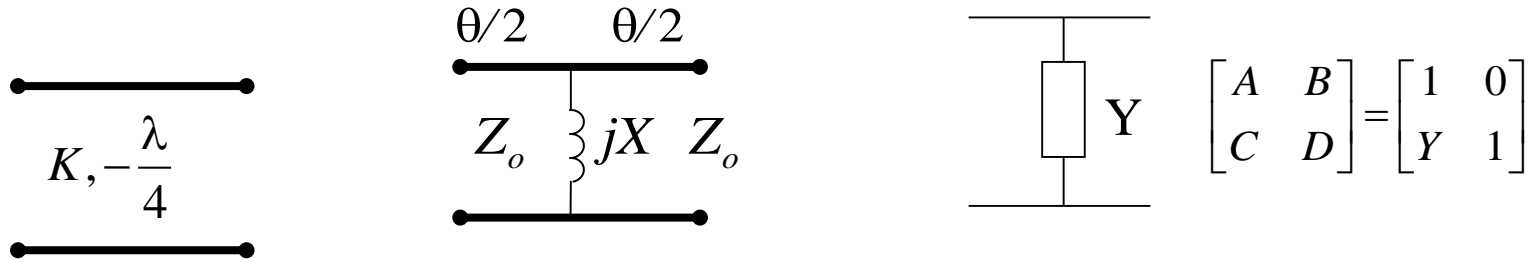

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_o \sin \beta l \\ jY_o \sin \beta l & \cos \beta l \end{bmatrix}, Z_o = K, \beta l = -\frac{\pi}{2} \rightarrow \begin{bmatrix} 0 & -jK \\ -\frac{j}{K} & 0 \end{bmatrix}, l = -\frac{\lambda}{4}$$

$$\begin{bmatrix} \cos \frac{\theta}{2} & jZ_o \sin \frac{\theta}{2} \\ \frac{j}{Z_o} \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{jX} & 1 \end{bmatrix} \begin{bmatrix} \cos \frac{\theta}{2} & jZ_o \sin \frac{\theta}{2} \\ \frac{j}{Z_o} \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} = \begin{bmatrix} \cos \theta + \frac{Z_o}{2X} \sin \theta & jZ_o \left(\sin \theta + \frac{Z_o}{X} \sin^2 \frac{\theta}{2} \right) \\ j \left(\frac{1}{Z_o} \sin \theta - \frac{1}{X} \cos^2 \frac{\theta}{2} \right) & \cos \theta + \frac{Z_o}{2X} \sin \theta \end{bmatrix}$$




$$\cos \theta + \frac{Z_o}{2X} \sin \theta = 0 \quad \theta = -\tan^{-1} \frac{2X}{Z_o} \quad (1) - (2) \rightarrow X = \frac{K}{1 - \left(\frac{K}{Z_o}\right)^2}$$

$$\rightarrow j \left(\frac{1}{Z_o} \sin \theta - \frac{1}{X} \cos^2 \frac{\theta}{2} \right) = -\frac{j}{K} \rightarrow \sin \theta - \frac{Z_o}{X} \cos^2 \frac{\theta}{2} = -\frac{Z_o}{K} \dots (1) \rightarrow$$


$$jZ_o \left(\sin \theta + \frac{Z_o}{X} \sin^2 \frac{\theta}{2} \right) = -jK \quad \sin \theta + \frac{Z_o}{X} \sin^2 \frac{\theta}{2} = -\frac{K}{Z_o} \dots (2)$$

$$\tan |\theta| = \frac{2X}{Z_o} = \frac{2K/Z_o}{1 - \left(\frac{K}{Z_o}\right)^2} = \frac{2 \tan \left| \frac{\theta}{2} \right|}{1 - \tan^2 \left| \frac{\theta}{2} \right|}, K = Z_o \tan \left| \frac{\theta}{2} \right|$$

(derivation of impedance inverter)

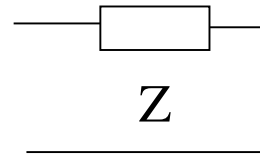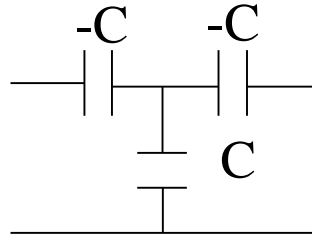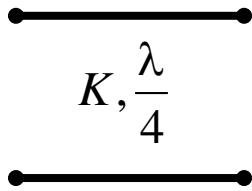
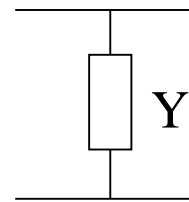
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$






$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_o \sin \beta l \\ jY_o \sin \beta l & \cos \beta l \end{bmatrix}, \quad Z_o = K, \quad \beta l = \frac{\pi}{2}, \quad l = \frac{\lambda}{4} \rightarrow \begin{bmatrix} 0 & jK \\ \frac{j}{K} & 0 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & -\frac{1}{j\omega C} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j\omega C & 1 \end{bmatrix} \begin{bmatrix} 1 & -\frac{1}{j\omega C} \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & j\frac{1}{\omega C} \\ j\omega C & 0 \end{bmatrix} \rightarrow K = \frac{1}{\omega C}$$

(derivation of admittance inverter)

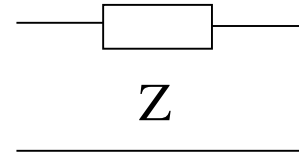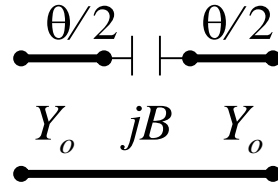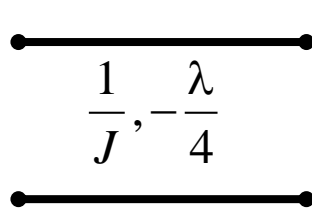

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_o \sin \beta l \\ jY_o \sin \beta l & \cos \beta l \end{bmatrix}, Y_o = J, \beta l = -\frac{\pi}{2} \rightarrow \begin{bmatrix} 0 & -\frac{j}{J} \\ -jJ & 0 \end{bmatrix}, l = -\frac{\lambda}{4}$$

$$\begin{bmatrix} \cos \frac{\theta}{2} & \frac{j}{Y_o} \sin \frac{\theta}{2} \\ jY_o \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{jB} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \cos \frac{\theta}{2} & \frac{j}{Y_o} \sin \frac{\theta}{2} \\ jY_o \sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix} = \begin{bmatrix} \cos \theta + \frac{Y_o}{2B} \sin \theta & j(\frac{1}{Y_o} \sin \theta - \frac{1}{B} \cos^2 \frac{\theta}{2}) \\ jY_o(\sin \theta + \frac{Y_o}{B} \sin^2 \frac{\theta}{2}) & \cos \theta + \frac{Y_o}{2B} \sin \theta \end{bmatrix}$$

$$\cos \theta + \frac{Y_o}{2B} \sin \theta = 0$$

$$\theta = -\tan^{-1} \frac{2B}{Y_o}$$




$$(1) - (2) \rightarrow B = \frac{J}{1 - (\frac{J}{Y_o})^2}$$

$$\rightarrow j(\frac{1}{Y_o} \sin \theta - \frac{1}{B} \cos^2 \frac{\theta}{2}) = -\frac{j}{J} \rightarrow \sin \theta - \frac{Y_o}{B} \cos^2 \frac{\theta}{2} = -\frac{Y_o}{J} \dots (1) \rightarrow$$


$$jY_o(\sin \theta + \frac{Y_o}{B} \sin^2 \frac{\theta}{2}) = -jJ \quad \sin \theta + \frac{Y_o}{B} \sin^2 \frac{\theta}{2} = -\frac{J}{Y_o} \dots (2)$$

$$\tan |\theta| = \frac{2B}{Y_o} = \frac{2J/Y_o}{1 - (\frac{J}{Y_o})^2} = \frac{2 \tan \left| \frac{\theta}{2} \right|}{1 - \tan^2 \left| \frac{\theta}{2} \right|}, J = Y_o \tan \left| \frac{\theta}{2} \right|$$

(derivation of admittance inverter)

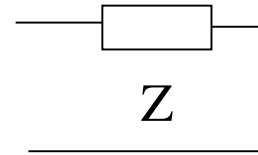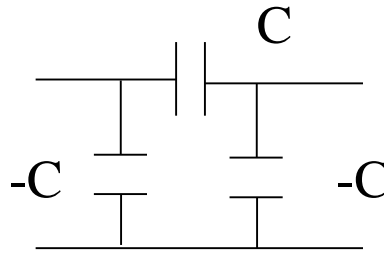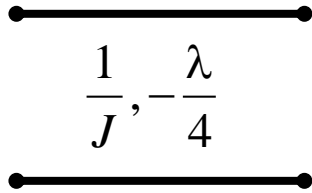
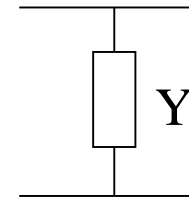
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \beta l & jZ_o \sin \beta l \\ jY_o \sin \beta l & \cos \beta l \end{bmatrix}, Y_o = J \beta l = -\frac{\pi}{2}, l = -\frac{\lambda}{4} \rightarrow \begin{bmatrix} 0 & \frac{1}{jJ} \\ -jJ & 0 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ -j\omega C & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{j\omega C} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j\omega C & 1 \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{j\omega C} \\ -j\omega C & 0 \end{bmatrix} \rightarrow J = \omega C$$

Discussion

1. $\textcircled{3} \leftarrow \theta \rightarrow \textcircled{4}$


$1/2 \ -1/2$ 

$1/2 \ 1/2$ 

$\textcircled{1}$

$\textcircled{2}$

design equation #1

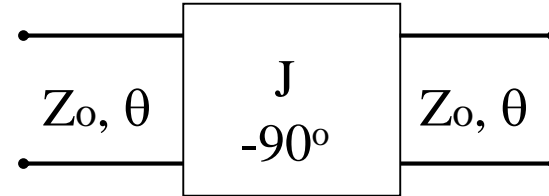

$$\theta = \frac{\pi}{2}, \begin{cases} Z_{oe} = Z_o [1 + JZ_o + (JZ_o)^2] \\ Z_{oo} = Z_o [1 - JZ_o + (JZ_o)^2] \end{cases}$$

For the left circuit: $V_1 = V_{1e}^+ + V_{1e}^- + V_{1o}^+ + V_{1o}^-$, $I_1 = \frac{V_{1e}^+}{Z_{oe}} - \frac{V_{1e}^-}{Z_{oe}} + \frac{V_{1o}^+}{Z_{oo}} - \frac{V_{1o}^-}{Z_{oo}}$

$$V_2 = V_{1e}^+ e^{-j\theta} + V_{1e}^- e^{j\theta} + V_{1o}^+ e^{-j\theta} + V_{1o}^- e^{j\theta}, I_2 = \frac{V_{1e}^+}{Z_{oe}} e^{-j\theta} - \frac{V_{1e}^-}{Z_{oe}} e^{j\theta} + \frac{V_{1o}^+}{Z_{oo}} e^{-j\theta} - \frac{V_{1o}^-}{Z_{oo}} e^{j\theta}$$

$$V_3 = V_{1e}^+ + V_{1e}^- - V_{1o}^+ - V_{1o}^-, I_3 = \frac{V_{1e}^+}{Z_{oe}} - \frac{V_{1e}^-}{Z_{oe}} - \frac{V_{1o}^+}{Z_{oo}} + \frac{V_{1o}^-}{Z_{oo}}$$

$$V_4 = V_{1e}^+ e^{-j\theta} + V_{1e}^- e^{j\theta} - V_{1o}^+ e^{-j\theta} - V_{1o}^- e^{j\theta}, I_4 = \frac{V_{1e}^+}{Z_{oe}} e^{-j\theta} - \frac{V_{1e}^-}{Z_{oe}} e^{j\theta} - \frac{V_{1o}^+}{Z_{oo}} e^{-j\theta} + \frac{V_{1o}^-}{Z_{oo}} e^{j\theta}$$


$$\begin{bmatrix} V_1 \\ V_4 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{14} \\ Z_{14} & Z_{11} \end{bmatrix} \begin{bmatrix} I_1 \\ I_4 \end{bmatrix}, Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_4=0}, Z_{14} = \left. \frac{V_4}{I_1} \right|_{I_4=0}$$

ports 2, 3 open, $I_2 = I_3 = 0$
 $I_4 = 0$

$$\Rightarrow \frac{V_{1e}^+}{Z_{oe}} = \frac{V_{1o}^+}{Z_{oo}} \Rightarrow \begin{aligned} Z_{11} &= -\frac{j}{2}(Z_{oe} + Z_{oo}) \cot \theta \\ Z_{14} &= -\frac{j}{2}(Z_{oe} - Z_{oo}) \csc \theta \end{aligned}$$

$$\frac{V_{1e}^-}{Z_{oe}} = \frac{V_{1o}^+}{Z_{oo}}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Z_{11}}{Z_{41}} & \frac{Z_{11}Z_{44}}{Z_{41}} - Z_{14} \\ 1 & \frac{Z_{44}}{Z_{41}} \end{bmatrix} = \begin{bmatrix} \frac{Z_{oe} + Z_{oo}}{Z_{oe} - Z_{oo}} \cos \theta & 2j \frac{(Z_{oe} - Z_{oo})^2 - (Z_{oe} + Z_{oo})^2 \cos \theta}{(Z_{oe} - Z_{oo}) \sin \theta} \\ 2j \frac{\sin \theta}{Z_{oe} - Z_{oo}} & \frac{Z_{oe} + Z_{oo}}{Z_{oe} - Z_{oo}} \cos \theta \end{bmatrix}$$

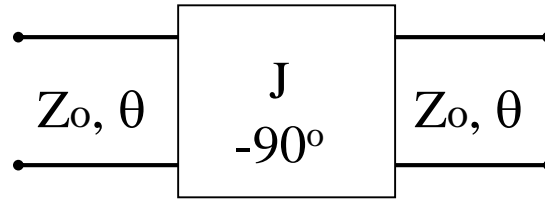

$$\begin{bmatrix} \cos \theta & jZ_o \sin \theta \\ jY_o \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} 0 & -\frac{j}{J} \\ -jJ & 0 \end{bmatrix} \begin{bmatrix} \cos \theta & jZ_o \sin \theta \\ jY_o \sin \theta & \cos \theta \end{bmatrix}$$


$$= \begin{bmatrix} (Z_o J + \frac{Y_o}{J}) \sin \theta \cos \theta & jZ_o^2 J \sin^2 \theta - \frac{j}{J} \cos^2 \theta \\ -jJ \cos^2 \theta + j \frac{Y_o^2}{J} \sin^2 \theta & (Z_o J + \frac{Y_o}{J}) \sin \theta \cos \theta \end{bmatrix}$$

$$"=" \Rightarrow (Z_o J + \frac{Y_o}{J}) \sin \theta \cos \theta = \frac{Z_{oe} + Z_{oo}}{Z_{oe} - Z_{oo}} \cos \theta, -jJ \cos^2 \theta + j \frac{Y_o^2}{J} \sin^2 \theta = \frac{j2 \sin \theta}{Z_{oe} - Z_{oo}}$$

$$\theta = \frac{\pi}{2} \Rightarrow \frac{Z_{oe} + Z_{oo}}{Z_{oe} - Z_{oo}} = Z_o J + \frac{Y_o}{J}, Z_{oe} - Z_{oo} = 2 \frac{J}{Y_o^2} = 2JZ_o^2$$

$$\Rightarrow Z_{oe} = Z_o (1 + JZ_o + J^2 Z_o^2)$$

$$Z_{oo} = Z_o (1 - JZ_o - J^2 Z_o^2)$$

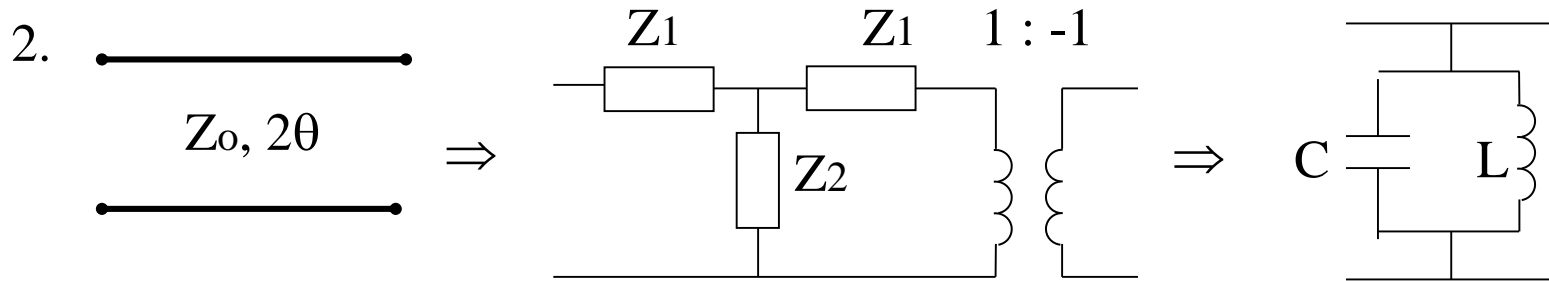


design equation #2 $L = \frac{2Z_o}{\omega_o \pi}, C = \frac{\pi}{2\omega_o Z_o}$

$$\begin{bmatrix} \cos 2\theta & jZ_o \sin 2\theta \\ jY_o \sin 2\theta & \cos 2\theta \end{bmatrix} = \begin{bmatrix} 1 + \frac{Z_1}{Z_2} & 2Z_1 + \frac{Z_1^2}{Z_2} \\ \frac{1}{Z_2} & 1 + \frac{Z_1}{Z_2} \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix} = - \begin{bmatrix} 1 + \frac{Z_1}{Z_2} & 2Z_1 + \frac{Z_1^2}{Z_2} \\ \frac{1}{Z_2} & 1 + \frac{Z_1}{Z_2} \end{bmatrix}$$

$$\Rightarrow \begin{aligned} Z_2 &= \frac{jZ_o}{\sin 2\theta} \\ -(1 + \frac{Z_1}{Z_2}) &= \cos 2\theta \end{aligned} \Rightarrow \begin{aligned} Z_2 &= \frac{jZ_o}{\sin 2\theta} \\ Z_1 &= -jZ_o \cot \theta \end{aligned}$$
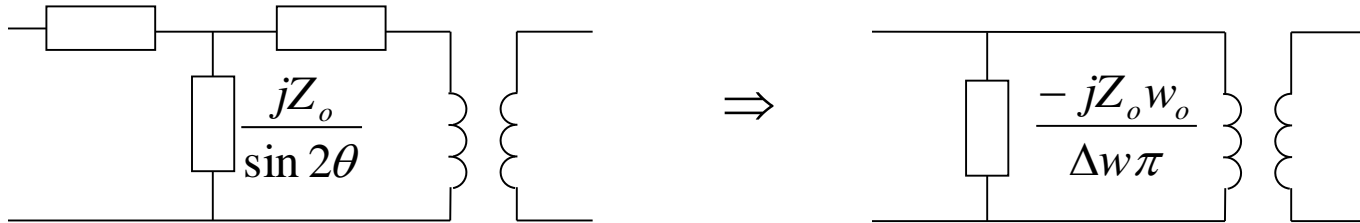
$$-jZ_o \cot \theta \quad -jZ_o \cot \theta \quad 1 : -1 \qquad \qquad \qquad 1 : -1$$




for $\theta \approx \frac{\pi}{2}$, $\cot \theta \approx 0$

$$2\theta = \beta l = \frac{\omega}{c} l = \frac{\omega_o + \Delta\omega}{\omega_o} \pi \rightarrow \sin 2\theta = \sin\left(\pi + \frac{\Delta\omega}{\omega_o} \pi\right) = -\sin \frac{\Delta\omega}{\omega_o} \pi \approx -\frac{\Delta\omega}{\omega_o} \pi$$

$$Z_{in} = \frac{1}{j\omega C + \frac{1}{j\omega L}} = \frac{j\omega L}{1 - \omega^2 LC} = \frac{j(\omega_o + \Delta\omega)L}{1 - (\omega_o + \Delta\omega)^2 LC}$$

$$= \frac{-j(\omega_o + \Delta\omega)L}{(2\omega_o \Delta\omega + \Delta\omega^2) \frac{1}{\omega_o^2}} \approx \frac{-j\omega_o (\omega_o + \Delta\omega)L}{2\Delta\omega} \approx \frac{-j\omega_o^2}{2\Delta\omega} L$$


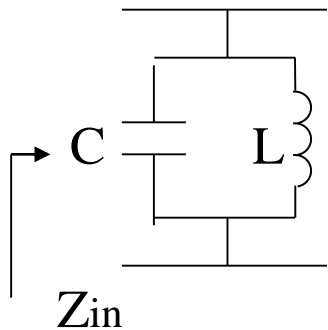
$$"=" \Rightarrow \frac{-j\omega_o^2}{2\Delta\omega} L = \frac{-j\omega_o Z_o}{\Delta\omega \pi} \Rightarrow L = \frac{2Z_o}{\omega_o \pi}, C = \frac{1}{L\omega_o^2} = \frac{\pi}{2\omega_o Z_o}$$




3. derivation of design equation #3 (8.121)


$$J_1 = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_1}}, J_i = \frac{\pi\Delta}{2Z_o \sqrt{g_{i-1}g_i}}, J_{N+1} = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_N g_{N+1}}}$$

“N=2” (p.434-435, Fig. 8.45 (e), (f))

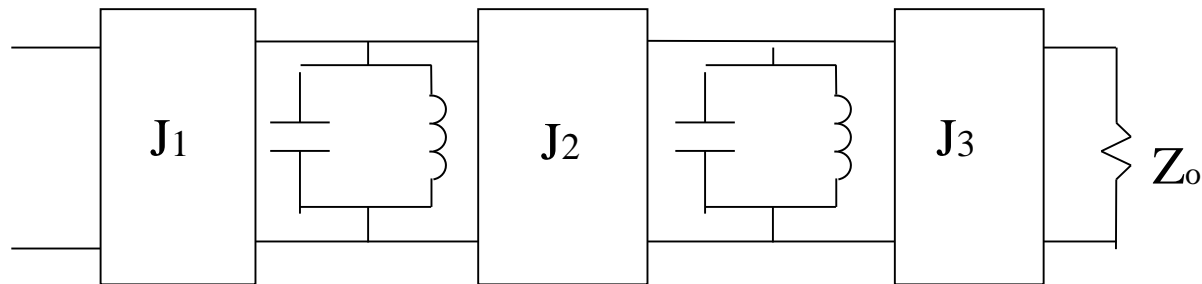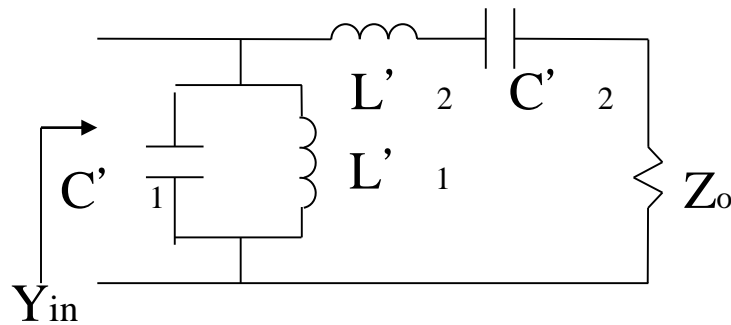


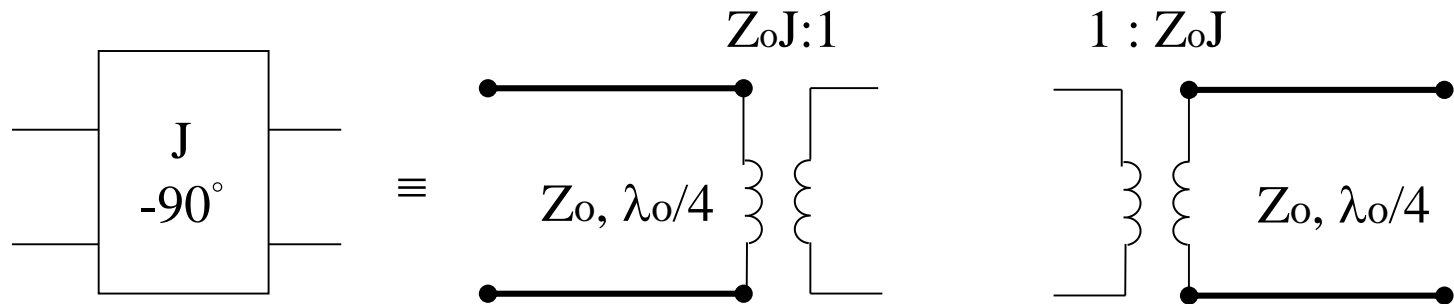

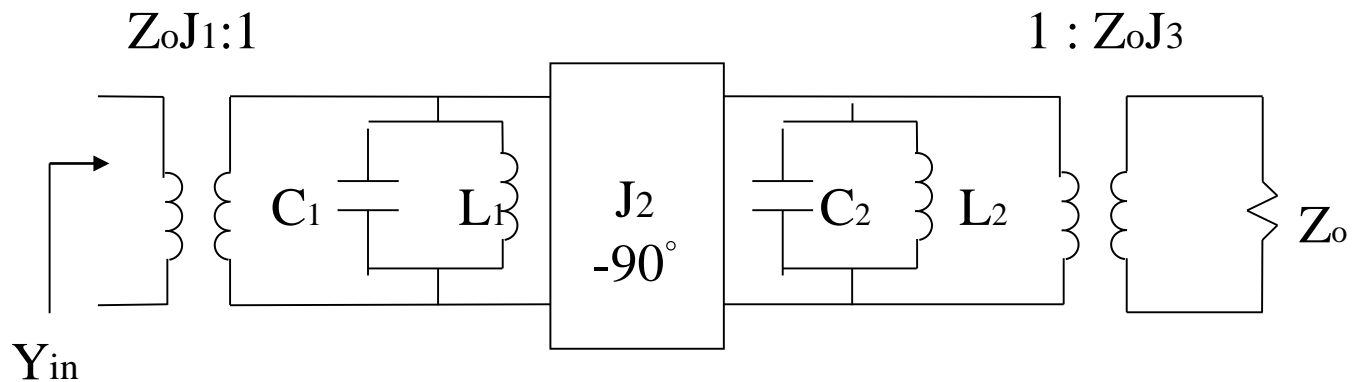
$$\text{left: } \begin{bmatrix} 0 & \frac{-j}{J} \\ -jJ & 0 \end{bmatrix} = \text{right: } \begin{bmatrix} 0 & -jZ_o \\ -jY_o & 0 \end{bmatrix} \begin{bmatrix} JZ_o & 0 \\ 0 & \frac{1}{JZ_o} \end{bmatrix}, \begin{bmatrix} \frac{1}{JZ_o} & 0 \\ 0 & JZ_o \end{bmatrix} \begin{bmatrix} 0 & -jZ_o \\ -jY_o & 0 \end{bmatrix}$$





4. Coupled line BPF design

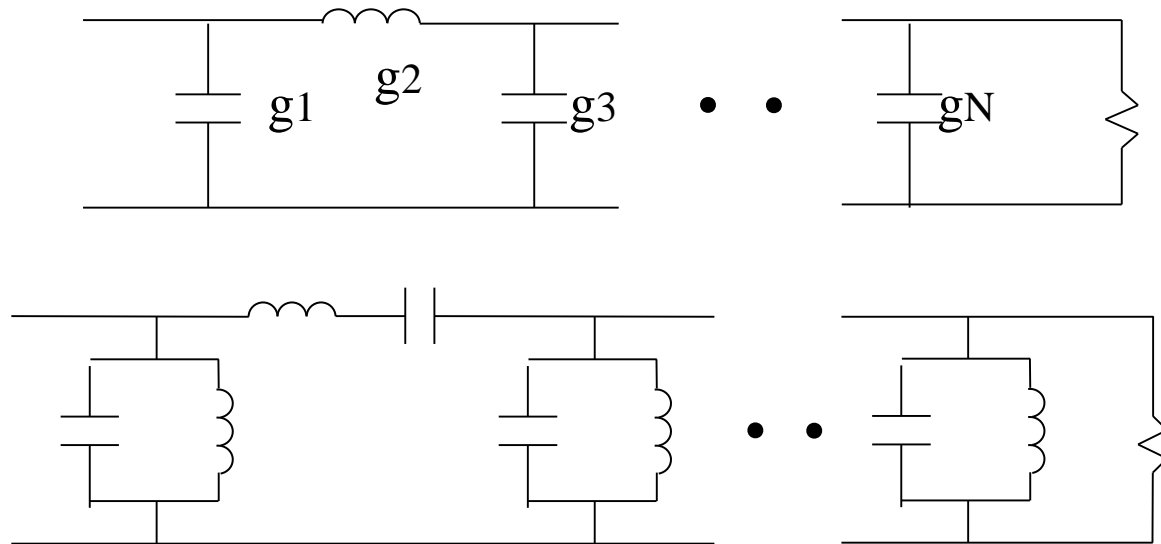
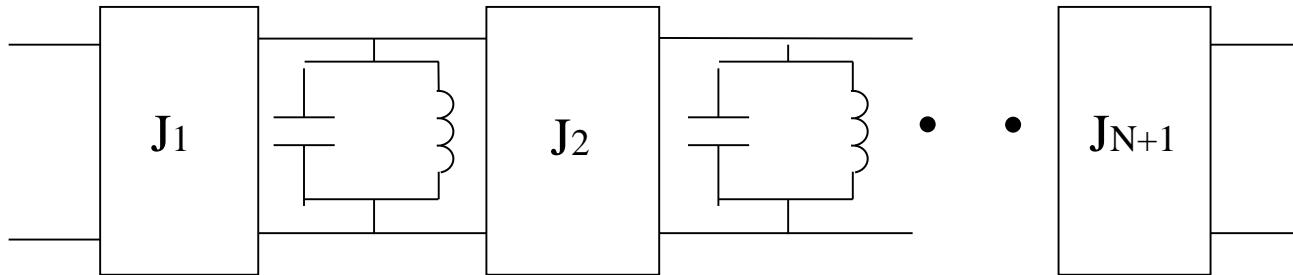
$$L_i = \begin{cases} \frac{\Delta Z_o}{\omega_o g_i} & \text{shunt element} \\ \frac{g_i Z_o}{\omega_o \Delta} & \text{series element} \end{cases}, C_i = \begin{cases} \frac{g_i}{\omega_o \Delta Z_o} & \text{shunt element} \\ \frac{\Delta}{\omega_o g_i Z_o} & \text{series element} \end{cases}, \Delta = \frac{\omega_2 - \omega_1}{\omega_o}$$



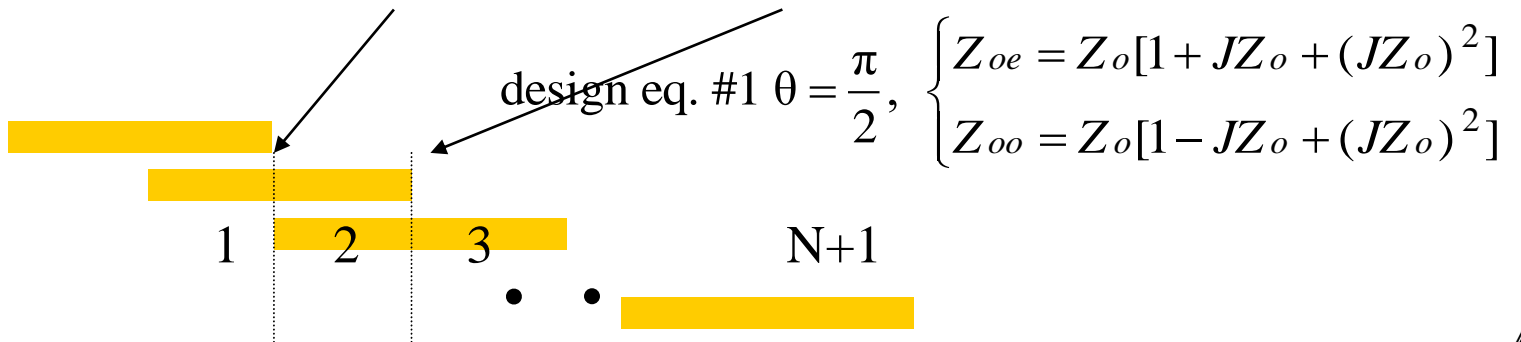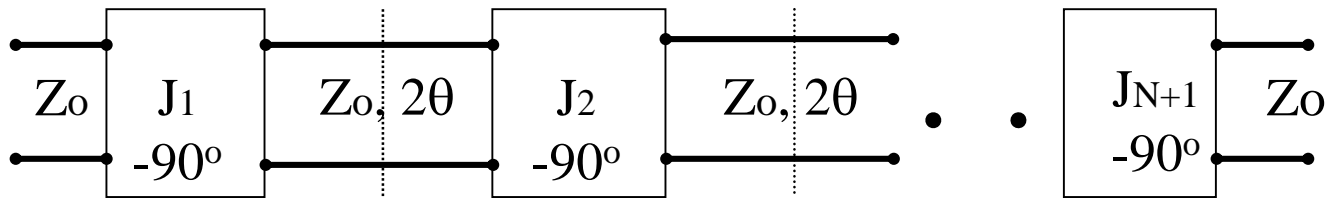design equation #3 $J_1 = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_1}}, J_i = \frac{\pi\Delta}{2Z_o\sqrt{g_{i-1}g_i}}, J_{N+1} = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_N g_{N+1}}}$



4. Microstrip coupled line BPF design procedure

LPF prototype $g_i \rightarrow J_i \rightarrow Z_{oei}, Z_{ooi} \rightarrow$ microstrip line W_i, S_i
 \rightarrow consider discontinuity effects

$$J_1 = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_1}}, J_i = \frac{\pi\Delta}{2Z_o \sqrt{g_{i-1}g_i}}, J_{N+1} = \frac{1}{Z_o} \sqrt{\frac{\pi\Delta}{2g_N g_{N+1}}}$$

$$Z_{oe} = Z_o[1 + JZ_o + (JZ_o)^2], Z_{oo} = Z_o[1 - JZ_o + (JZ_o)^2]$$



5. Ex.8.7 design a 0.5dB ripple equal-ripple coupled line BPF, $N=3$,
 $f_o=2\text{GHz}$, $\text{BW}=10\%$, $Z_o=50\Omega$

i	g_i	$Z_o J_i$	Z_{oe}	Z_{oo}
1	1.5963	0.3137	70.61	39.24
2	1.0967	0.1187	56.64	44.77
3	1.5963	0.1187	56.64	44.77
4	1.0000	0.3137	70.61	39.24

frequency response
 (p.436, Fig.8.46)
 $\text{IL}(1.8\text{GHz}) \cong 20\text{dB}$

8.8 Filters using coupled resonators

- $\lambda/4$ stub

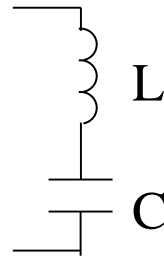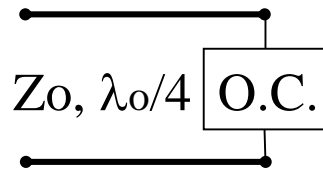

design equation



$$L = \frac{\pi Z_0}{4\omega_0}, C = \frac{4}{\omega_0 \pi Z_0}$$

$$\text{O.C. line: } Z_{in} = \frac{Z_0}{j \tan \theta}, \theta = \beta l = \frac{w \lambda_0}{c 4} = \frac{w c}{c 4 f_0} = \frac{\pi w}{2 w_0} = \frac{\pi w_0 + \Delta w}{2 w_0}$$

$$Z_{in} = \frac{Z_0}{j \tan\left(\frac{\pi}{2} + \frac{\pi \Delta w}{2 w_0}\right)} = j Z_0 \tan \frac{\pi \Delta w}{2 w_0} \approx j Z_0 \frac{\pi(w - w_0)}{2 w_0}$$

$$\text{series LC: } Z_{in} = j\omega L + \frac{1}{j\omega C} = j\sqrt{\frac{L}{C}}(w\sqrt{LC} - \frac{1}{w\sqrt{LC}}) = j\sqrt{\frac{L}{C}}\left(\frac{w}{w_0} - \frac{w_0}{w}\right)$$
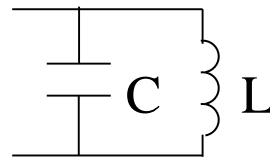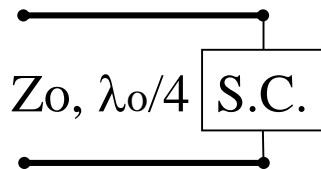
$$= j\sqrt{\frac{L}{C}} \frac{(w + w_0)(w - w_0)}{w_0 w} \approx j\sqrt{\frac{L}{C}} \frac{2(w - w_0)}{w_0} = j2L(w - w_0) \Rightarrow Z_0 = \frac{4w_0 L}{\pi}$$




design equation


$$C = \frac{\pi Z_0}{4\omega_0}, L = \frac{4}{\omega_0 \pi Z_0}$$

微波電路講義

Discussion

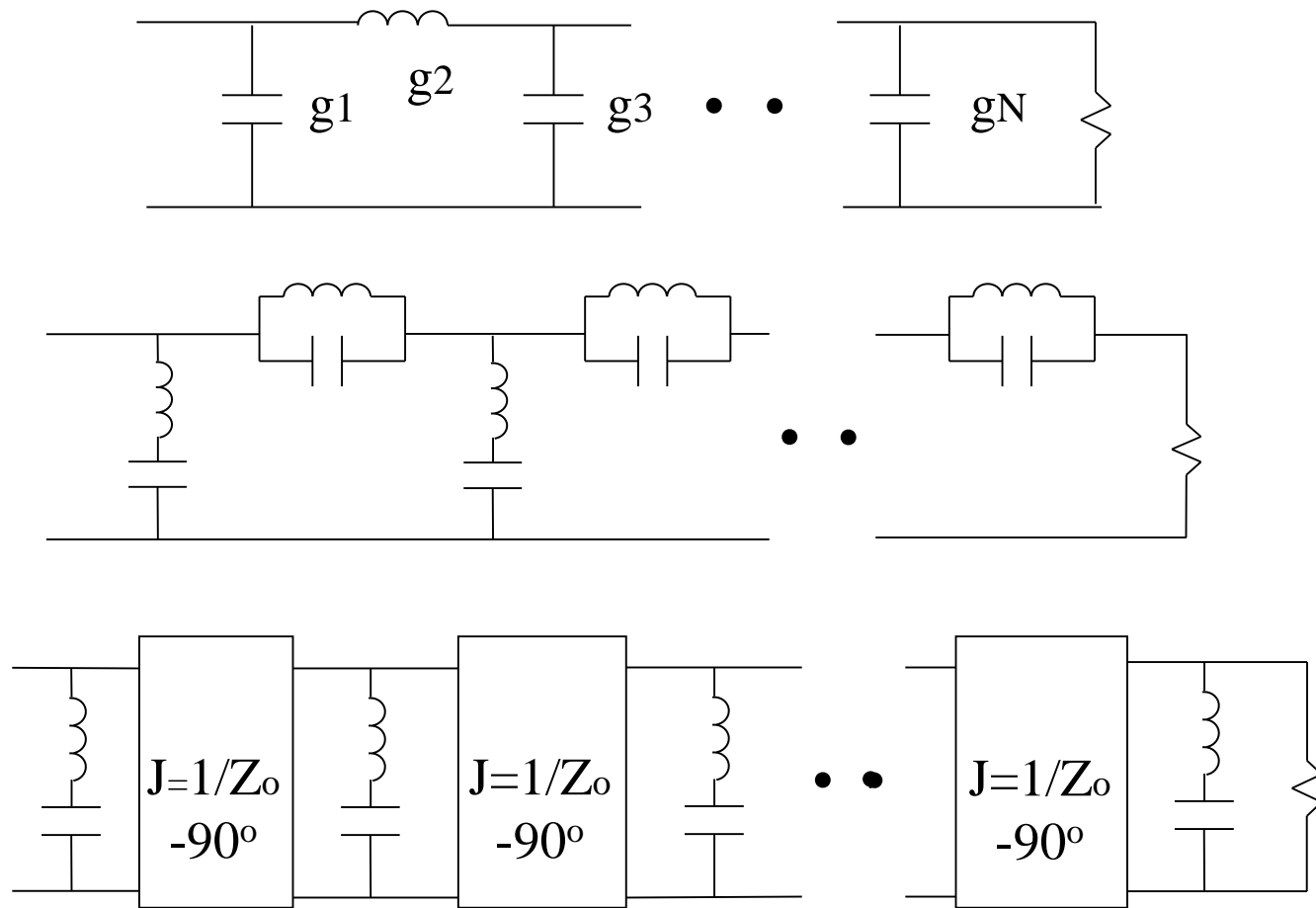1. BSF using $\lambda/4$ open-circuit stub



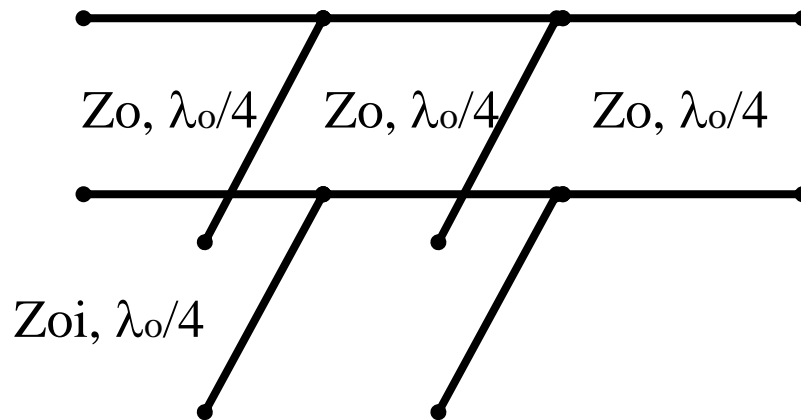

design equation BSF: $\frac{\lambda}{4}$ open-circuit shunt stub $Z_{oi} = \frac{4Z_o}{\pi g_i \Delta}$
 (BPF: $\frac{\lambda}{4}$ short-circuit shunt stub $Z_{oi} = \frac{\pi Z_o \Delta}{4g_i}$)

Derivation for N=2 is given in p.439-440.

2. Ex.8.8 design a 0.5dB ripple equal-ripple $\lambda/4$ stub BSF,
 $N=3$, $f_0=2\text{GHz}$, $\text{BW}=15\%$, $Z_0=50\Omega$


i	g_i	Z_{oi}
1	1.5963	265.9
2	1.0967	387
3	1.5963	265.9




frequency response (p.440, Fig.8.49)

3. Design procedure for microstrip BPF or BSF using $\lambda/4$ stub
 LPF prototype $g_i \rightarrow \lambda/4$ open-circuit or short-circuit stubs Z_{oi}
 \rightarrow microstrip line \rightarrow consider discontinuity effect

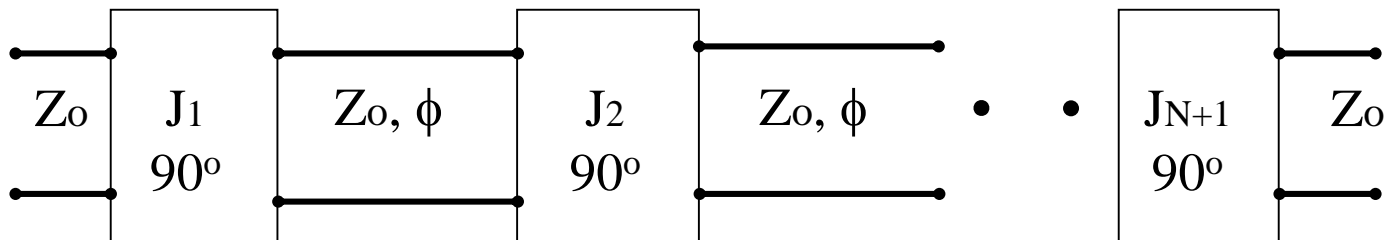4. BPF using capacitively coupled series resonator



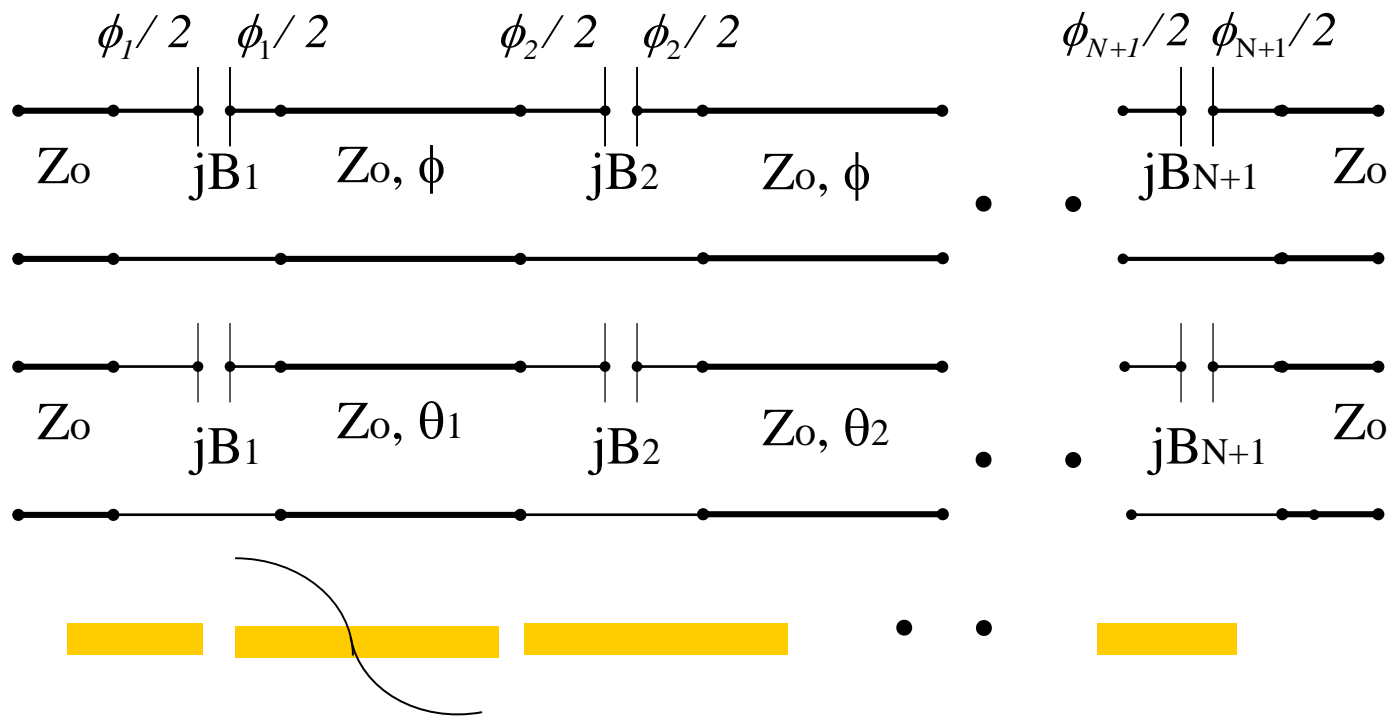

design
equation

$$\phi_o = \pi \left(l = \frac{\lambda_o}{2} \right), \theta_i = \pi + \frac{\phi_i}{2} + \frac{\phi_{i+1}}{2} = \pi - \left(\tan^{-1} \frac{2B_i}{Y_o} + \tan^{-1} \frac{2B_{i+1}}{Y_o} \right)$$

$$B_i = \frac{J_i}{1 - (Z_o J_i)^2}$$

5. Design procedure for microstrip BPF using capacitively coupled resonator


LPF prototype $g_i \rightarrow J_i \rightarrow B_i, \phi_i \rightarrow C_i, \theta_i \rightarrow$ microstrip gap width and line length \rightarrow consider discontinuity effect

6. Ex.8.9 design a 0.5dB ripple equal-ripple BPF using capacitively coupled resonators, $f_o=2\text{GHz}$, $\text{BW}=10\%$, $Z_o=50\Omega$, $\text{IL}(2.2\text{GHz}) > 20\text{dB}$

i	g_i	$Z_o J_i$	$B_i(\times 10^{-3})$	$C_i(\text{pF})$	$\theta_i(\text{deg})$
1	1.5963	0.3137	6.96	0.554	155.8
2	1.0967	0.1187	2.41	0.192	166.5
3	1.5963	0.1187	2.41	0.192	166.5
4	1.0000	0.3137	6.96	0.554	

frequency response (p.443, Fig.8.51)

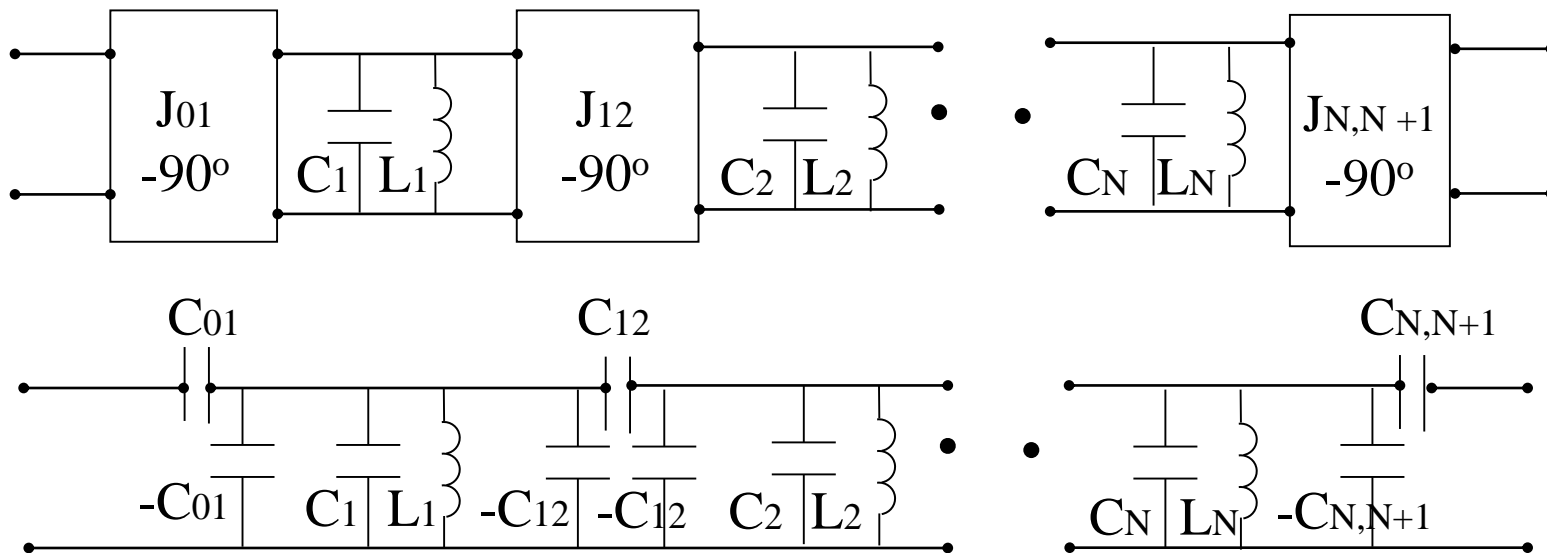
7. BPF using capacitively coupled shunt stub resonator



design equation

$$Z_o J_{01} = \sqrt{\frac{\pi\Delta}{4g_1}}, Z_o J_{n,n+1} = \frac{\pi\Delta}{4\sqrt{g_n g_{n+1}}}, Z_o J_{N,N+1} = \sqrt{\frac{\pi\Delta}{4g_N g_{N+1}}}$$
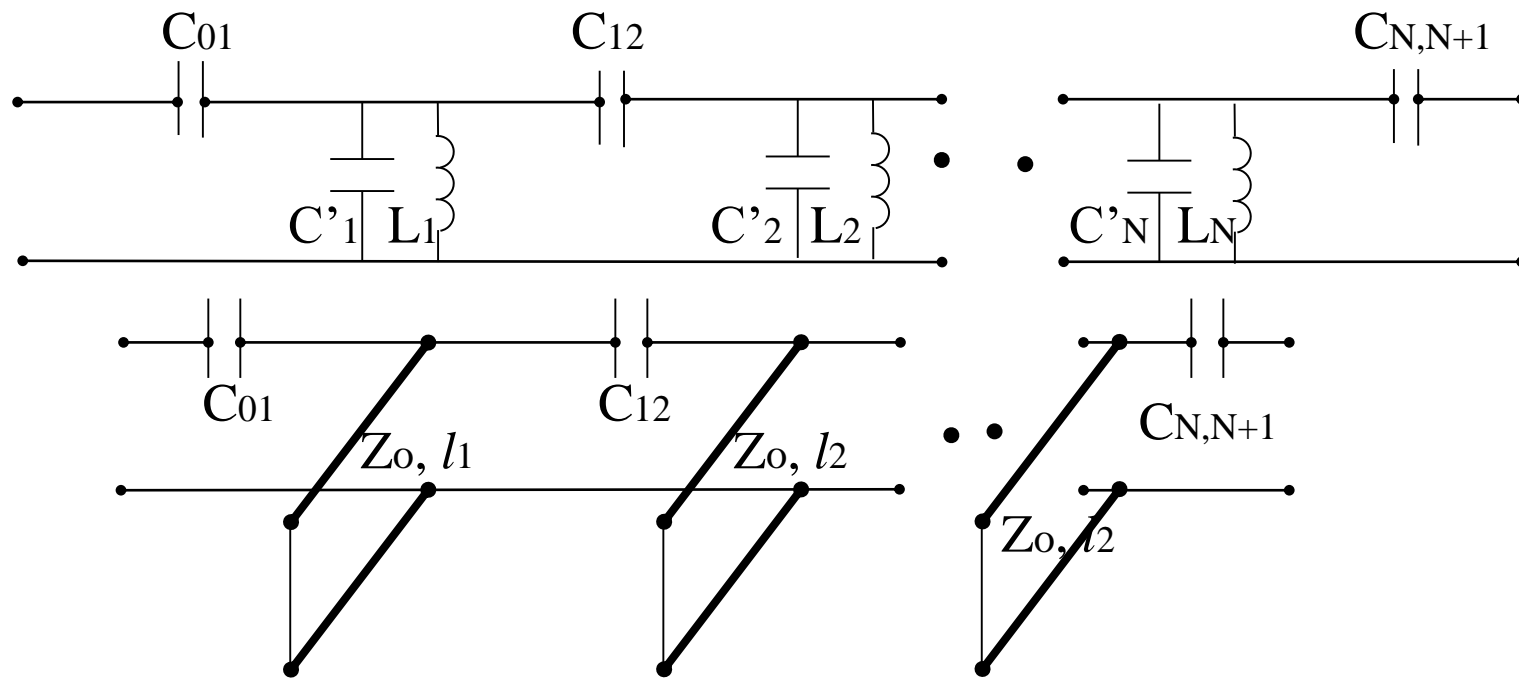
$$C_{01} = \frac{J_{01}}{w_0 \sqrt{1 - (Z_o J_{01})^2}}, C_{n,n+1} = \frac{J_{n,n+1}}{w_0}, C_{N,N+1} = \frac{J_{N,N+1}}{w_0 \sqrt{1 - (Z_o J_{N,N+1})^2}}$$





design equation

$$C'_n = C_n - C_{n-1,n} - C_{n,n+1} = C_n + \Delta C_n, \quad \Delta C_n = -C_{n-1,n} - C_{n,n+1}$$

$$l_n = \frac{\lambda}{4} + \frac{Z_o w_o \Delta C_n}{2\pi} \lambda$$

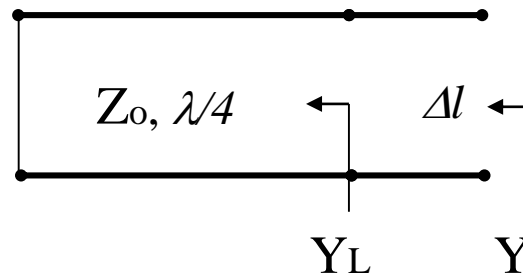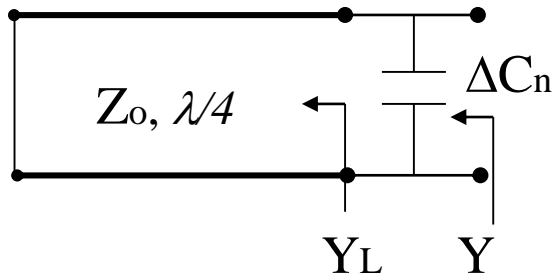(derivation of the change of stub length due to a shunt capacitor)



$$Y = Y_L + j\omega_o \Delta C_n$$

$$Y = \frac{1}{Z} = \frac{1}{Z_o \frac{Z_L + jZ_o \tan \beta \Delta l}{Z_o + jZ_L \tan \beta \Delta l}} = \frac{1}{Z_o} \frac{Z_o + jZ_L \tan \beta \Delta l}{Z_L + jZ_o \tan \beta \Delta l}$$

$$= \frac{1}{Z_o} \frac{Y_L + j \frac{1}{Z_o} \tan \beta \Delta l}{\frac{1}{Z_o} + jY_L \tan \beta \Delta l} \stackrel{\beta \Delta l \ll 1}{\approx} Y_L + j \frac{\beta \Delta l}{Z_o}$$

$$j\omega_o \Delta C_n = j \frac{\beta_o \Delta l}{Z_o} = j \frac{2\pi \Delta l}{Z_o \lambda} \rightarrow \Delta l = \frac{Z_o \omega_o \Delta C_n}{2\pi} \lambda$$

8. Design procedure for BPF using capacitively coupled shunt stub resonator

LPF prototype $g_i \rightarrow J_{i-1,i} \rightarrow C_i \rightarrow \Delta C_i \rightarrow \Delta l_i \rightarrow$ resonator length \rightarrow consider discontinuity effect

9. Ex.8.10 design a 0.5dB ripple 3rd order equal-ripple BPF using capacitively coupled shunt resonators, $f_o=2\text{GHz}$, $\text{BW}=10\%$, $Z_o=50\Omega$,

i	g_i	$Z_o J_{i-1,i}$	$C_{i-1,i}(\text{pF})$	$\Delta C_i(\text{pF})$	$\Delta l_i(\lambda)$	l
1	1.5963	0.2218	0.2896	-0.3652	-0.04565	73.6°
2	1.0967	0.0594	0.0756	-0.1512	-0.0189	83.2°
3	1.5963	0.0594	0.0756	-0.3652	-0.04565	73.6°
4	1.0000	0.2218	0.2896			

frequency response (p.447, Fig.8.54)

ADS examples: Ch8_prj