
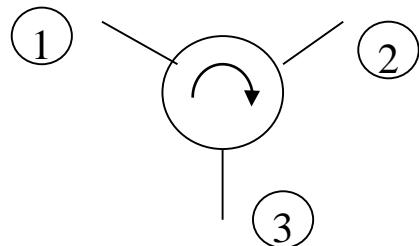


Chapter 9 Theory and Design of Ferrimagnetic Components

9.6 Ferrite circulator

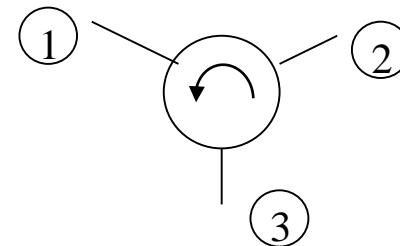

$$\begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$



$$\begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$


Discussion

1. Circular structure (p.487, Fig.9.22) includes stripline, ferrite disk and bias magnet.
2. A lossless, small mismatched Γ circulator

$$\begin{bmatrix} \Gamma & \Gamma & 1-\Gamma^2 \\ 1-\Gamma^2 & \Gamma & \Gamma \\ \Gamma & 1-\Gamma^2 & \Gamma \end{bmatrix}$$

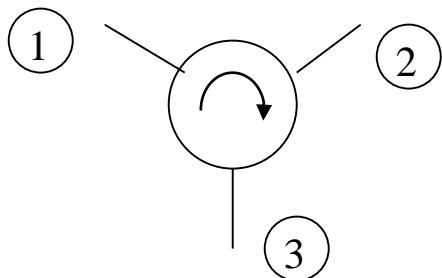3. Terminate one port of circulator \rightarrow isolator

(derivation of 2 for a lossless, small mismatched Γ circulator)



$$\begin{bmatrix} \Gamma & \beta & \alpha \\ \alpha & \Gamma & \beta \\ \beta & \alpha & \Gamma \end{bmatrix} \xrightarrow{\text{lossless}} |\Gamma|^2 + |\alpha|^2 + |\beta|^2 = 1$$

$$\Gamma\beta^* + \alpha\Gamma^* + \beta\alpha^* = 0$$

$$|\Gamma| \ll 1, |\alpha| \approx 1, |\beta| \ll 1$$

$$\rightarrow \alpha\Gamma^* + \beta\alpha^* \approx 0 \rightarrow |\Gamma| \approx |\beta|$$

$$\rightarrow 2|\Gamma|^2 + |\alpha|^2 = 1 \rightarrow |\alpha| \approx 1 - |\Gamma|^2$$

$$\Rightarrow \begin{bmatrix} \Gamma & \Gamma & 1 - \Gamma^2 \\ 1 - \Gamma^2 & \Gamma & \Gamma \\ \Gamma & 1 - \Gamma^2 & \Gamma \end{bmatrix}$$


isolation: $|S_{23}| \approx |S_{12}| \approx |S_{31}| \approx |\Gamma|$

Chapter 10 Noise and Nonlinear Distortion

- 10.1/2 Noise in microwave circuits/Noise figure
 - noise power, equivalent noise temperature, noise figure of various networks
- 10.3/4 Nonlinear distortion/Dynamic range
 - gain compression, third-order intermodulation distortion, 3rd-order intercept point, linear and spurious free dynamic range

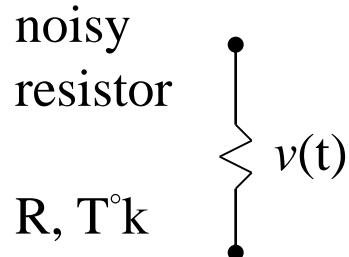
10.1/10.2 Noise in microwave circuits/Noise figure

- noise power, equivalent noise temperature, noise figure



$$\text{rms voltage } v_n = \sqrt{4kTBR}$$

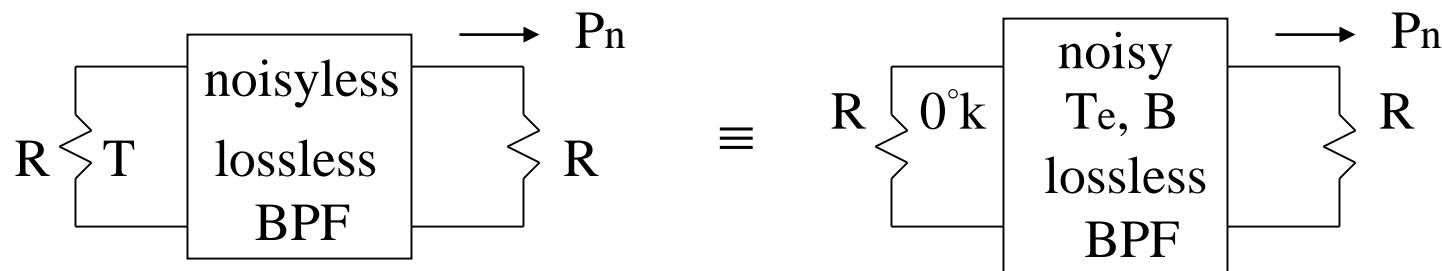at microwave frequencies: white noise source



maximum power delivered from the noisy resistor


$$P_n = \left(\frac{v_n}{2R}\right)^2 R = \frac{4kTBR}{4R^2} R = kTB$$

equivalent noise temperature $T_e \equiv P_n/kB$

excess noise ratio

$$ENR(dB) \equiv 10 \log \frac{P_n - P_o}{P_o} = 10 \log \frac{T_e - T_o}{T_o}, \quad T_o = 290^\circ K$$


微波電路講義

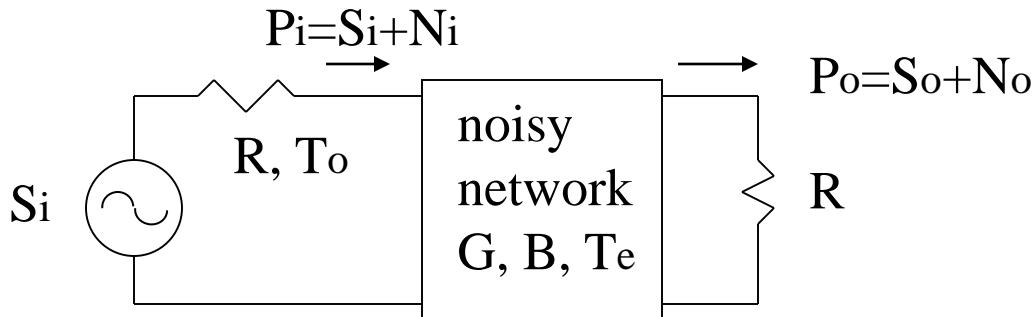

$$S_o = GS_i, N_i = kT_o B, N_o = Gk(T_o + T_e)B$$


$$\text{noise figure } F \equiv \frac{S_i/N_i}{S_o/N_o} = \frac{S_i}{S_o} \frac{N_o}{N_i} = \frac{1}{G} \frac{Gk(T_o + T_e)B}{kT_o B} = 1 + \frac{T_e}{T_o} > 1$$

$$T_e = (F - 1)T_o$$

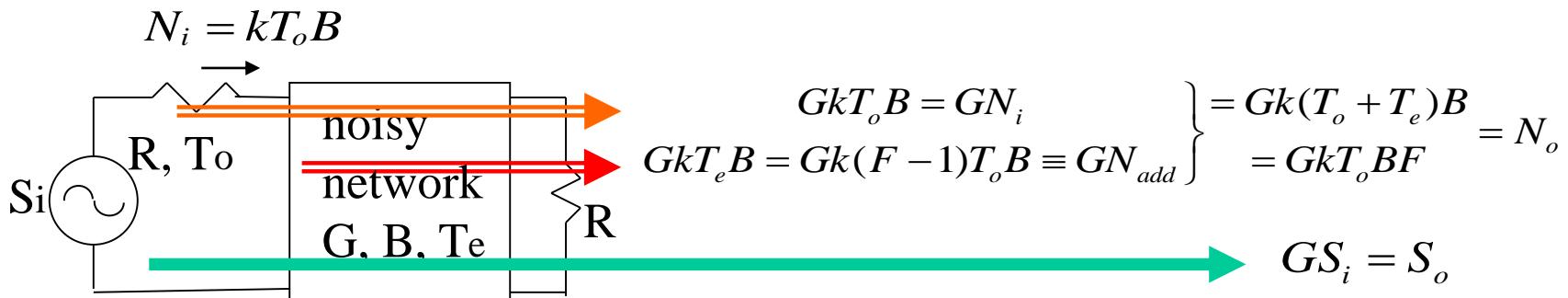


Discussion

1. noisy amplifier with Te

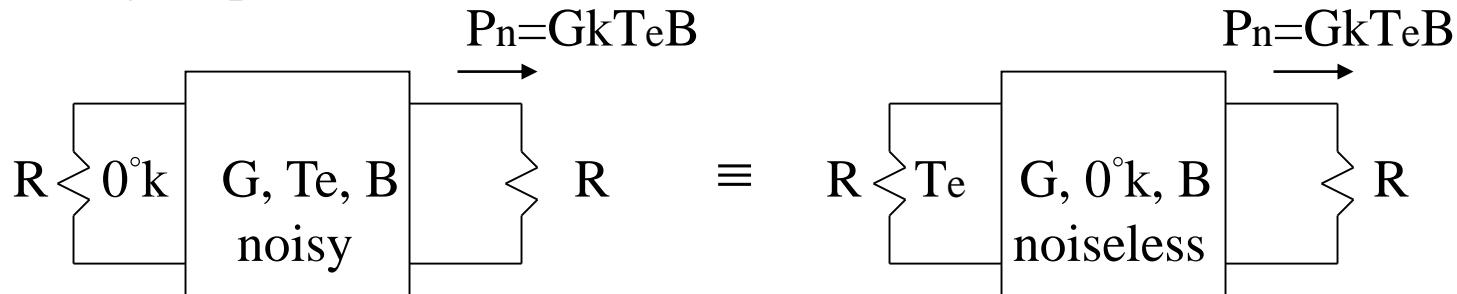

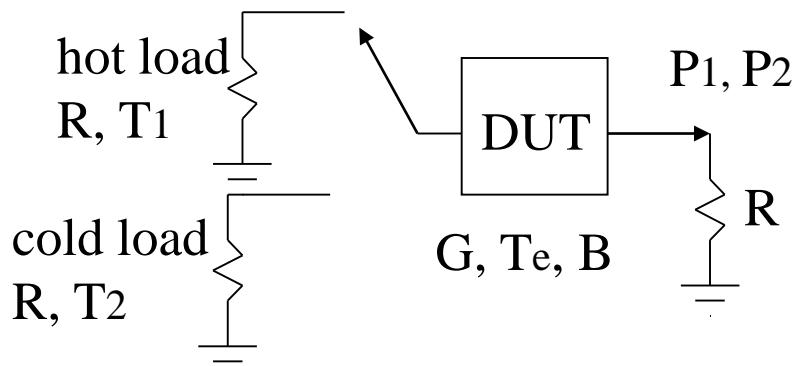2. Y-factor (noise figure, noise temperature) measurement method




$$Y \equiv \frac{P_1}{P_2} = \frac{Gk(T_1 + T_e)B}{Gk(T_2 + T_e)B} = \frac{T_1 + T_e}{T_2 + T_e}$$

$$\rightarrow T_e = \frac{T_1 - YT_2}{Y - 1}, \quad F = 1 + \frac{T_e}{T_o}$$

3. Ex10.1 X-band amplifier, $G=20\text{dB}$, $B=1\text{GHz}$, gives Y-factor measured results as $T_1=290^\circ\text{k}$, $P_1= -62\text{dBm}$, $T_2=77^\circ\text{k}$, $P_2= - 64.7\text{dBm}$.
 $Y = P_1 - P_2 = 2.7\text{dB} = 1.86 \rightarrow T_e = 170^\circ\text{k} \rightarrow F = 1.585 = 2\text{dB}$

if $T_s = 450^\circ\text{k} \rightarrow P_n = k(T_s + T_e)BG = -60.7\text{dBm}$

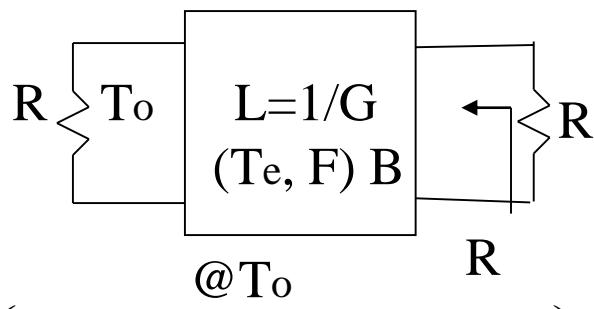4. F of a passive lossy matched 2-port circuit



@ T_o ∵ thermal equilibrium $N_o = N_i = kT_o B, S_o = \frac{S_i}{L}$

$$F = \frac{S_i/N_i}{S_o/N_o} = \frac{S_i}{S_o} \frac{N_o}{N_i} = L(= 1 + \frac{T_e}{T_o})$$

$$\begin{aligned} & @ T_o \quad R \\ & \left(\begin{array}{l} N_o = kT_o B = \frac{1}{L} kT_o B + \frac{1}{L} kT_e B \\ \rightarrow T_e = (L-1)T_o \end{array} \right) \quad \rightarrow T_e = (L-1)T_o = \frac{1-G}{G} T_o, N_{add} = kT_e B = (L-1)kBT_o \\ & \Rightarrow @ T, T_e = (L-1)T, F = 1 + \frac{(L-1)T}{T_o} \end{aligned}$$

5. Ex. 10.3 a matched lossy Wilkinson power divider ($IL=L_w$) with port 3 connected to a matched load, find its F


$$[S] = \frac{-j}{\sqrt{2L_w}} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}, L = \frac{1}{|S_{21}|^2} = 2L_w$$

$$T_e = (L-1)T = (2L_w - 1)T, F = 1 + \frac{T_e}{T_o} = 1 + (2L_w - 1) \frac{T}{T_o}$$

if $L_w = 1$ (lossless), $T = T_o \rightarrow F = 2 = 3dB$
10-5


微波電路講義

6. F of a cascaded circuit

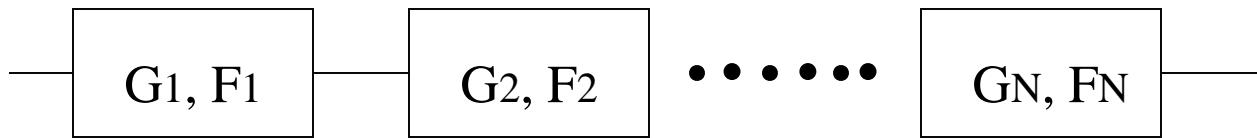

$$\begin{aligned}
 F &= \frac{S_i/N_i}{S_o/N_o} = \frac{S_i}{S_o} \frac{N_o}{N_i} \\
 &= \frac{1}{\prod_{i=1}^N G_i} \frac{kT_o B \prod_{i=1}^N G_i + k(F_1 - 1)T_o B \prod_{i=1}^N G_i + k(F_2 - 1)T_o B \prod_{i=2}^N G_i + \dots + k(F_N - 1)T_o B G_N}{kT_o B} \\
 &= 1 + (F_1 - 1) + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots + \frac{F_N - 1}{G_1 \dots G_{N-1}} \\
 &= F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots + \frac{F_N - 1}{G_1 \dots G_{N-1}} \\
 T &= T_{e1} + \frac{T_{e2}}{G_1} + \frac{T_{e3}}{G_1 G_2} + \dots + \frac{T_{eN}}{G_1 \dots G_{N-1}}
 \end{aligned}$$

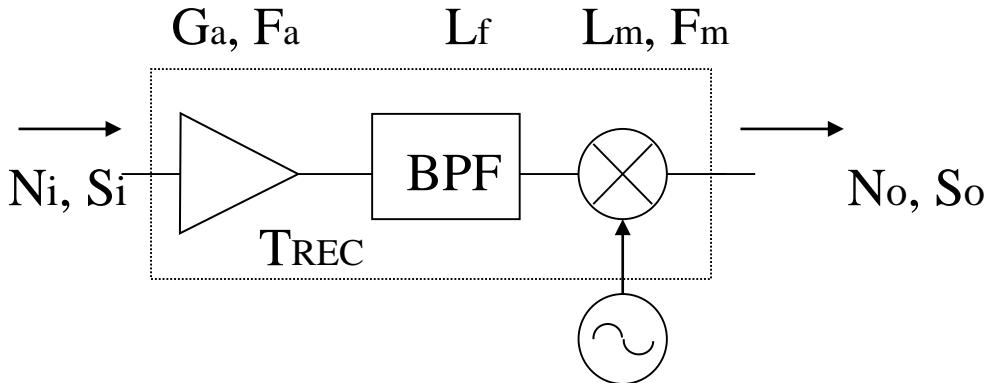7. noise analysis of a microwave receiver



i/p noise power from antenna $T_A \rightarrow N_i = kT_A B$


receiver noise $F_{REC} = F_a + \frac{F_f - 1}{G_a} + \frac{F_m - 1}{G_a G_f} \rightarrow T_{REC} = (F_{REC} - 1)T$

o/p signal power $S_o = S_i \frac{G_a G_m}{L_f} = S_i G_{REC}$

o/p noise power $N_o = (N_i + kBT_{REC})G_{REC} = kB(T_A + T_{REC})G_{REC}$

o/p $\frac{S_o}{N_o} = \frac{S_i}{kB(T_A + T_{REC})}$

8. Ex.10.2

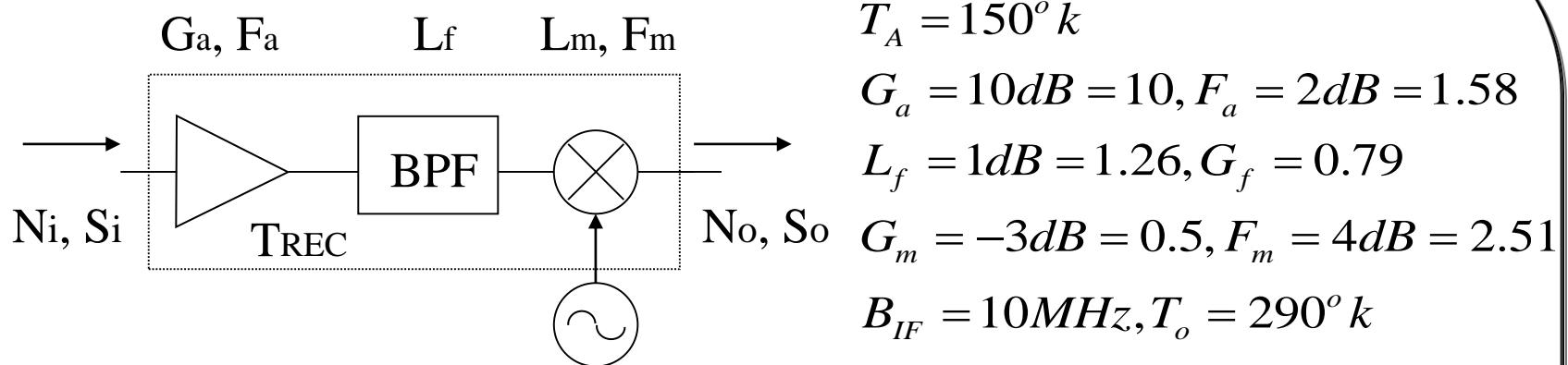

$$\text{i/p noise power } N_i = kT_A B = 1.38 \times 10^{-23} \times 150 \times 10^7 = 2.07 \times 10^{-14} W = -106.8 dBm$$

$$\text{receiver noise figure } F_{REC} = F_a + \frac{F_f - 1}{G_a} + \frac{F_m - 1}{G_a G_f} = 1.8 = 2.5 dB$$


$$\text{receiver noise temperature } T_{REC} = (F_{REC} - 1)T_o = 232^\circ k$$

$$\text{receiver gain } G_{REC} = \frac{G_a G_m}{L_f} = 3.95 = 6 dB$$

$$\begin{aligned} \text{o/p noise power } N_o &= kB(T_A + T_{REC})G_{REC} \\ &= 1.38 \times 10^{-23} \times 10^7 \times 382 \times 3.95 = 2.08 \times 10^{-13} W = -96.8 dBm \end{aligned}$$

$$\text{if } SNR_o = 20dB \xrightarrow{-96.8 dBm} S_o = -76.8 dBm \xrightarrow{-6dB} S_i = -82.8 dBm \rightarrow SNR_i \geq 24dB$$

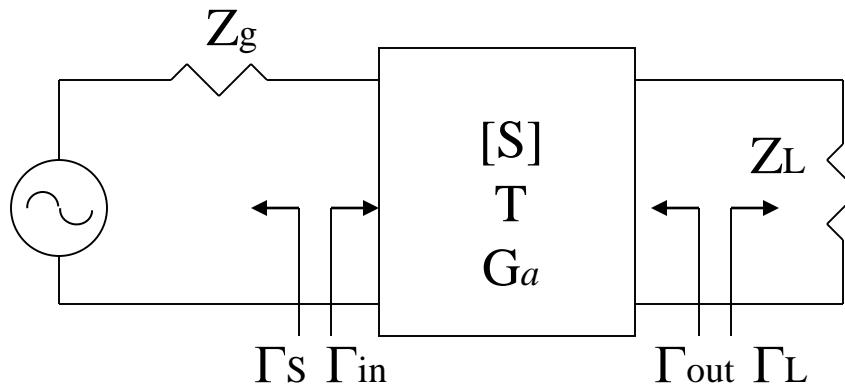9. F of a passive lossy mismatched ($\Gamma_s \neq 0, \Gamma_{out} \neq 0$) 2-port circuit



$$G_a = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \dots (12.12)$$

$$= |S_{21}|^2, \text{ for } \Gamma_s = \Gamma_{out} = 0$$


i/p noise power $N_i = kTB$

$$\text{available power gain } G_a \equiv \frac{P_{av_n}}{P_{av_s}} = \frac{P_L|_{\Gamma_L=\Gamma_{out}^*}}{P_{in}|_{\Gamma_{in}=\Gamma_s^*}} \equiv \frac{1}{L_a} < 1$$

$$\begin{aligned} \text{available o/p noise power } N_o &= G_a(N_i + N_{added}) = G_a k(T + T_e)B \\ &= kTB(\text{thermal equilibrium}) \end{aligned}$$

$$\rightarrow T_e = \frac{1 - G_a}{G_a} T = (L_a - 1)T, F = 1 + \frac{T_e}{T_o} = 1 + \frac{1 - G_a}{G_a} \frac{T}{T_o} = 1 + \frac{(L_a - 1)T}{T_o}$$

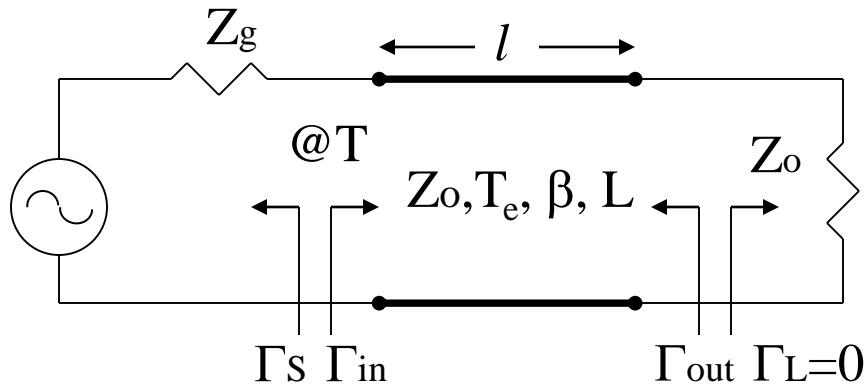10. F of a mismatched ($\Gamma_s \neq 0$) lossy line



$$[S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{L}} e^{-j\beta l} \\ \frac{1}{\sqrt{L}} e^{-j\beta l} & 0 \end{bmatrix}$$


$$\Gamma_s = \frac{Z_g - Z_o}{Z_g + Z_o}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} = \frac{\Gamma_s}{L} e^{-j2\beta l}$$

$$G_a = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)} = \frac{\frac{1}{L} (1 - |\Gamma_s|^2)}{1 - \frac{|\Gamma_s|^2}{L^2}} = \frac{L(1 - |\Gamma_s|^2)}{L^2 - |\Gamma_s|^2} \equiv \frac{1}{L_a}$$

$$\rightarrow T_e = (L_a - 1)T = \frac{(L - 1)(L + |\Gamma_s|^2)}{L(1 - |\Gamma_s|^2)} T > (L - 1)T|_{\Gamma_s=0}, F = 1 + \frac{(L_a - 1)T}{T_o}$$

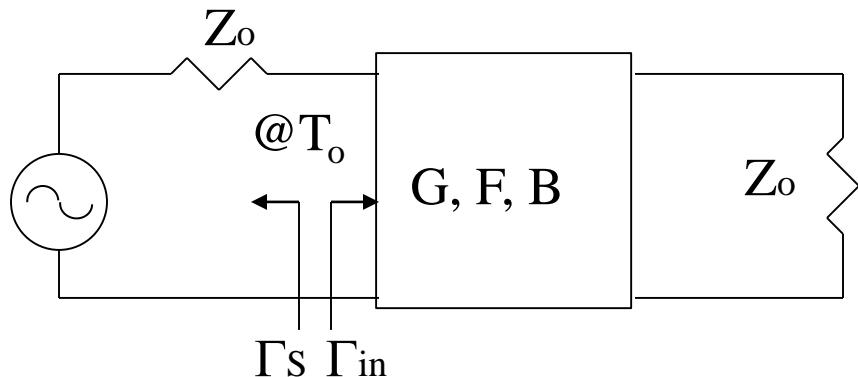11. F of a mismatched ($\Gamma_{in} \neq 0$) amplifier



$$N_i = kT_o B$$

$$N_o = kT_o GB(1 - |\Gamma_{in}|^2) + kT_o(F-1)GB = kT_o GB(F - |\Gamma_{in}|^2)$$

$$S_o = G(1 - |\Gamma_{in}|^2)S_i$$

$$\rightarrow F_m = \frac{S_i / N_i}{S_o / N_o} = \frac{S_i N_o}{S_o N_i} = \frac{S_i}{G(1 - |\Gamma_{in}|^2)S_i} \frac{kT_o GB(F - |\Gamma_{in}|^2)}{kT_o B} = \frac{F - |\Gamma_{in}|^2}{1 - |\Gamma_{in}|^2}$$

$$= 1 + \frac{F-1}{1 - |\Gamma_{in}|^2}, |\Gamma_{in}| = 0, F_m = F$$

10.3/4 Nonlinear distortion/Dynamic range

- gain compression

$$v_o = a_o + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots$$


$$OP1dB = IP1dB + G - 1dB$$

linear dynamic range of an amplifier
with gain G

$$MDS_{in} (\text{dBm}) = kTB + F (+3\text{dB})$$

$$MDS_{out} (\text{dBm}) = kTB + F + G (+3\text{dB})$$

$$DR_l (\text{dB}) = OP1dB - MDS_{out}$$

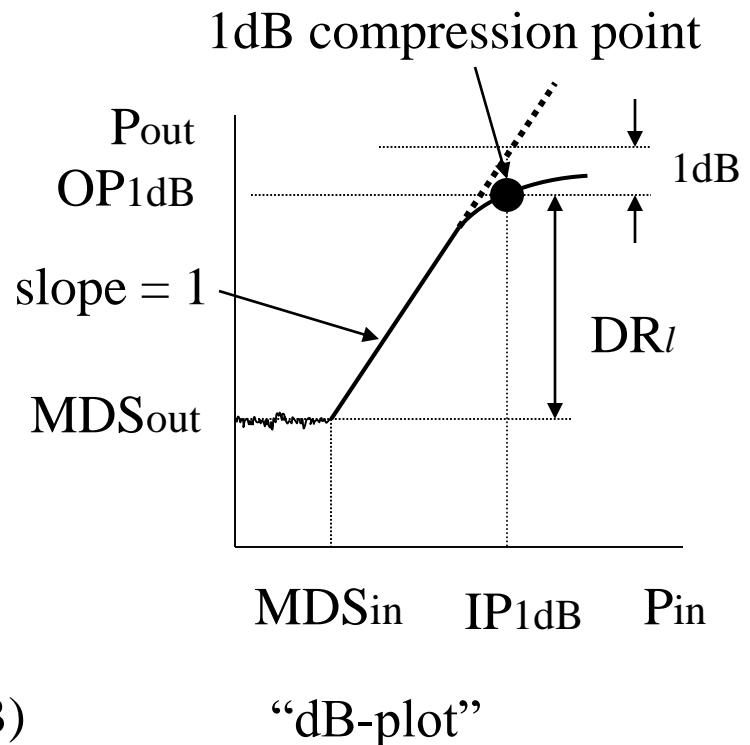

- intermodulation distortion



$$v_o = a_o + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots$$

$v_i^2 : w_1, w_2 \rightarrow 2w_1, 2w_2, w_1 - w_2, w_1 + w_2$ 2nd-order products


$v_i^3 : w_1, w_2 \rightarrow 3w_1, 3w_2, 2w_1 - w_2, 2w_1 + w_2, 2w_2 - w_1, 2w_2 + w_1$ 3rd-order products

$2w_1 - w_2, 2w_2 - w_1$: 3rd-order intermodulation distortion (IMD3)
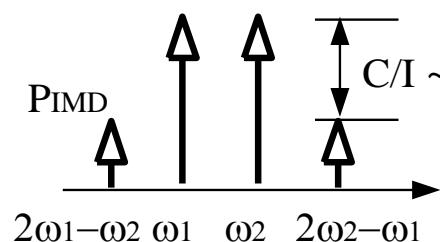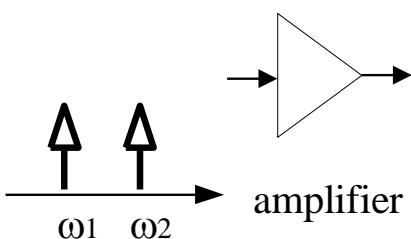
$$\text{OIP}_3(\text{dB}) = G + \text{IIP}_3$$



3rd-order intercept point (IP3)

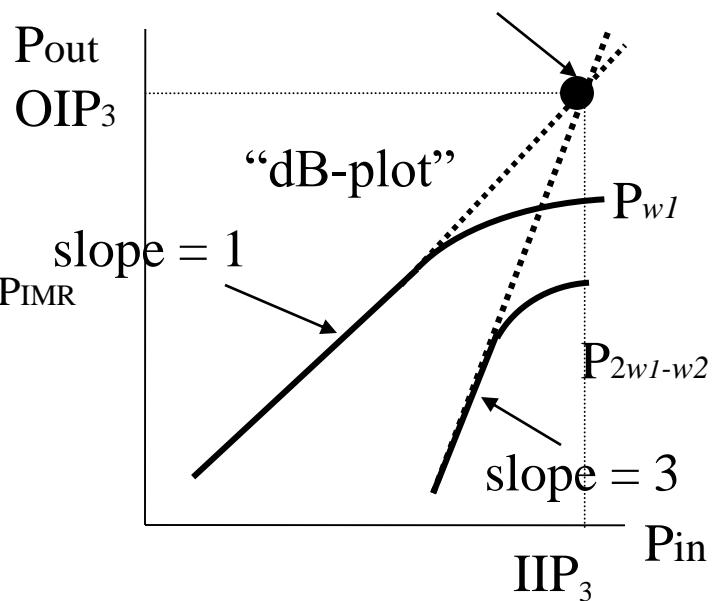

Discussion

1. device nonlinearity effect

$$\text{If } v_o = a_1 v_i + a_2 v_i^2 + a_3 v_i^3$$

$$\text{single tone input } v_i = A \cos w_1 t \Rightarrow v_o \Big|_{w_1} = (a_1 A + \frac{3}{4} a_3 A^3) \cos w_1 t$$

$$\rightarrow \text{voltage gain}@w_1 \quad G_v = a_1 + \frac{3}{4} a_3 A^2$$

$$\text{two tone input } v_i = A(\cos w_1 t + \cos w_2 t)$$

$$\Rightarrow v_o \Big|_{2w_1-w_2} = \frac{3}{4} a_3 A^3 \cos(2w_1 - w_2)t$$

$$\text{at third-order intercept point } a_1 A = \frac{3}{4} a_3 A^3 \rightarrow A^2 = \frac{4}{3} \frac{a_1}{a_3}$$


$$\rightarrow OIP_3 = \frac{1}{2} \frac{(a_1 A)^2}{R} = \frac{2}{3} \frac{a_1^3}{a_3 R}, P_{2w_1-w_2} (\equiv P_{IMD}) = \frac{1}{2} \frac{(\frac{3}{4} a_3 A^3)^2}{R} = \frac{9}{32} \frac{a_3^2 A^6}{R}$$

$$\frac{P_{w_1}^3}{OIP_3^2} = \frac{\frac{1}{2} \frac{(a_1 A)^2}{R}}{\left[\frac{2}{3} \frac{a_1^3}{a_3 R} \right]^2} = \frac{9}{32} \frac{a_3^2 A^6}{R} = P_{2w_1-w_2} \Rightarrow 3P_{w_1} - 2OIP_3 = P_{2w_1-w_2} (\text{dBm})$$

2. spurious-free dynamic range

$$\begin{aligned}
 DR_f &\equiv \frac{P_{w_1}}{P_{2w_1-w_2}} \Bigg|_{P_{2w_1-w_2}=P_n} \\
 &= \frac{\frac{1}{P_{2w_1-w_2}^{\frac{1}{3}}} OIP_3^{\frac{2}{3}}}{P_{2w_1-w_2}} \Bigg|_{P_{2w_1-w_2}=P_n} = \left(\frac{OIP_3}{P_n}\right)^{\frac{2}{3}}
 \end{aligned}$$

$$DR_f(dB) = \frac{2}{3}(OIP_3 - P_n)$$

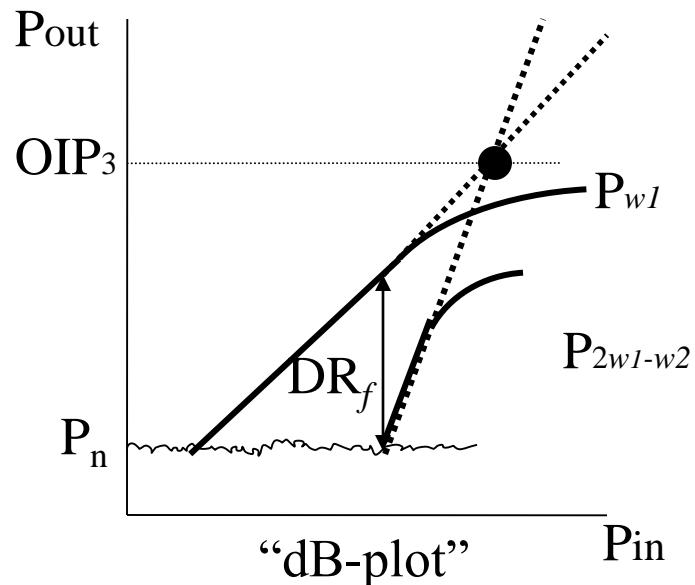


3. Ex. 10.5 A receiver with $F=7\text{dB}$, $OP_{1\text{dB}}=25\text{dBm}$, $G=40\text{dB}$, $OIP_3=35\text{dBm}$, $B=100\text{MHz}$, i/p antenna noise temperature $T_A=150^\circ\text{k}$, desired $SNR_o=10\text{dB}$, find DR_l and DR_f

$$\text{o/p noise power } P_n = GkB[T_A + (F-1)T_o] = 10^4 \times 1.38 \times 10^{-23} \times 10^8 \times [150 + (5-1) \times 290] = -47.4\text{dBm}$$

$$DR_l = OP_{1\text{dB}} - P_n = 25 - (-47.4) = 72.4\text{dB}$$

$$DR_f = \frac{2}{3}(OIP_3 - P_n) = 55\text{dB}, \text{ or } \frac{2}{3}(OIP_3 - P_n) - SNR_o = 45\text{dB}$$

4. Cascaded two-port circuits

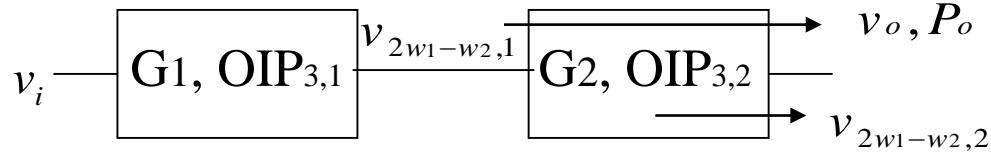

$$P_o = P_i G_1 G_2 = P_{o,1} G_2 (@ \text{ fundamental frequency } w_o)$$

$$\frac{P_o^3}{\text{OIP}_3^2} = P_{2w_1-w_2} \rightarrow v_{2w_1-w_2} = \sqrt{P_{2w_1-w_2} Z_o} = \frac{\sqrt{P_o^3 Z_o}}{\text{OIP}_3}$$

worst case, two intermods @ $2w_1 - w_2$ add in phase →

$$v_{2w_1-w_2} = v_{2w_1-w_2,1} \sqrt{G_2} + v_{2w_1-w_2,2} = \frac{\sqrt{G_2 P_{o,1}^3 Z_o}}{\text{OIP}_{3,1}} + \frac{\sqrt{P_o^3 Z_o}}{\text{OIP}_{3,2}} = \frac{\sqrt{G_2 (P_o^3 / G_2^3) Z_o}}{\text{OIP}_{3,1}} + \frac{\sqrt{P_o^3 Z_o}}{\text{OIP}_{3,2}}$$

$$= \left(\frac{1}{G_2 \text{OIP}_{3,1}} + \frac{1}{\text{OIP}_{3,2}} \right) \sqrt{P_o^3 Z_o}$$

$$P_{2w_1-w_2} = \frac{v_{2w_1-w_2}^2}{Z_o} = \left(\frac{1}{G_2 \text{OIP}_{3,1}} + \frac{1}{\text{OIP}_{3,2}} \right)^2 P_o^3 = \frac{P_o^3}{\text{OIP}_3^2}$$

$$\Rightarrow \frac{1}{\text{OIP}_3} = \frac{1}{G_2 \text{OIP}_{3,1}} + \frac{1}{\text{OIP}_{3,2}}$$

5. Ex. 10.4 An LNA with $G_1=20\text{dB}$ and $OIP_{3,1}=22\text{dBm}$, a mixer with $G_2=-6\text{dB}$ and $IIP_{3,2}=13\text{dBm}$, find the cascaded P_{IP3}

$$G_1 = 100, G_2 = 0.25, OIP_{3,1} = 22\text{dBm} = 158\text{mW}, OIP_{3,2} = 13 - 6 = 7\text{dBm} = 5\text{mW}$$

$$\frac{1}{OIP_3} = \frac{1}{G_2 OIP_{3,1}} + \frac{1}{OIP_{3,2}} = \frac{1}{0.25 \times 158} + \frac{1}{5} \rightarrow OIP_3 = 4.4\text{mW} = 6.4\text{dBm}$$

(case 2, interchange LNA and mixer, prob.10.15)

$$G_1 = 0.25, OIP_{3,1} = 13 - 6 = 7\text{dBm} = 5\text{mW}$$


$$G_2 = 100, OIP_{3,2} = 22\text{dBm} = 158\text{mW}$$

$$\frac{1}{OIP_3} = \frac{1}{G_2 OIP_{3,1}} + \frac{1}{OIP_{3,2}} = \frac{1}{100 \times 5} + \frac{1}{158} \rightarrow OIP_3 = 120\text{mW} = 20.8\text{dBm}$$

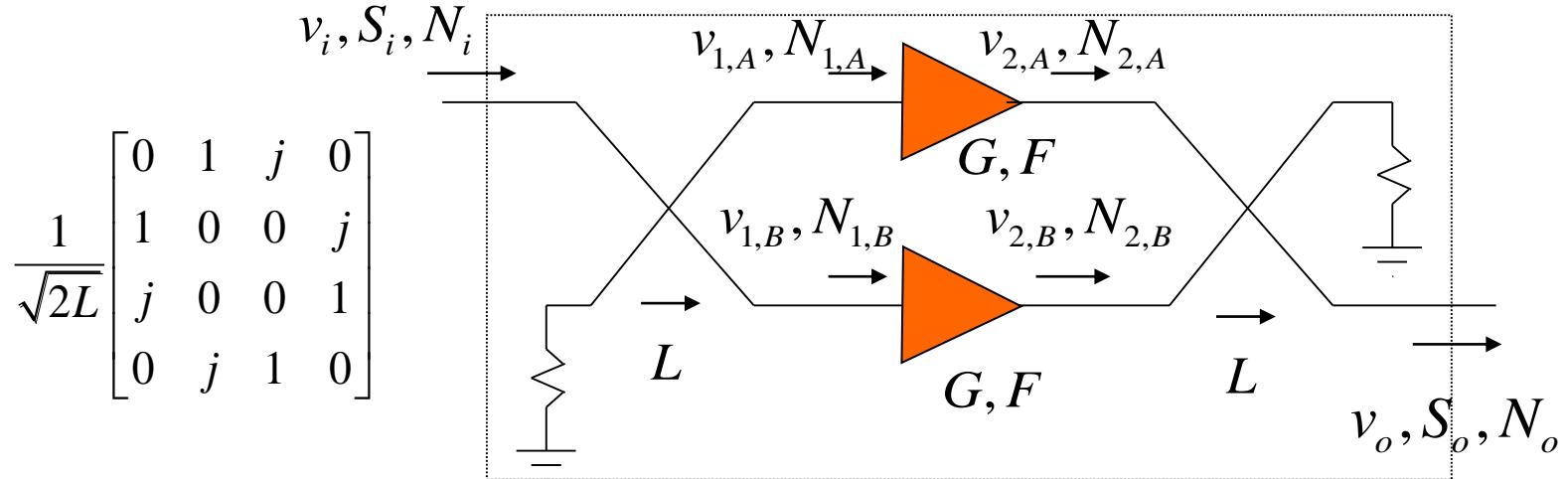6. OIP_3 of a cascaded circuit

$$\frac{1}{OIP_3} = \frac{1}{G_n \dots G_2 OIP_{3,1}} + \frac{1}{G_n \dots G_3 OIP_{3,2}} + \dots + \frac{1}{OIP_{3,n}}$$


Solved problems: Prob. 10.11 F of a balanced amplifier



$$S_i = \frac{1}{2} v_i^2, v_{1,A} = v_i \sqrt{\frac{1}{2L}}, v_{1,B} = jv_i \sqrt{\frac{1}{2L}} \rightarrow v_{2,A} = v_i \sqrt{\frac{G}{2L}}, v_{2,B} = jv_i \sqrt{\frac{G}{2L}}$$

$$v_o = j\sqrt{\frac{1}{2L}}v_{2,A} + \sqrt{\frac{1}{2L}}v_{2,B} = \frac{jv_i \sqrt{G}}{2L} + \frac{jv_i \sqrt{G}}{2L} = \frac{jv_i \sqrt{G}}{L}$$
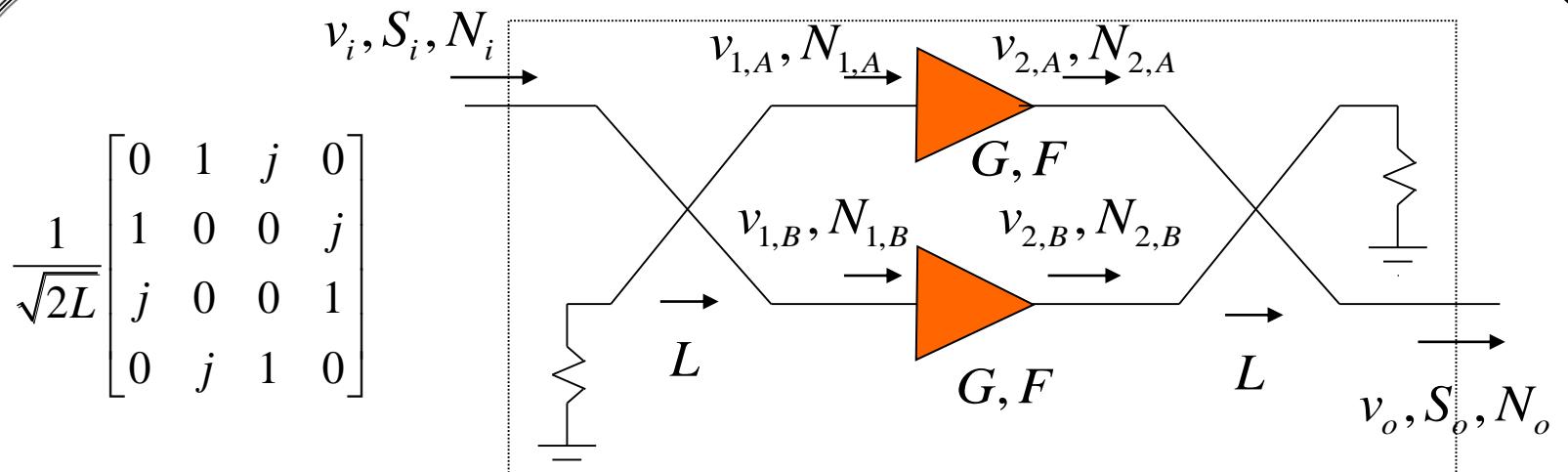
$$S_o = \frac{1}{2} v_o^2 = \frac{1}{2} v_i^2 \frac{G}{L^2} = \frac{G}{L^2} S_i$$



\because thermal equilibrium @ $T_o \rightarrow N_{1,A} = N_{1,B} = kT_o B$

$$N_{2,A} = N_{2,B} = kT_o B G + kT_o (F-1) B G = kT_o B G F$$

$$N_o = \frac{1}{2L} N_{2,A} + \frac{1}{2L} N_{2,B} + \frac{1}{L} kT_e B = \frac{1}{L} kT_o B G F + (1 - \frac{1}{L}) kT_o B = kT_o B \left(\frac{GF}{L} + 1 - \frac{1}{L} \right) = kT_o B \frac{GF + L - 1}{L}$$

$$\because \text{coupler } F = L, T_e = (F-1)T_o = (L-1)T_o \rightarrow \frac{1}{L} N_{add} = \frac{1}{L} kT_e B = \frac{1}{L} (L-1) kT_o B = (1 - \frac{1}{L}) kT_o B$$

$$F_{BA} = \frac{S_i / N_i}{S_o / N_o} = \frac{S_i N_o}{S_o N_i} = \frac{L^2}{G} \frac{GF + L - 1}{L} = LF + \frac{L}{G} (L-1) \rightarrow F_{BA} = F, \text{ for } L=1$$

ADS examples: Ch10_prj

Chapter 11 Active RF and Microwave Devices

11.1 Diodes and diode circuits

Schottky diode, PIN diode, varactor diode

11.2/3 Bipolar junction transistors/Field effect transistors

BJT, MESFET


11.4 Microwave integrated circuits

HMIC, MMIC

11.5 Microwave tubes

11.1 Diodes and diode circuits

- Diode

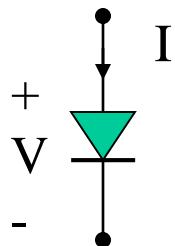

DC I-V characteristics

small signal approximation

$$I(V) = I_s(e^{\alpha V} - 1)$$

$$V = V_o + v$$

$$I(V) = I(V_o) + v \frac{dI}{dV} \Big|_{V_o} + \frac{1}{2} v^2 \frac{d^2 I}{dV^2} \Big|_{V_o} + \dots$$

$$= I_o + vG_d + \frac{1}{2} v^2 G_d' + \dots$$


$$= I_o + i$$

$$G_d' = \alpha G_d$$


AC model

R_j : junction resistance = $1/G_d$

C_j : junction capacitance

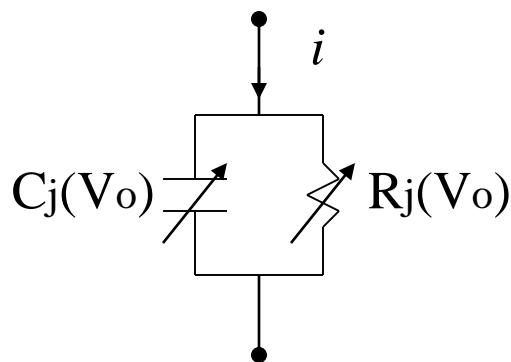

applications: detector, mixer,...

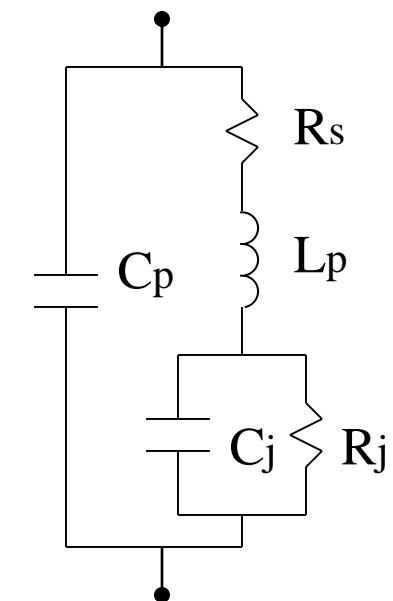

微波電路講義

Discussion

1. square-law detector

$$v(t) = V_o + v_o \cos w_o t$$

$$\begin{aligned} i(t) &= I_o + v_o G_d \cos w_o t + \frac{v_o^2}{2} G'_d \cos^2 w_o t \\ &= I_o + \frac{v_o^2}{4} G'_d + v_o G_d \cos w_o t + \frac{v_o^2}{4} G'_d \cos 2w_o t \end{aligned}$$

current sensitivity $\beta_i \equiv \frac{\Delta I_{dc}}{P_{in}} = \frac{\frac{v_o^2}{4} G'_d}{\frac{v_o^2}{2} G_d} = \frac{G'_d}{2G_d}$, voltage sensitivity $\beta_v = \beta_i R_j$


AM demodulation

$$\begin{aligned} v(t) &= v_o [1 + m(t) \cos w_m t] \cos w_o t \\ i(t) &= v G_d + \frac{v^2}{2} G'_d = v G_d + \frac{v_o^2}{4} G'_d [2m(t) \cos w_m t + \dots] \end{aligned}$$


$\propto P_{in}$

微波電路講義

2. spectrum analyzer

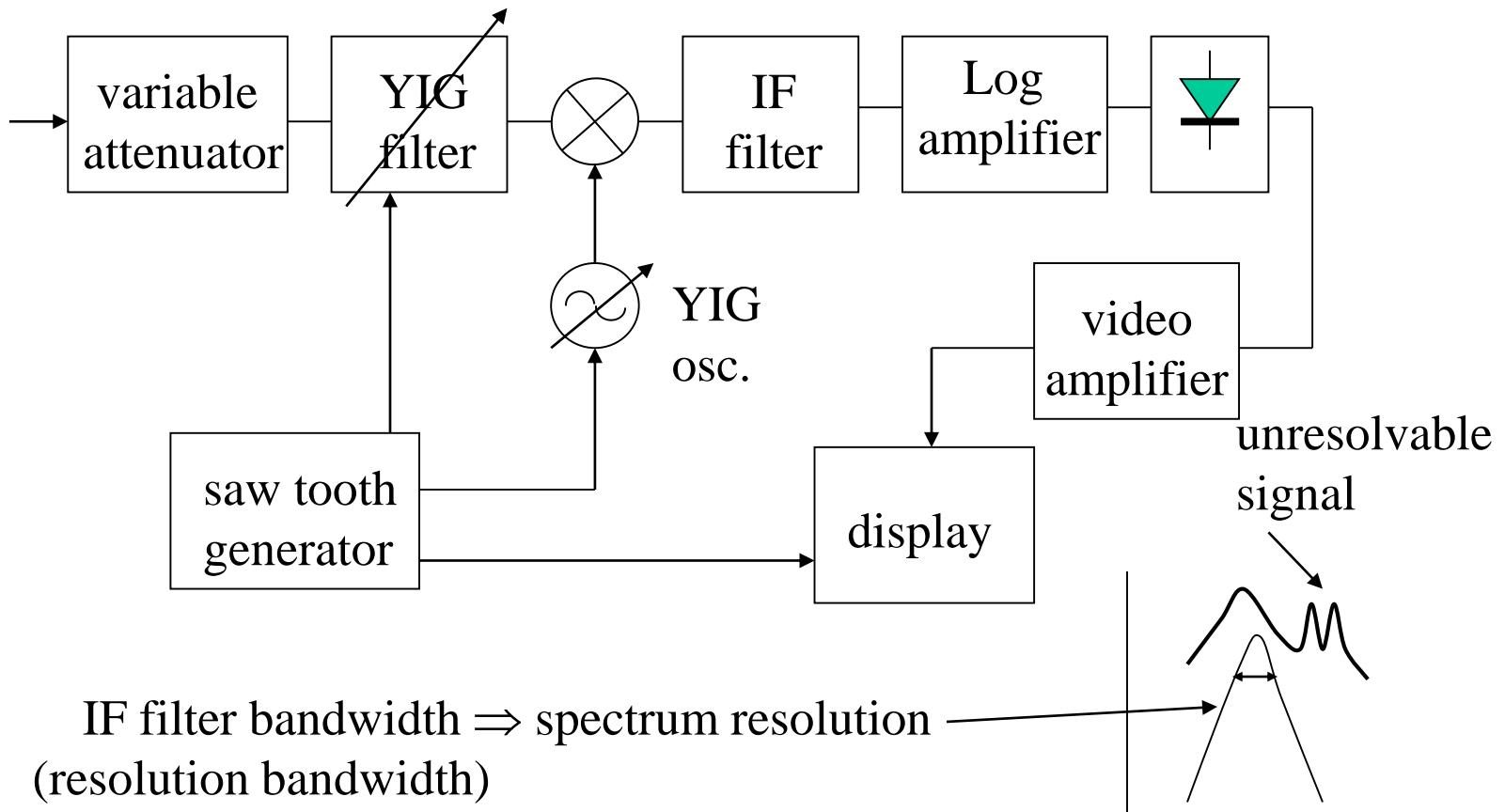


3. PIN diode

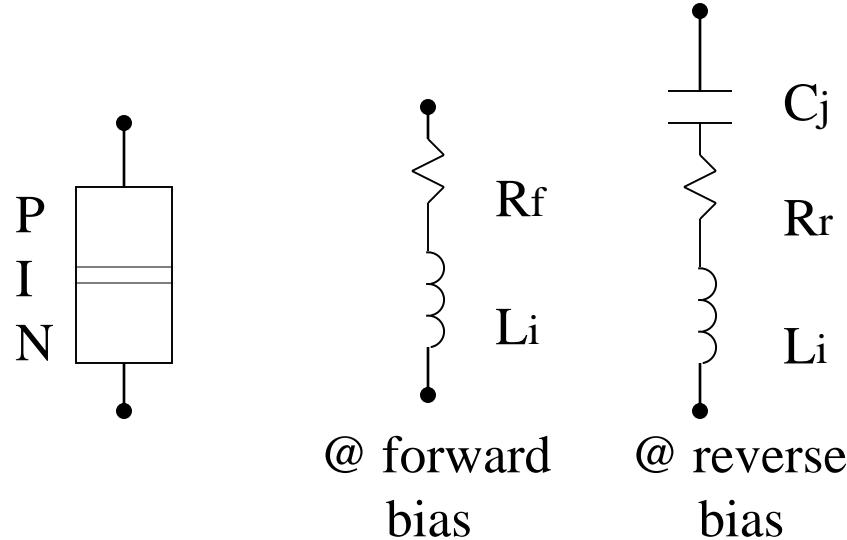

applications: microwave switch, pulse modulator, control elements for phase shifter and attenuator,...

4. SPST switch

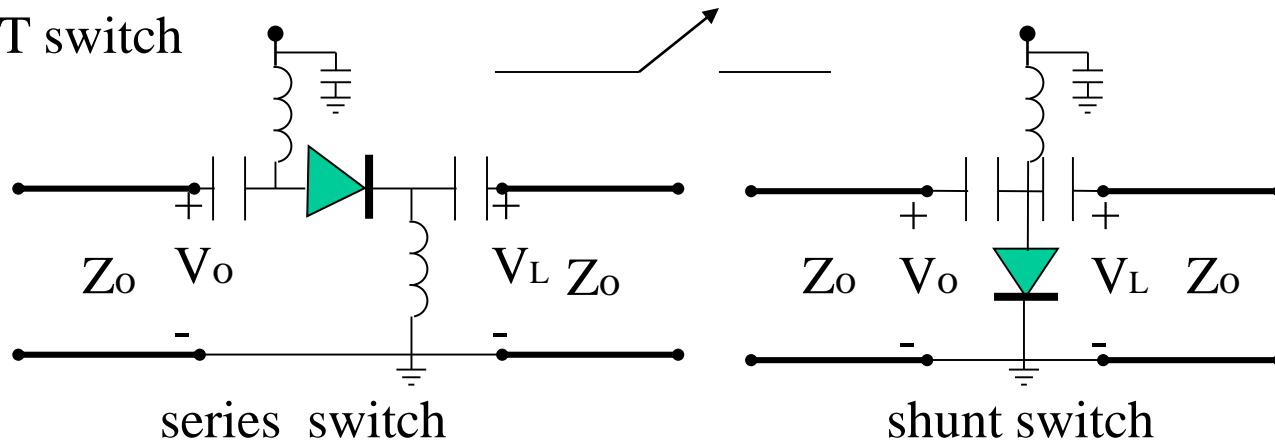


$$IL \equiv -20 \log \left| \frac{V_L}{V_o} \right|$$

$$IL = -20 \log \left| \frac{2Z_o}{2Z_o + Z_d} \right|$$

$$IL = -20 \log \left| \frac{2Z_d}{2Z_d + Z_o} \right|$$

$$Z_d = \begin{cases} R_f + jwL_i & \text{forward bias} \\ R_r + jwL_i + \frac{1}{jwC_j} & \text{reverse bias} \end{cases}$$


(derivation)

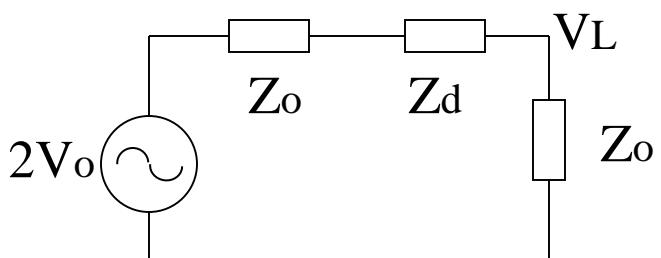

$$V_L = 2V_o \frac{Z_o}{2Z_o + Z_d} = V_o \frac{2Z_o}{2Z_o + Z_d}$$

$$IL \equiv -20 \log \left| \frac{V_L}{V_o} \right| = -20 \log \left| \frac{2Z_o}{2Z_o + Z_d} \right|$$

series switch

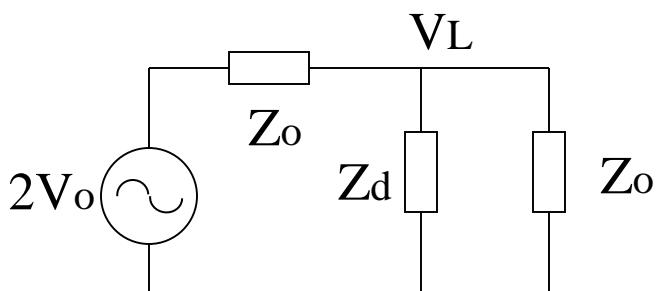

$$V_L = 2V_o \frac{Z_o // Z_d}{Z_o + Z_o // Z_d} = V_o \frac{\frac{Z_o Z_d}{Z_o + Z_d}}{Z_o + \frac{Z_o Z_d}{Z_o + Z_d}}$$

$$= V_o \frac{2Z_d}{2Z_d + Z_o}$$

$$IL \equiv -20 \log \left| \frac{V_L}{V_o} \right| = -20 \log \left| \frac{2Z_d}{2Z_d + Z_o} \right|$$


shunt switch

5. Ex.11.1 $C_j=0.5\text{pF}$, $L_i=0.5\text{nH}$, $R_r=2\Omega$, $R_f=1.5\Omega$, $f=1.8\text{GHz}$, $Z_0=50\Omega$


$$Z_d = \begin{cases} 1.5 + j5.6\Omega & \text{forward bias} \\ 2.0 - j171.2\Omega & \text{reverse bias} \end{cases}$$

$$\text{series switch } IL = \begin{cases} 0.14\text{dB} & \text{ON} \\ 6\text{dB} & \text{OFF} \end{cases} \quad \text{shunt switch } IL = \begin{cases} 0.11\text{dB} & \text{ON} \\ 13.3\text{dB} & \text{OFF} \end{cases}$$

6. SP2T switch

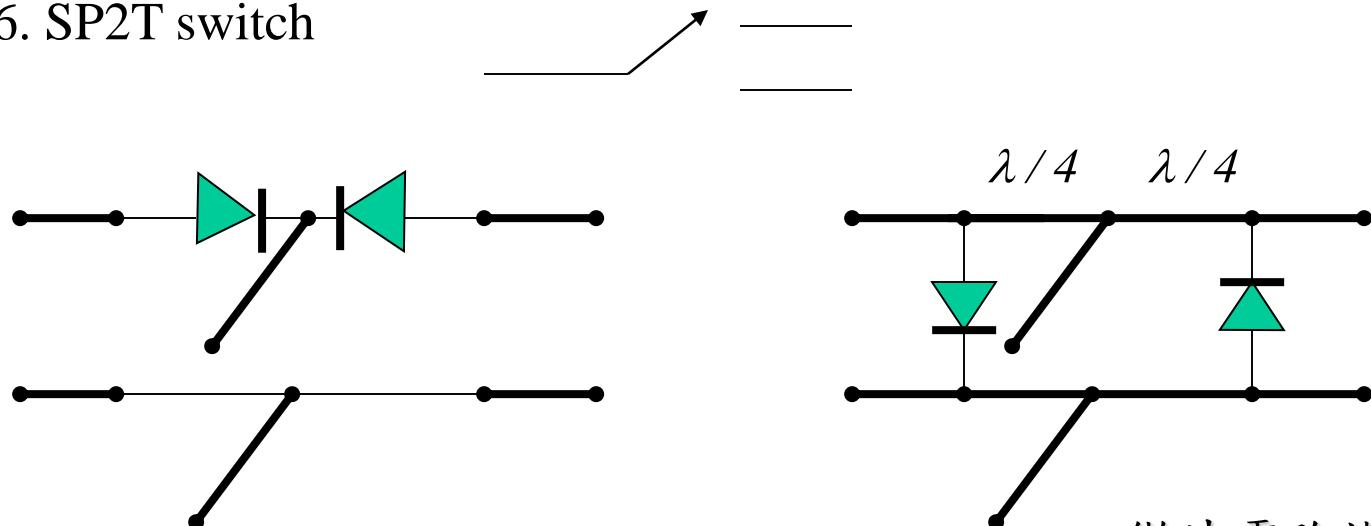


7. switched-line phase shifter

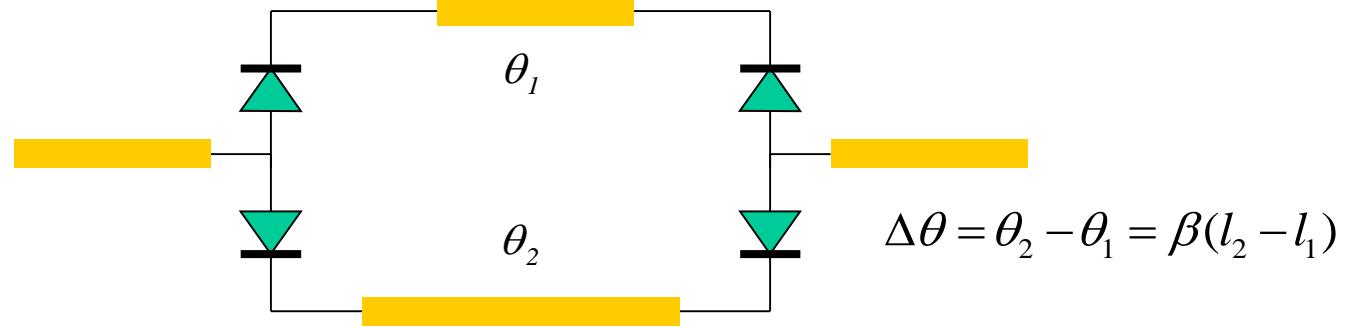

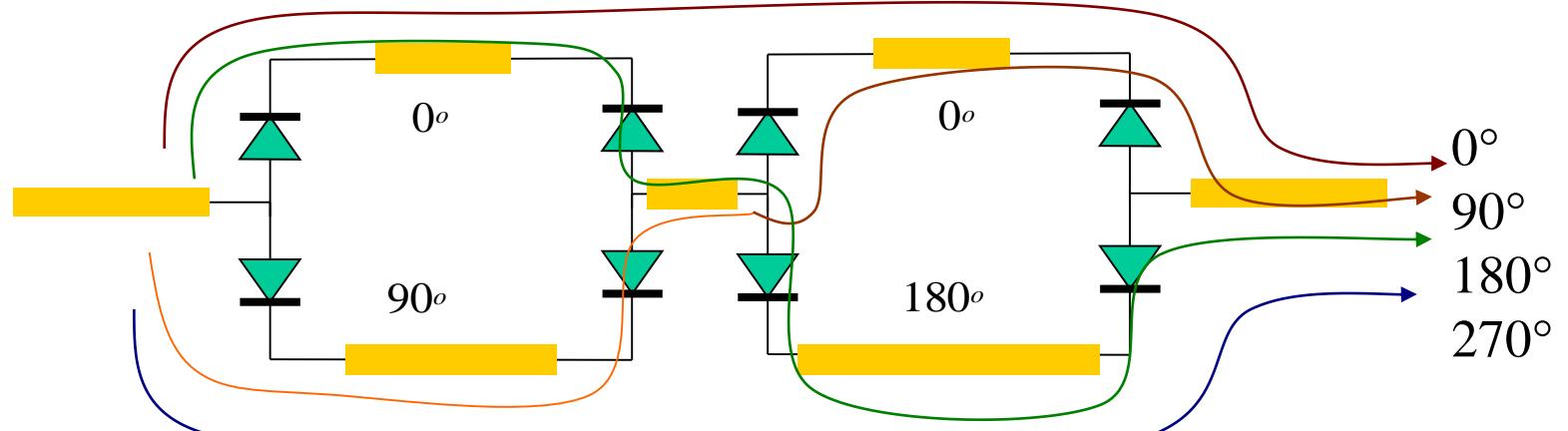
8. 2 bit phase shifter $90^\circ, 180^\circ$

$$2^2=4 \rightarrow 0^\circ, 90^\circ, 180^\circ, 270^\circ$$



3 bit phase shifter $45^\circ, 90^\circ, 180^\circ$

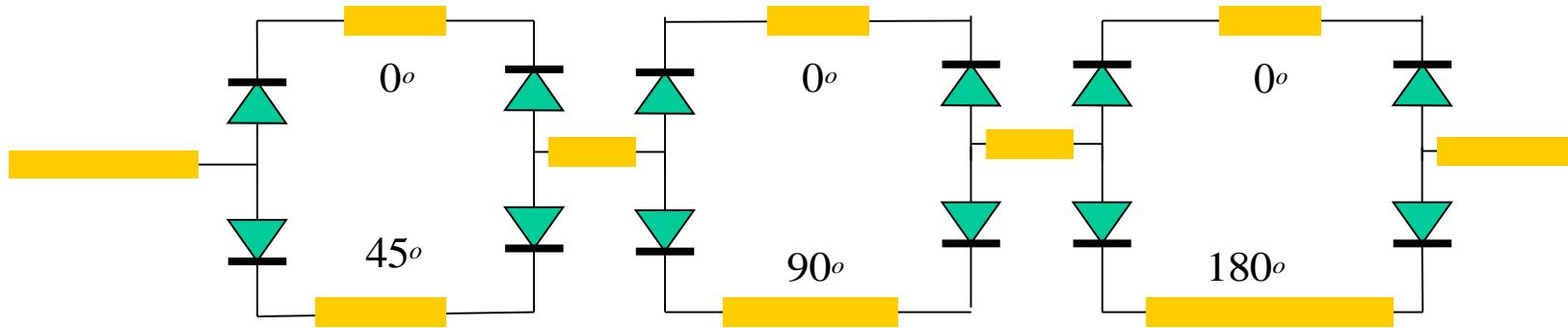
$$2^3=8 \rightarrow 0^\circ, 45^\circ, 90^\circ, 135^\circ, 180^\circ, 225^\circ, 270^\circ, 315^\circ$$



4 bit phase shifter $22.5^\circ, 45^\circ, 90^\circ, 180^\circ$

$$2^4=16 \rightarrow 0^\circ, 22.5^\circ, 45^\circ, 67.5^\circ, 90^\circ, 112.5^\circ, 135^\circ, 157.5^\circ, 180^\circ, 202.5^\circ, 225^\circ, 247.5^\circ, 270^\circ, 292.5^\circ, 315^\circ, 337.5^\circ$$

9. load-line phase shifter

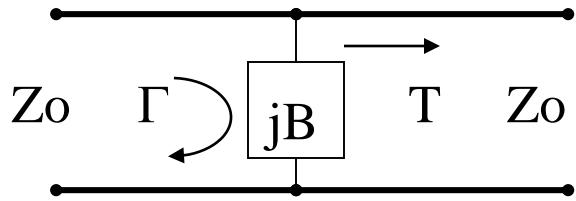


$$\Gamma = \frac{-jb}{2+jb}, T = 1 + \Gamma = \frac{2}{2+jb}$$

$$b = BZ_o, \angle T = -\tan^{-1} \frac{b}{2}$$

(derivation)

$$Z_L = Z_o // \frac{1}{jB} = \frac{1}{\frac{1}{Z_o} + jB} = \frac{Z_o}{1 + jBZ_o}, \frac{Z_L}{Z_o} = \frac{1}{1 + jb}, b = BZ_o$$

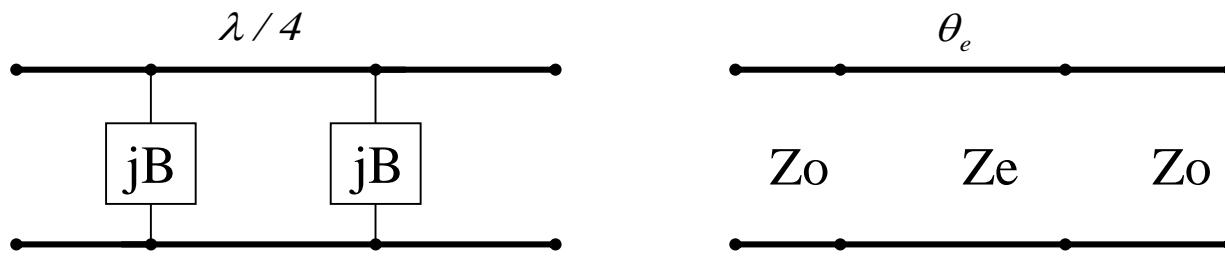
$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{Z_L / Z_o - 1}{Z_L / Z_o + 1} = \frac{\frac{1}{1+jb} - 1}{\frac{1}{1+jb} + 1} = \frac{-jb}{2+jb}$$



$$(\text{left}) \begin{bmatrix} 1 & 0 \\ jB & 0 \end{bmatrix} \begin{bmatrix} 0 & jZ_o \\ \frac{j}{Z_o} & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ jB & 0 \end{bmatrix} = \begin{bmatrix} -BZ_o & jZ_o \\ j\left(\frac{1}{Z_o} - B^2 Z_o\right) & -BZ_o \end{bmatrix}$$

$$(\text{right}) \begin{bmatrix} \cos \theta_e & jZ_e \sin \theta_e \\ \frac{j \sin \theta_e}{Z_e} & \cos \theta_e \end{bmatrix}$$

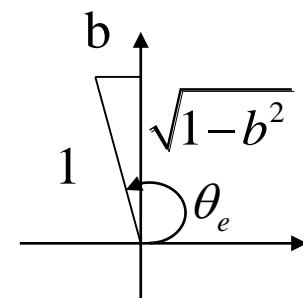
$$\begin{aligned} \cos \theta_e &= -BZ_o \equiv -b & \theta_e &\approx \frac{\pi}{2} + b \\ \Rightarrow Z_e &= \frac{Z_o}{\sin \theta_e} = \frac{Z_o}{\sqrt{1-b^2}} \xrightarrow{\text{small } b} Z_e \approx Z_o \left(1 + \frac{b}{2}\right) \end{aligned}$$



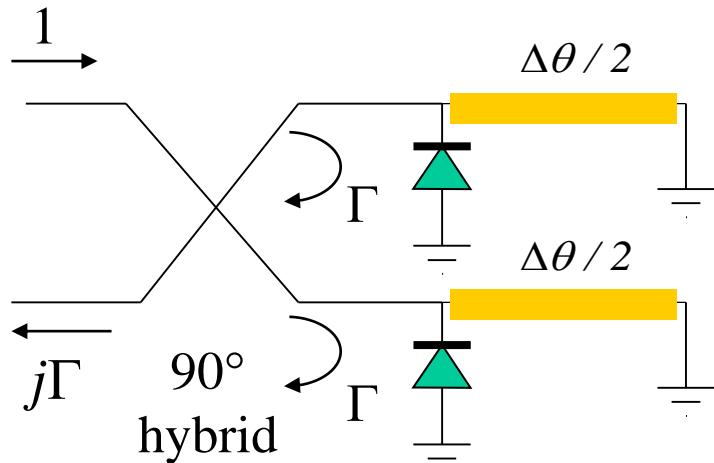10. reflection-type phase shifter



diode ON, $\Gamma = e^{j\theta}$

diode OFF, $\Gamma = e^{j(\theta+\Delta\theta)}$




$$\frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ \frac{1}{\sqrt{2}} \\ \frac{j}{\sqrt{2}} \\ 0 \end{bmatrix}, \quad \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix} \begin{bmatrix} \frac{\Gamma}{\sqrt{2}} \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ j\Gamma \end{bmatrix}$$

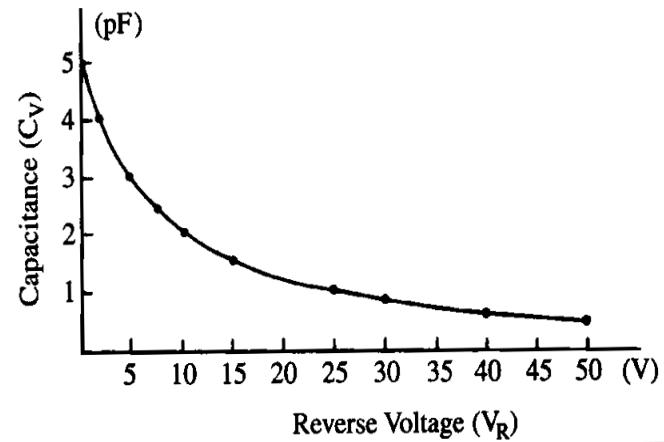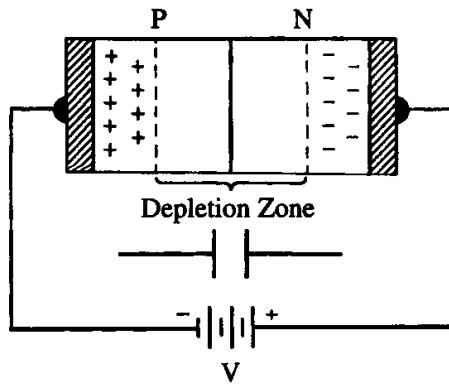11. varactor diode applications: VCO, frequency multiplier





10.2/3 Bipolar junction transistors/Field effect transistors

- microwave FET (depletion type)

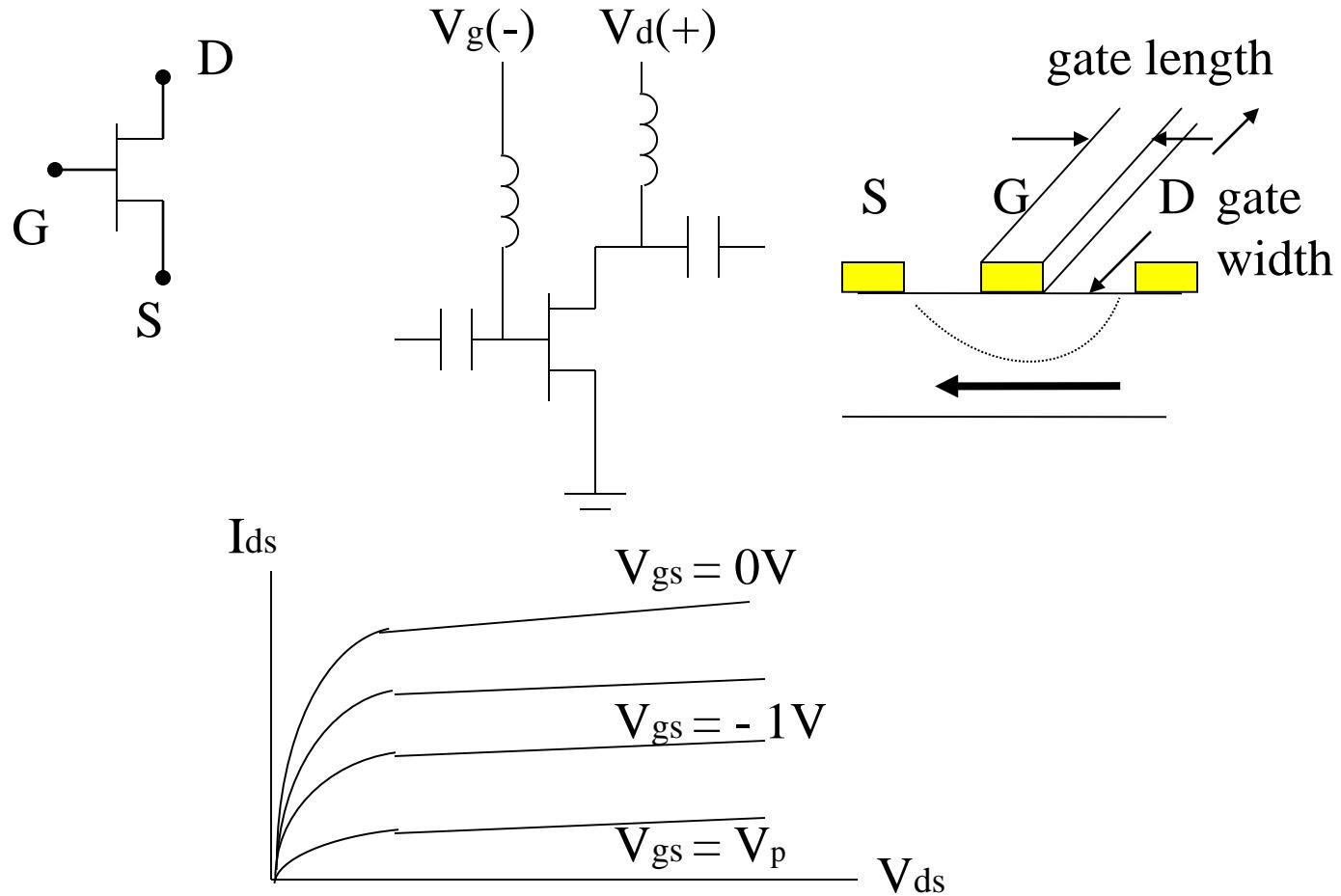

small-signal equivalent circuit

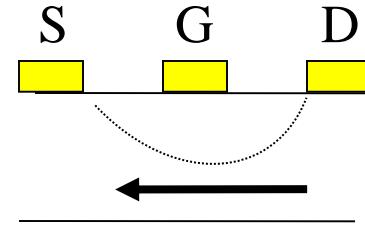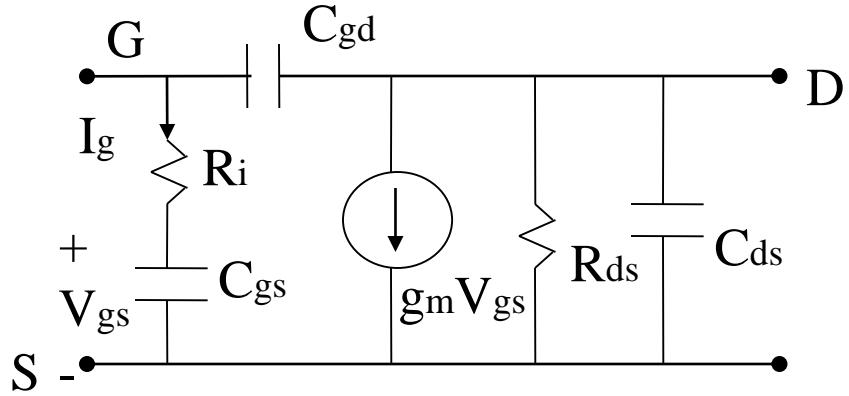

short circuit current gain

gate length $\downarrow \Rightarrow f \uparrow$



gate width $\uparrow \Rightarrow \text{power} \uparrow$

$$G_i^{SC} = \left| \frac{I_d}{I_g} \right| = \left| \frac{g_m V_{gs}}{I_g} \right| = \frac{g_m}{w C_{gs}}$$



$$G_i^{SC} = 1 @ f_T \rightarrow \text{cut off frequency } f_T = \frac{g_m}{2\pi C_{gs}}$$

$S(f, \text{bias}, T, P_{in}, \text{device geometry}, \text{device fabrication}, \dots)$

- microwave BJT

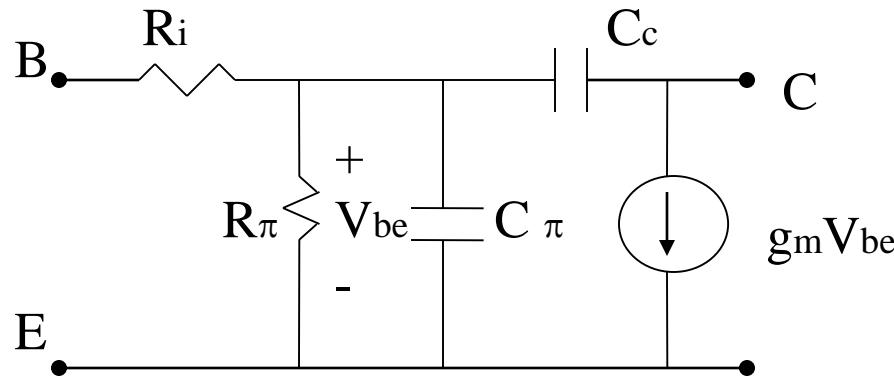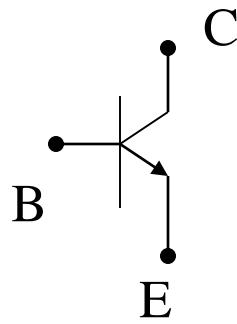

$$f_T = \frac{g_m}{2\pi C_\pi}$$

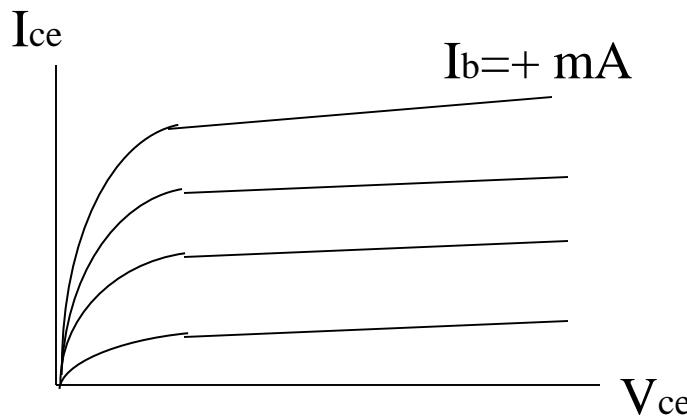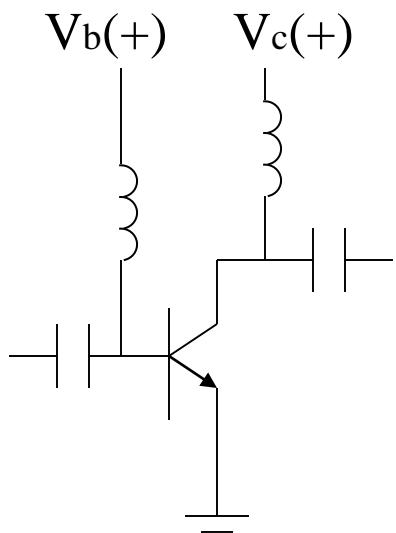

- comparison of microwave transistors

Property	D-mode FET/HEMT	III-V HBT	Si BJT	SiGe HBT	MOSFET
Cost	moderate and decreasing	high and decreasing	low and mature	moderate and decreasing	low to moderate
Single polarity supply	no	yes	yes	yes	yes
Integration capability	excellent (MMIC)	excellent	OK at low	OK at low	OK at low
Parasitic loss	very good	very good	modest	modest	modest
Turn-on voltage control	modest	very good	excellent	excellent	good
PAE	excellent	very good	poor	moderate	very good

10.5 Microwave integrated circuits

Discussion

1. HMIC (Fig. 11.25)

MMIC (Figs. 11.26 and 11.27)

2.

Feature	MMIC	HMIC
substrate	semi-insulator	insulator
interconnections	deposited	wire-bonded / deposited
distributed elements	microstrip, CPW	microstrip, CPW
lumped elements	deposited	discrete/deposited
solid state device	deposited	discrete
controlled parasitics	Yes	No
labor intensive	No	Yes
reparability	No	Yes
equipment costs	high	low

Feature	MMIC	HMIC
mass production	Yes	No
debugging	difficult	easy
integrated with digital and electrooptic ICs	possible	impossible
cost	low	high
size and weight	small	large
design flexibility	very good	good
circuit tweaking	impractical	practical
broadband performance	relatively good	limited
reproducibility	excellent	good
reliability	excellent	good

11.5 Microwave tubes

Discussion

1. Solid-state sources operate at lower power and lower frequency, while microwave tubes operate at higher power and higher frequency (p.553, Fig.11.28).
2. Solid-state sources use diode circuitss (Gunn diode, IMPATT diode) or transistor circuits (GaAs MESFET, DRO, YIG oscillator) with power combining circuits for higher output power (p.539).
3. Microwave tubes
 - power-frequency for oscillator tubes (p.555, Fig. 11.29)
 - power-frequency for amplifier tubes (p.556, Fig. 11.30)