

Microwave Review Quiz #1 Solution 2016.10.11


1. A lossless transmission line with a characteristic impedance of $Z_o = 75\Omega$ supports a forward-traveling wave with an average power of 0dBm. The line is terminated in a resistance of 100Ω .

(1) Plot the lumped-element equivalent circuit at the interface between the transmission line and the load.

(2) Calculate the reflection coefficient Γ_L , V_L^+ , V_L^- , V_L and average power P_L at the load.

(3) If the lossless transmission line has a length of $\lambda/4$, calculate the reflection coefficient Γ_{in} , V_{in}^+ , V_{in}^- , V_{in} and average power P_{in} at the input of transmission line.

(1)

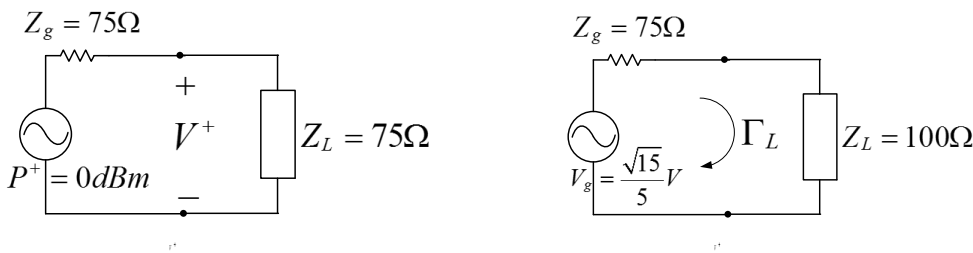

$$P_{inc} = \frac{1}{2} \frac{|V^+|^2}{Z_g} = 0dBm = 1mW = \frac{1}{2} \frac{|V^+|^2}{75} \rightarrow |V^+| = V^+ = \sqrt{150 \times 10^{-3}} = \frac{\sqrt{15}}{10} V \rightarrow V_g = 2V^+ = \frac{\sqrt{15}}{5} V$$

(2)


$$\Gamma_L = \frac{Z_L - Z_g}{Z_L + Z_g} = \frac{100 - 75}{100 + 75} = \frac{1}{7}$$

$$V_L = V_g \frac{Z_L}{Z_L + Z_g} = \frac{\sqrt{15}}{5} \frac{100}{100 + 75} = \frac{4\sqrt{15}}{35} V = V_L^+ + V_L^- = V_L^+ (1 + \Gamma_L) = V_L^+ \frac{8}{7} \rightarrow V_L^+ = \frac{\sqrt{15}}{10} V$$

$$V_L^- = V_L^+ \Gamma_L = \frac{\sqrt{15}}{10} \times \frac{1}{7} = \frac{\sqrt{15}}{70} V, V_L^+ + V_L^- = \frac{\sqrt{15}}{10} + \frac{\sqrt{15}}{70} = \frac{4\sqrt{15}}{35} V = V_L$$

$$P_{refl} = P_{inc} |\Gamma_L|^2 = 1 \times \left(\frac{1}{7}\right)^2 = \frac{1}{49} mW, P_L = P_{inc} - P_{refl} = 1 - \frac{1}{49} = \frac{48}{49} mW = \frac{1}{2} \frac{V_L^2}{Z_L} = \frac{1}{2} \frac{\left(\frac{4\sqrt{15}}{35}\right)^2}{100} \times 1000 = \frac{48}{49}$$

(3)

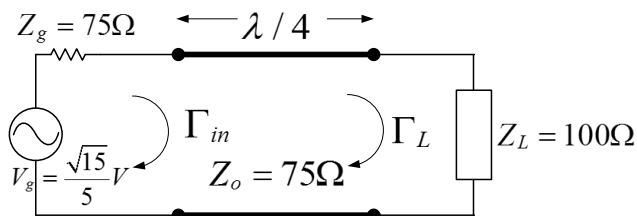

$$\Gamma_{in} = \Gamma_L e^{-2j\beta l} = \Gamma_L e^{-2j \frac{2\pi\lambda}{\lambda} \frac{\lambda}{4}} = \Gamma_L e^{-j\pi} = -\Gamma_L = -\frac{1}{7}$$

$$Z_{in} = \frac{Z_o^2}{Z_L} = \frac{75^2}{100} = \frac{225}{4}, V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} = \frac{\frac{225}{4}}{75 + \frac{225}{4}} = \frac{\sqrt{15} \cdot 225}{5 \cdot 525} = \frac{3\sqrt{15}}{35} V = V_{in}^+ + V_{in}^- = V_{in}^+ (1 + \Gamma_{in}) = V_{in}^+ \frac{6}{7}$$

$$\rightarrow V_{in}^+ = \frac{\sqrt{15}}{10} V$$

$$V_{in}^- = V_{in}^+ \Gamma_{in} = \frac{\sqrt{15}}{10} \times \left(-\frac{1}{7}\right) = -\frac{\sqrt{15}}{70} V, V_{in}^+ + V_{in}^- = \frac{\sqrt{15}}{10} - \frac{\sqrt{15}}{70} = \frac{3\sqrt{15}}{35} = V_{in}$$

$$P_{refl} = P_{inc} |\Gamma_{in}|^2 = 1 \times \left(\frac{1}{7}\right)^2 = \frac{1}{49} mW, P_{in} = P_{inc} - P_{refl} = 1 - \frac{1}{49} = \frac{48}{49} mW = \frac{1}{2} \frac{V_{in}^2}{Z_{in}} = \frac{1}{2} \frac{\left(\frac{3\sqrt{15}}{35}\right)^2}{\frac{225}{4}} \times 1000 = \frac{48}{49} mW$$