


## Microwave Review Quiz #3 solution 2016.10.25

1. Write down the scattering parameter of a 10dB attenuator circuit and its signal flow graph. The characteristic impedance for port 1 and port 2 is the same given as  $Z_o$ . Is it a lossy (lossless or lossy), reciprocal (reciprocal or non-reciprocal), symmetrical (symmetrical or non-symmetrical), and matched (matched or non-matched) circuit?


$$S_{11} = 0, S_{22} = 0 \rightarrow V_1 = V_1^+ + V_1^- (= 0), V_2 = V_2^+ (= 0) + V_2^-$$

$$P_{inc} = \frac{1}{2} \frac{|V_1^+|^2}{Z_o}, P_L = \frac{1}{10} P_{inc} = \frac{1}{10} \frac{1}{2} \frac{|V_1^+|^2}{Z_o} = \frac{1}{2} \frac{|V_2^-|^2}{Z_o} \rightarrow V_2^- = \frac{1}{\sqrt{10}} V_1^+$$
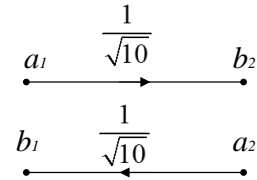
$$\rightarrow S_{21} = \frac{1}{\sqrt{10}} = S_{12} \Rightarrow [S] = \begin{bmatrix} 0 & \frac{1}{\sqrt{10}} \\ \frac{1}{\sqrt{10}} & 0 \end{bmatrix}$$



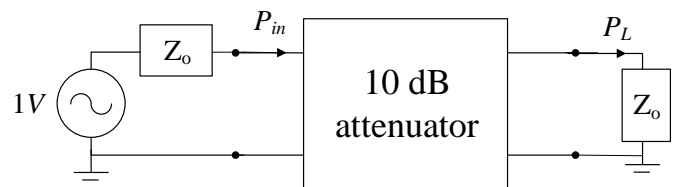
2. Given this attenuator is connected as shown in the right figure with  $Z_o = 50\Omega$ . Plot the signal flow diagram, then calculate  $P_{in}$  and  $P_L$ .





The expression of  $a_s$  uses the source representation given in slide (4-36) and the 10dB attenuator uses the result given in question 1.

### Discussion

#### 1. Source representation

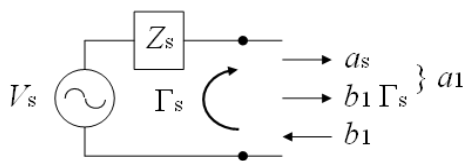

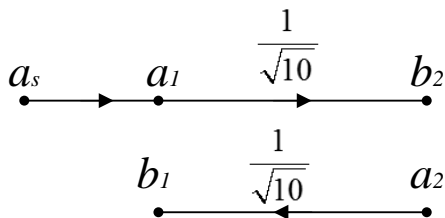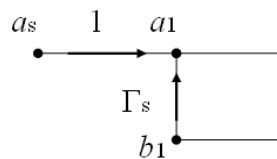
$$e_s = V_s \frac{Z_o}{Z_o + Z_s}, a_s \equiv \frac{e_s}{\sqrt{Z_o}}$$



$$a_s = \frac{e_s}{\sqrt{Z_o}} = \frac{1}{\sqrt{Z_o}} V_s \frac{Z_o}{Z_o + Z_s} = \frac{1}{\sqrt{50}} \frac{1}{2} = \frac{1}{10\sqrt{2}} V$$

$$a_1 = a_s \rightarrow P_{in} = \frac{1}{2} |a_1|^2 = \frac{1}{2} \frac{1}{200} = \frac{1}{400} W = \frac{5}{2} mW = 3.98 dBm$$

$$b_2 = \frac{1}{\sqrt{10}} a_1 \rightarrow P_L = \frac{1}{2} |b_2|^2 = \frac{1}{10} \frac{1}{2} |a_1|^2 = \frac{1}{10} P_{in} = \frac{1}{4} mW = -6.02 dBm$$

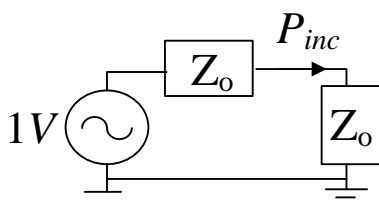

$$P_{inc} = \frac{1}{2} \frac{|V_1^+|^2}{Z_o} = \frac{1}{2} \frac{|V_g / 2|^2}{Z_o} = \frac{1}{2} \frac{|1/2|^2}{50} = \frac{1}{400} W = \frac{5}{2} mW = 3.98 dBm$$