

Microwave Review Quiz #4 solution 2016.12.20

1. As shown in Fig.1 (a), it is a linear and symmetric four-port network. One can then get its S-matrix by using the superposition of the S-matrixes of two-port even and odd networks as shown in Fig.1 (b) and Fig.1 (c). The input signal of Fig.1 (a) is a_1 at port 1.

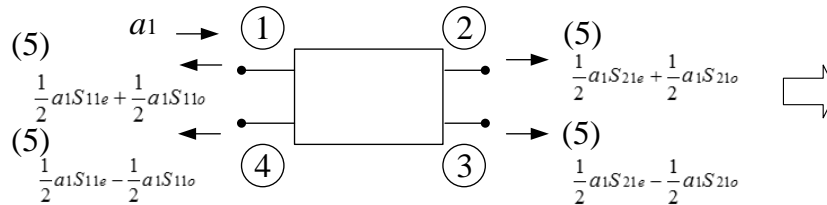


Fig.1 (a)

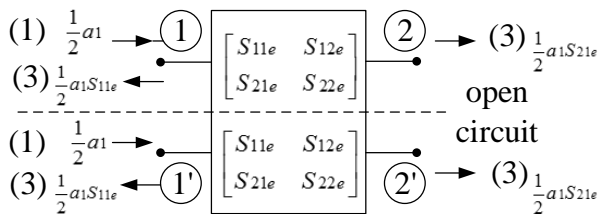


Fig.1 (b)


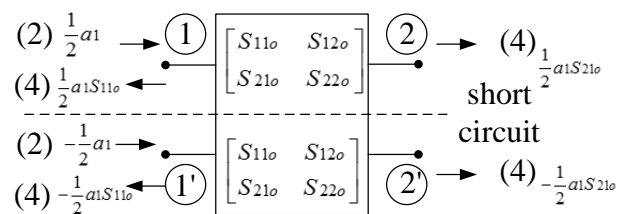



Fig.1 (c)

- (1) Give the excitation at ports 1 and 1' of an even-mode two-port network as $\frac{a_1}{2}$ and $\frac{a_1}{2}$.
- (2) Give the excitation at ports 1 and 1' of an odd-mode two-port network as $\frac{a_1}{2}$ and $-\frac{a_1}{2}$.
- (3) Give the responses at ports 1, 1', 2, and 2' of an even-mode two-port network as $\frac{a_1}{2} S_{11e}$, $\frac{a_1}{2} S_{11e}$, $\frac{a_1}{2} S_{21e}$, and $\frac{a_1}{2} S_{21e}$.
- (4) Give the responses at ports 1, 1', 2, and 2' of an odd-mode two-port network as $\frac{a_1}{2} S_{11o}$, $-\frac{a_1}{2} S_{11o}$, $\frac{a_1}{2} S_{21o}$, and $-\frac{a_1}{2} S_{21o}$.
- (5) Get the responses at ports 1, 2, 3, and 4 of the four-port network as $\frac{a_1}{2} (S_{11e} + S_{11o})$, $\frac{a_1}{2} (S_{21e} + S_{21o})$, $\frac{a_1}{2} (S_{21e} - S_{21o})$, and $\frac{a_1}{2} (S_{11e} - S_{11o})$.

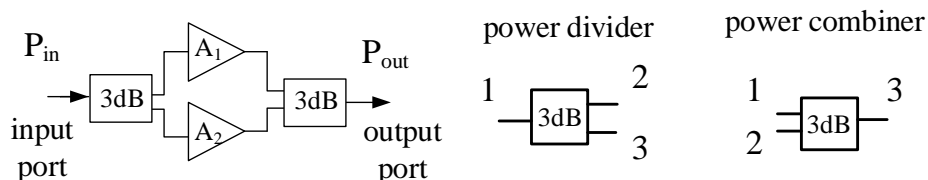
2. A power amplifier as shown in Fig.2 (a) with $P_{in}=1W$ includes two 3dB power dividers, two 3dB power combiners and two amplifiers. Each 3dB coupler is a Wilkinson coupler. Two amplifiers $A_1 \sim A_2$ are identical with 10dB power gain and $-\infty$ dB return loss for input port and output port.



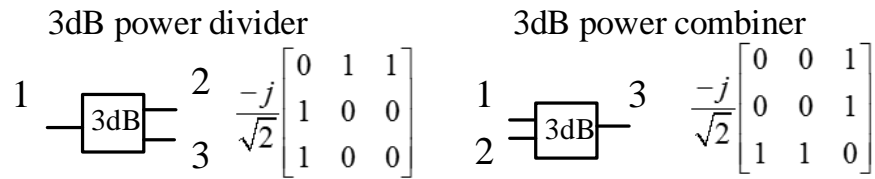- (1) Give the S-matrixes $\frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}$ and $\frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$ as a 3dB power divider and a 3dB power combiner as shown in Fig.2 (b).



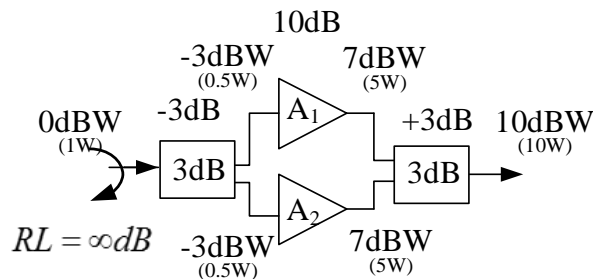
- (2) Give the input RL, output power and power gain ∞dB, 10dBW(10W) and 10dB of the power amplifier.



- (3) Give the input RL, output power and power gain 6dB, 4dBW(2.5W) and 4dB of the power amplifier as the amplifier A₁ fails as a short circuit.

Only the port 2 of the 3dB power divider gets an input signal at port 2 from a total reflection caused from a shorted amplifier A₁. The 3dB power divider then becomes as a power combiner. Its input signal is at port 1 to calculate the output signal to calculate the input RL (return loss).

$$\frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} a \\ 0 \\ 0 \end{bmatrix} = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 \\ 0 \\ a \end{bmatrix} \rightarrow \text{output power at port 3: } \frac{1}{2} \left| \frac{-j}{\sqrt{2}} a \right|^2 = \frac{1}{4} |a|^2 \text{ is a half of the input power.}$$

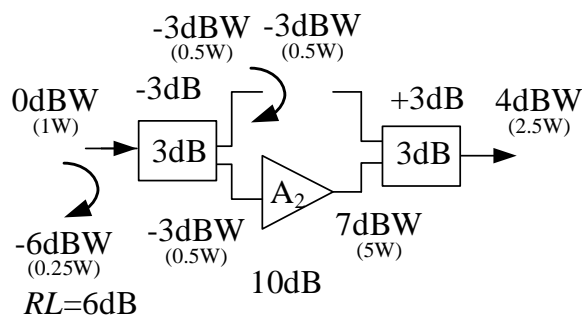

The input signal of the 3dB power combiner is only at port 2 to calculate the output signal.

$$\frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ a \\ 0 \end{bmatrix} = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 \\ 0 \\ a \end{bmatrix} \rightarrow \text{output power at port 3: } \frac{1}{2} \left| \frac{-j}{\sqrt{2}} a \right|^2 = \frac{1}{4} |a|^2 \text{ is a half of the input power.}$$