

Microwave Review Quiz #5 Solution 2016.12.27

1. Design a microstrip stepped impedance LPF as the example 8.6 in p.424~426 by using the ladder circuit given in Fig. 8.25(b) instead of that in Fig. 8.25(a).

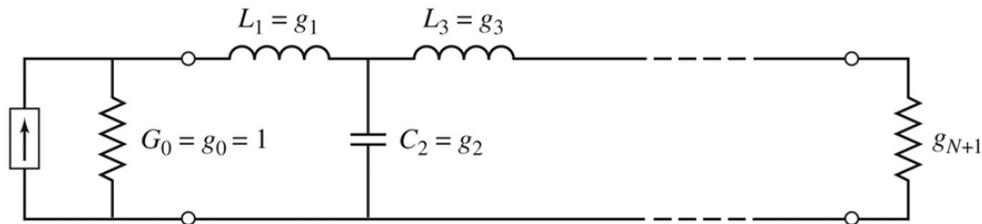


Fig. 8.25(b)

- (1) Give Fig. 8.26 to give the number of elements $N = \underline{6}$ for $\frac{\omega}{\omega_c} - 1 = \underline{0.6}$.
- (2) Give the low-pass prototype values $g_1 = \underline{0.517}$, $g_2 = \underline{1.414}$, $g_3 = \underline{1.932}$, $g_4 = \underline{1.932}$, $g_5 = \underline{1.414}$, $g_6 = \underline{0.517}$.
- (3) Give the low-pass prototype elements with unit $L_1 = \underline{0.517H}$, $C_2 = \underline{1.414F}$, $L_3 = \underline{1.932H}$, $C_4 = \underline{1.932F}$, $L_5 = \underline{1.414F}$, $C_6 = \underline{0.517F}$, and $\omega_c = \underline{1rad/sec}$.
- (4) Give the equations to calculate the impedance and frequency scaling for inductance $L' = \frac{R_o L}{\omega_c}$ and capacitance $C' = \frac{C}{R_o \omega_c}$, then give the equations of the impedance of high line impedance of L' as $j\omega_c L' = \underline{jZ_h \beta_{l_h}}$ and the impedance of low line impedance of C' as $\frac{1}{j\omega_c C'} = \underline{\frac{Z_l}{j\beta_{l_l}}}$.
- (5) Give the electrical lengths in terms of high and low line impedances of Z_h and Z_l as $\beta_{l_h} = \frac{\omega_c L'}{Z_h} = \frac{\omega_c R_o L}{Z_h} = \frac{R_o L}{Z_h}$ and $\beta_{l_l} = Z_l \omega_c C' = Z_l \omega_c \frac{C}{R_o \omega_c} = \frac{Z_l C}{R_o}$, where β_{l_l} and $\beta_{l_h} < \underline{45^\circ}$.
- (6) Give the electrical lengths of low-pass filter elements as $\beta_{l_{h,1}} = \frac{50 \times 0.517}{120} \frac{180}{\pi} = 12.3^\circ$,
 $\beta_{l_{l,2}} = \frac{20 \times 1.414}{50} \frac{180}{\pi} = 32.4^\circ$, $\beta_{l_{h,3}} = \frac{50 \times 1.932}{120} \frac{180}{\pi} = 46.1^\circ$, $\beta_{l_{l,4}} = \frac{20 \times 1.932}{50} \frac{180}{\pi} = 44.3^\circ$,
 $\beta_{l_{h,5}} = \frac{50 \times 1.414}{120} \frac{180}{\pi} = 33.8^\circ$, $\beta_{l_{l,6}} = \frac{20 \times 0.517}{50} \frac{180}{\pi} = 11.8^\circ$.
- (7) The results of lumped LPF, step-impedance LPF given in Fig. 8.25 (a) and Fig. 8.25 (b) are Y.

Simulation Results: The ports of LPF in this ADS simulation are given as the following table.

ports 1 and 2	lumped LPF in Ex. 8.6
ports 3 and 4	step-impedance LPF in Ex. 8.6
ports 5 and 6	lumped LPF in this examination
ports 7 and 8	step-impedance LPF in this examination

WAR
Z0=50
fc=2.5e9

S-PARAMETERS
S Param
SP1
Start=1 Hz
Stop=(1%) Hz

