

Chapter 4 Resonant circuits

4.1 Series resonant circuits

steady state response, Q factor, half power frequencies, input impedance,

4.2 Parallel resonant circuits

steady state response, input impedance, loaded Q, external Q

4.3 Transformer coupled circuits

equivalent resonator circuit

4.4 Transmission line resonant circuits

short-circuited $\lambda/2$ and $\lambda/4$ lines, open-circuited $\lambda/2$ and $\lambda/4$ lines

4.5 Microwave resonators


rectangular cavity, circular cylindrical cavity, dielectric resonator

4.1 Series resonant circuits

Basics

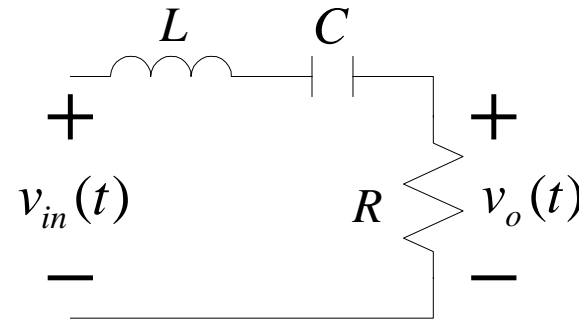1. Resonator applications: filter, frequency selective components in amplifier and oscillator, impedance transformer, matching element.
2. Steady state response

$$\begin{aligned}
 A(j\omega) &= \frac{V_o(j\omega)}{V_{in}(j\omega)} \\
 &= \frac{R}{j\omega L + \frac{1}{j\omega C} + R} = \frac{1}{\frac{j\omega L}{R} + \frac{1}{j\omega RC} + 1} \\
 &= \frac{1}{\frac{j}{RC} \left(LC\omega - \frac{1}{\omega} \right) + 1} = \frac{1}{\frac{j}{RC} \left(\frac{\omega}{\omega_o^2} - \frac{1}{\omega} \right) + 1} = \frac{1}{1 + \frac{j}{\omega_o RC} \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)} = \frac{1}{1 + jQ \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)}
 \end{aligned}$$



$$\text{resonant frequency } \omega_o \equiv \frac{1}{\sqrt{LC}}$$

$$\text{quality factor } Q \equiv \omega_o \frac{\text{average stored energy}}{\text{power loss}} = \omega_o \frac{W_m + W_e}{P_{loss}} = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC}$$

$$P_{loss} = \frac{1}{2} |I|^2 R, W_m = \frac{1}{4} |I|^2 L, W_e = \frac{1}{4} |V_c|^2 C = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C}$$

3. Half power frequencies $Q = \frac{\omega_o}{\omega_2 - \omega_1}$

4. Input impedance near resonance

$$Z_{in}(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\omega L \left(1 - \frac{\omega_o^2}{\omega^2}\right) = R + j\omega L \frac{(\omega + \omega_o)(\omega - \omega_o)}{\omega^2}$$

$$\approx R + j2\delta\omega L$$



$$(1) = R + \frac{j2RQ\delta\omega}{\omega_o}$$

$$(2) = \omega_o \frac{L}{Q} + j2(\omega - \omega_o)L = j2\left(\omega - \omega_o + \frac{\omega_o}{j2Q}\right)L$$

$$= j2\left[\omega - \omega_o \left(1 + j\frac{1}{2Q}\right)\right]L$$

Lossy resonator Z_{in}

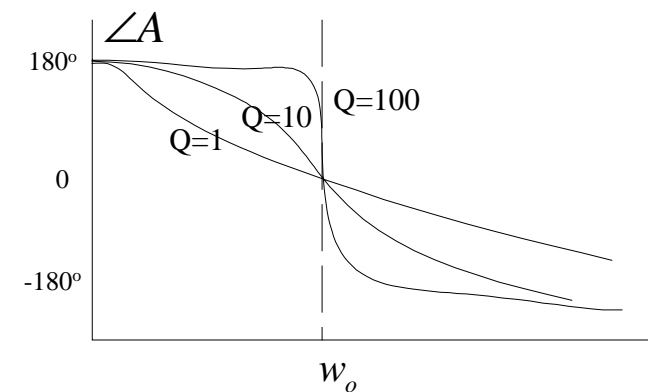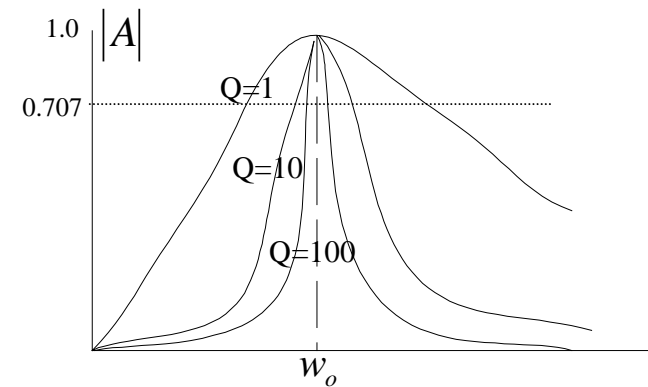= lossless resonator Z_{in} by letting $\omega_o \rightarrow \omega_o \left(1 + j\frac{1}{2Q}\right)$



Discussion

1. Derivation of half power frequencies equation $Q = \frac{w_o}{w_2 - w_1}$

$$\because A(jw) = \frac{V_o(jw)}{V_{in}(jw)} = \frac{1}{1 + jQ\left(\frac{w}{w_o} - \frac{w_o}{w}\right)}$$

$$\frac{1}{2} = \frac{1}{1 + Q^2\left(\frac{w}{w_o} - \frac{w_o}{w}\right)^2} \rightarrow 2 = 1 + Q^2\left(\frac{w}{w_o} - \frac{w_o}{w}\right)^2 \rightarrow Q\left(\frac{w}{w_o} - \frac{w_o}{w}\right) = \pm 1 \dots (1)$$

$$\rightarrow \frac{w_2}{w_o} - \frac{w_o}{w_2} = -\left(\frac{w_1}{w_o} - \frac{w_o}{w_1}\right) \rightarrow w_2 - \frac{w_o^2}{w_2} = -w_1 + \frac{w_o^2}{w_1} \rightarrow w_1 + w_2 = w_o^2\left(\frac{1}{w_1} + \frac{1}{w_2}\right)$$

$$\rightarrow w_1 w_2 = w_o^2 \dots (2)$$


$$(1) \rightarrow \frac{w_1}{w_o} - \frac{w_o}{w_1} = -\frac{1}{Q} \rightarrow w_1 - \frac{w_o^2}{w_1} = -\frac{w_o}{Q} \xrightarrow{(2)} w_1 - w_2 = -\frac{w_o}{Q} \rightarrow Q = \frac{w_o}{w_2 - w_1}$$

2. $Z_{in}(j\omega) = R + jX$, and $R = X$ at half power frequencies

$$Z_{in}(j\omega_1) = R + j\omega_1 L \frac{\omega_1^2 - \omega_o^2}{\omega_1^2}$$

$$\frac{1}{Q} = \frac{\omega_1^2 - \omega_o^2}{\omega_o \omega_1} \rightarrow Z_{in}(j\omega_1) = R + j \frac{\omega_o L}{Q}$$
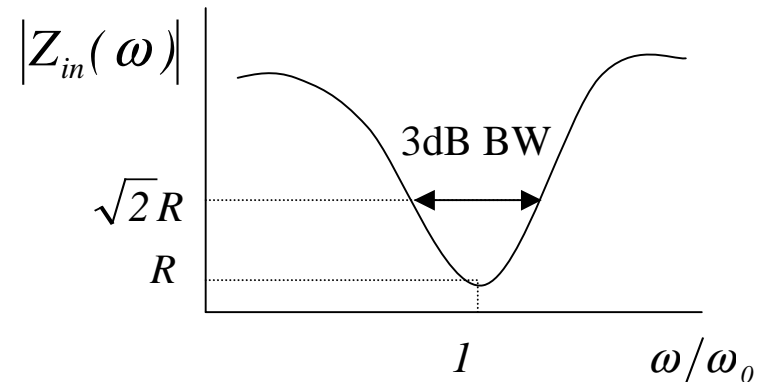
$$Q = \omega_o \frac{L}{R} \rightarrow R + jR$$



3. Ex.4.1 A series LC circuit passes signals from 9MHz to 11MHz, and is connected to a communication system with $Z_{in} = 50 \Omega$. $\rightarrow L, C$

$$f_o = \sqrt{f_1 f_2} = \sqrt{9 \times 11} = 9.5 \text{ MHz}$$

$$Q = \frac{\omega_o}{\omega_2 - \omega_1} = \frac{\omega_o L}{R} \rightarrow L = \frac{R}{\omega_2 - \omega_1} = \frac{50}{2\pi \times (11 - 9) \times 10^6} = 4 \mu\text{H}$$


$$C = \frac{1}{L\omega_o^2} = 64.3 \text{ pF}$$

4.2 Parallel resonant circuits

Basics

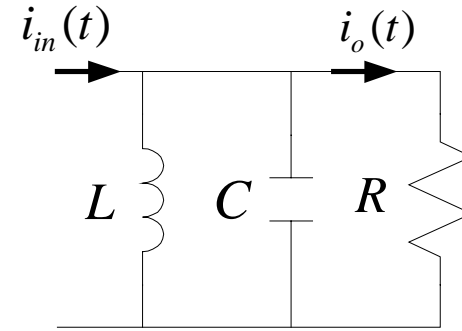1. Duality with series resonator: $V \rightarrow I$, $R \rightarrow G$, $L \rightarrow C$, $C \rightarrow L$
2. Steady state response

$$\begin{aligned}
 A(j\omega) &= \frac{I_o(j\omega)}{I_{in}(j\omega)} \\
 &= \frac{1/R}{j\omega C + \frac{1}{j\omega L} + \frac{1}{R}} = \frac{1}{j\omega RC + \frac{R}{j\omega L} + 1} \\
 &= \frac{1}{\frac{jR}{L}(LC\omega - \frac{1}{\omega}) + 1} = \frac{1}{\frac{jR}{L}(\frac{\omega}{\omega_o^2} - \frac{1}{\omega}) + 1} = \frac{1}{1 + \frac{jR}{\omega_o L}(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega})} = \frac{1}{1 + jQ(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega})}
 \end{aligned}$$



resonant frequency $\omega_o \equiv \frac{1}{\sqrt{LC}}$

quality factor $Q \equiv \omega_o \frac{W_m + W_e}{P_{loss}} = \frac{R}{\omega_o L} = \omega_o RC$

$$P_{loss} = \frac{1}{2} \frac{|V|^2}{R}, W_m = \frac{1}{4} |I_L|^2 L = \frac{1}{4} \frac{|V|^2}{\omega^2 L}, W_e = \frac{1}{4} |V|^2 C$$

3. Input impedance near resonance

$$Z_{in}(j\omega) = \left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right)^{-1} = \left[\frac{1}{R} + j\omega C \left(1 - \frac{\omega_o^2}{\omega^2} \right) \right]^{-1} = \left[\frac{1}{R} + j\omega C \frac{(\omega + \omega_o)(\omega - \omega_o)}{\omega^2} \right]^{-1}$$

$$\approx \left(\frac{1}{R} + j2\delta\omega C \right)^{-1}$$

$$(1) = \left(\frac{1}{R} + \frac{j2Q\delta\omega}{R\omega_o} \right)^{-1}$$

$$(2) = \left[\frac{\omega_o C}{Q} + j2(\omega - \omega_o)C \right]^{-1} = \left[j2(\omega - \omega_o) + \frac{C}{j2Q} \right]^{-1}$$

$$= \left\{ j2 \left[\omega - \omega_o \left(1 + j \frac{1}{2Q} \right) \right] C \right\}^{-1}$$

Lossy resonator Z_{in} = lossless resonator Z_{in} by letting $\omega_o \rightarrow \omega_o \left(1 + j \frac{1}{2Q} \right)$


Discussion

1. $Y_{in}(j\omega) = G + jB$, and $G = B$ at half power frequencies


$$Z_{in}(j\omega_1) = \left(\frac{1}{R} + j\omega_1 C \frac{\omega_1^2 - \omega_o^2}{\omega_1^2} \right)^{-1}$$

$$\frac{1}{Q} = \frac{\omega_1^2 - \omega_o^2}{\omega_o \omega_1} \rightarrow Z_{in}(j\omega_1) = \left(\frac{1}{R} + j \frac{\omega_o C}{Q} \right)^{-1}$$
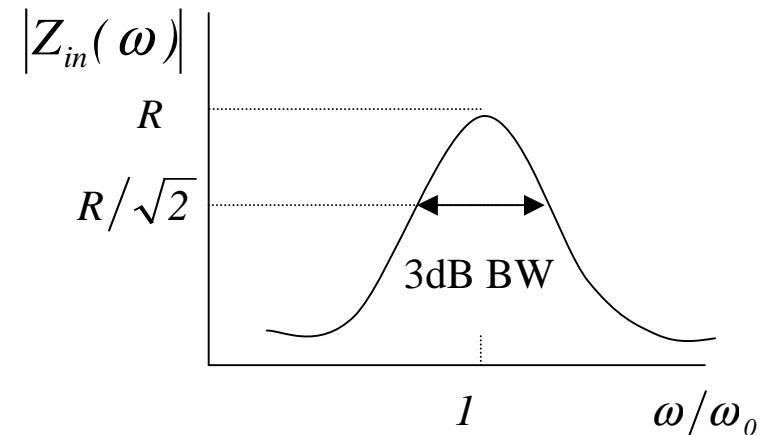
$$Q = \omega_o RC \rightarrow Z_{in}(j\omega_1) = \frac{R}{1 + j}$$



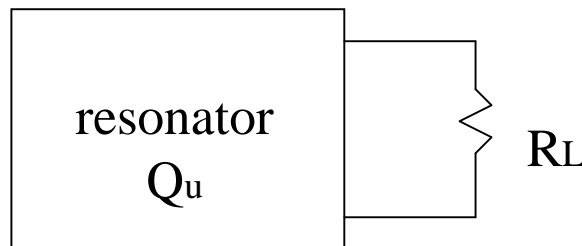2. Unloaded Q , Q_u , loaded Q , Q_L , external Q , Q_e



$$\frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q_u}$$

$$Q_e = \begin{cases} \frac{\omega_o L}{R_L} & \text{for series resonant circuit} \\ \frac{R_L}{\omega_o L} & \text{for parallel resonant circuit} \end{cases}$$

3. Resonator relations

	Series resonator	Parallel resonator
Z_{in}	$R + j\omega L + \frac{1}{j\omega C} \approx R + j2\delta\omega L$ $\approx R + j\frac{2RQ\delta\omega}{\omega_0}$	$\left(\frac{1}{R} + j\omega C + \frac{1}{j\omega L}\right)^{-1} \approx \left(\frac{1}{R} + j2\delta\omega C\right)^{-1}$ $\approx \left(\frac{1}{R} + j\frac{2Q\delta\omega}{R\omega_0}\right)^{-1}$
ω_0	$\frac{1}{\sqrt{LC}}$	
Q_u	$\frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$	$\omega_0 RC = \frac{R}{\omega_0 L}$
Q_e	$\frac{\omega_0 L}{R_L}$	$\frac{R_L}{\omega_0 L}$
Q_L	$\frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q_u}$	

4. Ex.4.2 A parallel resonator with $R=10\text{k}\Omega$, $L=10\mu\text{H}$, $C=10\text{pF}$ and its load $R_L=100\text{k}\Omega \rightarrow \omega_o, Q_u, Q_L$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-5} \times 10^{-11}}} = 10^8 \text{ rad/sec}$$

$$Q_u = \frac{R}{\omega_o L} = \frac{10^5}{10^8 \times 10^{-5}} = 100, Q_e = \frac{R_L}{\omega_o L} = 100, Q_L = 50$$

4.3 Transformer-coupled circuits

Basics

1. Equivalent circuit

$$V_1 = nV_2, I_1 = -\frac{I_2}{n}$$


$$\begin{cases} V_1 = j\omega L_1 I_1 + j\omega M I_2 \\ V_2 = j\omega M I_1 + j\omega L_2 I_2 \end{cases}$$

$$\begin{cases} V_1 = j\omega(1-\xi)L_1 I_1 + j\omega \xi L_1 (I_1 + \frac{I_2}{n}) = j\omega L_1 I_1 + j\omega \xi L_1 \frac{I_2}{n} \\ V_2 = \frac{1}{n} j\omega \xi L_1 (I_1 + \frac{I_2}{n}) \end{cases}$$

$$\rightarrow \frac{\xi L_1}{n} = M, \frac{\xi L_1}{n^2} = L_2$$

$$\rightarrow n = \sqrt{\frac{\xi L_1}{L_2}}, \xi = \frac{nM}{L_1} = \frac{M \sqrt{\xi}}{\sqrt{L_1 L_2}}$$
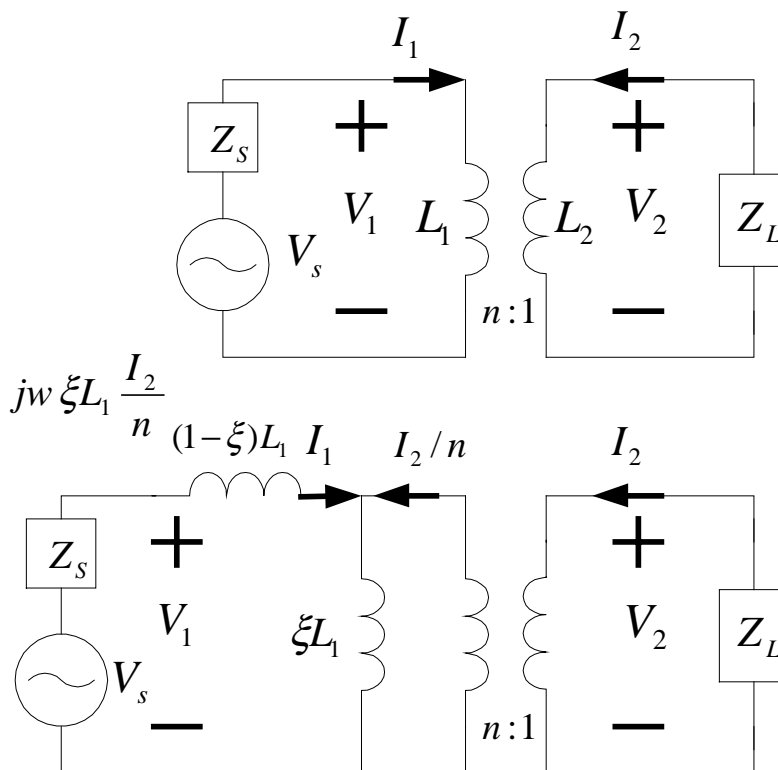
$$\rightarrow \xi = \frac{M}{\sqrt{L_1 L_2}} : \text{coefficient of coupling}$$



Discussion

1. Ex.4.3 A tightly coupled transformer circuit \rightarrow equivalent resonator circuit, ω_0 , Q

$$\xi \approx 1, n = \sqrt{\frac{\xi L_1}{L_2}} = \sqrt{\frac{320}{20}} = 4$$

$$Z_1 = n^2 Z_2 \rightarrow Y_1 = \frac{1}{n^2} \left(\frac{1}{62.5k} + j\omega \times 30.7p \right)$$



$$R = 16 \times 62.5 \times 10^3 = 1M\Omega$$

$$C = 6 + \frac{30.7}{16} = 7.9pF$$

$$L = 320nH$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 99.97MHz$$
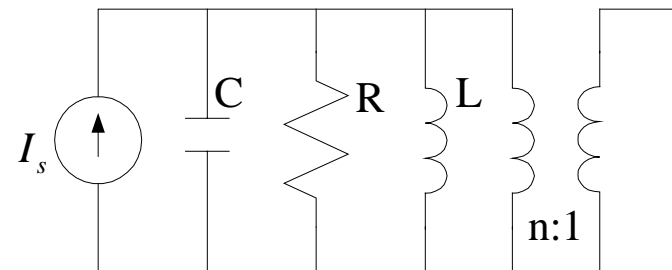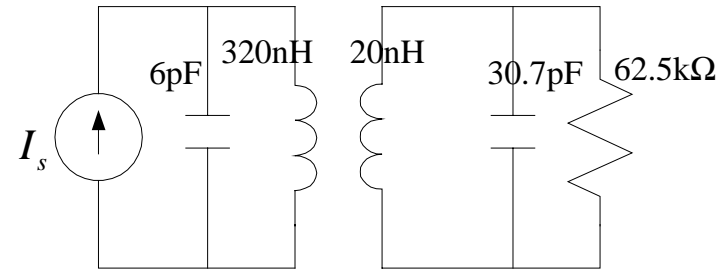
$$Q = \frac{R}{\omega_0 L} = \frac{10^6}{2\pi \times 99.7 \times 10^6 \times 320 \times 10^{-9}} = 4975$$




2. Ex.4.4 A double-tuned transformer-coupled circuit → equivalent circuit, (a) ω_0 and Z_{in} as R_1, C_1 removed (b) I_o/I_s with R_1, C_1

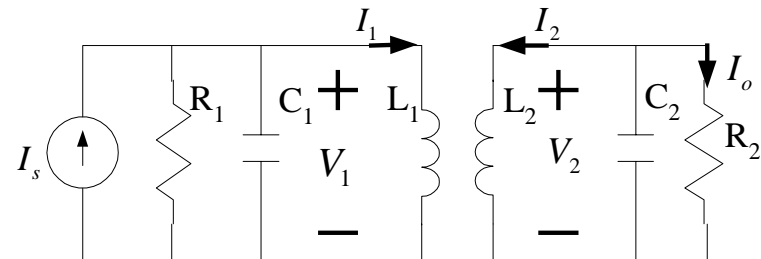(a) without R_1, C_1


$$\omega_0 = \frac{1}{\sqrt{L_2 C_2}}, Z_{in}(j\omega_0) = n^2 R_2$$

$$Z_{in}(j\omega) = j\omega L_1(1-\xi) + \frac{j\omega n^2 L_2}{- \omega^2 L_2 C_2 + j\omega \frac{L_2}{R_2} + 1}$$



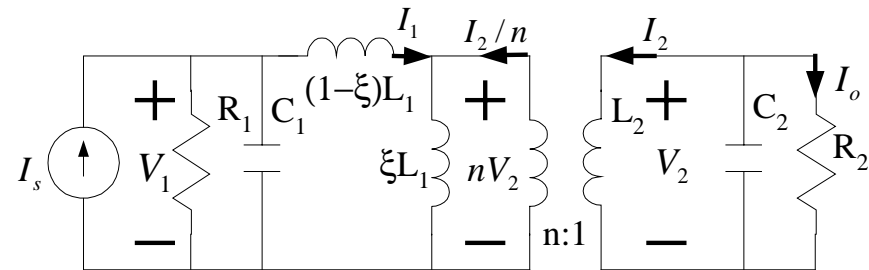(b) with R_1, C_1

$$\begin{cases} nV_2 = j\omega \xi L_1 (I_1 + \frac{I_2}{n}) \\ V_2 = -I_2 \frac{R_2}{1 + j\omega R_2 C_2} = I_o R_2 \\ I_s = I_1 + (\frac{1}{R_1} + j\omega C_1) [nV_2 + j\omega(1-\xi)L_1 I_1] \end{cases}$$



$$\rightarrow \frac{I_o}{I_s} = \frac{\frac{j\omega \xi L_1}{n R_2}}{(-\omega^2 L_2 C_2 + j\omega \frac{L_2}{R_2} + 1) [1 + j\omega(1-\xi)L_1 (\frac{1}{R_1} + j\omega C_1)] + j\omega \xi L_1 (\frac{1}{R_1} + j\omega C_1)} \quad \text{: four poles}$$

as $\xi \rightarrow 0$

$$\frac{I_o}{I_s} \approx \frac{\frac{jw\xi L_1}{nR_2}}{(-w^2 L_2 C_2 + jw \frac{L_2}{R_2} + 1)[1 + jwL_1(\frac{1}{R_1} + jwC_1)] + jw\xi L_1(\frac{1}{R_1} + jwC_1)}$$

for $w_1 = w_2 = w_o, Q_1 = Q_2 = Q_o$

$$L_1 C_1 = L_2 C_2 = \frac{1}{w_o^2}, \frac{R_1}{L_1} = \frac{R_2}{L_2} = w_o Q_o$$

$$\rightarrow \frac{I_o}{I_s} \approx \frac{\frac{jw\xi L_1}{nR_2}}{\left(-\frac{w^2}{w_o^2} + \frac{jw}{w_o Q} + 1\right)^2 + \xi \left(-\frac{w^2}{w_o^2} + \frac{jw}{w_o Q}\right)}$$

4.4 Transmission line resonant circuits

Basics

1. Short-circuited line


$$Z_{in} = Z_o \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \Big|_{Z_L=0} = Z_o \tanh \gamma l$$

$$= Z_o \tanh(\alpha + j\beta)l = Z_o \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tanh \alpha l \tan \beta l}$$

lowloss line $\tanh \alpha l \approx \alpha l$

$$\beta l = \frac{\omega l}{v_p} = \frac{(\omega_o + \delta\omega)l}{v_p} = \beta_r l + \frac{\delta\omega l}{v_p} = \begin{cases} \pi + \frac{\pi\delta\omega}{\omega_o} & l = \frac{\lambda}{2} \\ \frac{\pi}{2} + \frac{\pi\delta\omega}{2\omega_o} & l = \frac{\lambda}{4} \end{cases}$$
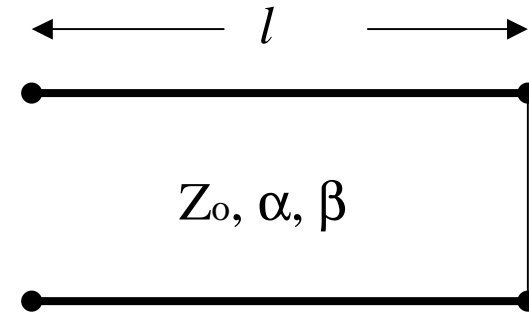
$$\tan \beta l = \begin{cases} \tan\left(\pi + \frac{\pi\delta\omega}{\omega_o}\right) = \tan \frac{\pi\delta\omega}{\omega_o} \approx \frac{\pi\delta\omega}{\omega_o} & l = \frac{\lambda}{2} \\ \tan\left(\frac{\pi}{2} + \frac{\pi\delta\omega}{2\omega_o}\right) = -\cot \frac{\pi\delta\omega}{2\omega_o} \approx -\frac{2\omega_o}{\pi\delta\omega} & l = \frac{\lambda}{4} \end{cases}$$



2. $\lambda/2$ short-circuited line \rightarrow series resonator

$$Z_{in} = Z_o \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tanh \alpha l \tan \beta l} \approx Z_o \frac{\alpha l + j \frac{\pi \delta \omega}{w_o}}{1 + j \alpha l \frac{\pi \delta \omega}{w_o}} \approx Z_o \alpha l + j \frac{Z_o \pi \delta \omega}{w_o}$$

for series resonator $Z_{in} \approx R + j2\delta\omega L$

\rightarrow equivalent circuit parameters

$$R \approx Z_o \alpha l = Z_o \alpha \frac{\lambda_r}{2}, L \approx \frac{\pi Z_o}{2w_o}, C = \frac{1}{w_o^2 L} \approx \frac{2}{\pi w_o Z_o}, Q = \frac{w_o L}{R} \approx \frac{\pi}{2\alpha l} = \frac{\beta_r}{2\alpha}$$

3. $\lambda/4$ short-circuited line \rightarrow parallel resonator

$$Z_{in} = Z_o \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tanh \alpha l \tan \beta l} \approx Z_o \frac{\alpha l - j \frac{2w_o}{\pi \delta \omega}}{1 - j \alpha l \frac{2w_o}{\pi \delta \omega}} \approx Z_o \frac{-j \frac{2w_o}{\pi \delta \omega}}{1 - j \alpha l \frac{2w_o}{\pi \delta \omega}} \times \frac{j \frac{\delta \omega \pi}{2w_o}}{j \frac{\delta \omega \pi}{2w_o}} = \frac{Z_o}{1 + j \frac{\pi \delta \omega}{\alpha l 2w_o}}$$

for parallel resonator $Z_{in} \approx \left(\frac{1}{R} + j2\delta\omega C \right)^{-1} = \frac{R}{1 + j2\delta\omega RC}$

\rightarrow equivalent circuit parameters


$$R \approx \frac{Z_o}{\alpha l} = \frac{4Z_o}{\alpha \lambda_r}, C \approx \frac{\pi}{4w_o Z_o}, L = \frac{1}{w_o^2 L} \approx \frac{4Z_o}{\pi w_o}, Q = \frac{R}{w_o L} \approx \frac{\pi}{4\alpha l} = \frac{\beta_r}{2\alpha}$$

4. Open-circuited line

$$Z_{in} = Z_o \frac{Z_L + Z_o \tanh \gamma l}{Z_o + Z_L \tanh \gamma l} \Big|_{Z_L = \infty} = \frac{Z_o}{\tanh \gamma l} = \frac{Z_o}{\tanh(\alpha + j\beta)l} = Z_o \frac{1 + j \tanh \alpha l \tan \beta l}{\tanh \alpha l + j \tan \beta l}$$

lowloss line $\tanh \alpha l \approx \alpha l$
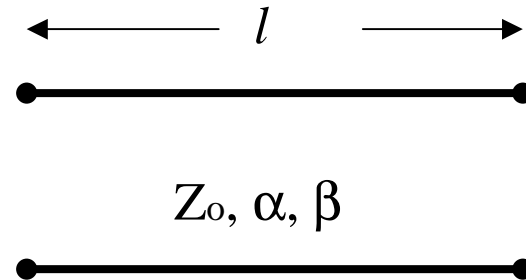
$$\tan \beta l \approx \begin{cases} \frac{\pi \delta w}{w_o} & l = \frac{\lambda}{2} \\ -\frac{2w_o}{\pi \delta w} & l = \frac{\lambda}{4} \end{cases}$$



5. $\lambda/2$ open-circuited line \rightarrow parallel resonator

$$Z_{in} = Z_o \frac{1 + j \tanh \alpha l \tan \beta l}{\tanh \alpha l + j \tan \beta l} \approx Z_o \frac{1 + j \alpha l \frac{\pi \delta w}{w_o}}{\alpha l + j \frac{\pi \delta w}{w_o}} \approx \frac{Z_o}{\alpha l + j \frac{\pi \delta w}{w_o}}$$

$$\text{for parallel resonator } Z_{in} \approx \left(\frac{1}{R} + j2\delta w C \right)^{-1} = \frac{R}{1 + j2\delta w RC}$$

\rightarrow equivalent circuit parameters

$$R \approx \frac{Z_o}{\alpha l} = \frac{2Z_o}{\alpha \lambda_r}, C \approx \frac{\pi}{2w_o Z_o}, L \approx \frac{2Z_o}{\pi w_o}, Q = \frac{\pi}{2\alpha l} = \frac{\beta_r}{2\alpha}$$

6. $\lambda/4$ open-circuited line \rightarrow series resonator

$$Z_{in} = Z_o \frac{1 + j \tanh \alpha l \tan \beta l}{\tanh \alpha l + j \tan \beta l} \approx Z_o \frac{1 - j \alpha l \frac{2w_o}{\pi \delta w}}{\alpha l - j \frac{2w_o}{\pi \delta w}} \approx Z_o \frac{1 - j \alpha l \frac{2w_o}{\pi \delta w}}{-j \frac{2w_o}{\pi \delta w}} = Z_o \left(\alpha l + j \frac{\pi \delta w}{2w_o} \right)$$

for series resonator $Z_{in} \approx R + j2\delta w L$

\rightarrow equivalent circuit parameters

$$R \approx Z_o \alpha l = Z_o \alpha \frac{\lambda_r}{4}, L \approx \frac{\pi Z_o}{4w_o}, C \approx \frac{4}{\pi w_o Z_o}, Q \approx \frac{\pi}{4\alpha l} = \frac{\beta_r}{2\alpha}$$

Discussion

1. Ex.4.5 A coaxial $\lambda/2$ short-circuited line has inner conductor radius $a=0.455\text{mm}$, outer conductor radius $b=1.499\text{mm} \rightarrow Q$ at 5GHz for air dielectric and Teflon dielectric ($\epsilon_r=2.08$, $\tan \delta=0.0004$)

$$\text{copper } R_s = \sqrt{\frac{w\mu_o}{2\sigma}} = \sqrt{\frac{2\pi \times 5 \times 10^9 \times 4\pi \times 10^{-7}}{2 \times 5.813 \times 10^7}} = 0.0184 \Omega$$

$$\alpha_c = \frac{R_s}{2 \sqrt{\frac{\mu_o}{\epsilon \epsilon_r} \ln \frac{b}{a}}} \left(\frac{1}{a} + \frac{1}{b} \right) = \begin{cases} 0.0588 \text{ Np/m} & \text{air} \\ 0.085 \text{ Np/m} & \text{Teflon} \end{cases}$$

$$\alpha_d = \frac{w}{2} \sqrt{\mu_o \epsilon_o \epsilon_r} \tan \delta = \begin{cases} 0 & \text{air} \\ 0.03 \text{ Np/m} & \text{Teflon} \end{cases}$$

$$\beta = \frac{2\pi f \sqrt{\epsilon_r}}{c} = \begin{cases} 104.7 \text{ rad/m} & \text{air} \\ 151.03 \text{ rad/m} & \text{Teflon} \end{cases}$$

$$Q = \frac{\beta}{2\alpha} = \begin{cases} 891 & \text{air} \\ 657 & \text{Teflon} \end{cases}$$

2. Ex.4.6 A 50Ω microstrip $\lambda/2$ short-circuited line has Teflon substrate ($\epsilon_r=2.08$, $\tan \delta=0.0004$) with thickness $h=0.159\text{cm}$, $t=0.159\mu\text{m} \rightarrow Q$ and l at 2GHz

$$\epsilon_r = 2.08, Z_o = 50\Omega, h = 0.159\text{cm} \left\{ \begin{array}{l} \xrightarrow{A2.29,30} w = 0.51\text{cm} \\ \xrightarrow{A2.21,22} \epsilon_{re} = 1.79 \end{array} \right.$$

$$l = \frac{\lambda}{2} = \frac{c}{2f\sqrt{\epsilon_{re}}} = 5.6\text{cm}$$

$$\left. \begin{array}{l} w = 0.51\text{cm}, h = 0.159\text{cm}, t = 0.159\mu\text{m} \\ \epsilon_r = 2.08, \sigma = 5.813 \times 10^7 \text{ S/m}, f = 2\text{GHz} \end{array} \right\} \xrightarrow{A2.26,27} \alpha_c = 0.0428 \text{ Np/m}$$

$$\left. \begin{array}{l} w = 0.51\text{cm}, h = 0.159\text{cm}, \epsilon_r = 2.08 \\ \tan \delta = 0.0004, f = 2\text{GHz} \end{array} \right\} \xrightarrow{A2.28} \alpha_d = 0.0095 \text{ Np/m}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{\pi}{l} = 56 \text{ rad/m}$$

$$Q = \frac{\beta}{2\alpha} = \frac{56}{2 \times (0.0428 + 0.0095)} = 535.4$$

4.5 Microwave resonators

Basics

1. Rectangular cavities dimension a, b, c

$$TE_{mnp}, TM_{mnp} \text{ mode resonant frequency } f_r = \frac{3 \times 10^8}{2\pi \sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 + \left(\frac{p\pi}{c}\right)^2}$$

$$TE_{10p} \text{ mode } Q_c = \frac{2W_e}{P_l} = \frac{60b(acw\sqrt{\mu\epsilon})^3}{\pi R_s(2p^2a^3b + 2bc^3 + pa^3c + ac^3)} \sqrt{\frac{\mu_r}{\epsilon_r}}$$

$$Q_d = \frac{1}{\tan \delta}$$

2. Circular cylindrical cavities

$$f_r = \frac{c}{2\pi \sqrt{\mu\epsilon}} \sqrt{\left(\frac{\chi_{nm}}{r}\right)^2 + \left(\frac{p\pi}{h}\right)^2}, p = \begin{cases} p_{nm} & TM_{nmp} \text{ mode} \\ p'_{nm} & TE_{nmp} \text{ mode} \end{cases}$$


p_{nm} : mth zero of the Bessel function $J_n(x)$ of the first kind and order n

p'_{nm} : mth zero of $J'_n(x)$: Table 4.3

$$Q_c = \begin{cases} 4.5.10 & TE_{nmp} \text{ mode} \\ 4.5.11 & TM_{nmp} \text{ mode} \end{cases}, Q_d = \frac{1}{\tan \delta}$$

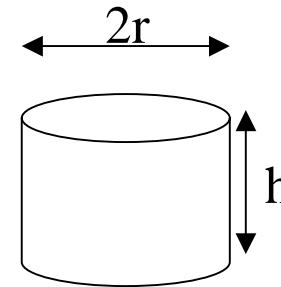3. Dielectric resonator (DR): high ϵ , low $\tan \delta$,
low temperature coefficient, $TE_{01\delta}$ mode

$$f_r = \frac{34}{r\sqrt{\epsilon_r}} \left(3.45 + \frac{r}{h}\right) \text{GHz} \quad TE_{01\delta} \text{ mode}$$



Discussion

1. Ex.4.7 A rectangular cavity made of WR-90 resonates at 9.379GHz
in TE_{101} mode \rightarrow length l and Q

WR-90 waveguide $a = 0.9\text{in} = 2.286\text{cm}$, $b = 0.4\text{in} = 1.016\text{cm}$

$$TE_{101} \text{ mode } 9.379 \times 10^9 = \frac{3 \times 10^8}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{\pi}{2.286}\right)^2 + \left(\frac{\pi}{l}\right)^2} \rightarrow l = 2.238\text{cm}$$

$$(4.5.2) Q_c = 7858$$

2. Ex.4.8 A rectangular cavity with $a=1.6\text{cm}$, $b=0.71\text{cm}$, $c=1.56\text{cm}$ is
filled with Teflon $\rightarrow TE_{101}$ mode f_r and Q

$$f_r = \frac{3 \times 10^8}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{\pi}{1.6}\right)^2 + \left(\frac{\pi}{1.56l}\right)^2} = 9.375\text{GHz}$$

$$(4.5.2) Q_c = 5489, Q_d = \frac{1}{\tan \delta} = 3417, \frac{1}{Q} = \frac{1}{Q_c} + \frac{1}{Q_d} \rightarrow Q = 2106$$

3. Ex.4.9 A cylindrical cavity is operated at 5GHz in TE₀₁₁ mode → Q and height h (h=2r)

$$\chi_{01} = p'_{01} = 3.832$$

$$5 \times 10^9 = \frac{c}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{3.831}{r}\right)^2 + \left(\frac{\pi}{2r}\right)^2} \rightarrow r = 0.0395 \text{ cm}, h = 0.079 \text{ cm}$$

$$Q = 39984.6$$

4. DR selection in the operation with microstrip line


$$\frac{1.2892 \times 10^8}{f_r \sqrt{\epsilon_s}} > r > \frac{1.2892 \times 10^8}{f_r \sqrt{\epsilon_r}}$$

$$(4.5.17) \sim (4.5.23) \rightarrow h$$

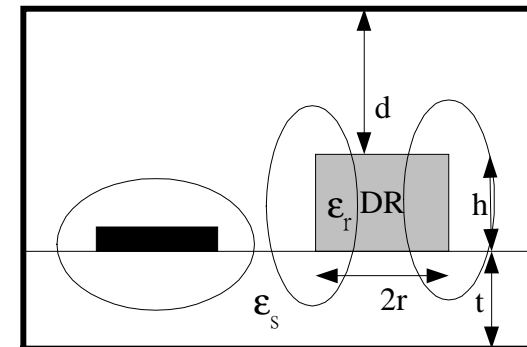5. Ex.4.10 DR $\epsilon_r=36$, substrate $\epsilon_s=9.9$,
t=0.25mm → DR dimensions for 35GHz

$$1.17 \text{ mm} > r > 6.139, \rightarrow r = 0.835 \text{ mm}$$

$$(4.5.17) \sim (4.5.23) \rightarrow h = 0.668 \text{ mm}$$



Hw #3(due 2 weeks) 5, 7,
12, 15, 18