



# *Magnetic Sensor and Interface Circuit (2)*

林宗賢

*GIEE/NTU*





## Outlines

- More on Hall sensors
  - Review
  - Hall sensor array
  - Integrated magnetic concentrator
  - Three-axis application


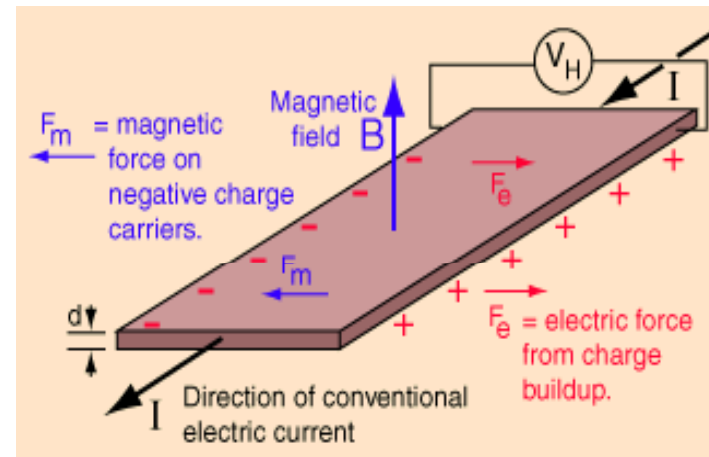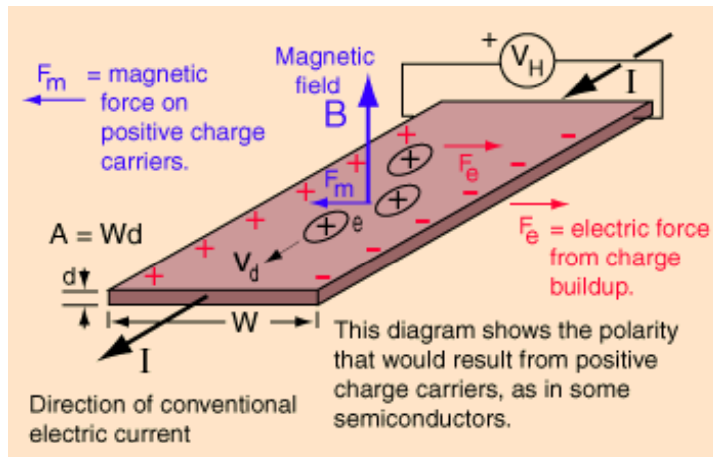
## Review: Hall Sensor

- Based on the interaction between moving electric carriers and an external magnetic field.



$$F_m = qv_d B \quad I = qnAv_d; \quad n: \text{density of the charge carriers}$$

$$\Rightarrow F_m = IB/nA$$

At equilibrium:  $F_m = F_e = qV_H/W$

$$\Rightarrow V_H = IB/qnd$$

$$I = \frac{E}{R_H} = \frac{E}{\rho(L/Wd)}; \quad \rho = \frac{1}{qn\mu_H}$$


$\mu_H$ : mobility of the carriers (E: driving voltage)

$$\Rightarrow V_H = \mu_H \frac{W}{L} EB$$


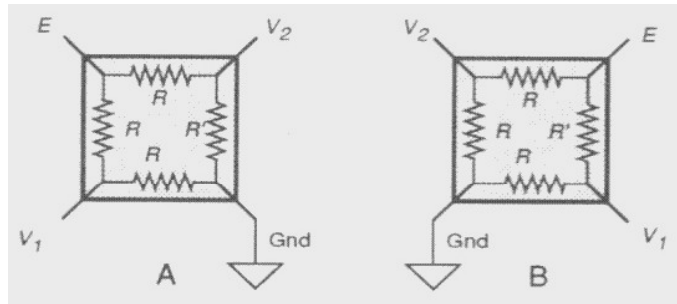
## Review: Hall Sensor Offset

- Major design issue: offset
  - Modeled as resistor mismatch in a Wheatstone bridge
  - Use multiple Hall plates with rotated connections
    - Limited by Hall plate mismatch
  - Spinning current techniques
    - Modulate either the Hall voltage or offset




$$V_a = V_2 - V_1 = V_H + \frac{R' - R}{2(R' + R)} E$$

$$V_b = V_2 - V_1 = -V_H + \frac{R' - R}{2(R' + R)} E$$

$$\Rightarrow V_{out} = V_a - V_b = 2V_H$$

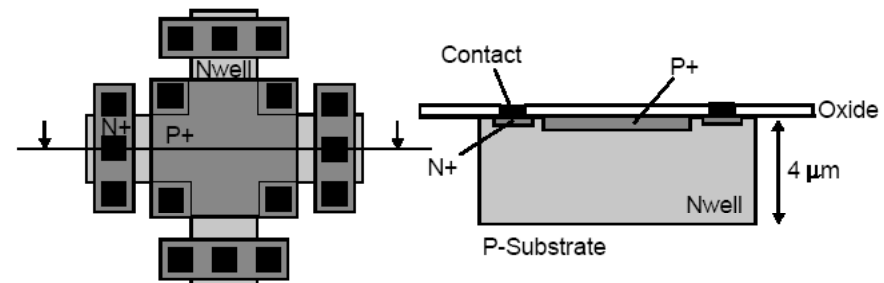- Inherent chopping
- Temperature compensation






# Hall Sensor Array


- Single plate vs. array

## Spinning-Current Hall Plate

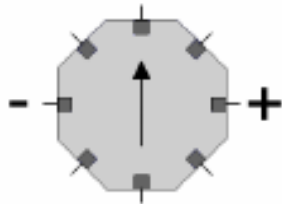

- Current is rotated, while the Hall voltage is summed
- Symmetrical offsets are canceled out
- Spinning-current Hall sensor offset 10-100 $\mu$ T
- Compensation over time  
 $\Rightarrow$  Varying offset sources remain a problem

## Hall Sensor Offset Reduction

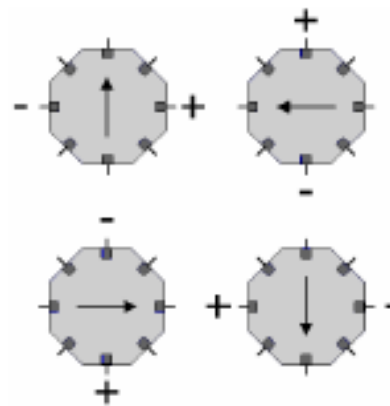


- Orthogonal coupling
  - Quad layout
  - Instantaneous compensation
- Time-varying offset is also compensated
  - Ambient temperature
  - Packaging stress
  - Intermodulation of Hall sensor & electronics

- ✓ SNR improvement
- ✓ Offset reduction
- × Increased current consumption
- × Area increased


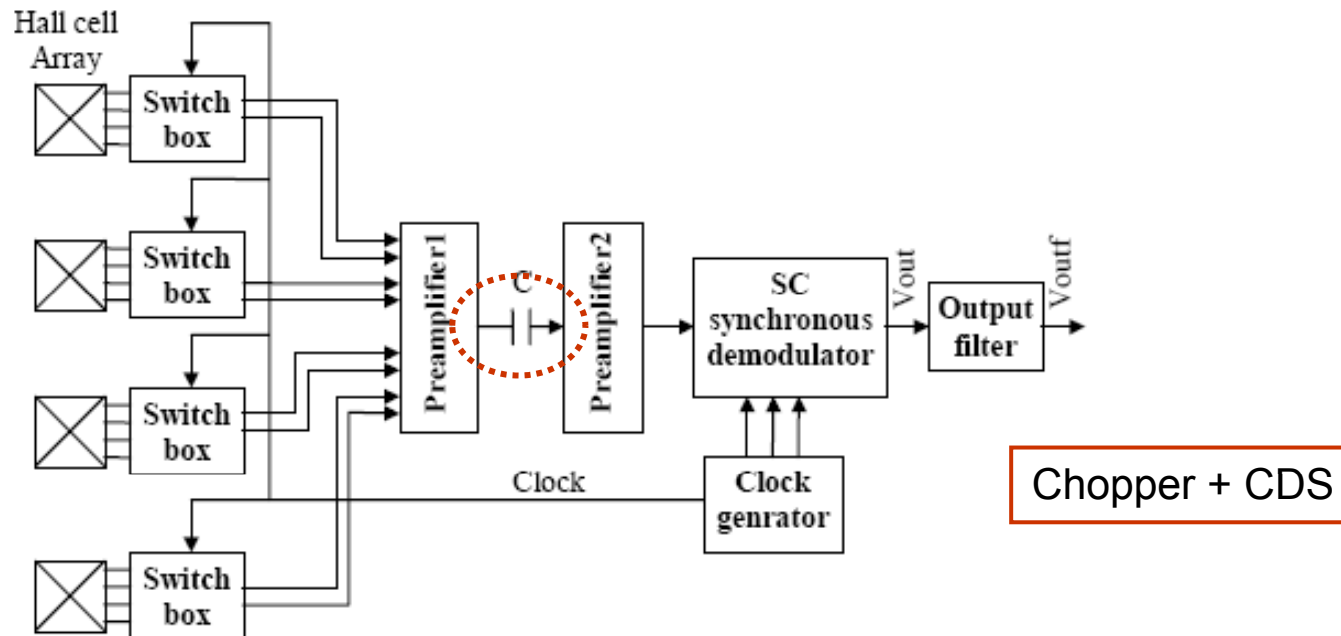
## Hall Sensor Array & Interface

- Spinning current technique with array of Hall sensors
  - Use smaller sensor
- Hall voltages change polarity in each state, whereas the offset voltages appear as DC at output nodes.




- J. Frounchi et al., "Integrated Hall Sensor Array Microsystem", *ISSCC*, pp.218-219, Feb. 2001.


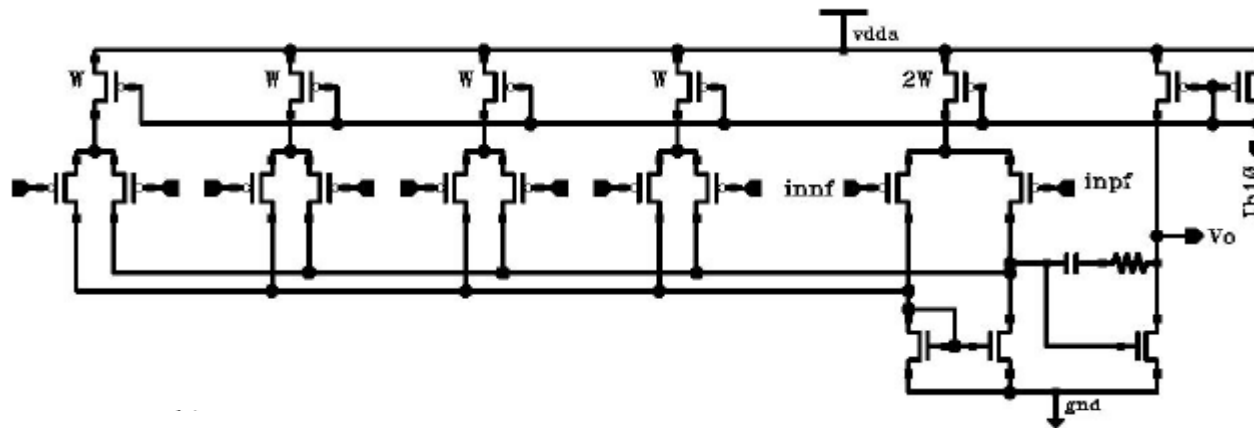
## Hall Sensor Array & Interface

- Preamplifier 1: 5-input Differential-Difference Amplifier (DDA)




Design issues:

- Input offset voltage of each input pair
- Transconductance ( $g_m$ ) of each pair
- Stability




# Differential-Difference Amplifier (DDA)

- Comparison

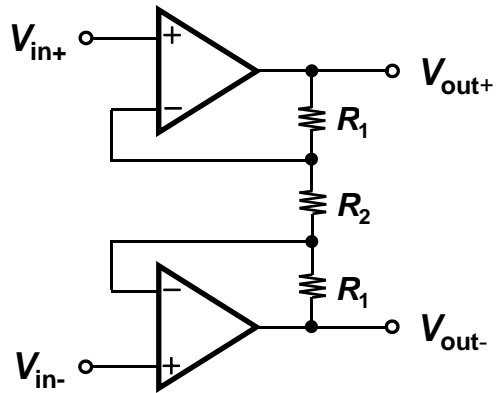

$$A_V = 1 + 2 \cdot \frac{R_1}{R_2}$$


**Consume more power!**

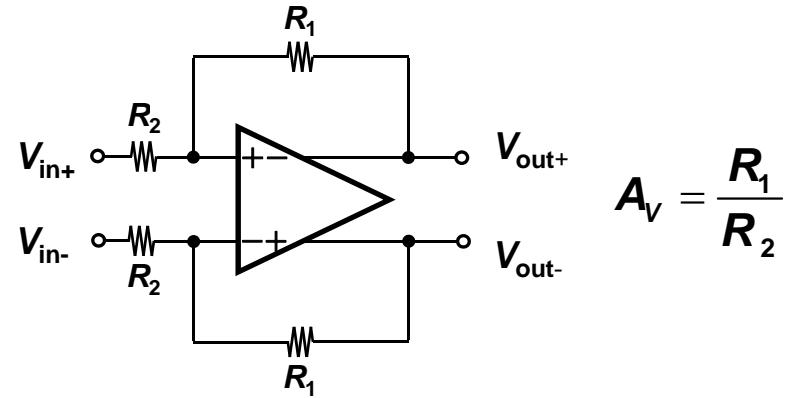

$$A_V = \frac{R_1}{R_2}$$

**Finite input impedance!**


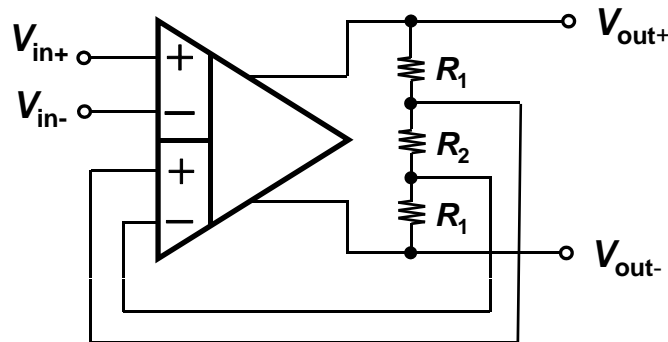
**Differential-Difference Amplifier (DDA)**



$$A_V = 1 + 2 \cdot \frac{R_1}{R_2}$$





# SC Synchronous Demodulator

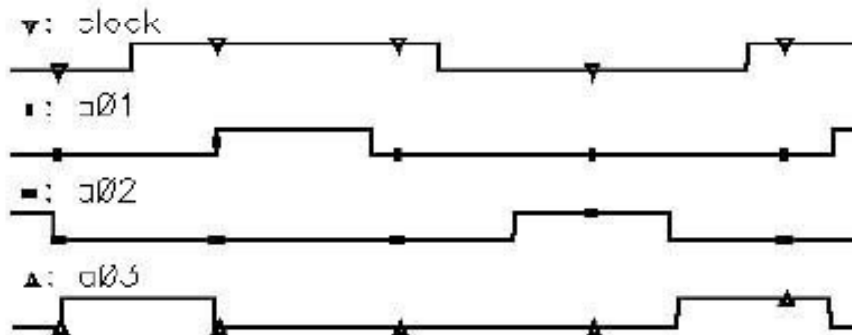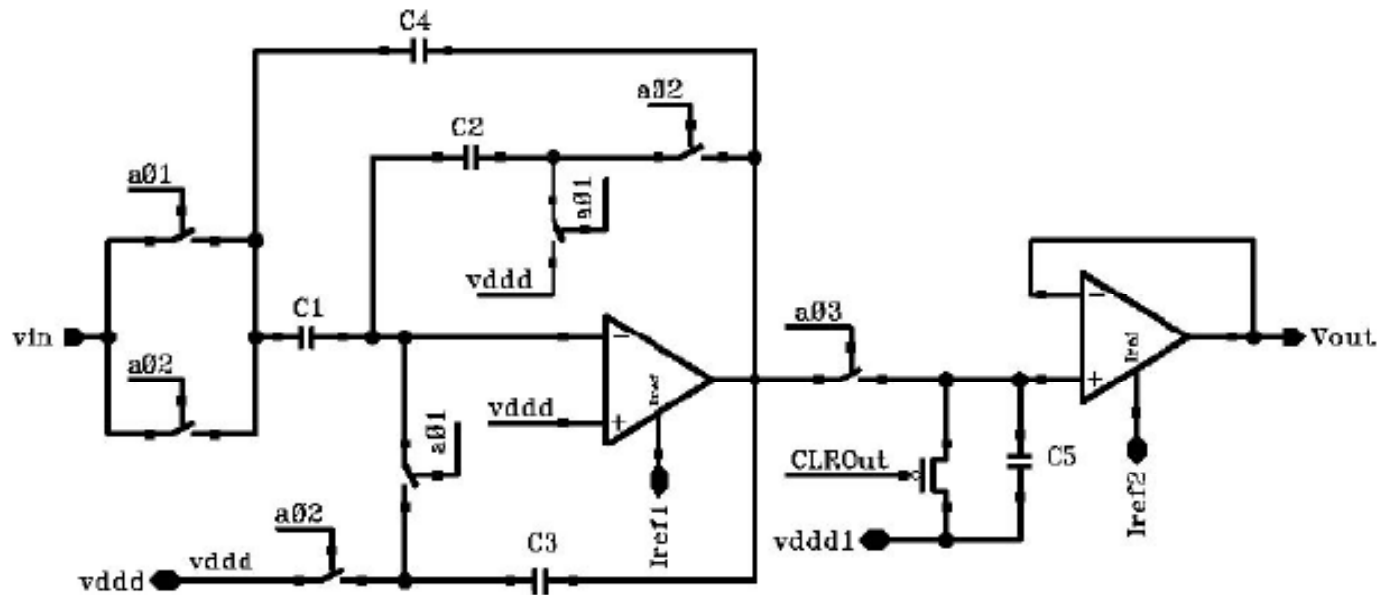


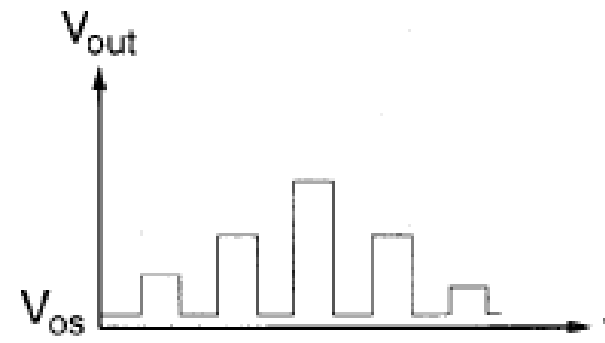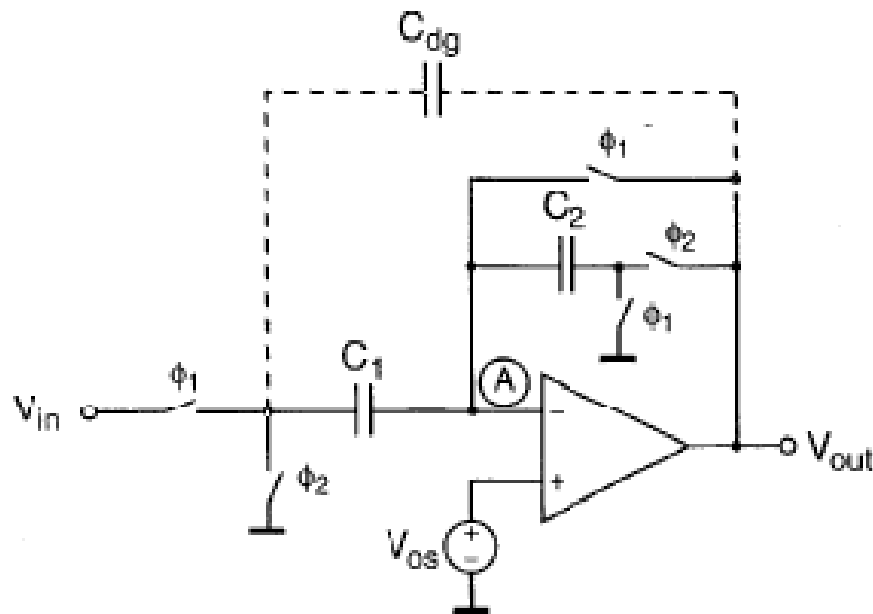
## Offset-Compensated SC Amplifier

- $V_{out}$  is pulled to  $V_{os}$  during  $\phi_1$ .




What is the purpose of  $C_{dg}$ ?

- C. C. Enz and G. C. Temes, "Circuit Techniques for Reducing the Effects of Op-Amp Imperfections: Autozeroing, Correlated Double Sampling, and Chopper Stabilization", *Proceedings of the IEEE*, pp.1584-1614, Nov. 1996




## Hall Sensor Array & Interface

- Apply nested-chopper technique

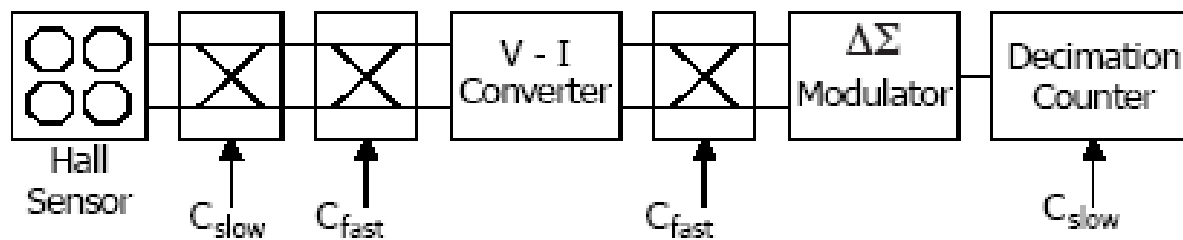

Nested chopper  
Charge injection deadband

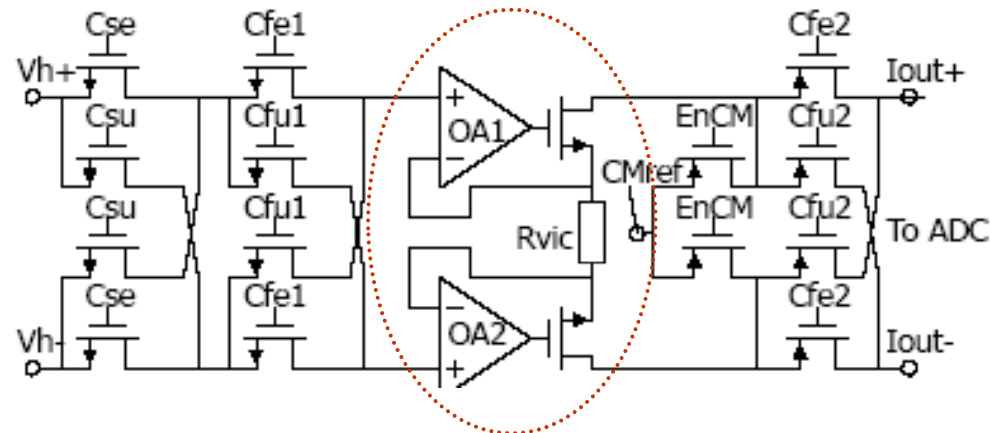- Chopper implementation with the high-linearity V-I converter




- J. C. van der Meer et al., "A Fully Integrated CMOS Hall Sensor with a  $3.65\mu\text{T}$   $3\sigma$  Offset for Compass Applications", *IEEE ISSCC*, pp. 246-247, Feb. 2005.


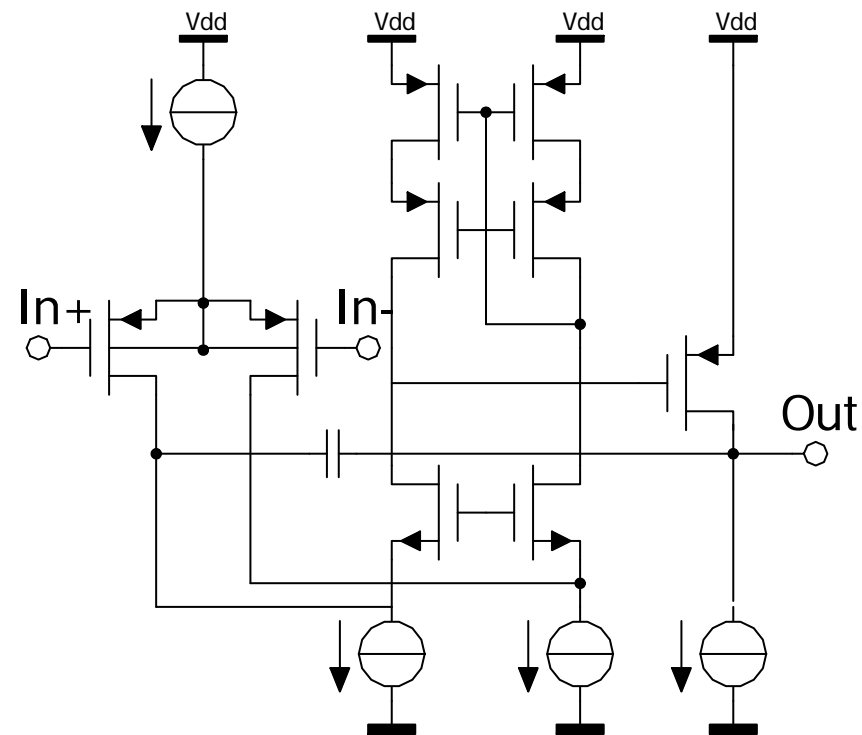
## Design of OA1




- Folded cascode input stage
- Large gain for high linearity





# Frequency Compensation

- Miller compensation

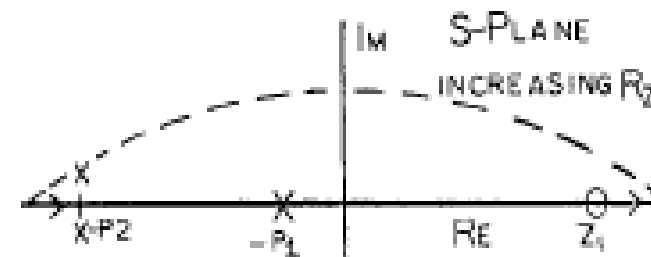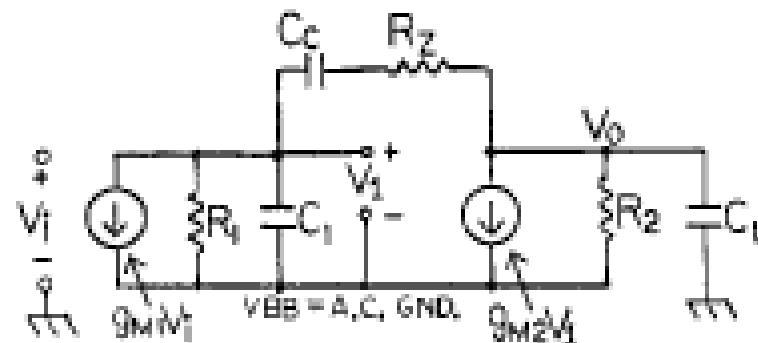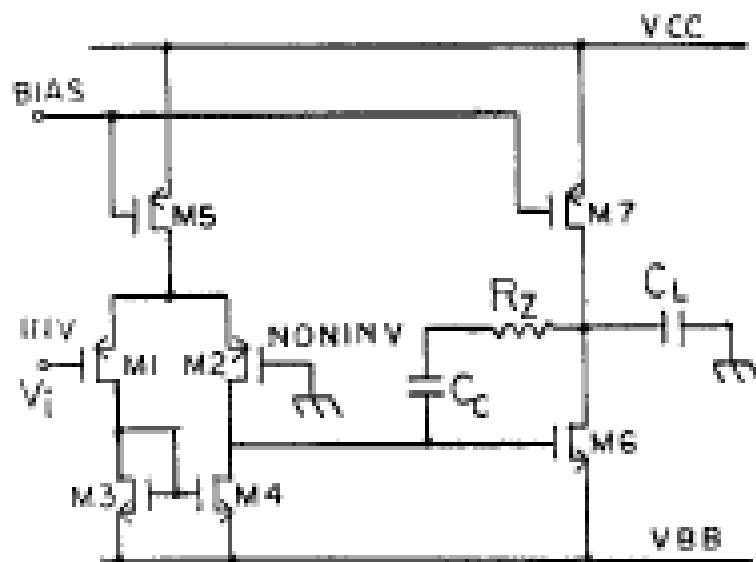

$$P_1 = \frac{1}{(1 + g_{m2}R_2)C_C R_1}$$

$$P_2 = \frac{g_{m2}C_C}{C_1 C_L + C_1 C_C + C_L C_C}$$

$$Z_1 = \frac{1}{C_C \left( \frac{1}{g_{m2}} - R_2 \right)}$$


- B. K. Ahuja, "An Improved frequency compensation technique for CMOS operational amplifiers", *IEEE JSSC*, vol. SC-18. no. 6, pp. 629-633, Dec. 1983.



# Capacitor Multiplier

- Manipulate the terminal voltage or current

## Control the terminal voltage

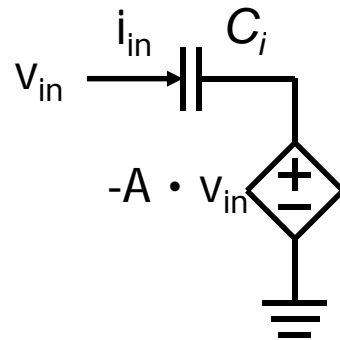


$$i_{in} = (v_{in} + A \cdot v_{in})sC_i$$

$$\frac{v_{in}}{i_{in}} = \frac{1}{s(1+A)C_i}$$

$$C_{eq} = (1+A)C_i$$

## Control the terminal current

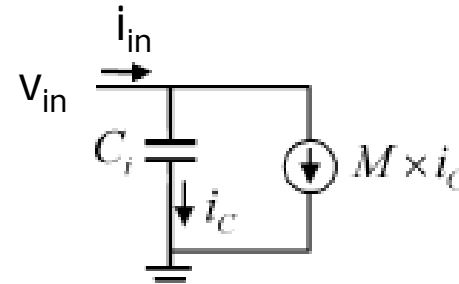


$$i_{in} = v_{in} \cdot sC_i + M \cdot v_{in} \cdot sC_i$$

$$\frac{v_{in}}{i_{in}} = \frac{1}{s(1+M)C_i}$$

$$C_{eq} = (1+M)C_i$$


- Application: PLL loop filter

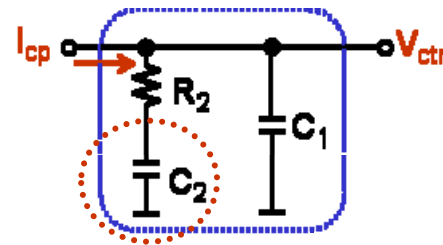


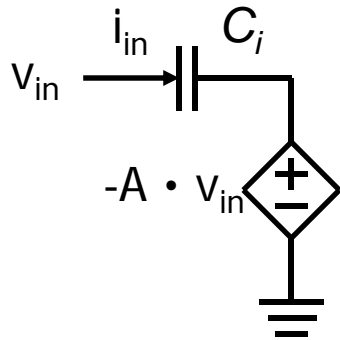
## Capacitor Multiplier


- Control the terminal voltage
  - Increase the amount of current flowing through a capacitor for a given  $V_{in}$



$$i_{in} = (v_{in} + A \cdot v_{in})sC_i$$

$$\frac{v_{in}}{i_{in}} = \frac{1}{s(1+A)C_i}$$

$$C_{eq} = (1+A)C_i$$

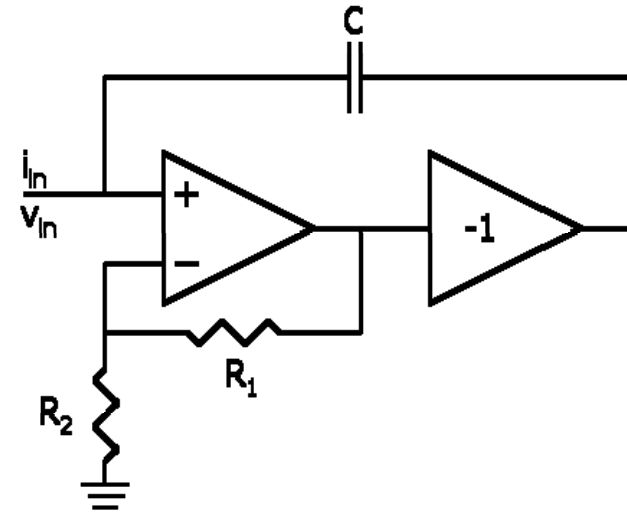

$$i_{in} = [v_{in} + v_{in}(1 + \frac{R_1}{R_2})]sC$$


$$\frac{v_{in}}{i_{in}} = \frac{1}{s(1+A)C} \quad A = 1 + \frac{R_1}{R_2}$$

$$C_{eq} = (1+A)C$$


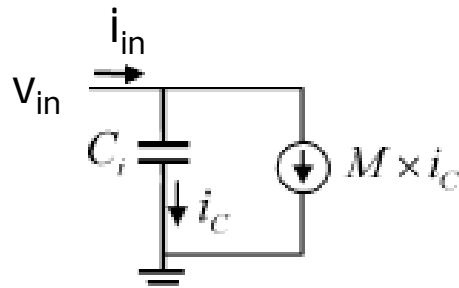
# Capacitor Multiplier


- Control the terminal current
  - Produce a larger input current for a given input voltage




$$i_{in} = v_{in} \cdot sC_i + M \cdot v_{in} \cdot sC_i$$

$$\frac{v_{in}}{i_{in}} = \frac{1}{s(1+M)C_i}$$

$$C_{eq} = (1+M)C_i$$

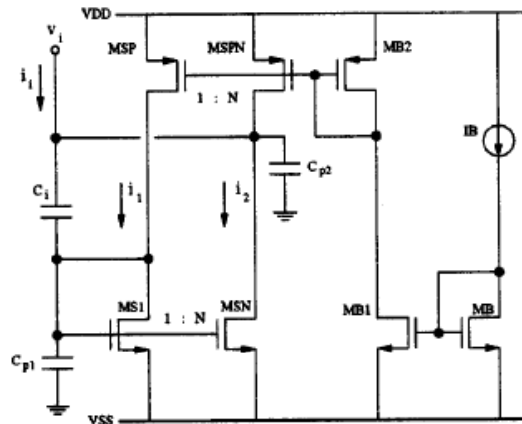

Basic circuit

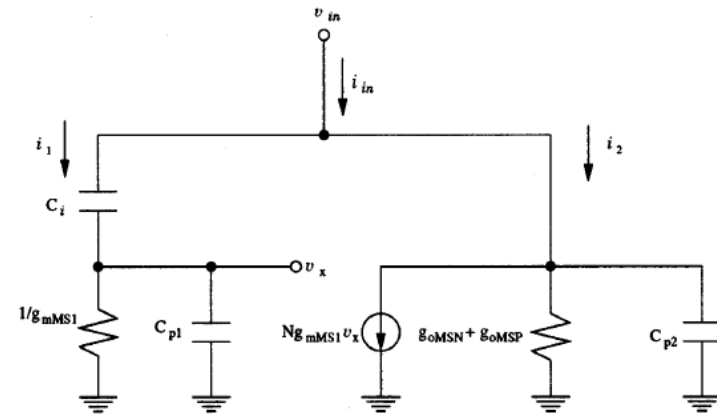

Small-signal circuit model





- S. Solis-Bustos et al., "A 60-dB Dynamic-Range CMOS Sixth-Order 2.4-Hz Low-Pass Filter for Medical Applications," *IEEE Tran. On Circuits and Systems-II*, vol. 47, pp. 1391-1398, Dec. 2000.





# Frequency Compensation



- Modified Miller compensation

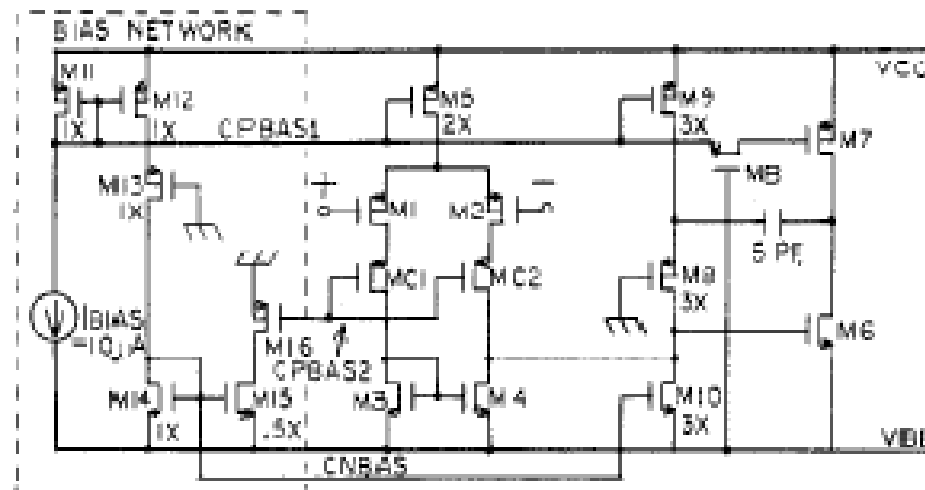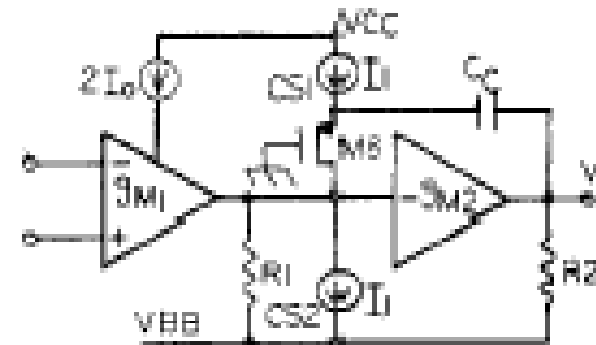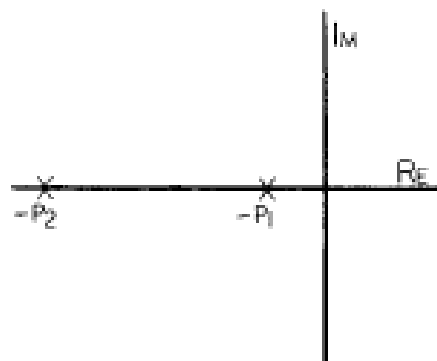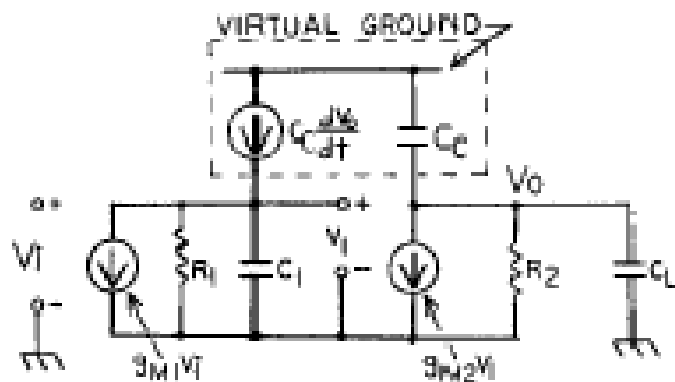


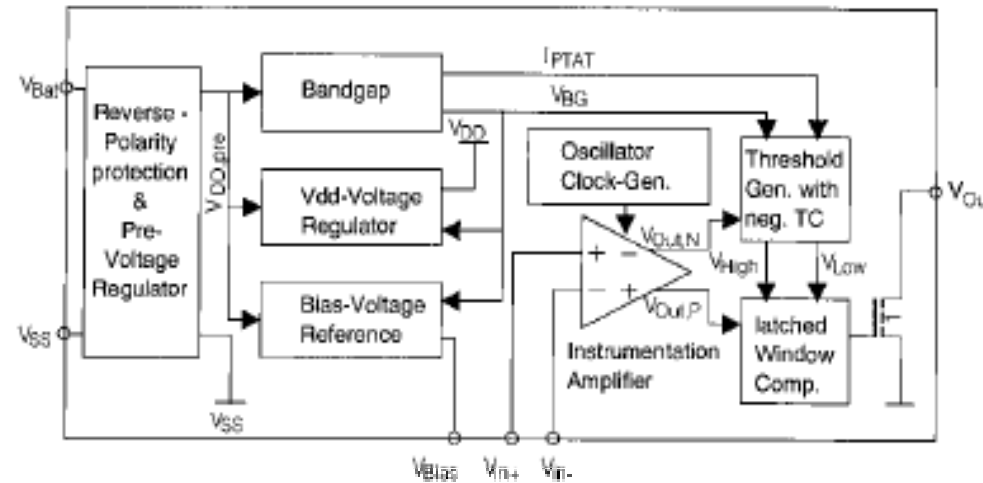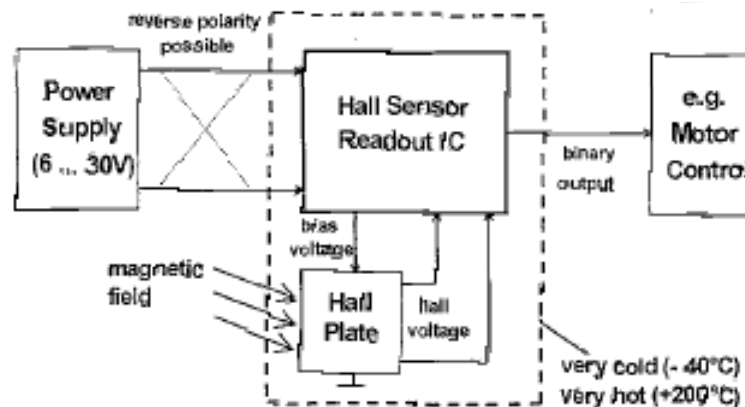
# Hall Sensor: Interface (1)

- Design considerations:
  - Offset and noise (Hall sensor and electronics)
  - Temperature compensation
  - Stable (BG) reference voltages ( $V_{DD}$  and bias voltage for Hall plate)




Switch-type application

- N. Kordas et al., "An SOI 0.6mV Offset Temperature-Compensated Hall Sensor Readout IC for Automotive Applications up to 200°C", *ISSCC*, pp.134-135, Feb. 1999.



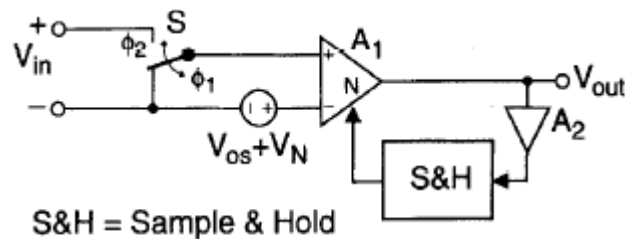
## Review: Auto-zeroing

- Sampling the unwanted offset and then subtracting from the output
- Two-phase operation:
  - Sampling phase
  - Signal-processing (amplification) phase
- Analog method



- Digital method


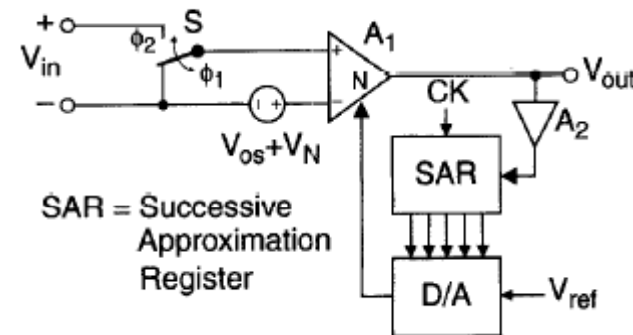


- A **sampling** process – sub-sampling the noise spectrum, noise folding occurs
- C. C. Enz and G. C. Temes, “Circuit Techniques for Reducing the Effects of Op-Amp Imperfections: Autozeroing, Correlated Double Sampling, and Chopper Stabilization”, *Proceedings of the IEEE*, pp.1584-1614, Nov. 1996


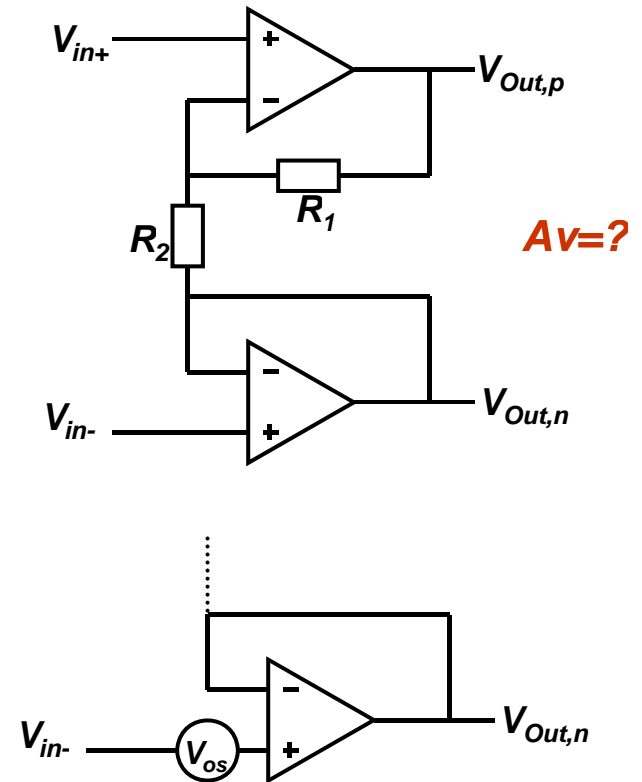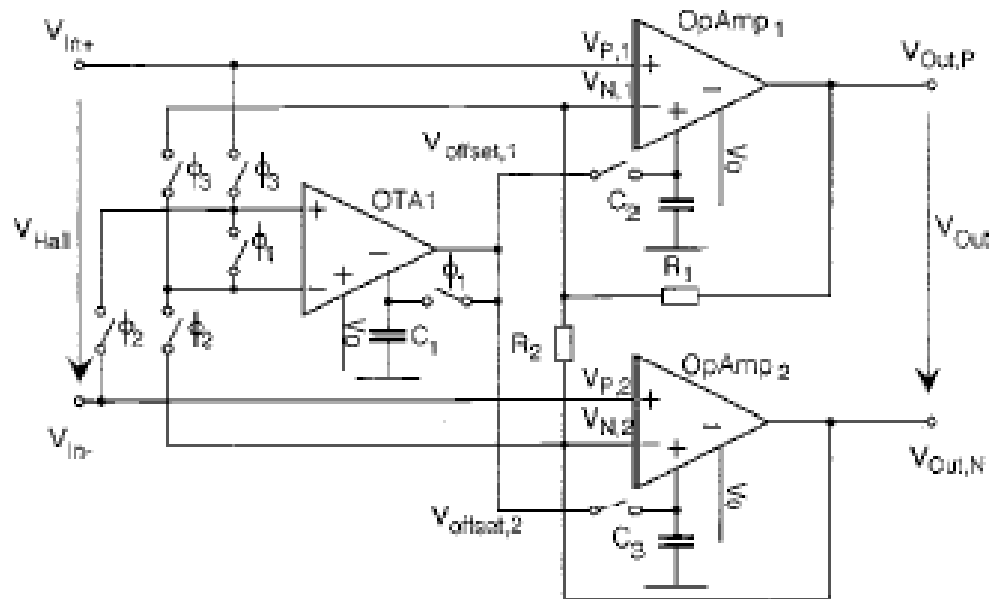
## Hall Sensor: Interface (2)



- Instrumentation Amplifier
  - Offset in the first amplification stage (IA) is the most important one.





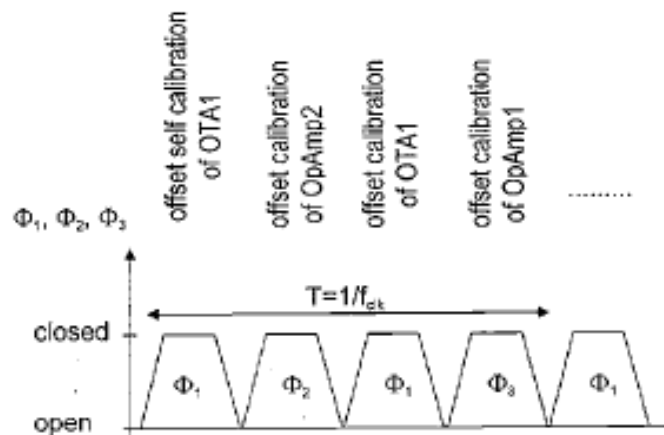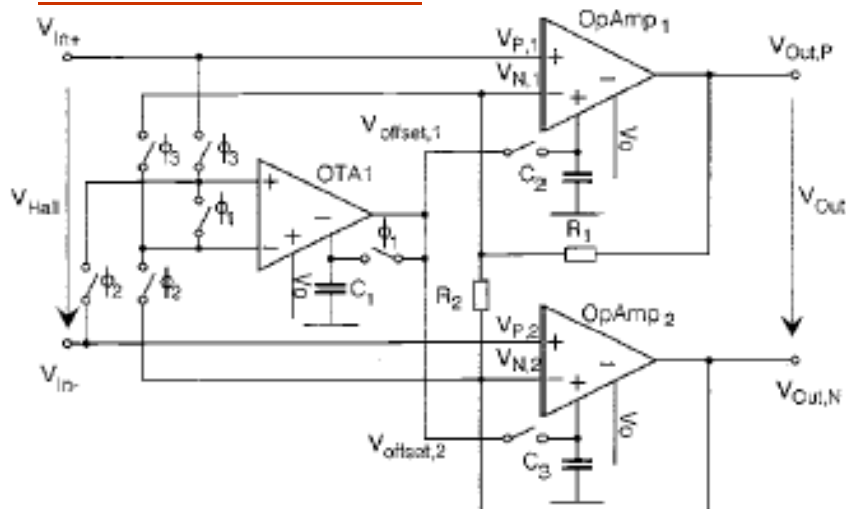
# Hall Sensor: Interface (3)

- **Time continuous** offset cancellation



During  $\phi_1$ , the offset of OTA1 is cancelled

During  $\phi_2$ :

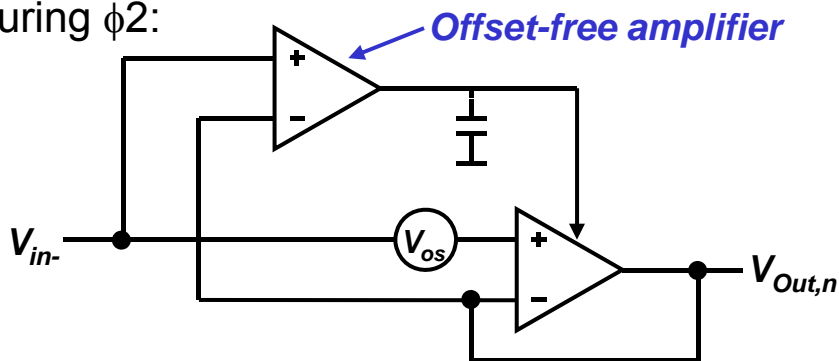



**Q: Does the bandwidth of the signal path depend on the offset cancellation frequency?**




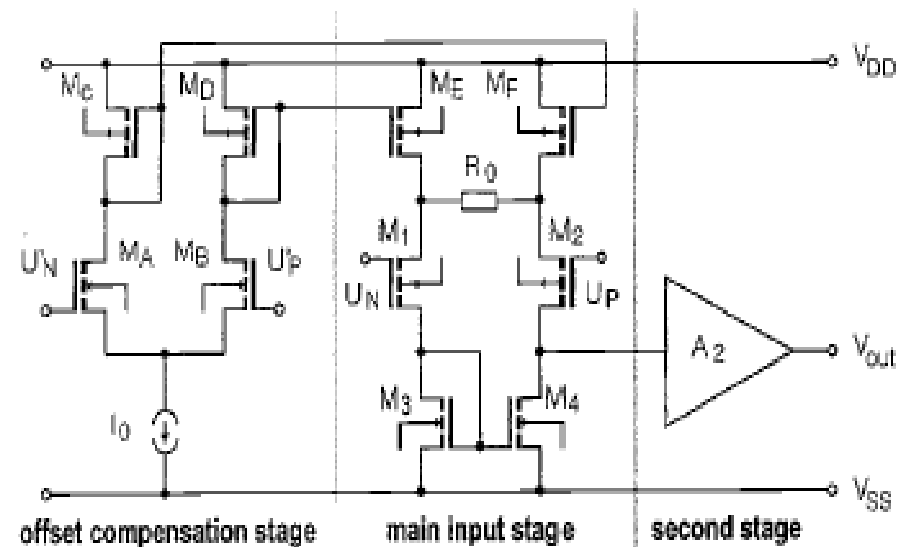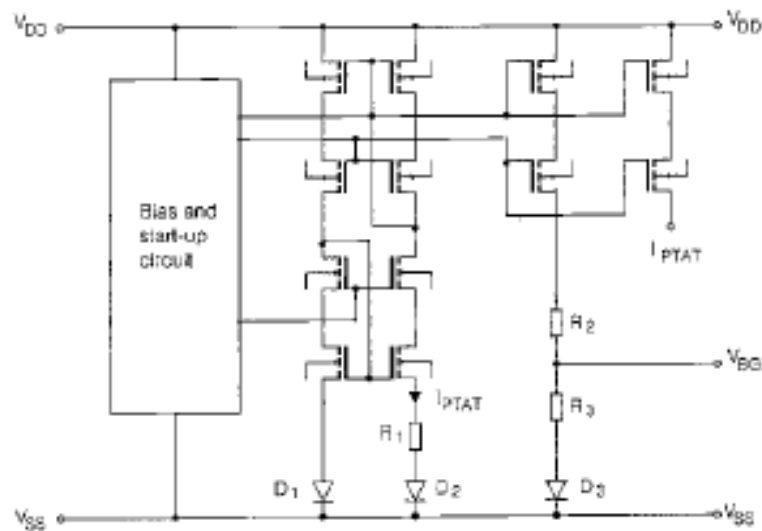
## Hall Sensor: Interface (5)

- Bandgap circuit & Amplifier with auxiliary input




$$V_{BG} = V_{D3} + \frac{R_3}{R_1} m \frac{kT}{q} \ln\left(\frac{A_2}{A_1}\right), \quad I_{PTAT} = \frac{m}{R_1} \frac{kT}{q} \ln\left(\frac{A_2}{A_1}\right)$$


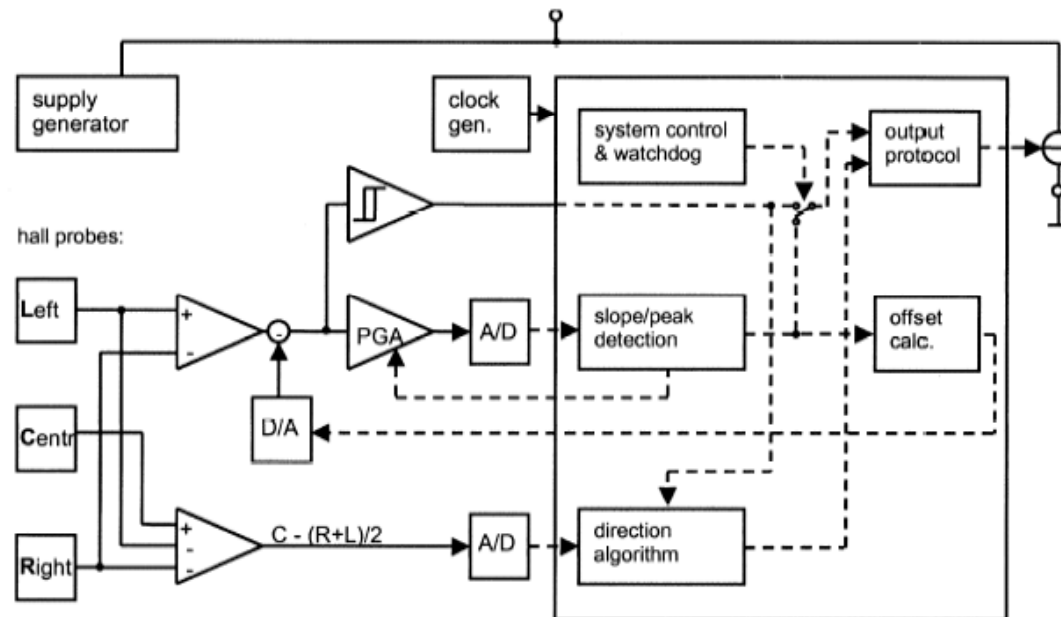
## Hall Sensor: Interface (6)

- Another offset cancellation topology
  - Estimate the offset in digital domain, then apply the correction in analog domain (similar to a wireless transceiver)
  - Noise and offset are particularly important in the front-end stage



- D. Draxelmayr, et al., "A Self-Calibrating Hall Sensor IC with Direction Detection", *IEEE JSSC*, pp.1207-1212, July 2003.




## Hall Sensor: Interface (7)

- Offset cancellation approach: high-pass filtering
  - Low corner frequency
    - Large time constant
    - Off-chip components
  - Long start-up time
  - Sensitive to leakage current
  
- D. Draxelmayr, et al., “A Dynamic Differential Hall IC with Current Interface for Automotive Sensor Applications”, *IEEE ISSCC*, pp. 204-205, 1997.


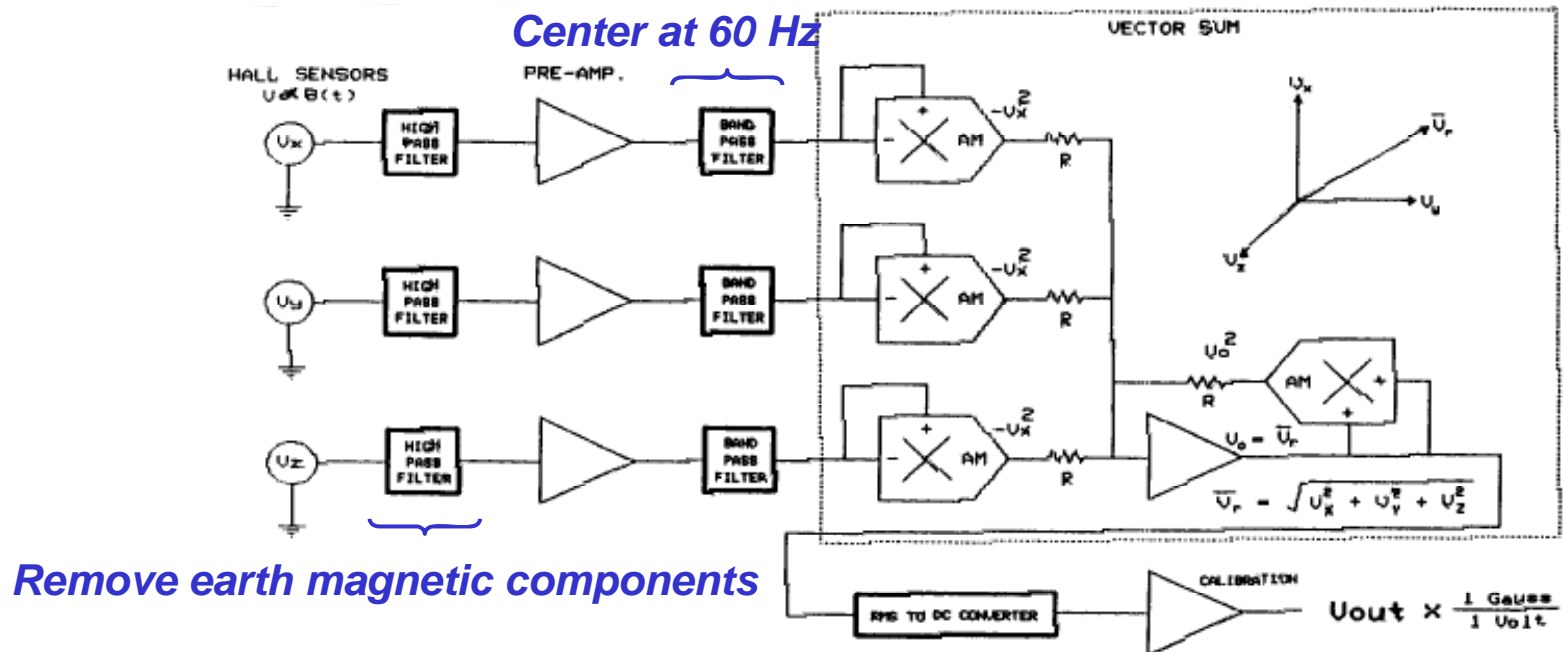
## Hall Sensor: Total-Field Magnetometer

- Measuring magnetic field from electrical appliance, power line, etc.
  - Not orientation dependent
- Tai power < 10m Gauss





- F. A. Phan, "A Hall-Effect Magnetic Field Detector", *IEEE Northeast Bioengineering Conf.*, pp.255-256, April 1991.


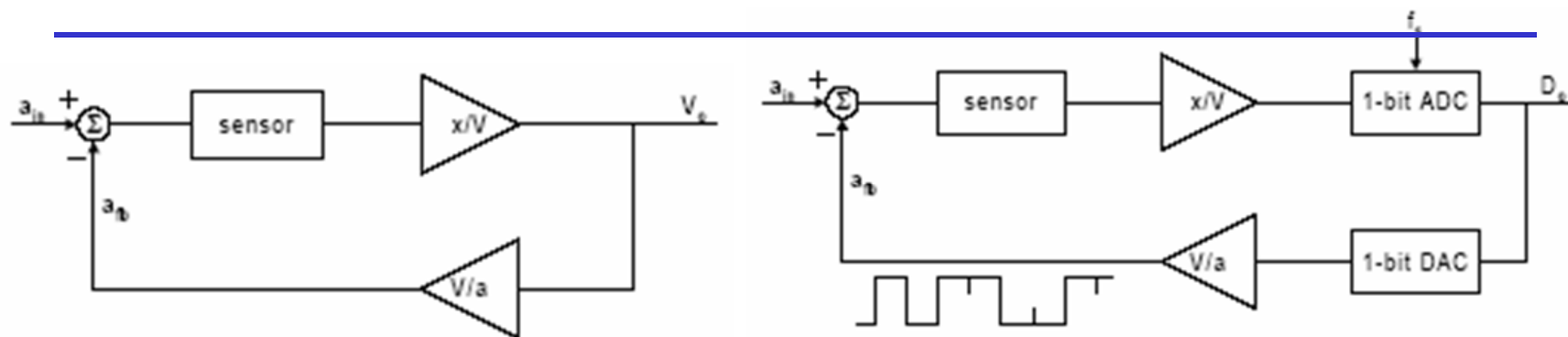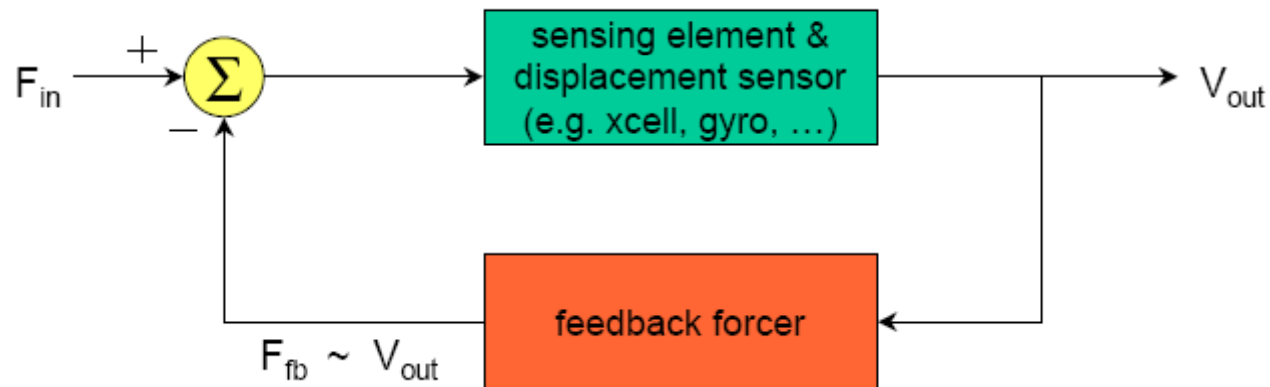
## Interface Technique: Closed-Loop

- Feedback to maintain zero influence
  - When stable,  $F_{in} = F_{fb} \Rightarrow V_{out}$  represents the sensed output signal




**How to apply the closed-loop method?**




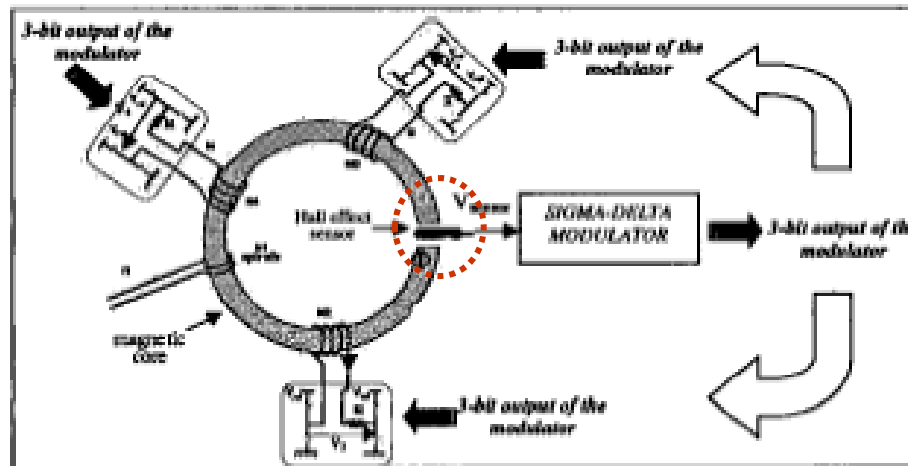
# Current Sensor

- Applying Hall effect for current sensing
  - Hall sensor placed in the air gap to measure the net magnetic flux



“sensor”

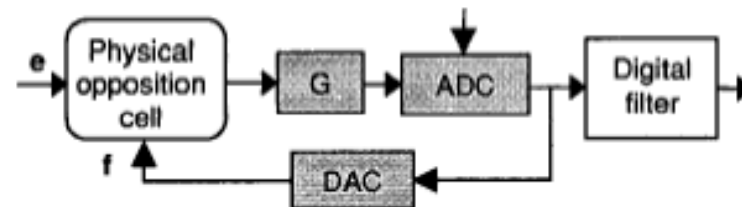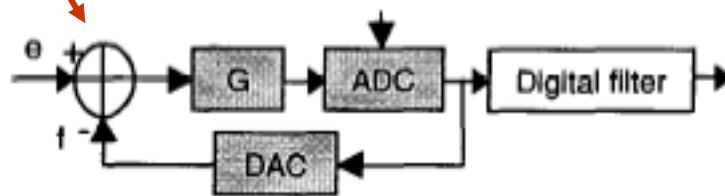



- Average of  $f$  tracks  $e$ .
- Hall sensor measures an average of zero flux.

- M. Jouini, et al., “High-Level Design of a Digital Current Sensor Using Multi-bit Sigma-Delta modulation”, *IEEE Sensors for Industry Conf.*, pp.23-28, Nov. 2001.


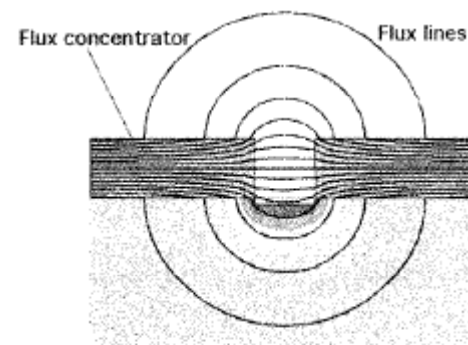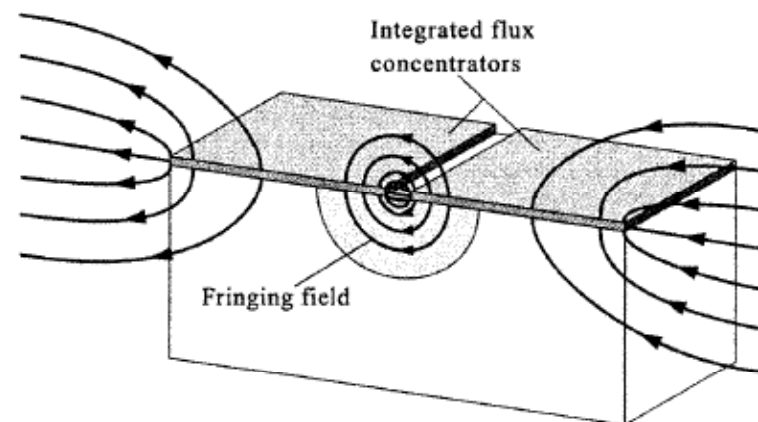
## Integrated Magnetic Concentrator (IMC)

- A high-permeability ferromagnetic layer is deposited
- Etched a gap in the middle and split into two pieces
- External magnetic field parallel to the chip surface is captured by IMC
- In the vicinity of the gap, the magnetic flux splits into two parts: horizontal and fringing parts
- Integrated magnetic concentrator
  - Change the direction
  - Focus the magnetic flux
- Z. B. Randjelvoic, et al., “Highly Sensitivity Hall Magnetic Sensor Microsystem in CMOS Technology”, *IEEE JSSC*, vol. 37, pp. 151-159, Feb. 2002.




Produce vertical flux from a horizontal field




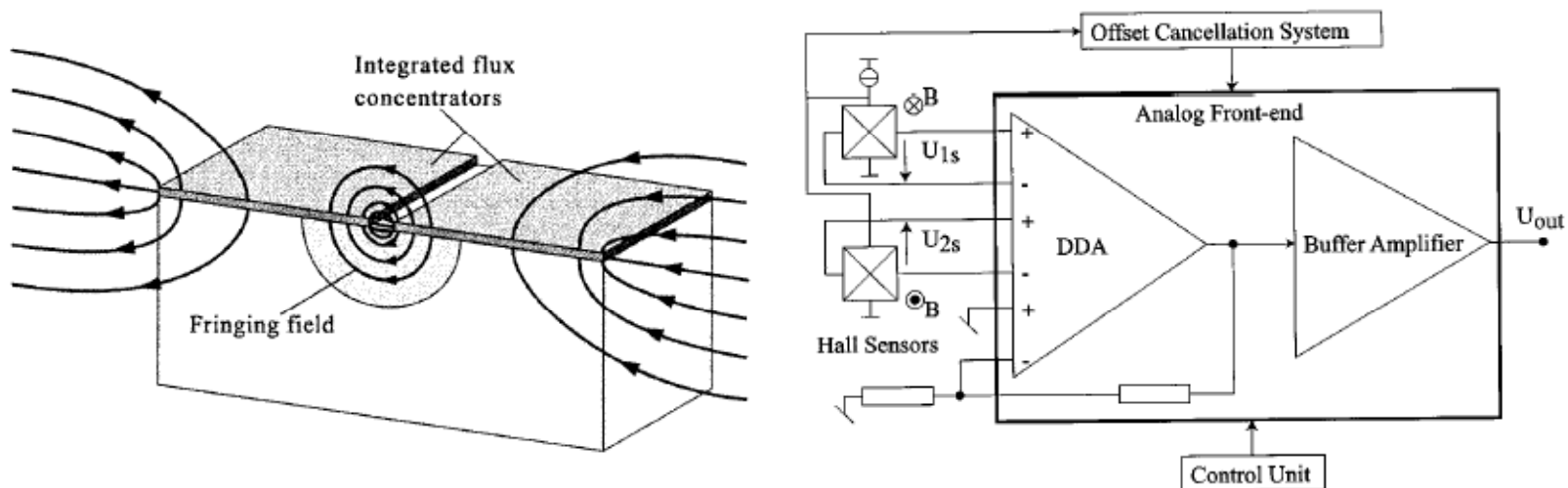
## Interface Circuitry

- The hall plates are placed just below the edges of the IMC near the gap






- Amplifier schematic

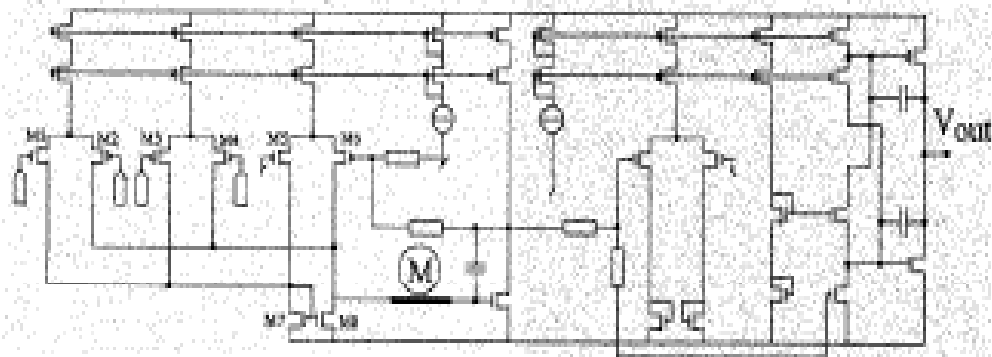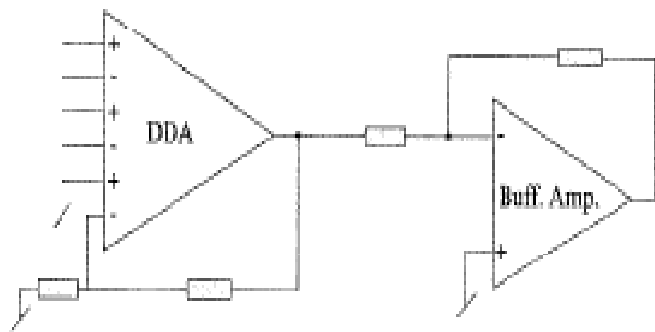



# DDA Offset Cancellation


- DDA offset cancellation scheme

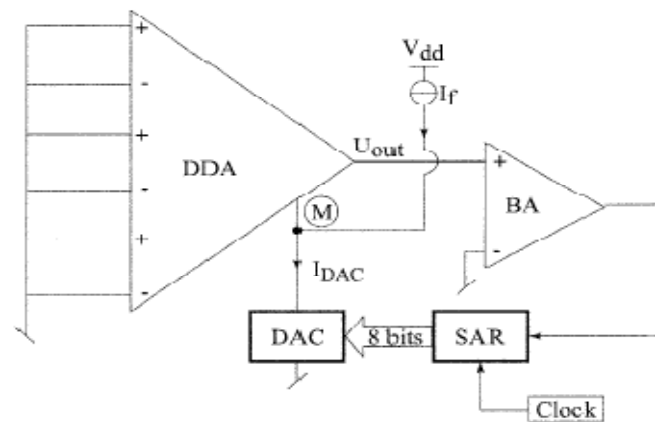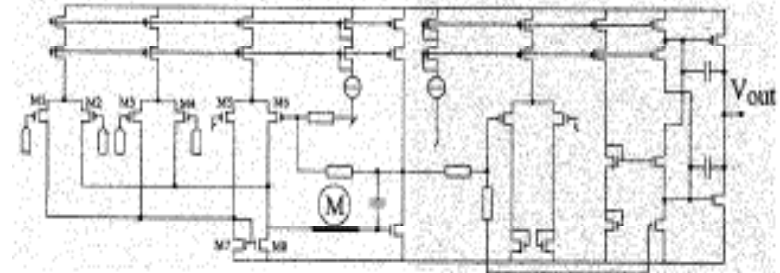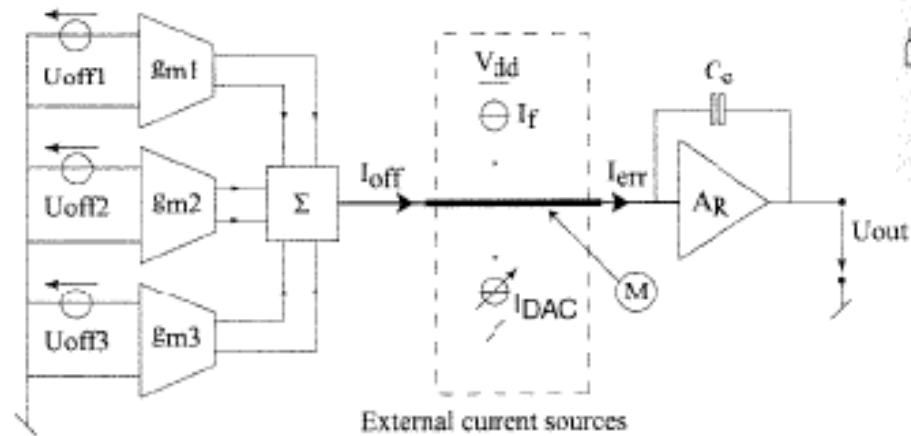


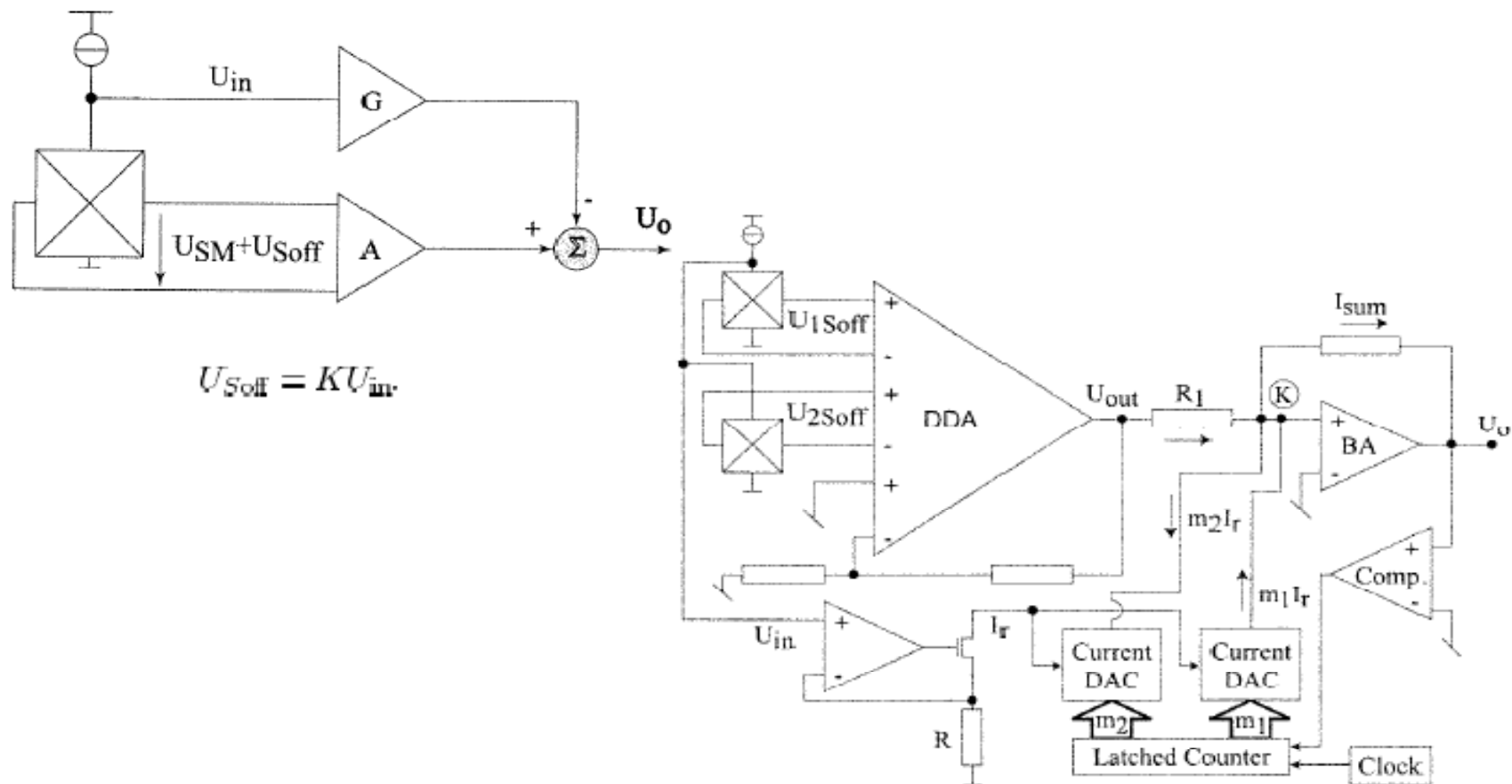
## Sensor Offset Cancellation



- Did not rely on dynamic spinning-current technique





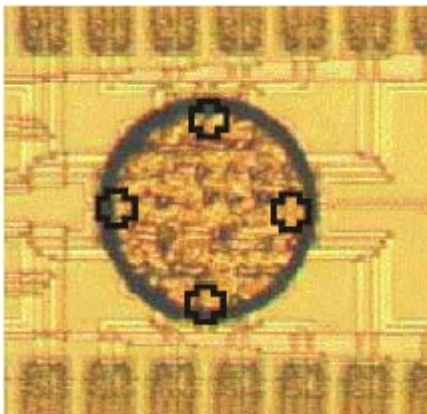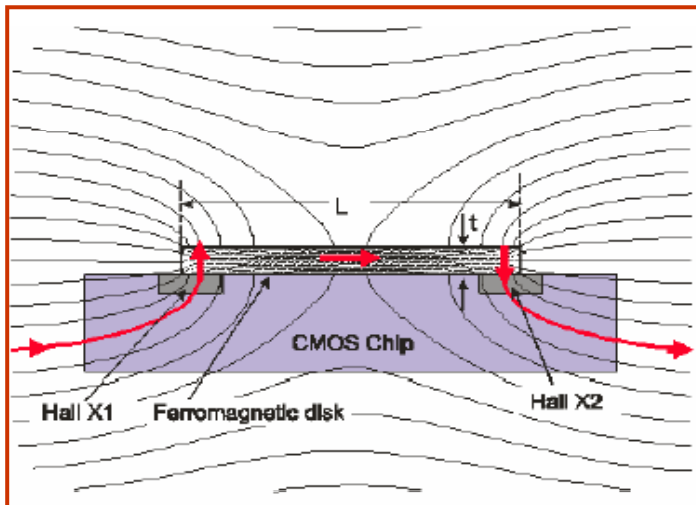
## Three-Axis Hall Sensor (1)

- Based on the **IMC** technology instead of assembling 3 Hall sensors



Disk shape

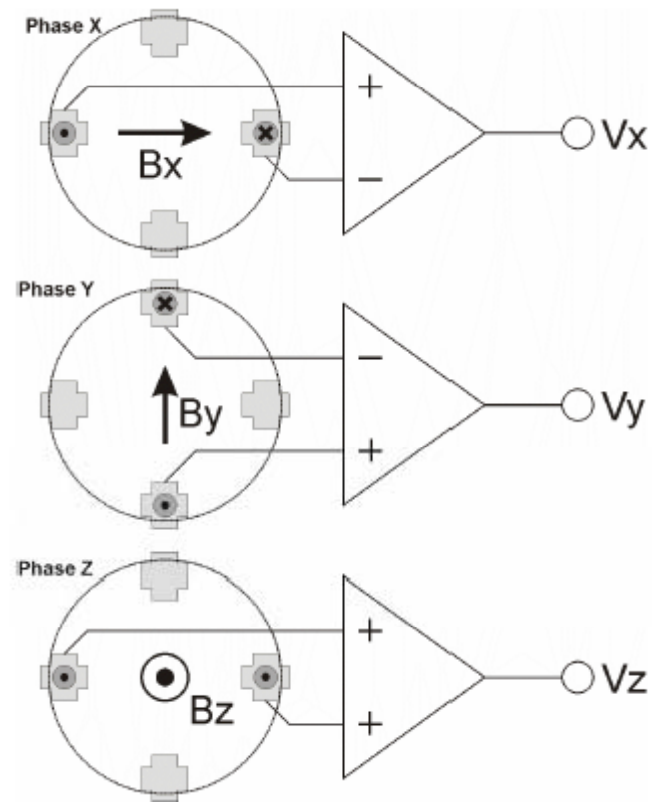

## Three-Axis Hall Sensor (2)

- Joystick application



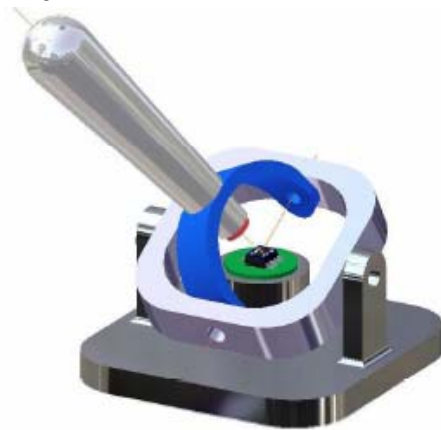


Figure 8: Gimbaled Mount Type Joystick

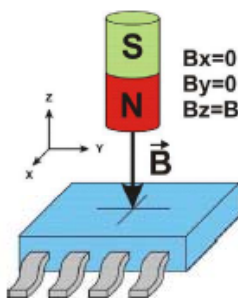

In center position all the field is perpendicular to the chip
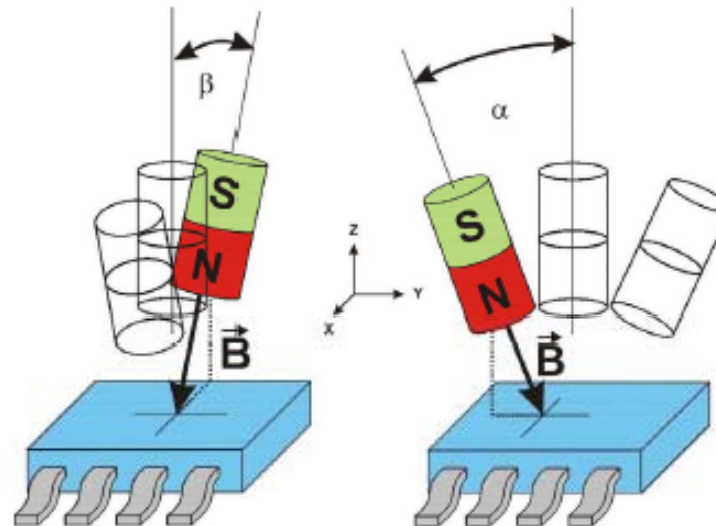
$$\begin{aligned} B_x &= 0 \\ B_y &= 0 \\ B_z &= B \end{aligned}$$



$$\begin{aligned} B_x &= B \cdot \sin \beta \\ B_y &= 0 \\ B_z &= -B \cdot \cos \beta \\ \rightarrow \beta &= \text{Atan}(B_x/B_z) \end{aligned}$$

$$\begin{aligned} B_x &= 0 \\ B_y &= B \cdot \sin \alpha \\ B_z &= -B \cdot \cos \alpha \\ \rightarrow \alpha &= \text{Atan}(B_y/B_z) \end{aligned}$$

Figure 10: The horizontal field components depend on the total field strength  $B$ , whereas the ratios  $B_x/B_z$  and  $B_y/B_z$  are independent of  $B$ .

- C. Schott, et al., "CMOS Three Axis Hall Sensor and Joystick Application", *IEEE Sensors*, pp. 977-980, Oct. 2004.



## Three-Axis Hall Sensor (3)

- Ratio measurement

Why 3-axis?

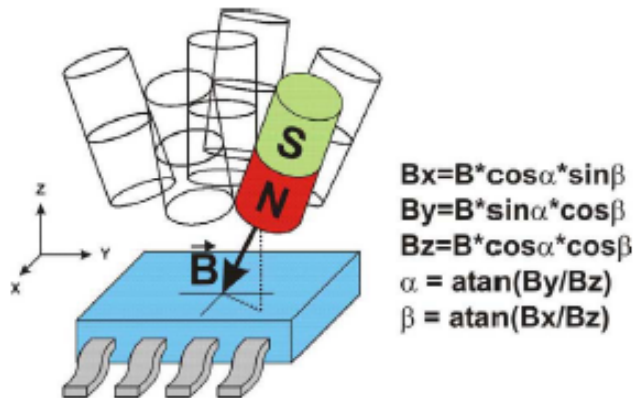


Figure 11: All three magnetic field components depend on both inclination angles  $\alpha$  and  $\beta$ .

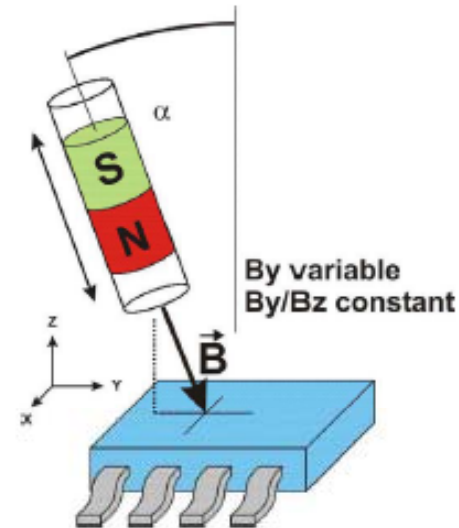


Figure 12: By changing the distance magnet to sensor the total field strength and the one of the components changes, whereas the ratios  $B_x/B_z$  and  $B_y/B_z$  remain constant.

Why about the temperature dependency?



## Magnetic Sensor Interface Summary

- Offset cancellation (Hall cell and circuit)
  - Array of Hall sensors
  - Spinning current
    - Either the offset voltage or the Hall voltage can be chopped
  - Continuous-time auto-zeroing
  - Digital approach
  - High-pass filtering (AC couple)
- Temperature compensation
- Insensitive to supply
- Employing sigma-delta modulation for direct digital output
- Magnetic concentrator
- Three-axis Hall sensor