

Chapter 9 Signal-flow graphs and applications

9.1 Definitions and manipulation of signal-flow graphs

definition, reduction rules

9.2 Signal-flow graph representation of a voltage source

9.3 Signal-flow graph representation of a passive single-port device

9.4 Power gain equations

transducer power gain, operating power gain, available power gain

9.1 Definitions and manipulation of signal-flow graphs

Basics

1. Definitions:


signal-flow graph: representation of a linear system

node (input and output nodes) : representation of a variable

branch: representation of direction and relation between nodes


path: a continuous succession of branches traversed in the same direction

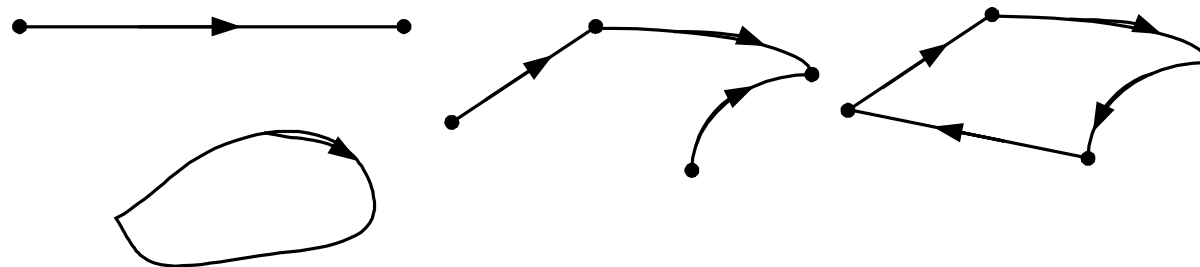loop: a path originates and ends at the same node without encountering other nodes more than once along its traverse




Discussion

1. Scattering parameters

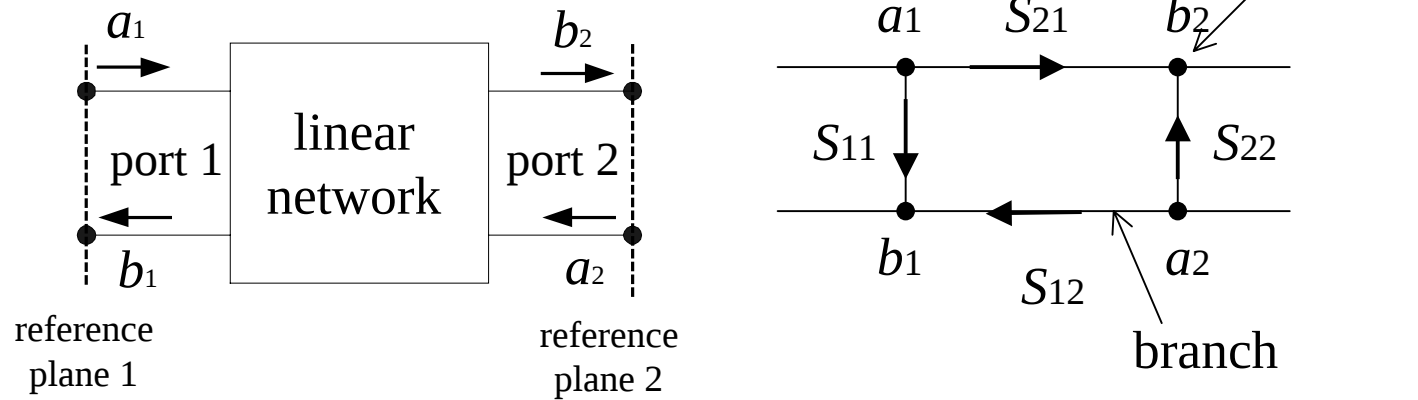


$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \quad \begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 \end{aligned}$$

2. Reduction rules

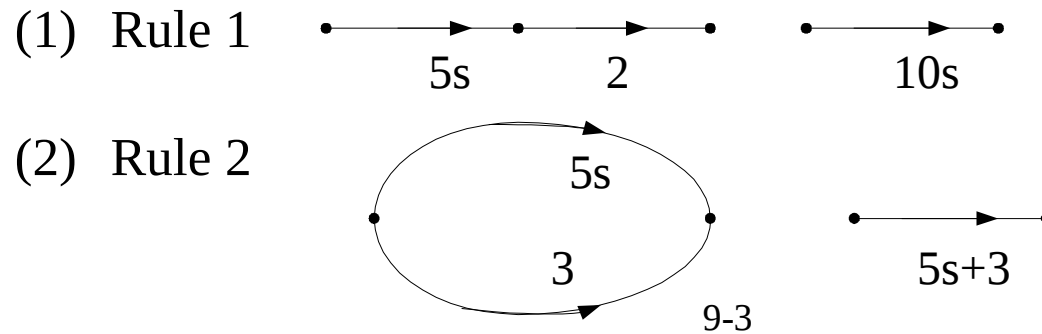


(3) Rule 3

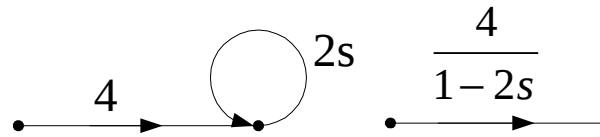


$$b = 4a + 2sb \rightarrow b - 2sb = 4a \rightarrow b = \frac{4a}{1-2s}$$

(4) Rule 4

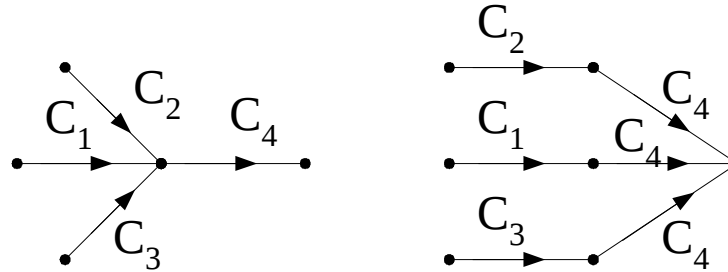

(5) Rule 5

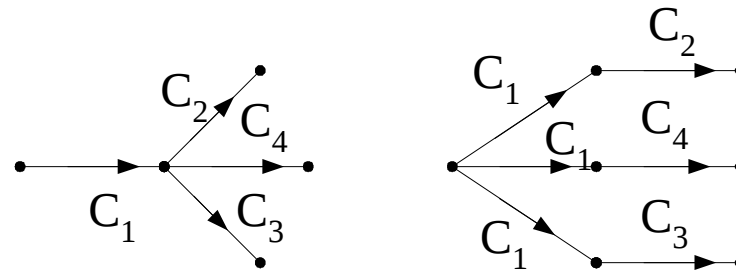

3. Mason's gain rule:

$$\text{transfer function } T(s) = \frac{P_1\Delta_1 + P_2\Delta_2 + P_3\Delta_3 + \dots}{\Delta}$$

P_i : gain of the i th forward path

$$\Delta = 1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots$$

$$\Delta_1 = 1 - \sum L(1)^{(1)} + \sum L(2)^{(1)} - \sum L(3)^{(1)} + \dots$$

$$\Delta_2 = 1 - \sum L(1)^{(2)} + \sum L(2)^{(2)} - \sum L(3)^{(2)} + \dots$$

$\sum L(1)$: sum of all first - order loop gains

$\sum L(2)$: sum of all second - order loop gains

$\sum L(1)^{(1)}$: sum of all first - order loop gains that do not touch path P_1 at any node


$\sum L(2)^{(1)}$: sum of all second - order loop gains that do not touch path P_1 at any node

$\sum L(1)^{(2)}$: sum of all first - order loop gains that do not touch path P_2 at any node

2nd order loop gain : product of 2 first order loops that don't touch at any point

3rd order loop gain : product of 3 first order loops that don't touch at any point

4. Ex. 9.5 find the transfer function

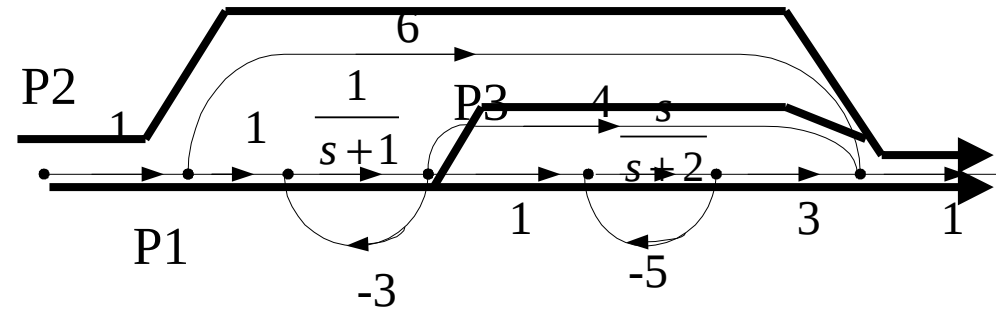


$$\text{3 forward paths} \left\{ \begin{array}{l} P_1 = 1 \times 1 \times \frac{1}{s+1} \times 1 \times \frac{s}{s+2} \times 3 \times 1 = \frac{3s}{(s+1)(s+2)} \\ P_2 = 1 \times 6 \times 1 = 6 \\ P_3 = 1 \times 1 \times \frac{1}{s+1} \times (-4) \times 1 = \frac{-4}{s+1} \end{array} \right.$$

$$\text{2 loops} \left\{ \begin{array}{l} L_1 = \frac{-3}{s+1} \\ L_2 = \frac{-5s}{s+2} \end{array} \right.$$

$$H(s) = \frac{P_1 + P_2(1 - L_1 - L_2 + L_1L_2) + P_3(1 - L_2)}{1 - L_1 - L_2 + L_1L_2}$$

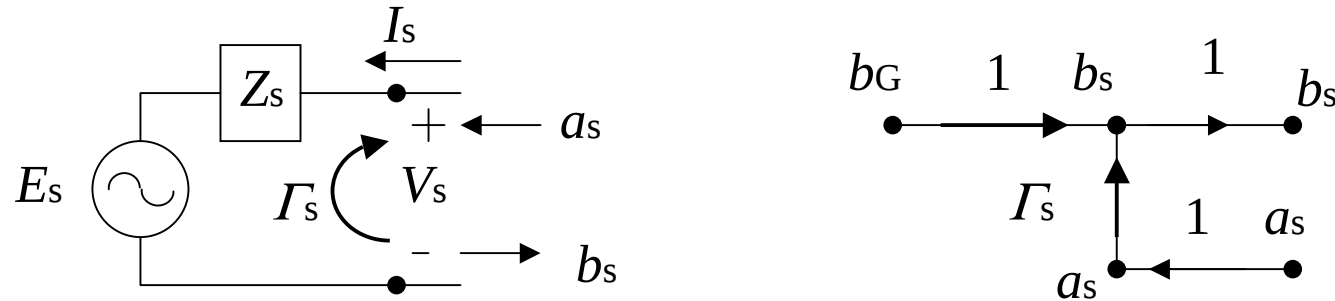9.2 Signal-flow graph representation of a voltage source



$$E_s = -I_s Z_s + V_s = -(I_{s,in} + I_{s,ref}) Z_s + (V_{s,in} + V_{s,ref})$$


$$= -\frac{V_{s,in} - V_{s,ref}}{Z_o} Z_s + V_{s,in} + V_{s,ref} = (1 - \frac{Z_s}{Z_o}) V_{s,in} + (1 + \frac{Z_s}{Z_o}) V_{s,ref}$$

$$\rightarrow V_{s,ref} = \frac{Z_o}{Z_o + Z_s} E_s - \frac{Z_o - Z_s}{Z_o + Z_s} V_{s,in}$$

$$\rightarrow \frac{V_{s,ref}}{\sqrt{2Z_o}} = \frac{Z_o}{Z_o + Z_s} \frac{E_s}{\sqrt{2Z_o}} + \frac{Z_s - Z_o}{Z_o + Z_s} \frac{V_{s,in}}{\sqrt{2Z_o}}$$

$$\rightarrow b_s = b_G + \Gamma_s a_s$$

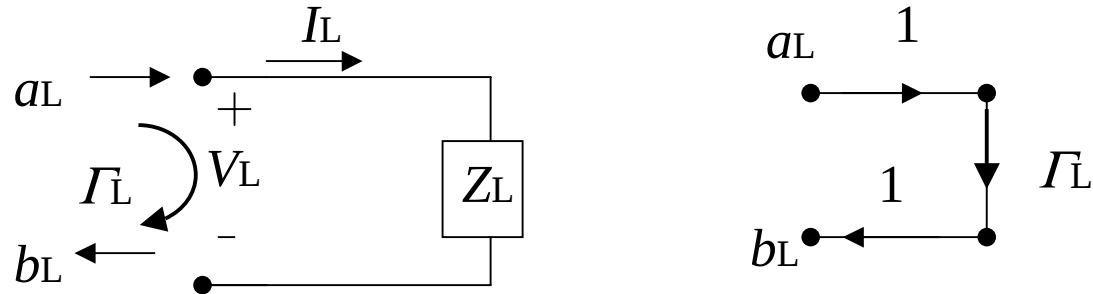9.3 Signal-flow graph representation of a passive single-port device



$$V_L = I_L Z_L = (I_{L,in} + I_{L,ref}) Z_L = \frac{V_{L,in} - V_{L,ref}}{Z_o} Z_L$$

$$= V_{L,in} + V_{L,ref}$$


$$\rightarrow V_{L,ref} = \frac{Z_L - Z_o}{Z_L + Z_o} V_{L,in}$$

$$\rightarrow \frac{V_{L,ref}}{\sqrt{2Z_o}} = \frac{Z_L - Z_o}{Z_L + Z_o} \frac{V_{L,in}}{\sqrt{2Z_o}}$$

$$\rightarrow b_L = \Gamma_L a_L$$

Discussion

1. Ex.9.6 find Γ_{in}

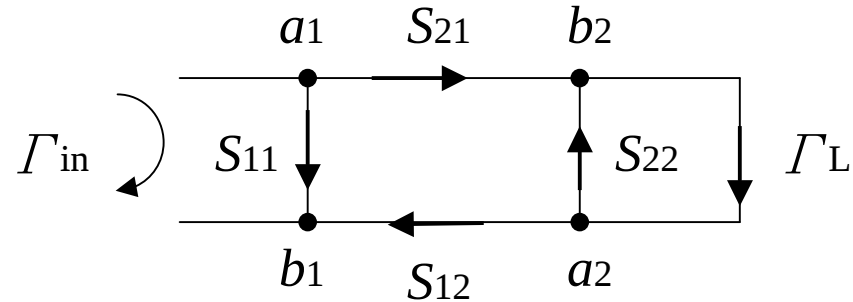

$$\begin{aligned} (1) \Gamma_{in} &= S_{11} + S_{21}\Gamma_L S_{12} + S_{21}\Gamma_L S_{12} S_{22}\Gamma_L + S_{21}\Gamma_L S_{12} S_{22}\Gamma_L S_{22}\Gamma_L + \dots \\ &= S_{11} + S_{21}\Gamma_L S_{12} (1 + S_{22}\Gamma_L + \dots) = S_{11} + \frac{S_{21}\Gamma_L S_{12}}{1 - S_{22}\Gamma_L} \end{aligned}$$



(2) Mason's rule

$$2 \text{ forward paths} \begin{cases} P_1 = S_{11} \\ P_2 = S_{21}\Gamma_L S_{12} \end{cases}$$

$$1 \text{ loop } L_1 = S_{22}\Gamma_L$$

$$\Gamma_{in} = \frac{P_1(1 - L_1) + P_2}{1 - L_1} = \frac{S_{11}(1 - S_{22}\Gamma_L) + S_{21}\Gamma_L S_{12}}{1 - S_{22}\Gamma_L} = S_{11} + \frac{S_{21}\Gamma_L S_{12}}{1 - S_{22}\Gamma_L}$$

2. Ex.9.7 find Γ_{out}

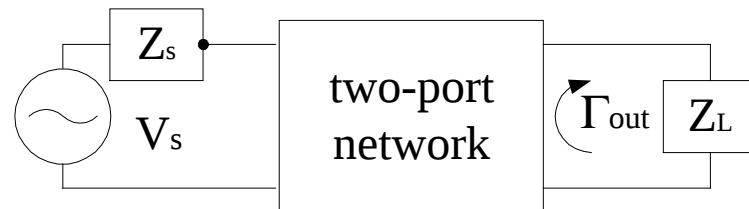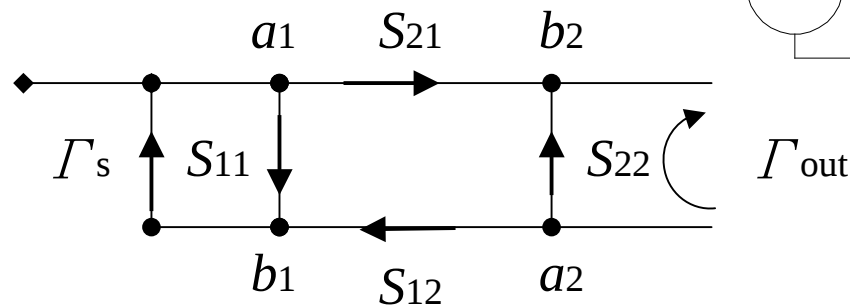

$$(1) \Gamma_{out} = S_{22} + S_{21}\Gamma_s S_{12} + S_{21}\Gamma_s S_{12} S_{11}\Gamma_s + S_{21}\Gamma_s S_{12} S_{11}\Gamma_s S_{11}\Gamma_s + \dots$$

$$= S_{22} + S_{21}\Gamma_s S_{12} (1 + S_{11}\Gamma_s + \dots) = S_{22} + \frac{S_{21}\Gamma_s S_{12}}{1 - S_{11}\Gamma_s}$$

(2) Mason's rule

$$2 \text{ forward paths} \begin{cases} P_1 = S_{22} \\ P_2 = S_{21}\Gamma_s S_{12} \end{cases}$$

$$1 \text{ loop } L_1 = S_{11}\Gamma_s$$

$$\Gamma_{out} = \frac{P_1(1 - L_1) + P_2}{1 - L_1} = \frac{S_{22}(1 - S_{11}\Gamma_s) + S_{21}\Gamma_s S_{12}}{1 - S_{11}\Gamma_s} = S_{22} + \frac{S_{21}\Gamma_s S_{12}}{1 - S_{11}\Gamma_s}$$

3. Ex.9.8 find P_d :power delivered from source, P_L :power delivered to the load, P_{avs} :maximum power available from source

$$b_s = b_G + a_s \Gamma_s = b_G + b_L \Gamma_s = b_G + a_L \Gamma_L \Gamma_s = b_G + b_s \Gamma_L \Gamma_s$$


$$\rightarrow \begin{cases} b_s = \frac{b_G}{1 - \Gamma_L \Gamma_s} \\ a_s = \frac{b_s - b_G}{\Gamma_s} = \frac{1}{\Gamma_s} \left(\frac{b_G}{1 - \Gamma_L \Gamma_s} - b_G \right) = \frac{b_G \Gamma_L}{1 - \Gamma_L \Gamma_s} \end{cases}$$

$$P_d = |b_s|^2 - |a_s|^2 = \left| \frac{b_G}{1 - \Gamma_L \Gamma_s} \right|^2 - \left| \frac{b_G \Gamma_L}{1 - \Gamma_L \Gamma_s} \right|^2 = \left| \frac{b_G}{1 - \Gamma_L \Gamma_s} \right|^2 (1 - |\Gamma_L|^2) = |b_s|^2 (1 - |\Gamma_L|^2) = P_L$$



$$P_L = |a_L|^2 - |b_L|^2 = |a_L|^2 (1 - |\Gamma_L|^2) = |b_s|^2 (1 - |\Gamma_L|^2)$$

conjugate match condition : $\Gamma_s = \Gamma_L^*$

$$P_{avs} = P_d \big|_{\Gamma_s = \Gamma_L^*} = \left| \frac{b_G}{1 - |\Gamma_s|^2} \right|^2 (1 - |\Gamma_s|^2) = \frac{|b_G|^2}{1 - |\Gamma_s|^2}$$

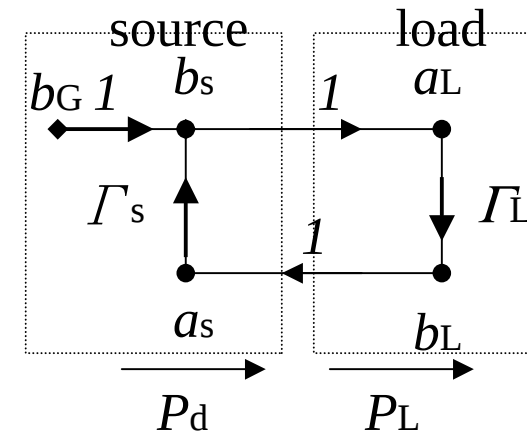

4. Ex.9.9 find b_3/b_s

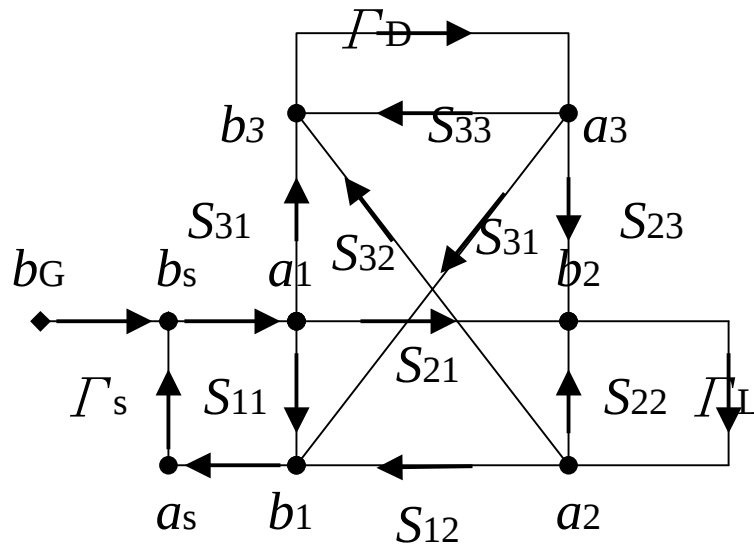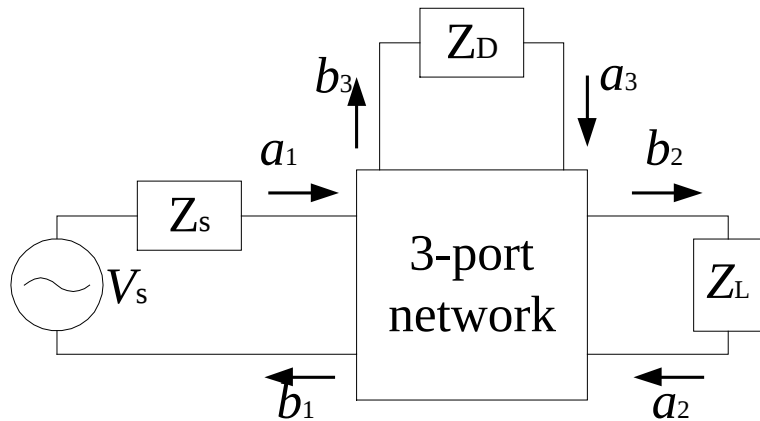

2 forward paths $\begin{cases} P_1 = S_{31} \\ P_2 = S_{21}\Gamma_L S_{32} \end{cases}$

8 loop $\begin{cases} L_1 = S_{11}\Gamma_s \\ L_2 = S_{22}\Gamma_L \\ L_3 = S_{22}\Gamma_D \\ L_4 = S_{21}S_{12}\Gamma_s\Gamma_L \\ L_5 = S_{31}S_{23}S_{12}\Gamma_s\Gamma_L\Gamma_D \\ L_6 = S_{13}S_{21}S_{32}\Gamma_s\Gamma_L\Gamma_D \\ L_7 = S_{23}S_{32}\Gamma_L\Gamma_D \\ L_8 = S_{31}S_{13}\Gamma_s\Gamma_D \end{cases}$

$$\frac{b_3}{b_s} = \frac{P_1\Delta_1 + P_2\Delta_2}{1 - \sum L(1) + \sum L(2) - \sum L(3)}$$

$$\Delta_1 = 1 - S_{22}\Gamma_L, \Delta_2 = 1$$


$$\sum L(1) = L_1 + \dots + L_8$$

$$\sum L(2) = L_1L_2 + L_1L_3 + L_2L_3 + L_3L_4 + L_1L_7 + L_2L_8$$

$$\sum L(3) = L_1L_2L_3$$

9.4 Power gain equations

Basics

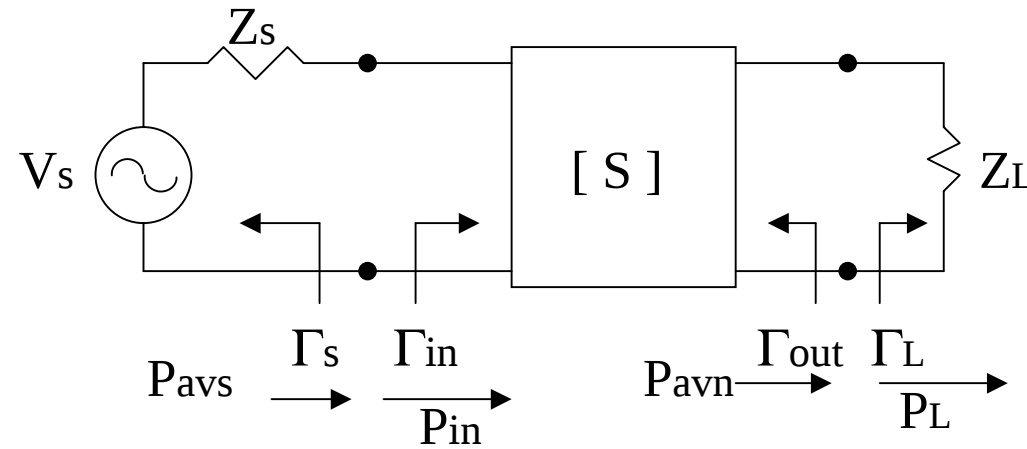

$$\text{operating power gain } G_p \equiv \frac{P_L}{P_{in}}(S, \Gamma_L)$$

$$\text{available power gain } G_A \equiv \frac{P_{avn}}{P_{avs}}(S, \Gamma_S)$$

$$\text{transducer power gain } G_T \equiv \frac{P_L}{P_{avs}}(S, \Gamma_S, \Gamma_L)$$

$$P_{avs} = P_{in} \big|_{\Gamma_{in} = \Gamma_S^*}, P_{avn} = P_L \big|_{\Gamma_L = \Gamma_{out}^*}$$

Discussion

$$1. \quad \because b_s = b_G + \Gamma_s \Gamma_{in} b_s \rightarrow b_s = \frac{b_G}{1 - \Gamma_s \Gamma_{in}} = a_1$$

$$P_{in} = |a_1|^2 - |b_1|^2 = |a_1|^2 (1 - |\Gamma_{in}|^2) = \frac{(1 - |\Gamma_{in}|^2)}{|1 - \Gamma_s \Gamma_{in}|^2} |b_G|^2$$


$$\because a_L = b_2 = \frac{S_{21} a_1}{1 - S_{22} \Gamma_L} = \frac{S_{21} b_G}{(1 - S_{22} \Gamma_L)(1 - \Gamma_s \Gamma_{in})}$$

$$P_L = |a_L|^2 - |b_L|^2 = |a_L|^2 (1 - |\Gamma_L|^2) = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22} \Gamma_L|^2 |1 - \Gamma_s \Gamma_{in}|^2} |b_G|^2$$

$$P_{avn} = P_L \Big|_{\Gamma_L = \Gamma_{out}^*} = \frac{|S_{21}|^2 (1 - |\Gamma_{out}|^2)}{|1 - S_{22} \Gamma_{out}^*|^2 |1 - \Gamma_s \Gamma_{in}|^2} |b_G|^2, \because |1 - \Gamma_s \Gamma_{in}|^2 \Big|_{\Gamma_L = \Gamma_{out}^*} = \frac{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)^2}{|1 - S_{22} \Gamma_{out}^*|^2}$$

$$= \frac{|S_{21}|^2}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)} |b_G|^2$$

$$P_{avs} = P_{in} \Big|_{\Gamma_s = \Gamma_{in}^*} = \frac{1}{1 - |\Gamma_s|^2} |b_G|^2$$

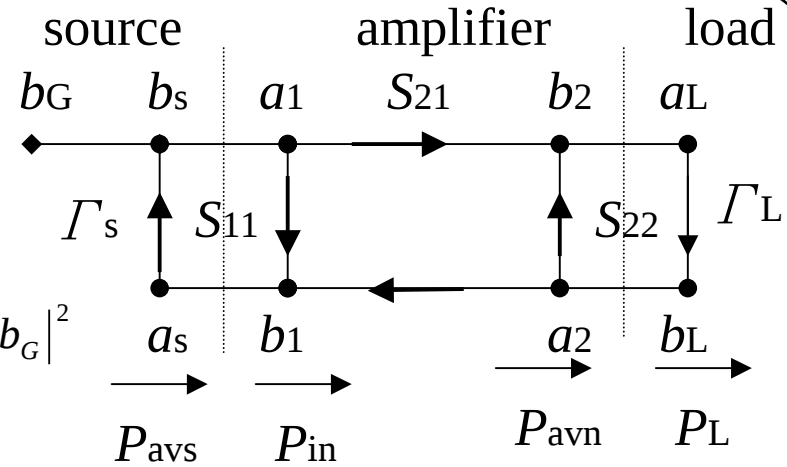

2.

$$P_{in} = \frac{(1-|\Gamma_{in}|^2)}{|1-\Gamma_s\Gamma_{in}|^2} |b_G|^2, P_L = \frac{|S_{21}|^2(1-|\Gamma_L|^2)}{|1-S_{22}\Gamma_L|^2|1-\Gamma_s\Gamma_{in}|^2} |b_G|^2$$


$$P_{avn} = P_L|_{\Gamma_L=\Gamma_{out}^*} = \frac{|S_{21}|^2}{|1-S_{11}\Gamma_s|^2(1-|\Gamma_{out}|^2)} |b_G|^2, P_{avs} = P_{in}|_{\Gamma_s=\Gamma_{in}^*} = \frac{1}{1-|\Gamma_s|^2} |b_G|^2$$

$$G_P = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2(1-|\Gamma_L|^2)}{|1-S_{22}\Gamma_L|^2(1-|\Gamma_{in}|^2)}$$

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2(1-|\Gamma_s|^2)}{|1-S_{11}\Gamma_s|^2(1-|\Gamma_{out}|^2)}$$

$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2(1-|\Gamma_L|^2)(1-|\Gamma_s|^2)}{|1-S_{22}\Gamma_L|^2|1-\Gamma_s\Gamma_{in}|^2} = \frac{|S_{21}|^2(1-|\Gamma_L|^2)(1-|\Gamma_s|^2)}{|1-S_{11}\Gamma_s|^2|1-\Gamma_L\Gamma_{out}|^2}$$

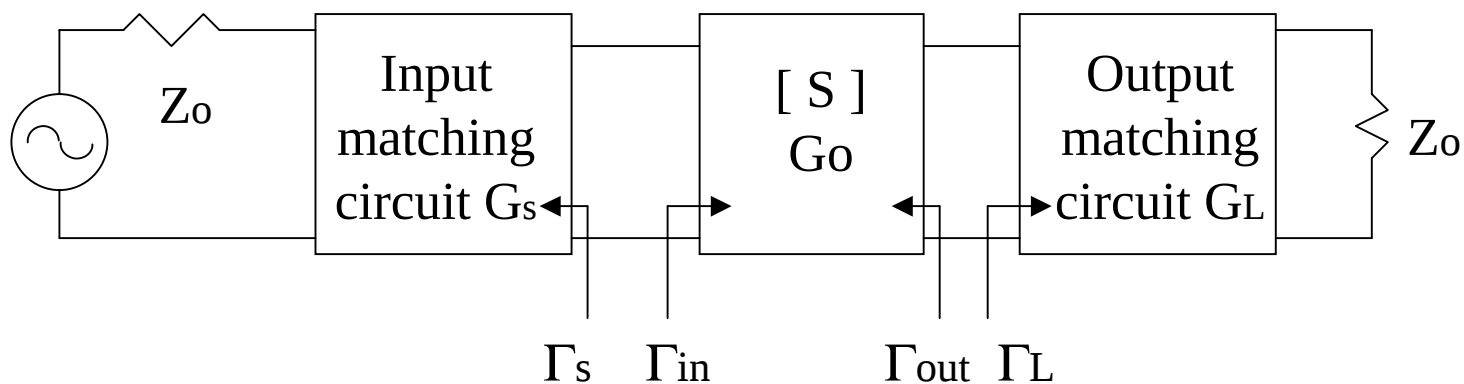5. Unilateral transducer power gain G_{TU}



$$S_{12} = 0 \rightarrow \Gamma_{in} = S_{11}$$

$$G_{TU} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = G_s G_o G_L$$

$$S_{11} = \Gamma_s^*, S_{22} = \Gamma_L^* \rightarrow G_{TU \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

6. A 800MHz amplifier ($Z_o=50\Omega$) with $S_{11}=0.45\angle 150^\circ$, $S_{12}=0.01\angle -10^\circ$, $S_{21}=2.0\angle 10^\circ$, $S_{22}=0.4\angle -150^\circ$, $Z_s=20\Omega$, $Z_L=30\Omega \rightarrow G_T, G_P, G_A$

$$\Gamma_s = \frac{Z_s - Z_o}{Z_s + Z_o} = -0.429, \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = -0.25$$

$$\Gamma_{in} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} = 0.455\angle 150.32^\circ, \Gamma_{out} = S_{22} + \frac{S_{21}S_{12}\Gamma_s}{1 - S_{11}\Gamma_s} = 0.408\angle 150.87^\circ$$

$$G_P \equiv \frac{P_L}{P_{in}} = \frac{|S_{21}|^2(1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2)|1 - S_{22}\Gamma_L|^2} = 5.937 = 7.7dB$$

$$G_A \equiv \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2(1 - |\Gamma_s|^2)}{(1 - |\Gamma_{out}|^2)|1 - S_{11}\Gamma_s|^2} = 5.855 = 7.7dB$$

$$G_T \equiv \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2(1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_s\Gamma_{in}|^2|1 - S_{22}\Gamma_L|^2} = 5.487 = 7.4dB$$

7. A 2GHz amplifier ($Z_0=50\Omega$) with $S_{11}=0.97 \angle -43^\circ$, $S_{12}=0$,
 $S_{21}=3.39 \angle 140^\circ$, $S_{22}=0.63 \angle -32^\circ$, $\Gamma_s=0.97 \angle 43^\circ$, $\Gamma_L=0.63 \angle 32^\circ$,
 $\rightarrow G_T, G_P, G_A$

$$S_{12} = 0 \rightarrow \Gamma_{in} = S_{11}, \Gamma_{out} = S_{22}$$

$$\Gamma_s = S_{11}^*, \Gamma_L = S_{22}^*$$

$$G_P \equiv \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22} \Gamma_L|^2}, G_A \equiv \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{(1 - |\Gamma_{out}|^2) |1 - S_{11} \Gamma_s|^2}$$

$$G_T \equiv \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2}$$

$$G_T = G_A = G_P = G_{TU \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} = 322.42 = 25dB$$

Hw #7 (due 2 weeks)

5, 10, 14